

ELECTRONICS

Course Contents

- Introduction
- Electronics
 - Basics, Concepts, Numbers & Analogies
 - Magnetism & Electromagnetism,
 - Resistors, Capacitors, Inductors,
 - AC Theory,
 - Semiconductors, Transistors & Diodes.

Introduction

Introduction.

- Basic Units.
- Resistors, Resistor Network Calculations.
- Capacitors.
- Inductors.
- Diodes and Transistors.
- Operational Amplifiers.
- AC Theory.


Basics

The Basics.

- This section will cover :-
- The basics and structure of atoms.
- Conductors and Insulators.
- Electrical charge

The Basics.

The Atom

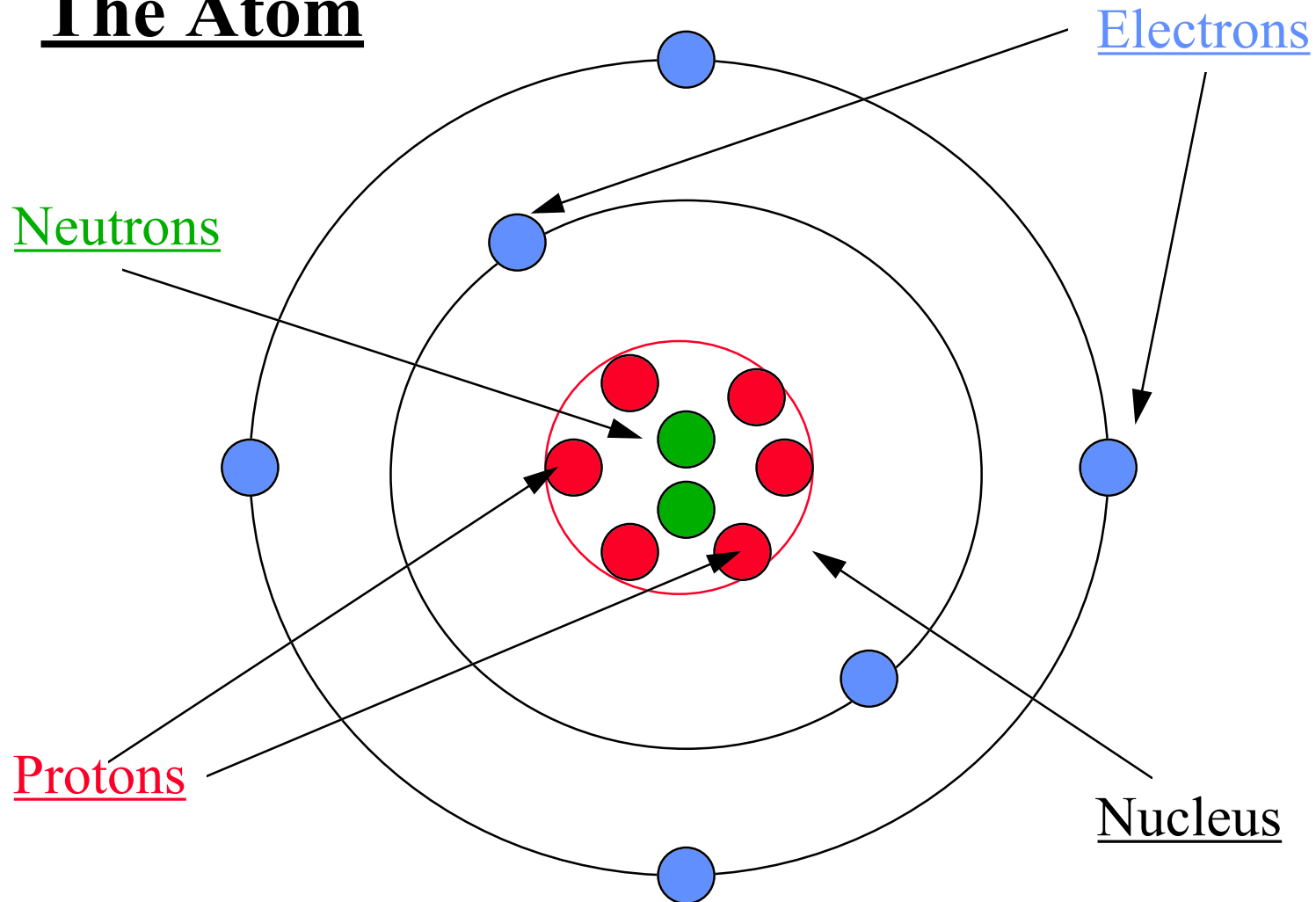


The Basics.


- Electrons have a **negative** charge.
- Protons have a **positive** charge.
- Neutrons are **uncharged**.
- The overall charges in an atom in their normal state **Cancel**.
- The **atomic number** is the count of protons in the nucleus.
- The **atomic weight** is based on the count of protons and neutrons in the nucleus.

The Basics.

The Atom

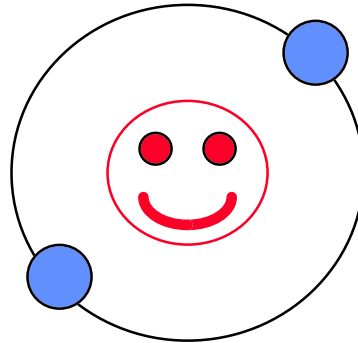


Overall Charge
Neutral

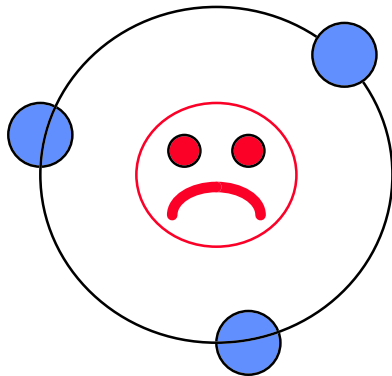

Overall Charge
Negative

Note:

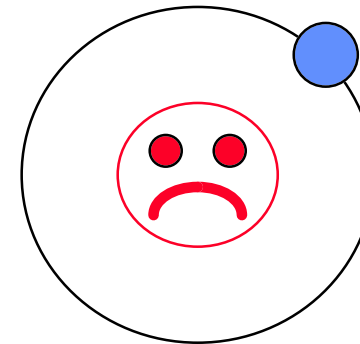
All these atoms
are assumed to
have two protons.



Overall Charge
Positive

The Basics.

The Atom

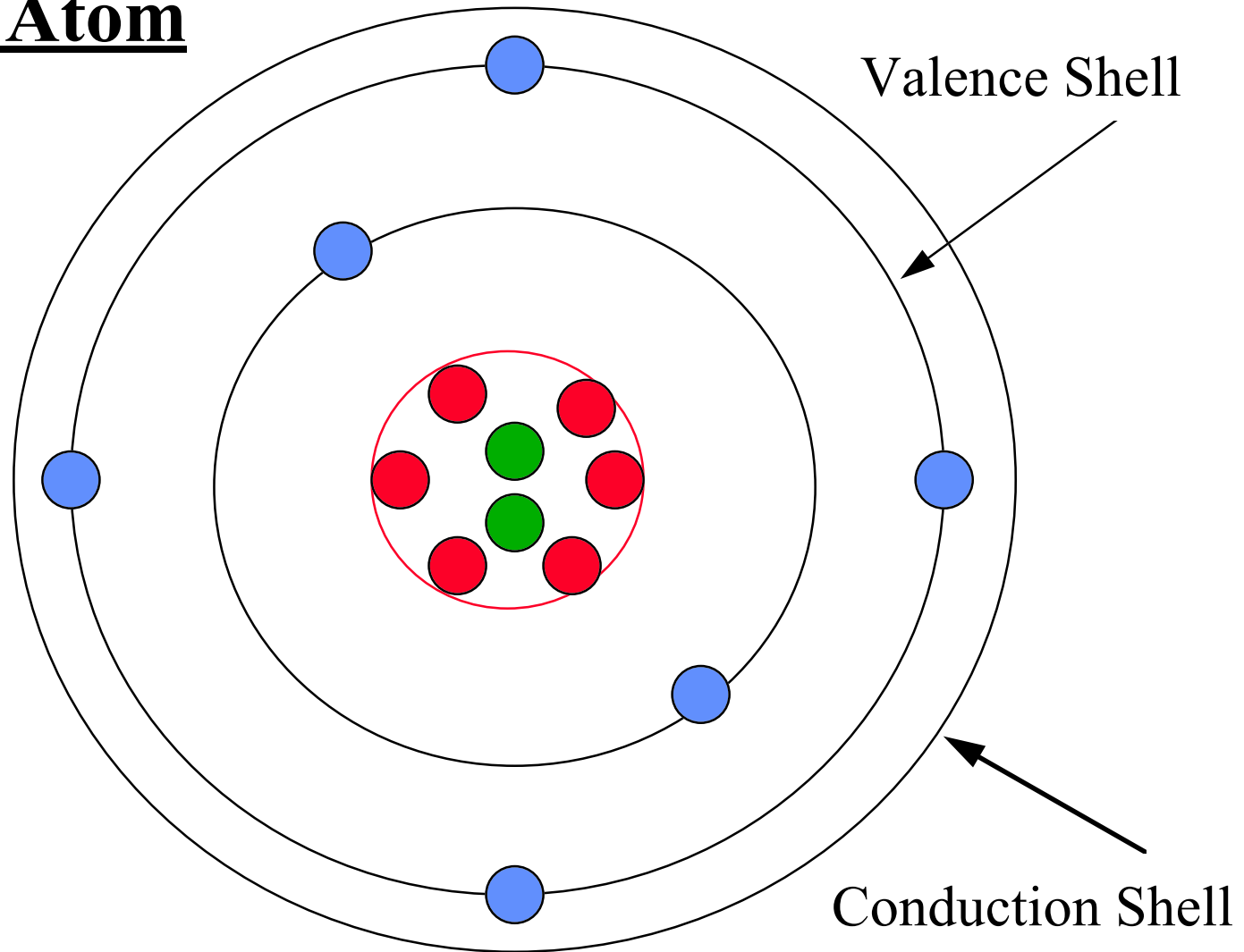


The Basics.

- The number of electrons per shell is based on the formula $2N^2$.
- Hence shell 1 can have $2*1^2 = 2$ electrons.
- Hence shell 2 can have $2*2^2 = 8$ electrons.
- Hence shell 3 can have $2*3^2 = 18$ electrons.
- The outer shell is the **valence** shell. It is this shell that defines the behavior and the way the atom will react with other atoms and can have a maximum of 8 electrons.

The Basics.

The Atom

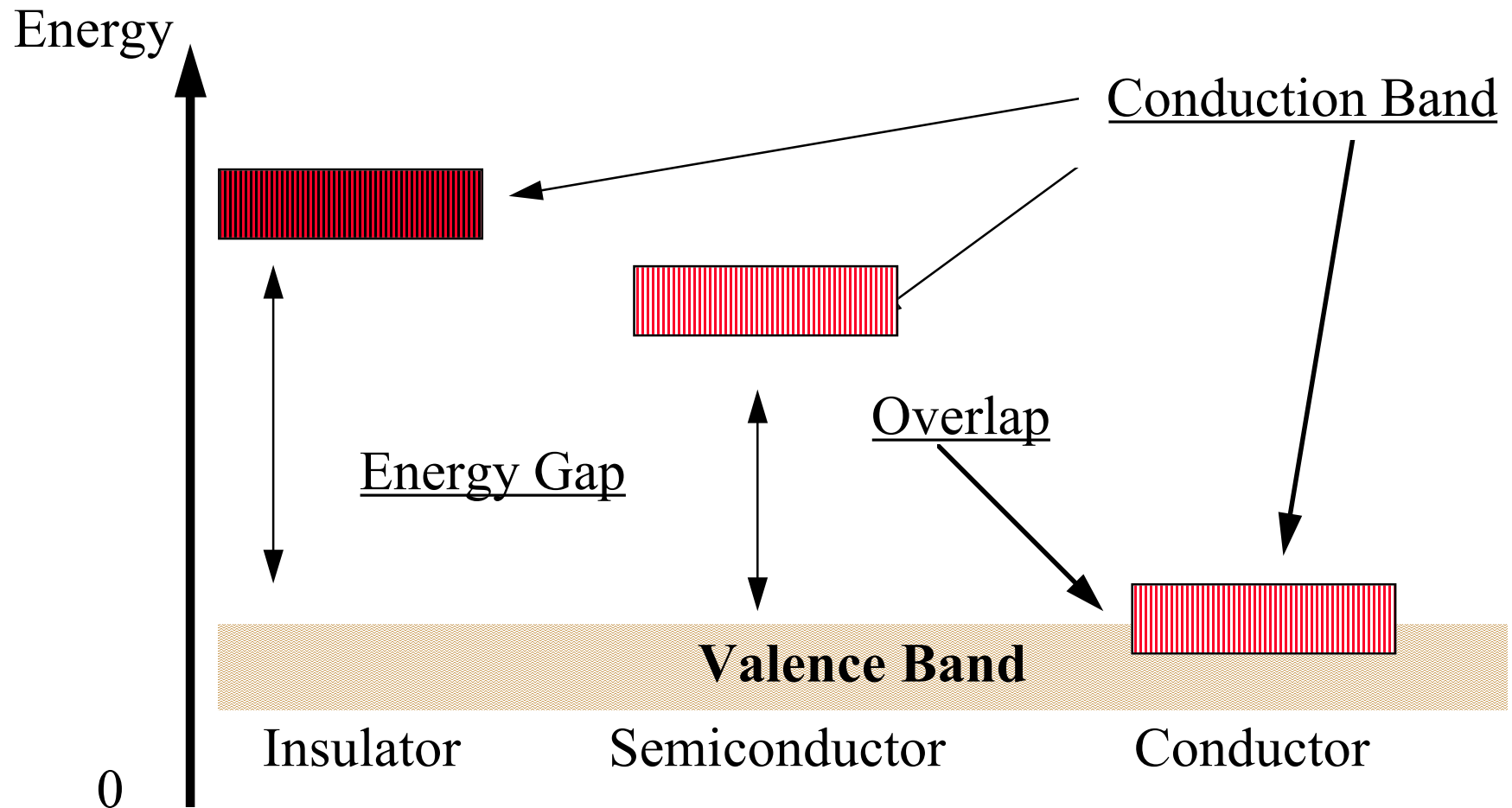

The Basics.

- An atom with few electrons in the outer shell can have them dislodged easily and will conduct electricity.
- An atom with many electrons in the outer shell are difficult to dislodge and is an insulator.
- An atom with four electrons in the outer shell are called semiconductors (more about this special case later).

The Basics.


- The charge of an electron and that of a proton are equal in magnitude.
- Electrical charge is given the symbol Q .
- Materials with opposite charge attract.
- Materials with same charge repel.
- The force that acts between charges is called the *electric field* .

The Basics.

- Summary:-
- The overall charge on the atom depends on the sum of **Protons** and **Electrons** and should be neutral.
- The weight of the atom is the sum of **Protons** and **Neutrons** in the nucleus..
- Electrons need sufficient energy to move into the conduction band before they can start to migrate through the material.

The Basics.

The Atom

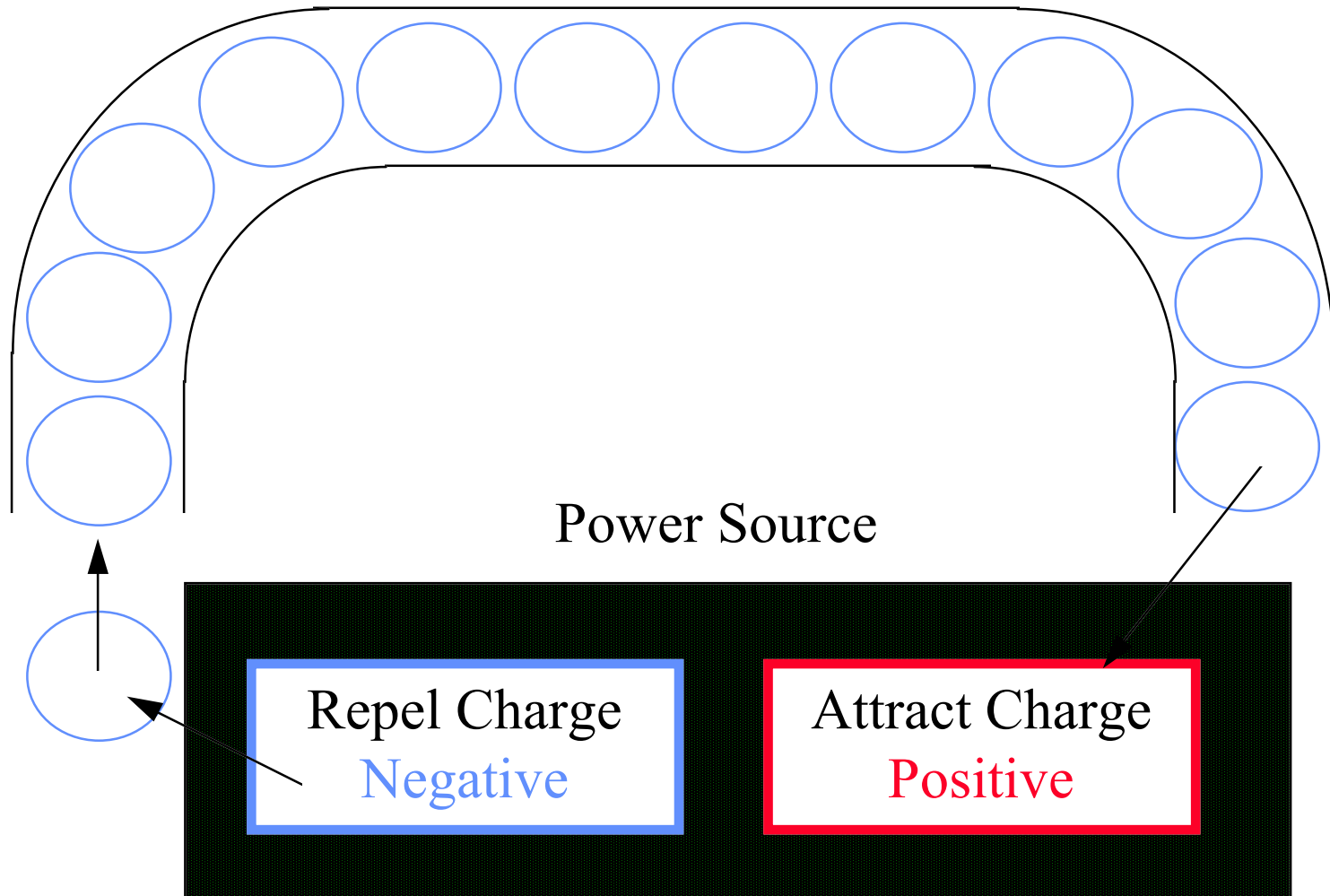

Sources and Effects

The Basics.

Sources of e.m.f. (electromotive force) :-

- Friction giving Static electric charge.
- Chemical reactions (Battery)
- Magnetic (Conductor moving through a magnetic field [generator]).
- Energy converters
 - Heat to electricity (thermocouple).
 - Light to electricity (photocell).

The Basics.

Main effects of electric current are :-

- Magnetic effect.
- Heating effect.
- Chemical effect
- Energy converter
 - Current to Light (LED).
- **Any others you can think of ?**

Definitions

The Basics.

- Electrical charge is measured in **coulombs** and is abbreviated **C**.
- A single electron has a charge of $1.6 \times 10^{-19} \text{ C}$
- One **coulomb** is the total charge on :-
 6.25×10^{18} electrons.
- Note

$$\frac{1}{1.6 \times 10^{-19}} = 6.25 \times 10^{18}$$

The Basics.

- Definitions of a unit of Energy or Work :-
- Measurement unit is the Joule.
- Defined as *the work done when a force of 1 newton is exerted through a distance of 1 metre in the direction of the force.*
- or defined as One Watt for One Second.
- The newton is defines as *the force which when applied to a mass of 1kg, gives it an acceleration of 1 m/s²*

The Basics.

- Force = **Mass** * **Acceleration**
 - Force {Units = Newtons }
 - **Mass** { Units = Kilograms }
 - **Acceleration** { Units = metres per second per second }
- Force {N} = **M** {Kg} * **A** {m/s²}
- Speed (v) = Distance (s) / Time (t)
- Acceleration (f) is the change in Speed in a time period.

$$(v_{\text{final}} - v_{\text{initial}}) / (t_{\text{final}} - t_{\text{initial}})$$

The Basics.

Summary


$$\text{Charge } Q = \frac{\text{Number of electrons}}{6.25 \cdot 10^{18} \text{ electrons per Coulomb}}$$

$$\text{Voltage } V = \frac{\text{Energy } W \text{ (expressed in joules)}}{\text{Charge } Q \text{ (expressed in coulombs)}}$$

$$\text{Current } I = \frac{\text{Charge } Q \text{ (expressed in coulombs)}}{\text{Time } t \text{ (expressed in seconds)}}$$

Analogy Concepts


The Basics.

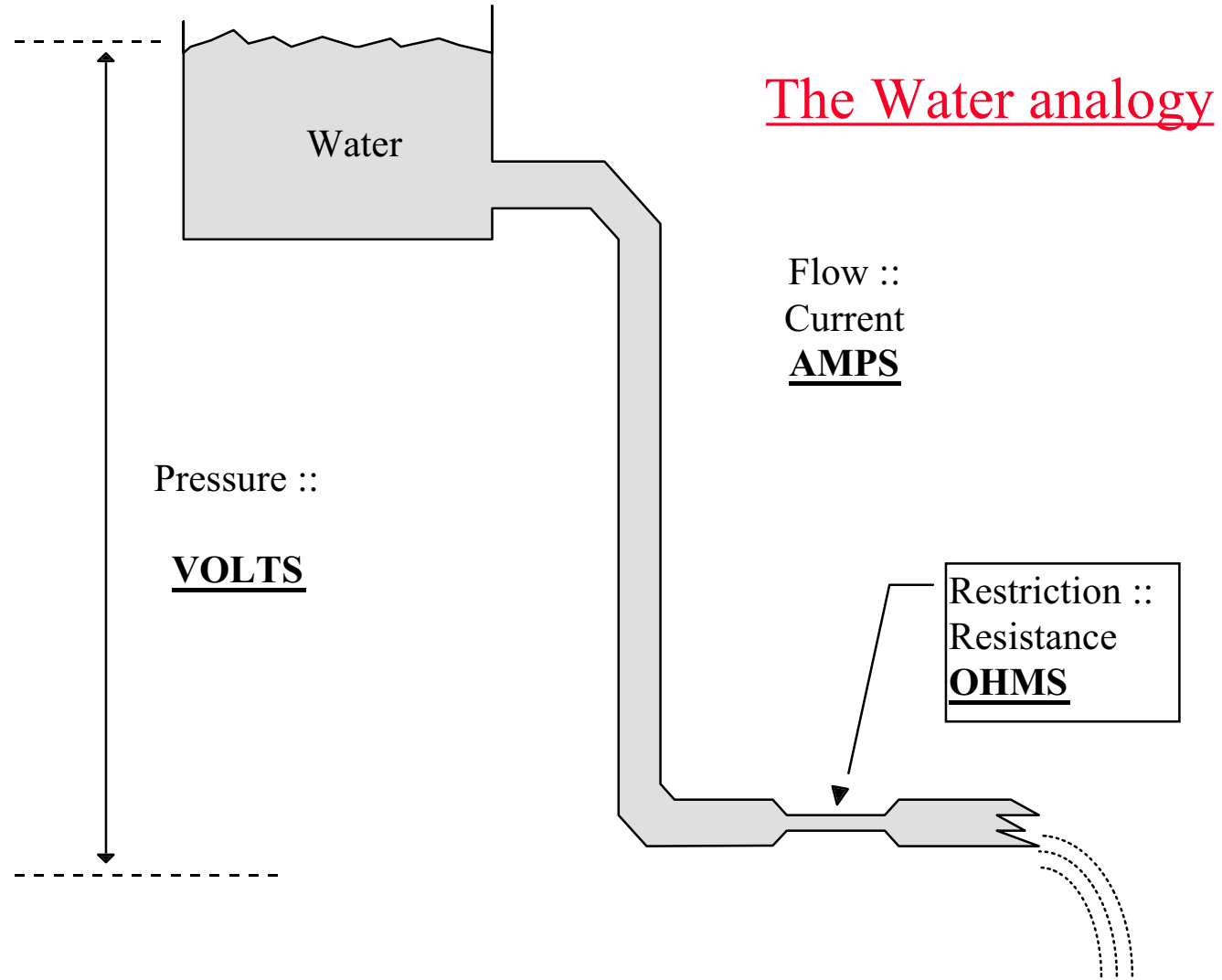

The Basics.

The Water analogy


The Fall of potential

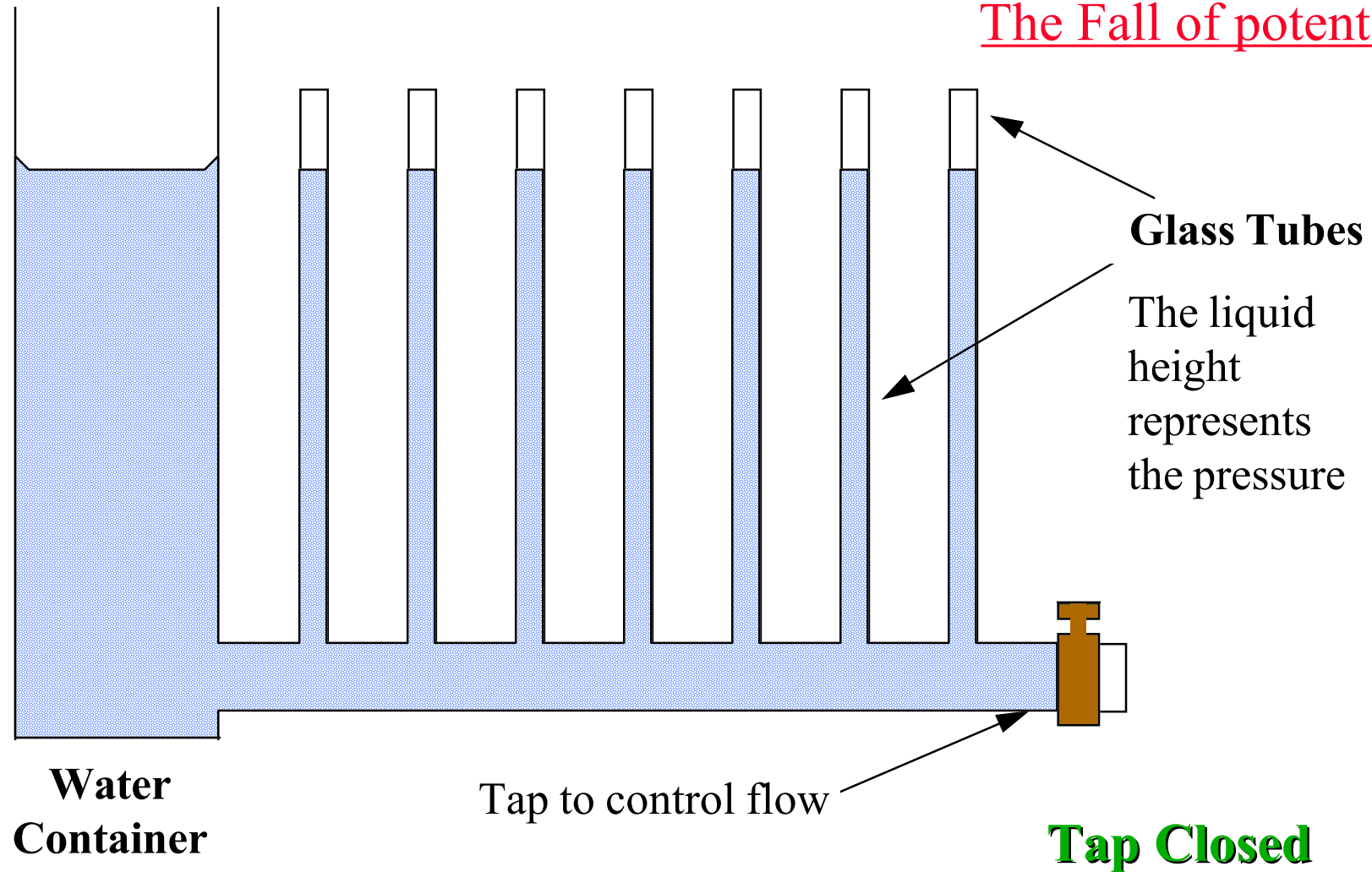

The Basics.

The Water analogy


The Fall of potential

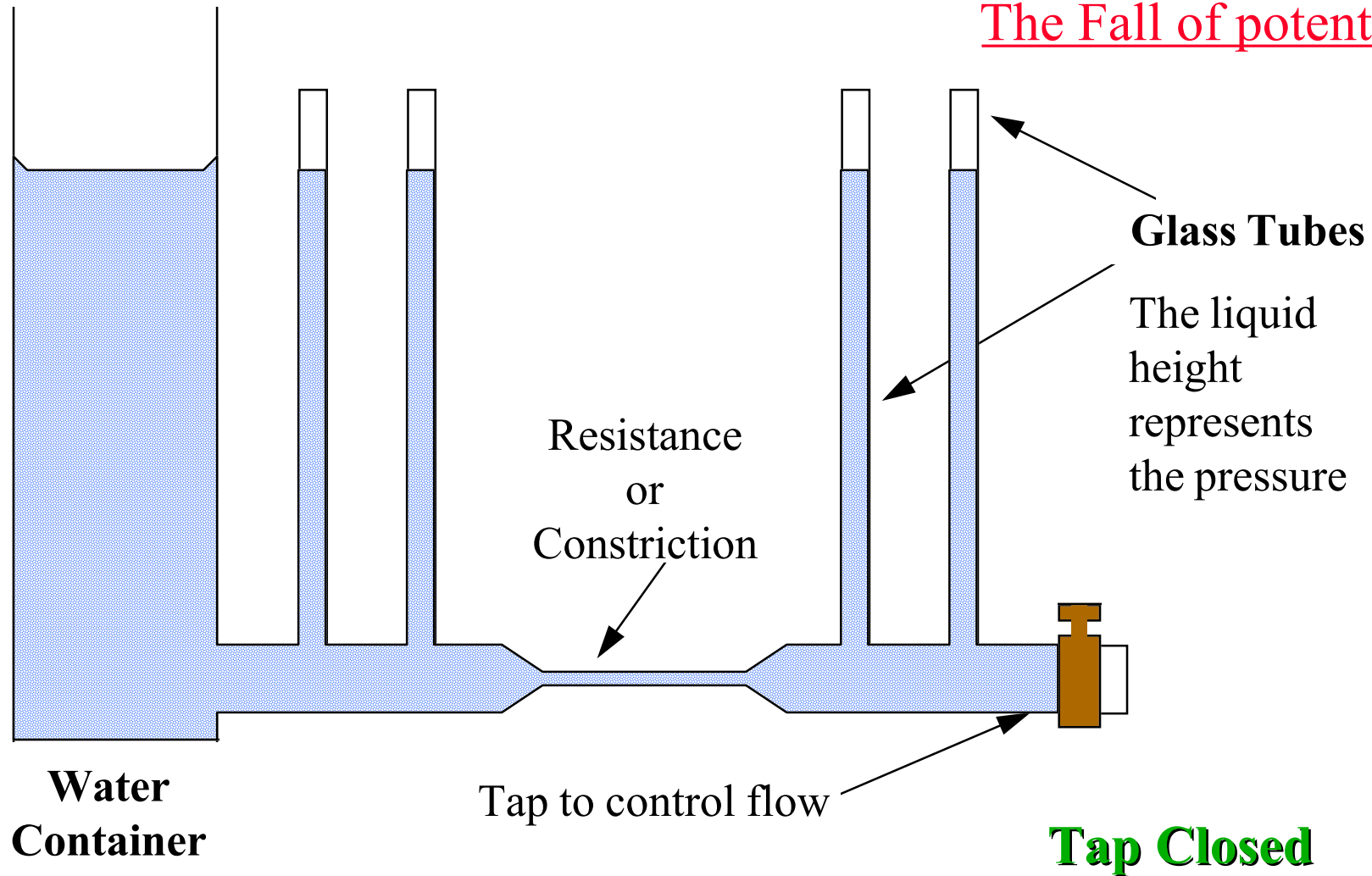

The Basics.

The Water analogy

The Fall of potential

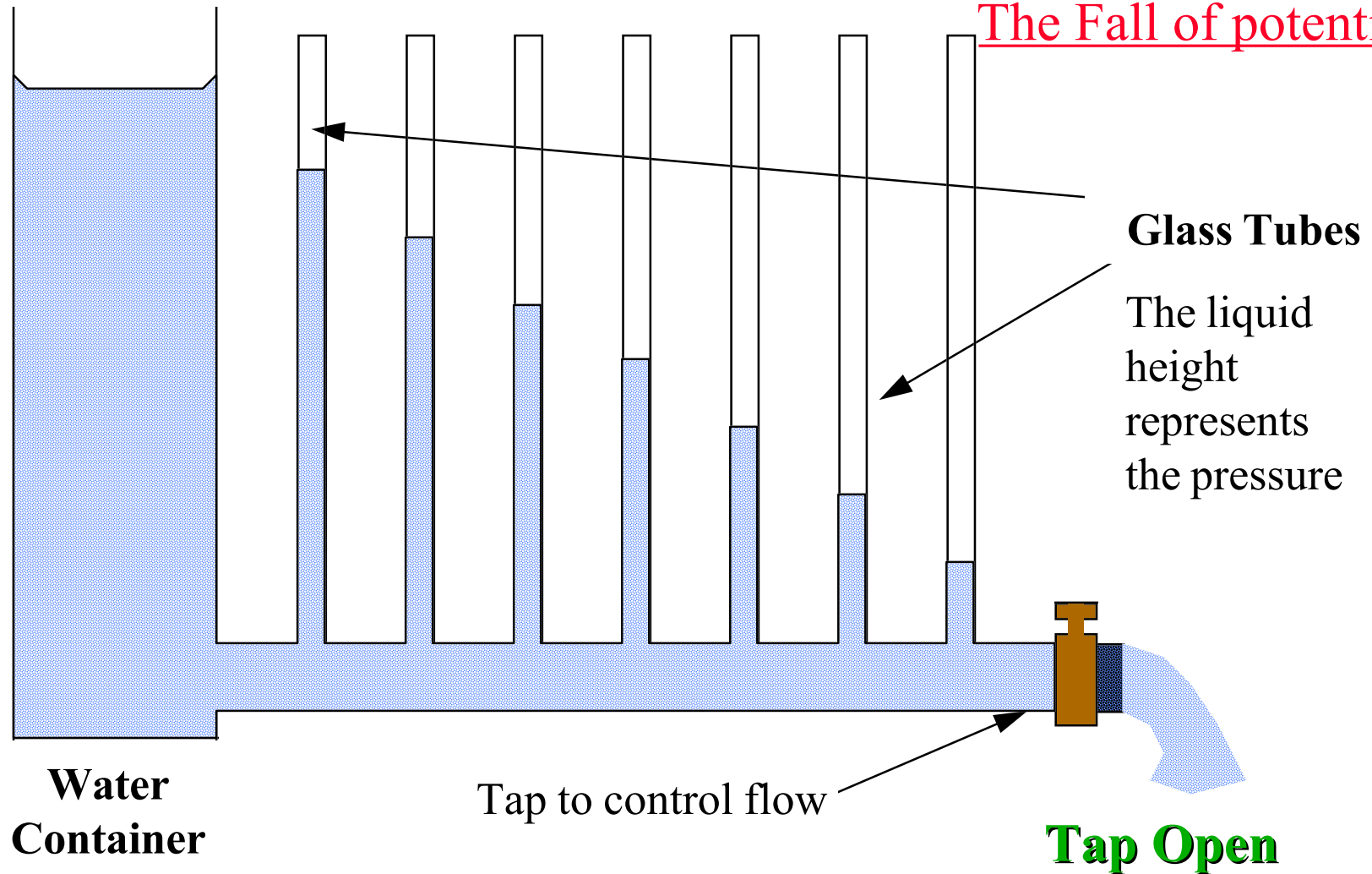


The Basics.

Slope of potential drops.

The Water analogy


The Fall of potential

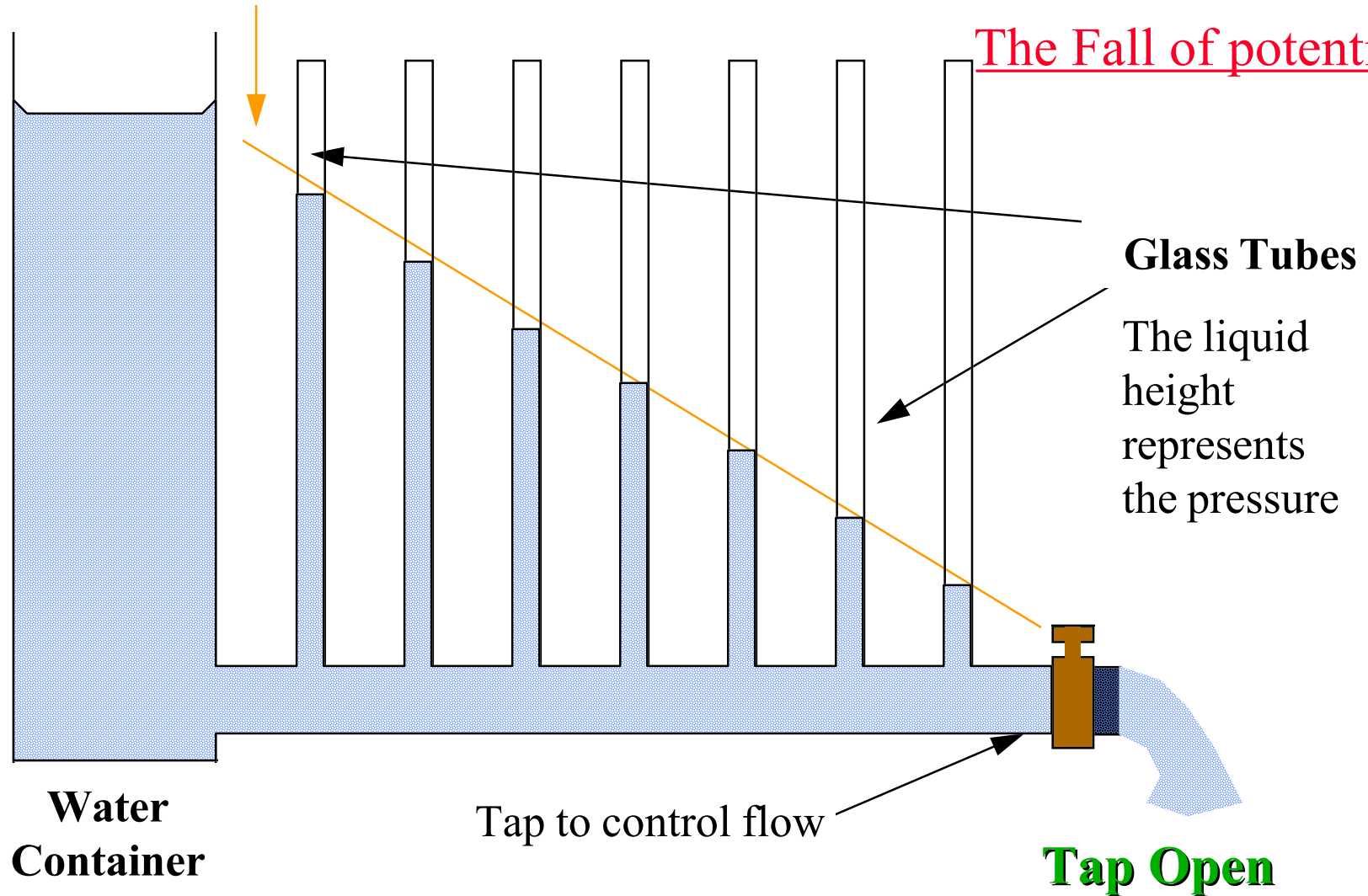

The Basics.

Water
Container

The Water analogy
potential difference.

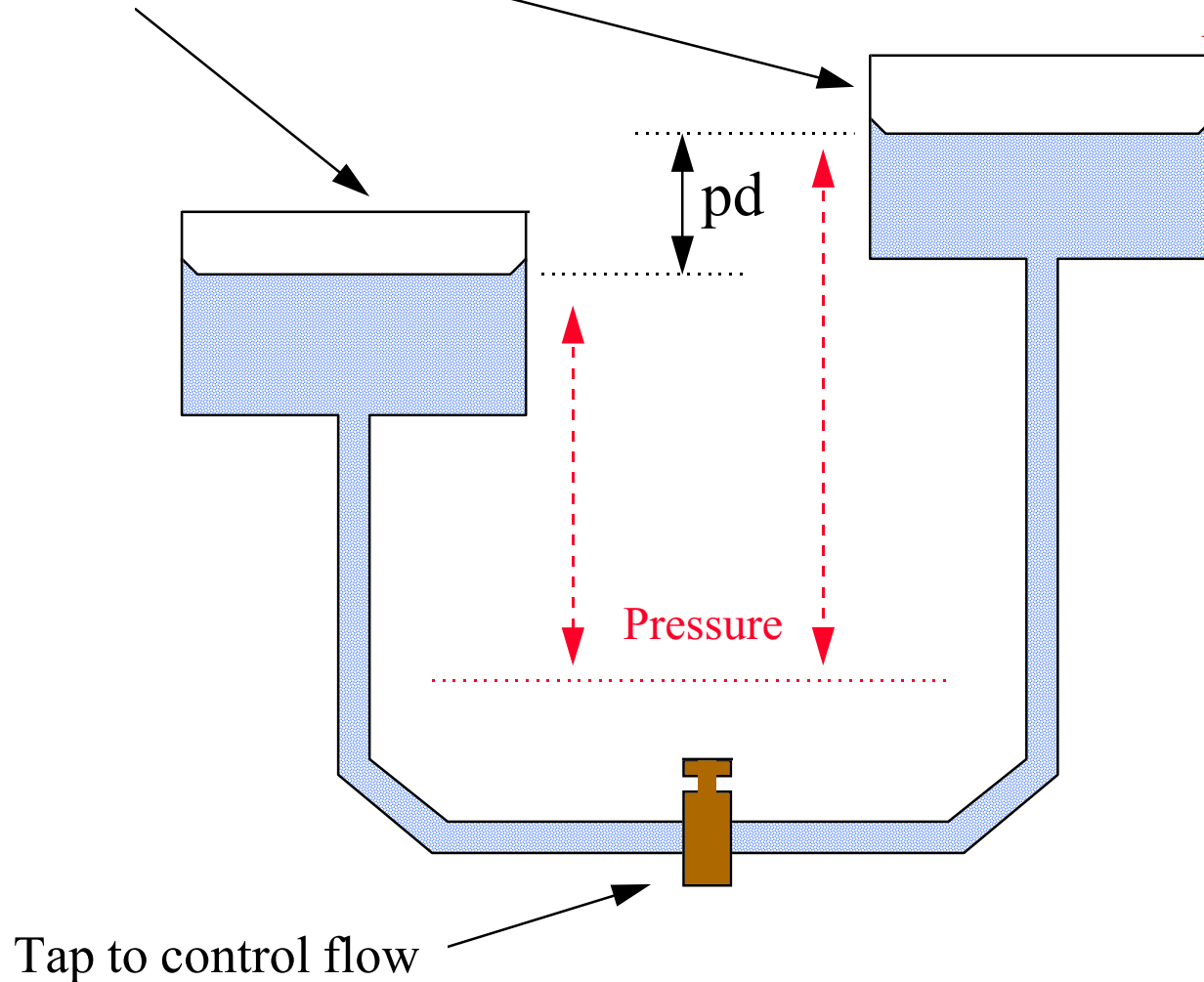


Question

When the
Tap is
opened
which
direction
will the
liquid flow.

The Basics.

The Water analogy
potential difference.

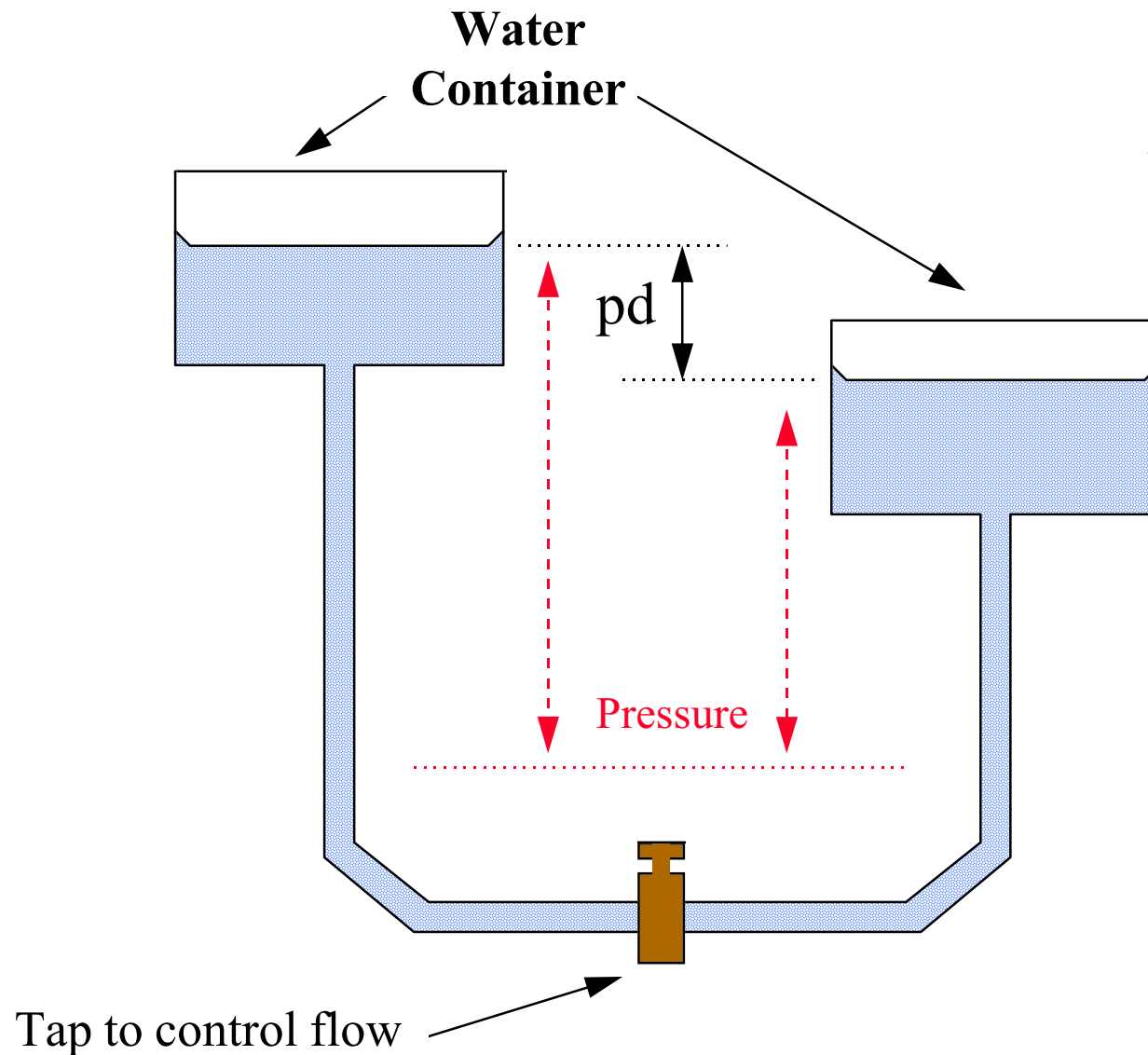


Question

When the Tap is opened which direction will the liquid flow.

The Basics.

Water
Container

The Water analogy
potential difference.

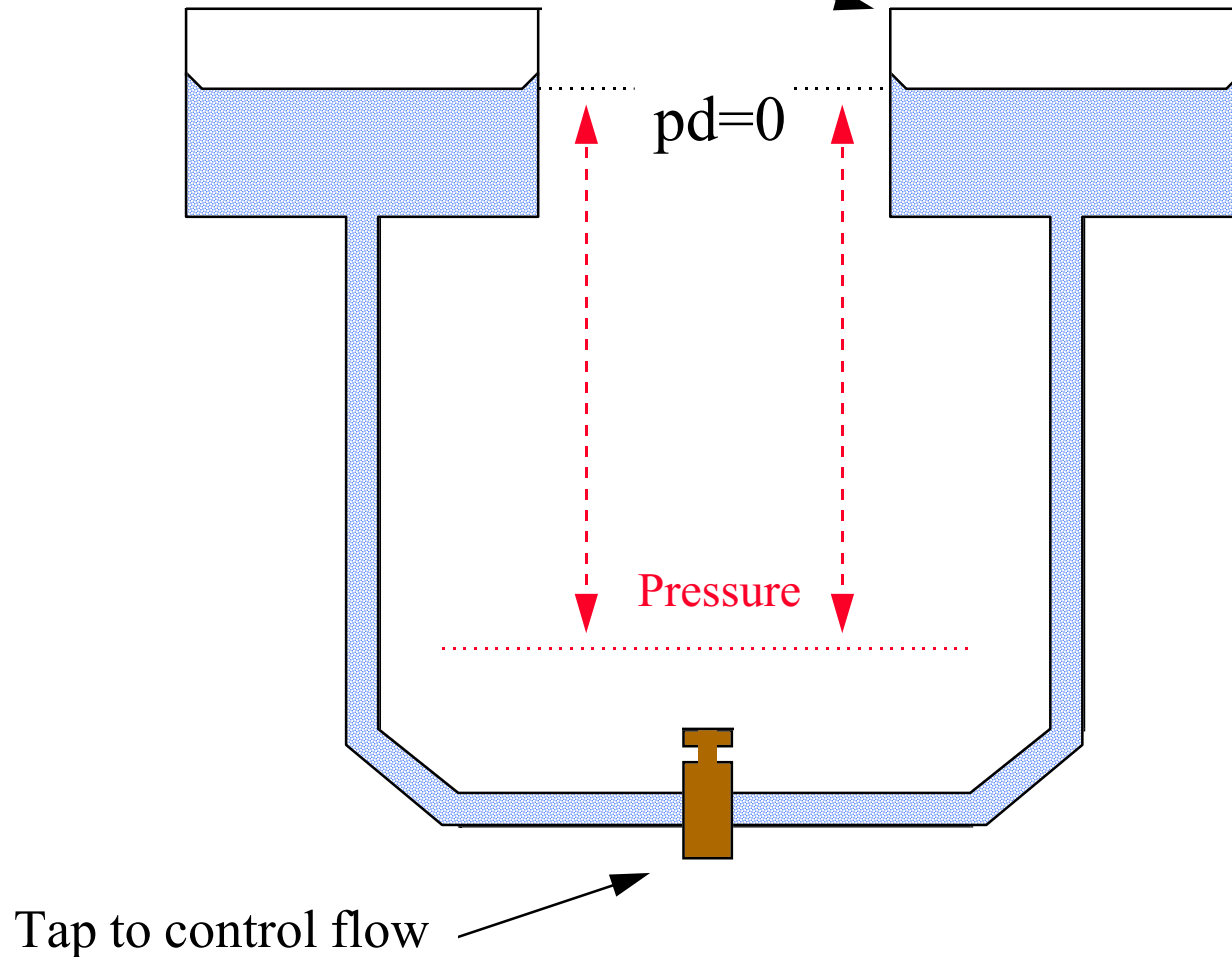

Question

When the
Tap is
opened
which
direction
will the
liquid flow.

Summary


The Basics.

- For a **Current** to flow there must be a Pressure or **Potential difference** to drive that current flow.
- Whenever **Current** flows through a Resistance then a Pressure or **Potential difference** can be measured across the Resistance.
- If **NO Current** flows through a Resistance then the voltage or Pressure across the Resistance is Zero. (**The Voltage is the same at both ends.**)

The Basics.

Water
Container

The Water analogy
Fill Rate (Charging).

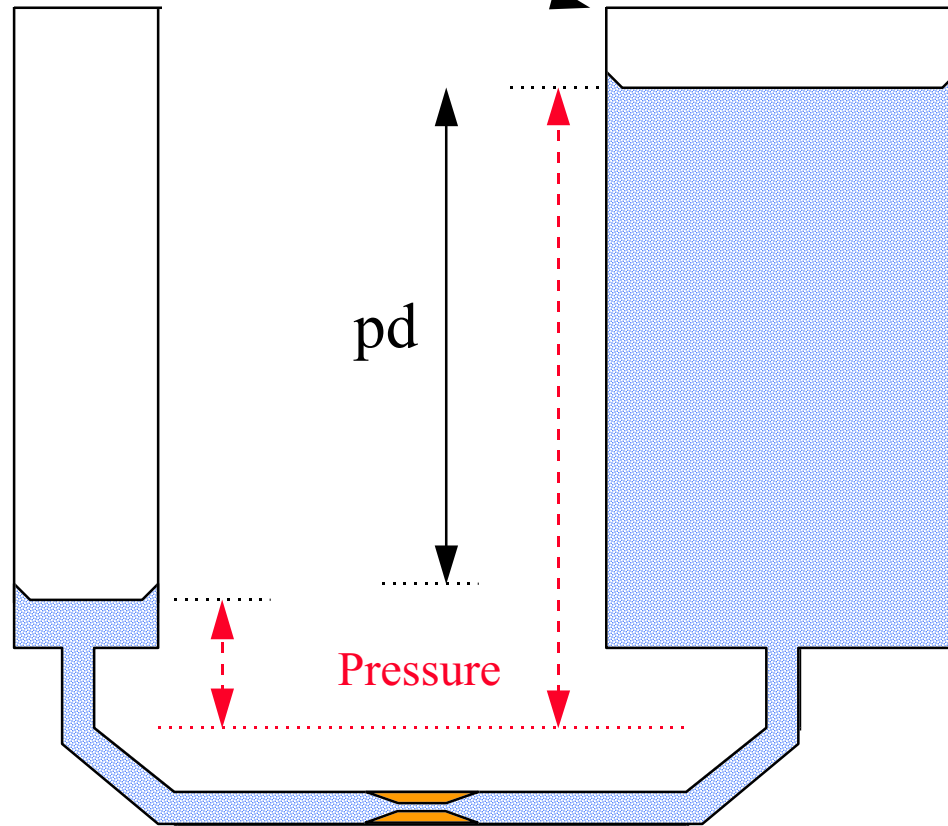

Questions


What
controls the
rate of flow
between the
tanks ?

Restriction in the feeder pipe.

The Basics.

Water
Container

The Water analogy
Fill Rate (Charging).

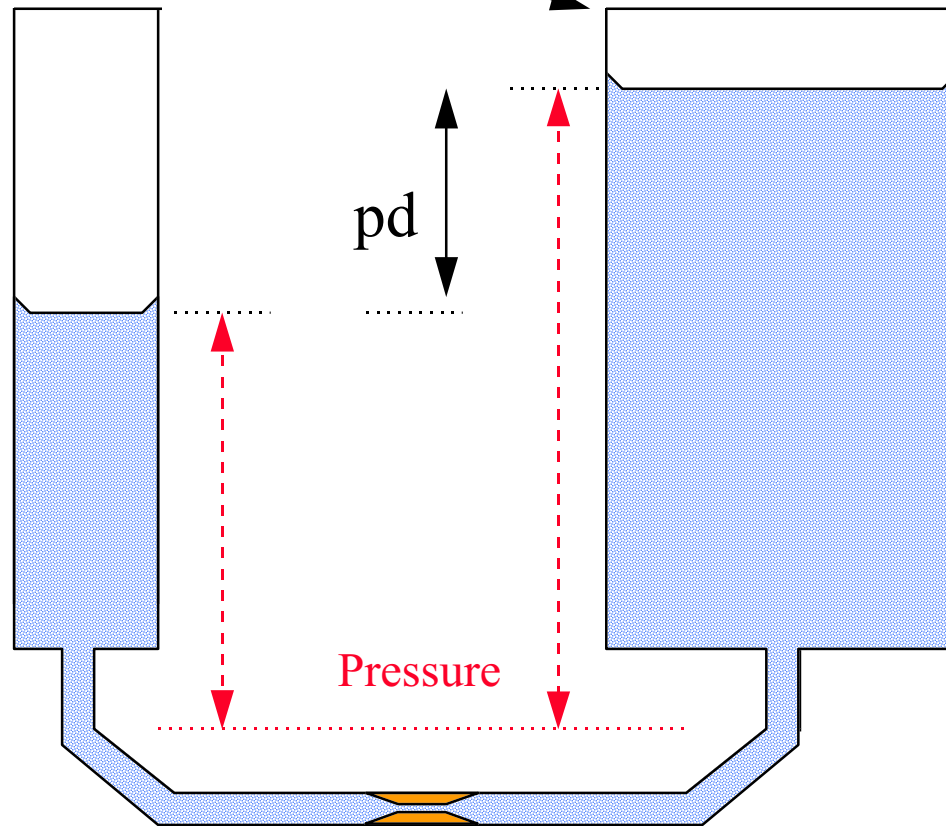

Questions

When does
the greatest
flow rate
occur ?

How long
does it take
for the levels
to be
identical.

Restriction that will control flow rate

Summary



The Basics.

- Maximum flow rate occurs when greatest pressure difference is across restriction.
- As the container fills the pressure difference reduces and so flow rate reduces.
- The **time** to fill is **proportional to** the restriction **resistance** and the **capacity** of the container.
- Additional information:-
The relationship of change takes an **exponential** form (Shape of the curve)


Summary

The Basics.

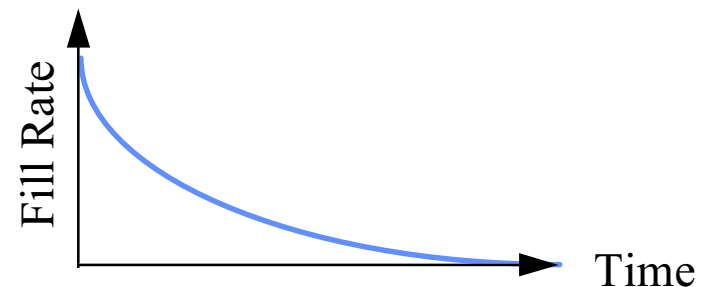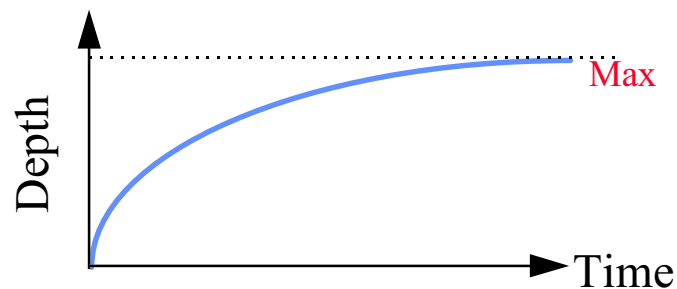- Controlling factors are the **capacity** of the container, the **potential difference** between levels and the restriction **resistance**.
- Graphically the fill rate will take the form as follows :-




The Basics.

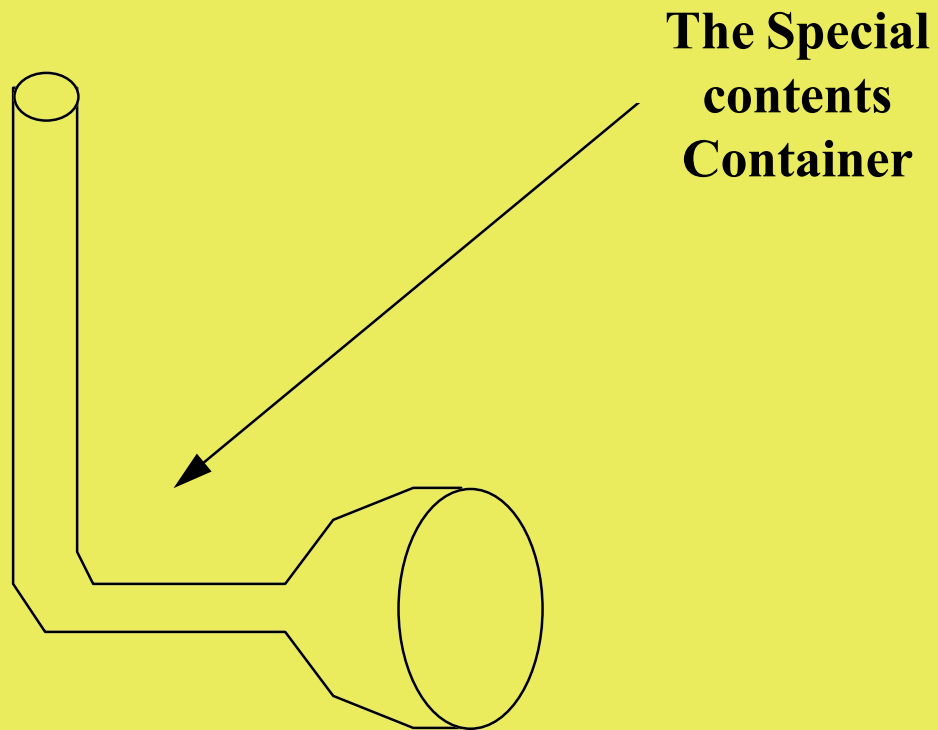


Capacitor concepts.

The Basics.

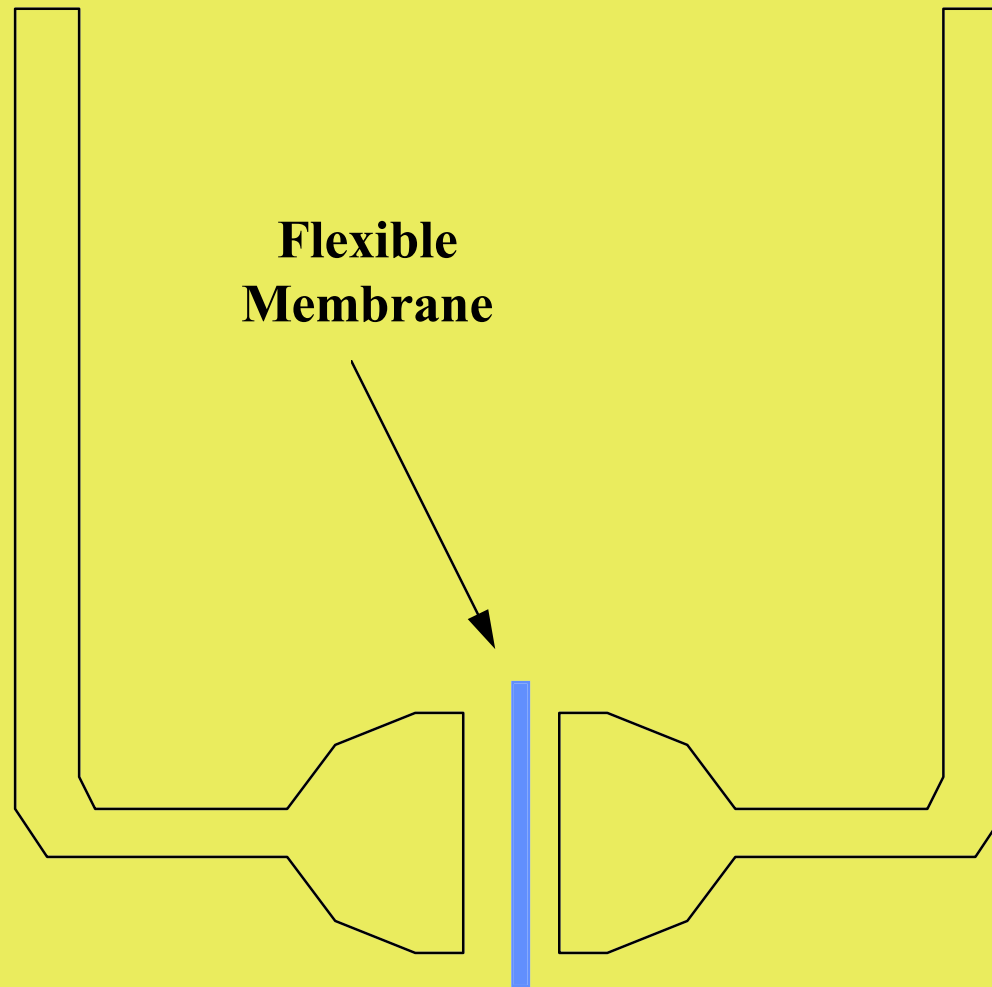

Take two containers separated by a flexible membrane.


The Basics.

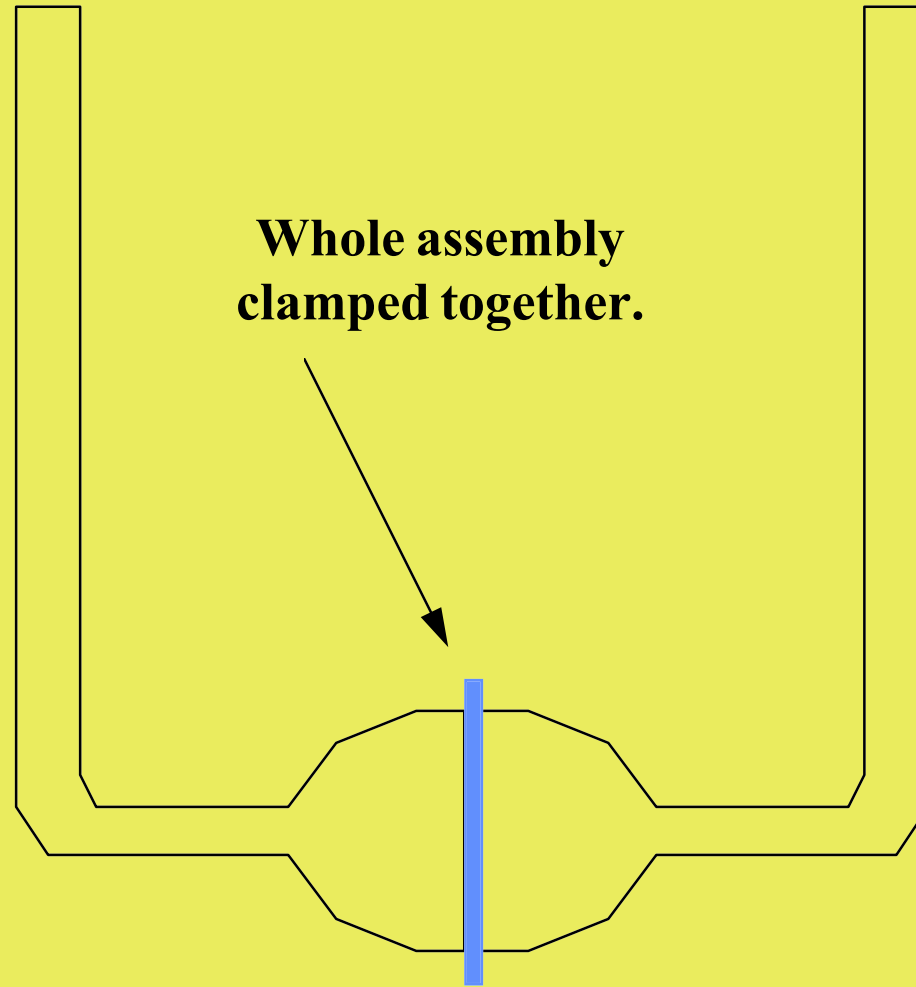

**Whole assembly
clamped together.**


Clamp whole assembly together.

The Basics.

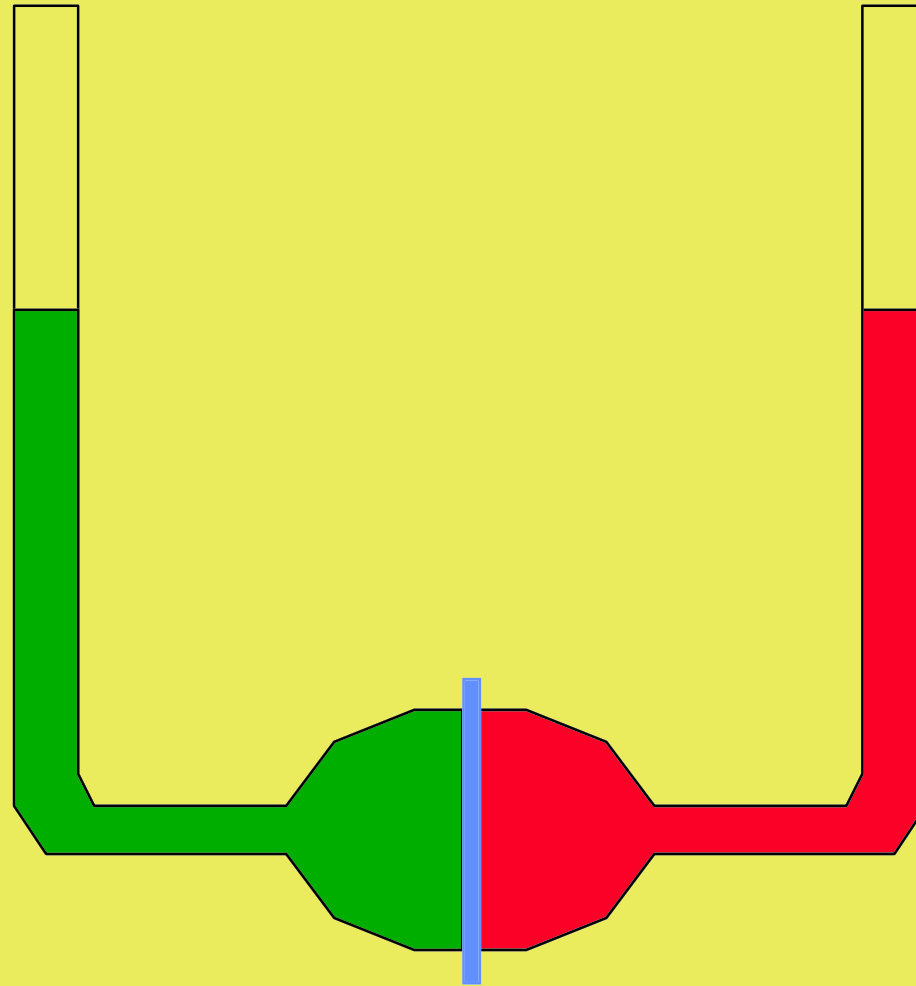

We now fill with our favourite coloured liquid.

The Basics.

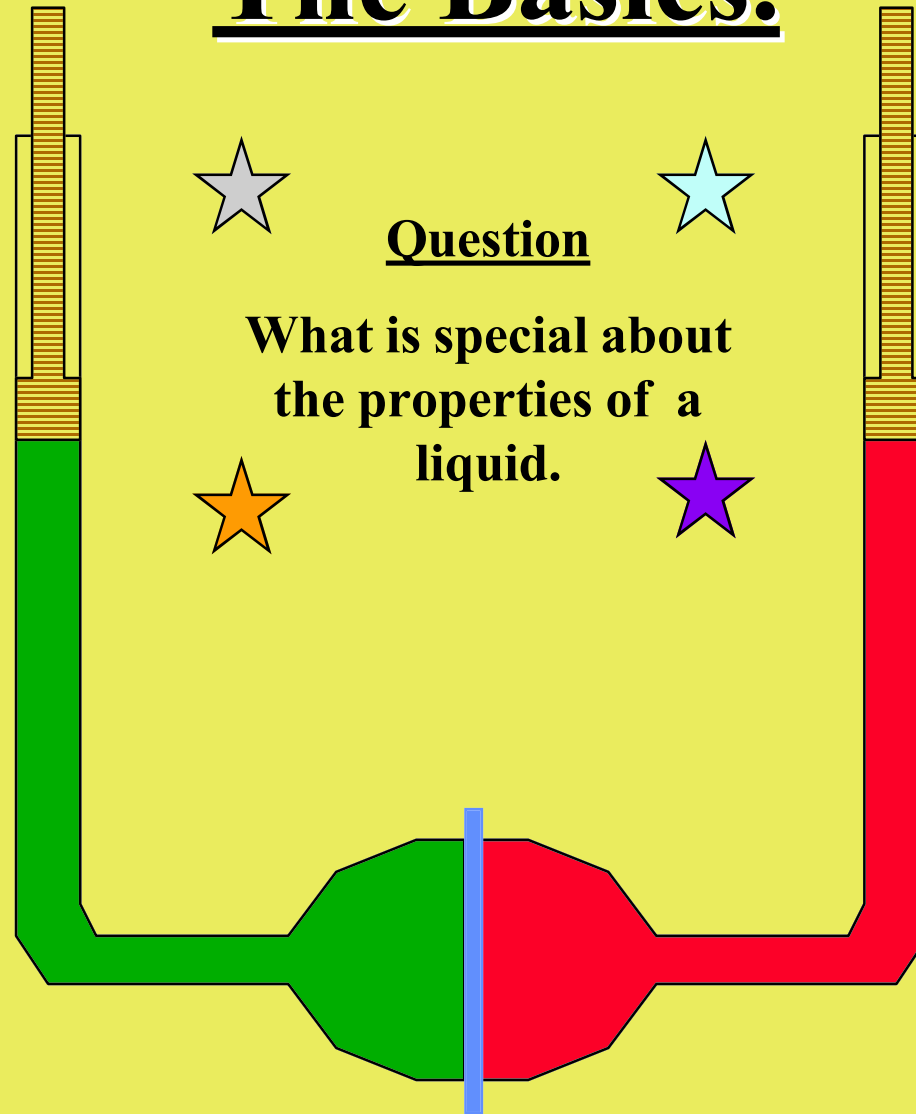

Question


What is special about
the properties of a
liquid.

Place plunger on top of each liquid.

The Basics.

Question

What should
happen?

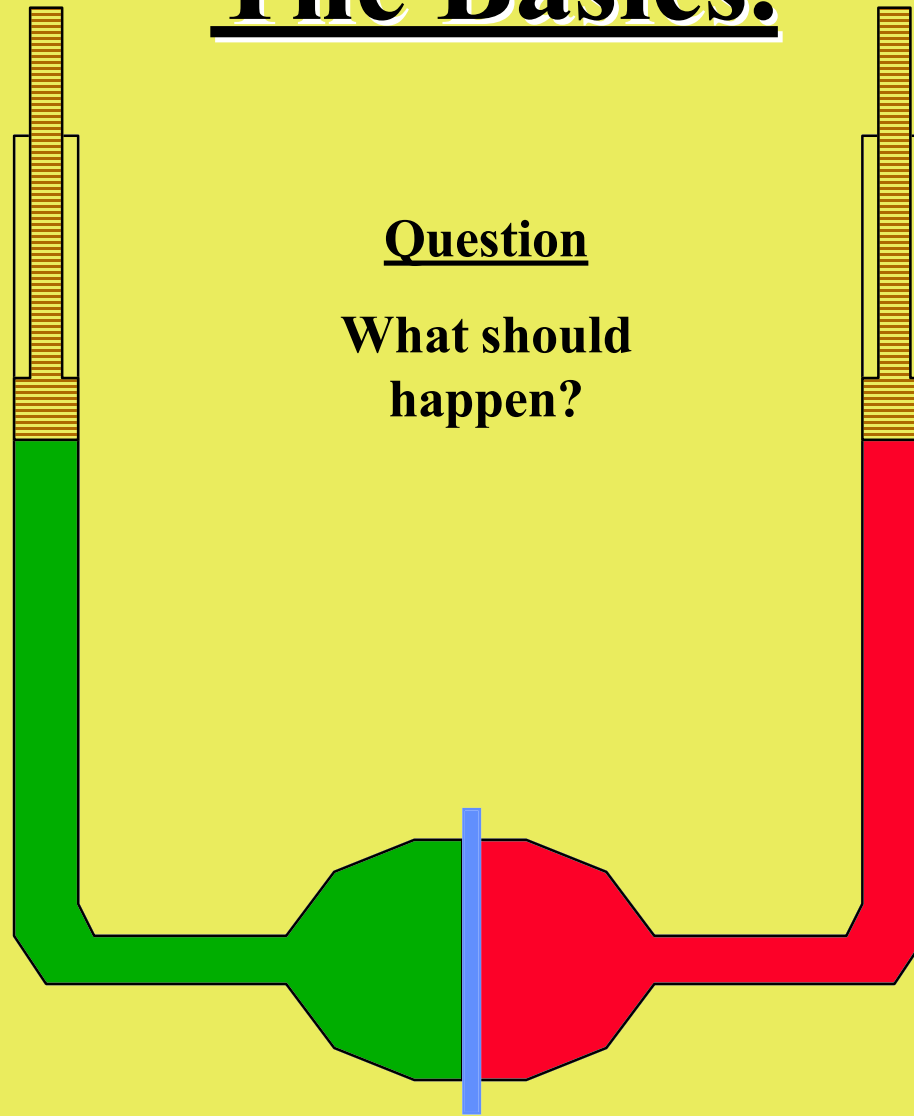


If we apply pressure to right hand Plunger.

The Basics.

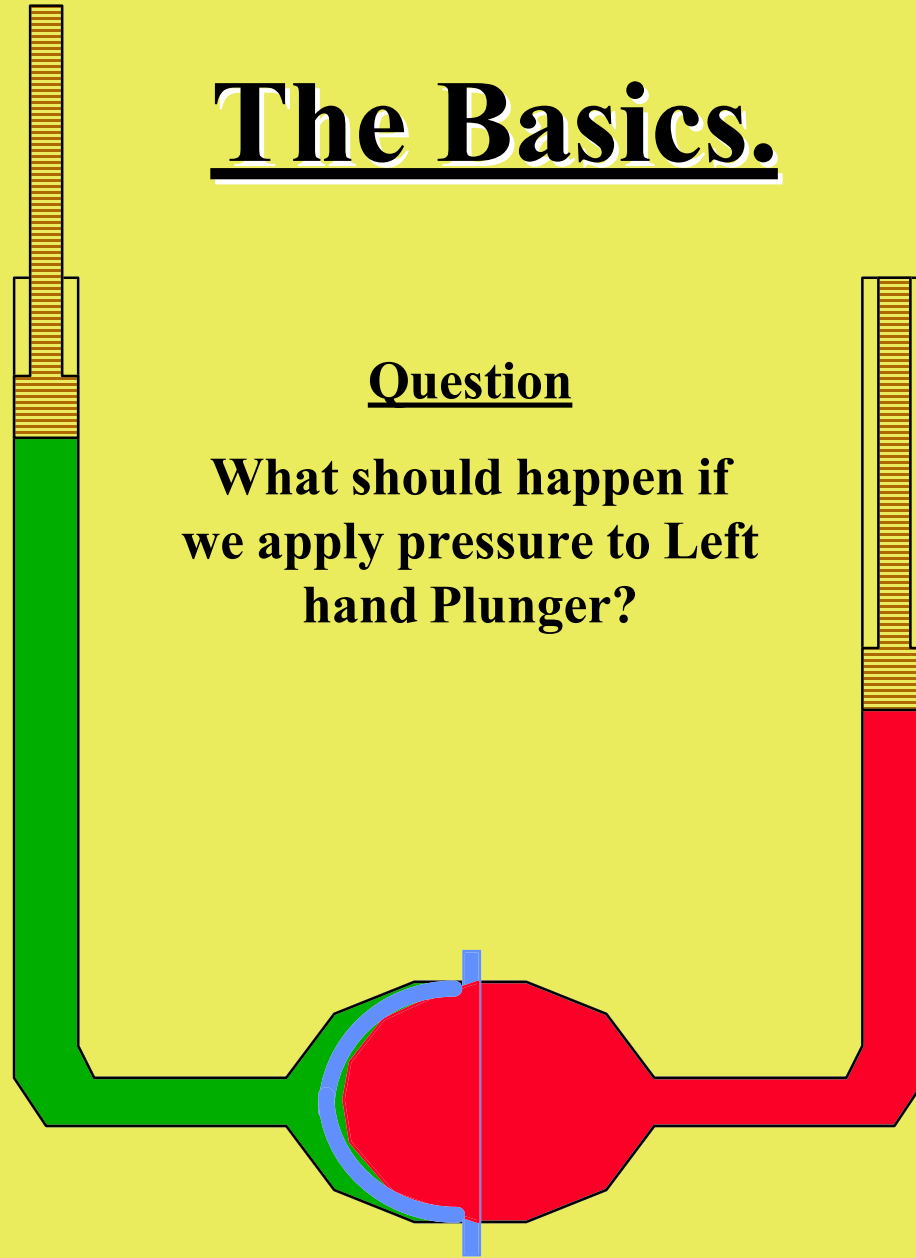Question

What should happen if we apply pressure to Left hand Plunger?




The effect with pressure applied to right hand Plunger.


The Basics.

Question

What have you
observed ?

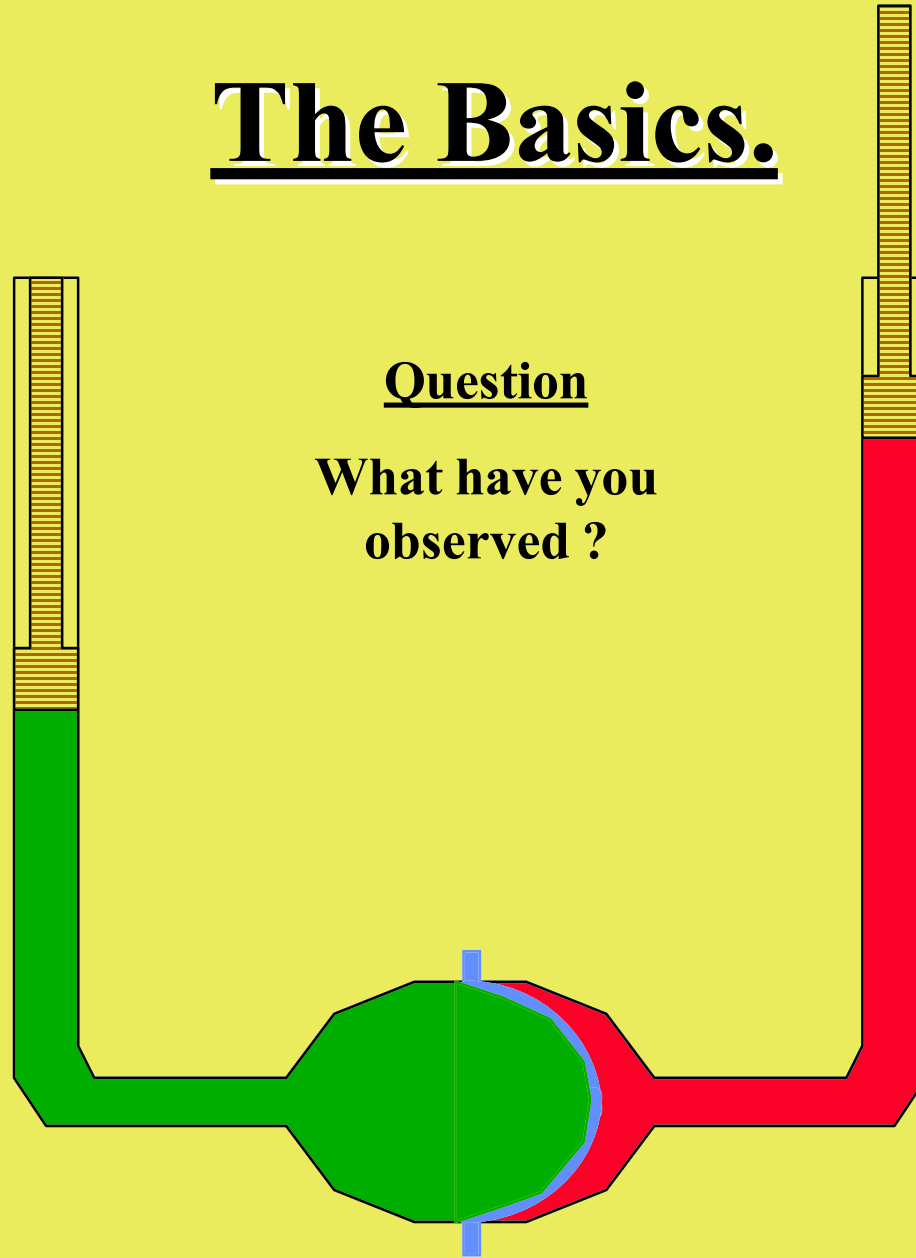


The Basics.

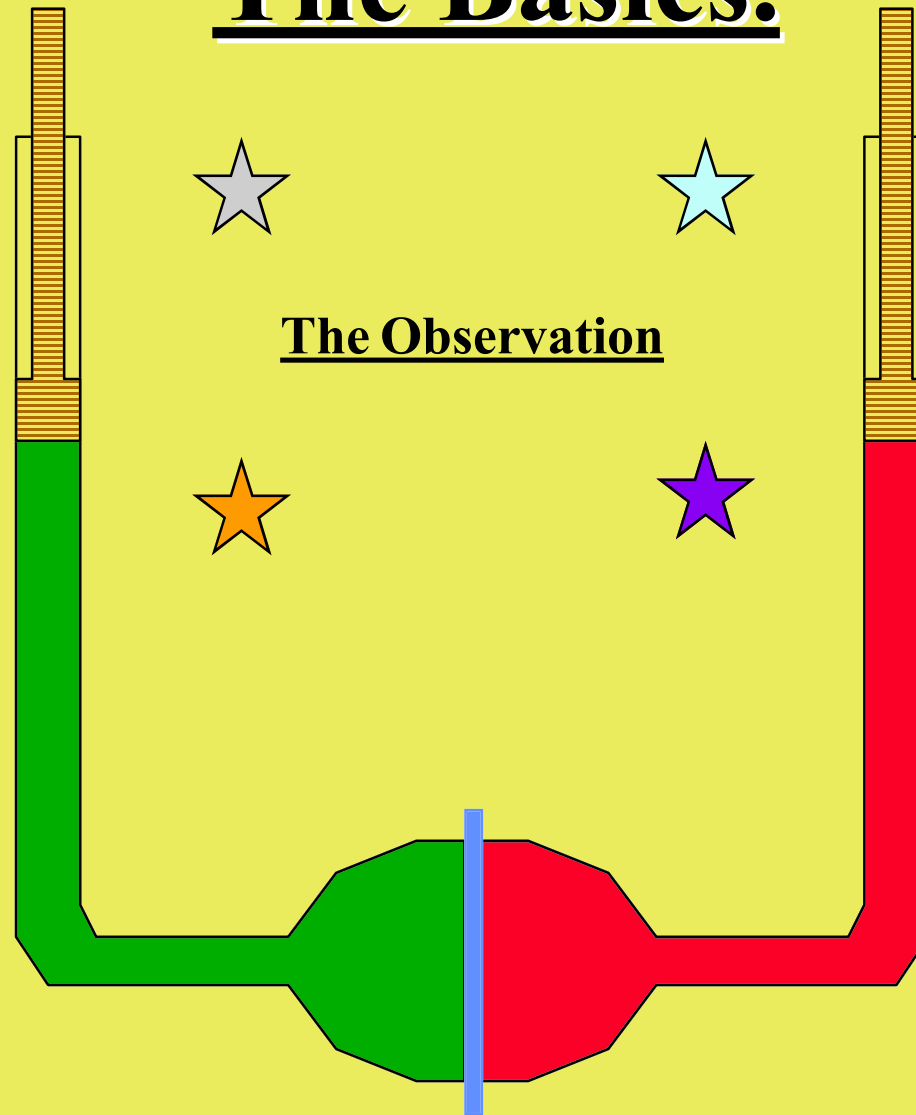

Energy can be transferred through the device without direct contact.

The Basics.

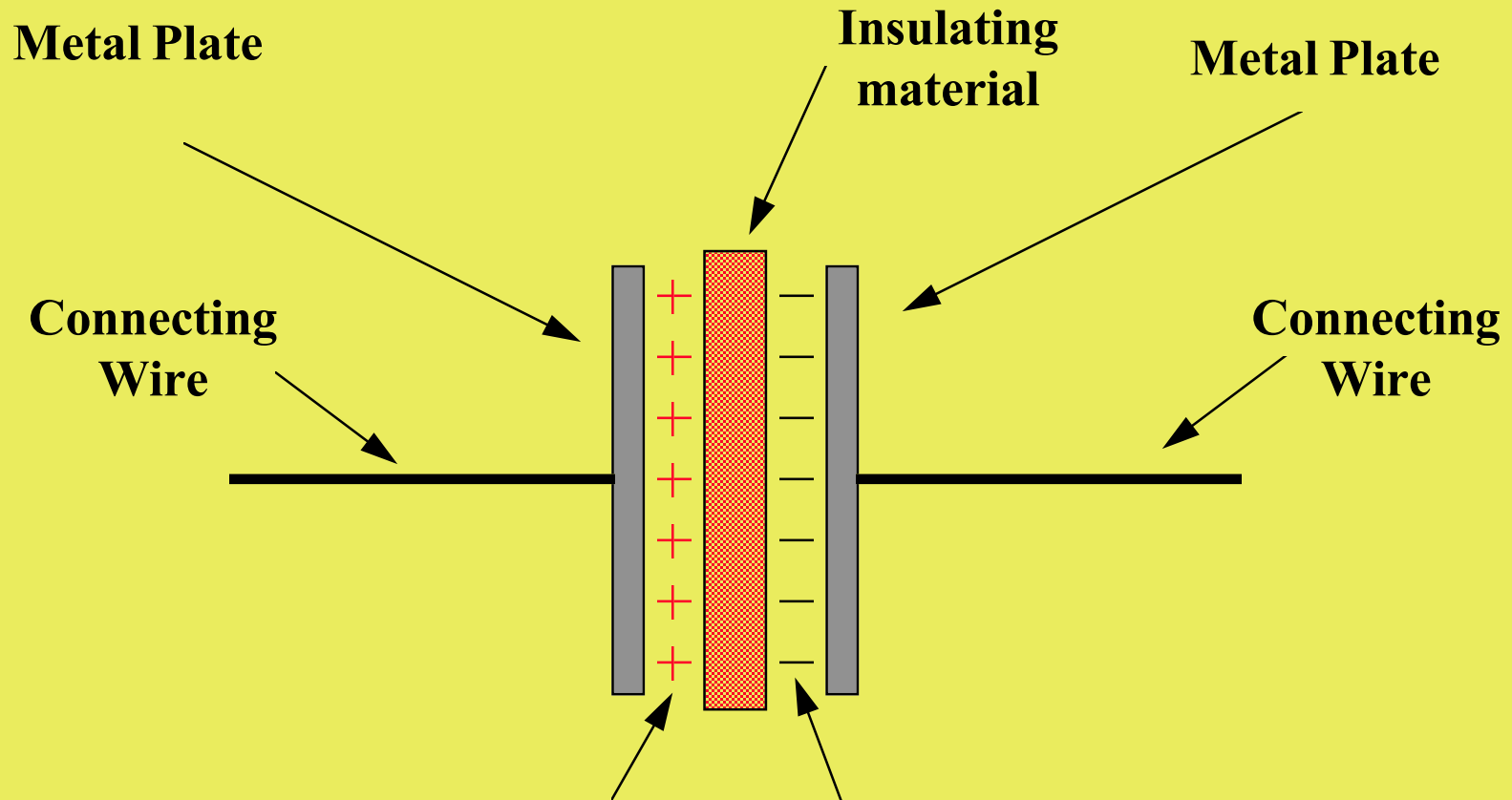

An Electric Charge can be built up on the plates

Capacitor concepts.

Summary

The Basics.

- The liquids never mix (The membrane acts as a liquid block).
- The insulator in the capacitor acts as a DC block.
- Energy can be transferred providing pressure is changing.
- With capacitors they enable energy to transfer when an Alternating current is applied AC.
- If an excess pressure is applied the membrane will fail, insulation will fail.

Engineering Numbers

Engineering Numbers.

- 1 Yotta Y = 1,000,000,000,000,000,000,000,000
- 1 Zetta Z = 1,000,000,000,000,000,000,000
- 1 Exa E = 1,000,000,000,000,000,000
- 1 Peta P = 1,000,000,000,000,000
- 1 Tera T = 1,000,000,000,000
- 1 Giga G = 1,000,000,000
- 1 Mega M = 1,000,000
- 1 Kilo K = 1,000
- 1 (units) = 1
- 1 milli m = 0.001
- 1 micro μ = 0.000 001
- 1 nano n = 0.000 000 001
- 1 pico p = 0.000 000 000 001
- 1 femto f = 0.000 000 000 000 001
- 1 atto a = 0.000 000 000 000 000 001

Engineering Numbers.

• 1 **Peta** P = 1,000,000,000,000,000

• 1 Tera T = 1,000,000,000,000

• 1 Giga G = 1,000,000,000

• 1 Mega M = 1,000,000

• 1 Kilo K = 1,000

• 1 (units) = 1

• 1 milli m = 0.001

• 1 micro μ = 0.000 001

• 1 nano n = 0.000 000 001

• 1 pico p = 0.000 000 000 001

• 1 femto f = 0.000 000 000 000 001

• 1 atto a = 0.000 000 000 000 000 001

NOT in common
usage **YET**

Engineering Numbers.

- 1 Tera T = 1,000,000,000,000
- 1 Giga G = 1,000,000,000
- 1 Mega M = 1,000,000
- 1 Kilo K = 1,000
- 1 = 1

- 1 milli m = 0.001
- 1 micro μ = 0.000 001
- 1 nano n = 0.000 000 001
- 1 pico p = 0.000 000 000 001

**Let us highlight
the significant
parts of these
numbers.**

Engineering Numbers.

- 1 Tera T = 1,000,000,000,000
- 1 Giga G = 1,000,000,000
- 1 Mega M = 1,000,000
- 1 Kilo K = 1,000
- 1 = 1

- 1 **milli** m = 0.001
- 1 **micro** μ = 0.000 001
- 1 **nano** n = 0.000 000 001
- 1 **pico** p = 0.000 000 000 001

It is also perfectly acceptable to add zeros to the end of a decimal fraction.

Engineering Numbers.

- 1 Tera T = 1,000,000,000,000
 - 1 Giga G = 1,000,000,000
 - 1 Mega M = 1,000,000
 - 1 Kilo K = 1,000
 - 1 = 1
-
- 1 **milli** m = 0.**001** **000** **000** 000
 - 1 **micro** μ = 0.**000** **001** **000** 000
 - 1 **nano** n = 0.**000** **000** **001** 000
 - 1 **pico** p = 0.**000** **000** **000** 001

Engineering Numbers.

How could we express

98 **micro** units in terms of **nano** units ?

-
- 1 **milli** m = 0.**001** **000** **000** 000
 - 1 **micro** μ = 0.**000** **001** **000** 000
 - 1 **nano** n = 0.**000** **000** **001** 000
 - 1 **pico** p = 0.**000** **000** **000** 001

Engineering Numbers.

How could we express

98 **micro** units in terms of **nano** units ?

0 **9** **8** **0** **0** **0** or 98,000 n

-
- 1 **milli** m = 0.**001** **000** **000** 000
 - 1 **micro** μ = 0.**000** **001** **000** 000
 - 1 **nano** n = 0.**000** **000** **001** 000
 - 1 **pico** p = 0.**000** **000** **000** 001

Engineering Numbers.

How could we express

98 **micro** units in terms of **milli** units ?

-
- 1 **milli** m = 0.**001** **000** **000** 000
 - 1 **micro** μ = 0.**000** **001** **000** 000
 - 1 **nano** n = 0.**000** **000** **001** 000
 - 1 **pico** p = 0.**000** **000** **000** 001

Engineering Numbers.

How could we express

98 **micro** units in terms of **milli** units ?

0 0 0 0 9 8 or 0.098 m

-
- 1 **milli** m = 0.**001** **000** **000** 000
 - 1 **micro** μ = 0.**000** **001** **000** 000
 - 1 **nano** n = 0.**000** **000** **001** 000
 - 1 **pico** p = 0.**000** **000** **000** 001

Engineering Numbers.

Let us now look the numbers greater than one.

-
- 1 **milli** m = 0.**001** **000** **000** 000
 - 1 **micro** μ = 0.**000** **001** **000** 000
 - 1 **nano** n = 0.**000** **000** **001** 000
 - 1 **pico** p = 0.**000** **000** **000** 001

Engineering Numbers.

- 1 Tera T = 1,000,000,000,000
- 1 Giga G = 1,000,000,000
- 1 Mega M = 1,000,000
- 1 Kilo K = 1,000
- 1 = 1
- 1 milli m = 0.001 000 000 000
- 1 micro μ = 0.000 001 000 000
- 1 nano n = 0.000 000 001 000
- 1 pico p = 0.000 000 000 001

It is also perfectly acceptable to add zeros to the front of a decimal number without changing its value.

Engineering Numbers.

- 1 Tera T = 1,000,000,000,000
- 1 Giga G = 0,001,000,000,000
- 1 Mega M = 0,000,001,000,000
- 1 Kilo K = 0,000,000,001,000
- 1 = 0,000,000,000,001
- 1 milli m = 0.001 000 000 000
- 1 micro μ = 0.000 001 000 000
- 1 nano n = 0.000 000 001 000
- 1 pico p = 0.000 000 000 001

**Let us look
at numbers
greater or
equal to
one and
colour code
them.**

Engineering Numbers.

- 1 Tera T = 1,000,000,000,000
- 1 Giga G = 0,001,000,000,000
- 1 Mega M = 0,000,001,000,000
- 1 Kilo K = 0,000,000,001,000
- 1 = 0,000,000,000,001
- 1 milli m = 0.001 000 000 000
- 1 micro μ = 0.000 001 000 000
- 1 nano n = 0.000 000 001 000
- 1 pico p = 0.000 000 000 001

**Let us look
at numbers
greater or
equal to
one and
colour code
them.**

Engineering Numbers.

How could we express

98 **Mega** units in terms of **Kilo** units ?

-
- 1 Tera T = 1,000,000,000,000
 - 1 Giga G = 0,001,000,000,000
 - 1 Mega M = 0,000,001,000,000
 - 1 Kilo K = 0,000,000,001,000
 - 1 = 0,000,000,000,001

Engineering Numbers.

How could we express

98 Mega units in terms of Kilo units ?

0 9 8 0 0 0 or 98000K

-
- 1 Tera T = 1,000,000,000,000
 - 1 Giga G = 0,001,000,000,000
 - 1 Mega M = 0,000,001,000,000
 - 1 Kilo K = 0,000,000,001,000
 - 1 = 0,000,000,000,001

Engineering Numbers.

How could we express

98 **Mega** units in terms of **Giga** units ?

-
- 1 Tera T = 1,000,000,000,000
 - 1 Giga G = 0,001,000,000,000
 - 1 Mega M = 0,000,001,000,000
 - 1 Kilo K = 0,000,000,001,000
 - 1 = 0,000,000,000,001

Engineering Numbers.

How could we express

98 Mega units in terms of Giga units ?

00 0098 or 0.098G

-
- 1 Tera T = 1,000,000,000,000
 - 1 Giga G = 0,001,000,000,000
 - 1 Mega M = 0,000,001,000,000
 - 1 Kilo K = 0,000,000,001,000
 - 1 = 0,000,000,000,001

Three Digit Numbers

Three Digit Numbers.

- This is a short hand method to describe Engineering number values but never using more than three characters.
- Many engineering values have a tolerance of 10% therefore we never need more than two significant digits to express the value.
- The rest of the Three Digit Number is the multiplier or division factor .
- Example 12K = 12 times 1000 = 12000
- Example 22μ = 22 times 0.000001 = 0.000022
- **So how would we deal with a number like 1800.**

Three Digit Numbers.

- So how would we deal with a number like 1800.
- We could write 1800 as $1.8 * 1000 = 1.8K$
- However $1.8K$ is four characters we want just **three**.
- A second point is that the reader could easily miss the decimal point.



Solution ...

- Use the multiplier value to identify where the decimal point would be located.
- So 1800 would be written as $1K8$
- also 270,000 would be written as $0.27 * 1000000 = 0.27M$
- Therefore 270,000 could be written as $M27$

Electrical Circuits


Electrical Circuits.

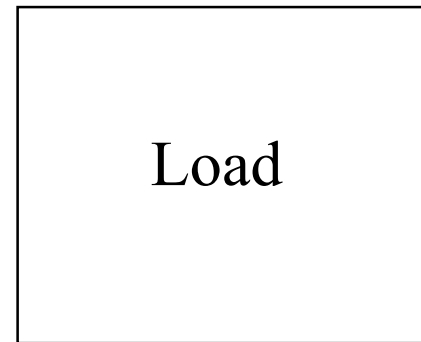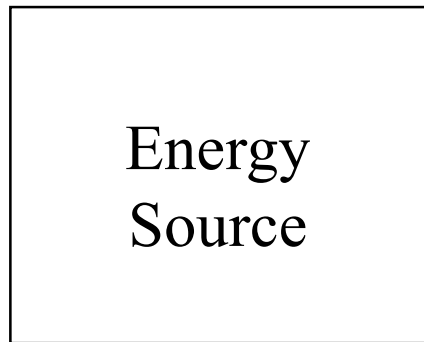All circuits consist of a Source and Load :-



Electrical Circuits.


The Energy source is measured in Volts:-

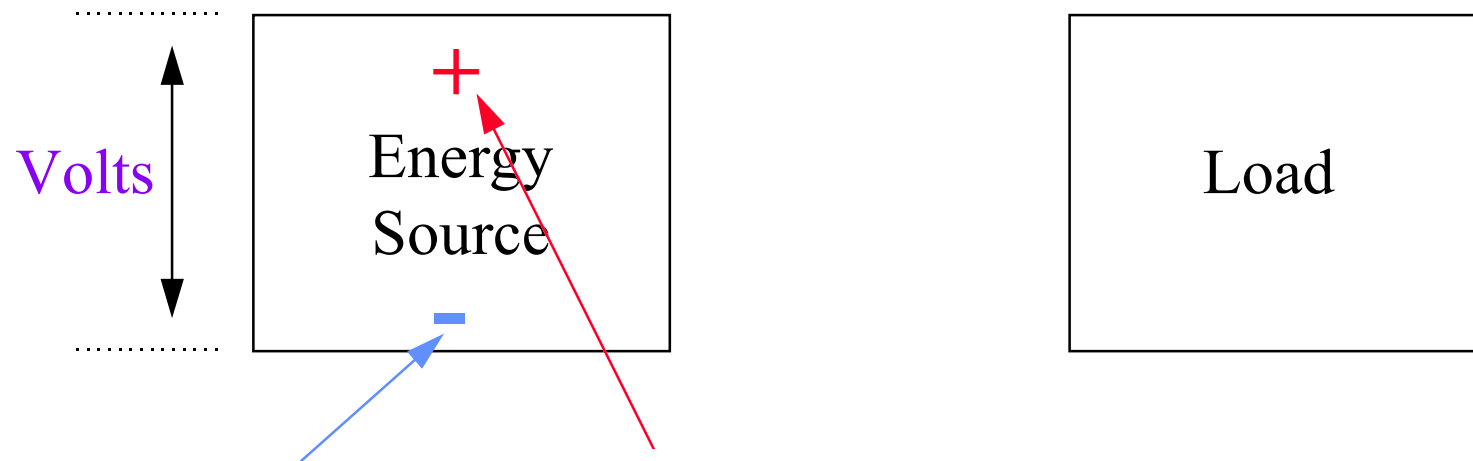

Note The energy source may also be identified with polarity as well.

Electrical Circuits.

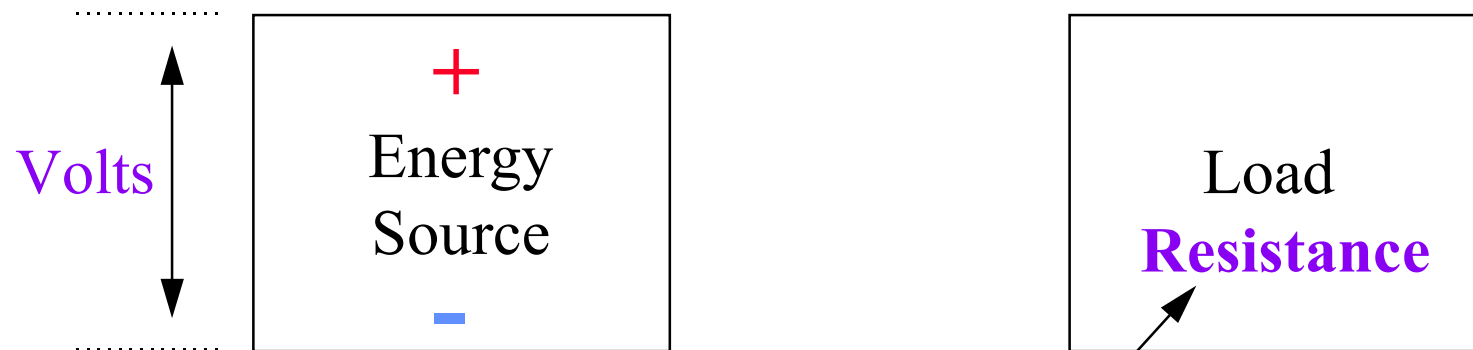
The Load presents a resistance for the Source :-



This is where all the energy that is supplied by the source will be dissipated.

Electrical Circuits.

The Source is connected to the Load :-

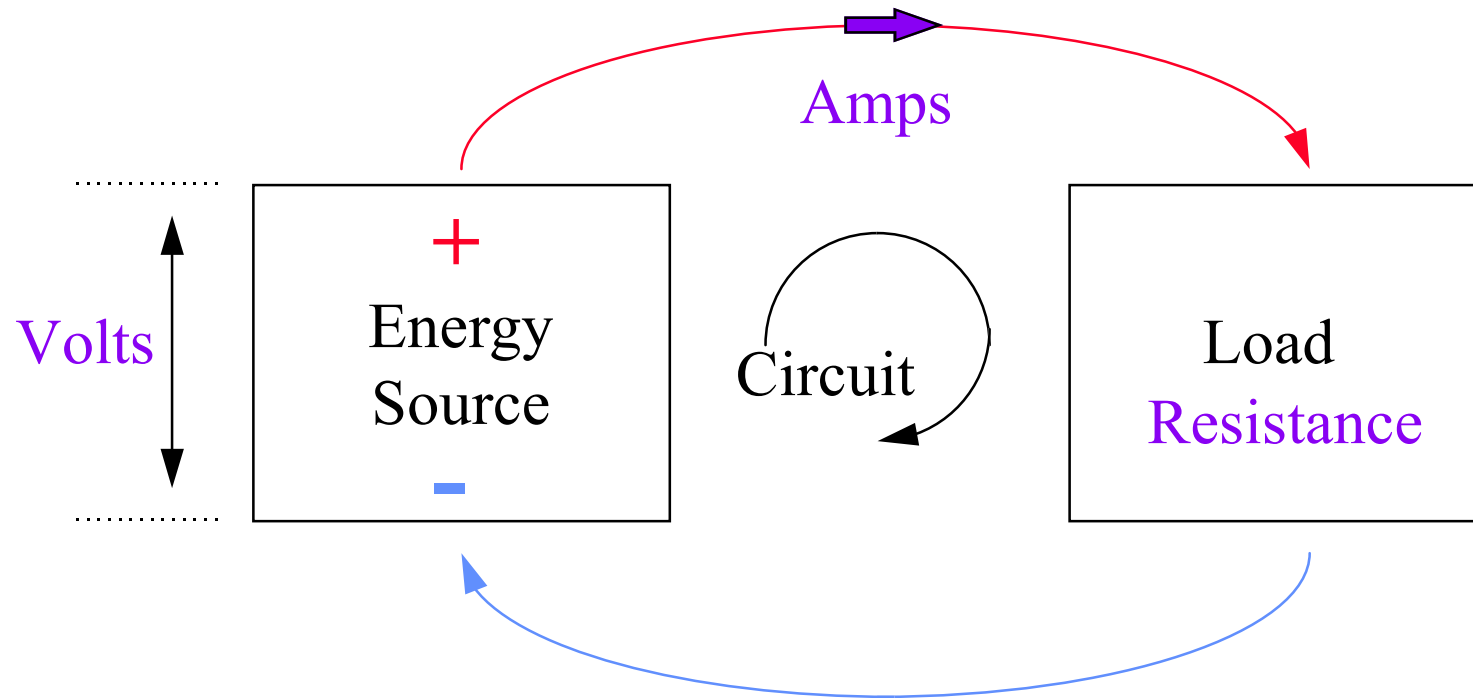

and Energy transferred around
the circuit.

Electrical Circuits.

Summary:

- An Electrical circuit must have an **Energy source** and a **Load**.
- There must be a **direct connection** from source **to Load** and a return path back **to the Source**.
- The relationship between the units of Voltage, Current and Resistance is known as **Ohms Law**.


Resistors

Resistors

Ohms Law


Resistors.

Ohm's Law

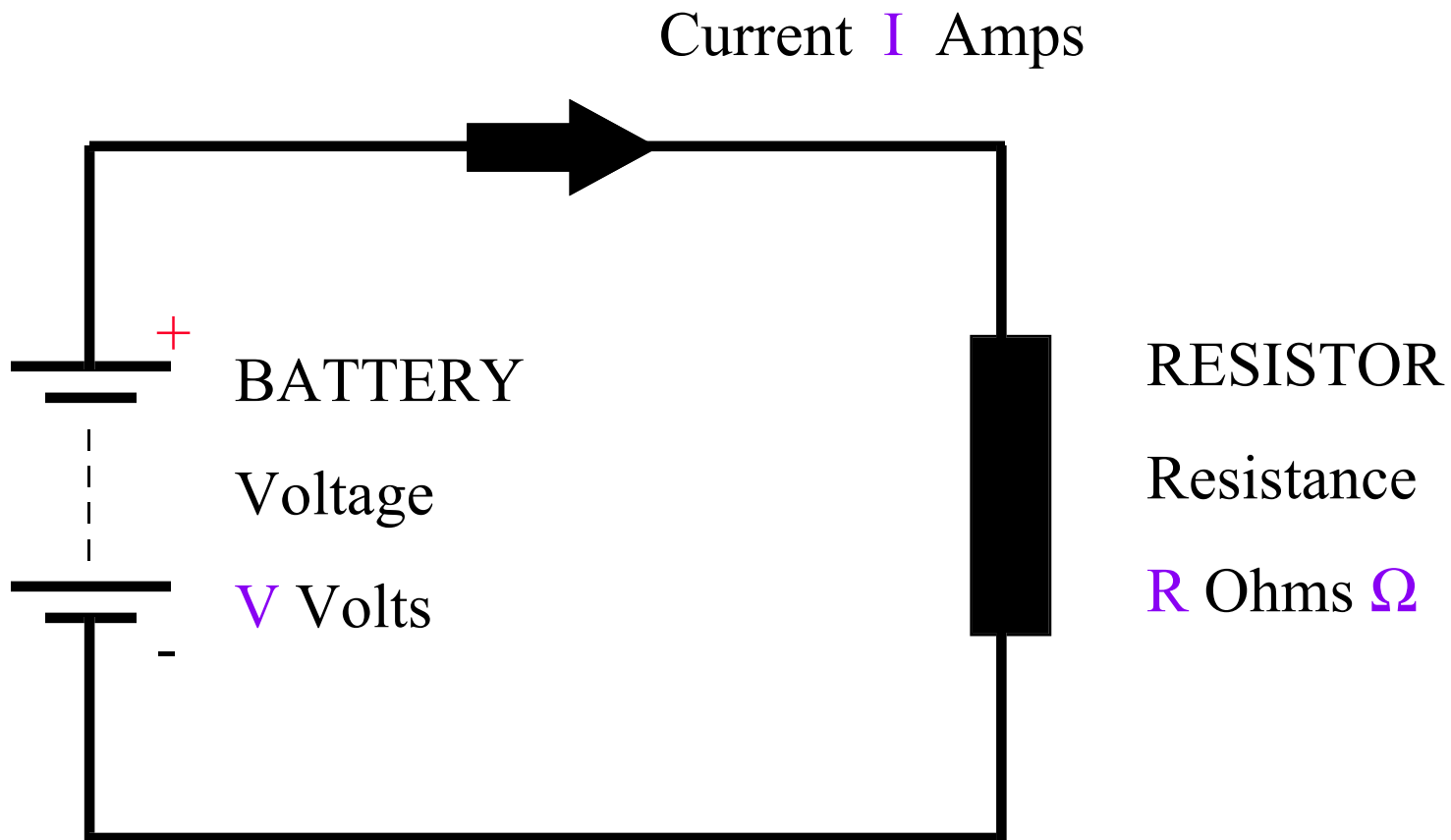

Resistors.


Ohm's Law

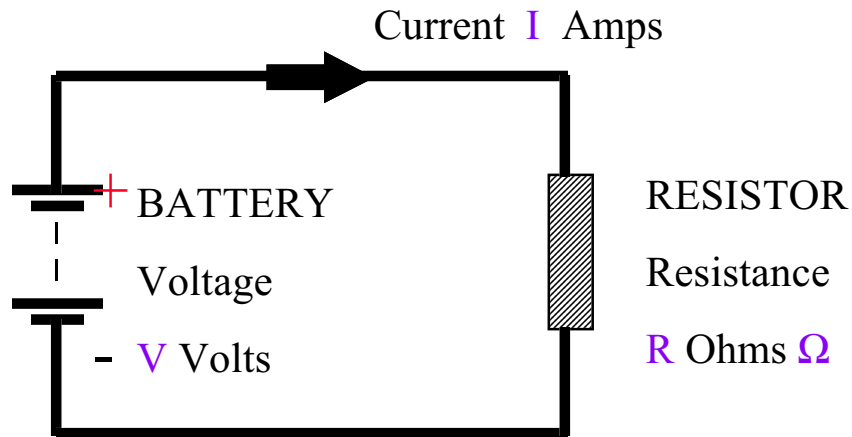

In the circuit : The applied Voltage **V** across resistor **R** causes a current **I** to flow. The relationship between these three quantities is known as Ohm's Law and the ratio is described as follows :-

$$R = \frac{V}{I}$$

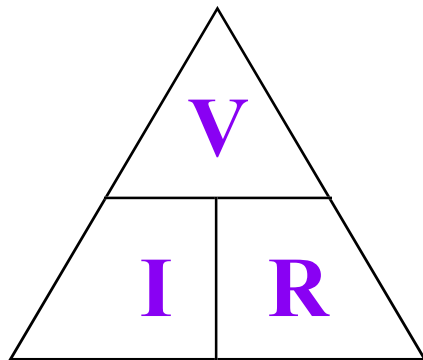Where **I** is in Amps, **V** is Volts and **R** in Ohms.



Resistors.

Volts	Amps	Ohms
10V	2A	.
52V	.	13Ω
.	0.25A	500Ω
104V	5mA	.
12V	110A	.
5V	.	250Ω
9V	20mA	.
.	25μA	2KΩ

Resistors.

Volts	Amps	Ohms
10V	2A	5Ω
52V	4A	13Ω
125V	0.25A	500Ω
104V	5mA	20.8KΩ
12V	110A	0.109Ω
5V	20mA	250Ω
9V	20mA	450Ω
50mV	25μA	2KΩ

Resistors

Power

Definitions.

Resistors.

Power

Power (P) is the amount of effort that can be delivered or absorbed by an entity.

Power is measured in Watts, where :-

One Watt of Power is developed when One Volt causes One Amp of current to flow in a circuit.

$$\text{Watts} = \text{Volts} * \text{Amps}$$

Energy

Energy (E) is the amount of power that can be delivered or absorbed by an entity over a specific time.


Energy is measured in Joules, where :-

One Joule = One Watt for One Second

Resistors.

Power is measured in
Watts, where :-

One Watt = One Volt *
One Amp

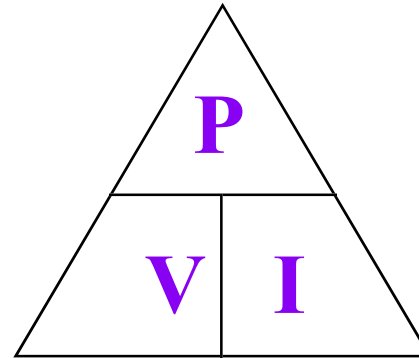

Where **I** is in Amps, **V** is
Volts and **P** in Watts.

Resistors.

Volts	Amps	Watts
10V	2A	.
52V	.	13W
.	0.25A	500W
104V	5mA	.
12V	110A	.
5V	.	250W
9V	20mA	.
.	25 μ A	1.25 μ W

Resistors.

Volts	Amps	Watts
10V	2A	20W
52V	0.25A	13W
2KV	0.25A	500W
104V	5mA	0.52W
12V	110A	1.32KW
5V	50A	250W
9V	20mA	180mW
50mV	25 μ A	1.25 μ W

Resistors.

Question

Can we relate the units of

$$P = V * I$$

Voltage
Current
Resistance
and Power

$$R = V / I$$

into a common relationship ?

Resistors.

(1) Power $P = V * I$

(2) Resistance $R = V / I$

Note in (3) $V = I * R$
 or in (4) $I = V / R$



Substitute (3) in (1)

$$P = I * R * I = I^2 * R$$

Substitute (4) in (1)

$$P = V * V / R = V^2 / R$$

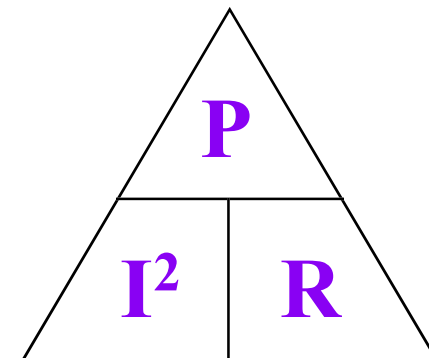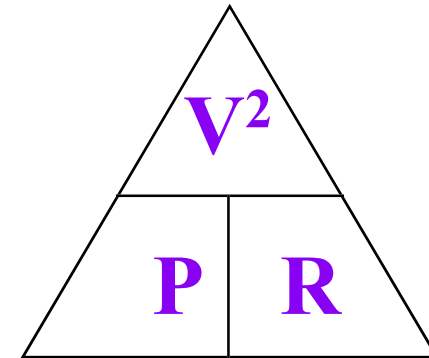Where **P** is in Watts, **I** is in Amps, **V** is Volts and **R** in Ohms.



Resistors

Calculations

Resistor Network Calculations.

- Series and Parallel Resistors
- Voltage divider
- Measurement loading
- Kirchhoff's laws
- Thevenin's Theorem
- Norton's Theorem
- Superposition Method


Resistors.

Series Resistor Proof

Series Connection

Resistors.

The Proof

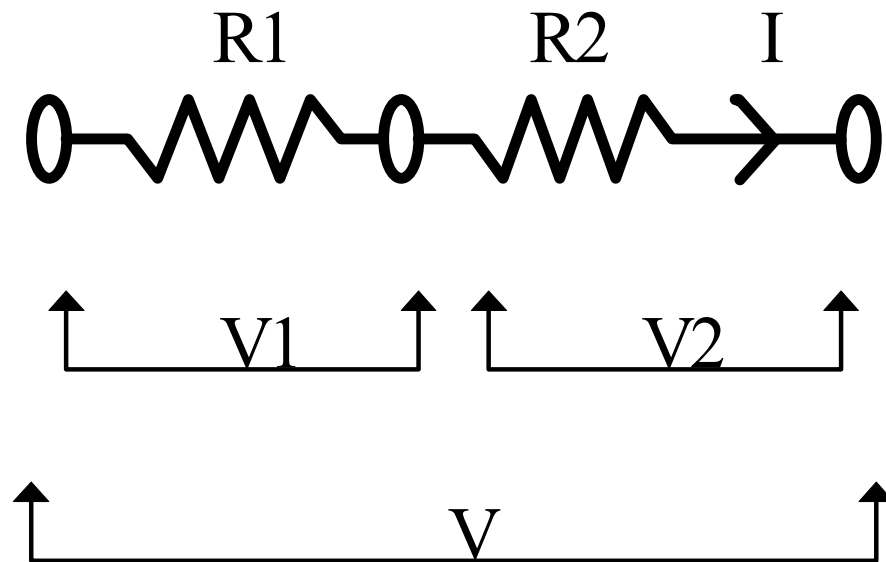

$$\frac{V}{I} = R$$

Series Connection

Resistors.

The Proof

As “I” is Common through both R1 & R2

$$\therefore V = V1 + V2$$

$$V1 = I * R1$$

$$V2 = I * R2$$

$$V = I * R(\text{Total})$$

Series Connection

Resistors.

The Proof

$$\therefore I * R(\text{Total}) = I * R1 + I * R2$$

Now divide through by “I” gives

$$I * R(\text{Total}) = I * R1 + I * R2$$

giving :-

$$R(\text{Total}) = R1 + R2 + \dots \text{ etc}$$


Resistors.

Parallel Resistor Proof

Parallel Connection

Resistors.

The Proof

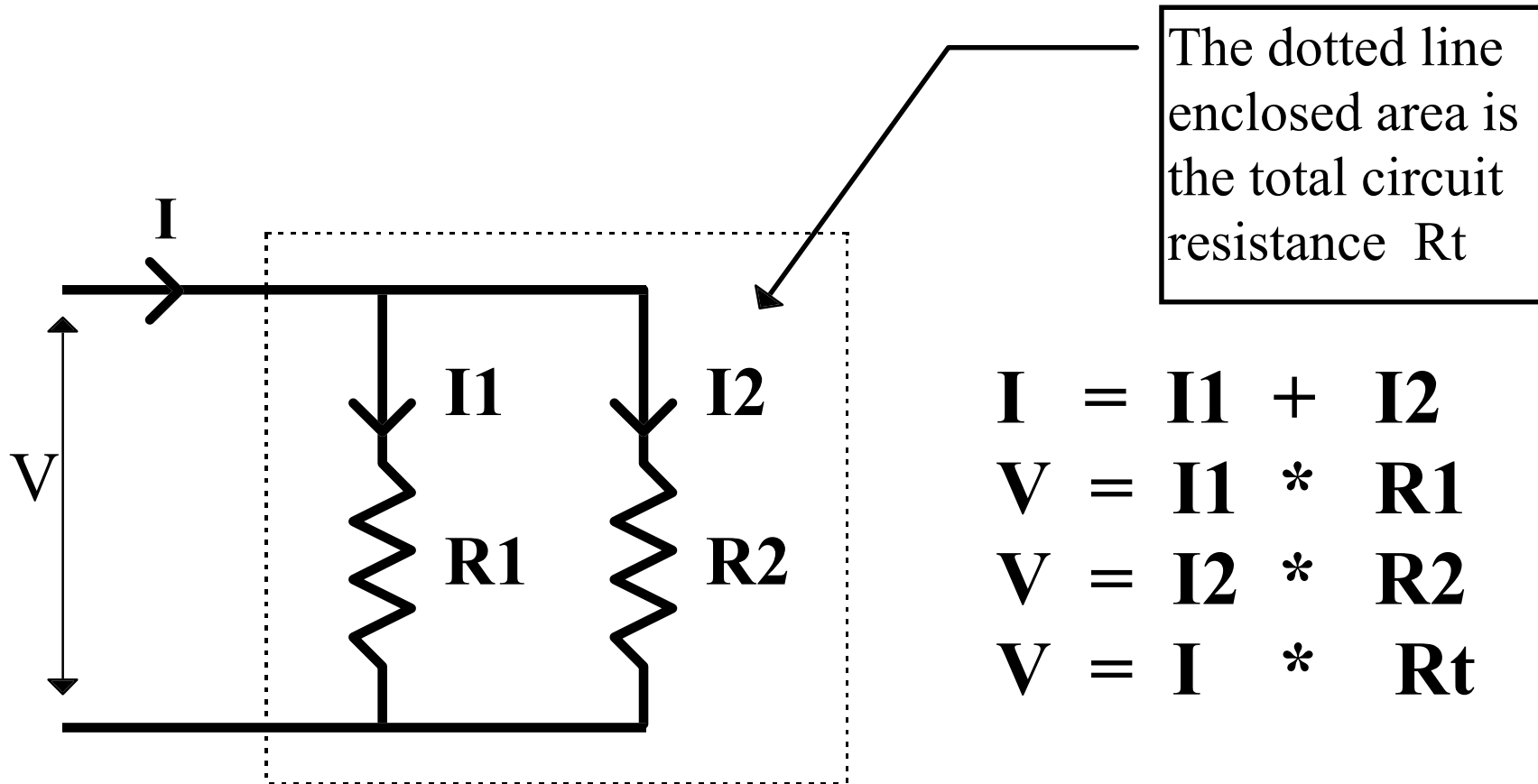

Parallel Connection

Resistors.

The Proof

This Gives

$$\frac{V}{R_t} = I \quad , \quad \frac{V}{R_1} = I_1 \quad , \quad \frac{V}{R_2} = I_2$$

Parallel Connection

Resistors.

The Proof

However If

I = I1 + I2 THEN

$$\frac{V}{R_t} = \frac{V}{R_1} + \frac{V}{R_2} \dots\dots\dots \text{(and Dividing)}$$

$$\text{(by } V \text{ gives)}$$

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} \dots\dots\dots \text{etc.}$$

Resistors.

Two Parallel Resistors

Parallel Connection

Resistors.

Two Resistors

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2}$$

Using a Common denominator ($R_1 * R_2$)

$$\frac{1}{R_t} = \frac{(R_1) + (R_2)}{(R_1 * R_2)}$$

Parallel Connection

Resistors.

Two Resistors

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} \quad \text{or} \quad \frac{R_1 + R_2}{R_1 * R_2}$$

Multiply both sides by (R1 * R2)

$$\frac{1 * R_1 * R_2}{R_t} = \frac{(R_1 + R_2) * (R_1 * R_2)}{R_1 * R_2}$$

Parallel Connection

Resistors.

Two Resistors

Which gives :-

$$\frac{R1 * R2}{Rt} = \frac{(R1 + R2)}{1}$$

Multiply both sides by Rt

$$\frac{R1 * R2 * Rt}{Rt} = \frac{(R1 + R2) * Rt}{1}$$

Parallel Connection

Resistors.

Two Resistors

Which gives :-

$$\frac{R1 * R2}{1} = \frac{(R1 + R2) * Rt}{1}$$

Divide both sides by (R1 + R2)

$$\frac{R1 * R2}{(R1 + R2)} = \frac{(R1 + R2) * Rt}{(R1 + R2)}$$

Parallel Connection

Resistors.

Two Resistors

Which gives :-

$$\frac{R1 * R2}{(R1 + R2)} = \frac{Rt}{1}$$

or The Product over Sum Rule

$$Rt = \frac{R1 * R2}{(R1 + R2)}$$

Note: This is often used to evaluate two resistors in parallel.

Resistors.

Resistors Summary

Summary

Resistors.

Resistors in Series

$$R_t = R_1 + R_2 + R_3 \dots \text{etc...}$$

Resistors in Parallel

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} \dots \text{etc.}$$

or
$$R_t = \frac{R_1 * R_2}{(R_1 + R_2)}$$
 The two resistor option.

Resistors.

Circuit Evaluation

Resistors.

The Circuit Evaluation process.

Step 1 , Understand what is required or being asked.

Step 2 , Understand the Circuit Connections.

Step 3 , (Repeat as required)


Simplify any Parallel or Series networks.

Step 4 , Answer the asked Question/s

Step 5 , Process next activity.

Resistors.


Examples

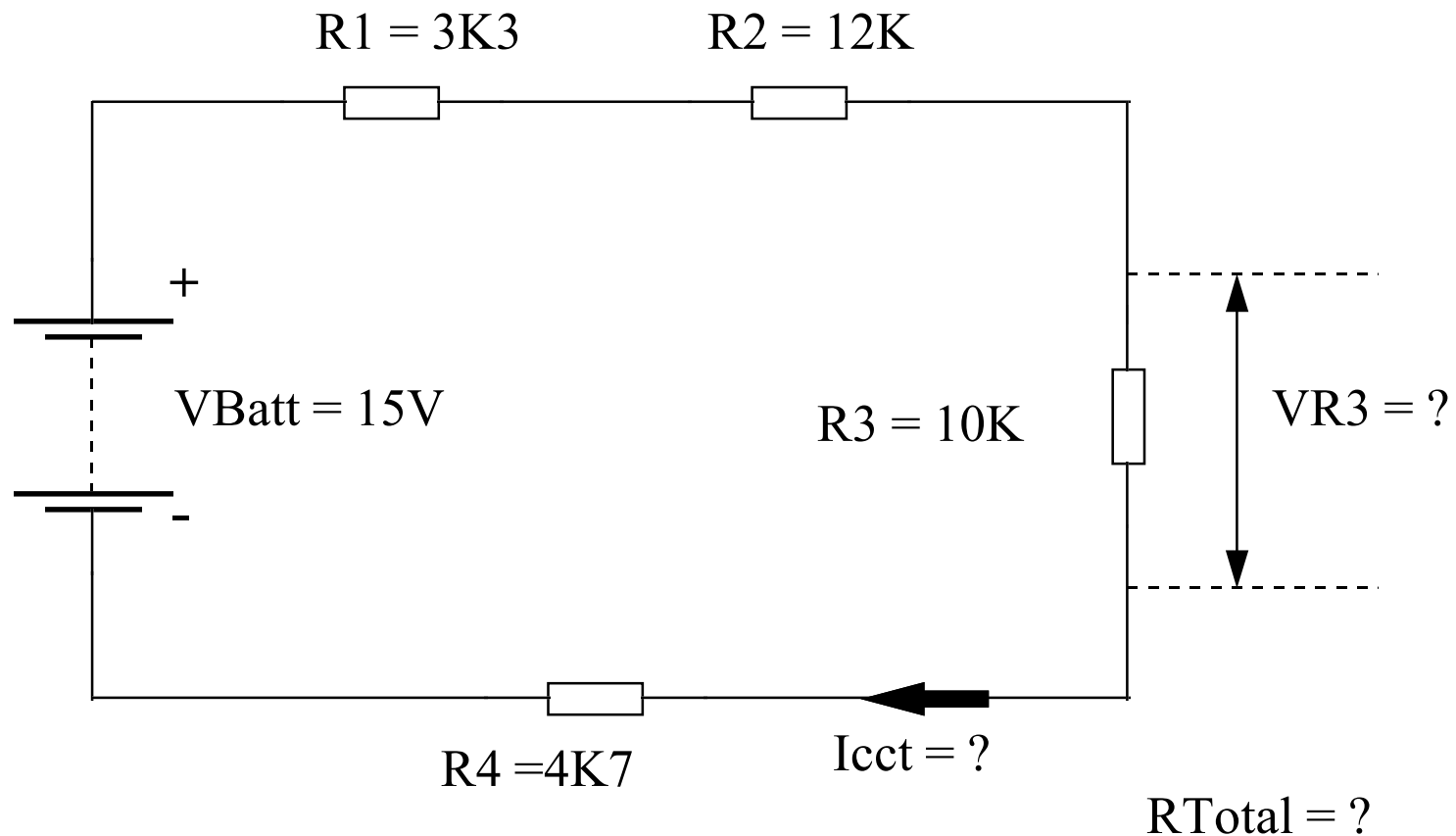

Resistors.

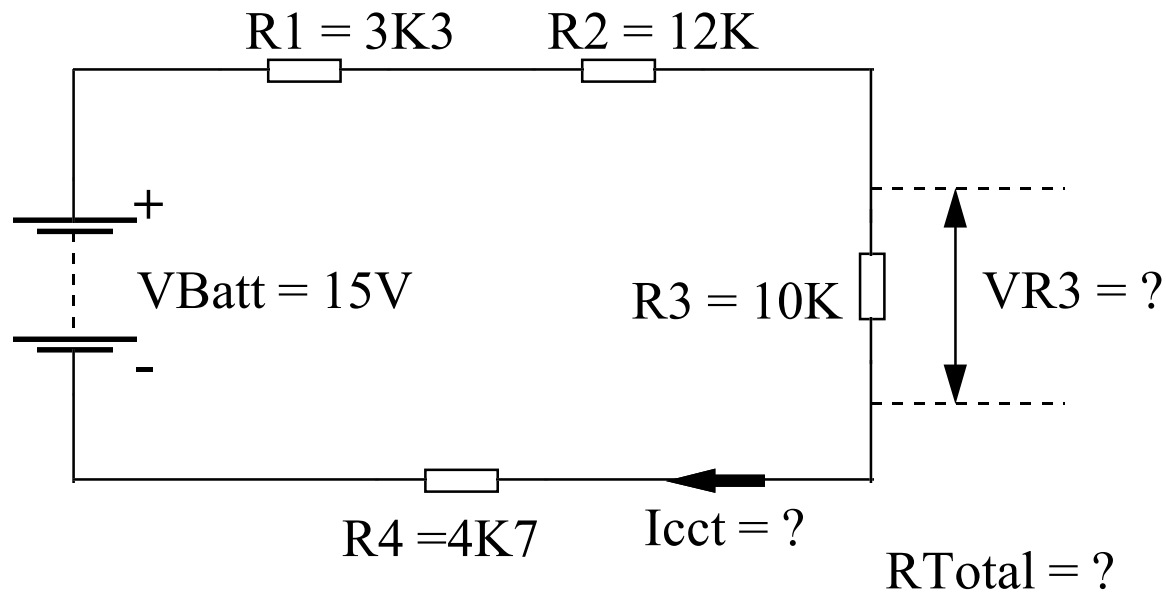
Examples

- Resistors in series $R_T = R_1 + R_2 + R_3 \dots$
- Therefore $R_T = 3K3 + 12K + 10K + 4K7 = 30K\Omega \dots (30 * 10^3) \text{ Ohms}$
- $I_{cct} = V_{Batt} / R_T$, Therefore $15/30K = 0.5\text{mA} \dots (15) / (30 * 10^3) \text{ Amps}$
- $V_{R3} = I * R_3$, Therefore $0.5\text{mA} * 10K = 5\text{V} \dots (0.5 * 10^{-3}) * (10 * 10^3) \text{ Volts}$



Resistors.

Examples

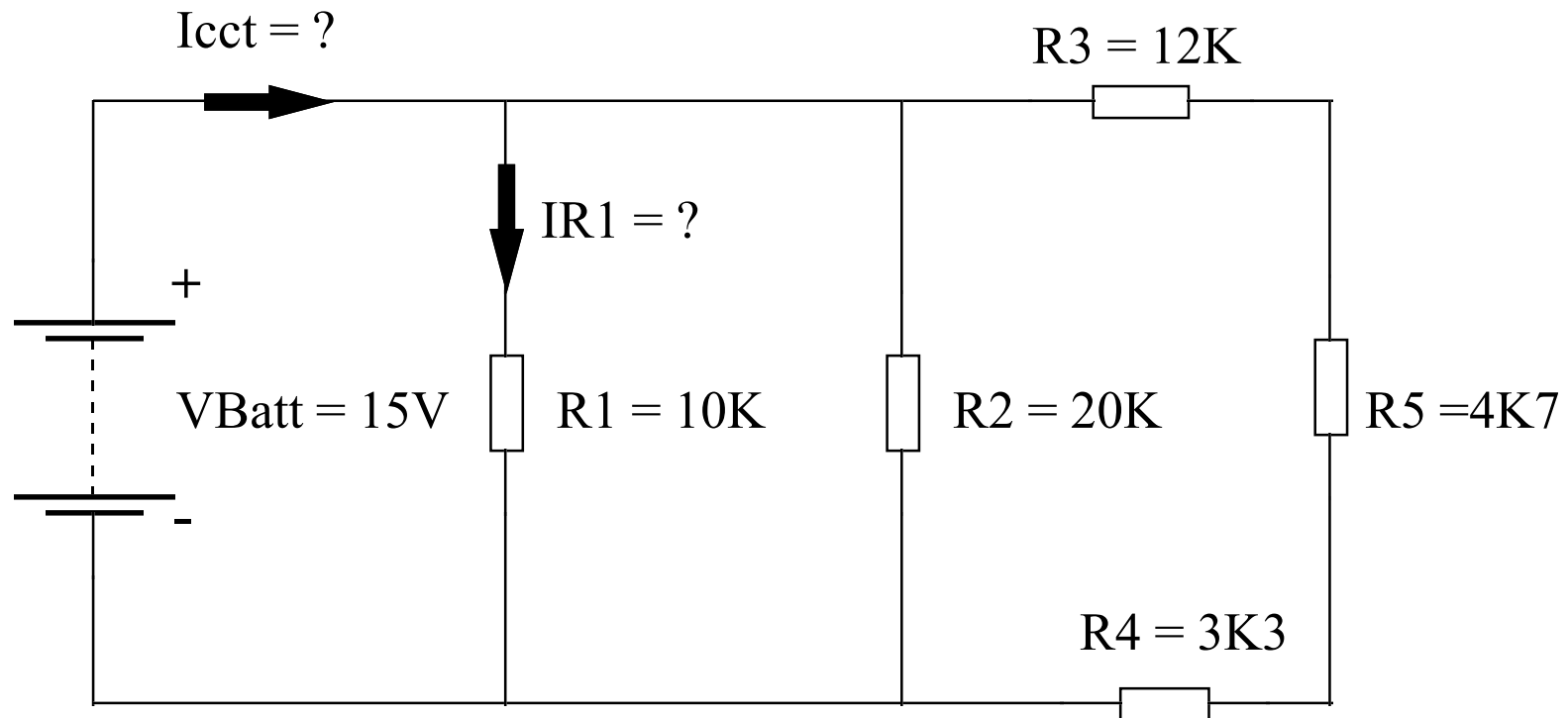


$R_{Total} = ?$

SPCA entry = (12,4.7,3.3)!20!10


Resistors.

Examples

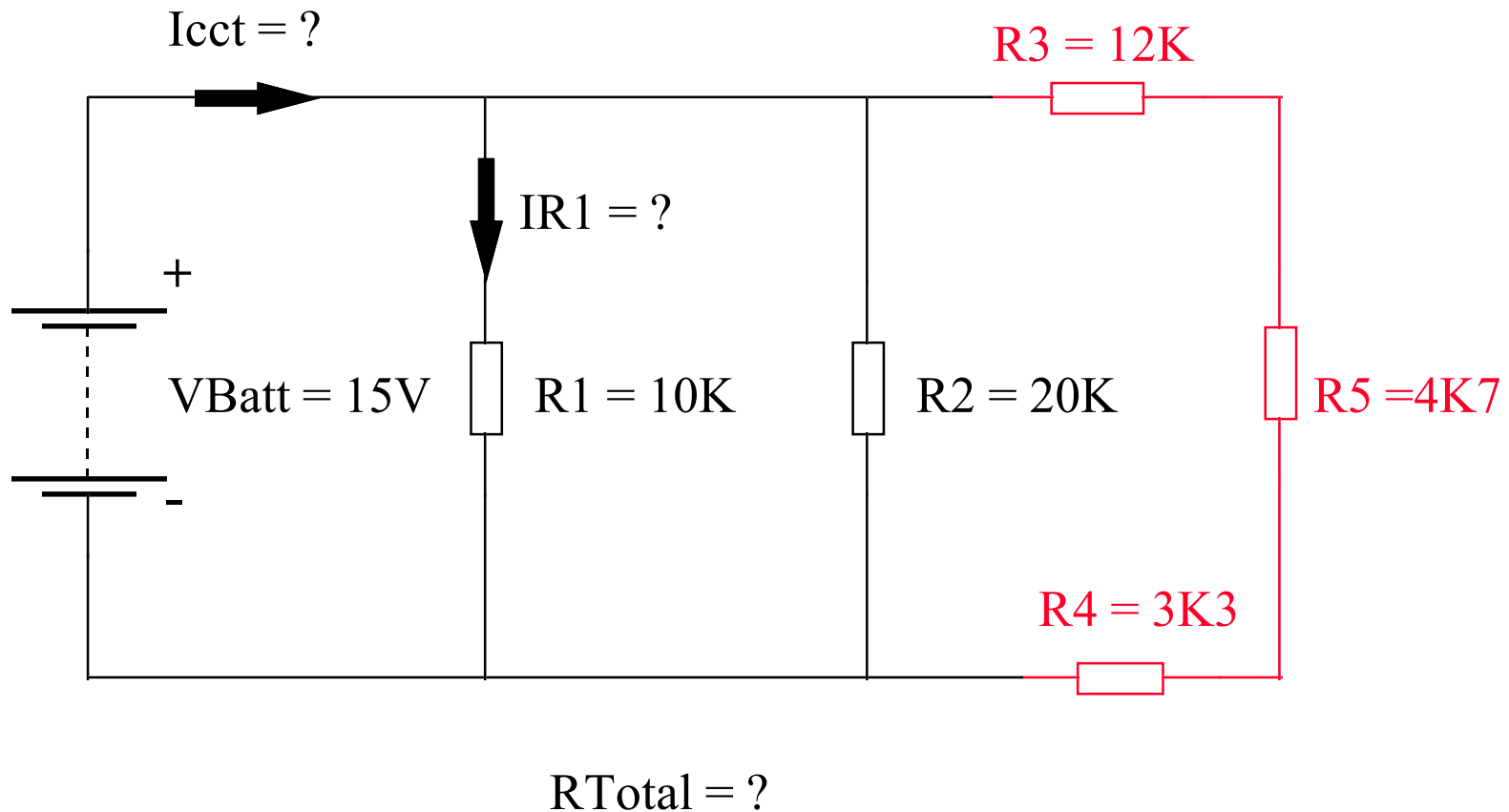

Resistors.

Examples

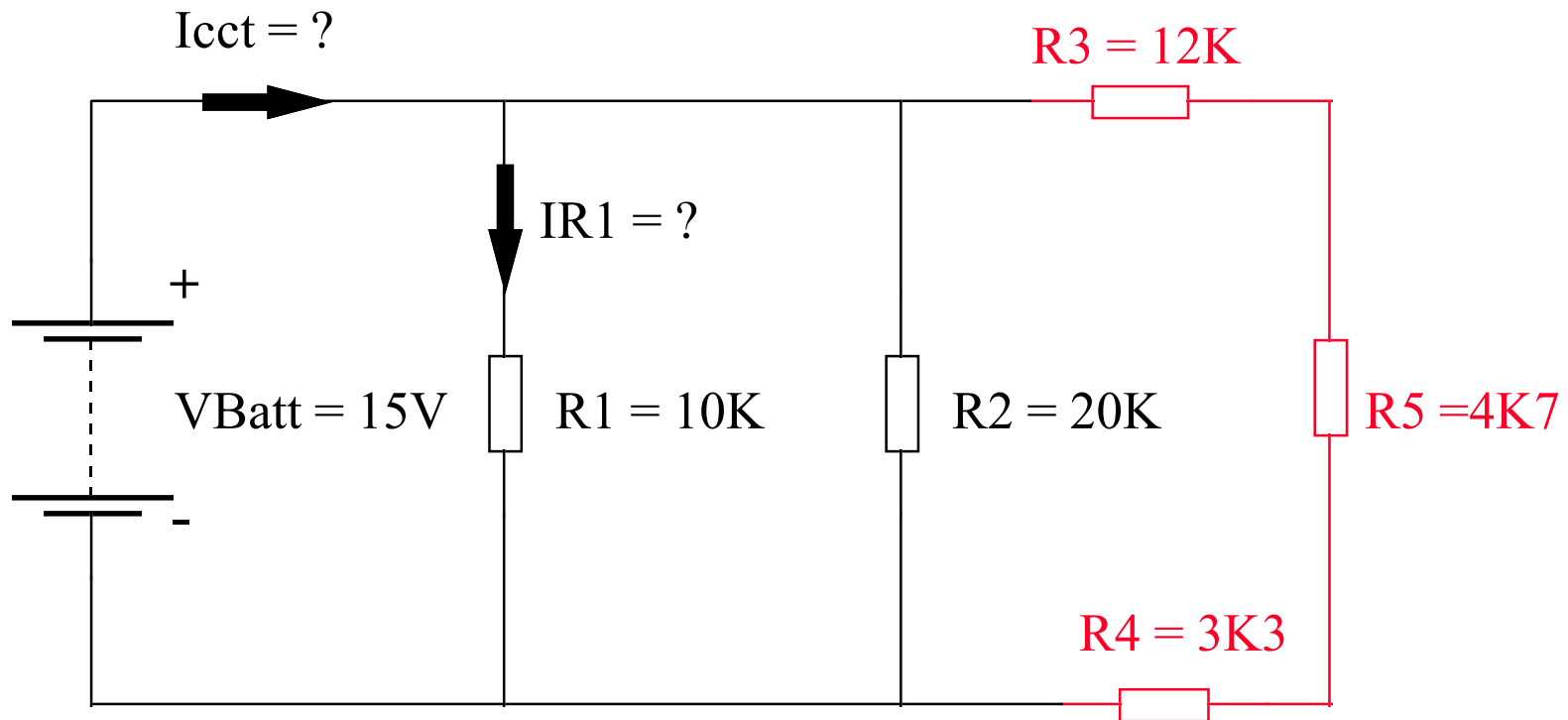


$$R_{Total} = ?$$

$$R_s = R3 + R4 + R5 = 12K + 4K7 + 3K3 = 20K \text{ Ohms}$$

Resistors.


Examples

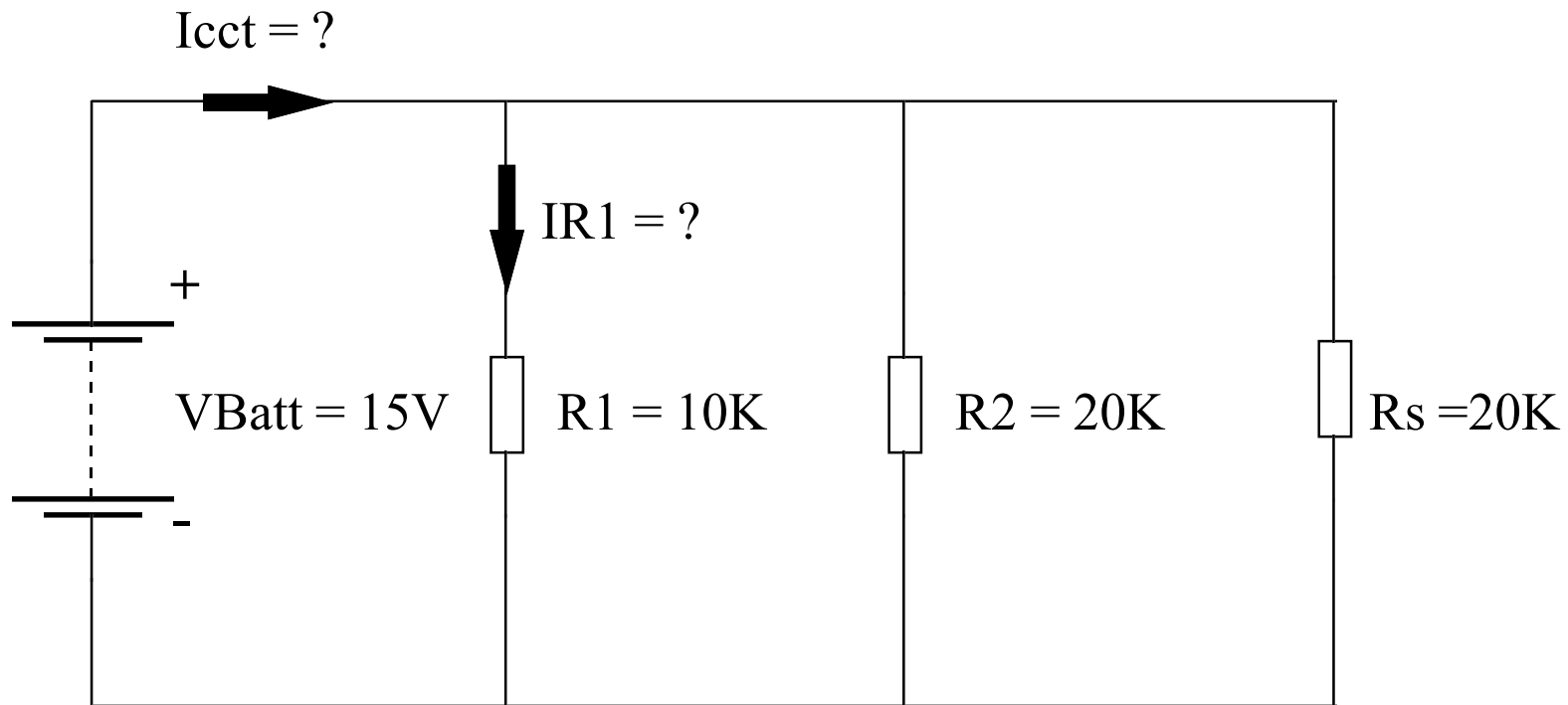

$R_{\text{Total}} = ?$

Resistors.


Examples

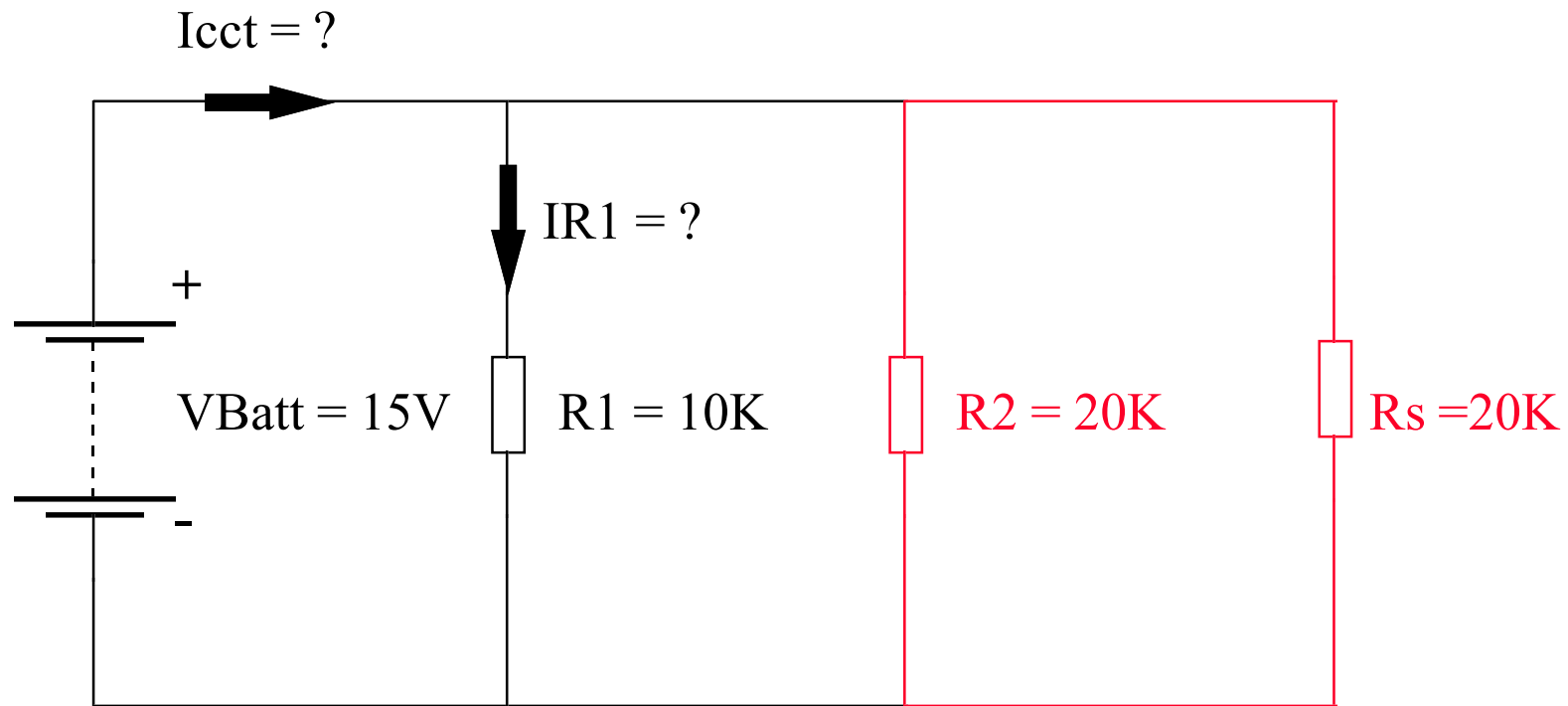

$R_{\text{Total}} = ?$

Resistors.

Examples

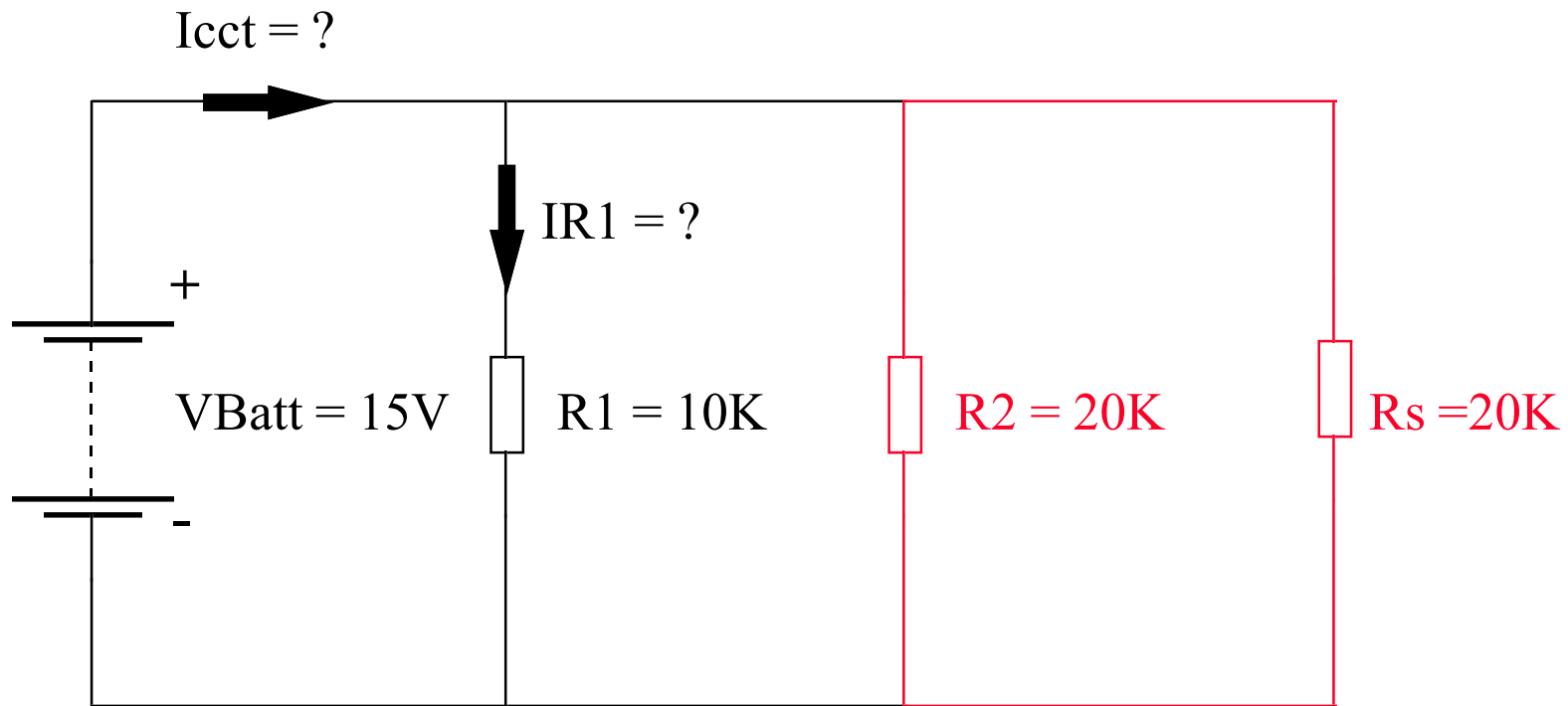


$R_{Total} = ?$

Using Product over sum rule

$$R_2 // R_s = 20K * 20K / (20K + 20K) = 400K / 40K = 10K$$

Resistors.

Examples

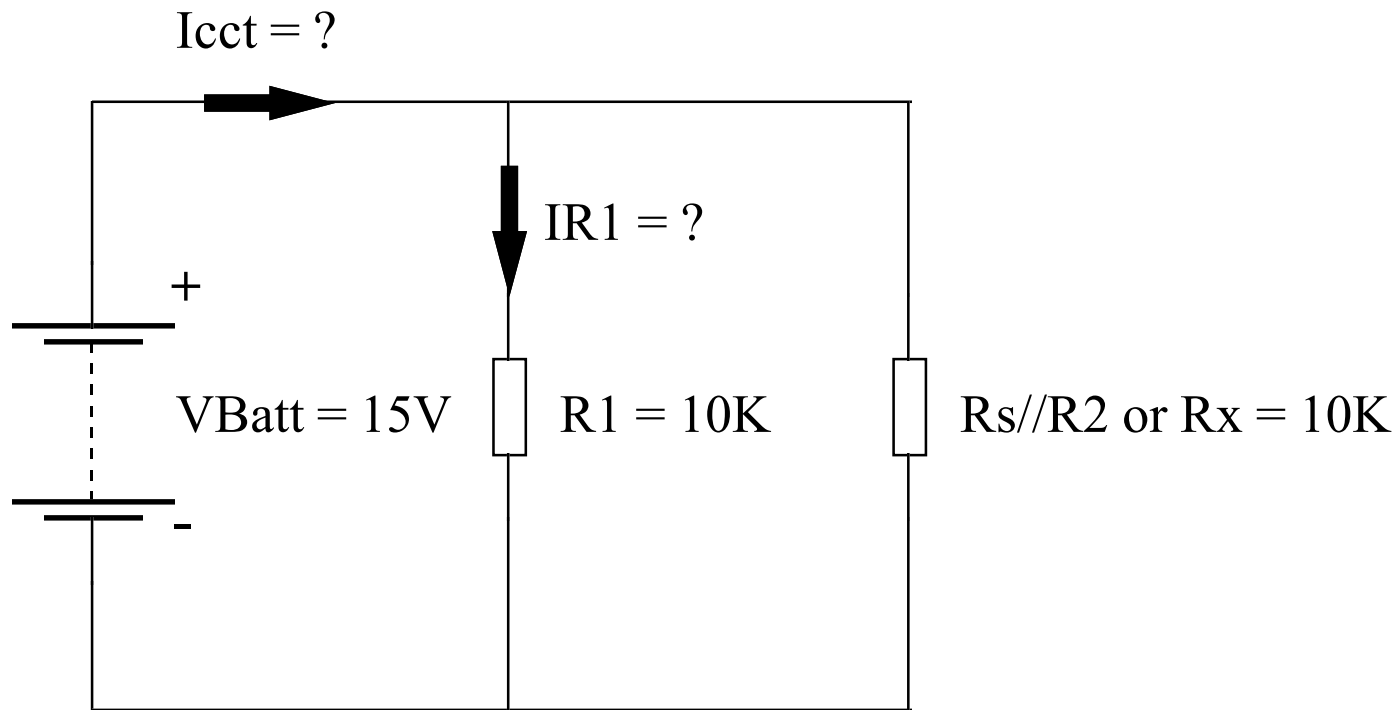


$R_{\text{Total}} = ?$

Resistors.

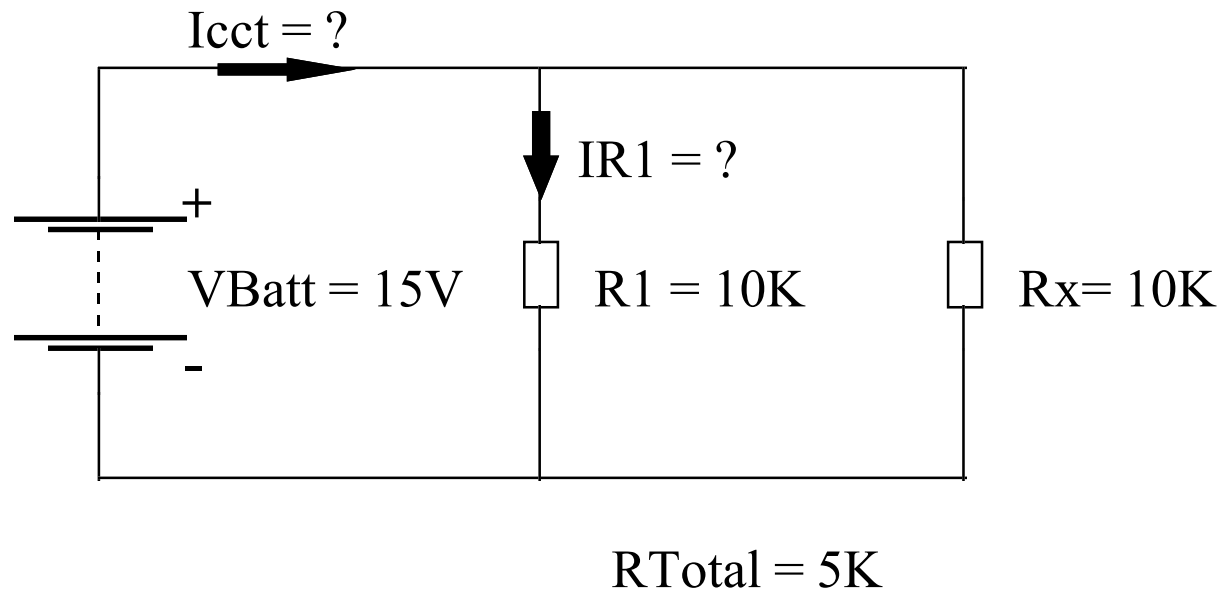Examples

- Resistors in parallel $R1//R_x = 10K * 10K / (10K + 10K) = 100K / 20K = 5K$
Again using Product over sum rule.
- Therefore $R_{Total} = 5K\Omega .. (5 * 10^3) \text{ Ohms}$
- $I_{cct} = V_{Batt} / R_{Total}$, Therefore $15/5K = 3mA .. (15) / (5 * 10^3) \text{ Amps}$
- $I_{R1} = V / R1$, Therefore $15V / 10K = 1.5mA .. (15) / (10 * 10^3) \text{ Amps}$



Resistors

Practice

Resistors.

Using Series Parallel Component Analyzer.

- This is a simple programme that will perform the analysis calculations.
- Components in series are separated by commas ie. R1,R2,R3
- Components in Parallel are separated by the Exclamation mark ie. R1!R2!R3
- Brackets may be used to force calculation order priority.

Resistors.

Using Series Parallel Component Analyzer.

- Example of usage :-
- $R1 = 1\text{K}\Omega$, $R2 = 200\Omega$ and $R3 = 500\Omega$.
- $R3$ and $R2$ in series would be entered as 500,200
- $R1$ and $R3$ in Parallel would be entered as 1000!500
- $R1$ in series $R2$ all in Parallel with $R3$ would be entered as (1000,200)!500.


Resistors.

Using Series Parallel Component Analyzer.

- Entering Numbers :-
- $1\text{K}\Omega$ could be entered as 1000 or 1E3
- Likewise $1\mu\text{F}$ could be entered as 0.000001 or 1E-6
- The “E” indicates the exponent format quite often used in computers.
- The normal mathematical representation of 1E6 would be written as $1*10^6$.

Resistors.

Without using
calculator

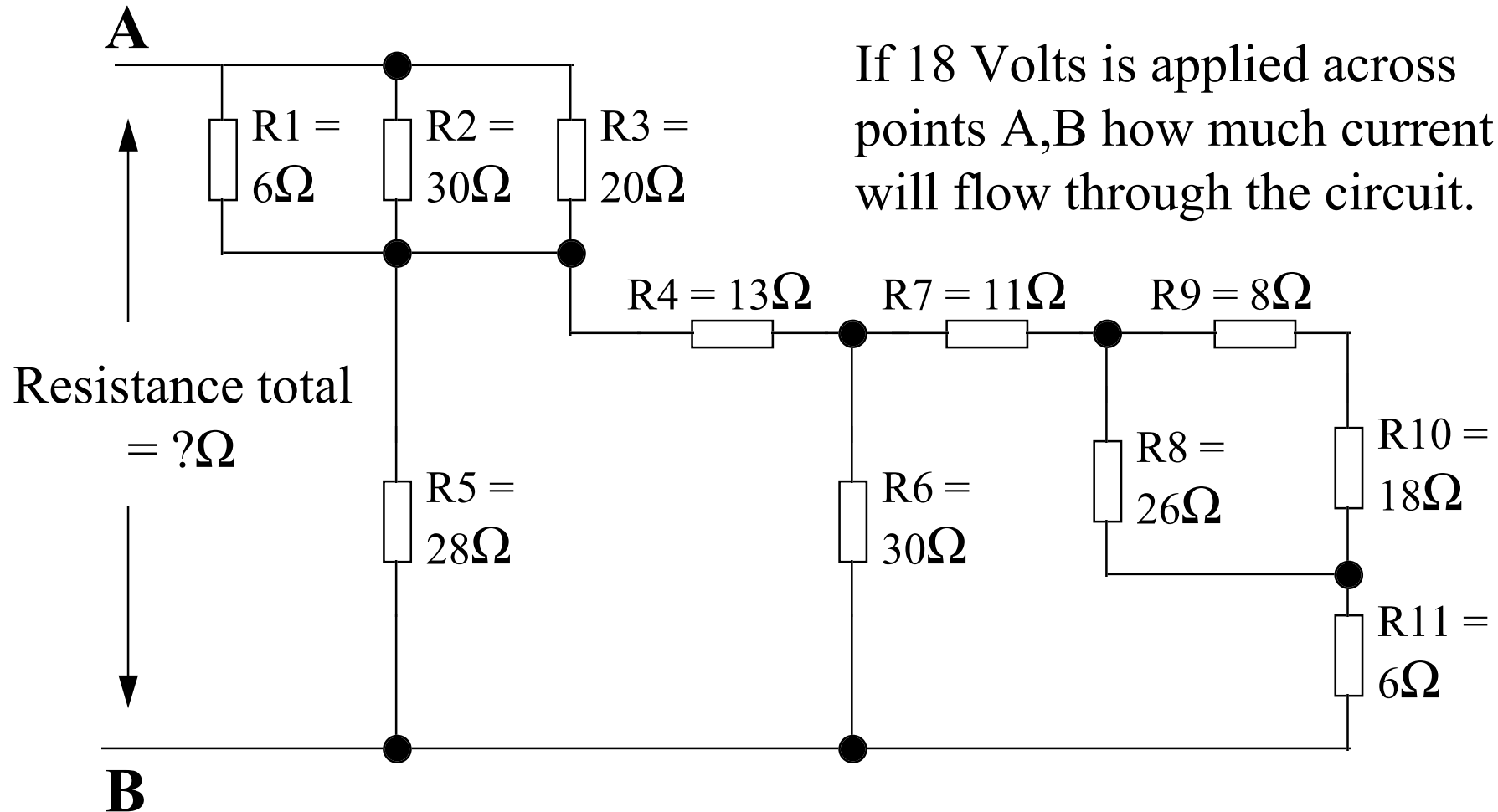


If 18 Volts is applied across points A,B how much current will flow through the circuit.

Resistance total
= $?\Omega$


$$\text{SPCA entry} = (((((8,18)!26),6,11)!30),13)!28,(6!30!20)$$

Resistors.

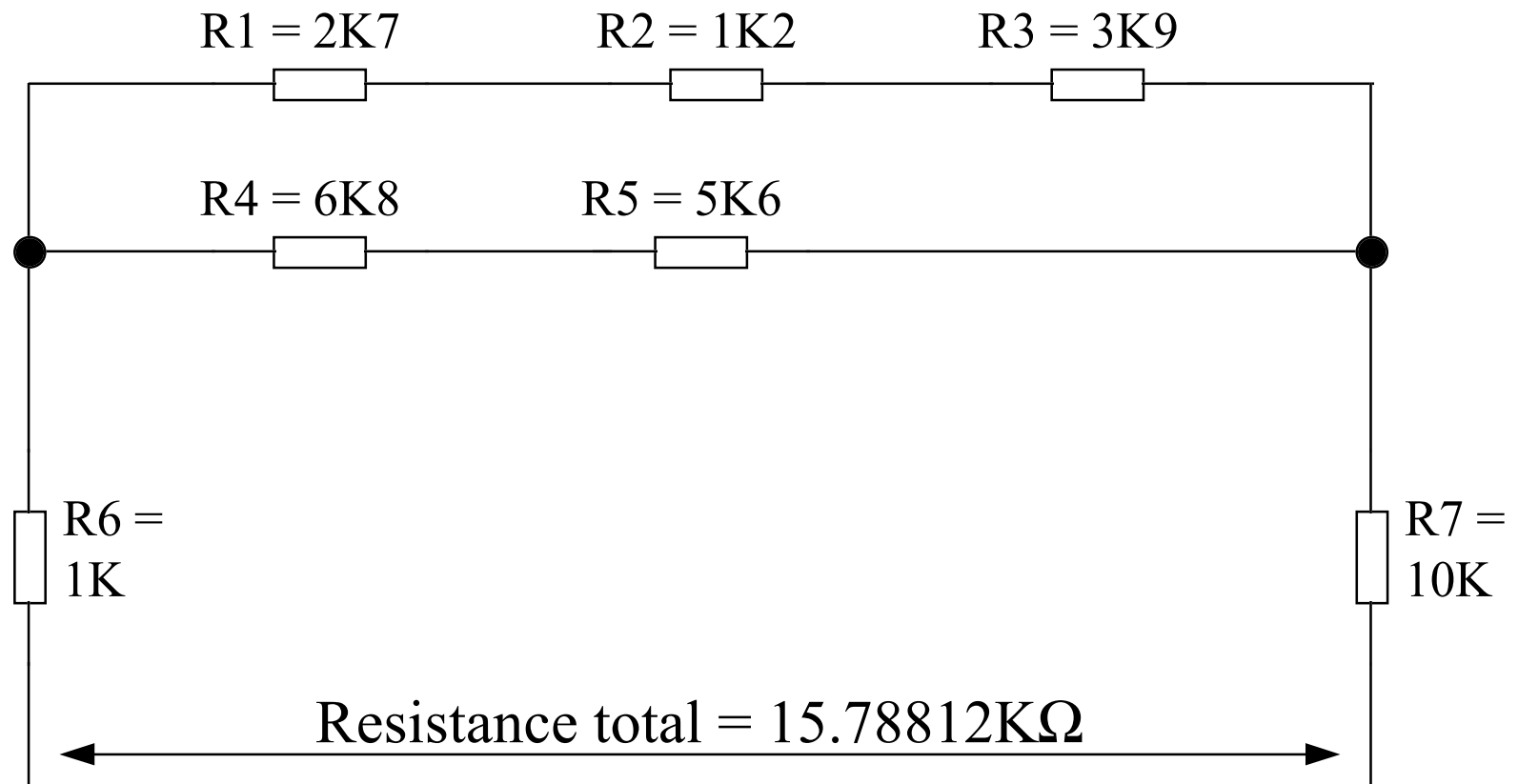


SPCA entry = $1,((2.7,1.2,3.9)!(6.8,5.6)),10$

Resistors.

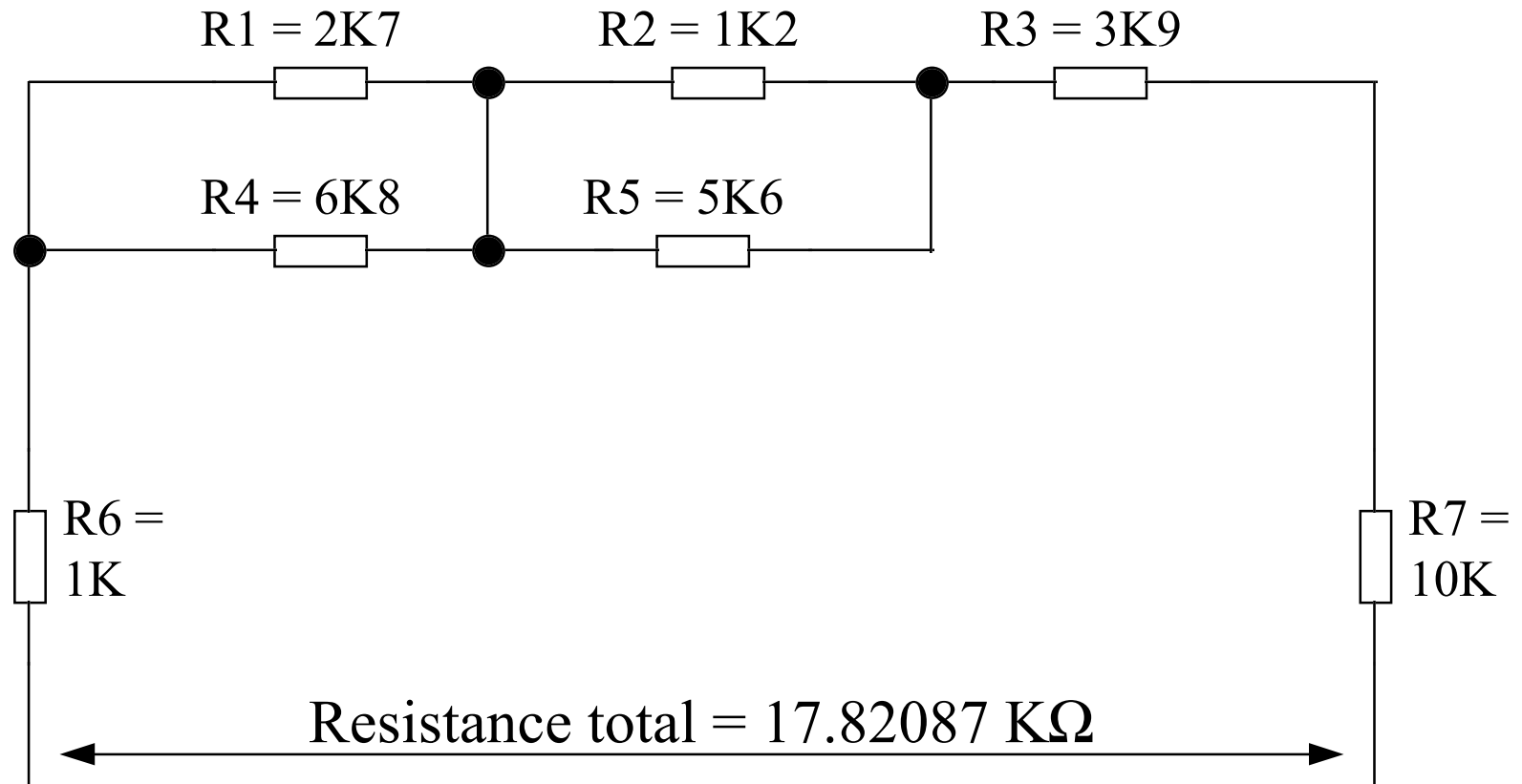

SPCA entry = 1,((2.7!6.8),(1.2!5.6)),3.9,10

Resistors.

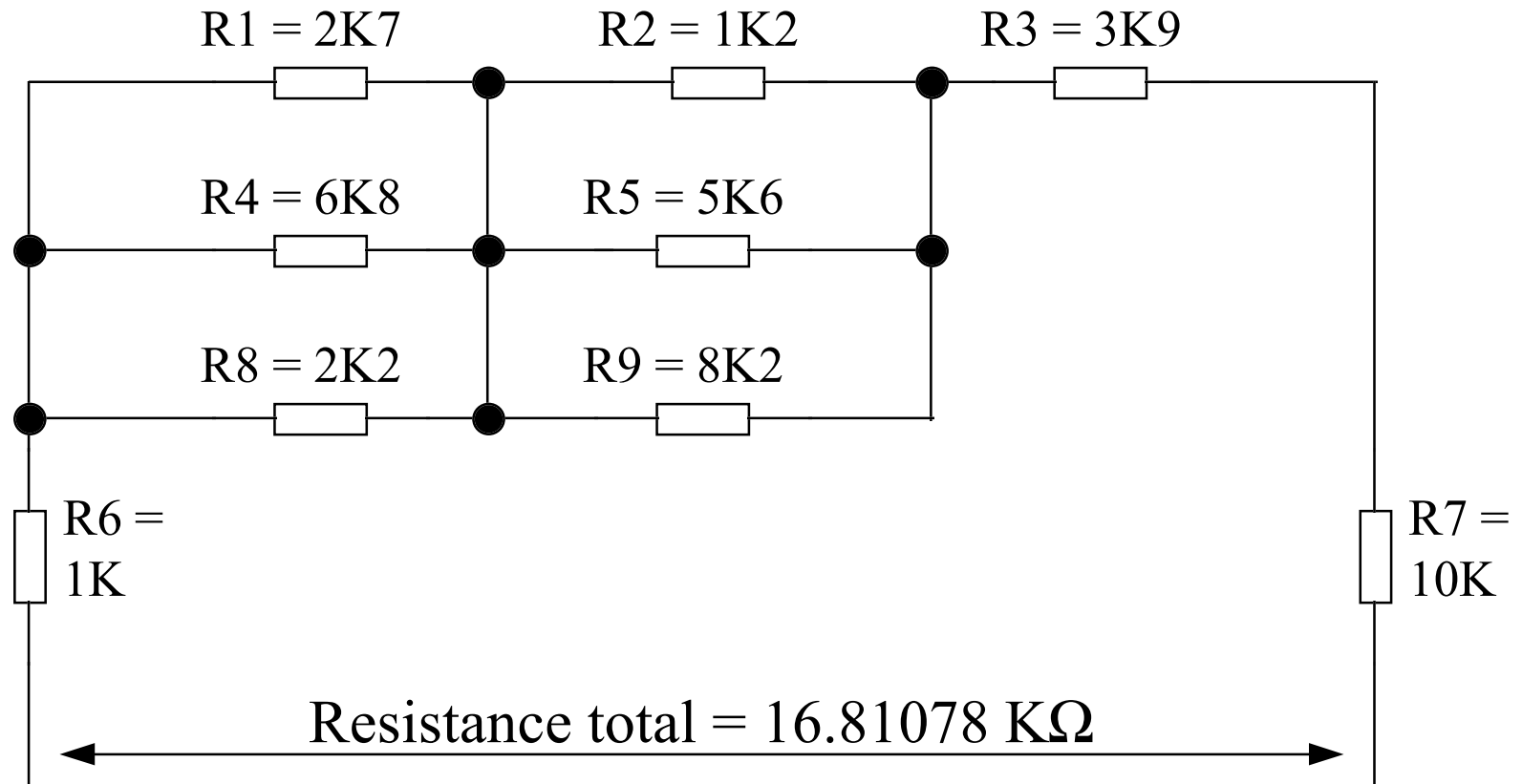


SPCA entry = 1,((2.7!6.8!2.2),(1.2!5.6!8.2)),3.9,10

Resistors

Voltage Divider


Resistors.

Voltage Dividers.

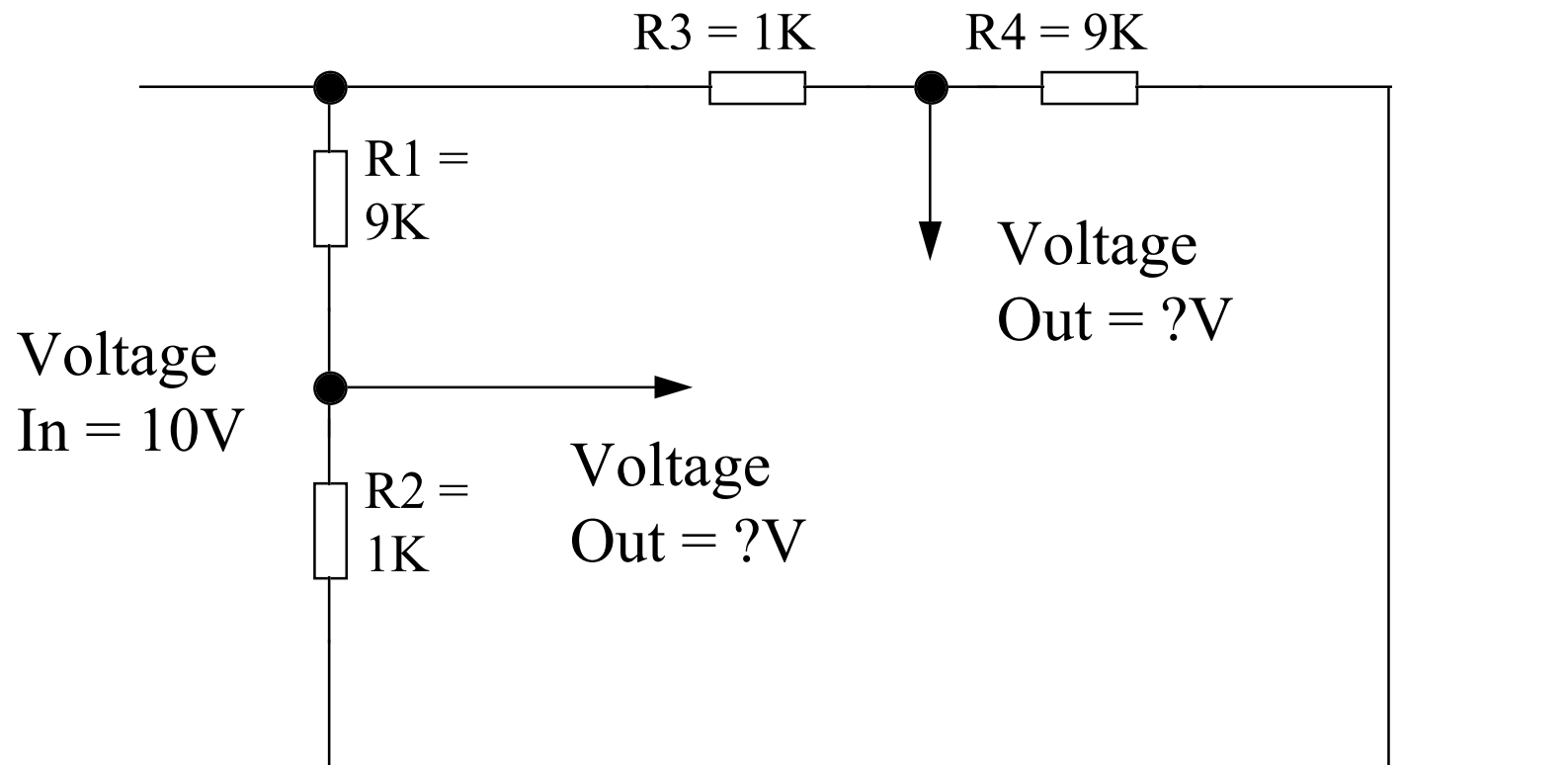


Resistors.

Voltage Dividers.

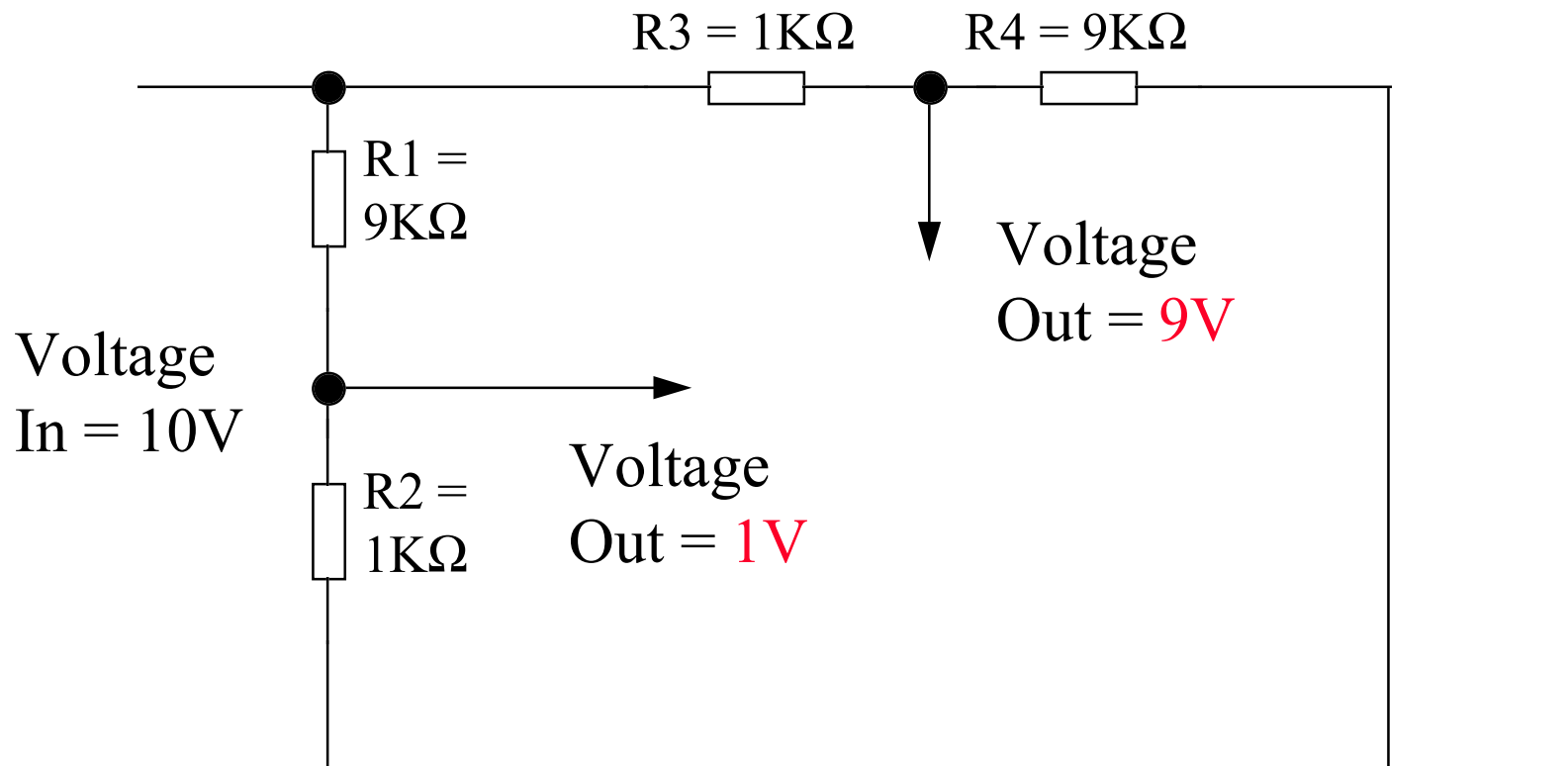

Resistors.

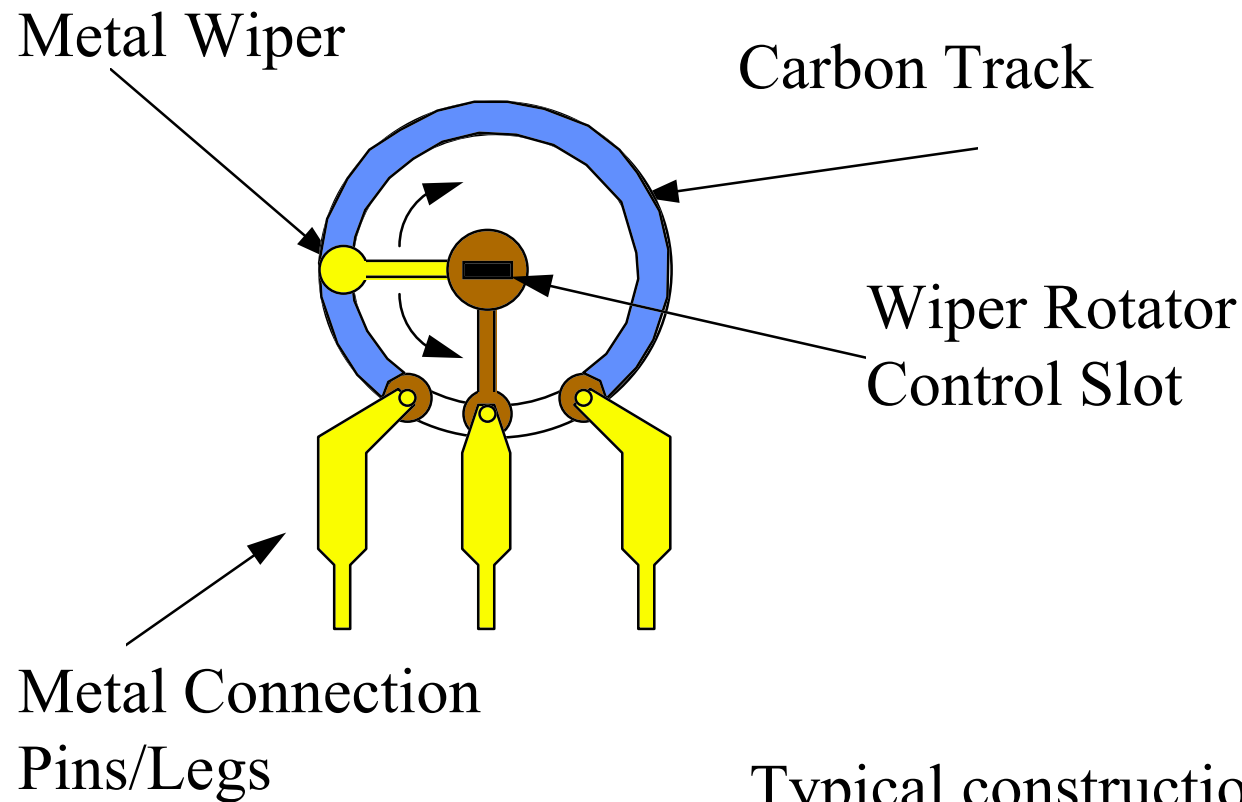


Variable Resistor or Potentiometer.



Typical construction of a
270° Potentiometer.

Resistors.


Variable Resistor or Potentiometer.

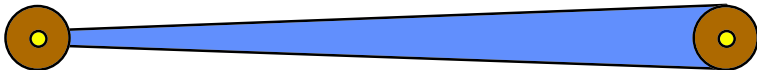- This device can be used to extract some fraction of an applied voltage.
- This device can be used to limit current.
(When it is used in this mode it is called a Rheostat.)
- The track can take one of three forms :-
 - Linear 
 - Log 
 - Anti Log 
- The device's value = The total track resistance.


Resistors.

Variable Resistor or Potentiometer and Rheostat.


Circuit symbols

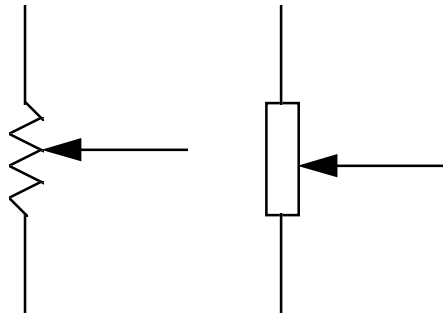

The
Potentiometer

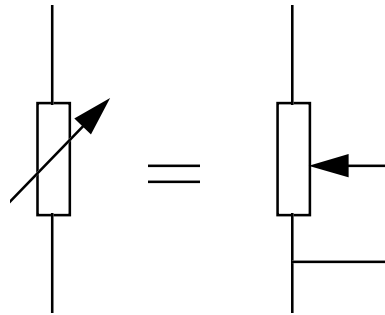

The Rheostat

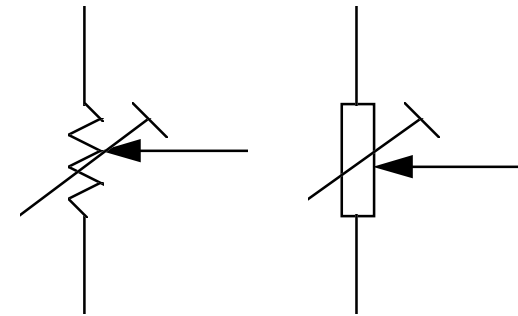

The Preset
Potentiometer



Resistors.


Variable Resistor or Potentiometer.

- When a Potentiometer has a linear track then the rotation angle of the wiper is proportional to the sample voltage.
- The Log and Anti Log tracks are used when a linear rotational angle is needed to represent a logarithmic value such as the volume control on an audio system.
- With audio a ten times increase in power will only give double the volume.

Resistors.

Variable Resistor or Potentiometer and Rheostat.

Example Calculation

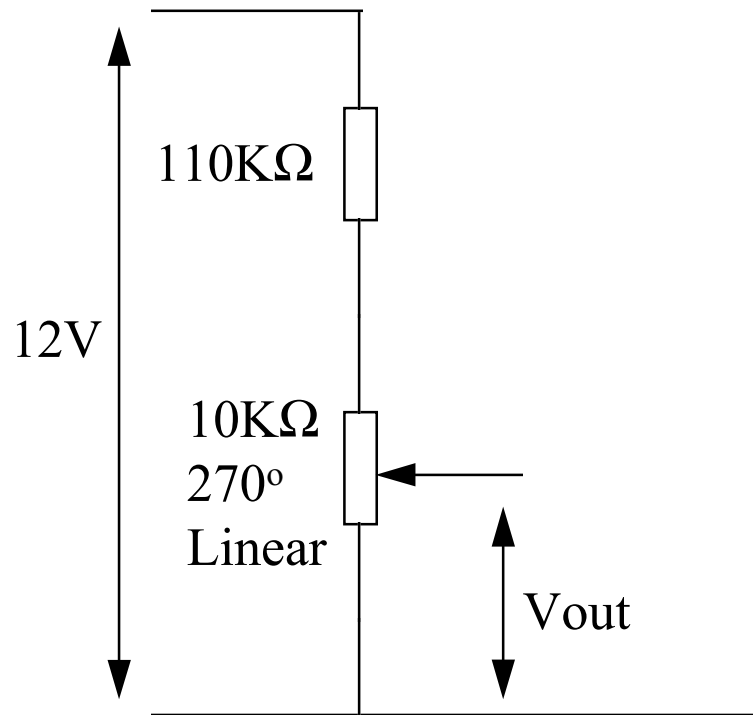

Q1. What is the voltage V_{out} when rotation angle is 10° .

Total circuit resistance = $120K\Omega$.

Current = $12V / 120K = 100\mu A$.


Voltage across Potentiometer = $I * R = 100\mu A * 10K\Omega = 1V$.

$V_{out} = 10/270 * 1V \cong 0.037V$
or 37mV.

Resistors.

Variable Resistor or Potentiometer and Rheostat.

Calculation Practice

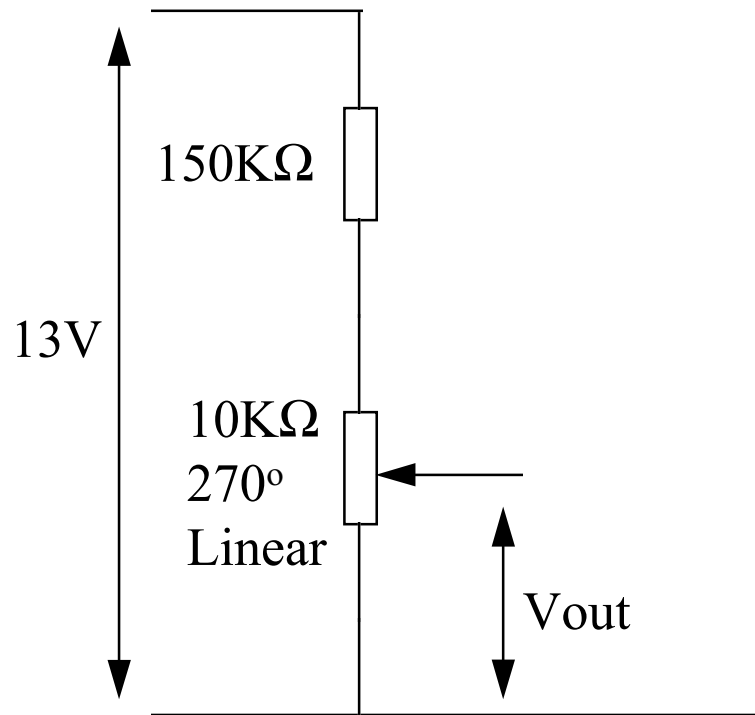

Q2. What is the voltage “V_{out}” when rotation angle is stepped in 5° units across the whole range of the potentiometer.

Suggest a suitable and convenient method of resolving this calculation problem.


Resistors

More Example

Calculations


Resistors.

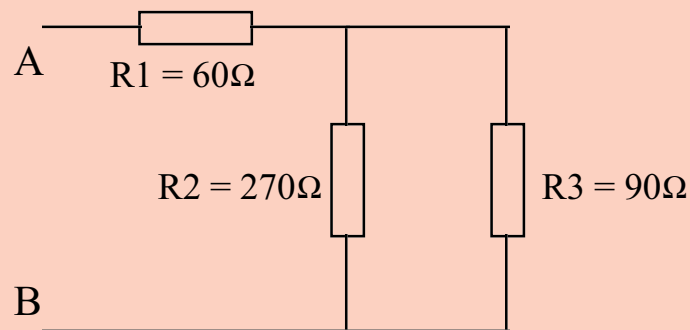- Example:-
- The circuit below has 30 volts across points AB.
- What current will flow in R1?
- How much power is dissipated in R2?




Resistors.

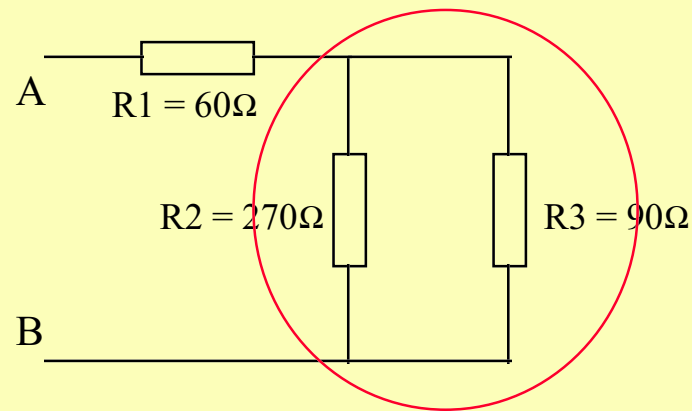- Step 1 Simplify (Convert into 2 series resistors):-
- $1/R_{Tp} = 1/R_2 + 1/R_3 = 1/270 + 1/90 = (1 + 3)/270$
- $R_{Tp} = 270/4\Omega$.





Resistors.

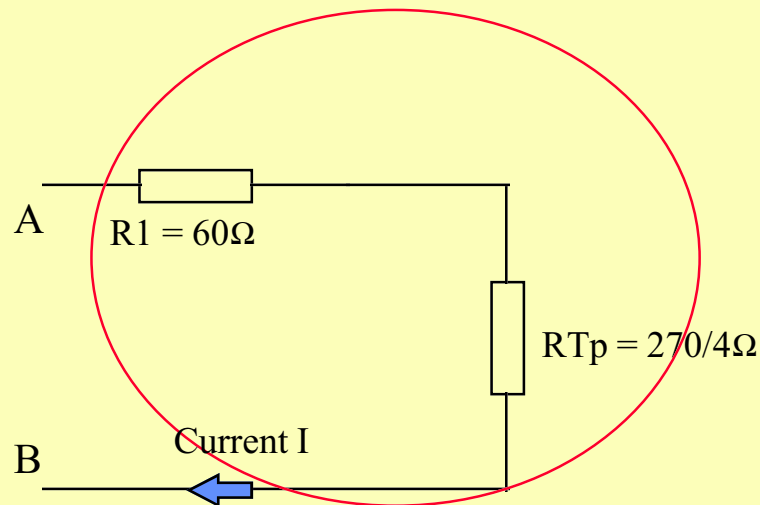- Step 2 Simplify (Convert to single resistors):-
- $R_{Ts} = R_1 + R_{Tp} = 60 + 270/4 = (240+270)/4$
- $R_{Ts} = 510/4\Omega$.




Resistors.

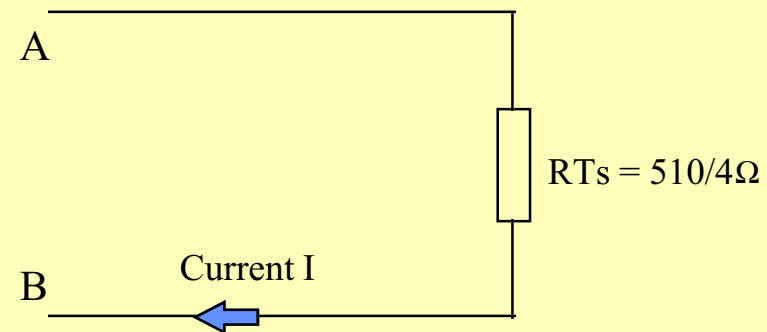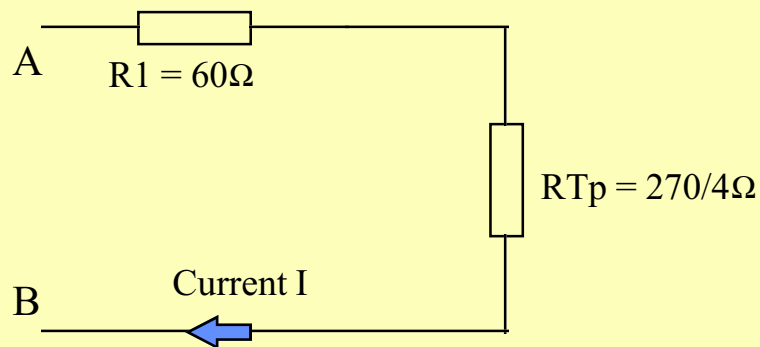- Step 3 Calculate Current in circuit:-
- $I = V/RT_s = 30/(510/4) = 30*4/510 = 120/510$
- $I = 0.235A$ which also the current that flows through R1.




Resistors.

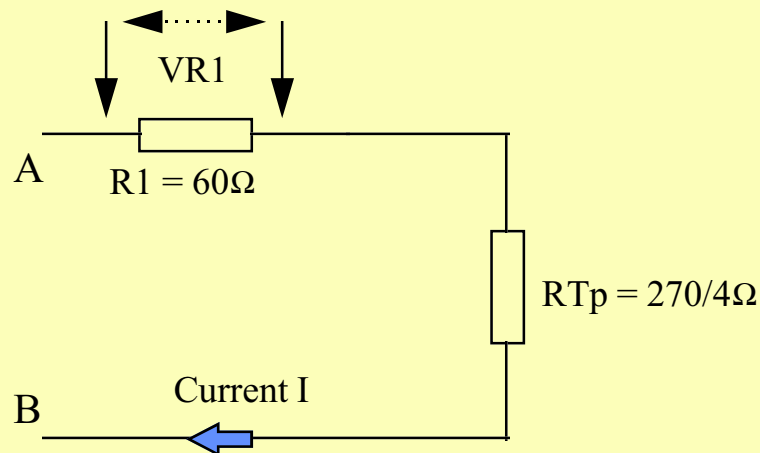- Step 4 Calculate Voltage across Resistor R1:-
- $V = I * R1 = 0.235 * 60 = 14.1 \text{ Volts}$
- Voltage across Parallel Resistor section is the Applied voltage - $VR1 = 30V - 14.1V = 15.9V$




Resistors.

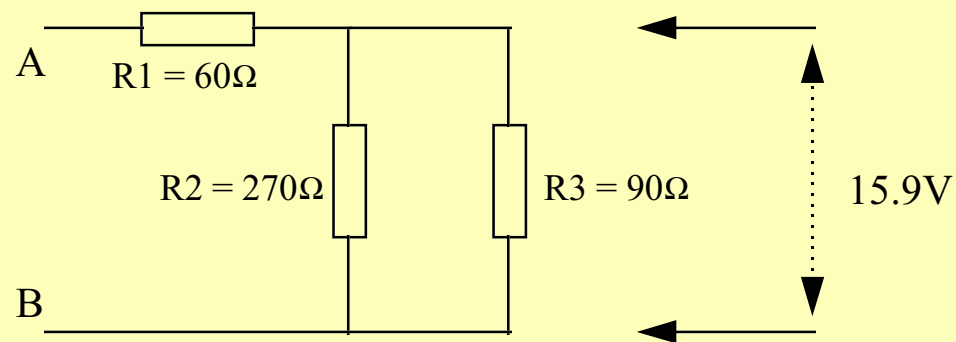- Step 5 Calculate power in R2:-
- Voltage across Parallel section = 15.9V
- Power = $V \cdot A$ or V^2/R or $I^2 \cdot R$.
- Hence Power in R2 =
 $(15.9 \cdot 15.9)/270 = 0.936 \text{ Watts}$




Resistors.

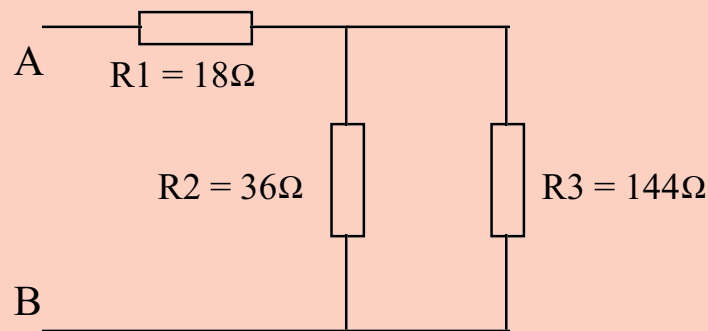- Example:-
- The circuit below has 25 volts across points AB.
- What current will flow in R1?
- How much power is dissipated in R2?




Resistors.

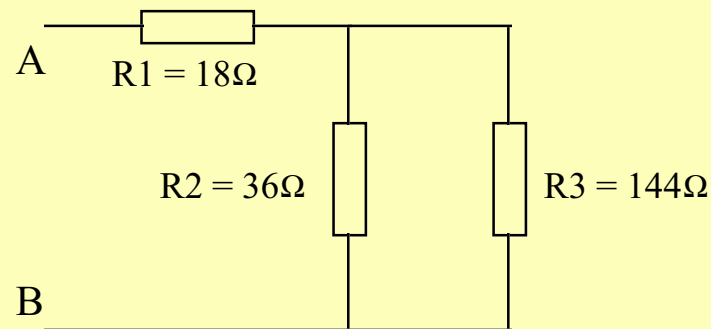- Example:-
- The circuit below has 25 volts across points AB.
- What current will flow in R1?
 - Answer = 0.534 Amps
- How much power is dissipated in R2?
 - Answer = 6.57 Watts




Resistors.

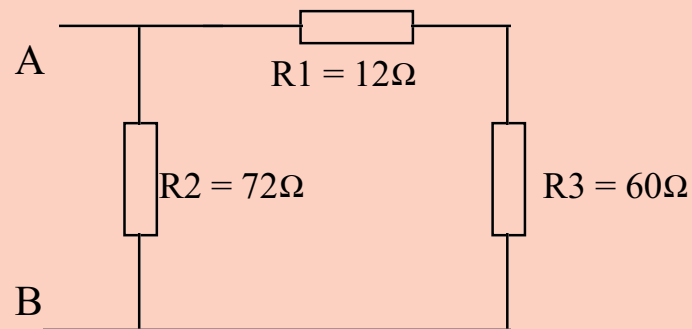- Example:-
- The circuit below has 12 volts across points AB.
- What current will flow in R3?
- How much power is dissipated in R2?
- How much power is dissipated in whole circuit?



Resistors.

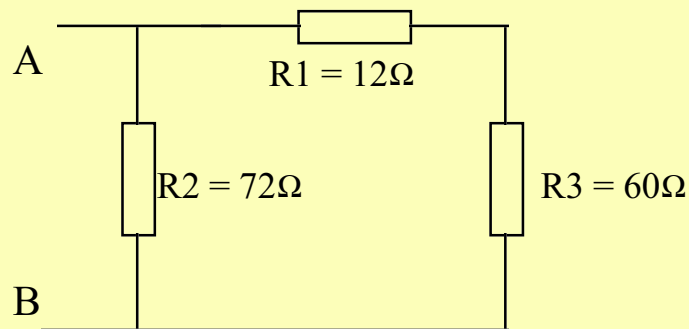- Example:-
- The circuit below has 12 volts across points AB.
- What current will flow in R3?
 - Answer 1/6 Amp
- How much power is dissipated in R2?
 - Answer 1/3 Watt
- How much power is dissipated in whole circuit?
 - Answer 4 Watts




Resistors

**Identifying
Current flow**

Example 1.

Resistors.

Current Flow
Indicator 

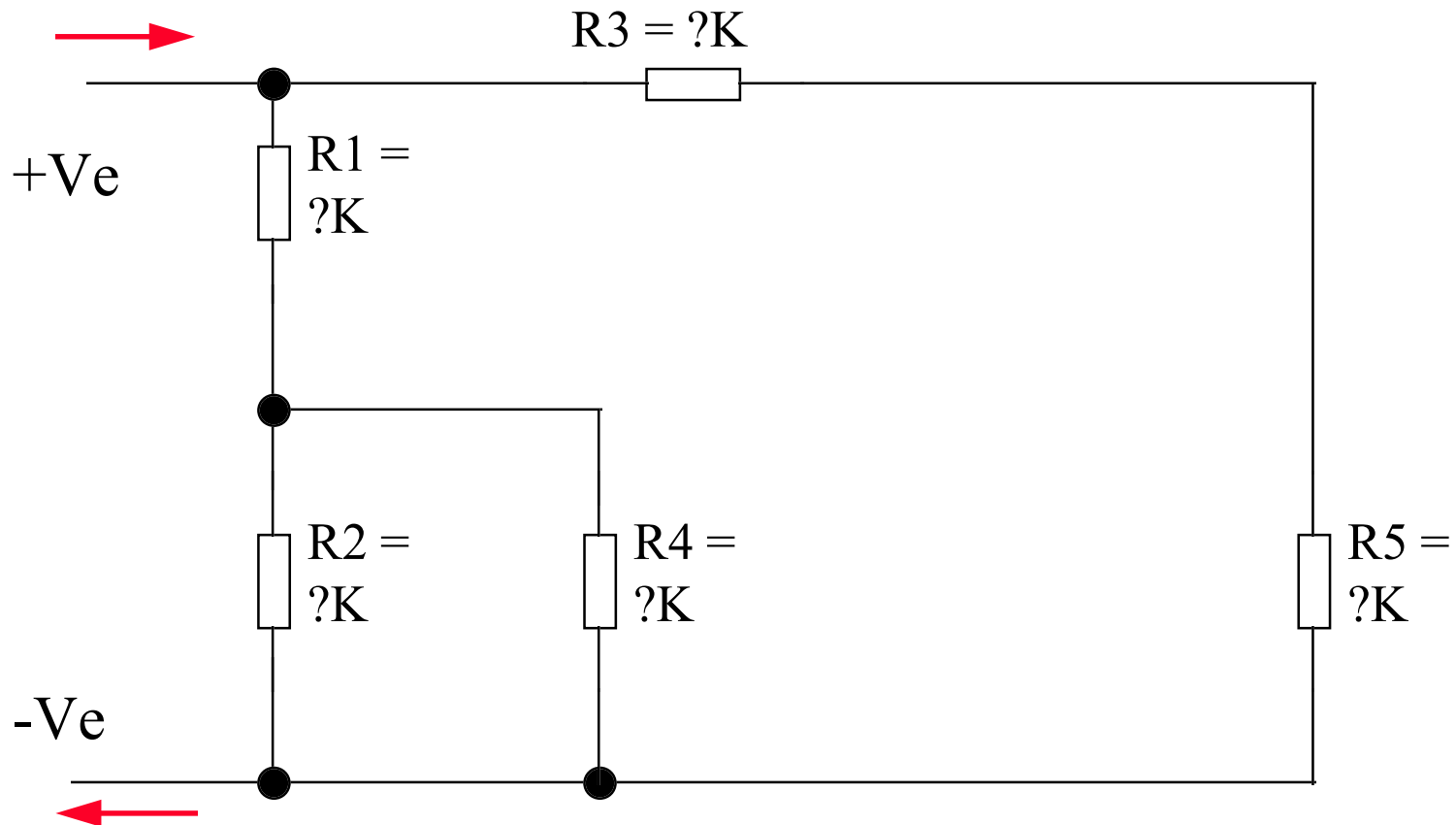


Identify Current Flow Direction in above circuit.

Example 1.

Resistors.

Current Flow
Indicator 

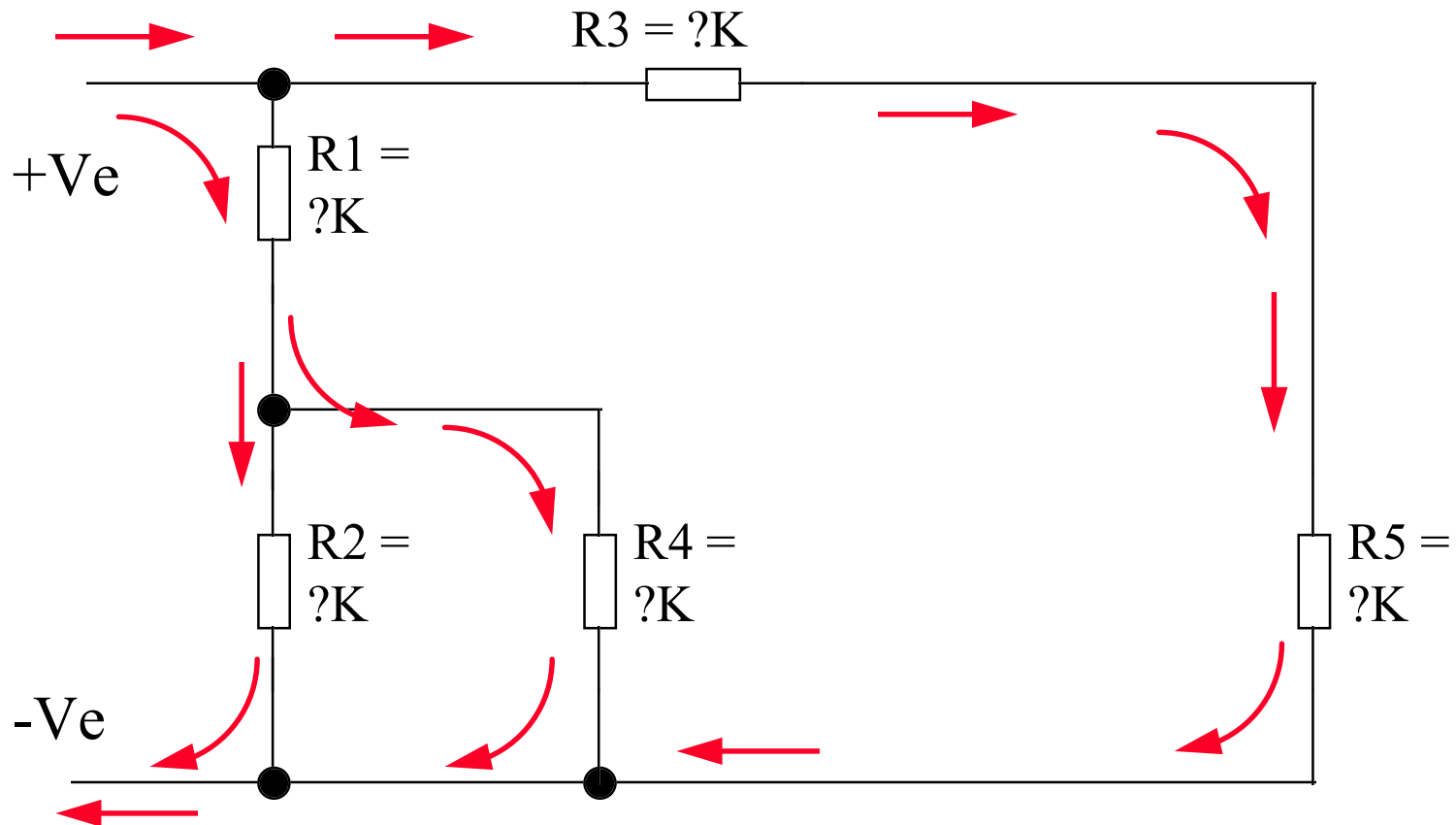


Identify Current Flow Direction in above circuit.

Example 1.

Resistors.

Current Flow
Indicator 

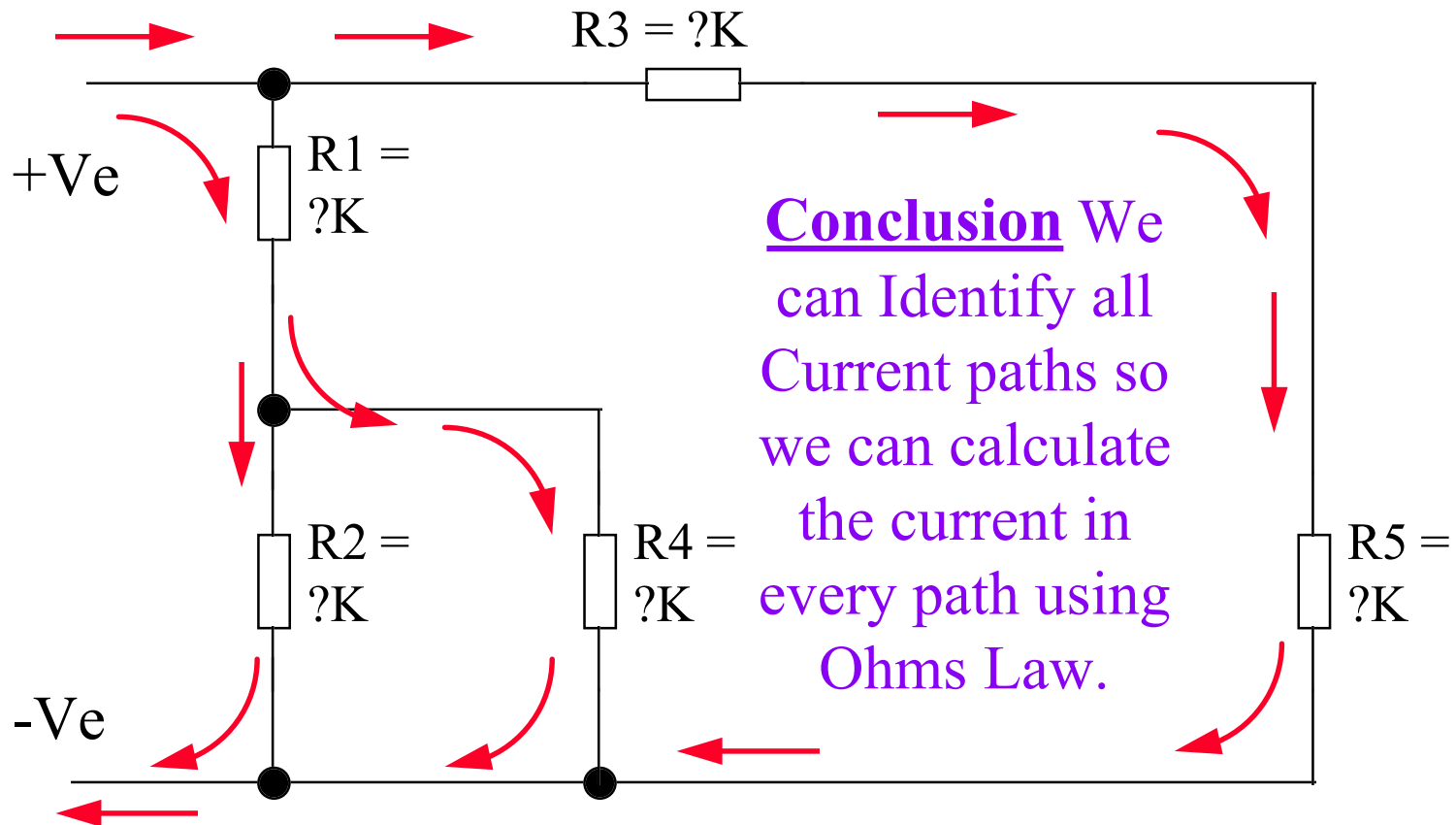


Identify Current Flow Direction in above circuit.

Example 2.

Resistors.

Current Flow
Indicator 

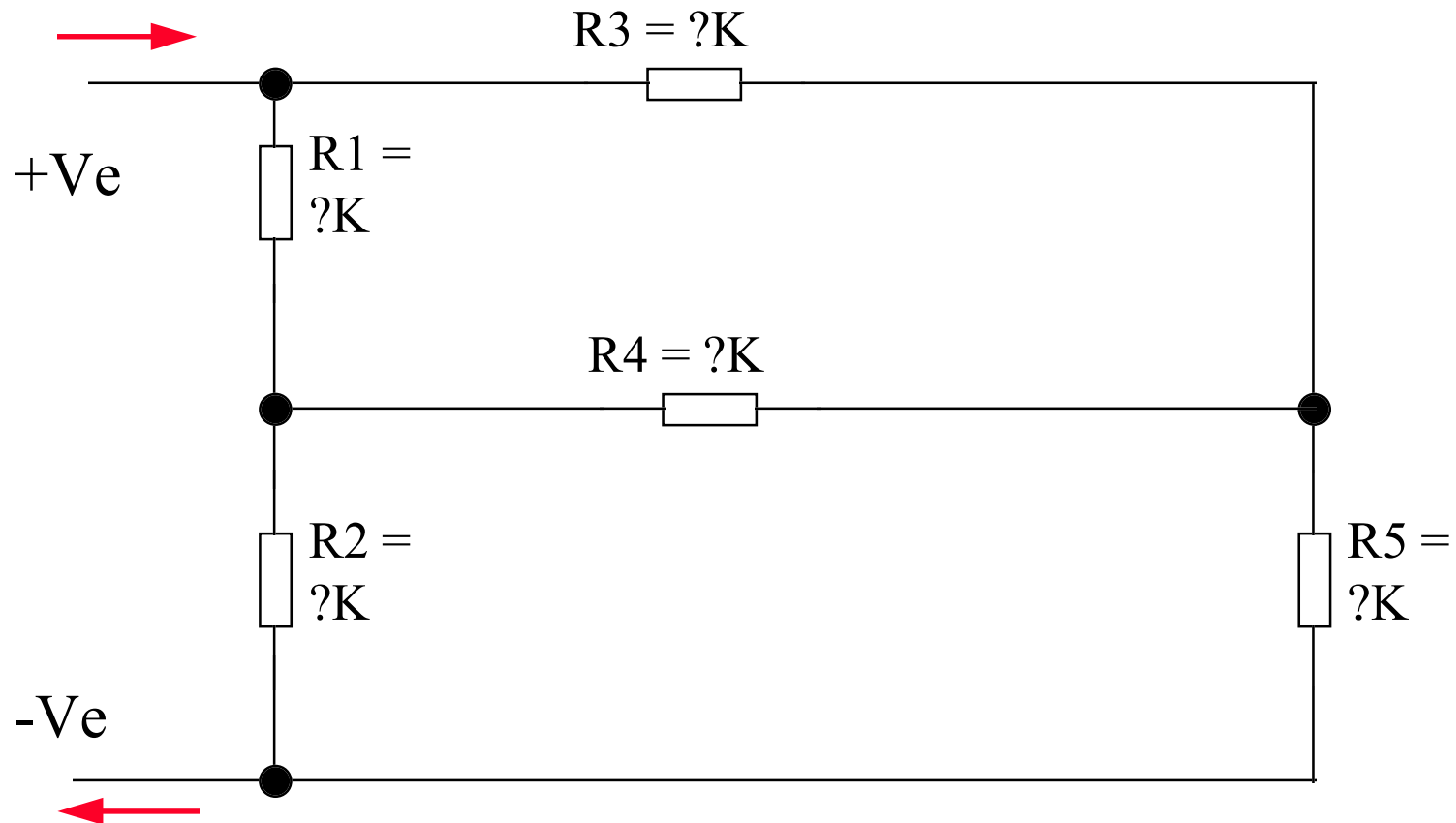


Identify Current Flow Direction in above circuit.

Example 2.

Resistors.

Current Flow
Indicator 

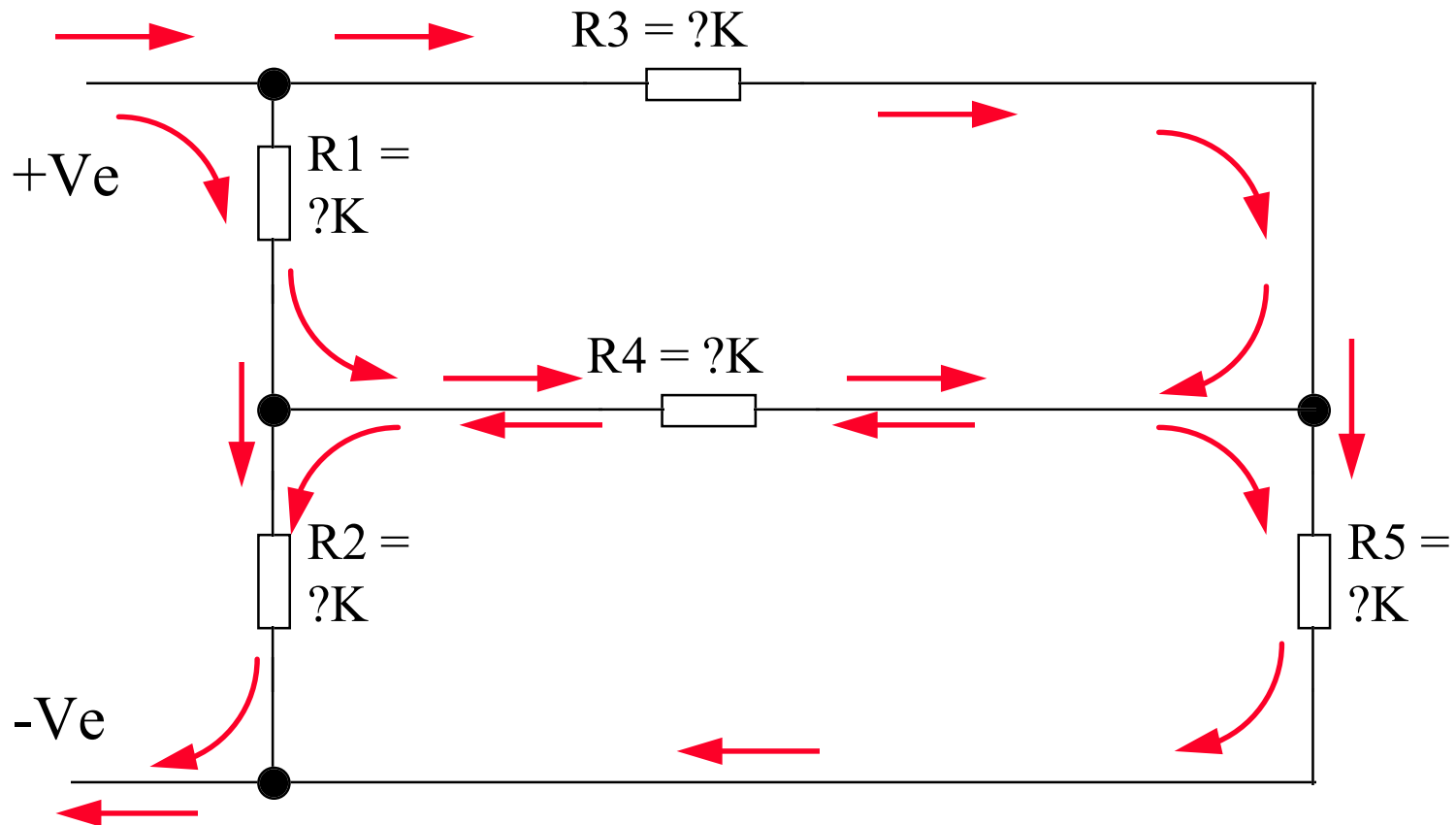


Identify Current Flow Direction in above circuit.

Example 2.

Resistors.

Current Flow
Indicator 

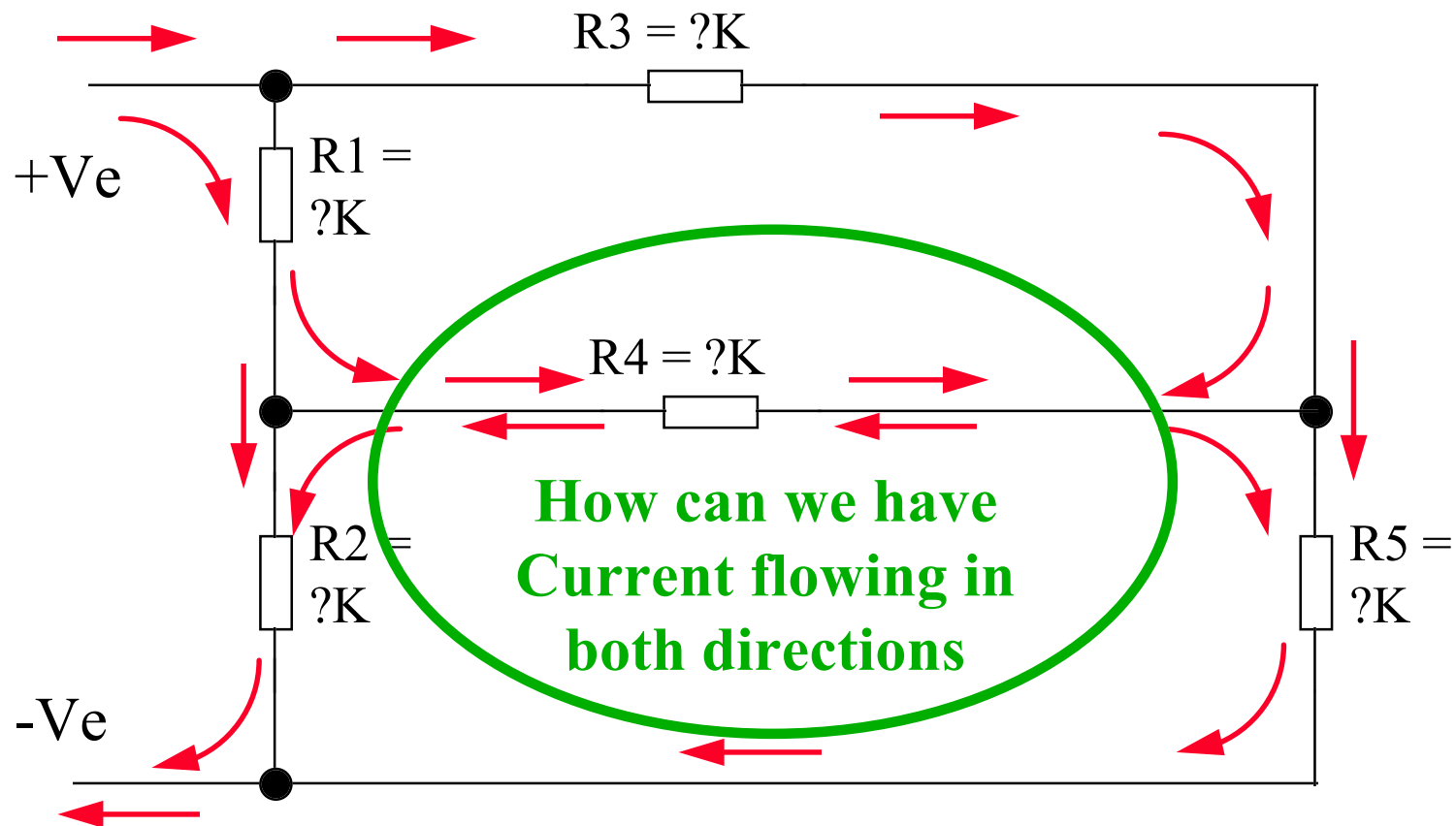


Identify Current Flow Direction in above circuit.

Example 2.

Resistors.


Current Flow
Indicator 

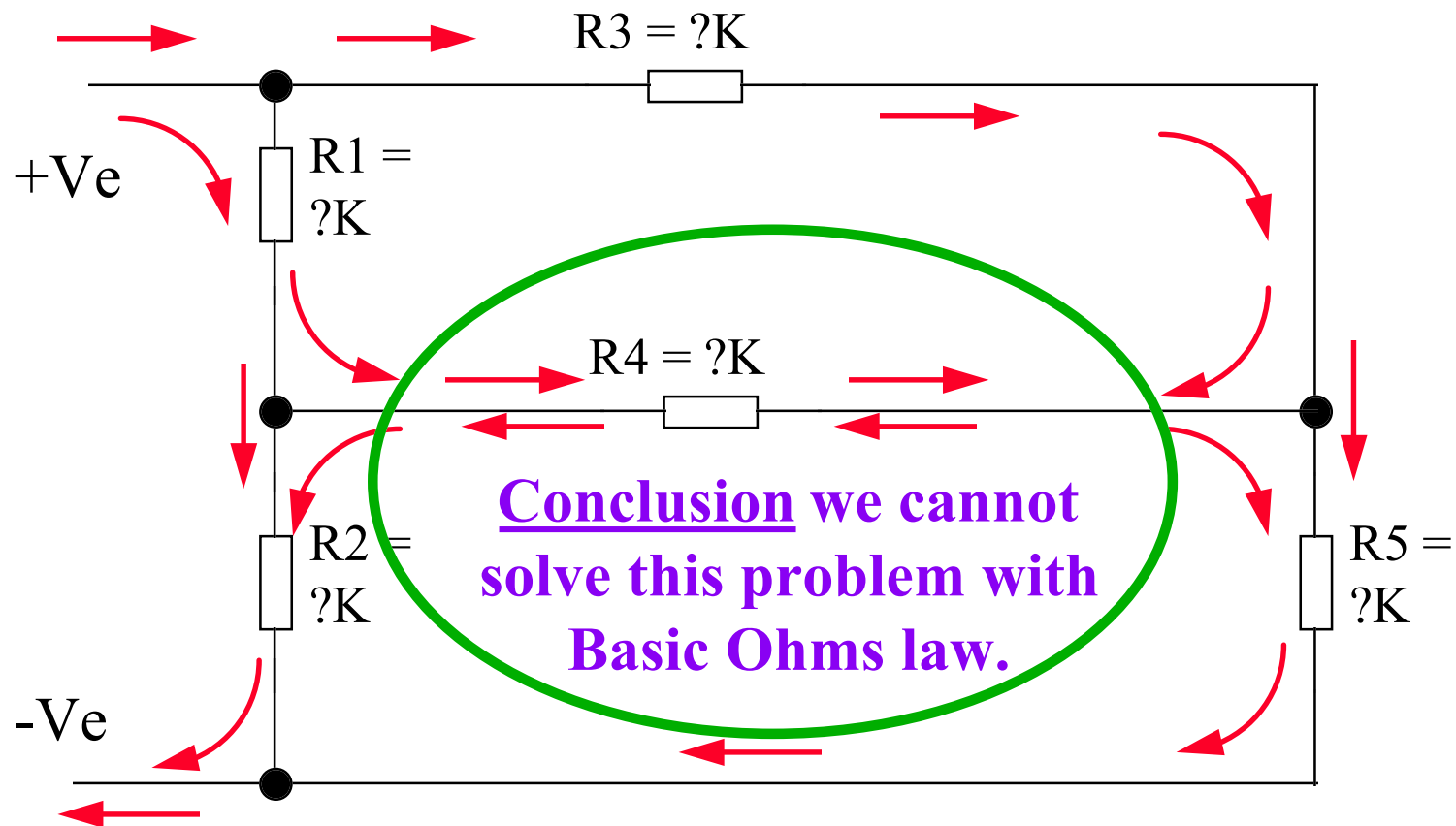


Identify Current Flow Direction in above circuit.

Cells and Batteries


Cells and Batteries.

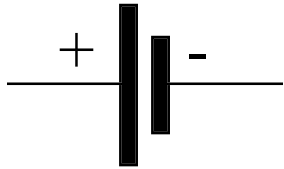

The Basic Cell.

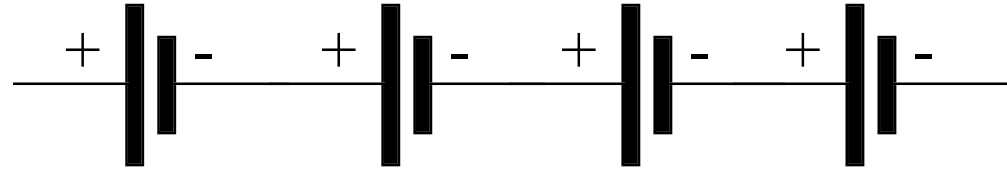

Cells connected in series.


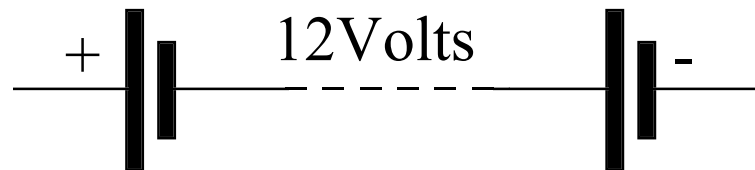


A Battery or a set of Cells connected in series.

Note. Voltage across a Battery is the sum of the Voltages of all the Cell in the battery.


Cells and Batteries.

If the voltage of each cell is 1.5 volts

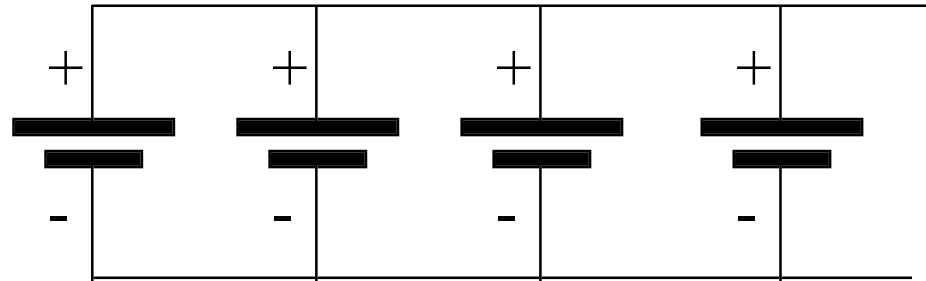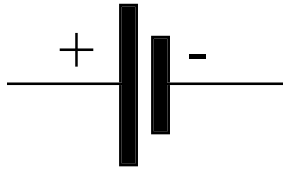

The Basic Cell.

Cells connected in parallel.

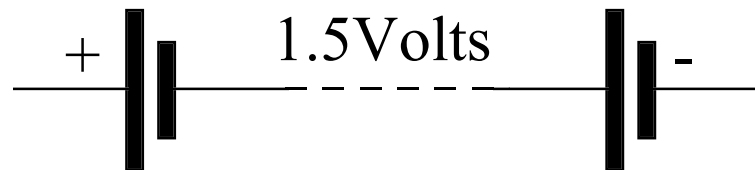

A Battery or a set of Cells connected in parallel.

Note. The term Battery does not imply that the cells are connected in series (just a collection of cells).



Cells and Batteries.

Battery connections

- Why might we need to connect cells in series?
 - To produce an **Increased Voltage**.
- Why might we need to connect cells in parallel?
 - To give an **Increased Current** capability.
- How do we calculate the voltage of cells connected in series?
 - Add voltages together, however do remember to take into account Cell polarity.

Cells and Batteries.

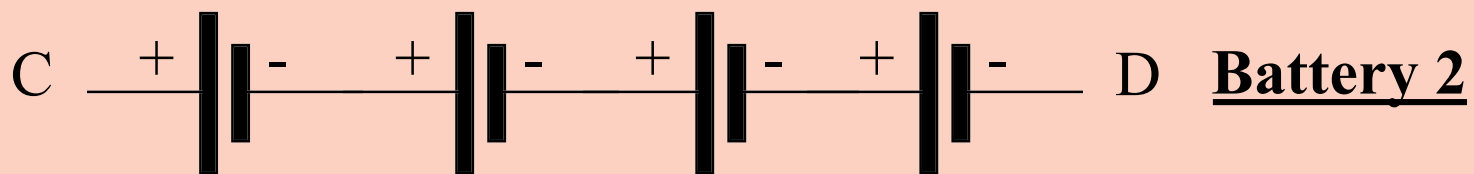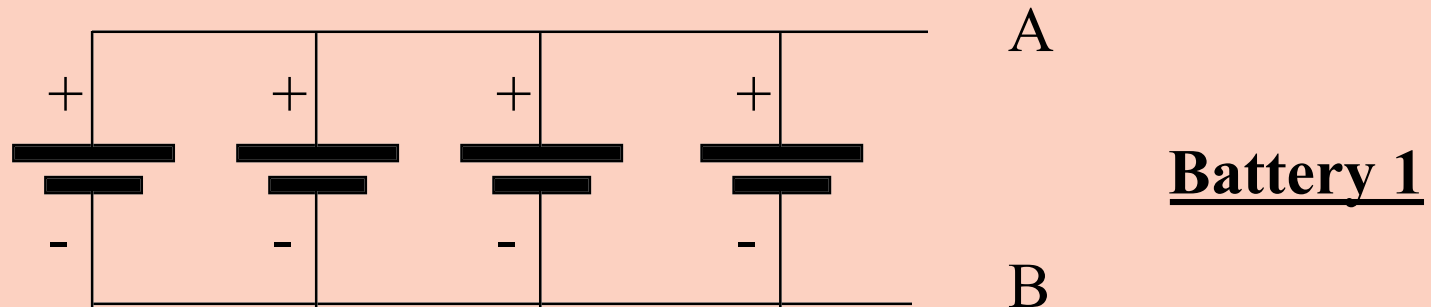If the voltage of each cell is 1.5 volts and they can deliver 2A.




What is the current and voltage capability of the batteries shown above? Points A,B and Points C,D

Cells and Batteries.


- Battery 1: As all the cells are in parallel and they are all the same voltage therefore voltage at point “AB” is 1.5Volts, however each cell can deliver 2A therefore at point “AB” the system can deliver $4*2A = 8$ Amps.
- Battery 2: As all the cells are in series and they are all the same voltage therefore voltage at point “CD” is $4*1.5 = 6$ Volts, however each cell can deliver 2A therefore at point “CD” the system can only deliver 2 Amps.

Meters


and Test Equipment

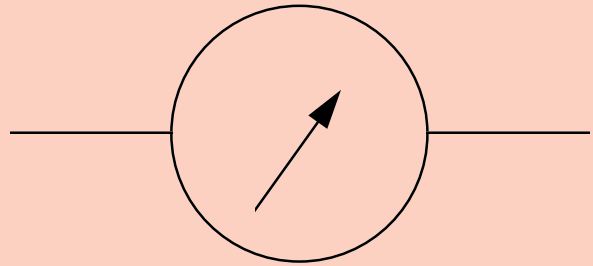


Meters.

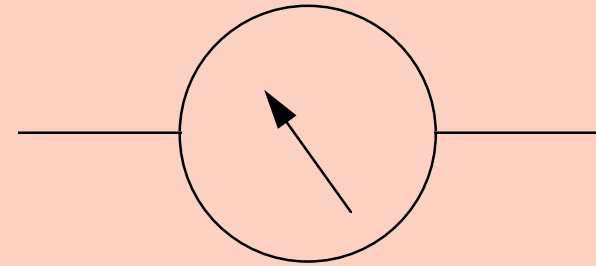

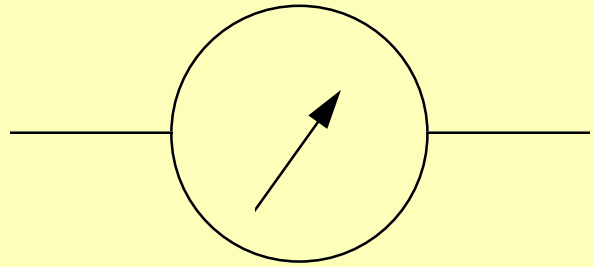- The typical Analogue Meter requires 1mA of current to enable its pointer to move across the meters scale. FSD (Full Scale Deflection).
- A typical Meter coil resistance is about 1000Ω .
- How do we get this Meter to measure :-
 - Voltage ?
 - Current ?
 - Resistance ?




Meters.

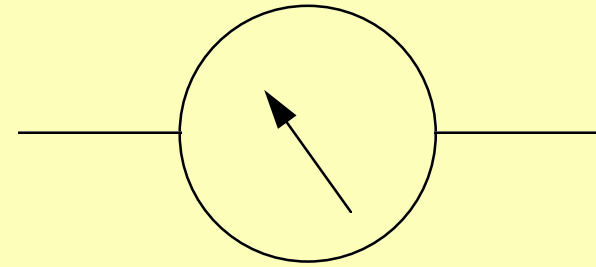


What do we know about this device ?

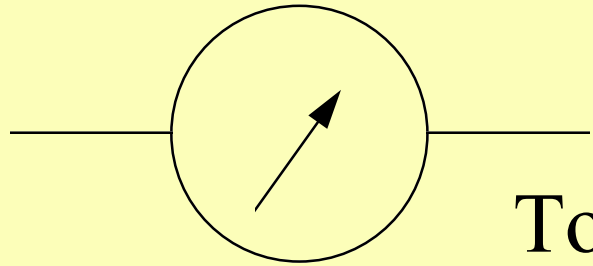- Meter Voltage : $V_{\text{Meter}} = \text{Current} * \text{Resistance}$
- $V_{\text{Meter}} = 1\text{mA} * 1000\Omega = 1 * 10^{-3} * 1 * 10^3$
- V_{Meter} for Full Scale Deflection = 1 Volt
- So what do we do if we want this Meter to measure :- 100 Volts.
- **Solution**
- **One Volt** must be present **across** the **Meter** and **Ninety Nine Volts** lost **somewhere else**.






Meters.

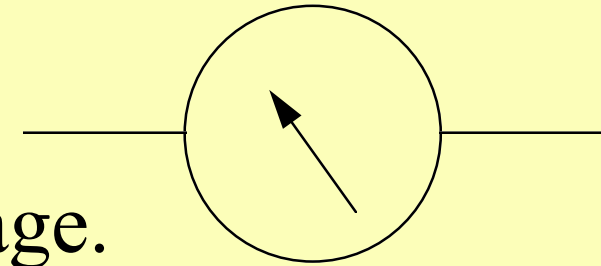


To Measure Voltage.

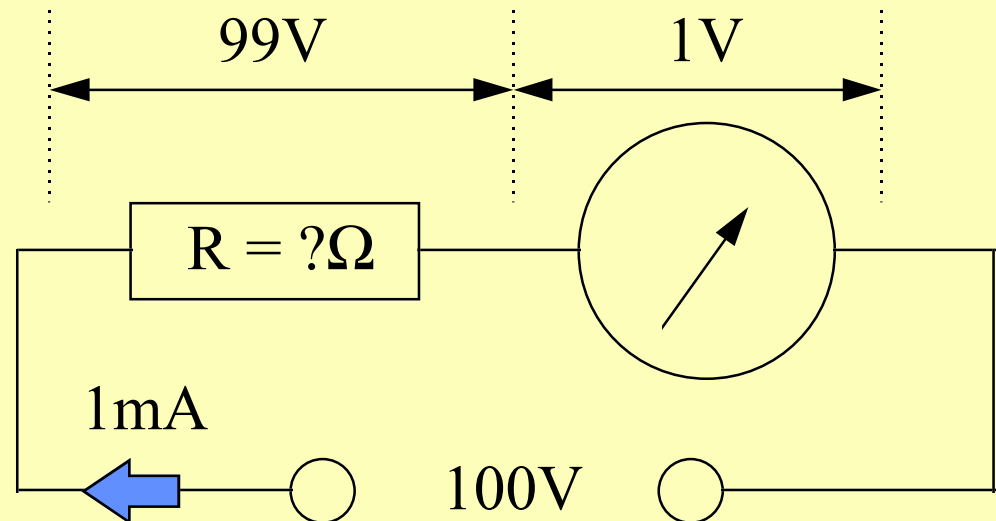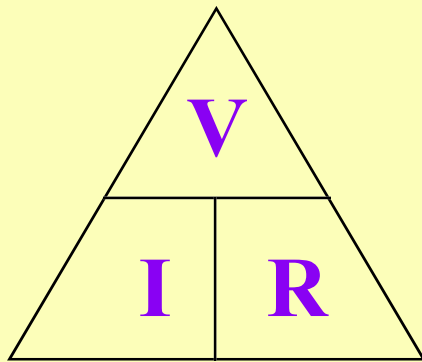- Theory :- Resistance = Voltage / Current
- Mystery Resistance = 99 volts / 1mA
= $99 / (1 * 10^{-3})$
= 99000Ω or 99KΩ
- Mystery Resistance needs to be 99KΩ




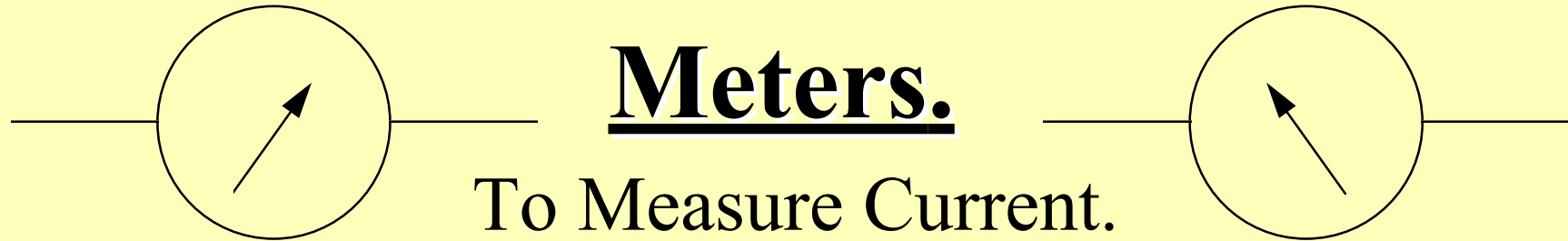

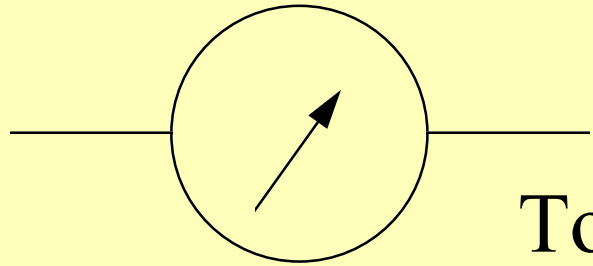- Current for Full Scale Deflection = 1mA
- So if we want the same Meter to measure :-
2 Amps.
- **Solution**
- **One milli Amp** must be present **through** the **Meter** and **1999mA** routed **elsewhere**.






Meters.

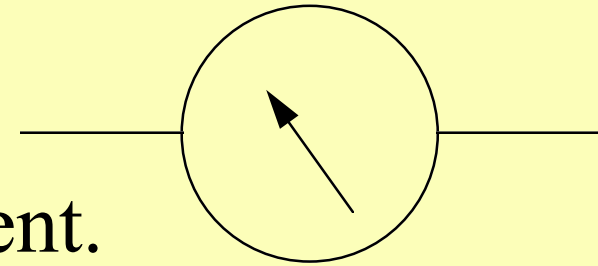

To Measure Current.

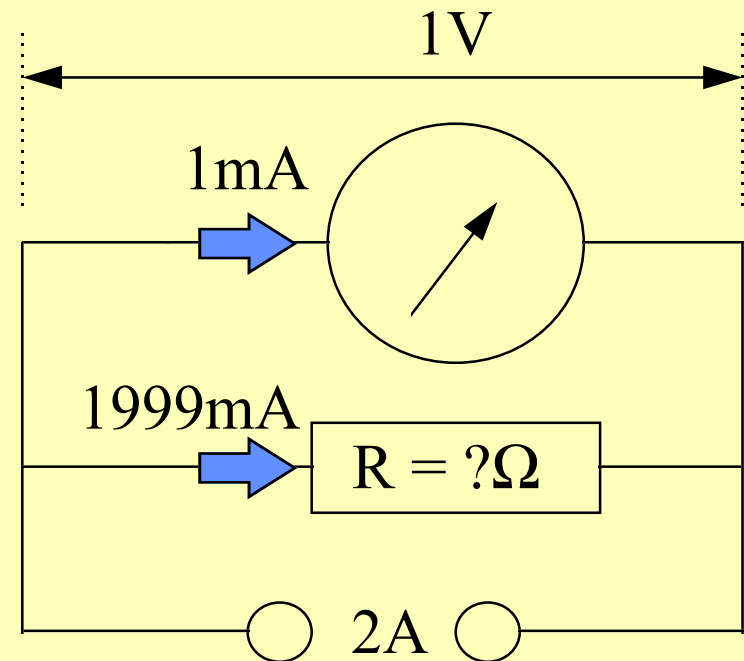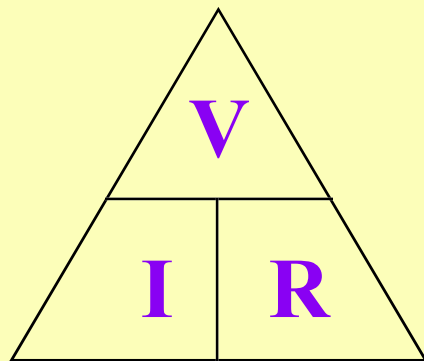
- Theory : Resistance = Voltage / Current
- Mystery Resistance = 1 volts / 1999mA
= $1 / 1999 * 10^{-3}$
- Mystery Resistance needs to be 0.50025Ω



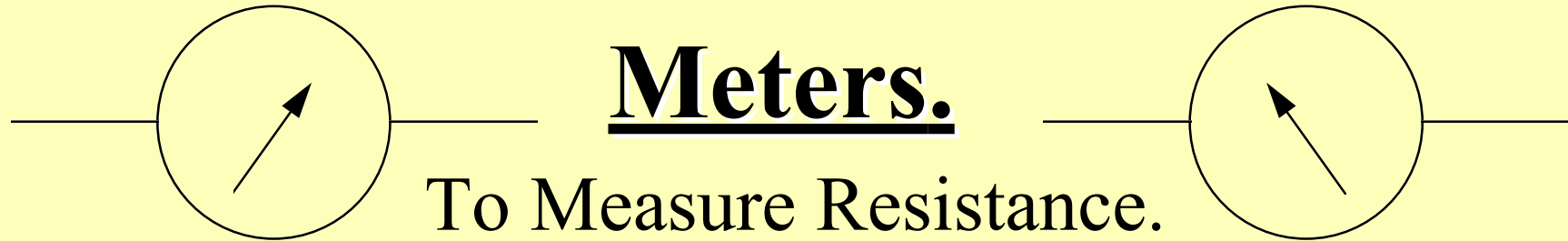

- Current for Full Scale Deflection = 1mA.
- or Voltage for Full Scale Deflection = 1 Volt.
- So if we want the same Meter to measure :-
Ohms (Resistance = Volts/Amps)
- **Solution**
- **Measure current** but **calibrate** the **scale** in ohms.
- **Measure Volts** but **calibrate** the **scale** in ohms.
- so using current method.

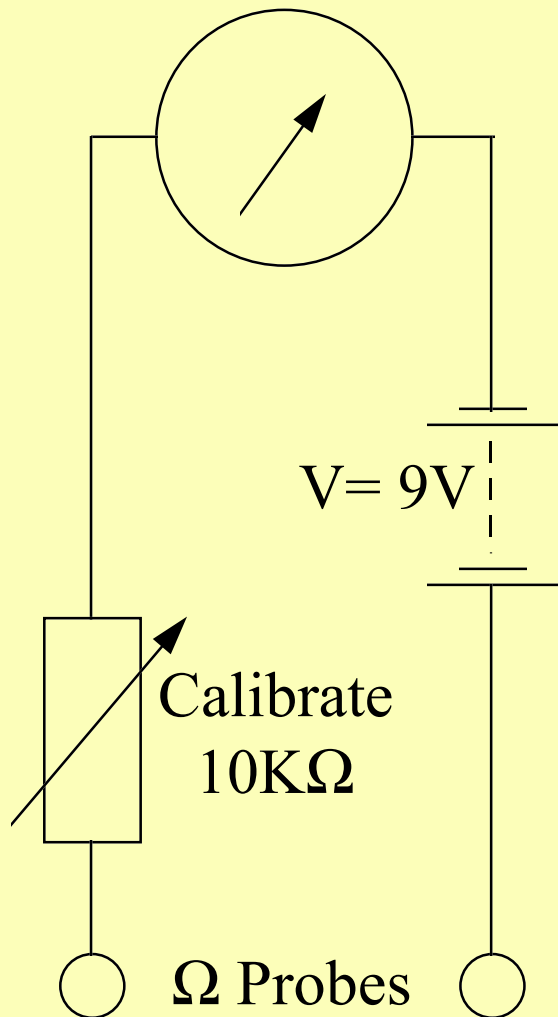
To Calibrate:
Short Probes and
adjust for zero Ohms



Meters.

- Using a 9V Power Source and a 10KΩ calibration variable resistor.
- @Zero Ohms : Circuit current = 1mA or 100% FSD
- Resistance = Meter + Calibrate = $9V / 1mA = 9000\Omega$
- Meter = 1000Ω ∴ Calibrate = 8000Ω
- @1K Ohms: Circuit Resistance = $1000 + (8000 + 1000) = 10K\Omega$
- @1K Ohms : Circuit current = $9V / 10K\Omega = 0.9mA$ or 90% FSD

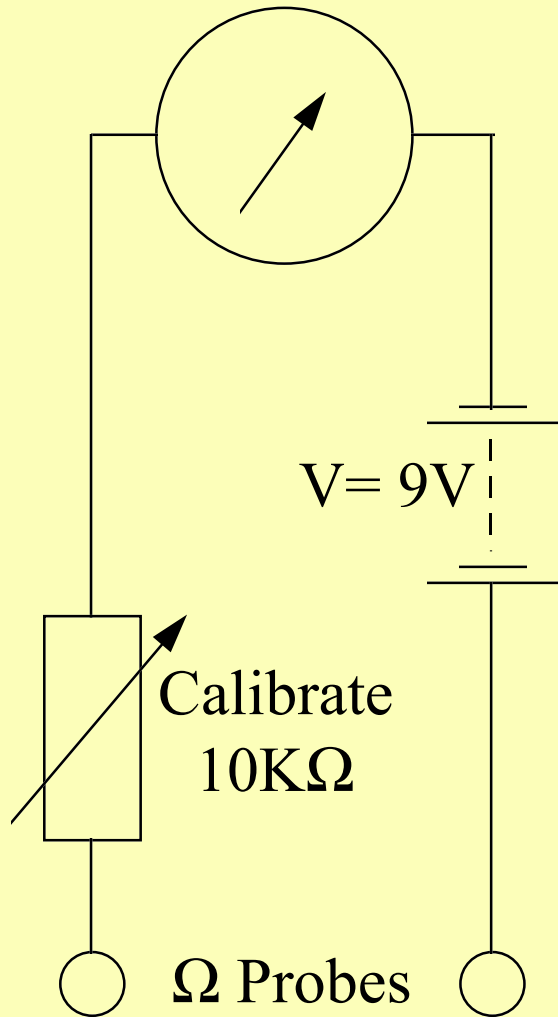To Calibrate:
Short Probes and
adjust for zero Ohms




Meters.

Full Calibration Table


<u>Unknown Resistance</u>	<u>Scale Mark</u>
0 Ω	100.00 %
1,000 Ω	90.00%
2,000 Ω	81.82 %
5,000 Ω	64.29 %
10,000 Ω	47.37 %
20,000 Ω	31.03 %
50,000 Ω	15.25 %
100,000 Ω	8.26 %
200,000 Ω	4.31 %
500,000 Ω	1.77 %
1,000,000 Ω	0.89 %
2,000,000 Ω	0.45 %
5,000,000 Ω	0.18 %
10,000,000 Ω	0.09 %

Meters.


Accuracy and Loading.

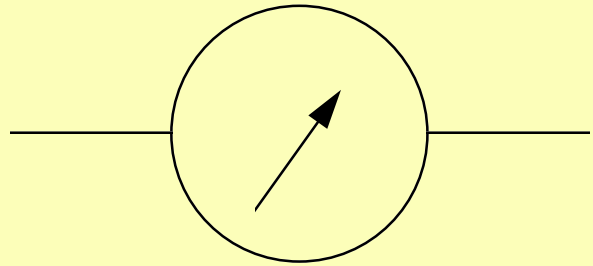


Meters.

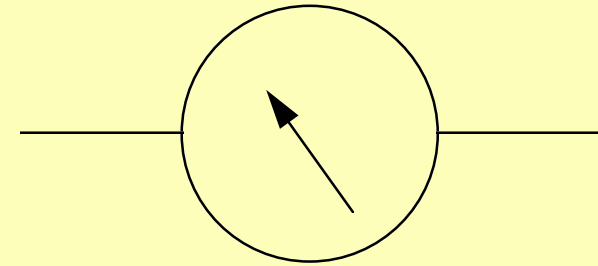

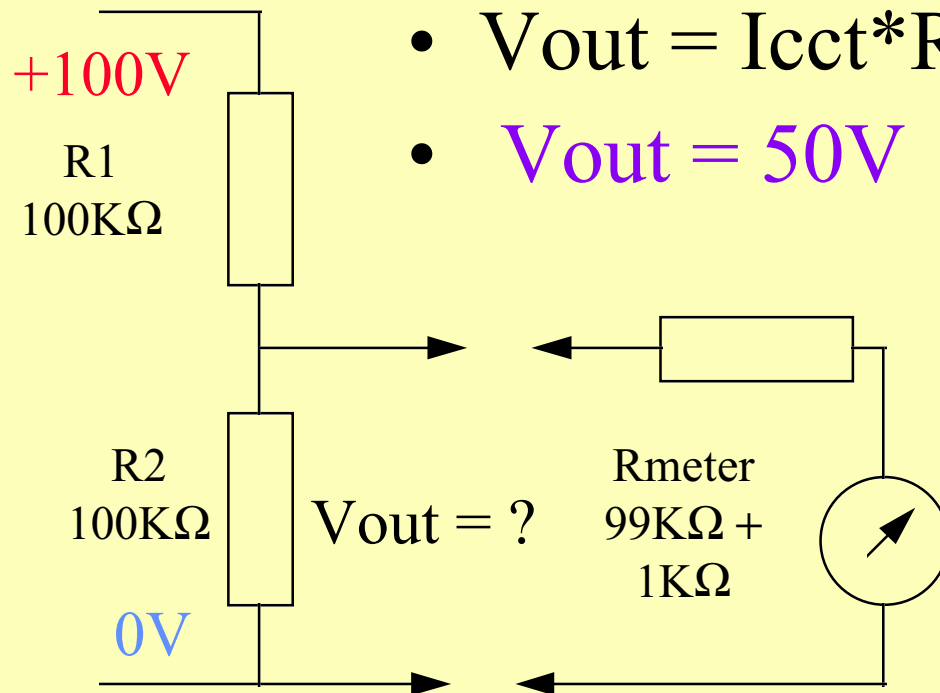
- What voltage do we expect to read ?
- $R_{Ts} = 100K\Omega + 100K\Omega = 200K\Omega$
- $I_{cct} = V/R = 100/200K = 0.5mA$
- $V_{out} = I_{cct} * R2 = 0.5mA * 100K\Omega$
- $V_{out} = 50V$




Using our “Meter”
to measure voltage.

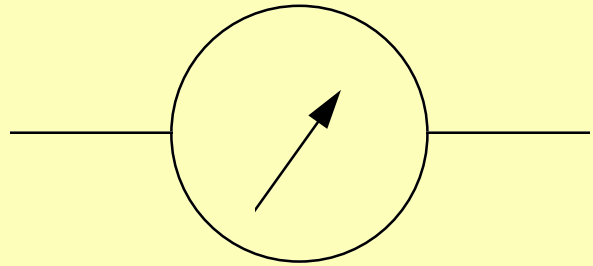


Meters.

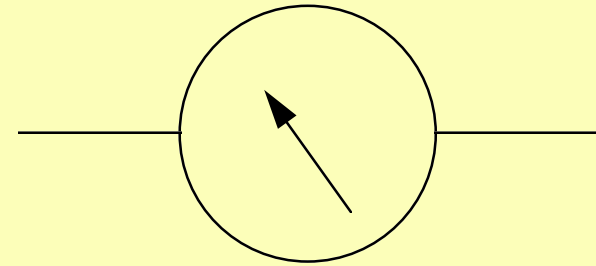


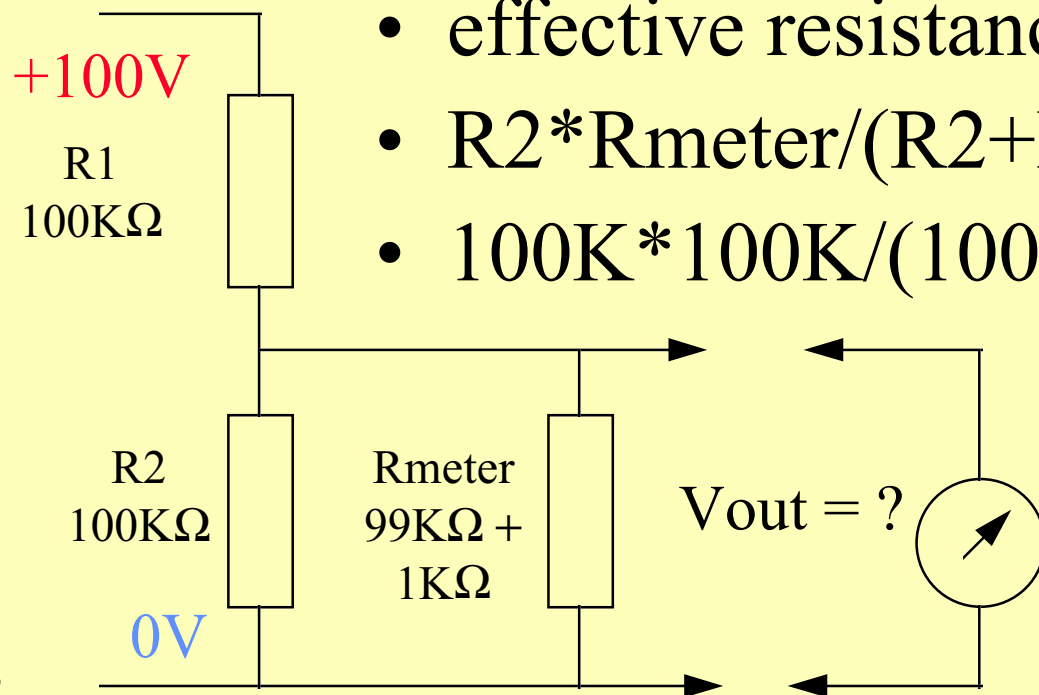- What voltage will we read ?
- $R_{\text{meter}} = 99\text{K}\Omega + 1\text{K}\Omega = 100\text{K}\Omega$
- R_{meter} is in Parallel with R_2
- effective resistance = $R_2 \parallel R_{\text{meter}} =$
- $R_2 * R_{\text{meter}} / (R_2 + R_{\text{meter}}) =$
- $100\text{K} * 100\text{K} / (100\text{K} + 100\text{K}) = 50\text{K}\Omega$




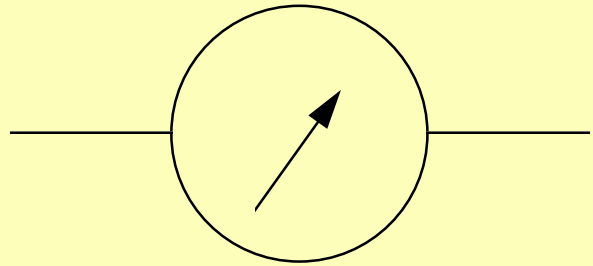


Meters.

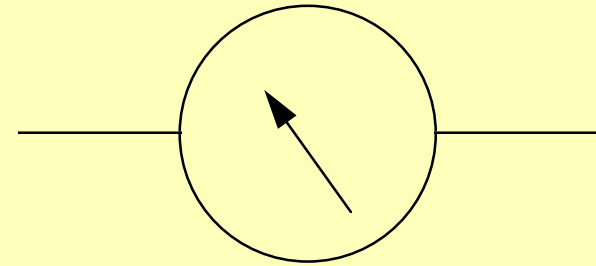

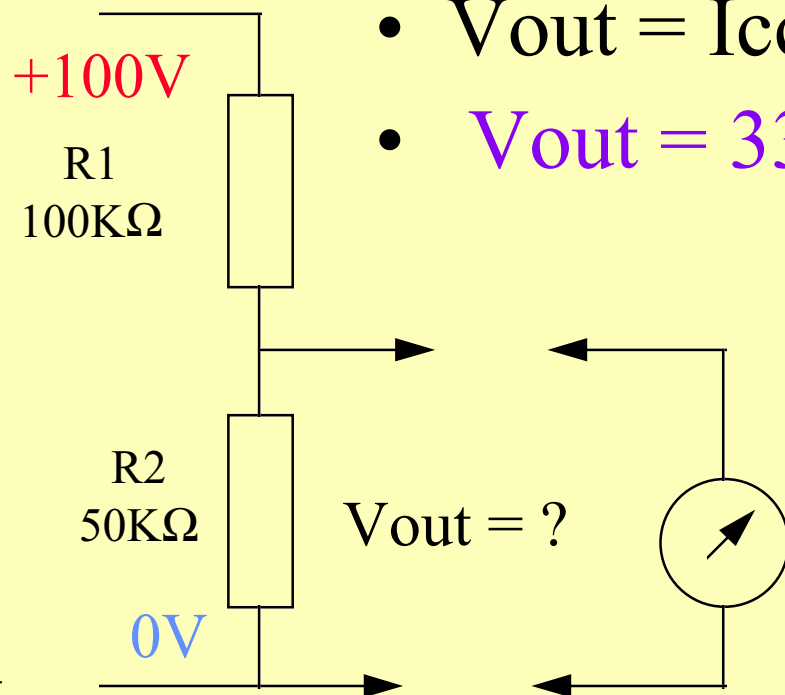
- What voltage will we read ?
- $R_{Ts} = 100\text{K}\Omega + 50\text{K}\Omega = 150\text{K}\Omega$
- $I_{cct} = V/R = 100/150\text{K} = 0.666\text{mA}$
- $V_{out} = I_{cct} * R_2 = 0.666\text{mA} * 50\text{K}\Omega$
- $V_{out} = 33.333\text{V}$



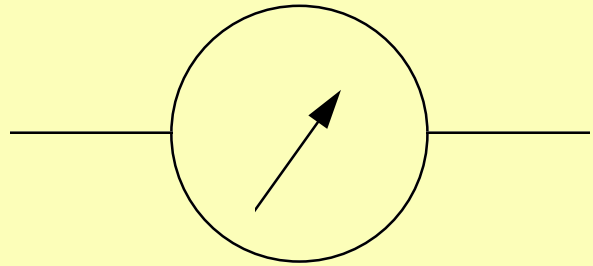

Meters.

Summary.

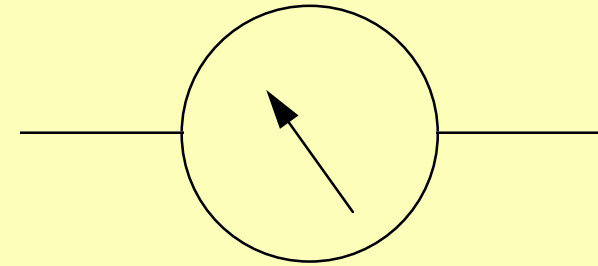

- By switching Shunts (Resistor in parallel) and Droppers / Multiplier (resistor in series) with the meter a range of measurements can be made (the basis of the multi-meter (needs multi scales)).
- The Impedance / Resistance of the meter can significantly effect the readings being taken.
- A scale parallax mirror can assist the accuracy of any readings taken.

Kirchhoff

Kirchhoff.

- As part of your work duties you are required to collect the daily order from canteen van.
- You are given £10 each day to pay for the order.
- A new person is looking after the van on the last day. Did they give you the correct change?

Kirchhoff.

Tea	Coffee	KitKats	Snacks	Change
-----	--------	---------	--------	--------

Order for first four days

5	9	3	2	£5.52
7	5	4	1	£6.07
8	8	2	3	£5.37
2	7	2	2	£6.88

Last day Order

9	6	5	7	£1.34
---	---	---	---	-------

Kirchhoff.

- General Guidance.
- To solve this type of problem if you have **four unknown** values.
- You need **four unique equations.**
- Note the equations must not be multiples of each other.
- **3 unknowns** need **3 unique equations.**
- **2 unknowns** need **2 unique equations** etc.

Kirchhoff.

Tea	Coffee	KitKats	Snacks	Change
5T	9C	3K	2S	=5.52
7T	5C	4K	1S	=6.07
8T	8C	2K	3S	=5.37
2T	7C	2K	2S	=6.88

Calculate actual cost of Goods

Kirchhoff.

Tea	Coffee	KitKats	Snacks	Change
5T	9C	3K	2S	=4.48
7T	5C	4K	1S	=3.93
8T	8C	2K	3S	=4.63
2T	7C	2K	2S	=3.12

Convert cost to pence to make calculations easier.

Draw out calculation as a table and identify the lines.

Kirchhoff.

Try to eliminate a variable and leave 3 equations.

$$\begin{array}{rcccccc} A & 5T & 9C & 3K & 2S & = & 448 \\ B & 7T & 5C & 4K & 1S & = & 393 \\ C & 8T & 8C & 2K & 3S & = & 463 \\ D & 2T & 7C & 2K & 2S & = & 312 \end{array}$$

Kirchhoff.

Try to eliminate a variable and leave 3 equations.

$$\begin{array}{rcccccccl} A & 5T & 9C & 3K & 2S & = & 448 \\ B & 7T & 5C & 4K & 1S & = & 393 \\ C & 8T & 8C & 2K & 3S & = & 463 \\ D & 2T & 7C & 2K & 2S & = & 312 \end{array}$$

Action 1 Subtract D from A

Action 2 Subtract (B*2) from A

Action 3 Subtract (B*3) from C

Kirchhoff.

$$\begin{array}{rccclclcl} A & 5T & 9C & 3K & 2S & = & 448 \\ D & 2T & 7C & 2K & 2S & = & 312 \\ A-D & 3T & 2C & 1K & 0S & = & 136 \end{array}$$

- Action 1 Subtract D from A
- Action 2 Subtract (B*2) from A
- Action 3 Subtract (B*3) from C

Kirchhoff.

$$\begin{array}{rcccccc} A & 5T & 9C & 3K & 2S & = & 448 \\ B*2 & 14T & 10C & 8K & 2S & = & 786 \\ A-2B & -9T & -1C & -5K & 0S & = & -338 \end{array}$$

- Action 1 Subtract D from A
- Action 2 Subtract (B*2) from A
- Action 3 Subtract (B*3) from C

Kirchhoff.

$$\begin{array}{rcccccc} C & 8T & 8C & 2K & 3S & = & 463 \\ B*3 & 21T & 15C & 12K & 2S & = & 1179 \\ C-3B & -13T & -7C & -10K & 0S & = & -716 \end{array}$$

- Action 1 Subtract D from A
- Action 2 Subtract (B*2) from A
- Action 3 Subtract (B*3) from C

Kirchhoff.

$$\begin{array}{rcccccc} \text{E} & 3\text{T} & 2\text{C} & 1\text{K} & 0\text{S} & = & 136 \\ \text{F} & -9\text{T} & -1\text{C} & -5\text{K} & 0\text{S} & = & -338 \\ \text{G} & -13\text{T} & -7\text{C} & -10\text{K} & 0\text{S} & = & -716 \end{array}$$

Start a new table from processed values.

Kirchhoff.

Try to eliminate another variable and leave 2 equations.

$$\begin{array}{rcccccccl} \text{E} & 3\text{T} & 2\text{C} & 1\text{K} & 0\text{S} & = & 136 \\ \text{F} & -9\text{T} & -1\text{C} & -5\text{K} & 0\text{S} & = & -338 \\ \text{G} & -13\text{T} & -7\text{C} & -10\text{K} & 0\text{S} & = & -716 \end{array}$$

Kirchhoff.

Try to eliminate another variable and leave 2 equations.

$$\begin{array}{rcccccccl} \text{E} & 3\text{T} & 2\text{C} & 1\text{K} & 0\text{S} & = & 136 \\ \text{F} & -9\text{T} & -1\text{C} & -5\text{K} & 0\text{S} & = & -338 \\ \text{G} & -13\text{T} & -7\text{C} & -10\text{K} & 0\text{S} & = & -716 \end{array}$$

Action 1 Add (E*5) to F

Action 2 Add (E*10) to G

Kirchhoff.

Try to eliminate another variable.

$$\begin{array}{rcccccc} 5 * E & 15T & 10C & 5K & 0S & = & 680 \\ F & -9T & -1C & -5K & 0S & = & -338 \\ 5E-F & 6T & 9C & 0K & 0S & = & 342 \end{array}$$

Action 1 Add (E*5) to F
Action 2 Add (E*10) to G

Kirchhoff.

Try to eliminate another variable.

$$\begin{array}{rcccccc} 10^*E & 30T & 20C & 10K & 0S & = & 1360 \\ G & -13T & -7C & -10K & 0S & = & -716 \\ 10E+G & 17T & 13C & 0K & 0S & = & 644 \end{array}$$

Action 1 Add (E*5) to F
Action 2 Add (E*10) to G

Kirchhoff.

$$\begin{array}{rcccccc} \text{H} & 6\text{T} & 9\text{C} & 0\text{K} & 0\text{S} & = & 342 \\ \text{J} & 17\text{T} & 13\text{C} & 0\text{K} & 0\text{S} & = & 644 \end{array}$$

Start a new table from processed values.

Kirchhoff.

$$\begin{array}{r} \text{H} \quad 6\text{T} \quad 9\text{C} \quad 0\text{K} \quad 0\text{S} \quad = \quad 342 \\ \text{J} \quad 17\text{T} \quad 13\text{C} \quad 0\text{K} \quad 0\text{S} \quad = \quad 644 \end{array}$$

Action 1 Multiply H * 13

Action 2 Multiply J * 9

Action 3 Subtract (13*H) from (9*J)

Kirchhoff.

$$\begin{array}{r} H*13 \quad 78T \quad 117C \quad 0K \quad 0S \quad = \quad 4446 \\ J \quad 17T \quad 13C \quad 0K \quad 0S \quad = \quad 644 \end{array}$$

- Action 1 Multiply H * 13
- Action 2 Multiply J * 9
- Action 3 Subtract (13*H) from (9*J)

Kirchhoff.

$$\begin{array}{r} H*13 \quad 78T \quad 117C \quad 0K \quad 0S \quad = \quad 4446 \\ J*9 \quad 152T \quad 117C \quad 0K \quad 0S \quad = \quad 5796 \end{array}$$

- Action 1 Multiply H * 13
- Action 2 Multiply J * 9
- Action 3 Subtract (13*H) from (9*J)

Kirchhoff.

$$\begin{array}{r} J*9 \quad 152T \quad 117C \quad 0K \quad 0S \quad = \quad 5796 \\ H*13 \quad 78T \quad 117C \quad 0K \quad 0S \quad = \quad 4446 \\ 9*J- \quad 75T \quad 0C \quad 0K \quad 0S \quad = \quad 1350 \\ 13H \end{array}$$

Action 1 Multiply H * 13

Action 2 Multiply J * 9

Action 3 Subtract (13*H) from (9*J)

Kirchhoff.

$$K \quad 75T \quad 0C \quad 0K \quad 0S \quad = \quad 1350$$

Start a new table from processed values.

As we have only one Variable the process is complete.

Kirchhoff.

- So $75 \text{ Teas} = 1350 \text{ pence.}$
- Therefore a tea = $1350/75$ or 18 pence
 - Substitute in equation “H”
- Where $6 \text{ Teas} + 9 \text{ Coffees} = 342 \text{ pence.}$
- $(6 * 18 = 108)$ from $342 = 234\text{p}$
- Therefore a coffee = $234/9$ or 26 pence

Kirchhoff.

- Substitute in equation “E”
- Where $3 \text{ Teas} + 2 \text{ Coffees} + 1 \text{ KitKat} = 136$.
- $(3 * 18 = 54) + (2 * 26 = 52)$ from 136 pence
- $54 + 52 + 1 \text{ KitKat} = 136$ pence
- $106 + 1 \text{ KitKat} = 136$ pence
- $1 \text{ KitKat} = 136 \text{ pence} - 106 \text{ pence}$.
- Therefore a KitKat is 30 pence.

Kirchhoff.

- Substitute in equation “D”
- Where 2 Teas, 7 Coffees, 2 KitKat, 2 Snacks is 312 pence.
- $(2*18= 36) + (7*26=182) + (2*30 =60)$
from 312 pence
- $36 + 182 + 60 + 2 \text{ Snacks} = 312 \text{ pence}$
- $278 + 2 \text{ Snacks} = 312 \text{ pence}$
- $2 \text{ Snacks} = 312 - 278 \text{ pence} = 34 \text{ pence.}$
- Therefore a Snack = $34/2$ which is 17 pence.

Kirchhoff.

- So did you get the correct change.
- How much does 9 Teas, 6 Coffees, 5 KitKat and 7 Snacks cost?
- $(9*18 = 162) + (6*26 = 156) + (5*30 = 150)$ and $(7 * 17 = 119)$ which gives:-
- $162 + 156 + 150 + 119 = 587$ pence
- Change from £10 = $1000 - 587 = £4.13$
- If you were given £1.34 change then the driver owes you $£4.13 - £1.34 = £2.79$.

Kirchhoff.

**Practice
Example.**

Kirchhoff.

X	Y	Z	Value
1	2	3	=14
2	3	1	=11
3	1	2	=11

Calculate values of X, Y and Z

Kirchhoff.

- Solution
- $X = 1$
- $Y = 2$
- $Z = 3$

Kirchhoff.

**Back to
Electronics.**


Kirchhoff.

Kirchhoff's Laws (Circuit Analysis)

- Circuits are made up of Components and Interconnection.
- Each Connection point is called a **Node**.
- The sections between two nodes is a **Net**.
- A complete interconnected ring of components is a **Closed Loop** or **Mesh**.
- Only complete **Loop** can operate as current needs to flow around circuit to work.

Kirchhoff.

Kirchhoff's Laws

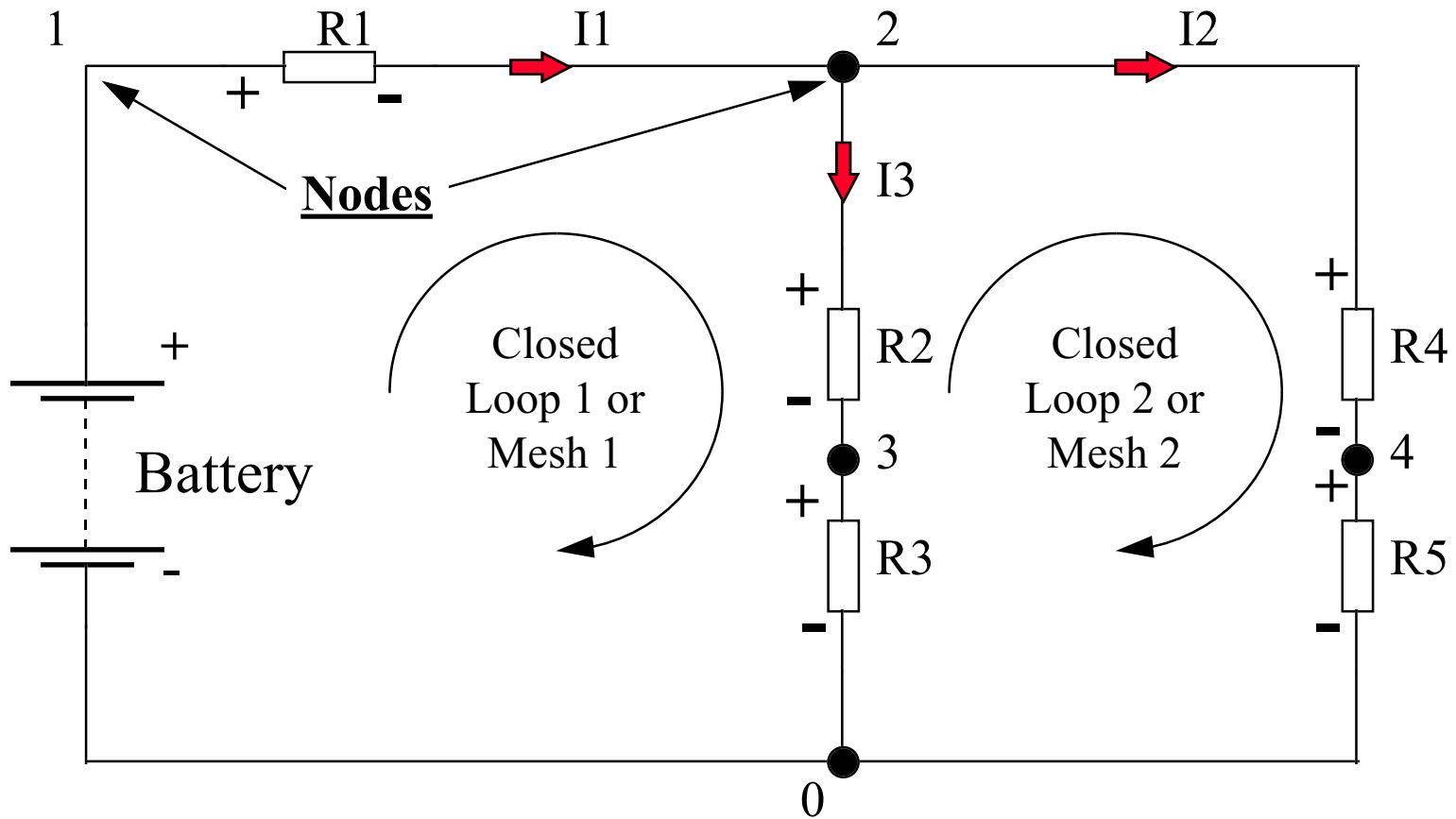

Kirchhoff.

Kirchhoff's Laws

Number 1.

The algebraic sum of all the voltages around a closed loop is zero. (or Sum of Voltage sources equals Sum of Voltage drops)

eg. $V_{\text{batt}} - V_{R1} - V_{R2} - V_{R3} = 0$


Number 2.

The sum of the currents flowing into a junction(node) equals the sum of the currents flowing out of that junction.

eg. $I_1 = I_2 + I_3 \dots$

Kirchhoff.


Kirchhoff's Laws

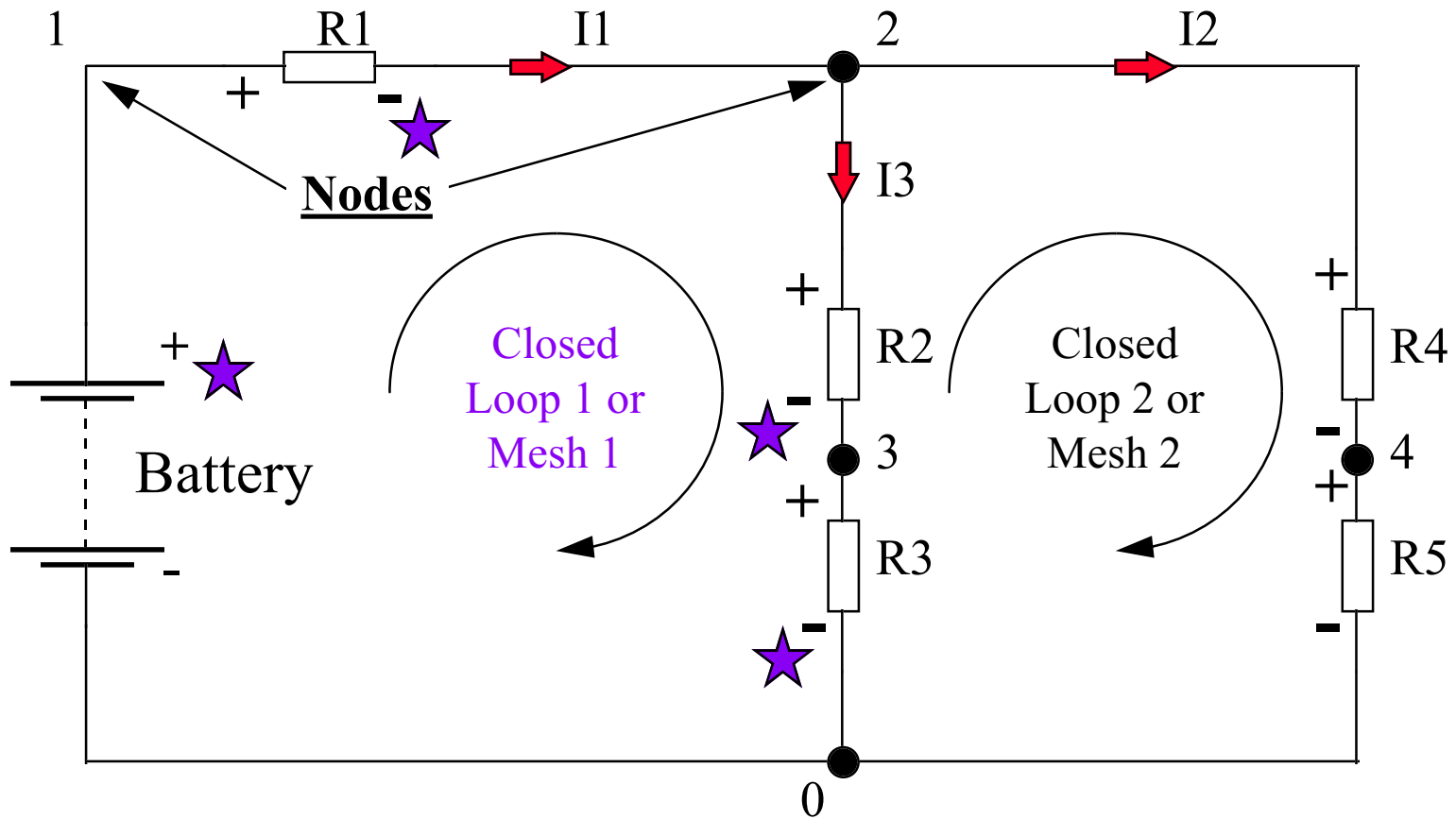

$$\text{Battery} - VR1 - VR2 - VR3 = 0$$

Kirchhoff.

Kirchhoff's Laws

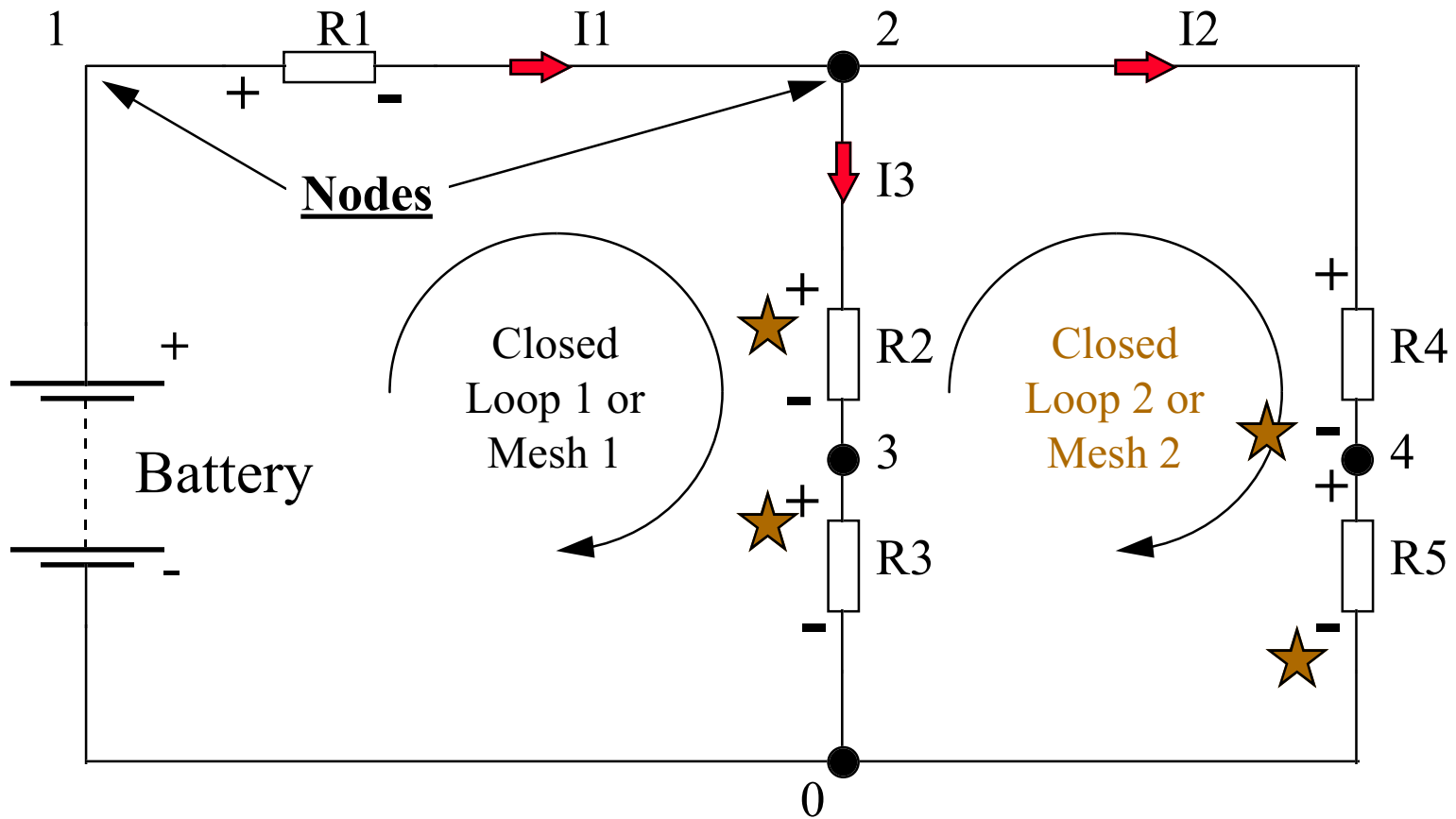

$$VR_2 + VR_3 - VR_4 - VR_5 = 0$$


Kirchhoff.

Kirchhoff's Laws (The basic Steps)

- Step 1 , Identify the Nodes and Loops.
 - Ensure all components included.
 - Keep loop count to absolute minimum.
- Step 2 , Identify presumed polarity on components (this is to ensure the equations are correct, the actual direction will be identified once the equations are solved).
- Step 3 , Solve equations.

Kirchhoff.

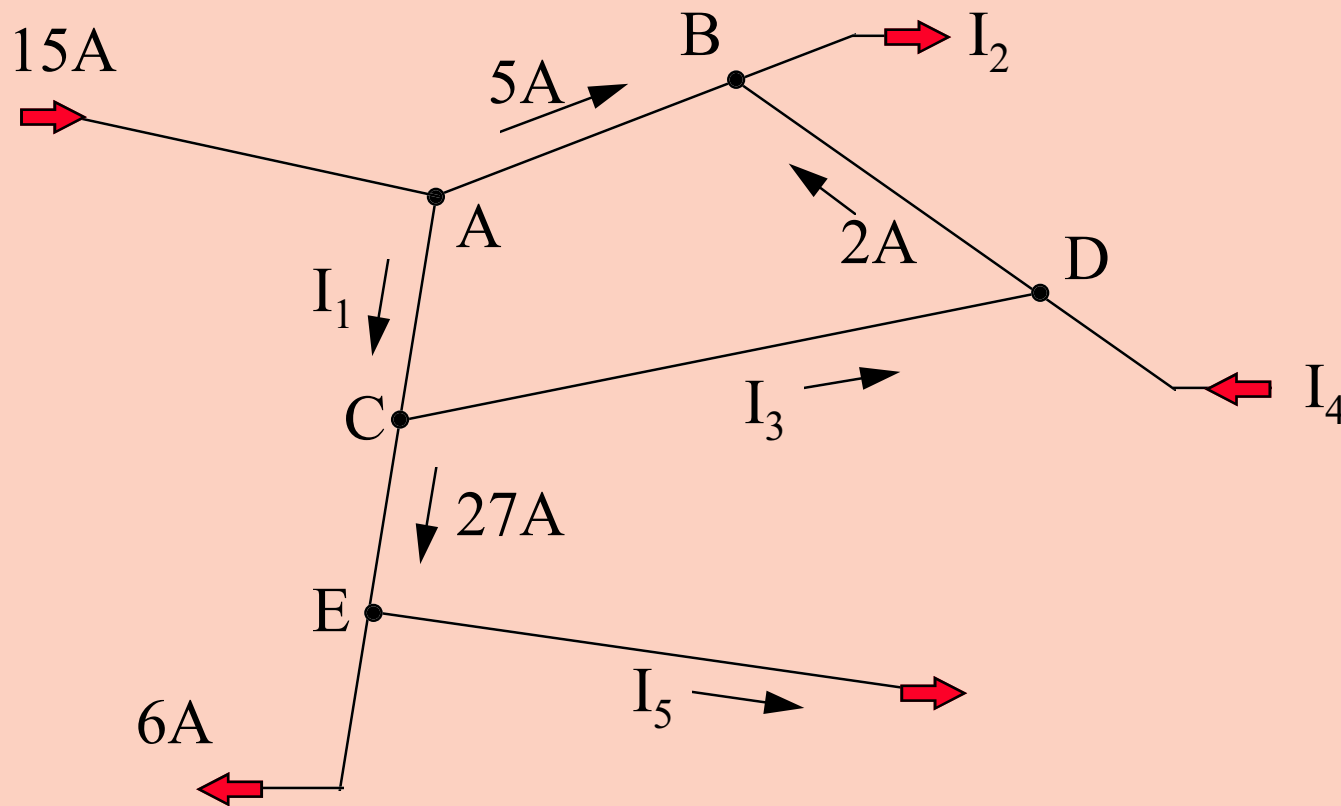- Example:-
- Determine the value of the unknown currents.




Example:-

Kirchhoff.

- Junction A: $15 = 5 + I_1$ therefore $I_1 = 10A$
- Junction B: $5 + 2 = I_2$ therefore $I_2 = 7A$
- Junction C: $I_1 = 27 + I_3$ or $10 = 27 + I_3$
- or $10 - 27 = I_3$ therefore $I_3 = -17A$
- Junction D: $I_3 + I_4 = 2$ or $-17 + I_4 = 2$
- or $I_4 = 2 + 17$ therefore $I_4 = 19A$
- Junction E: $I_5 = 27 - 6 = 21A$

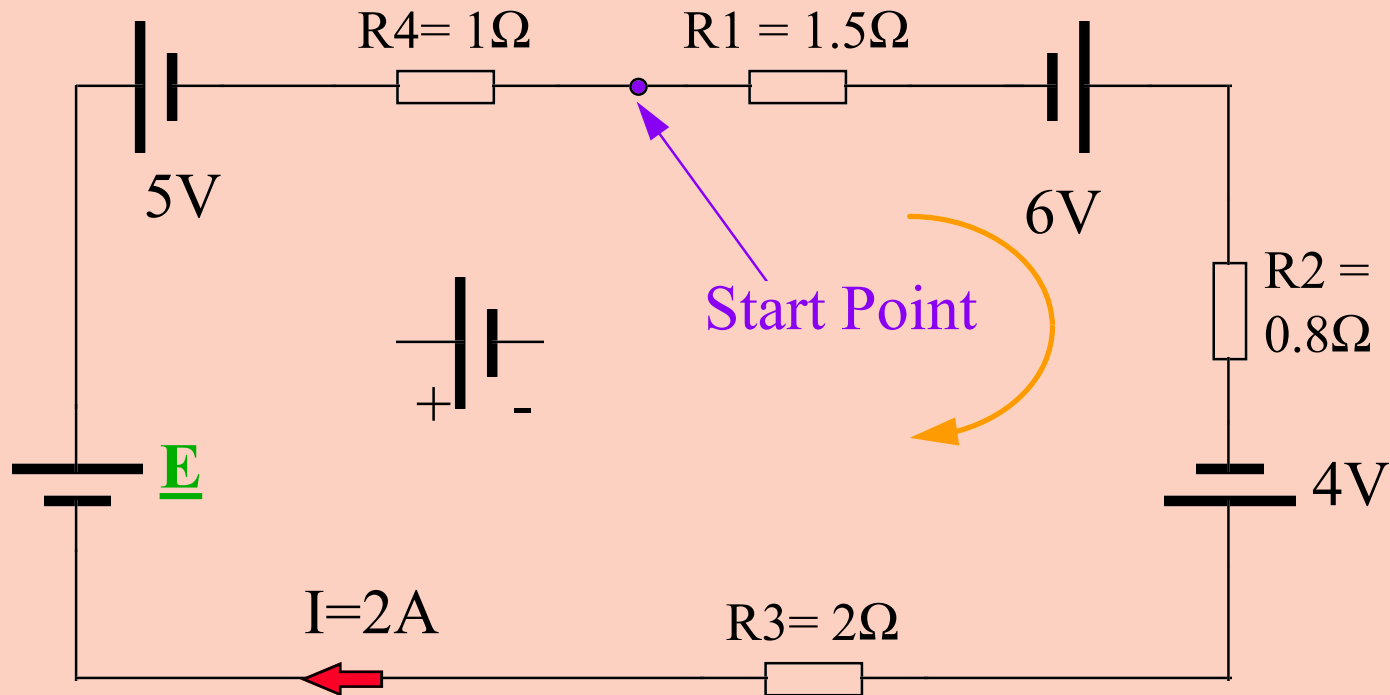
Example:- **Kirchhoff.**

- Determine the value of the e.m.f **E** in volts.



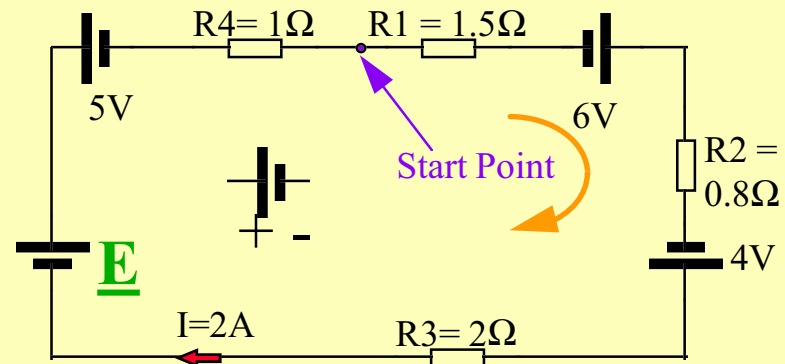Example:- Kirchhoff.


- Calculate sum of e.m.f = $6 + 4 + E - 5$ Volts
- = $5 + E$ Volts
- Note current in circuit = I Volt Drop = $I \cdot R$
-
- Calculate sum of Volt drops = $1.5I + 0.8I + 2I + 1I$ Volts
- = $5.3I$ Volts
-
- Note that $I = 2$ Amps therefore :-
- Volt drops = $5.3 \cdot 2 = 10.6$ Volts
- From Kirchhoff . . . **Sum of Voltages = Sum of Drops**
- So $5 + E = 10.6$
- or $E = 10.6 - 5$
- Therefore $E = 5.6$ Volts



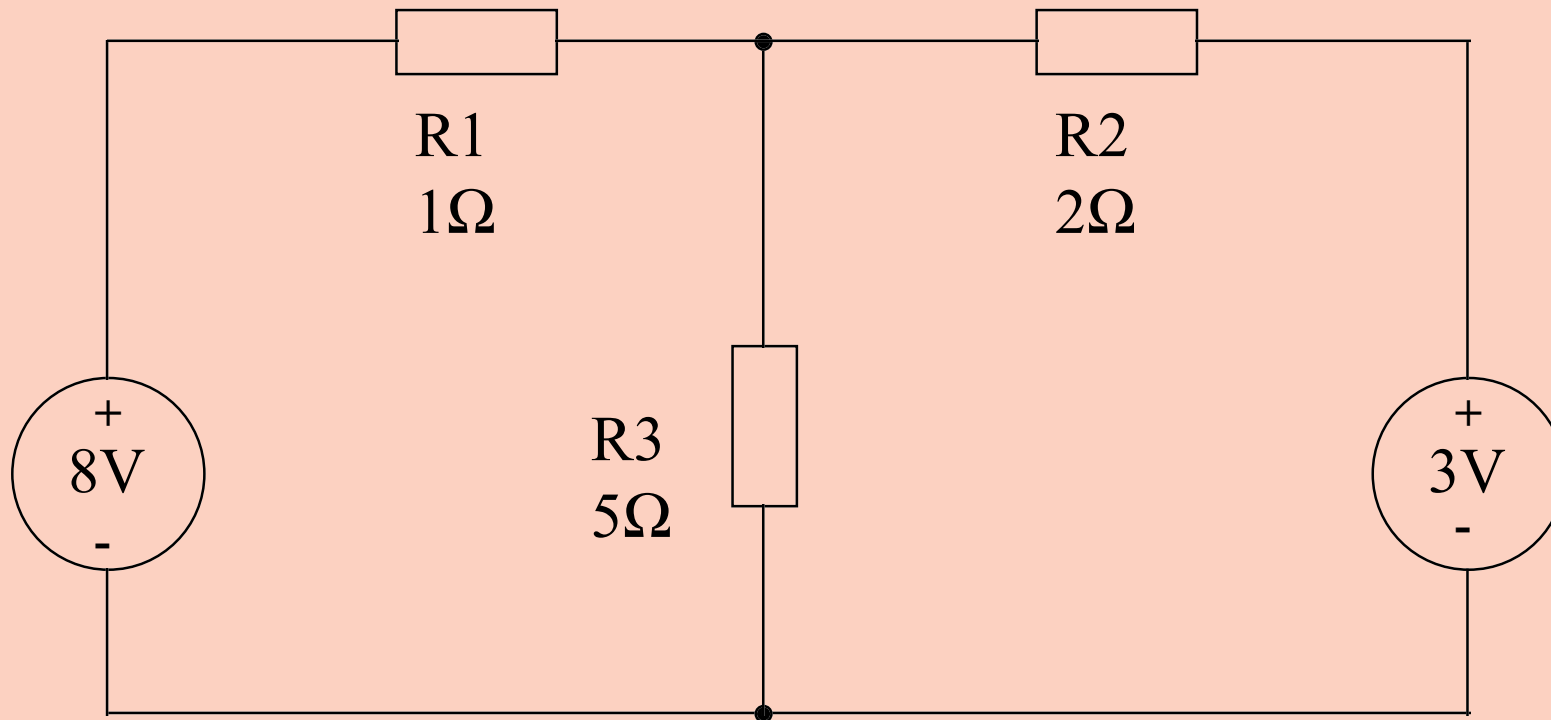Example:

Kirchhoff.


- Calculate
 - The current flowing in R3.
 - The voltage developed across R3.



Solution:

Kirchhoff.

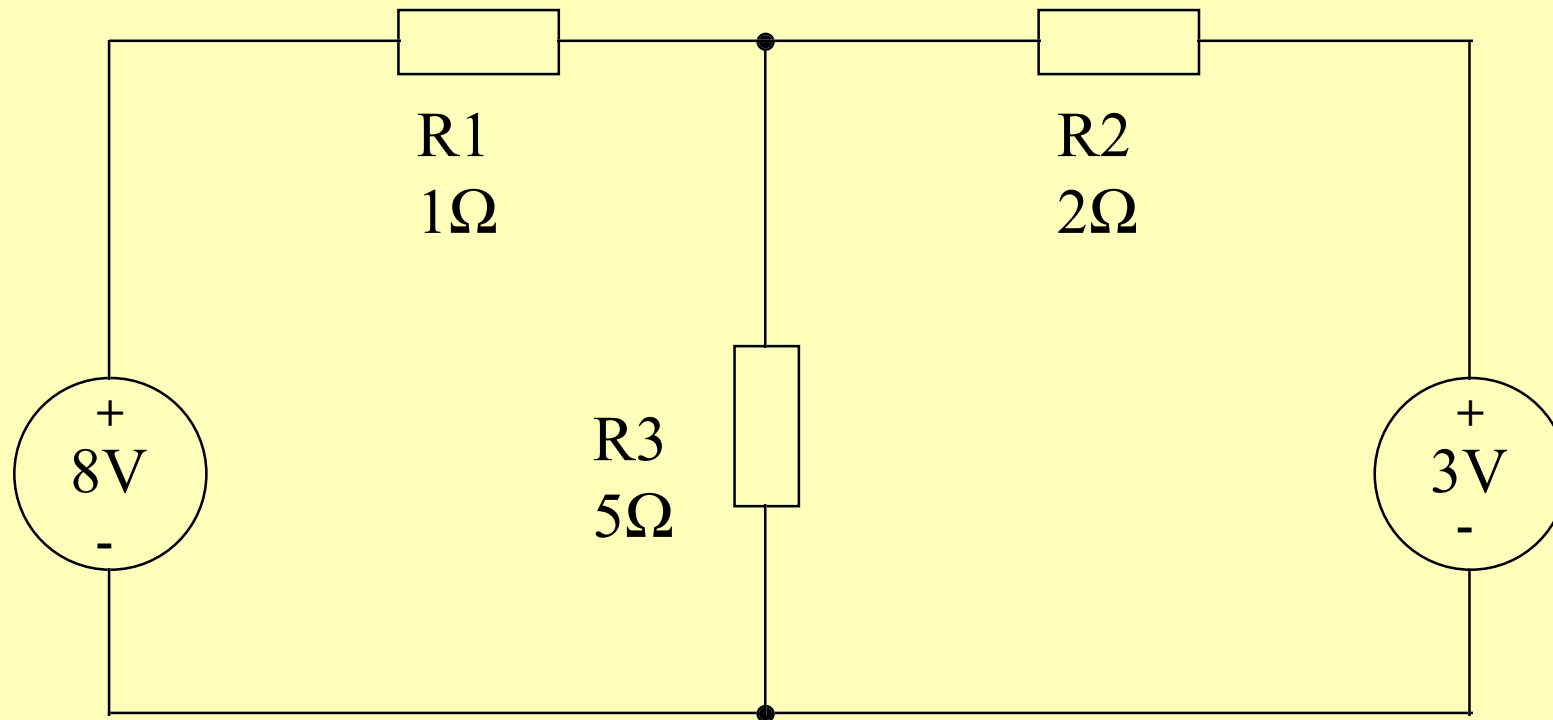
- **Getting Started :-**
- Let us consider the circuit shown below and identify where the Closed Loops are.



Solution:

Kirchhoff.

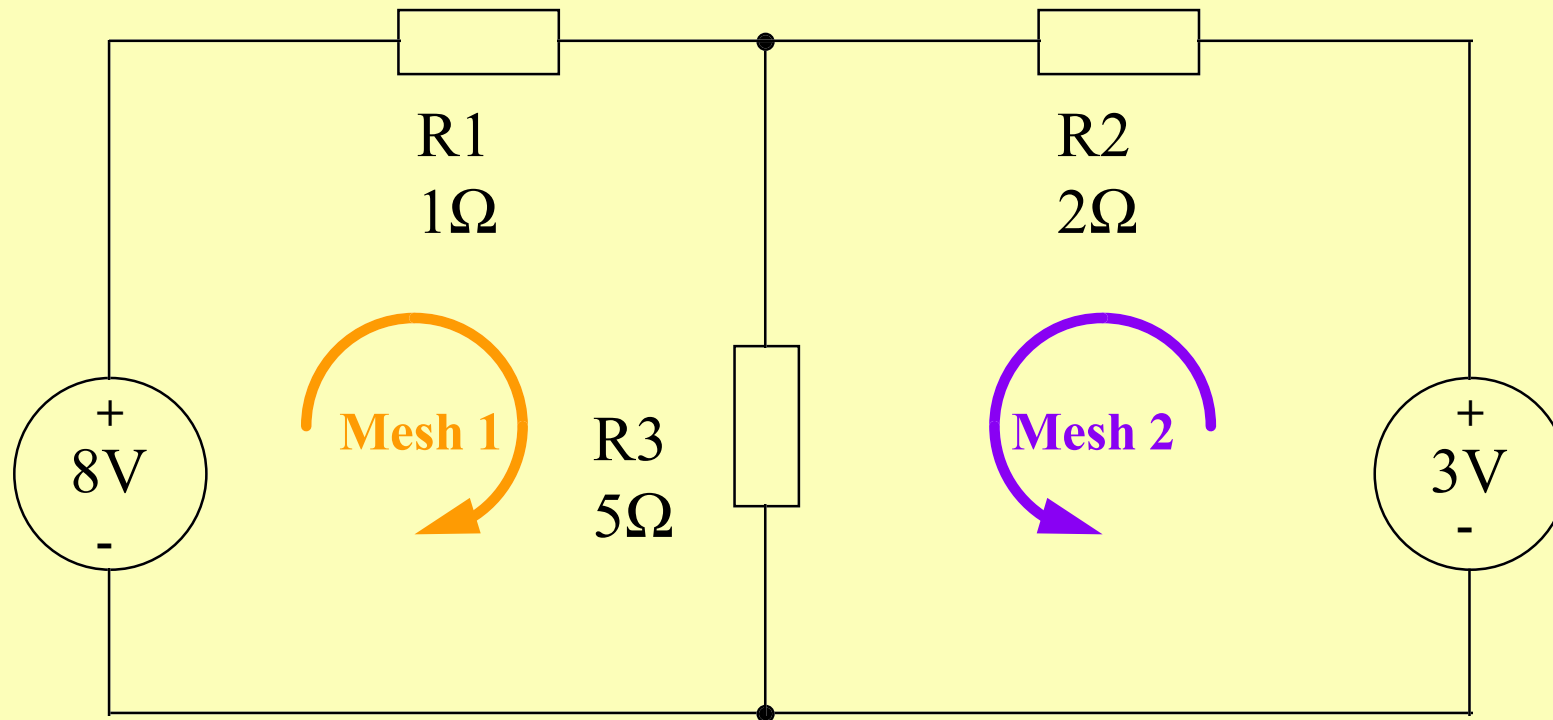
- Now annotate the current flows around the circuit.



Solution:

Kirchhoff.

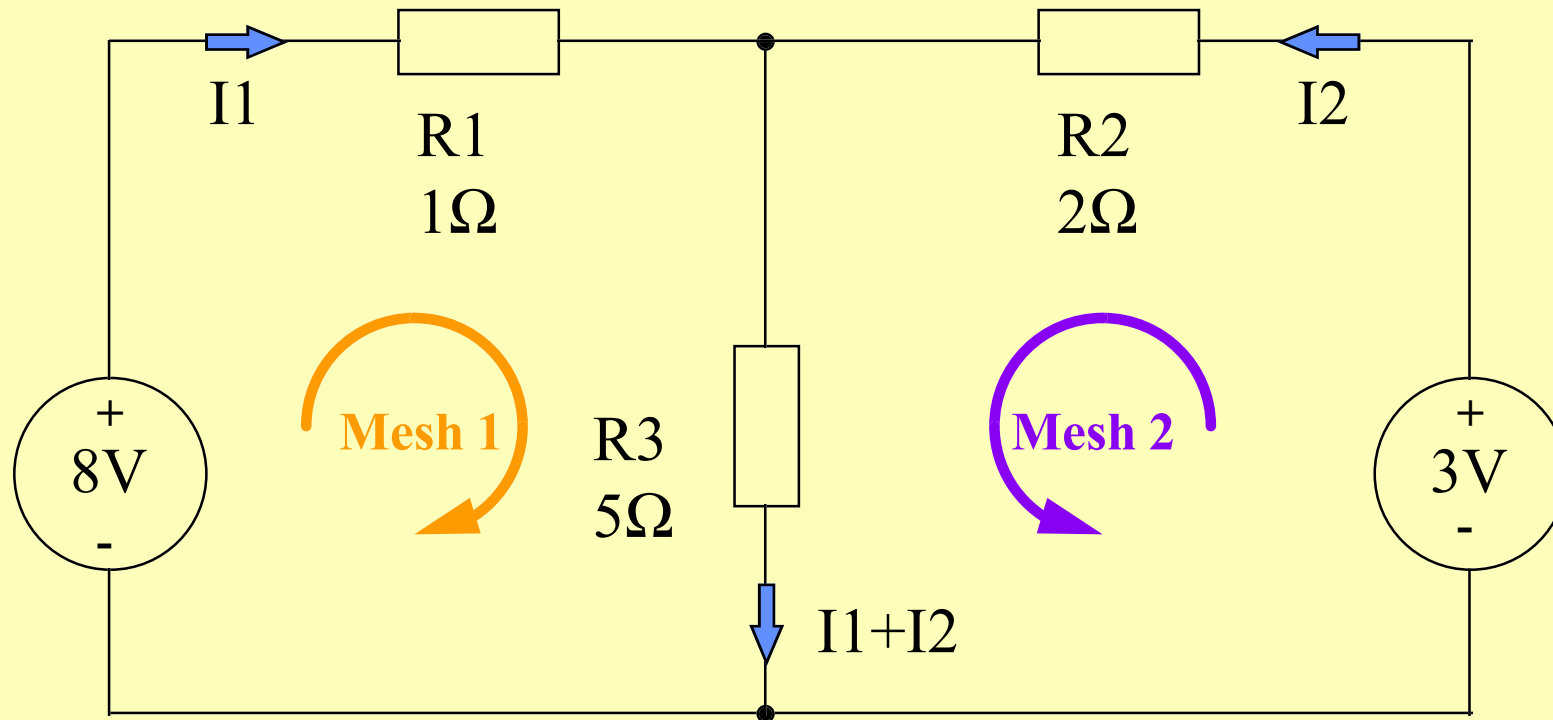
- Annotate with assumed polarities of the circuit - observing the Voltage drops and Voltage sources.



Solution:

Kirchhoff.

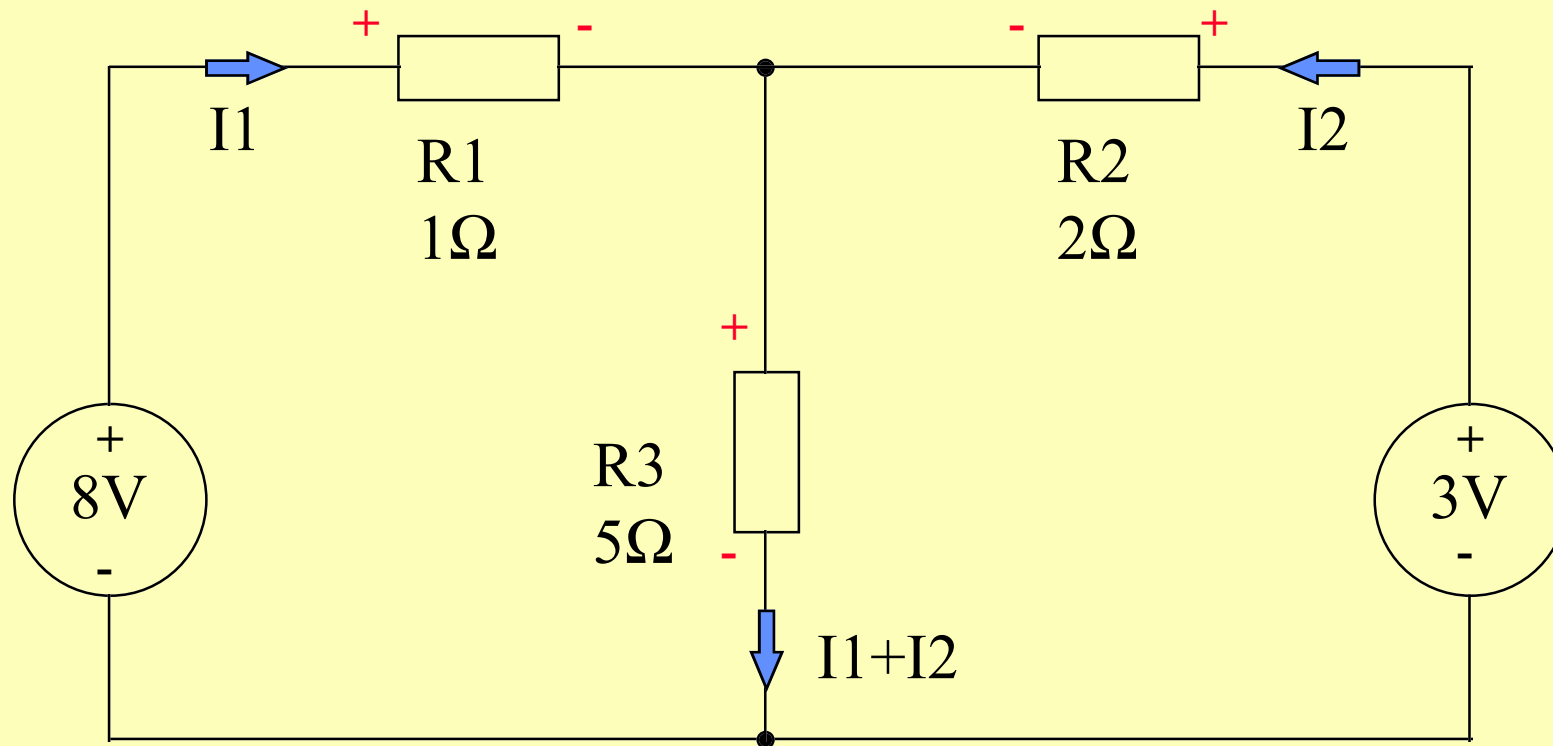
- Develop the voltage equations for Mesh 1 and Mesh 2.



Solution:

Kirchhoff.

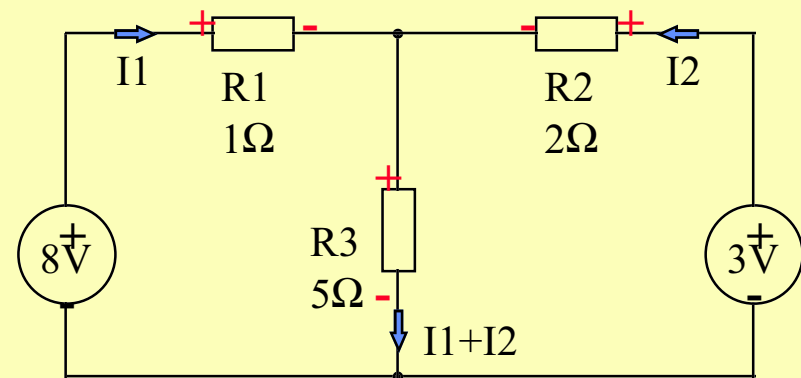
- $8\text{Volts} - (R1 \cdot I1 + R3 \cdot (I1 + I2))\text{Volts} = 0$
- $3\text{Volts} - (R2 \cdot I2 + R3 \cdot (I1 + I2))\text{Volts} = 0$
- Expand the equations:-
- $8 - (R1 \cdot I1 + R3 \cdot I1 + R3 \cdot I2) = 0$
- $3 - (R2 \cdot I2 + R3 \cdot I1 + R3 \cdot I2) = 0$
- Re-arrange the equations:-
- $R1 \cdot I1 + R3 \cdot I1 + R3 \cdot I2 = 8$
- $R2 \cdot I2 + R3 \cdot I1 + R3 \cdot I2 = 3$



Solution:

Kirchhoff.

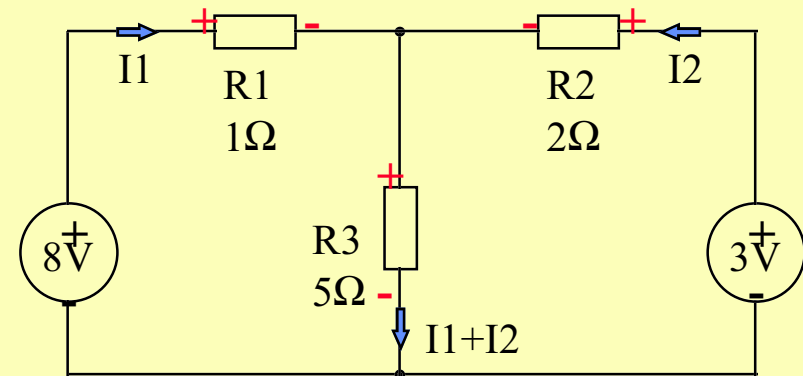
- Substitute in Resistance values:-
- $1I_1 + 5I_1 + 5I_2 = 8$
- $2I_2 + 5I_1 + 5I_2 = 3$
- Giving
- $6I_1 + 5I_2 = 8$
- $5I_1 + 7I_2 = 3$



Solution:

Kirchhoff.

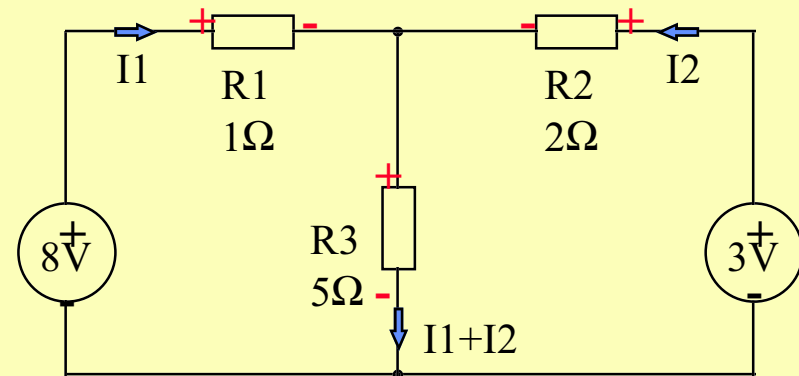
- $6I_1 + 5I_2 = 8$ (Equation "A")
- $5I_1 + 7I_2 = 3$ (Equation "B")
- Multiply Eqn A * 5 and Eqn B * 6 this gives:-
- $30I_1 + 25I_2 = 40$ (Equation "C")
- $30I_1 + 42I_2 = 18$ (Equation "D")
- Subtract Eqn "D" from Eqn "C"
- $0I_1 - 17I_2 = 22$
- Therefore
- $I_2 = -22/17$ Amps
- or $I_2 = -1.294$ Amps



Solution:

Kirchhoff.

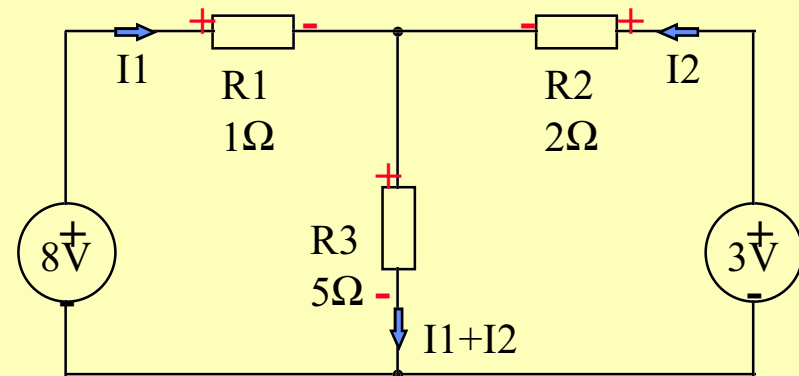
- Substitute ($I_2 = -22/17$) in Equation “A”
- $6I_1 + 5*(-22/17) = 8$ or
- $6I_1 + (-110/17) = 8$ or
- $6I_1 = 8 + (110/17)$
- $6I_1 = (8 * 17)/17 + (110/17)$
- $6I_1 = (136)/17 + (110/17)$
- $6I_1 = 136/17 + 110/17$
- $6I_1 = 246/17$
- Therefore
- $I_1 = 246/(17*6)$ Amps
- $I_1 = 246/102$ Amps
- or $I_1 = 2.411$ Amps



Solution:

Kirchhoff.

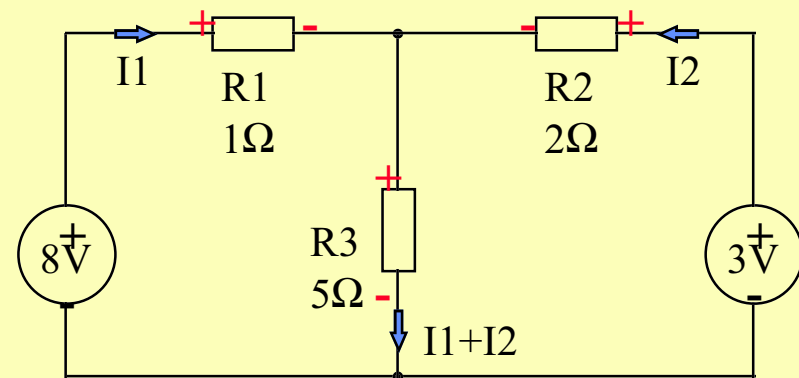- Current in R3 = $I_1 + I_2$
- $I_1 = 246/102$ Amps and $I_2 = -22/17$ Amps
- Therefore
- $IR_3 = 246/102 + (-22/17) = 246/102 - 132/102$ A
- $IR_3 = (246-132)/102 = 114/102 = 1.117$ Amps
- Voltage across R3 = $I \cdot R$ or $IR_3 * 5$
- $VR_3 = 114/102 * 5 = 570/102 = 5.588$ Volts




Solution:

Kirchhoff.

- Current in R3 = $I_1 + I_2$
- $I_1 = 246/102$ Amps and $I_2 = -22/17$ Amps
- Therefore
- $IR_3 = 246/102 + (-22/17) = 246/102 - 132/102$ A
- $IR_3 = (246-132)/102 = 114/102 = 1.117$ Amps
- Voltage across R3 = $I \cdot R$ or $IR_3 \cdot 5$
- $VR_3 = 114/102 \cdot 5 = 570/102 = 5.588$ Volts

Note:

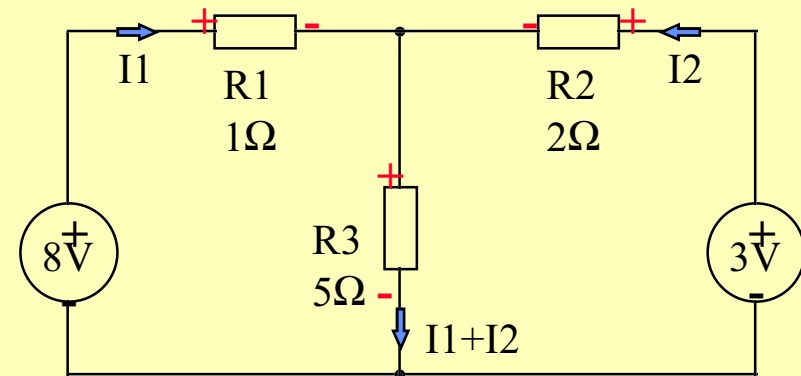
If you convert to decimals during the calculation process you will get slightly different results.



Practice:

Kirchhoff.

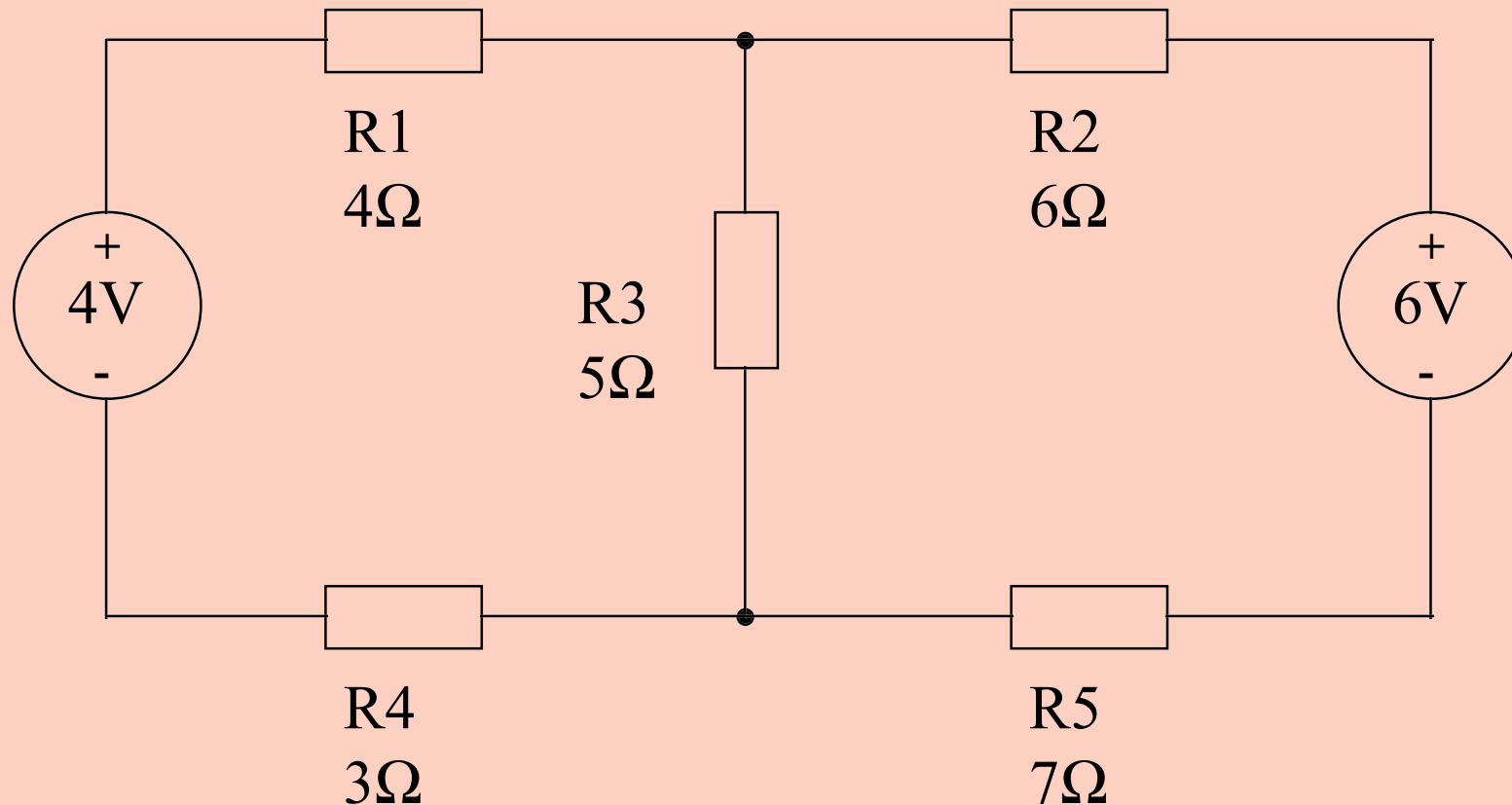
- Calculate showing all working.
 - The current flowing in R3.
 - The voltage developed across R3.



Practice:

Kirchhoff.

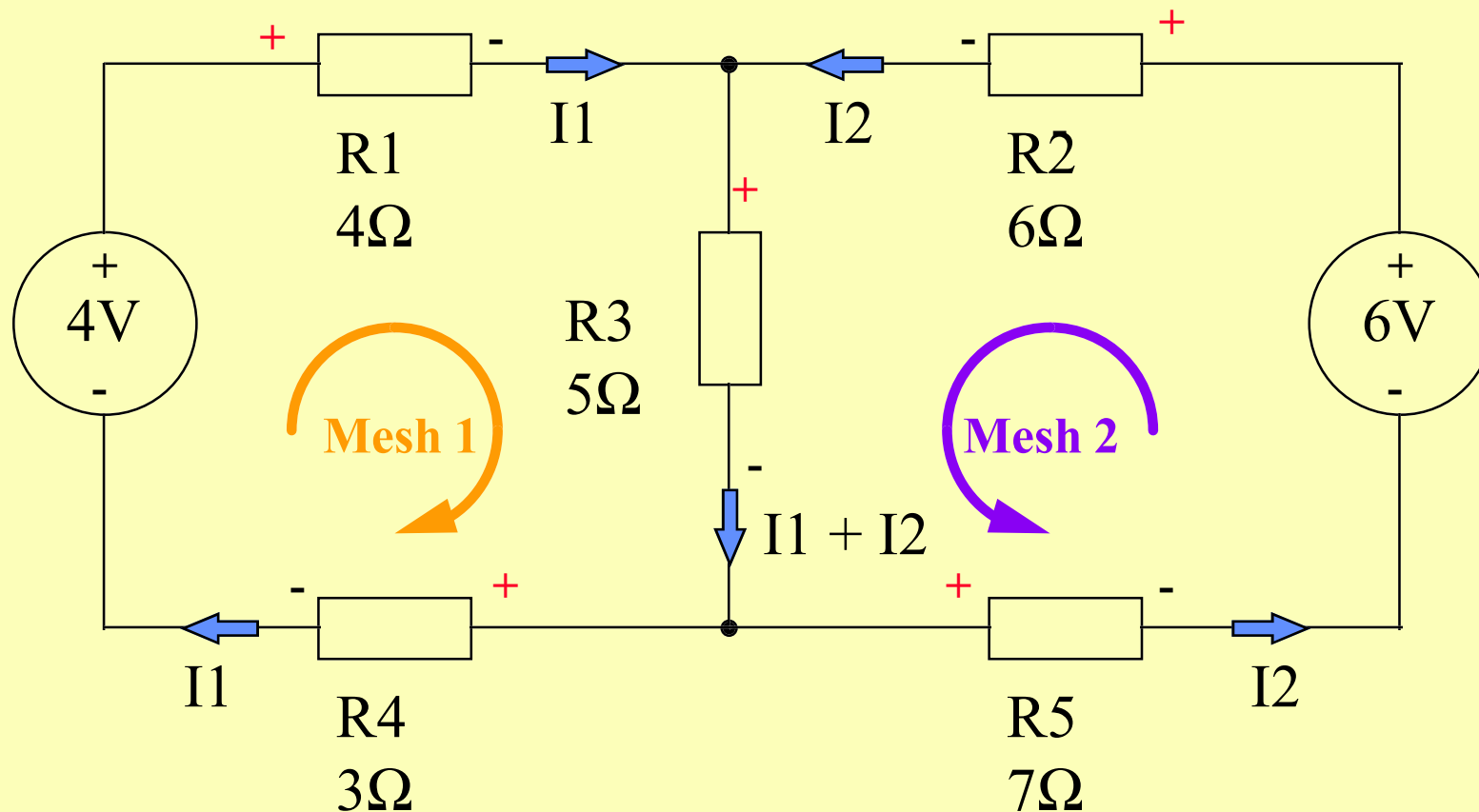
- Develop the voltage equations for Mesh 1 and Mesh 2.



Solution:

Kirchhoff.

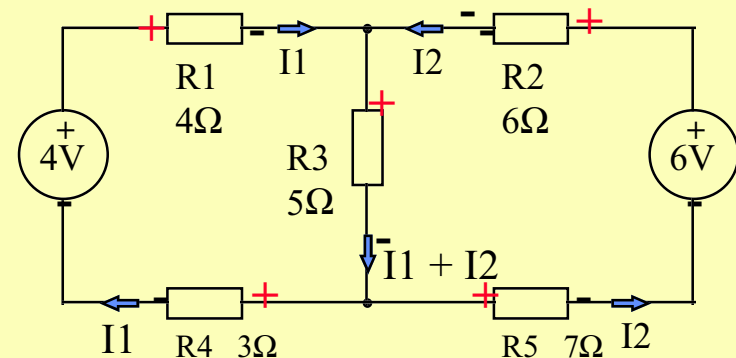
- $4\text{Volts} - (R1 * I1 + R3 * (I1 + I2) + R4 * I1) = 0$
- $6\text{Volts} - (R2 * I2 + R3 * (I1 + I2) + R5 * I2) = 0$
- Expand the equations:-
- $4 - (R1 * I1 + R3 * I1 + R3 * I2 + R4 * I1) = 0$
- $6 - (R2 * I2 + R3 * I1 + R3 * I2 + R5 * I2) = 0$
- Re-arrange the equations:-
- $4 = R1 * I1 + R3 * I1 + R3 * I2 + R4 * I1$
- $6 = R2 * I2 + R3 * I1 + R3 * I2 + R5 * I2$



Solution:

Kirchhoff.

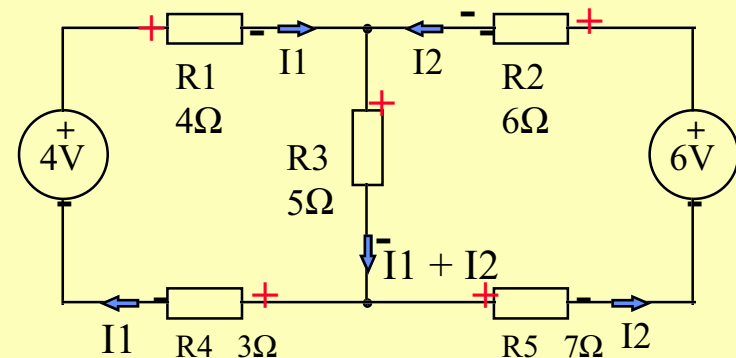
- Substitute in Resistance values:-
- $4 = 4 \cdot I_1 + 5 \cdot I_1 + 5 \cdot I_2 + 3 \cdot I_1 = 4I_1 + 5I_1 + 5I_2 + 3I_1$
- $6 = 6 \cdot I_2 + 5 \cdot I_1 + 5 \cdot I_2 + 7 \cdot I_2 = 6I_2 + 5I_1 + 5I_2 + 7I_2$
- Giving
- $4 = 12I_1 + 5I_2$
- $6 = 5I_1 + 18I_2$
- or
- $12I_1 + 5I_2 = 4$
- $5I_1 + 18I_2 = 6$



Solution:

Kirchhoff.

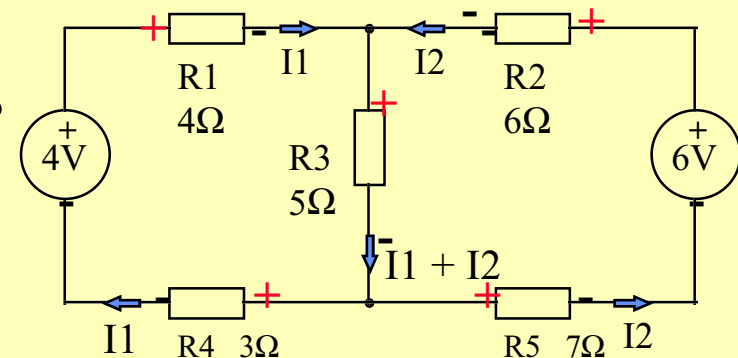
- Define the equations
- $12I_1 + 5I_2 = 4$ (Equation "A")
- $5I_1 + 18I_2 = 6$ (Equation "B")
- Multiply Eqn A * 5 and Eqn B * 12 this gives:-
- $60I_1 + 25I_2 = 20$ (Equation "C")
- $60I_1 + 216I_2 = 72$ (Equation "D")
- Subtract Eqn "D" from Eqn "C"
- $0I_1 - 191I_2 = -52$
- Therefore
- $I_2 = -52/-191$ or $52/191$ Amps
- or $I_2 = 0.272$ Amps



Solution:

Kirchhoff.

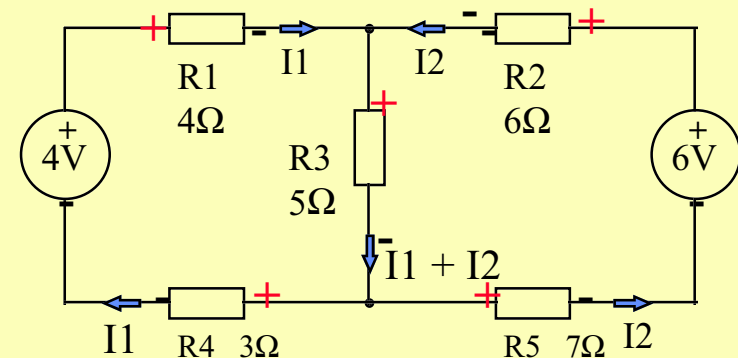
- Substitute ($I_2 = 52/191$) in Equation “A”
- $12I_1 + 5*(52/191) = 4$ or
- $12I_1 + (260/191) = 4$ or
- $12I_1 = 4 - (260/191)$
- $12I_1 = (4 * 191)/191 - (260/191)$
- $12I_1 = (764)/191 - (260/191)$
- $12I_1 = 504/191$
- Therefore
- $I_1 = 504/(191*12)$ Amps
- $I_1 = 504/2292$ Amps
- or $I_1 = 0.2198$ Amps



Solution:

Kirchhoff.

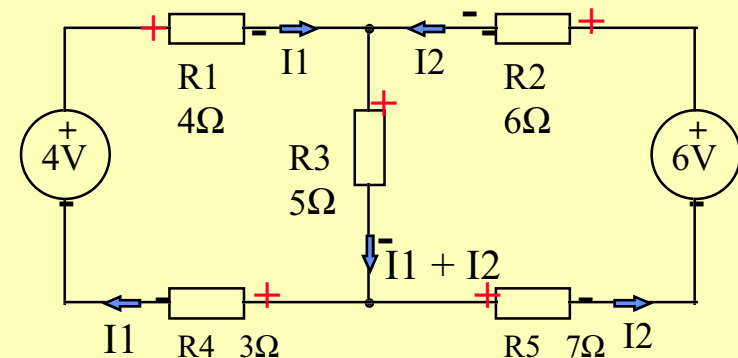
- Current in R3 = $I_1 + I_2$
- $I_1 = 504/2292$ Amps and $I_2 = 52/191$ Amps
- Therefore
- $IR_3 = 504/2292 + 52/191 = 504/2292 + 624/2292$ A
- $IR_3 = (502 + 624)/2292 = 1126/2292 = 0.4912$ Amps
- Voltage across R3 = $I * R$ or $IR_3 * 5$
- $VR_3 = 1126/2292 * 5 = 5630/2292 = 2.456$ Volts



Practice:


Kirchhoff.

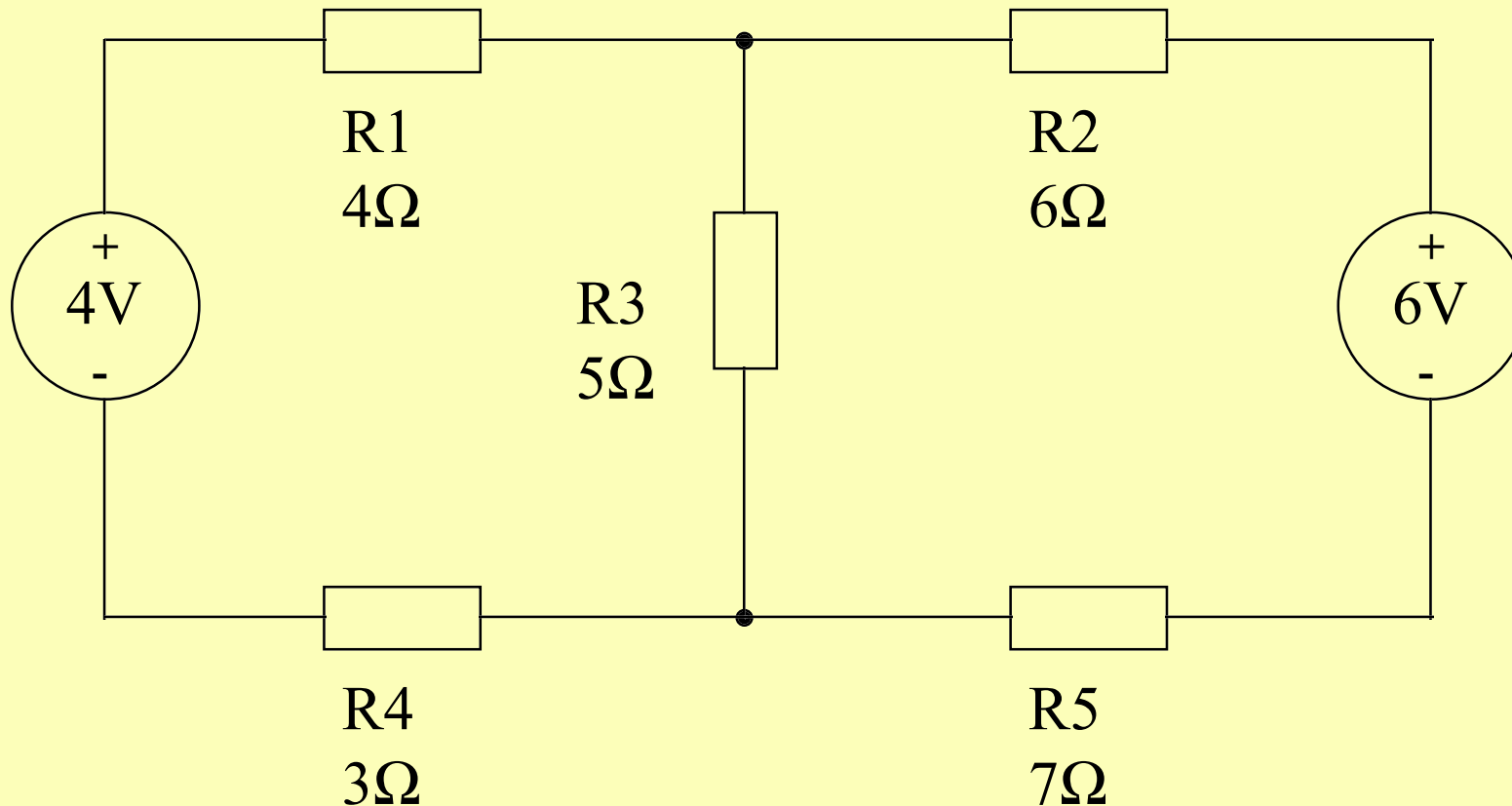- Calculate showing all working.
 - The current flowing in R3 = **0.4912Amps.**
 - The voltage developed across R3 = **2.456 Volts.**




Practice: **Using Kirchhoff.**

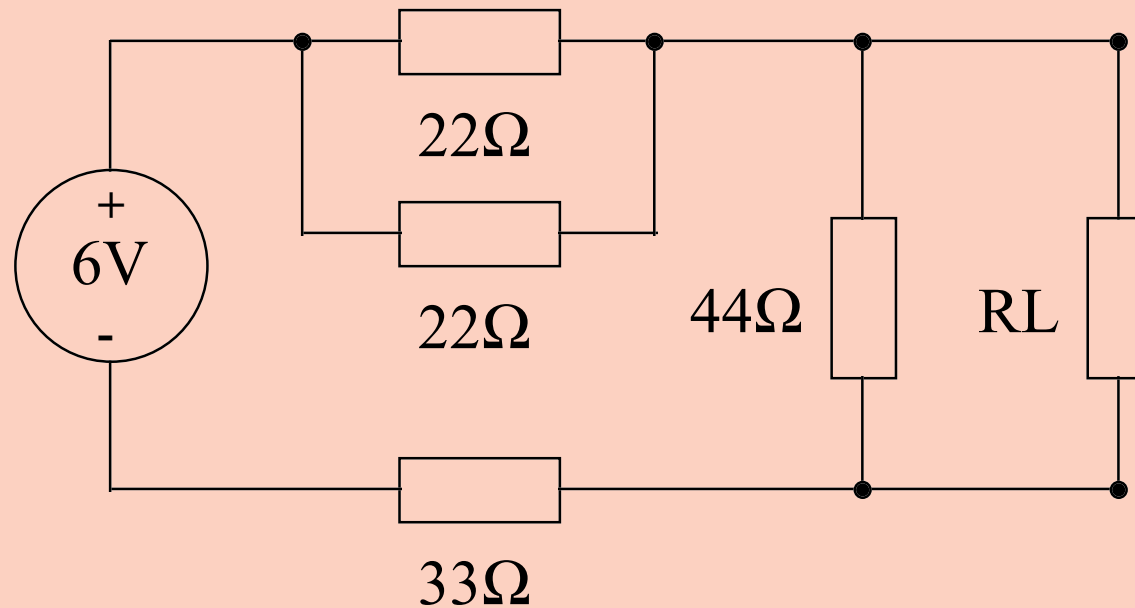- Calculate showing all working ($R_L = 11\Omega$).
 - The current flowing in R_L .
 - The voltage developed across R_L .



Practice: Using Kirchoff.

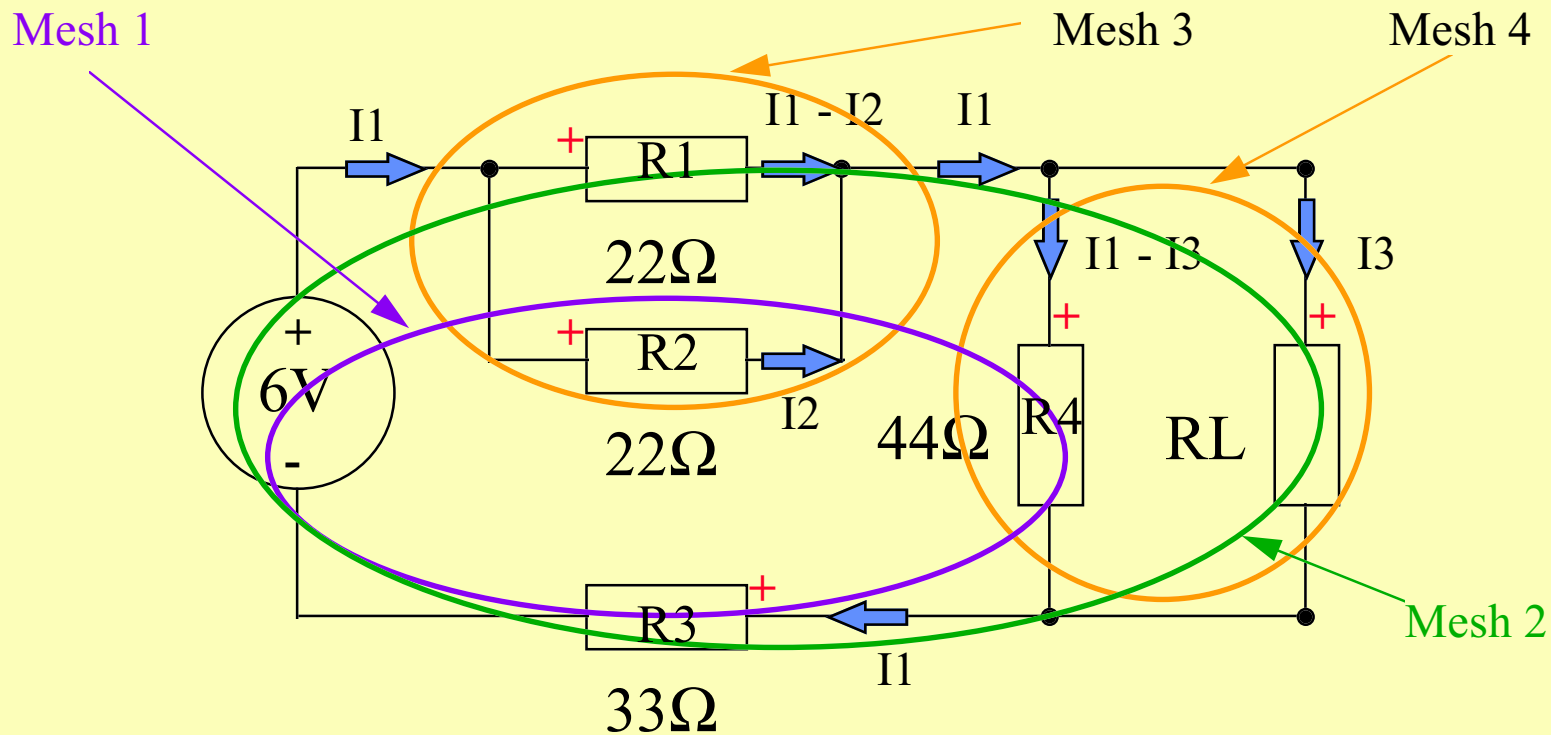- Calculate showing all working ($R_L = 11\Omega$).
 - The current flowing in R_L .
 - The voltage developed across R_L .



Solution:

Kirchhoff.

- Step 1. Identify the unique mesh circuits
- Mesh 1
- $6\text{Volts} - (R2 * I2 + R4 * (I1 - I3) + R3 * I1) = 0$
- Mesh 2
- $6\text{Volts} - (R1 * (I1 - I2) + RL * I3 + R3 * I1) = 0$
- Mesh 3
- $R2 * I2 - R1 * (I1 - I2) = 0$
- Mesh 4
- $R4 * (I1 - I3) - RL * I3 = 0$

Solution:

Kirchhoff.

- Expand the equations:-
- $6 - (R2*I2 + R4*I1 - R4*I3 + R3*I1) = 0$
- $6 - (R1*I1 - R1*I2 + RL*I3 + R3*I1) = 0$
- $R2*I2 - R1*I1 + R1*I2 = 0$
- $R4*I1 - R4*I3 - RL*I3 = 0$
- Re-arrange the equations:-
- $R4*I1 + R3*I1 + R2*I2 - R4*I3 = 6$
- $R1*I1 + R3*I1 - R1*I2 + RL*I3 = 6$
- $-R1*I1 + R2*I2 + R1*I2 = 0$
- $R4*I1 - R4*I3 - RL*I3 = 0$

Solution:

Kirchhoff.

- Substitute in Resistance values:-
- $44I_1 + 33I_1 + 22I_2 - 44I_3 = 6$
- $22I_1 + 33I_1 - 22I_2 + 11I_3 = 6$
- $-22I_1 + 22I_2 + 22I_2 = 0$
- $44I_1 - 44I_3 - 11I_3 = 0$
- Giving
- $77I_1 + 22I_2 - 44I_3 = 6$ (Eqn A)
- $55I_1 - 22I_2 + 11I_3 = 6$ (Eqn B)
- $-22I_1 + 44I_2 = 0$ (Eqn C)
- $44I_1 - 55I_3 = 0$ (Eqn D)

Solution:

Kirchhoff.

- Add Eqn A to Eqn B to give Eqn E :-
- $77I_1 + 22I_2 - 44I_3 = 6$ (Eqn A)
- $55I_1 - 22I_2 + 11I_3 = 6$ (Eqn B)
- $132I_1 - 33I_3 = 12$ (Eqn E)
- Mult Eqn D by 3 to give Eqn F :-
- $132I_1 - 33I_3 = 12$ (Eqn E)
- $132I_1 - 165I_3 = 0$ (Eqn D*3)
- and subtract gives
- $132I_3 = 12$
- Therefore $I_3 = 12/132 = 0.0909 \text{ A}$
- Voltage across RL = $RL * I_3 = 12/132 * 11 = 1 \text{ Volt}$

Solution:

Kirchhoff.

- Substitute I3 in Eqn D :-
- $44I_1 - 55I_3 = 0$ (Eqn D)
- $44I_1 - 55*(12/132) = 0$ or
- $44I_1 = 55*12/132 = 660/132$ amps
- Therefore
- $I_1 = 660/(132*44) = 660/5808 = 0.1136A$
- Substitute I1 in Eqn C :-
- $-22I_1 + 44I_2 = 0$ (Eqn C)
- $-22*(660/5808) + 44I_2 = 0$ or
- $22*(660/5808) = 44I_2 = 14520/5808$ amps
- Therefore
- $I_2 = 14520/(5808*44) = 14520/255552 = 0.0568A$


Solution:

Kirchhoff.

- Conclusion
- Current in RL = I3
- Voltage across RL = $R \cdot I = RL \cdot I3$
- $RL = 11\Omega$ and $I3 = 12/132$ Amps or = 0.0909 A
- Therefore
- Voltage across RL = $12/132 * 11 = 1$ Volt


Practice: **Using Kirchoff.**

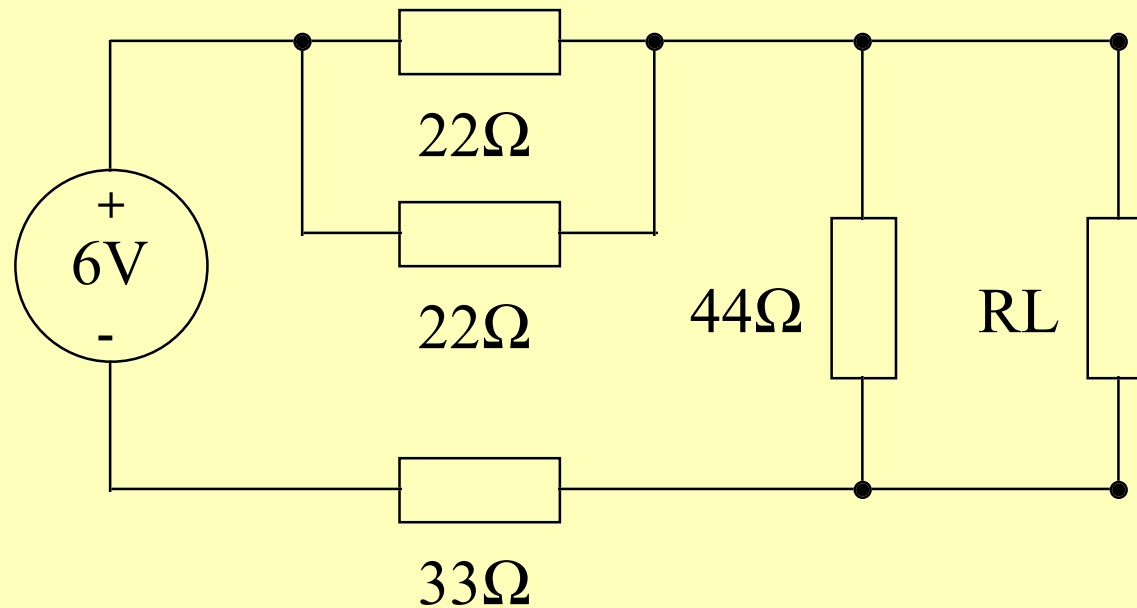- Calculate showing all working ($R_L = 11\Omega$).
 - The current flowing in R_L . (12/132 Amps)
 - The voltage developed across R_L . (1 volt)




Circuit Analysis Symbols

Circuit Analysis.

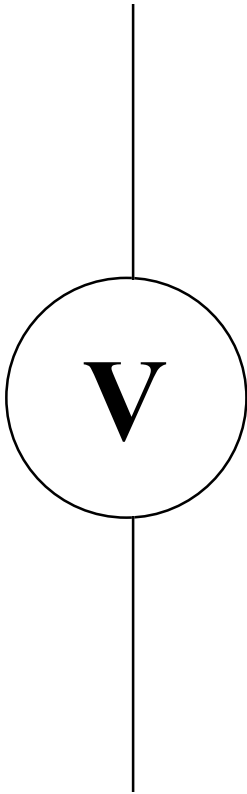


The Voltage Source

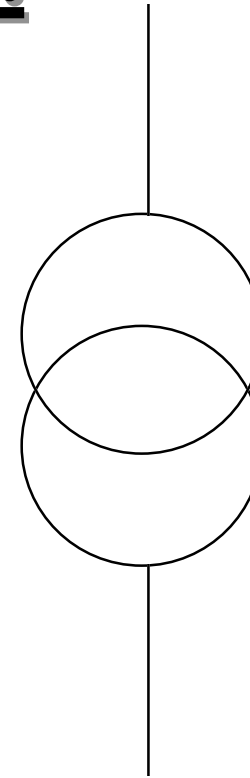

The Constant
Current Source

Symbols used to assist with the analysis of circuits.

Circuit Analysis.

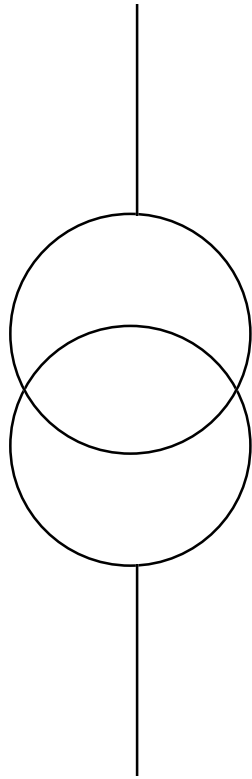


The Constant
Current Source

When you use a Current source in a calculation it is acceptable to assume that it has Infinite resistance.

A Current Source is therefore treated as an Open Circuit.

Symbols used to assist with the analysis of circuits.

Circuit Analysis.

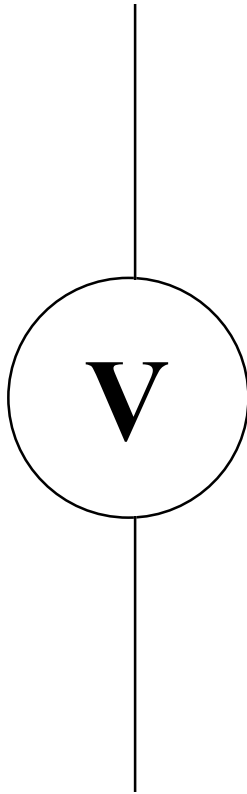

The Voltage Source

When you use a Voltage source in a calculation it is acceptable to assume that it has NO resistance.


A Voltage Source is therefore treated as a SHORT Circuit.

Symbols used to assist with the analysis of circuits.

Resistance Evaluation


Resistance Evaluation.

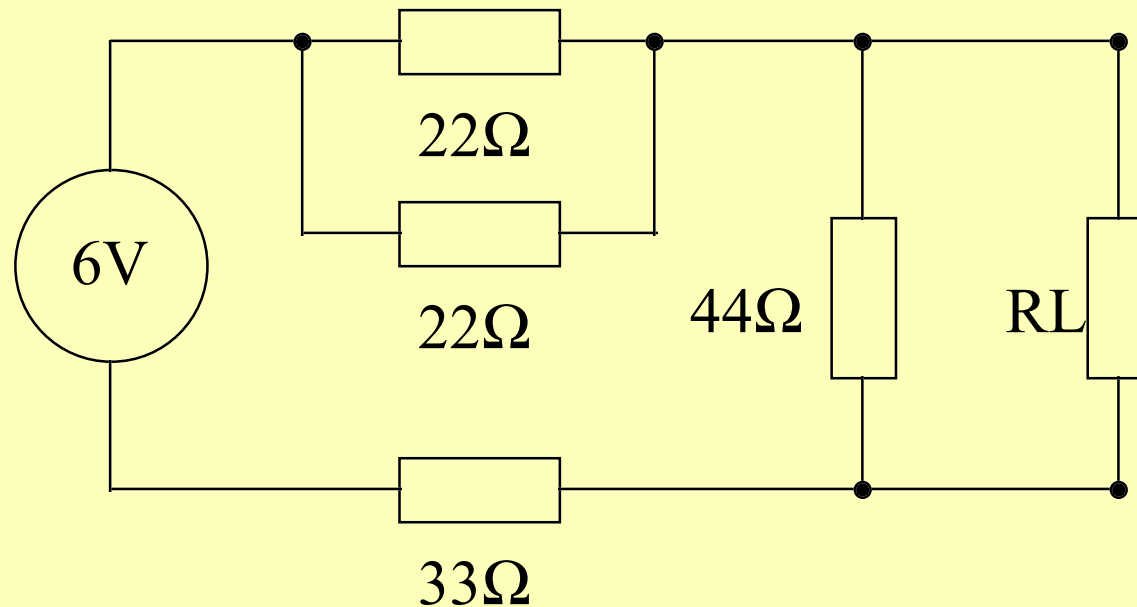- Calculation exercise:
- Assume $R_L = 11\Omega$ then
 - Calculate the Current through R_L .
 - Calculate the Voltage across R_L .




Resistance Evaluation.

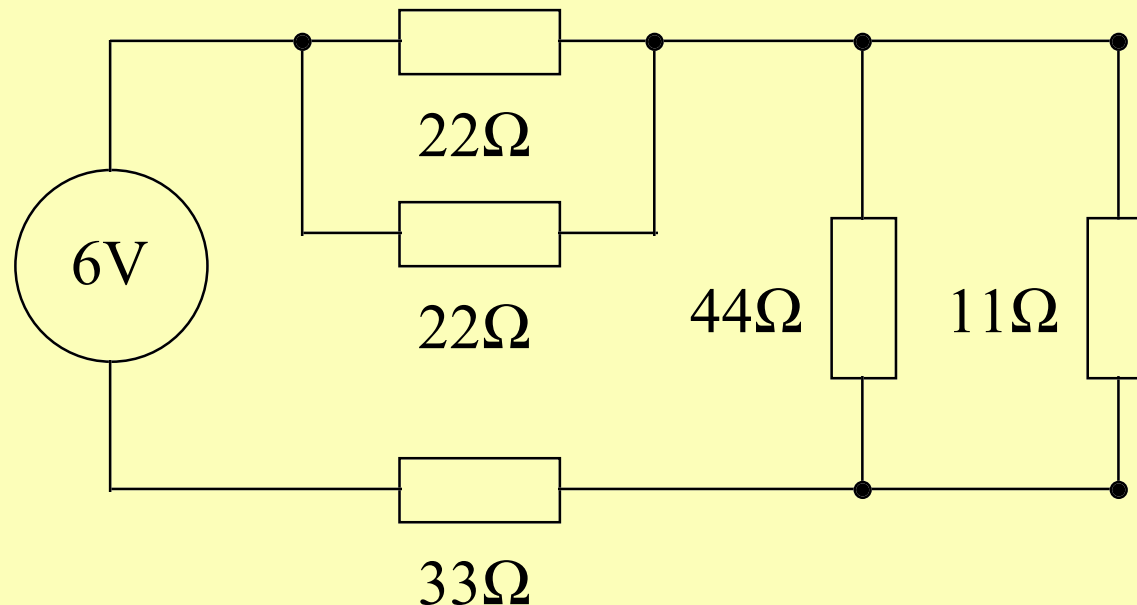- $R_{cct} = (22 \parallel 22) + (44 \parallel 11) + 33$
- $R_{cct} = (22 * 22 / (22 + 22)) + (44 * 11 / (44 + 11)) + 33$
- $R_{cct} = (11) + (8.8) + 33 = 52.8 \Omega$
- $I_{cct} = V/R = 6/52.8 = 0.1136A$
- V across RL section = $I * R = 6/52.8 * 8.8 = 1 \text{ Volt}$
- I through RL = $V/R = 1/11 = 0.09 \text{ Amps}$



Norton

Norton.

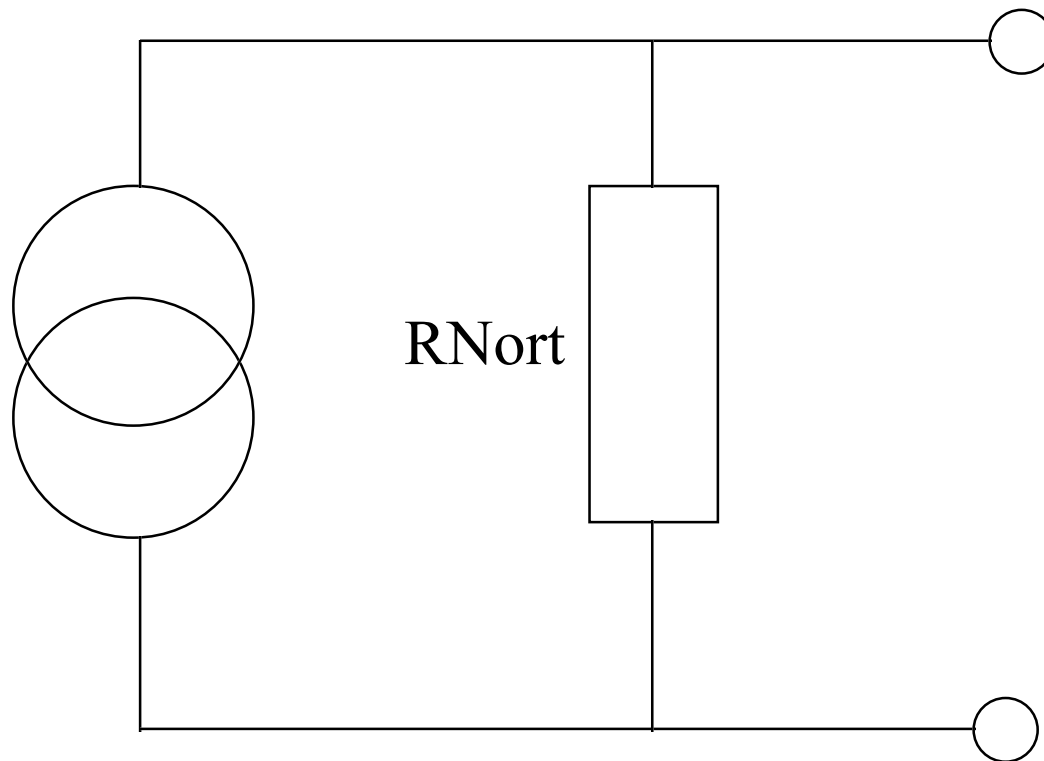

The Norton equivalent Circuit.


Norton.

- The Norton Process:
- Replace the load of the circuit you want to find its Norton equivalent with a **Short Circuit**.
- Determine the Current through the terminal points where the load was connected (I_{Nort}).
- Determine the Resistance looking into the terminal points where the load was connected (R_{Nort}).
(Replace all voltage sources with a short circuit)
(Replace all current sources with an open circuit)
- Redraw circuit using the calculated I_{Nort} and R_{Nort} to replace the original circuit.

Example:

Norton.

- Calculate the Norton equivalent for the circuit shown below.
- $R_L = 11\Omega$: Calculate the Current through R_L :-
 - using the Norton equivalent circuit.
 - using circuit below.

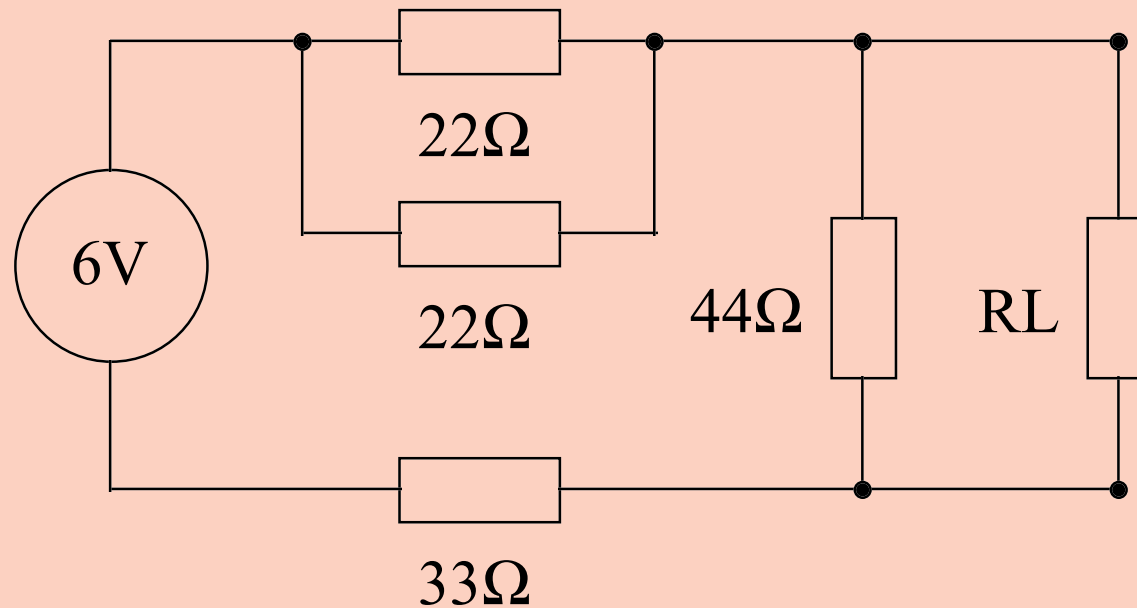


Part 1:

Norton.

- Calculate $R_{Nort} = (22!22 + 33) ! 44$
- first part $22!22 = 22*22/(22+22) = 11\Omega$
- second part $(22!22 + 33) = (11 + 33) = 44\Omega$
- overall $44!44 = 44*44/(44+44) = 22\Omega$

! = In Parallel


+ = In Series

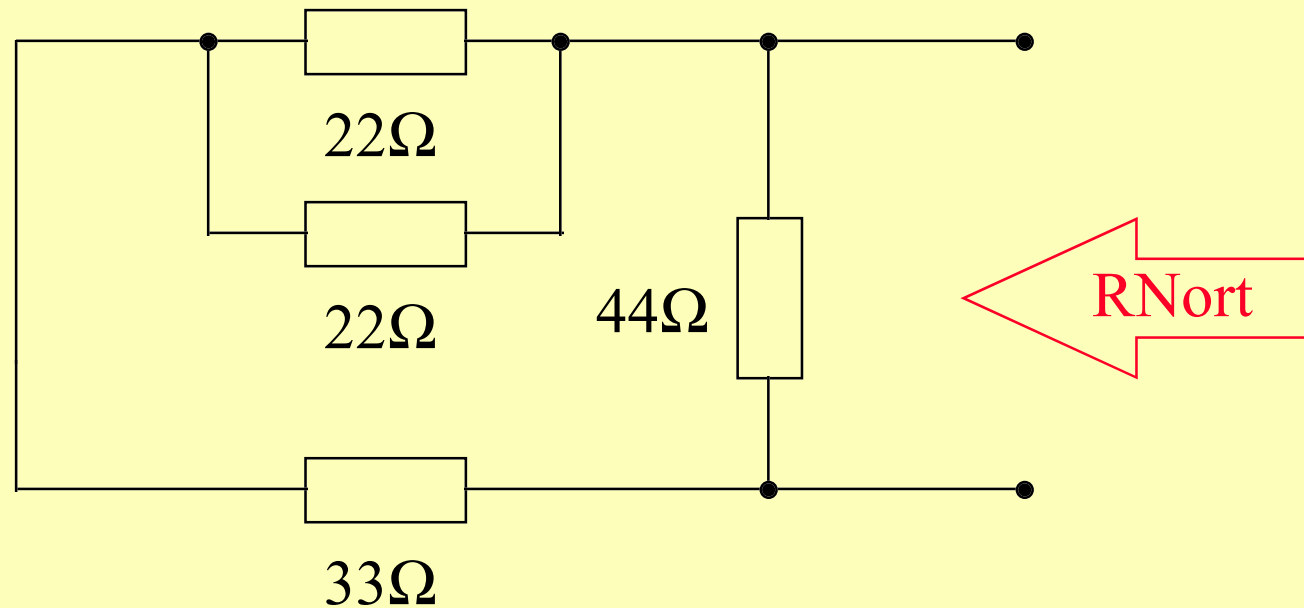

Part 1:

Norton.


- Calculate $R_{cct} = (22 \parallel 22 + 33)$
- first part $22 \parallel 22 = 22 * 22 / (22 + 22) = 11 \Omega$
- overall $(22 \parallel 22 + 33) = (11 + 33) = 44 \Omega$
- Circuit Current $I = V/R = 6/44$ Amps
- $I_{Nort} = 6/44$ Amps

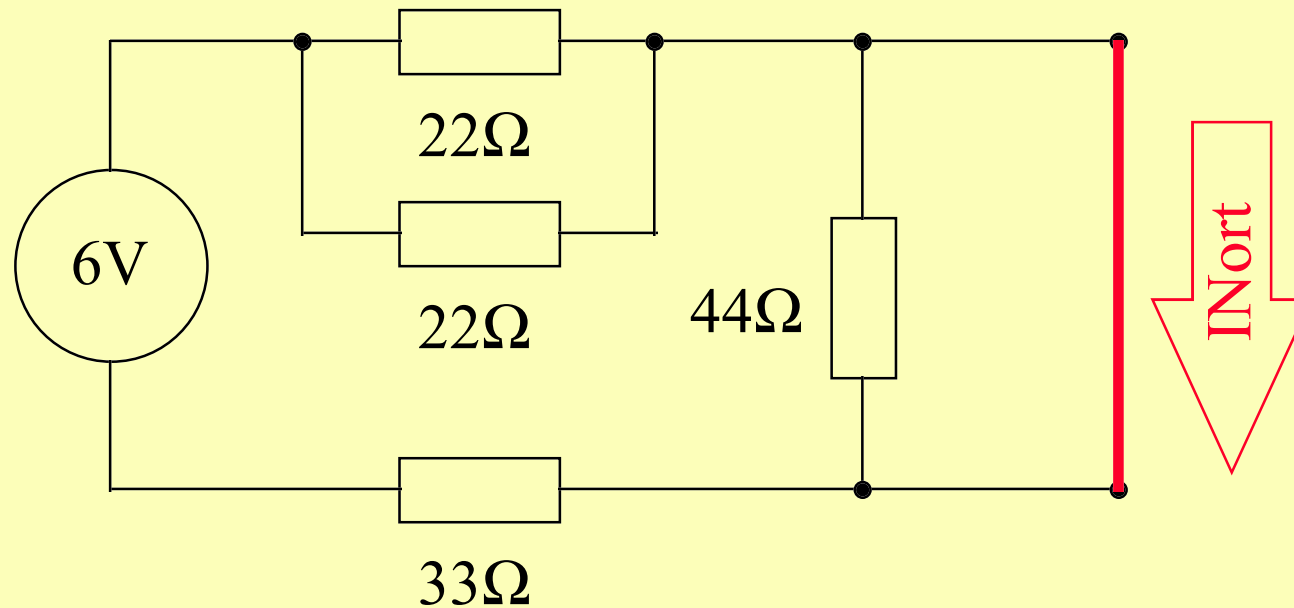

Part 1:

Norton.


- Equivalent Norton Circuit
- $R_{Nort} = 22\Omega$
- $I_{Nort} = 6/44$ or 0.136 Amps

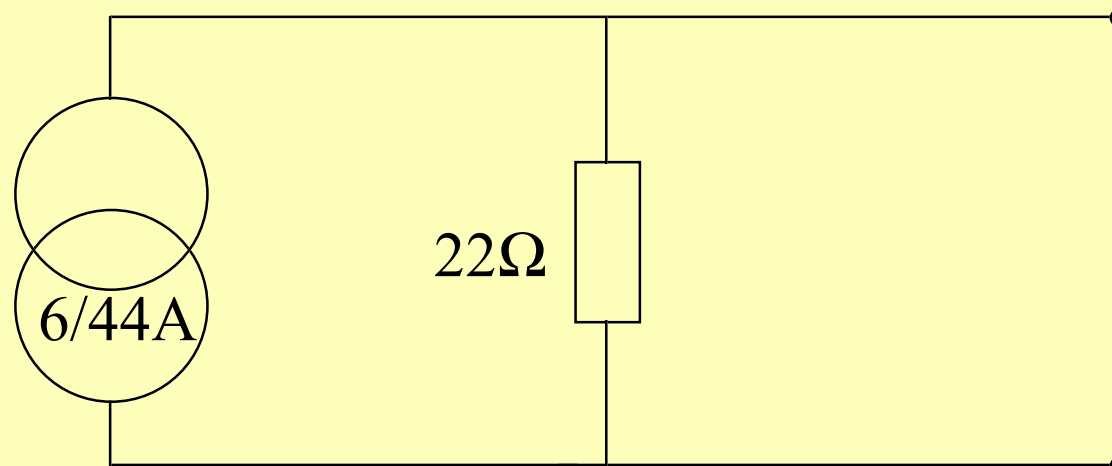

Part 2:

Norton.


- Re-connect the load to the equivalent circuit.

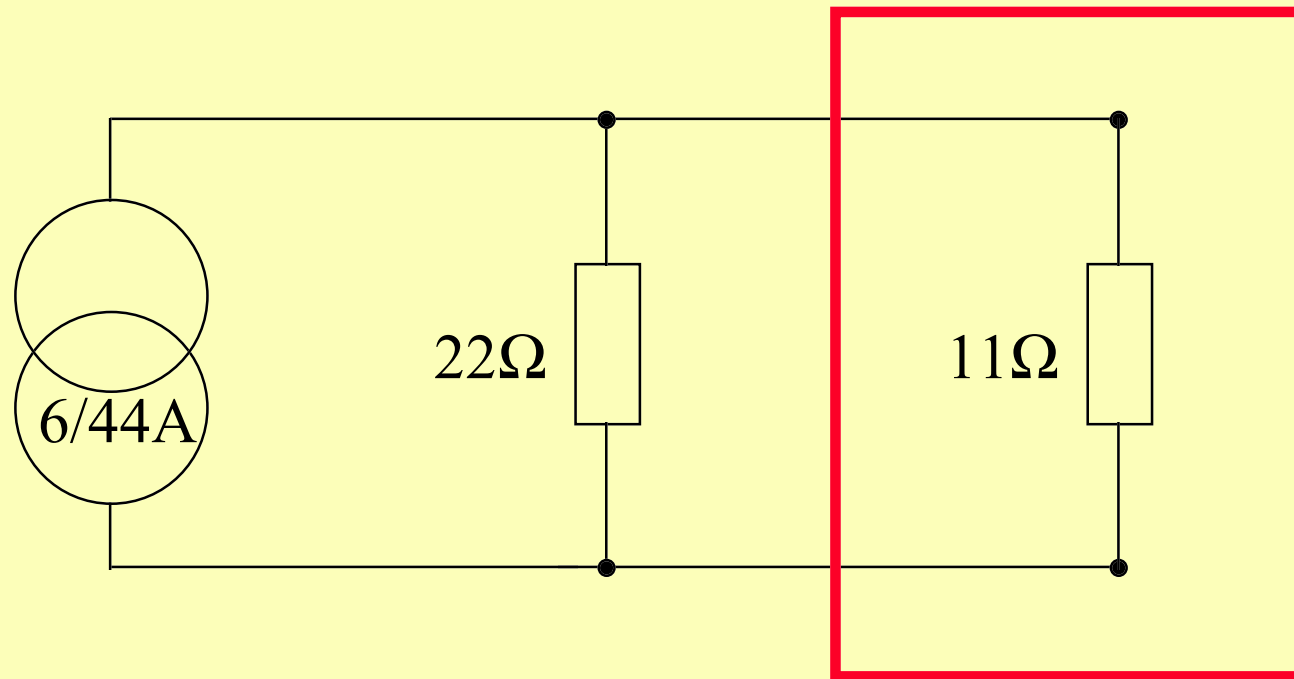

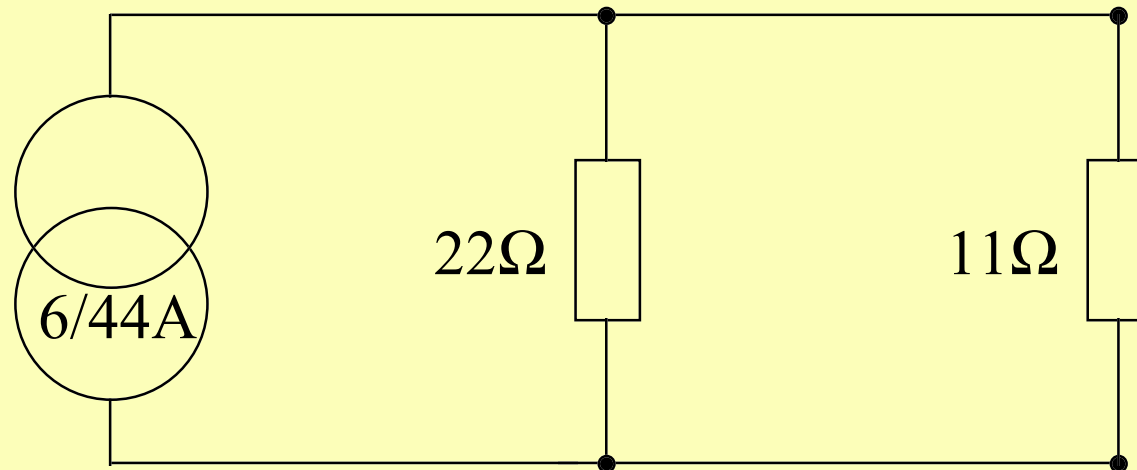Part 2:


Norton.

- $R_{cct} = 22 \parallel 11 = 22 * 11 / (22 + 11) = 242 / 33 \Omega$
- $V_{cct} = I * R = 6 / 44 * 242 / 33 = 1$ Volts
- Current through $R_L = V / R_L = 1 / 11 = 0.09$ Amps



Thevenin


Thevenin.

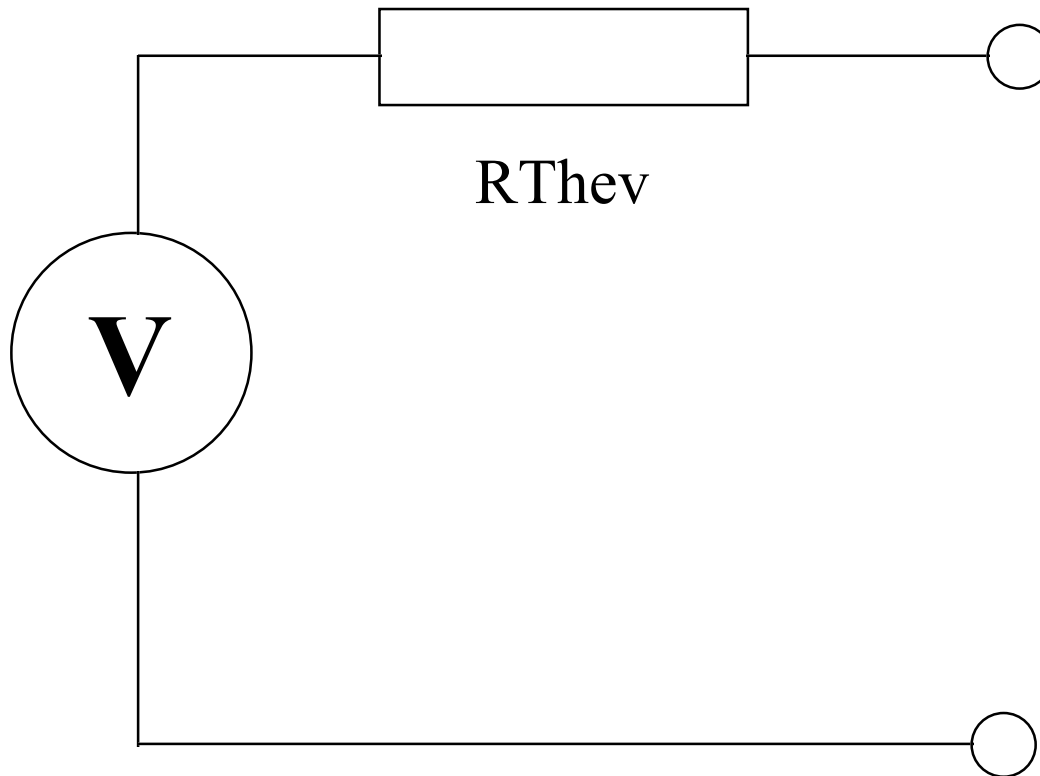

The Thevenin equivalent Circuit.

Thevenin.

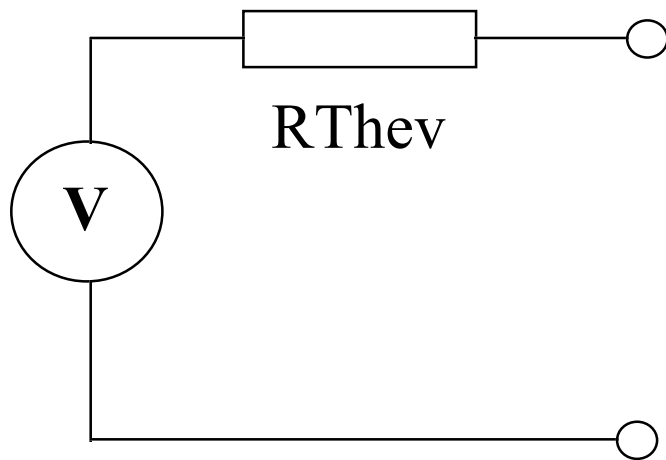Question: Why does a car battery become less effective on a very cold day ?



Answer:

The internal resistance of the battery becomes higher due to low temperature.


Starting Solutions:

Add Charge or or Warm battery.


The Thevenin equivalent Circuit or a Car battery.

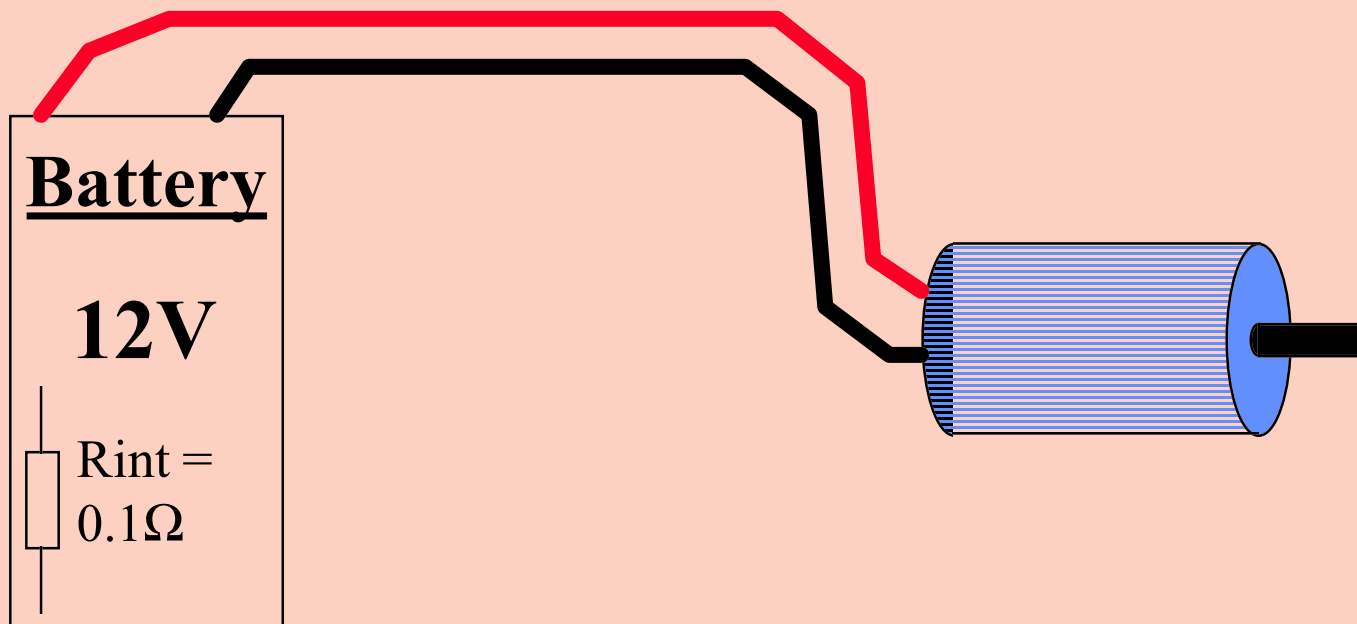Example:- **Thevenin.**

- The starter motor needs 110Amps to turn the engine. What voltage will appear across the Battery terminals.



Example:- **Thevenin.**

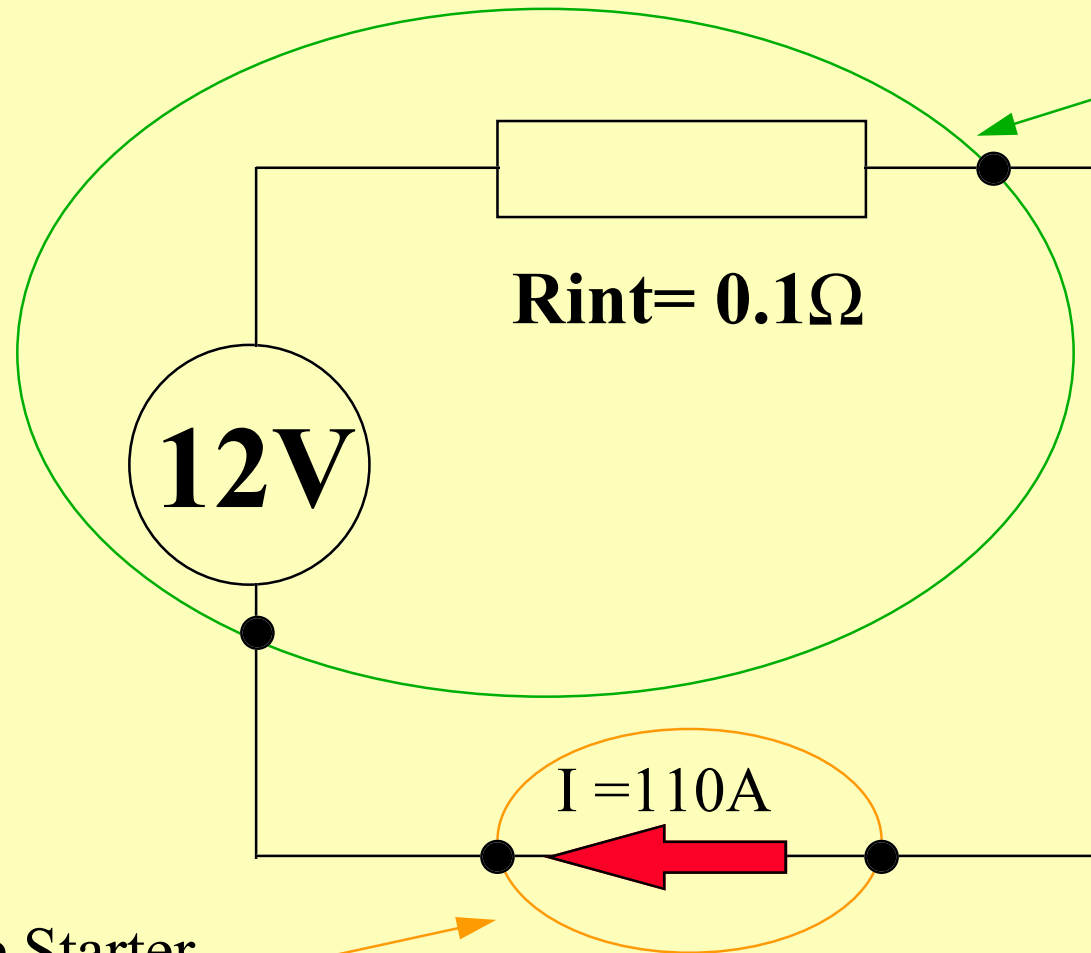

The Battery

Voltage Drop
across R_{int} is V_{int} .

$$V_{int} = IR$$

$$V_{int} = 0.1 * 110$$

$$V_{int} = 11 \text{ Volts}$$


Voltage across the
Battery terminals =
 $12V - 11V = 1V$

The Starter
Motor

Application of the Thevenin equivalent Circuit.


Thevenin.

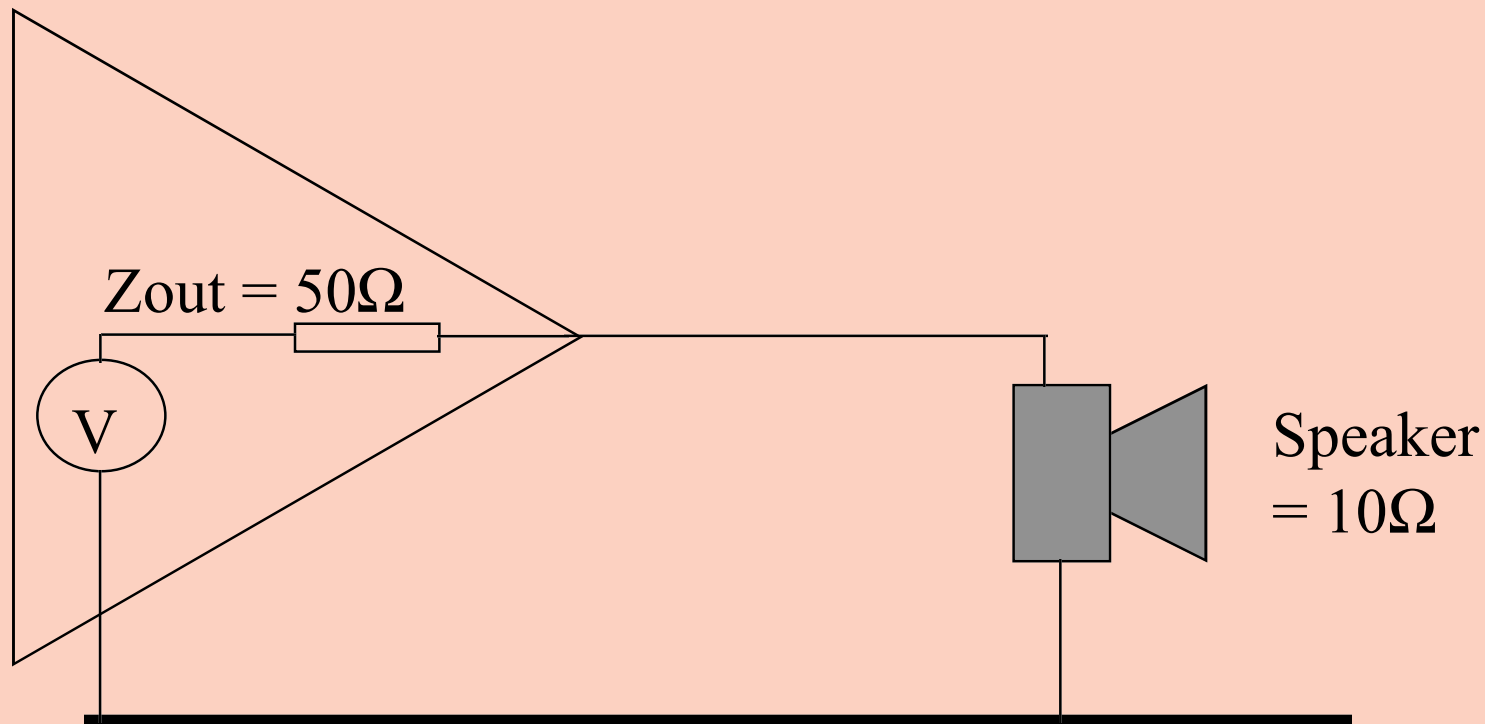- The Amplifier generates a 6 volt signal and it is connected to a 10Ω speaker. How much power is developed by the speaker.




Thevenin.

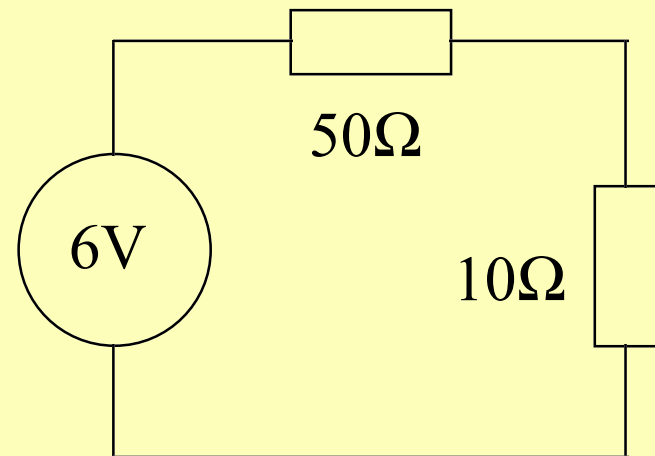- Total circuit resistance = $50\Omega + 10\Omega = 60\Omega$
- Current in circuit $I = V/R = 6/60 = 0.1\text{Amps}$
- Power in speaker = $I^2R = (0.1 * 0.1)\text{A} * 10\Omega = 0.1\text{Watts}$ or 100mW




Thevenin.

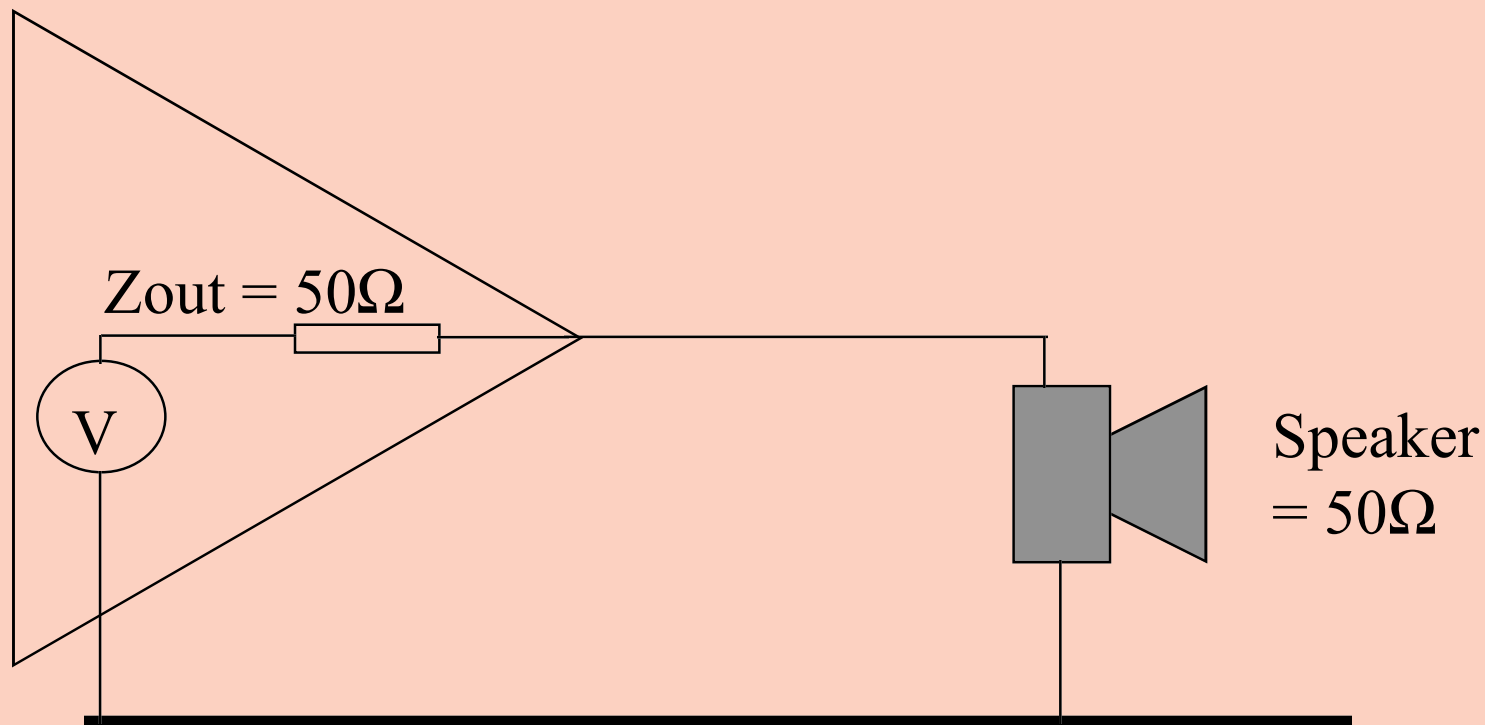- The Amplifier generates a 6 volt signal and it is connected to a 50Ω speaker. How much power is developed by the speaker.




Thevenin.

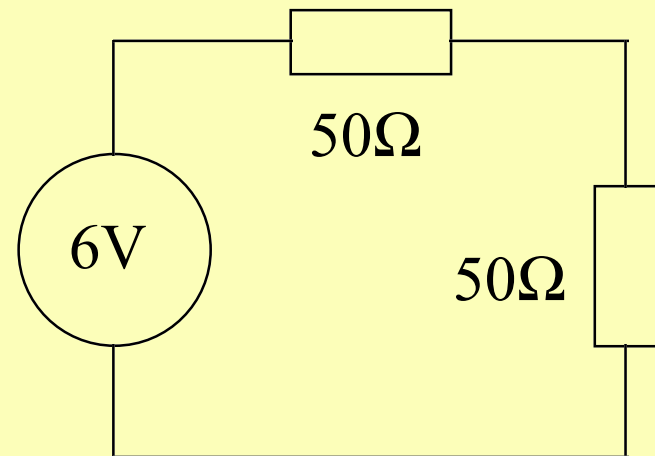- Total circuit resistance = $50\Omega + 50\Omega = 100\Omega$
- Current in circuit $I = V/R = 6/100 = 0.06\text{Amps}$
- Power in speaker = $I^2R = (0.06 * 0.06)\text{A} * 50\Omega = 0.18\text{Watts}$ or 180mW




Thevenin.

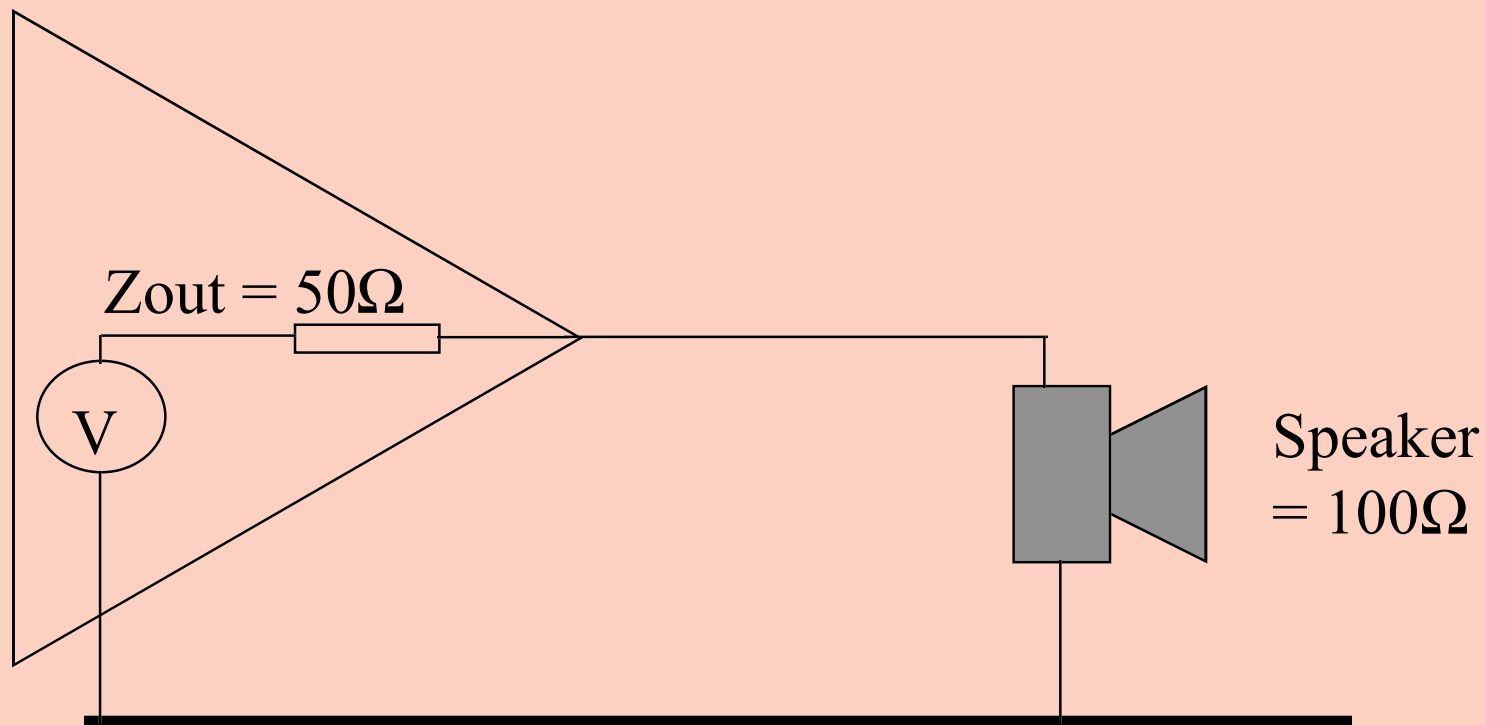- The Amplifier generates a 6 volt signal and it is connected to a 100Ω speaker. How much power is developed by the speaker.



Thevenin.

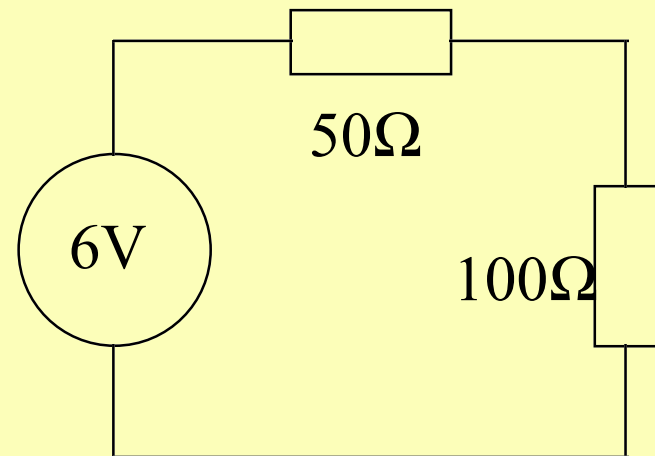- Total circuit resistance = $50\Omega + 100\Omega = 150\Omega$
- Current in circuit $I = V/R = 6/150 = 0.04\text{Amps}$
- Power in speaker = $I^2R = (0.04 * 0.04)\text{A} * 100\Omega = 0.16\text{Watts}$ or 160mW



Thevenin.

**What have you
Observed from
last 3 sets of
calculations?**

Thevenin.

Source Impedance Less than Sink Impedance.

- Source Impedance = 50Ω , Sink Impedance = 10Ω
- Output power Power in speaker = 100mW .

Source Impedance Same as Sink Impedance.

- Source Impedance = 50Ω , Sink Impedance = 50Ω
- Output power Power in speaker = 180mW .

Source Impedance More than Sink Impedance.

- Source Impedance = 50Ω , Sink Impedance = 100Ω
- Output power Power in speaker = 160mW .

Thevenin.

Maximum Power

Transfer occurs when

**Output Impedance
matches**

Input Impedance


Thevenin.

- The Thevenin Process:
- Remove the load from the circuit you want to find its Thevenin equivalent (**Terminals Open Circuit**).
- Determine the Voltage across the terminal points where the load was connected (V_{Thev}).
- Determine the Resistance looking into the terminal points where the load was connected (R_{Thev}).
(Replace all voltage sources with a short circuit)
(Replace all current sources with an open circuit)
- Redraw circuit using the calculated V_{Thev} and R_{Thev} to replace the original circuit.

Example:

Thevenin.

- Calculate the Thevenin equivalent for the circuit shown below.
- $R_L = 11\Omega$: Calculate the Voltage across R_L :-
 - using the Thevenin equivalent circuit.
 - using circuit below.

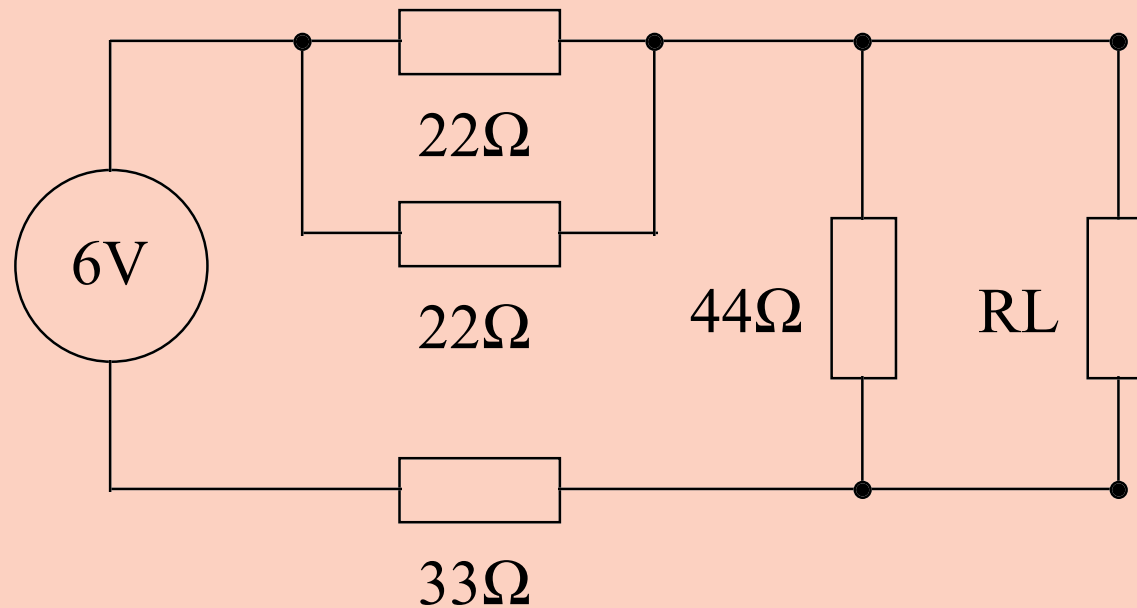


Part 1:

Thevenin.

- Calculate $R_{Thev} = (22!22 + 33) ! 44$
- first part $22!22 = 22*22/(22+22) = 11\Omega$
- second part $(22!22 + 33) = (11 + 33) = 44\Omega$
- overall $44!44 = 44*44/(44+44) = 22\Omega$

! = In Parallel


+ = In Series

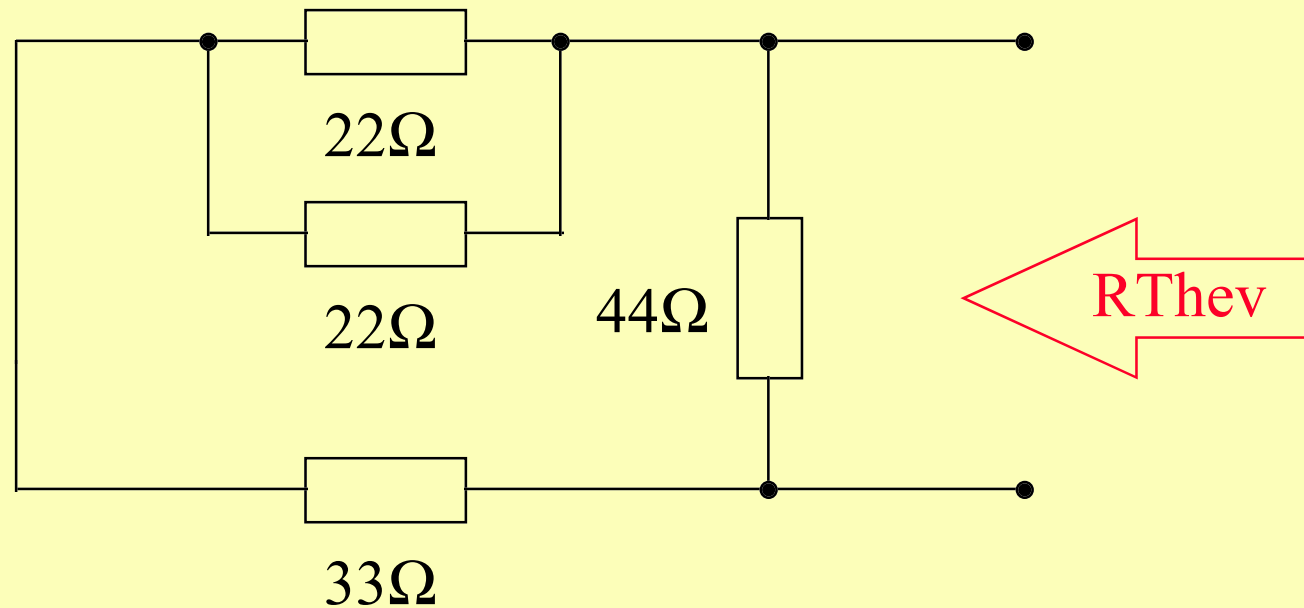

Part 1:

Thevenin.


- Calculate $R_{cct} = (22 \parallel 22 + 44 + 33)$
- first part $22 \parallel 22 = 22 * 22 / (22 + 22) = 11 \Omega$
- overall $(22 \parallel 22 + 44 + 33) = (11 + 44 + 33) = 88 \Omega$
- Circuit Current $I = V/R = 6/88$
- $V_{Thev} = I * R = 6/88 * 44 = 3 \text{ Volts}$

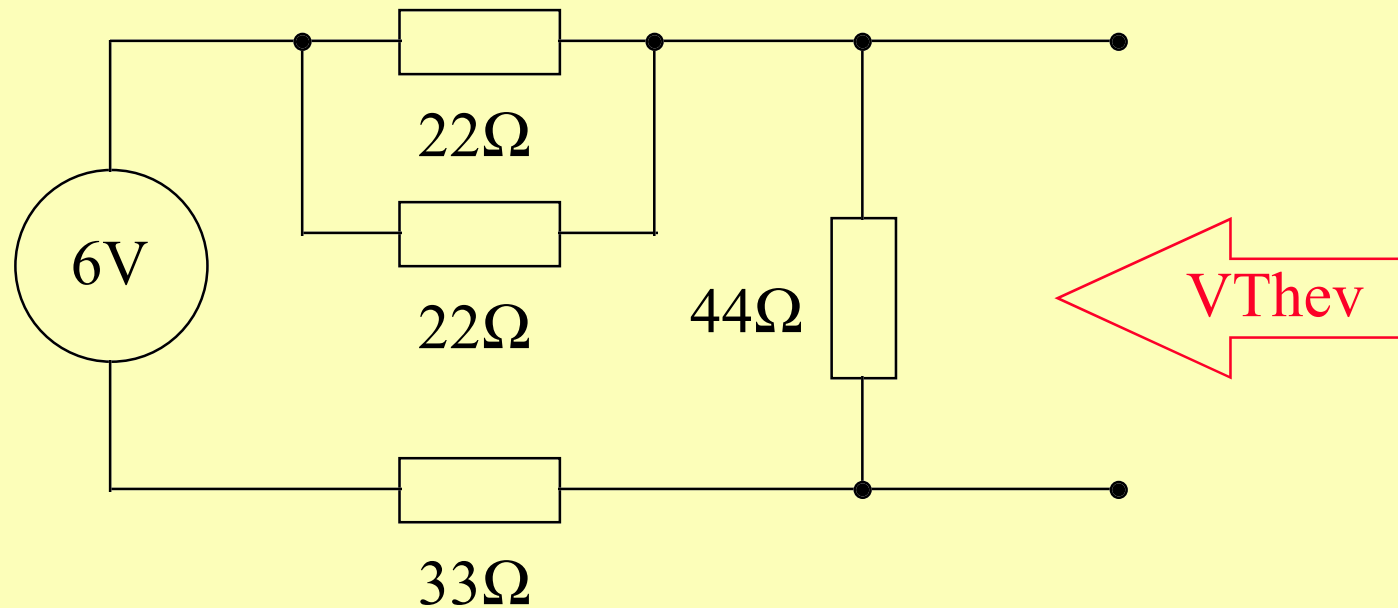

Part 1:

Thevenin.


- Equivalent Thevenin Circuit
- $R_{Thev} = 22\Omega$
- $V_{Thev} = 3\text{Volts}$

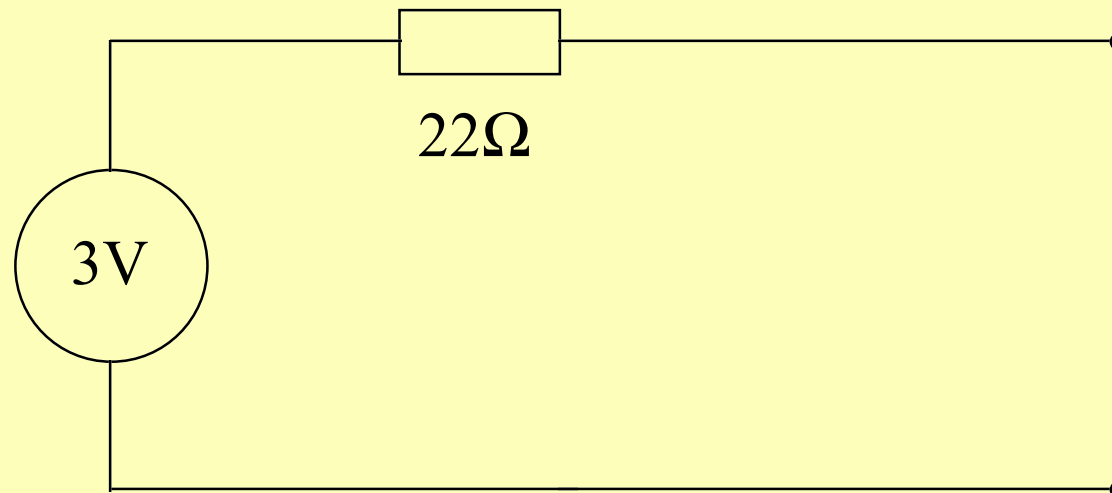

Part 2:

Thevenin.


- $R_{cct} = 22 + 11 = 33\Omega$
- $I_{cct} = V/R = 3/33$
- $V \text{ across } R_L = I * R_L = 3/33 * 11 = 1 \text{ Volt}$

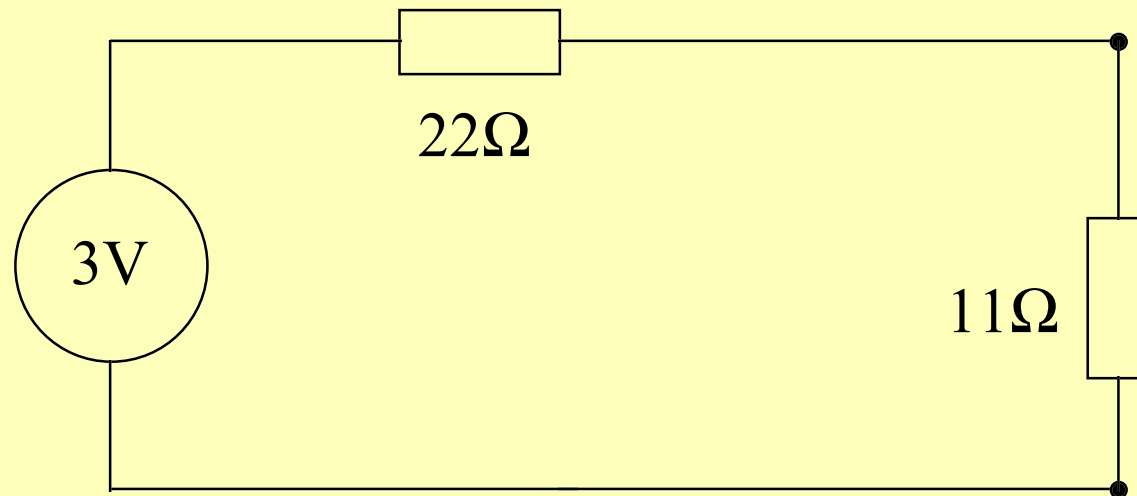

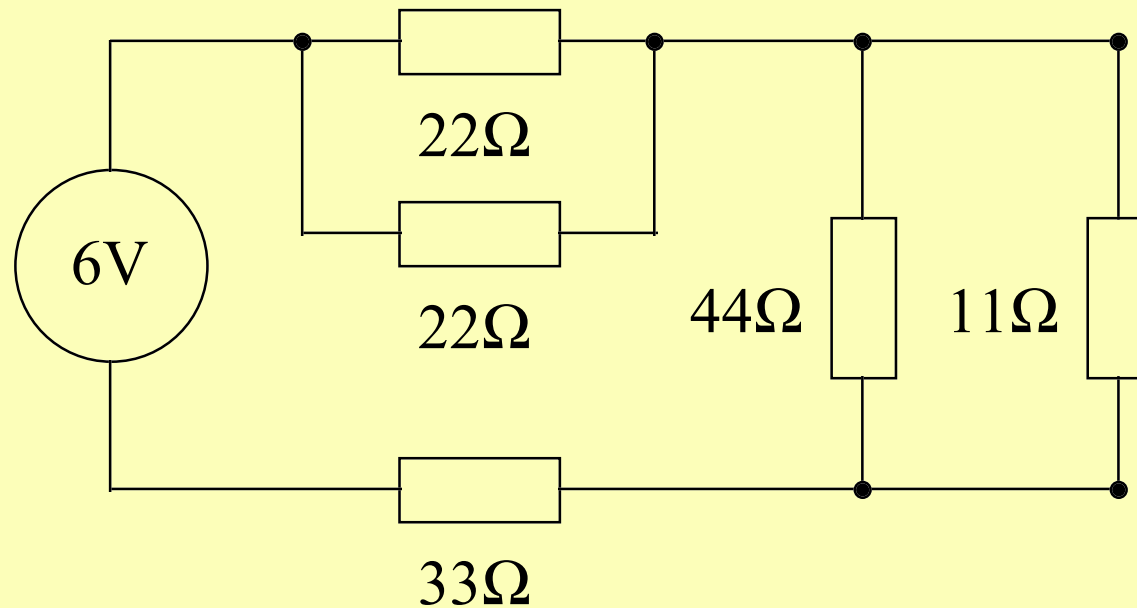Part 3:

Thevenin.

- $R_{cct} = (22 \parallel 22) + (44 \parallel 11) + 33$
- $R_{cct} = (22 * 22 / (22 + 22)) + (44 * 11 / (44 + 11)) + 33$
- $R_{cct} = (11) + (8.8) + 33 = 52.8 \Omega$
- $I_{cct} = V/R = 6/52.8$
- $V \text{ across RL section} = I * R = 6/52.8 * 8.8 = 1 \text{ Volt}$



Norton and Thevenin Conversions

Norton and Thevenin Conversions.

- Convert a Norton Circuit to a Thevenin Circuit:
- As $R_{Nort} = R_{Thev}$ therefore no conversion needed.
- Calculate V_{Thev} from I_{Nort} Process:
- Calculate voltage across R_{Nort} using I_{Nort} using the calculation $V_{Thev} = I_{Nort} * R_{Nort}$
- Redraw circuit using the newly calculated values to replace the original circuit.


Norton and Thevenin Conversions.

- Convert a Thevenin Circuit to a Norton Circuit:
- As $R_{Nort} = R_{Thev}$ therefore no conversion needed.
- Calculate I_{Nort} from V_{Thev} Process:
- Short out the terminals of Thevenin circuit
- Calculate current through R_{Thev} using V_{Thev} using the calculation $I_{Nort} = V_{Thev} / R_{Nort}$
- Redraw circuit using the newly calculated values to replace the original circuit.

Norton and Thevenin Calculations

Norton and Thevenin Calculations.

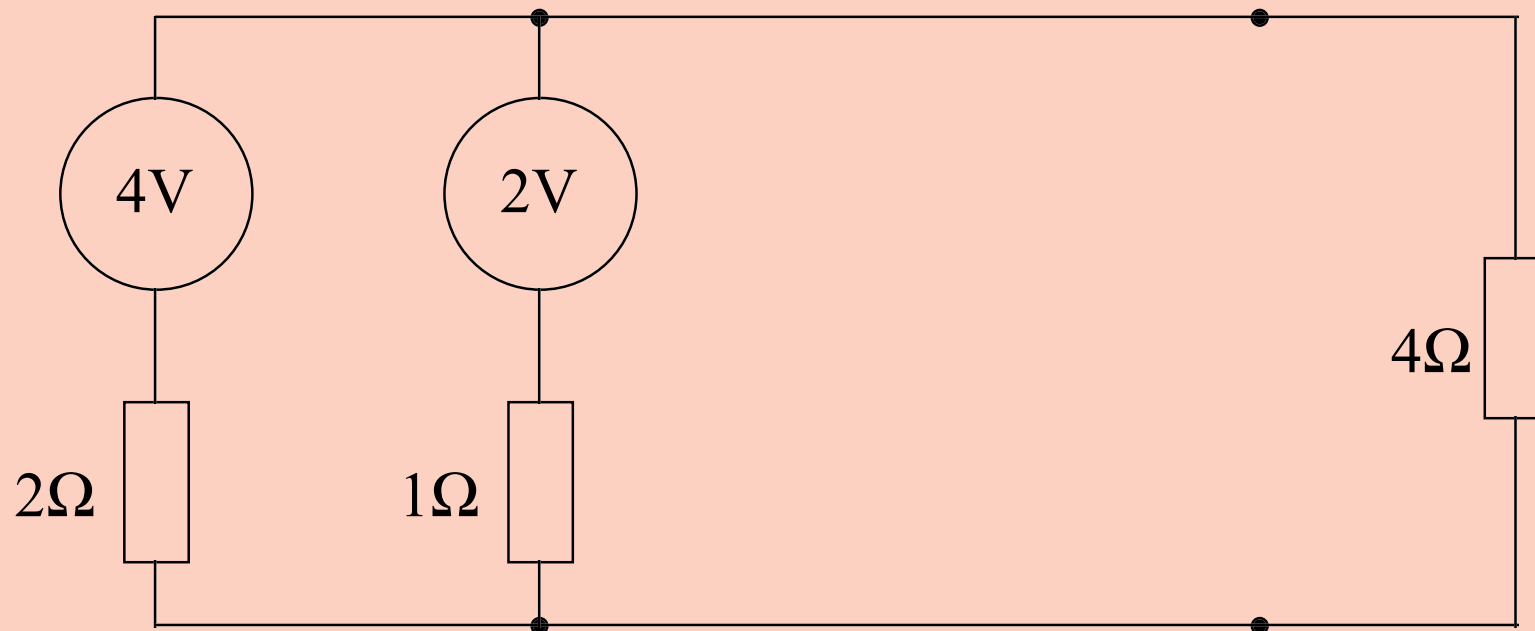
- The circuit shown below shows a 4Ω Resistor supplied by two generators with internal resistance's shown.
 - (a) Use Norton Theorem to determine the value of current in the 4Ω Resistor
 - b) Calculate the internal voltage drop in each generator.



Norton and Thevenin Calculations.

- Step 1. Short out load
- $I_{Nort} = I_1 + I_2$ and $I = V/R = 2/1 + 4/2 = 2 + 2 = 4A$


Generator 1

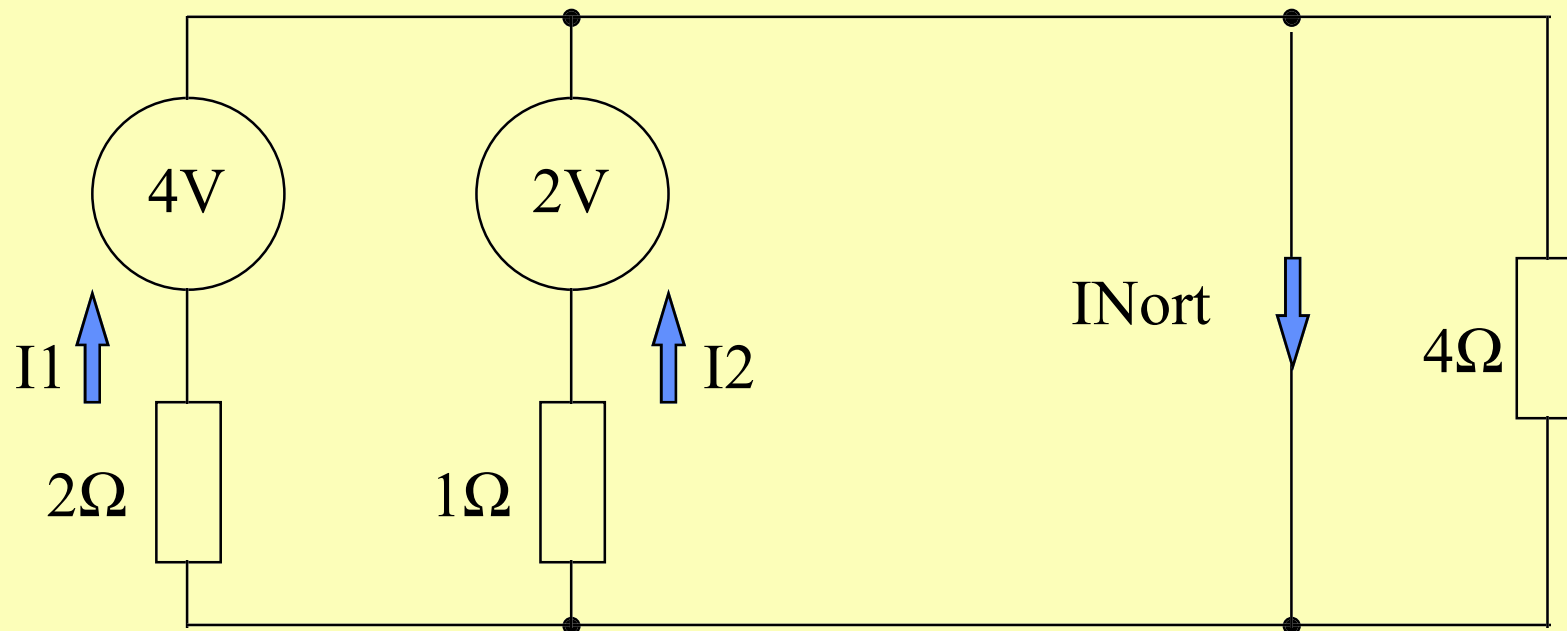

Norton and Thevenin Calculations.


- Step 2. Remove load, Short out Voltages sources, Open Circuit Current sources
- $R_{Nort} = 2\Omega \parallel 1\Omega = (2*1)/(2+1) = 2/3\Omega$

Generator 1

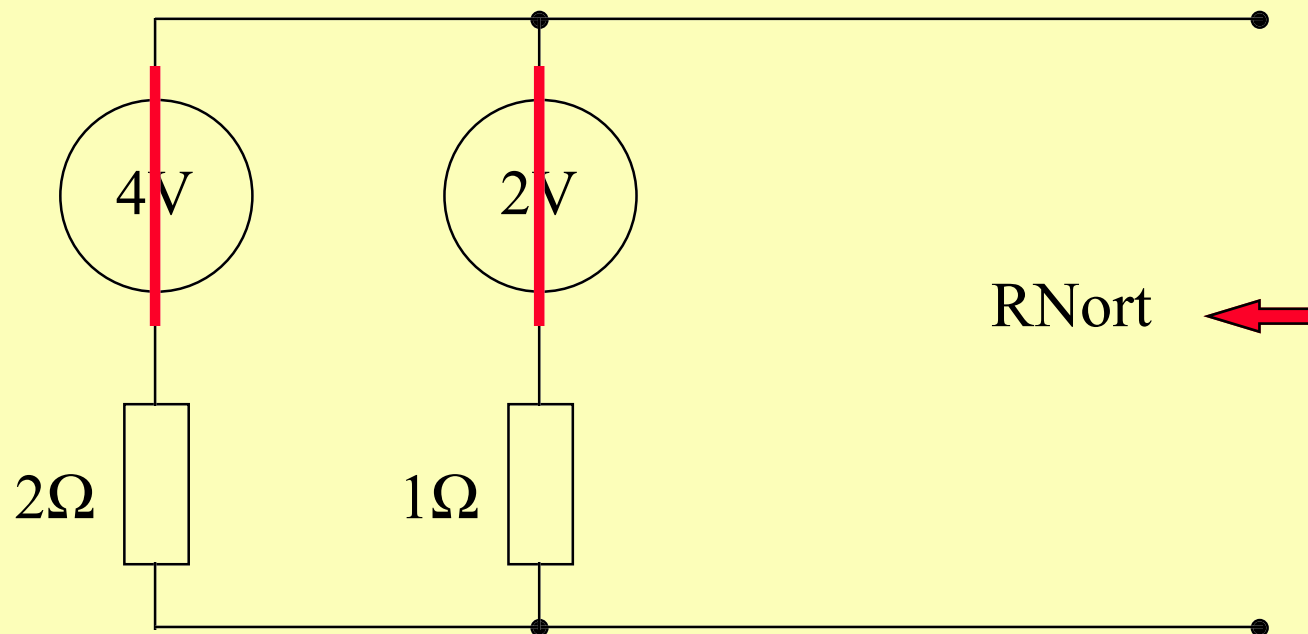


Norton and Thevenin Calculations.

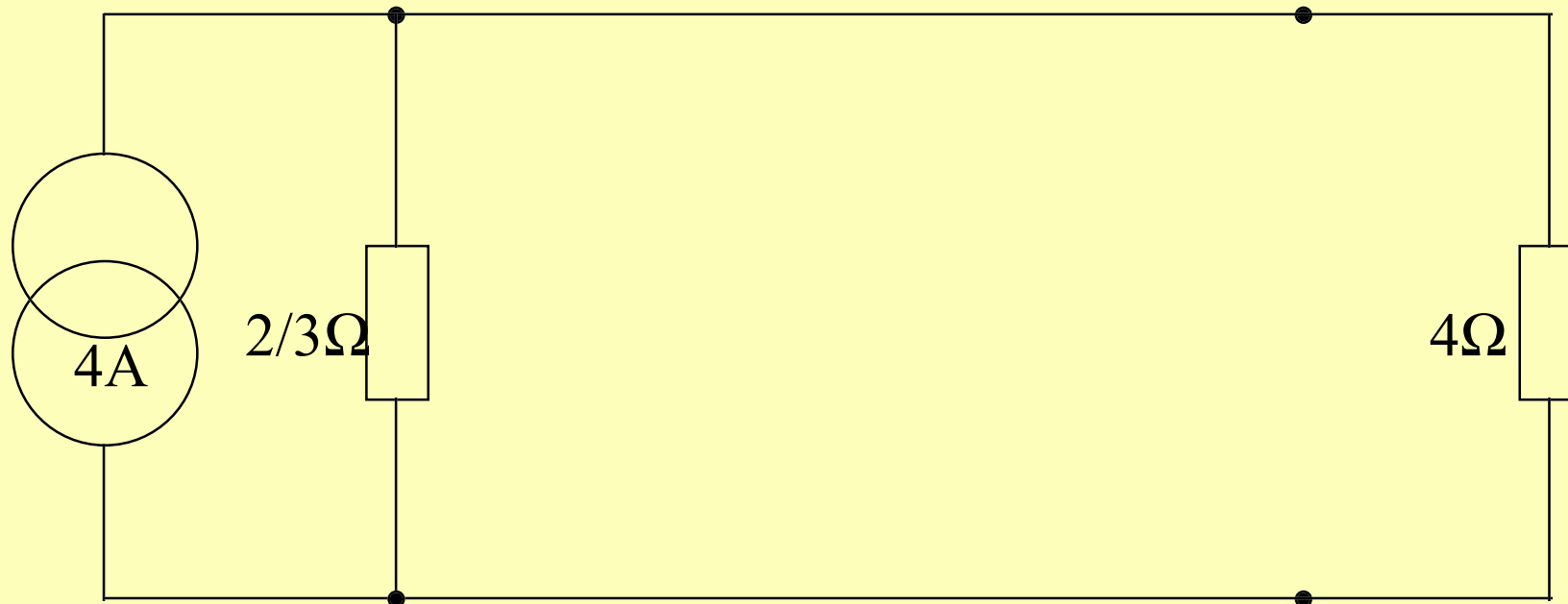- Step 3. Re-Draw circuit using equivalent Norton Circuit.



Norton and Thevenin Calculations.

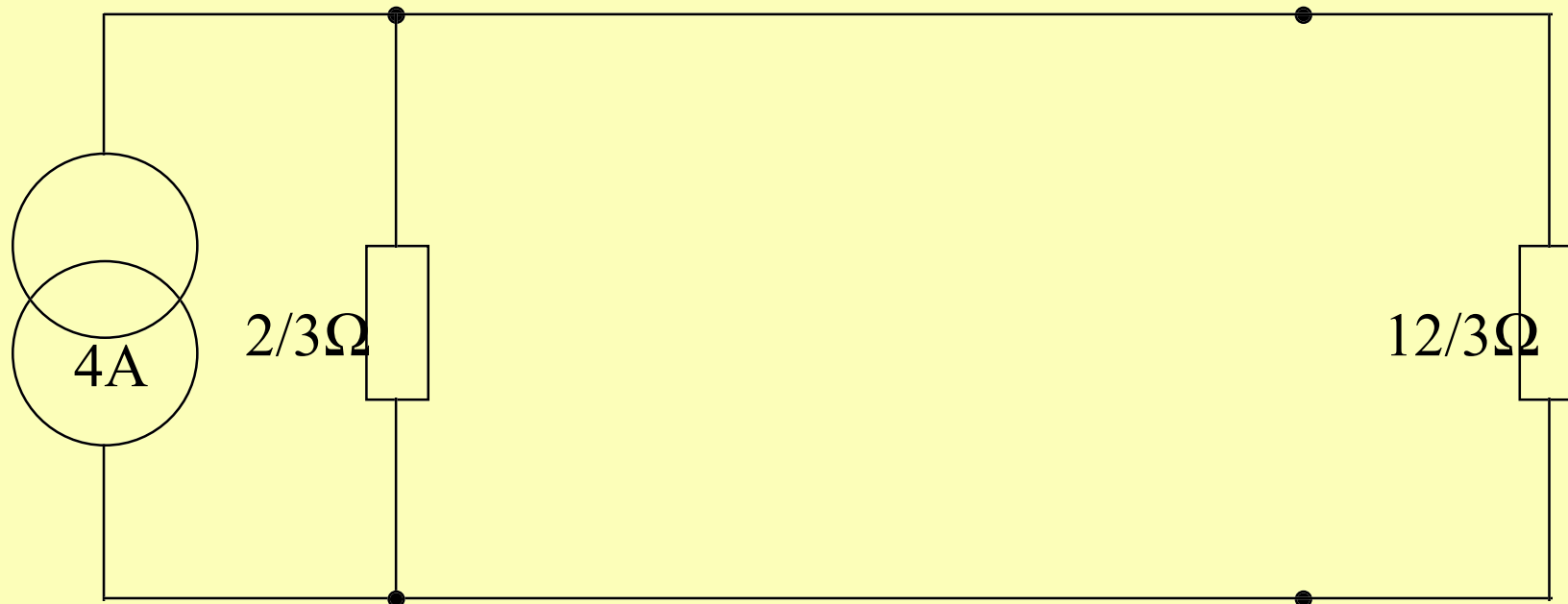- Step 4. Calculate total circuit resistance.
- Step 4a Convert resistance's into convenient $1/3\Omega$.
- $R_{cct} = 2/3 * 12/3 / (2/3 + 12/3) = 24/9 / 14/3$
 $= 8/3 / 14/3 = 8/3 * 3/14 = 8/14\Omega.$




Norton and Thevenin Calculations.

- Step 5. Calculate Voltage across total circuit resistance.
- $V_{Load} = I * R_{cct} = 4 * 8/14 = 32/14$ Volts
- We could also find current in load
- $I_{Load} = V/R = (32/14) / 4 = 8/14 = 0.57A$




Norton and Thevenin Calculations.

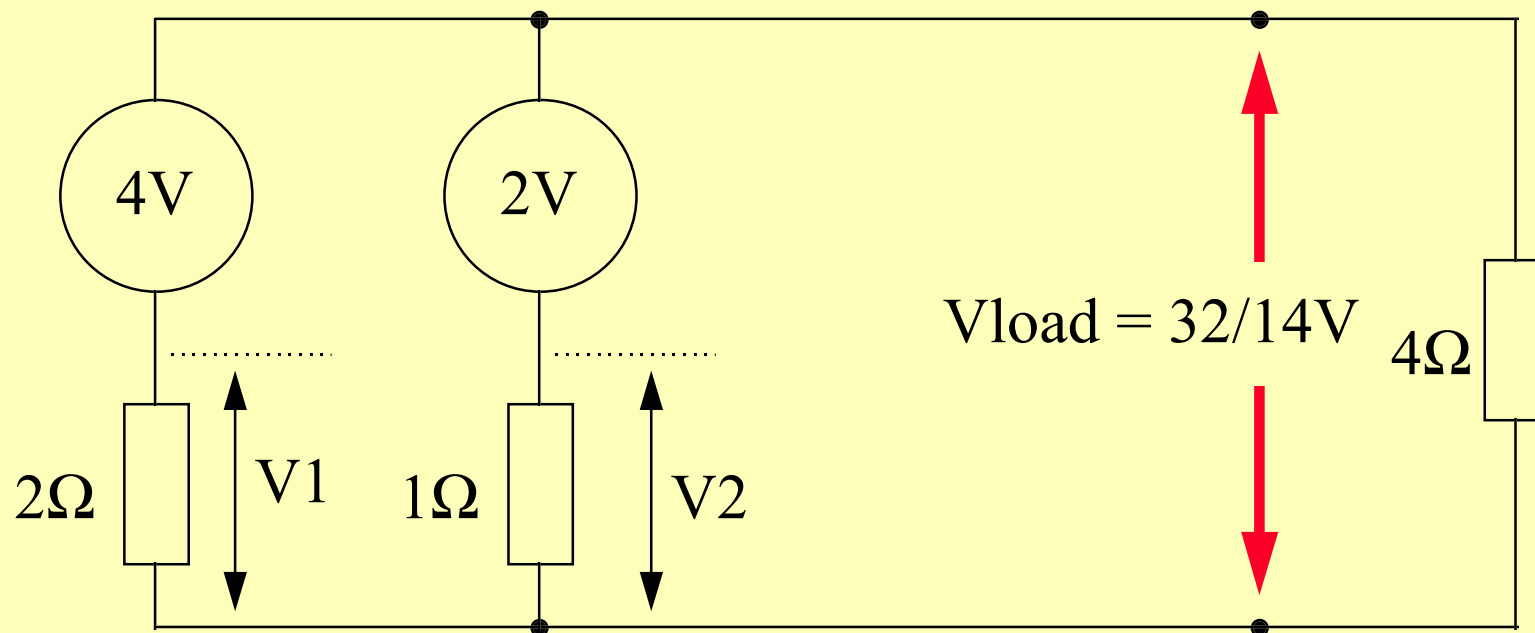- Step 6. Find voltage drop across each generator.
- $V_1 = 4\text{Volts} - V_{\text{load}} = 4 - 32/14 = 56/14 - 32/14 = 24/14 = 1.714 \text{ Volts}$
- $V_2 = 2\text{Volts} - V_{\text{load}} = 2 - 32/14 = 28/14 - 32/14 = -4/14 = -0.286 \text{ Volts}$



Norton and Thevenin Calculations.

Signal Generator.

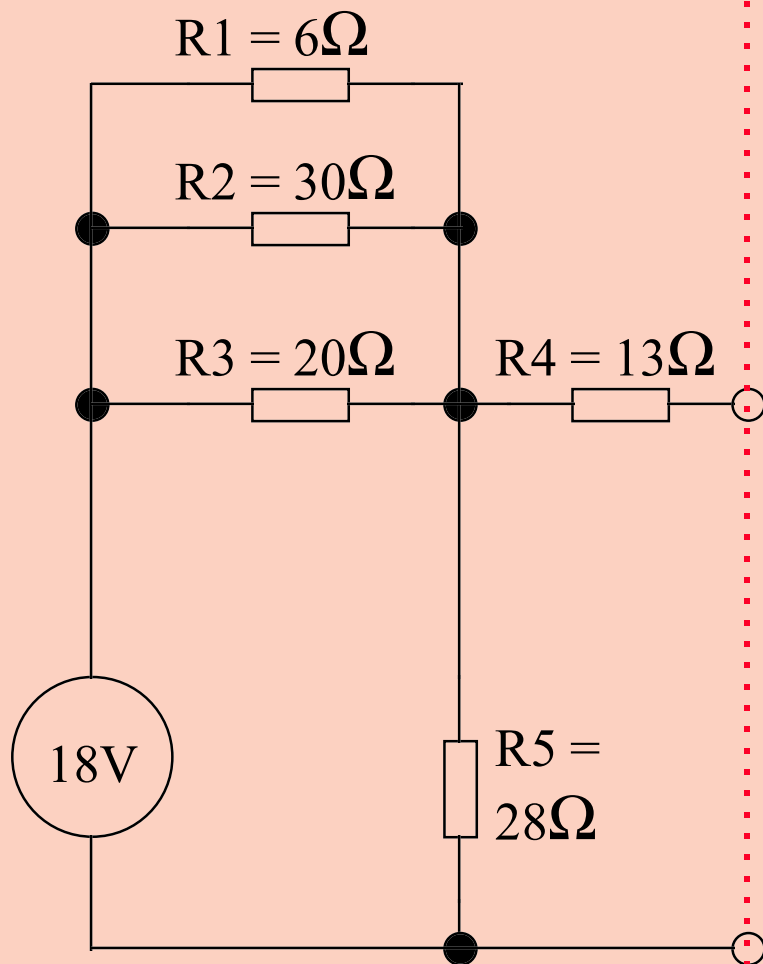


What is the Generator Output voltage with and without the load connected?

Calculate V_{Thev} , I_{Nort} , R_{Nort} , R_{Thev} .


Draw Equivalent circuits.

Signal Load.

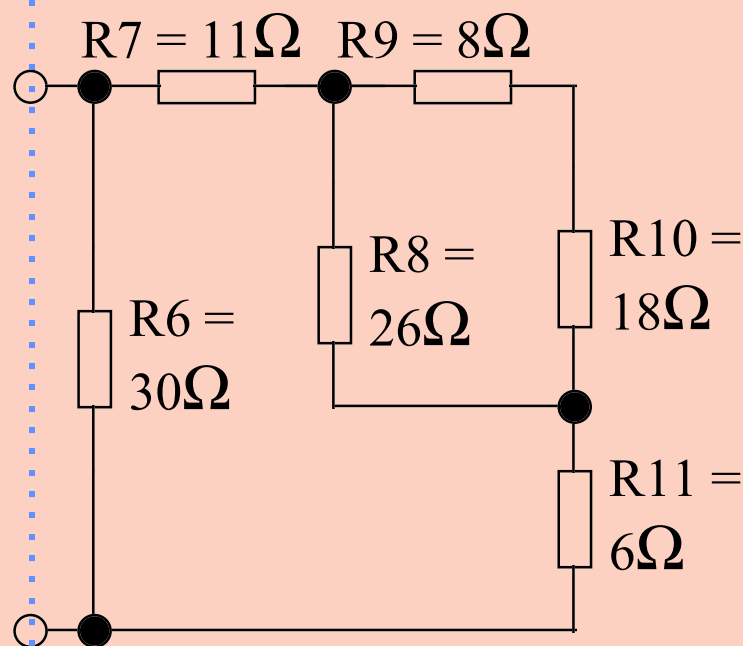


Norton and Thevenin Calculations.

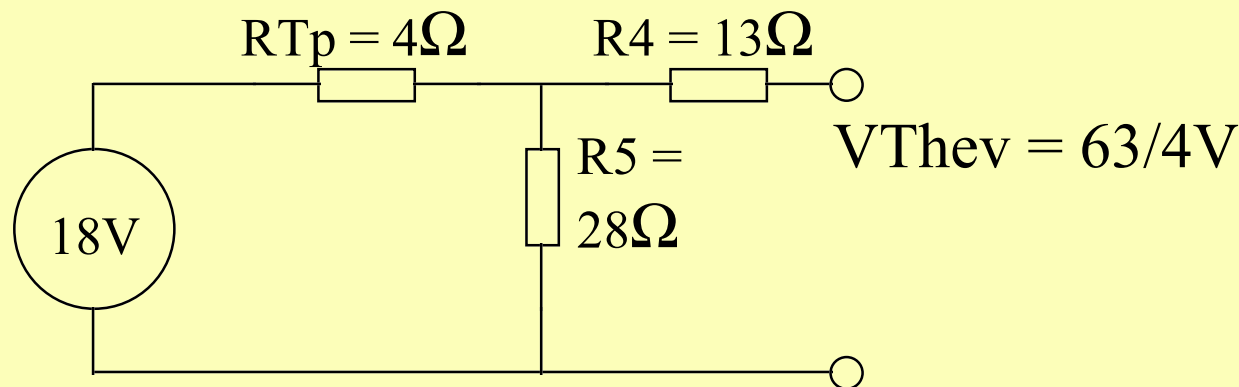- Calculate Thevenin Voltage
- Step 1. Calculate resistance of R1 ! R2 ! R3.
- $1/R_{Tp} = 1/6 + 1/30 + 1/20$ (Common denominator 60)
- $1/R_{Tp} = (10 + 2 + 3)/60 = 15/60$
- Therefore $R_{Tp} = 60/15 = 4 \Omega$
- $R_{cct} = R_{Tp} + R5 = 28 + 4 = 32 \Omega$
- $I_{cct} = V/R = 18/32$ Amps
- $V_{Thev} = I_{cct} * R5 = 18/32 * 28 = 504/32 = 63/4 V$




Norton and Thevenin Calculations.

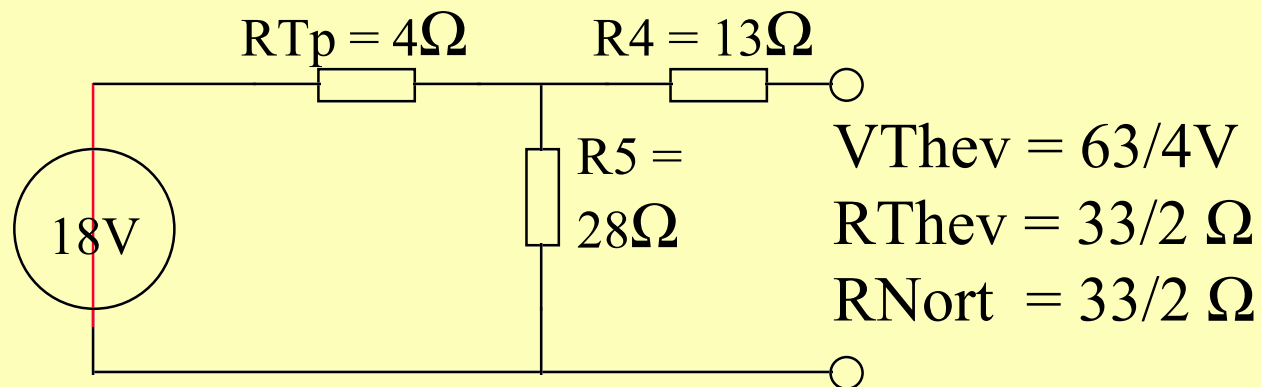- Calculate Thevenin Resistance / Norton Resistance
- Step 2. Calculate resistance of $(R_{Tp} \parallel R_5) + R_4$.
- $1/R_{Tpa} = 1/4 + 1/28$ (Common denominator 28)
- $1/R_{Tpa} = (7 + 1)/28 = 8/28 = 4/14 = 2/7$
- Therefore $R_{Tpa} = 7/2 \Omega$
- $R_{Thev} = R_{Tpa} + R_4 = 7/2 + 13 = (7 + 26)/2 = 33/2 \Omega$



Norton and Thevenin Calculations.

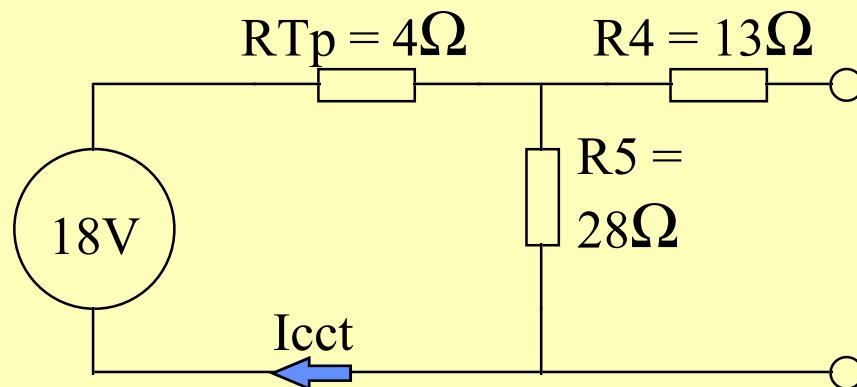- Calculate Norton Current
- Step 3a. Calculate resistance of R4 ! R5.
- $1/R_{Tpb} = 1/13 + 1/28$ (Common denominator 364)
- $1/R_{Tpb} = (13 + 28)/364 = 41/364$
- Therefore $R_{Tpb} = 364/41\Omega = 8.878\Omega$
- $R_{cct} = R_{Tpb} + R_{Tp} = 364/41 + 4 = (364 + 164)/41 \Omega$
- $R_{cct} = 528/41 \Omega = 12.878 \Omega$
- $I_{cct} = V/R = 18/(528/41) = (18*41)/528$ Amps




$$I_{cct} = 738/528 \text{ Amps}$$

$$I_{cct} = 1.398 \text{ Amps}$$

Norton and Thevenin Calculations.

- Step 3b. Calculate voltage drop across R_{Tp} .
- $V_{RTp} = I_{cct} * R = 738/528 * 4 = 2952/528$ or 5.59 Volts
- $2952/528 (\div 4) = 738/132 (\div 2) = 369/66 (\div 3) = 123/22$
- Voltage drop across remainder of the circuit is
 $V_{source} - V_{RTp} = 18V - 123/22 = (396-123)/22V$
- $V_{RTpb} = 273/22$ or 12.409 Volts
- $I_{Nort} = V_{RTpb} / R4 = (273/22)/13 = 273/(22*13) A$
 $= 273/286$ or 0.9545 Amps


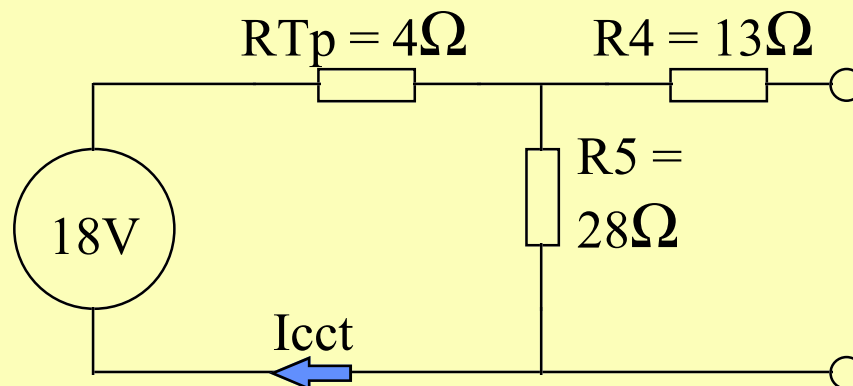


$$I_{Nort} = 273/286 \text{ Amps}$$

$$I_{Nort} = 0.9545 \text{ Amps}$$


Norton and Thevenin Calculations.

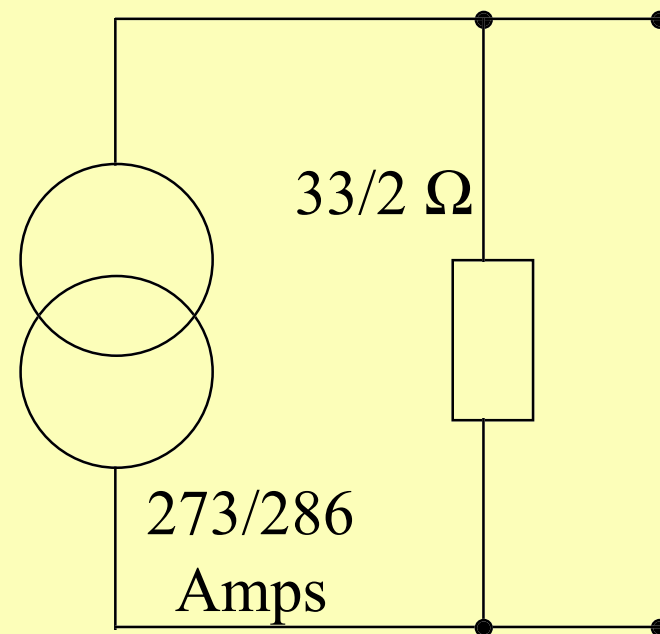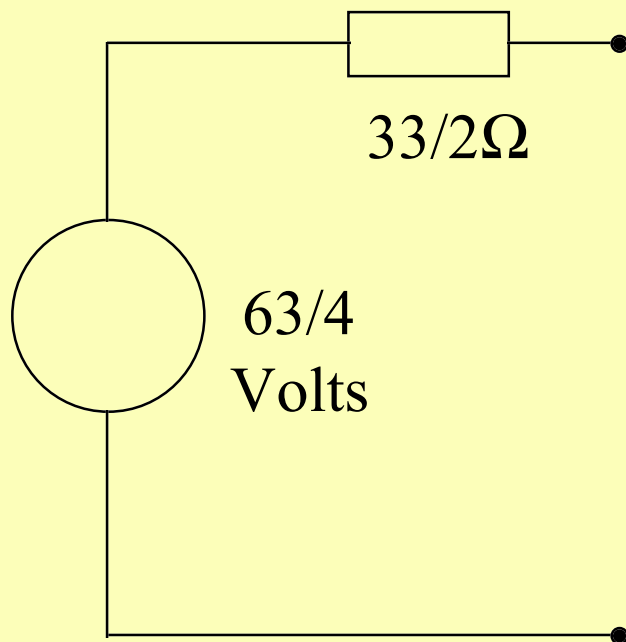- Step 4a. Re-Draw circuit using equivalent Norton Circuit.
- Step 4b. Re-Draw circuit using equivalent Thevenin Circuit.




Norton and Thevenin Calculations.

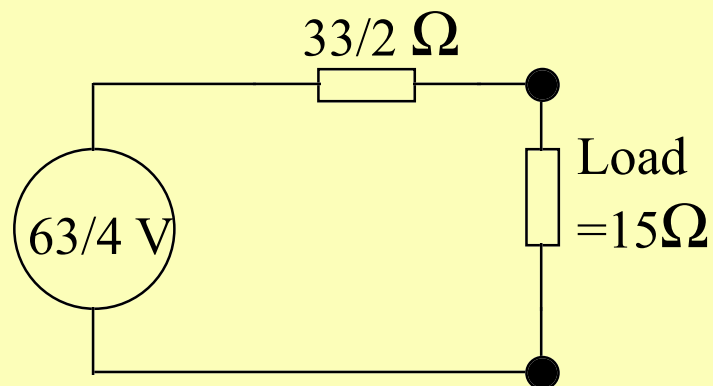- Calculate The Load Resistance.
- Step 5. Calculate resistance of $R9 + R10 = 8+18 = 26 \Omega$
- In Parallel with $R8 = 26 \parallel 26 = 13 \Omega$
- In Series with $R7 + R11 = 13 + 11 + 6 = 30 \Omega$
- In Parallel with $R6 = 30 \parallel 30 = 15 \Omega$
- This gives :-




Norton and Thevenin Calculations.

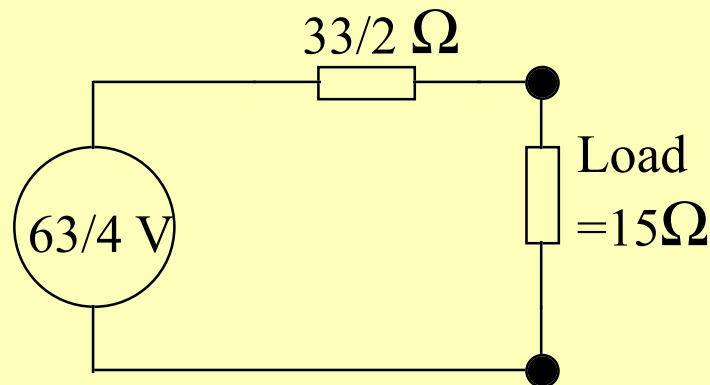- Calculate The Total circuit Resistance.
- Step 6. $R_{Thev} + Load = 33/2 + 15 = (33+30)/2 = 63/2 \Omega$
- Circuit current = $V/R = (63/4)/(63/2) = (63/4)*(2/63)$
 $= (63*2)/(63*4) = 2/4 = 1/2$ or **0.5** Amps
- Voltage across load = $I*R = 1/2 * 15 = 15/2$ Volts
- Voltage with no load = $63/4$ or **15.75** Volts
- Voltage with load = $15/2$ or **7.5** Volts




Norton and Thevenin Calculations.

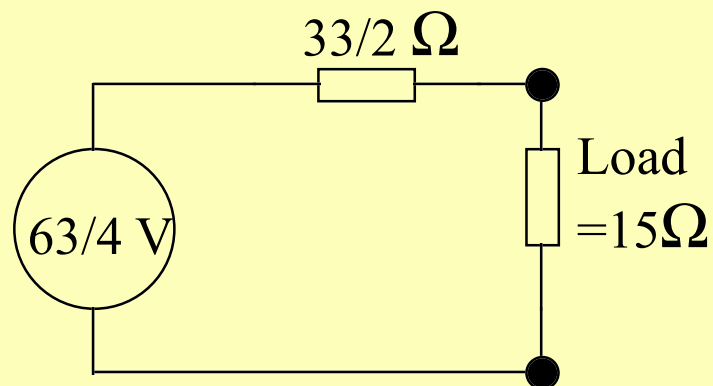- Calculate The Total circuit Resistance.
- Step 6. $R_{Thev} + Load = 33/2 + 15 = (33+30)/2 = 63/2 \Omega$
- Circuit current = $V/R = (63/4)/(63/2) = (63/4)*(2/63)$
 $= (63*2)/(63*4) = 2/4 = 1/2$ or **0.5** Amps
- Voltage across load = $I*R = 1/2 * 15 = 15/2$ Volts
- Voltage with no load = $63/4$ or **15.75** Volts
- Voltage with load = $15/2$ or **7.5** Volts




Norton and Thevenin Calculations.

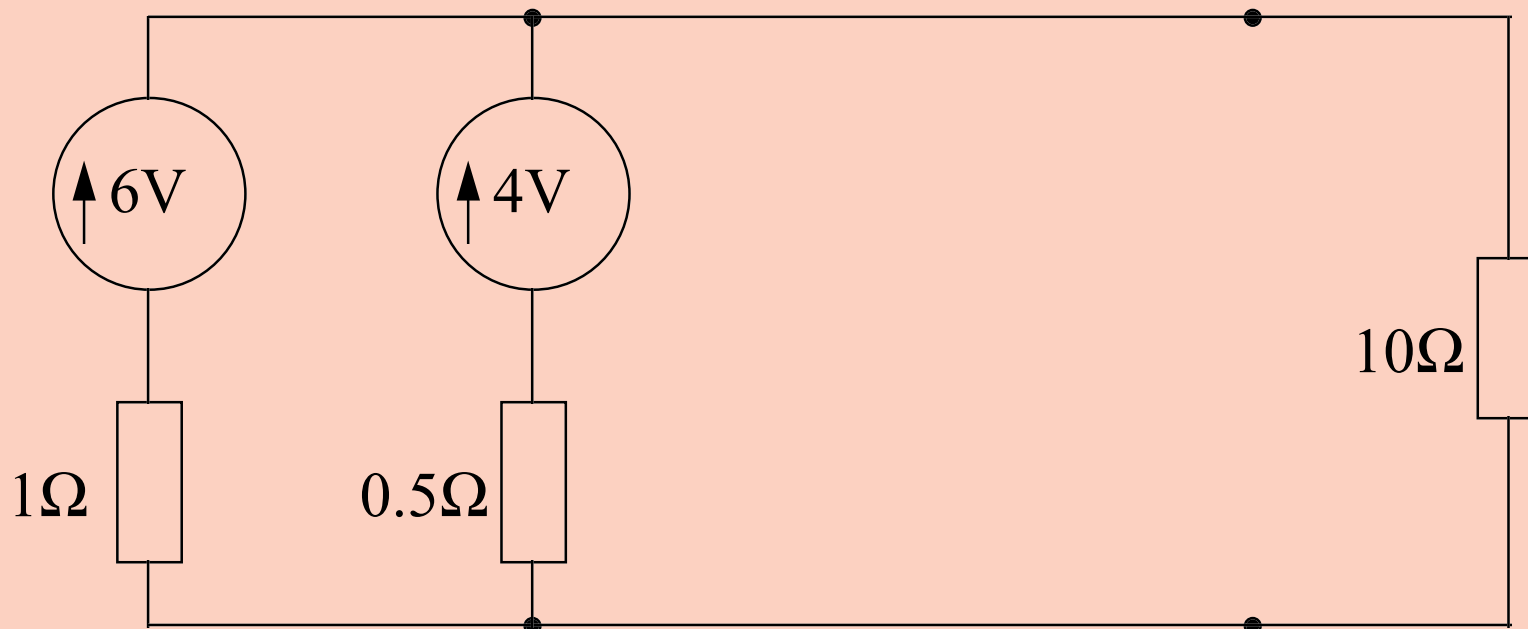- The circuit shown below shows a 10Ω Resistor supplied by two generators with internal resistance's shown.
 - (a) Use Thevenin Theorem to determine the value of current in the 10Ω Resistor
 - b) Calculate the internal voltage drop in each generator.




Norton and Thevenin Calculations.

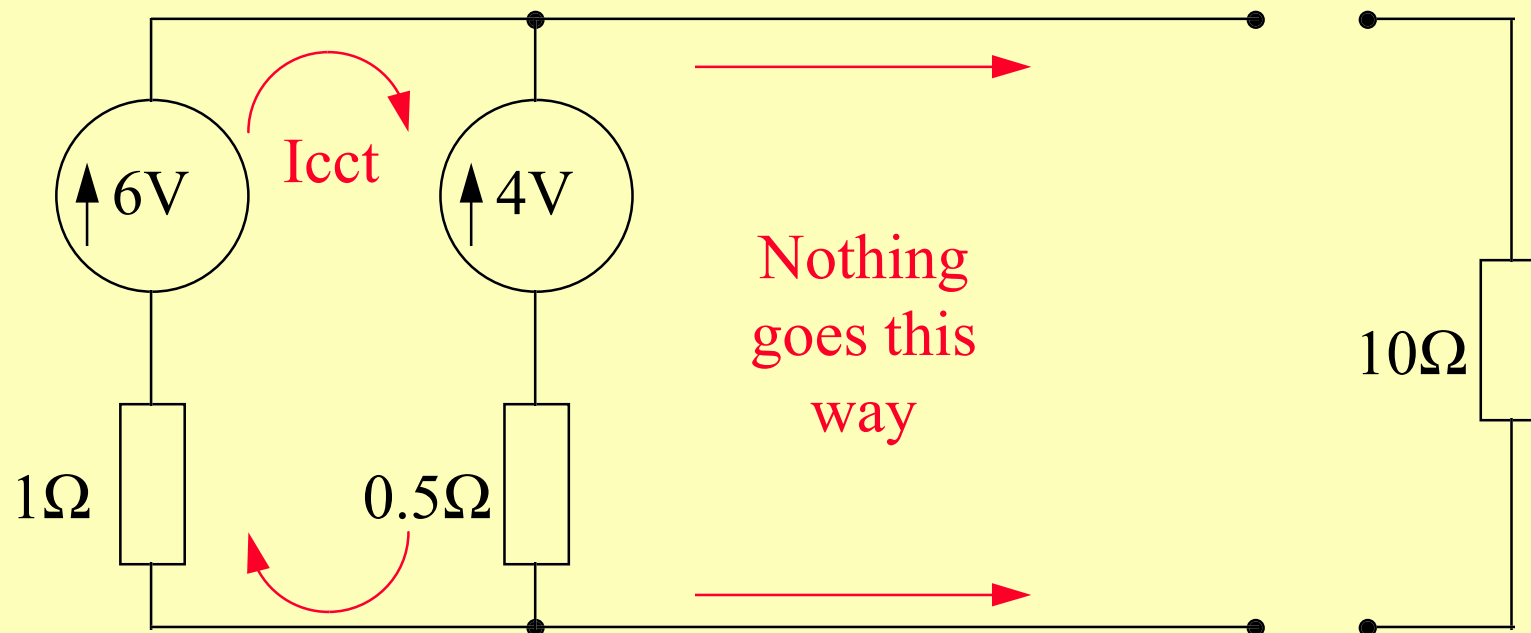- Step 1. Remove load.
- Make an assumption about current flow around circuit.
- Remember that Kirchhoff tells use that sum of voltage drops plus sum of sources equal zero.




Norton and Thevenin Calculations.

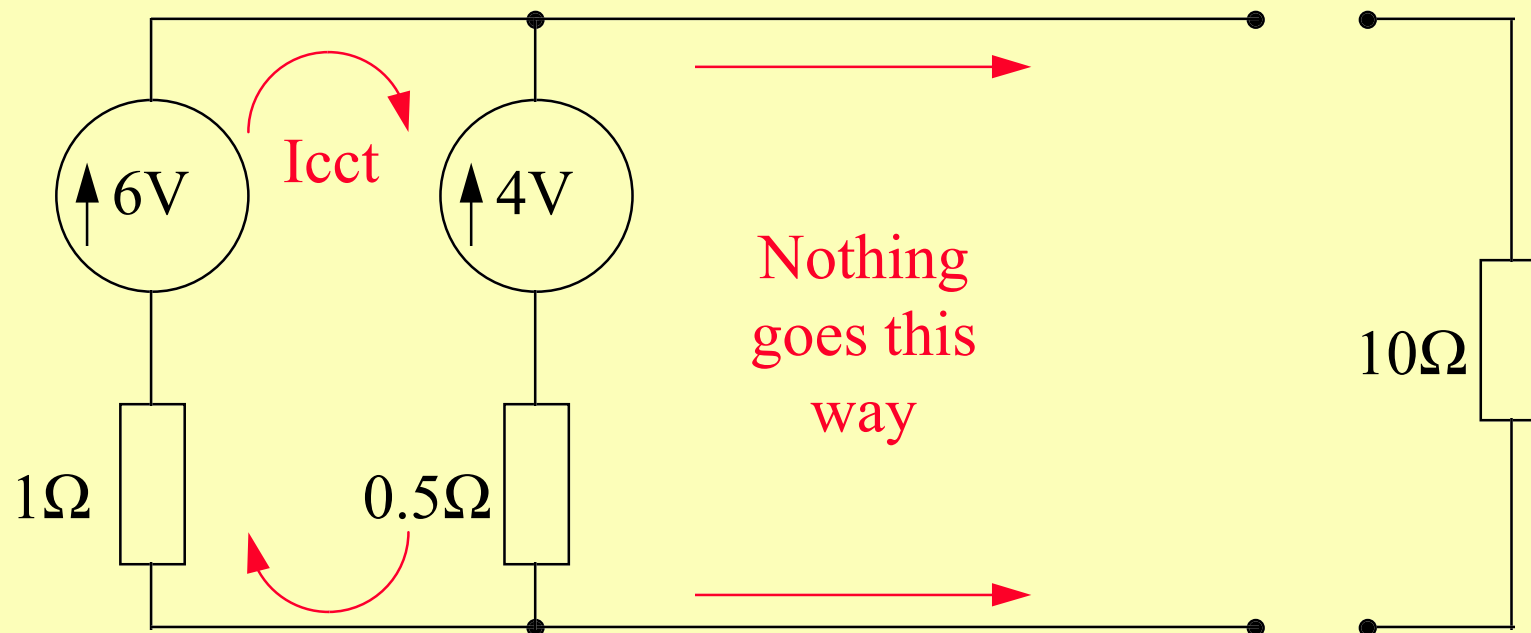- Step 2. Calculate Current.
- $6V - 4V - 0.5I_{cct} - 1I_{cct} = 0$
- $2V - 1.5I_{cct} = 0$ or $2V = 1.5I_{cct}$
- Therefore $I_{cct} = 2/1.5$ or $4/3$ Amps




Norton and Thevenin Calculations.

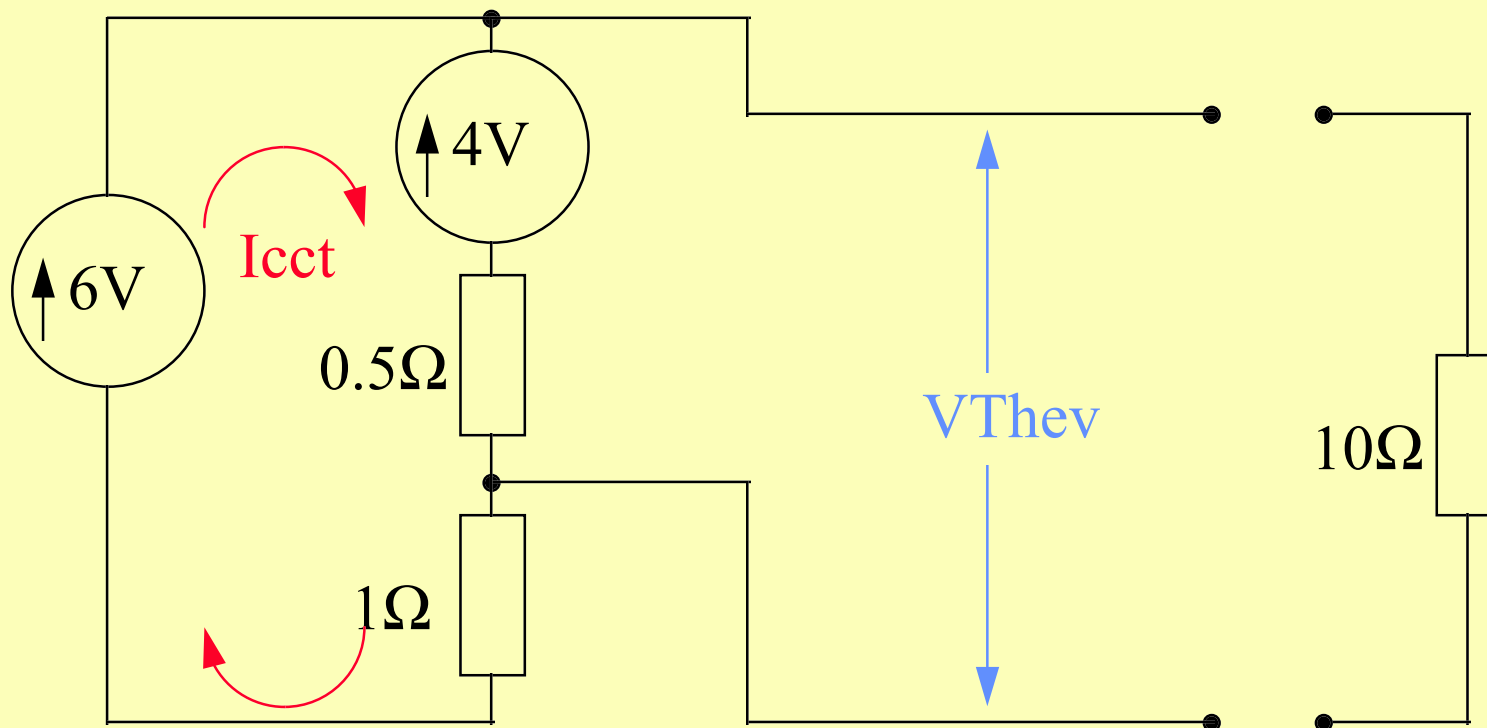- Step 3. Redraw circuit to show V_{Thev} .
- $V_{Thev} = 4V + (1/2 * I_{cct} = 1/2 * 4/3) = 4/1 + 4/6$ Volts
- $V_{Thev} = (24 + 4)/6 = 28/6 = 14/3$ Volts




Norton and Thevenin Calculations.

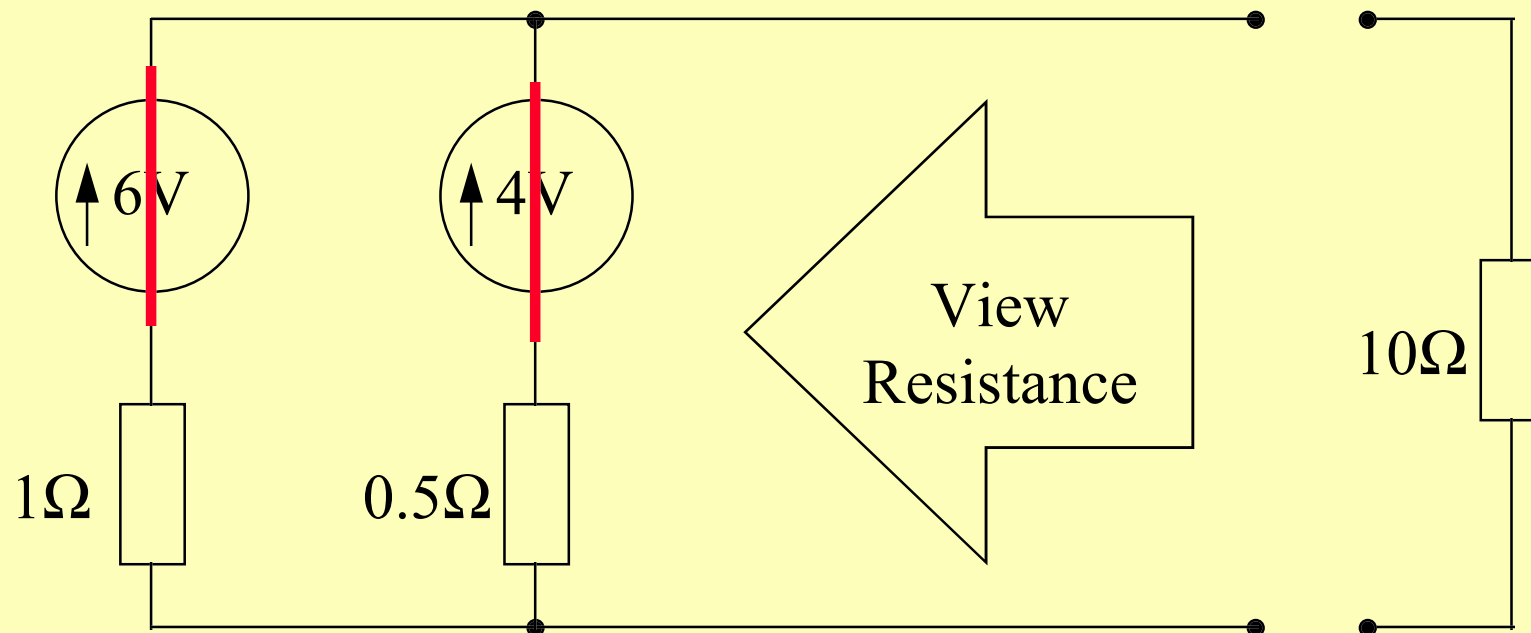- Step 4. Calculate Thevenin Resistance.
- Short out voltage sources, Open Current Sources.
- For ease use (Produce over Sum calculation method).
- $R_{Thev} = (1 * 0.5) / 1 + 0.5 = 0.5 / 1.5 = 1/3\Omega$




Norton and Thevenin Calculations.

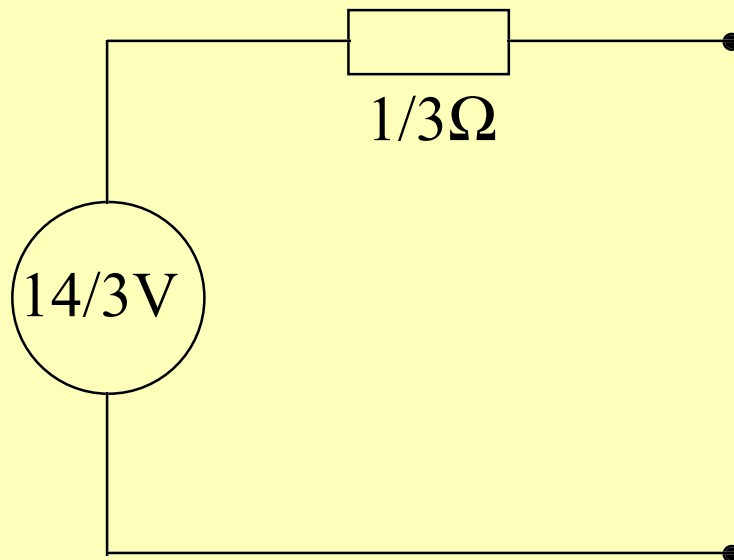- Step 5. Draw Thevenin equivalent circuit.




Norton and Thevenin Calculations.

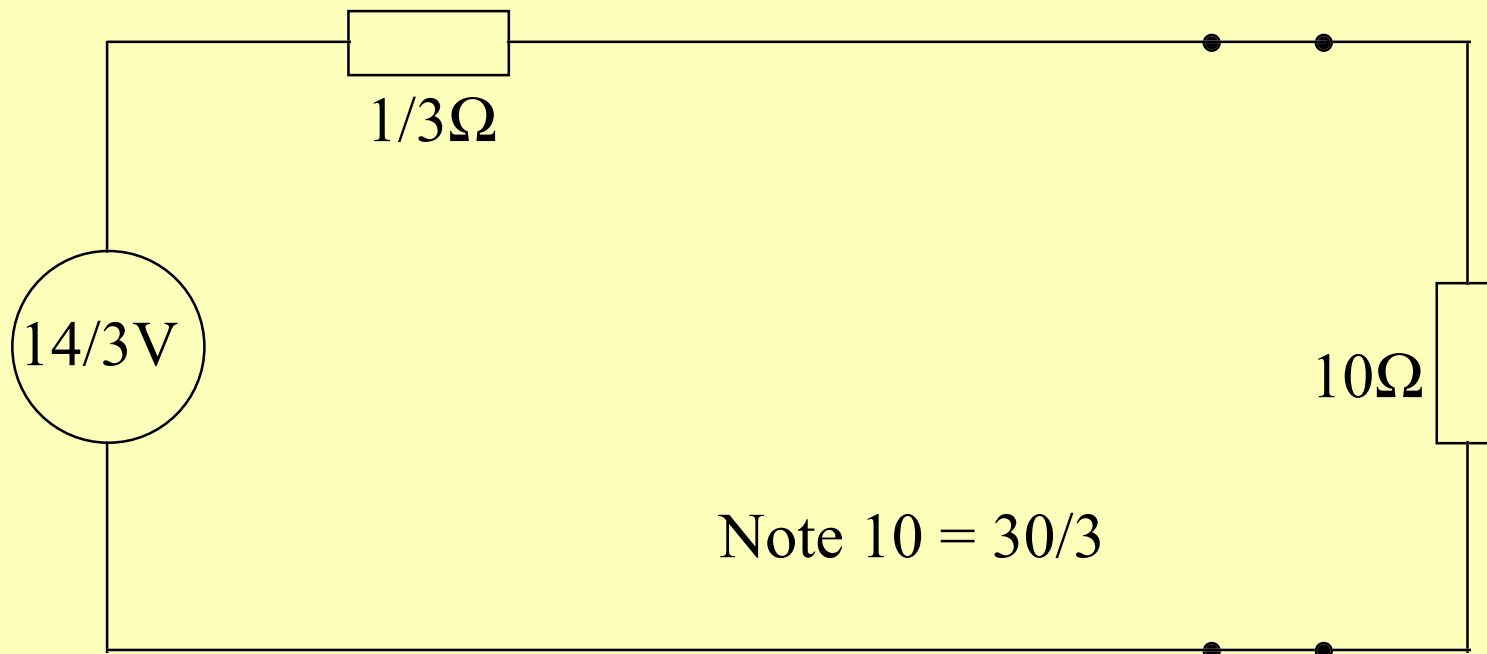- Step 6. Calculate total circuit resistance.
- Step 6a Convert resistance's into convenient $1/3\Omega$.
- $R_{cct} = 1/3 + 30/3 = 31/3\Omega$.




Norton and Thevenin Calculations.

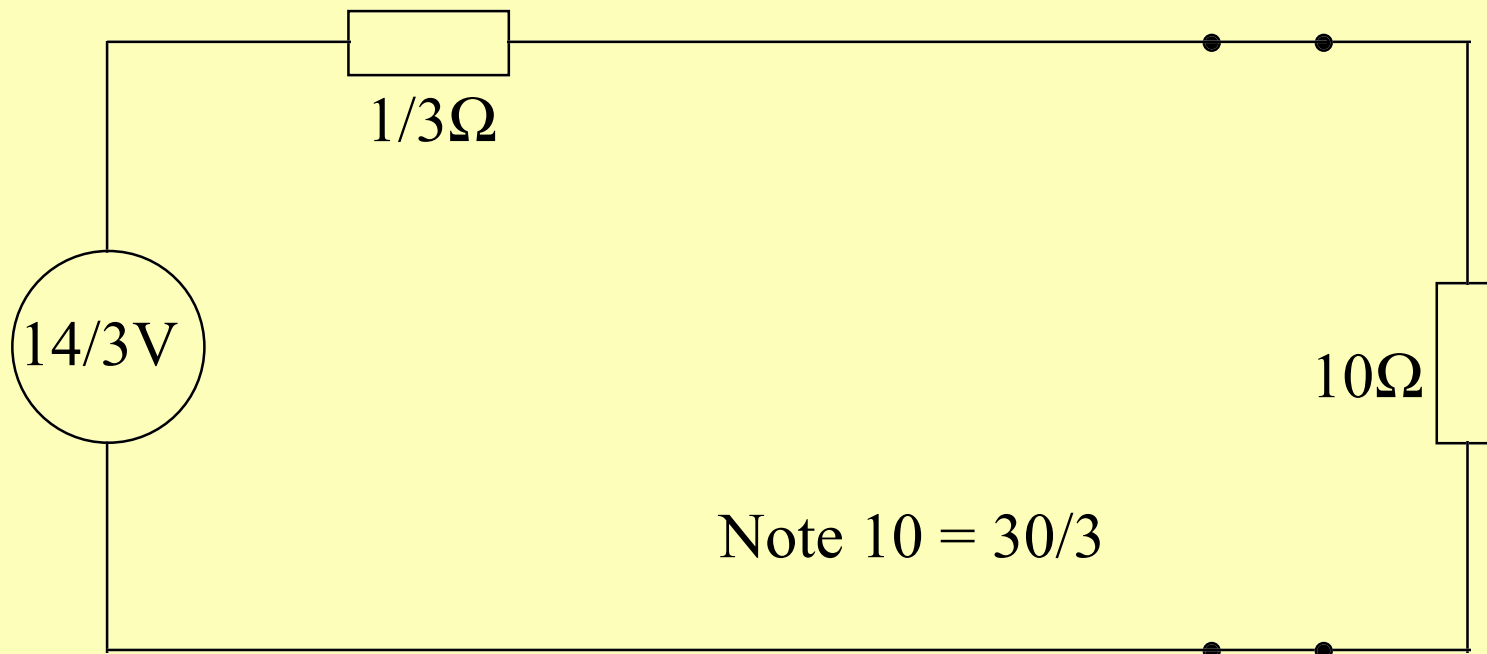- Step 7. Calculate Current in total circuit resistance.
- $I_{Load} = V / R_{cct} = (14/3) / (31/3) = (14/3) * (3/31)$
 $= 14/31$ Amps
- We could also find Voltage across load
- $V_{Load} = I * R = (14/31) * 10 = 140/31 = 4.516V$



Norton and Thevenin Calculations.

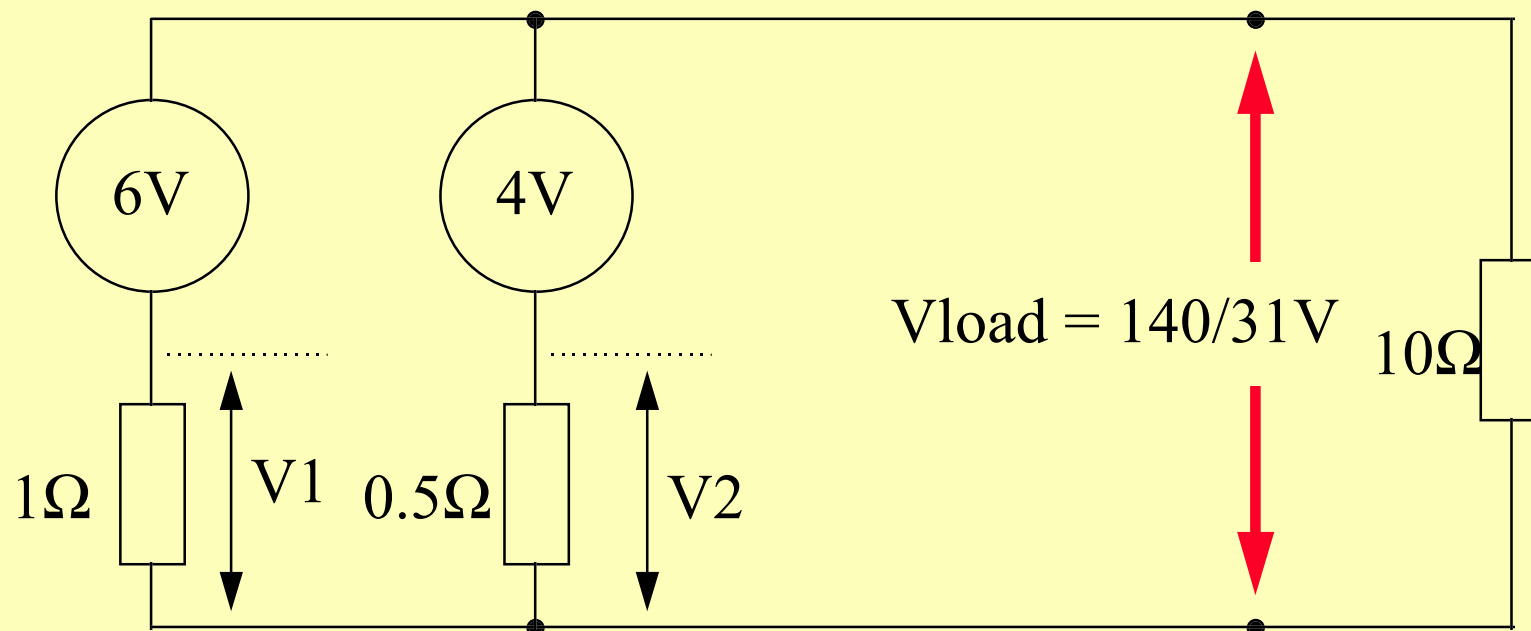- Step 8. Find voltage drop across each generator.
- $V_1 = 6\text{Volts} - V_{\text{load}} = 6 - 140/31 = 186/31 - 140/31 = 46/31 = 1.484 \text{ Volts}$
- $V_2 = 4\text{Volts} - V_{\text{load}} = 4 - 140/31 = 124/31 - 140/31 = -16/31 = -0.516 \text{ Volts}$




Superposition

Superposition.

- The Superposition Process:
- This process can be used when multiple sources of current or voltage are present in a circuit.
- The process states that in any circuit of linear elements with more than one source of voltage and/or current, the currents flowing are made up of the sum of the currents generated by each source when all other sources are replaced by their characteristic impedances.


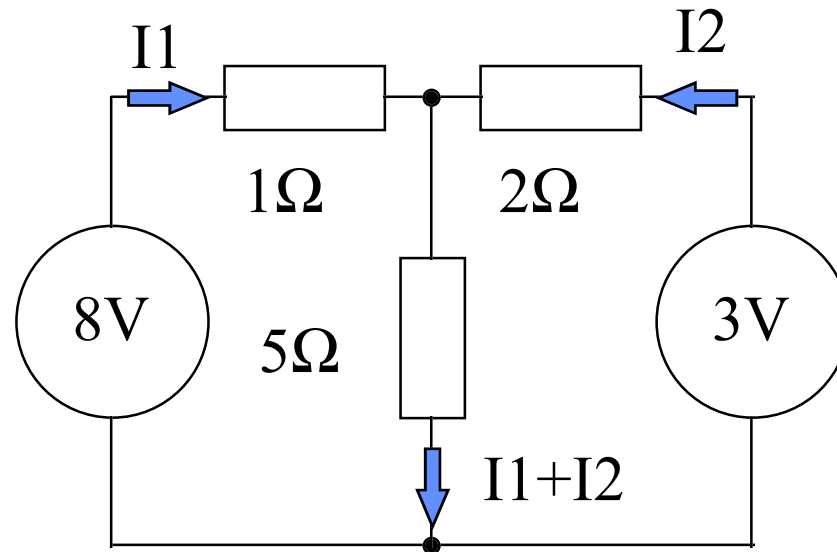
Example: **Superposition.**

- Let us consider the circuit shown below.




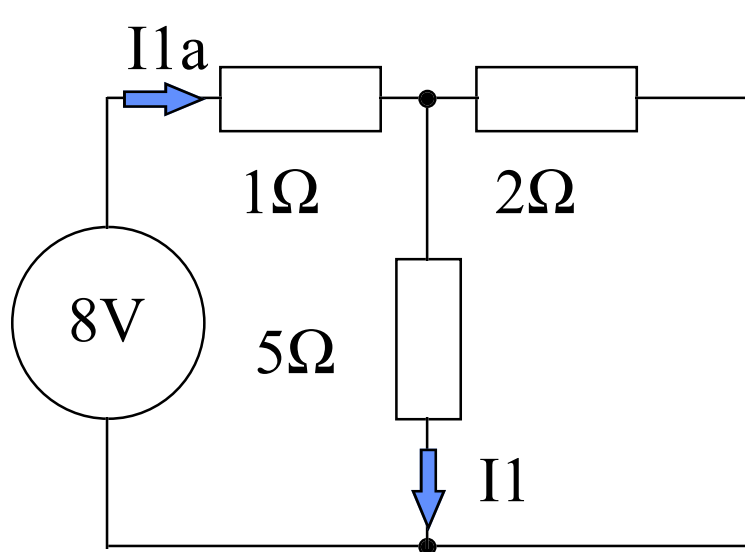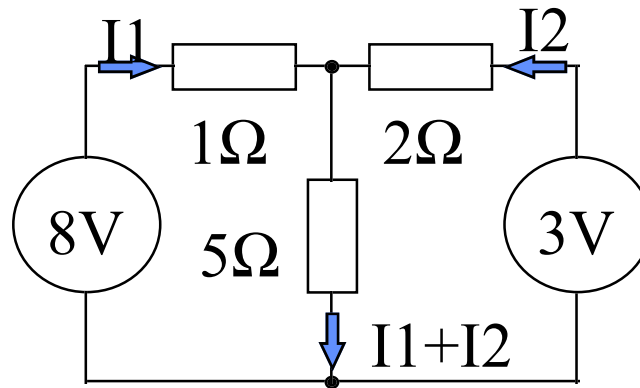Example: **Superposition.**

- This circuit can be treated as following two circuit shown below.




+

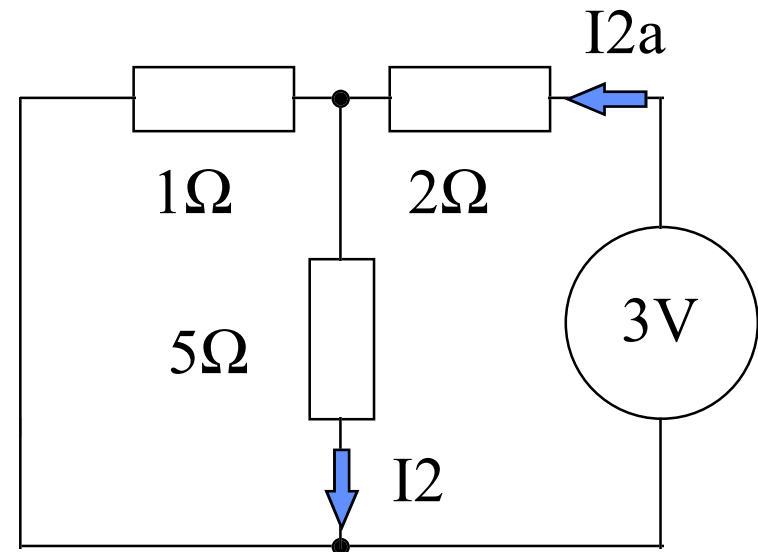

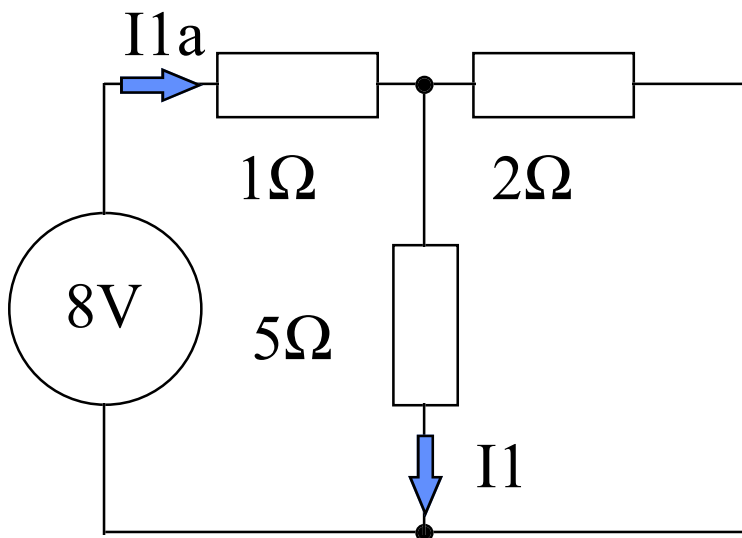
Example: **Superposition.**

- $R_{cct} = 1 + (2 \parallel 5) = 1 + (2 * 5 / (2 + 5)) = 1 + 10/7 = 17/7 \Omega$
- I_{cct} or $I_{1a} = V/R = 8 / (17/7) = 56/17$ Amps
- Voltage across $5\Omega = 8V - I_{cct} * 1\Omega = 8 - 56/17 * 1$
 $= 136/17 - 56/17 = 80/17 = 4.705V$ (V1)
- $I_1 = V/R = 80/17 / (5) = 16/17 = 0.941$ Amps



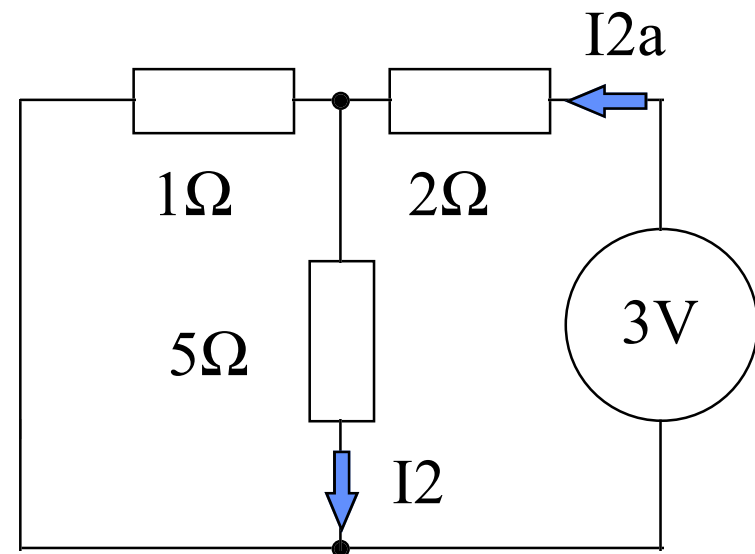
Example: **Superposition.**

- $R_{cct} = 2 + (1 \parallel 5) = 2 + (1 * 5 / (1 + 5)) = 2 + 5/6 = 17/6 \Omega$
- I_{cct} or $I_{2a} = V/R = 3 / (17/6) = 18/17$ Amps
- Voltage across $5\Omega = 3V - I_{cct} * 2\Omega = 3 - 18/17 * 2$
 $= 51/17 - 36/17 = 15/17 = 0.882$ Volts (**V2**)
- $I_2 = V/R = (15/17) / (5) = 3/17 = 0.176$ Amps



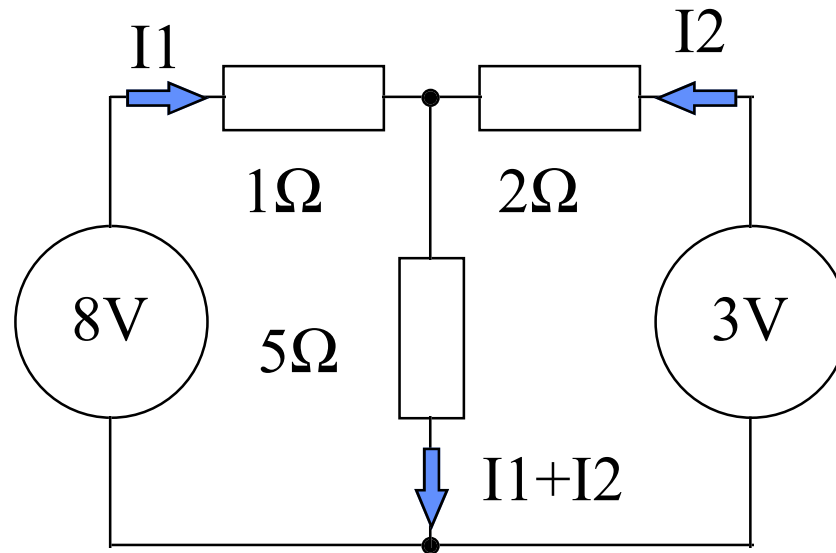
Example: **Superposition.**

- $I_1 = V/R = 80/17/(5) = 16/17 = 0.941$ Amps
- $I_2 = V/R = 15/17/(5) = 3/17 = 0.176$ Amps
- Current in 5Ω resistor = $I_1 + I_2 = 16/17 + 3/17 = 19/17A$
or $0.941 + 0.176 = 1.117$ Amps
- V across resistor = $I * R = 19/17 * 5 = 95/17 = 5.588$ Volts



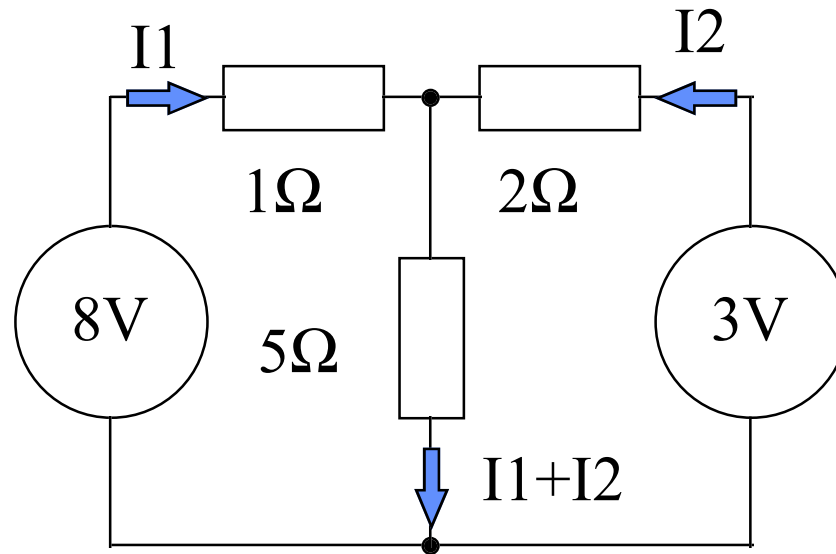Example: **Superposition.**



- $V_1 = 80/17 = 4.7V$ (**V1**)
- $V_2 = 15/17 = 0.882\text{Volts}$ (**V2**)
- V across resistor = $V_1 + V_2 = 80/17 + 15/17$
 $= 95/17 = 5.588$ Volts
- Current in 5Ω resistor = $V/R = (95/17)/5$
 $= 95/85A = 1.117$ Amps



Capacitors

Capacitors.


Dielectric (Insulating Material)

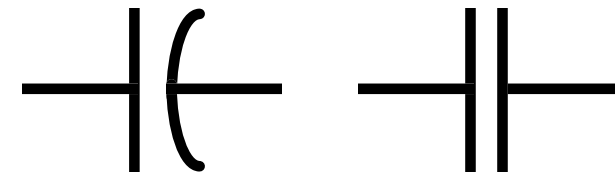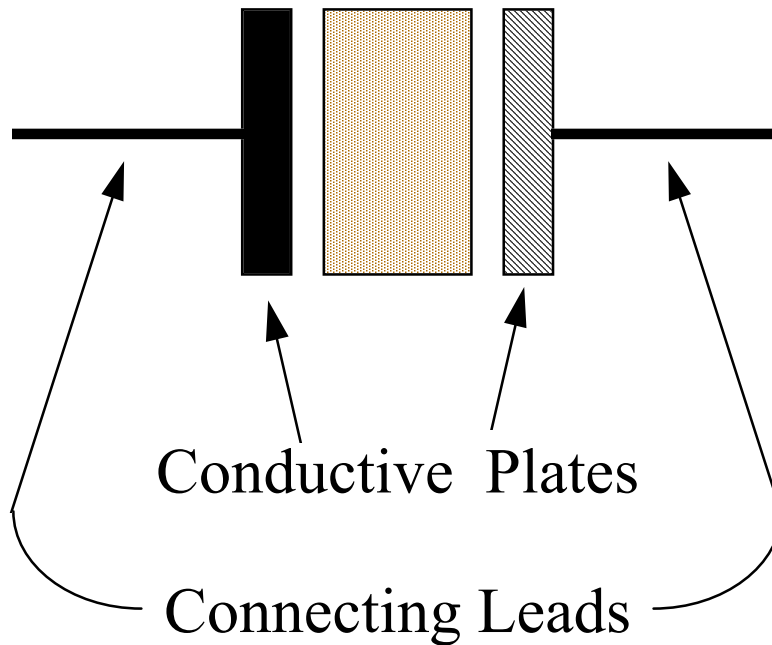


Circuit Symbols for
a Capacitor.

Physical Construction of a Capacitor


Capacitors.

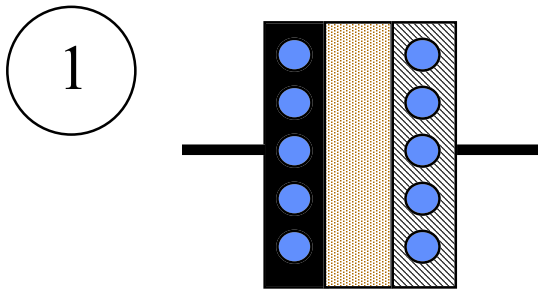


Neutral Uncharged Capacitor

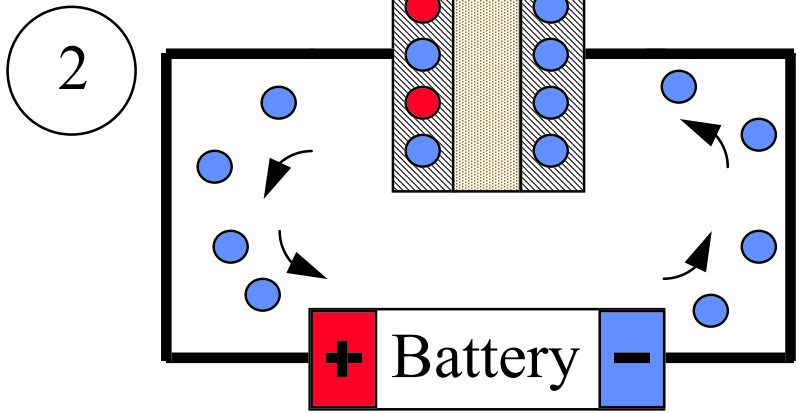

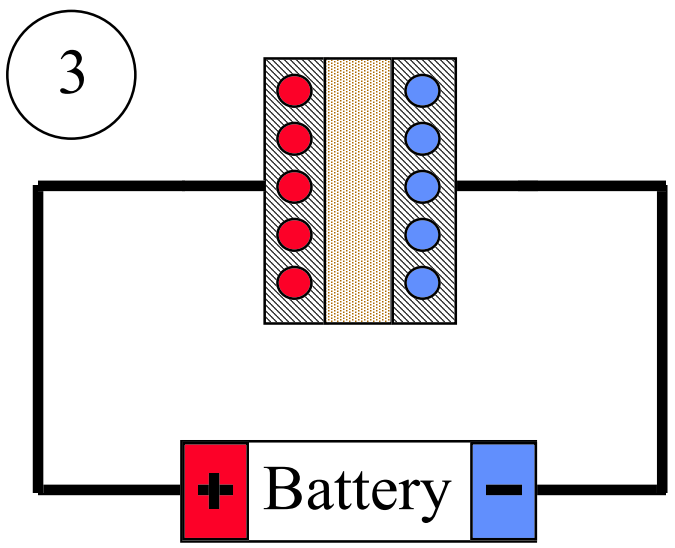Electron Flowing as Capacitor is charging



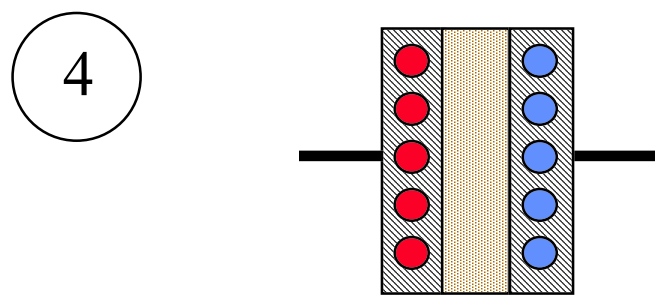Capacitor Fully Charged No more electrons moving.



Capacitor hold charge even when removed from source.

Capacitors.

- Summary :-
- The amount of Charge that a Capacitor can store across its plates is its **Capacitance**.
- The Capacitance is a measure of a Capacitors ability to store a charge. The more charge per unit of Voltage that a capacitor can store the greater the Capacitance and is expressed by the formula :-

$$C = \frac{Q}{V}$$

or $Q = C V$

Where :-

C = The Capacitance in Farads.


Q = The charge in coloumbs.

V = The voltage

Capacitors.


- The Unit of Capacitance.
- The **farad** (F) is the basic unit of capacitance and the **coulomb** (C) is the unit of electrical charge.
Remember that One **coulomb** is the same as One **Amp** for One **second**. $C = \text{current in Amps} * \text{time}$.
- Definition :-
- One farad is the amount of capacitance when one coulomb of charge is stored with one volt across the plates
- Most capacitors in electronics are measured in (μF) 10^{-6} micro farads or (pF) 10^{-12} pico farads

Capacitors.

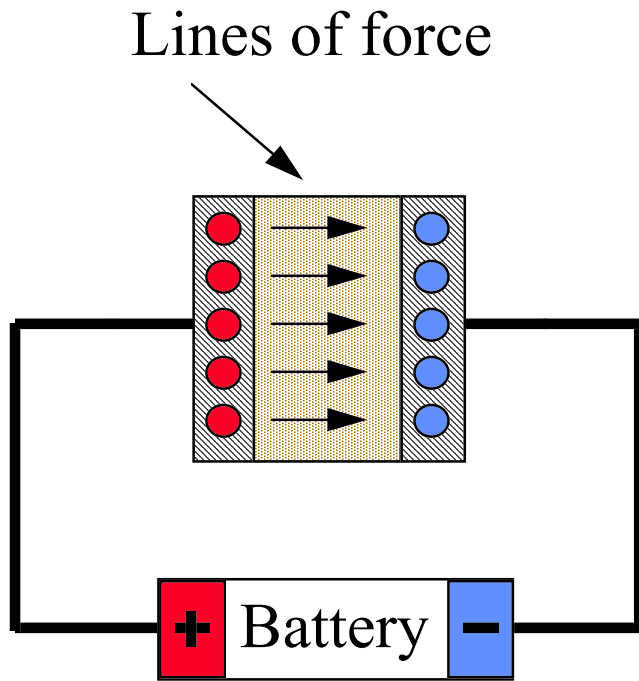

The electric field stores the charge in a capacitor.

Coulombs Law

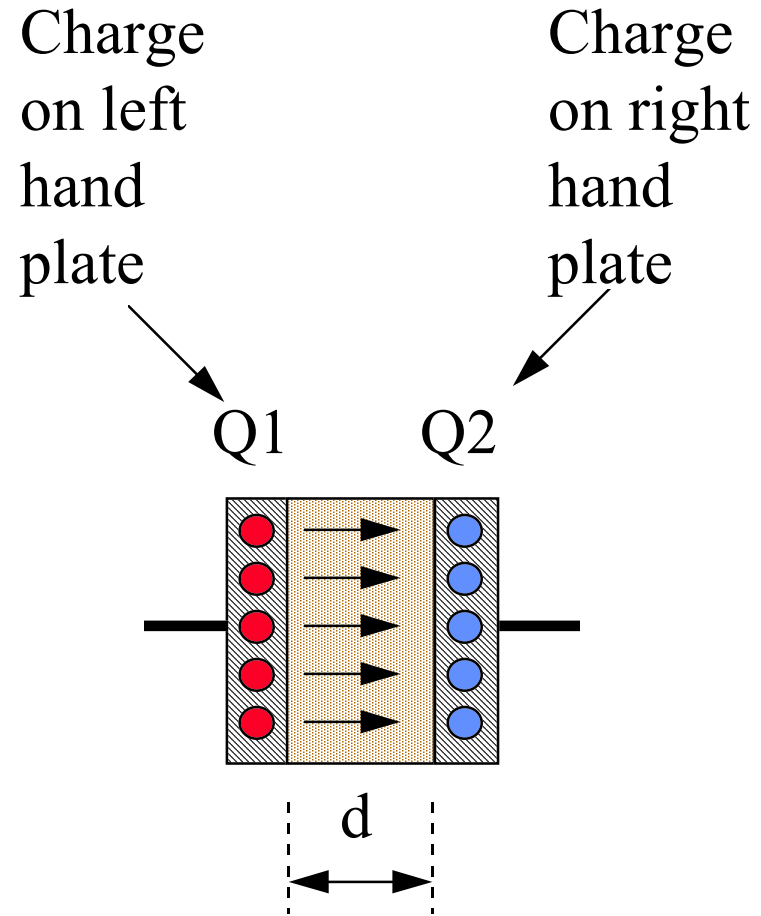

The force $F = k * Q1 * Q2 / d^2$

Capacitors.

- Coulombs Law states :-
- A force exists between two charged bodies that is directly proportional to the product of the two charges and inversely proportional to the square of the distance between the bodies.

$$F = \frac{kQ_1Q_2}{d^2}$$

F = force in newtons.

Q1 & Q2 are the charges in coulombs.

k = proportionality constant equal to 9×10^9 .

d = distance between charges in metres.

Capacitors.

- Energy stored in a capacitor :-
- The amount of energy stored in the capacitor is directly proportional to the capacitance and from $Q=CV$. The charge is directly related to the Voltage as well as the capacitance. Therefore the amount of energy stored is also dependent on the square of the voltage across the plates of the capacitor.
- The formula for the energy stored in a capacitor is as follows :-

$$W = \frac{1}{2} CV^2$$

W = energy in joules.

C = capacitance in farads.

V = Voltage in volts.

Capacitors.

- Physical characteristics of a capacitor :-
- **Plate Area** Capacitance is directly proportional to the physical size of the plates as determined by the plate area.
- **Plate Separation** Capacitance is inversely proportional to the distance between the plates.
- **Dielectric Constant** Capacitance is directly proportional to the dielectric constant (a vacuum = 1).
 - The insulating material between the plates of the capacitor is the **dielectric**.
 - The measure of a material's ability to establish an electric field is called the dielectric constant or relative permittivity, symbolized by ϵ_r (the Greek letter epsilon)

Capacitors.

- Calculating the Capacitance of a Capacitor :-
- The Capacitance of a capacitor is directly proportional to the area and inversely proportional to the distance between the plates.
- The Permittivity value $\epsilon = \epsilon_0 * \epsilon_r$ (in Farads per metre)
 - where ϵ_0 = permittivity of a vacuum $8.85 * 10^{-12}$ F/m).
 - and ϵ_r = relative permittivity of the material.
- The formula for the capacitance of a capacitor is as follows :-

$$C = \frac{\epsilon A}{d}$$

A = Area of one of the two equal plates.

d = Distance between plates.

ϵ = permittivity of the material.

C = capacitance in farads.

Capacitors.

- Formula Summary:-

$$Q = CV$$

$$W = \frac{1}{2} CV^2$$

$$C = \frac{\epsilon A}{d}$$

Where :-

C = The Capacitance in Farads.

Q = The charge in coulombs.

V = The voltage

W = energy in joules.

C = capacitance in farads.

V = Voltage in volts.

A = Area of one of the two equal plates.

d = Distance between plates.

ϵ = permittivity of the material.

C = capacitance in farads.

Capacitors.

- Example:-
- A Capacitor has a capacitance of $0.1\mu\text{F}$ and has 30V p.d. across its conductors.
- What amount of charge is stored?

Capacitors.

- Example:-
- A Capacitor has a capacitance of $0.1\mu\text{F}$ and has 30V p.d. across its conductors.
- How much energy is stored?

- Solution

$$C = \frac{Q}{V} \quad \text{or} \quad Q = CV$$

Therefore amount of stored charge is

$$Q = 0.1 * 10^{-6} * 30 = 3\mu\text{C}$$

Capacitors.

- Example:-
- A Capacitor has a capacitance of $0.1\mu\text{F}$ and has 30V p.d. across its conductors.
- How much energy is stored?

Capacitors.

- Example:-
- A Capacitor has a capacitance of $0.1\mu\text{F}$ and has 30V p.d. across its conductors.
- How much energy is stored?
- Solution

$$W = \frac{1}{2} CV^2$$

Therefore amount of stored energy is

$$W = 0.5 * 0.1 * 10^{-6} * 30 * 30 = 45\mu\text{J}$$

Capacitors.

- Example:-
- A Capacitor consists of two plates $1\text{cm} * 0.5\text{cm}$ spaced 0.2mm apart and using a dielectric of permittivity $6 * 10^{-11} \text{ F/m}$
- Find the capacitance value.

Capacitors.

- Example:-
- A Capacitor consists of two plates 1cm * 0.5cm spaced 0.2mm apart and using a dielectric of permittivity $6 \cdot 10^{-11}$ F/m

- **Solution** The capacitance value is found from

- Convert cm values to metres

- $A = (1 \cdot 10^{-2}) * (0.5 \cdot 10^{-2}) = 0.5 \cdot 10^{-4}$ m

$$C = \frac{\epsilon A}{d}$$

$$C = \frac{6 \cdot 10^{-11} * 0.5 \cdot 10^{-4}}{0.2 \cdot 10^{-3}} \quad \text{Farads}$$

$$C = 1.5 \cdot 10^{-11} \text{ F or } 15 \cdot 10^{-12} \text{ F} \quad \text{which is } 15 \text{ pF}$$

Capacitors.

- Extended Example:-
- A Capacitor consists of two plates 2cm by 3cm spaced 0.5mm apart and using a dielectric of permittivity 7×10^{-10} F/m
- Find the capacitance value.
- If the capacitor has 22V across the conductors.
- Find the amount of stored charge.
- Find the amount of stored energy.

Capacitors.

- Example:-
- A Capacitor consists of two plates 2cm by 3cm spaced 0.5mm apart and using a dielectric of permittivity 7×10^{-10} F/m
- Find the capacitance value.
- Convert cm values to metres
- $A = (2 \times 10^{-2}) * (3 \times 10^{-2}) = 6 \times 10^{-4}$ m

$$C = \frac{\epsilon A}{d}$$

$$C = \frac{7 \times 10^{-10} * 6 \times 10^{-4}}{0.5 \times 10^{-3}} \quad \text{Farads}$$

$$C = 8.4 \times 10^{-10} \text{ F or } 840 \times 10^{-12} \text{ F} \quad \text{which is } 840 \text{ pF}$$

Capacitors.

- Example:-
- A Capacitor consists of two plates 2cm by 3cm spaced 0.5mm apart and using a dielectric of permittivity 7×10^{-10} F/m
- The capacitance value. = 840pF $V=22V$

$$C = \frac{Q}{V} \quad \text{or} \quad Q = CV$$

Therefore amount of stored charge is

$$Q = 840 \times 10^{-12} * 22 = 18.48 \times 10^{-9} \text{ C or } 18.48 \text{ nC}$$

Capacitors.


- Example:-
- A Capacitor consists of two plates 2cm by 3cm spaced 0.5mm apart and using a dielectric of permittivity 7×10^{-10} F/m
- The capacitance value. = 840pF $V=22V$

$$W = \frac{1}{2} CV^2$$


Therefore amount of stored energy is

$$W = 0.5 * 840 * 10^{-12} * 22 * 22 = 203.28 * 10^{-9} \text{J or } 203.28 \text{nJ}$$


Capacitors.

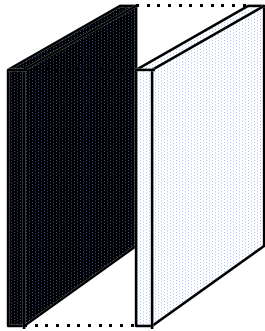


Full plate area
more capacitance

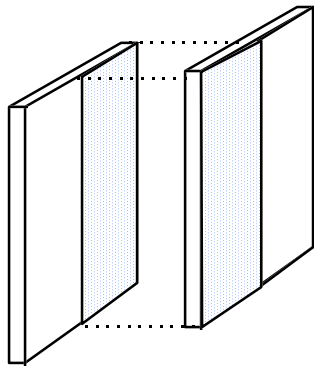

Reduced plate area
less capacitance

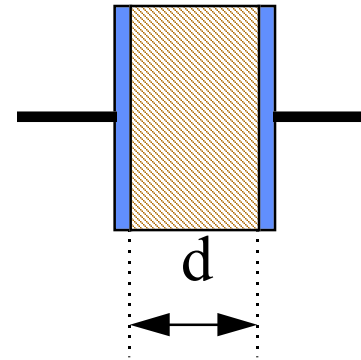

More capacitance

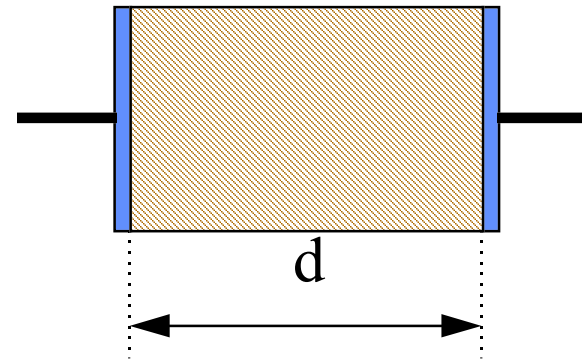


Less capacitance

Capacitors Summary


Capacitors.

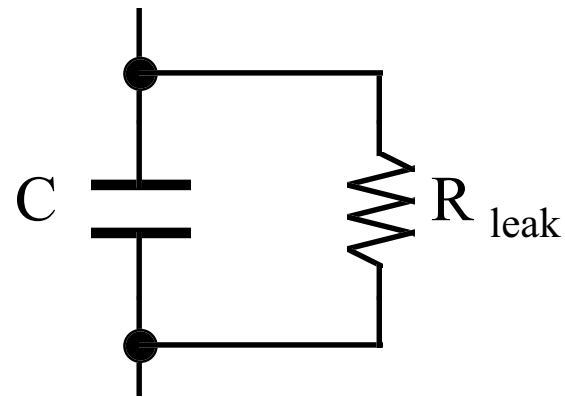- Leakage in a capacitor :-
- No insulation material is perfect hence the dielectric of any capacitor will conduct some small amount of current. The charge on the capacitor will eventually leak away.
- The equivalent circuit of a non ideal capacitor.



Capacitors in series

Capacitors.

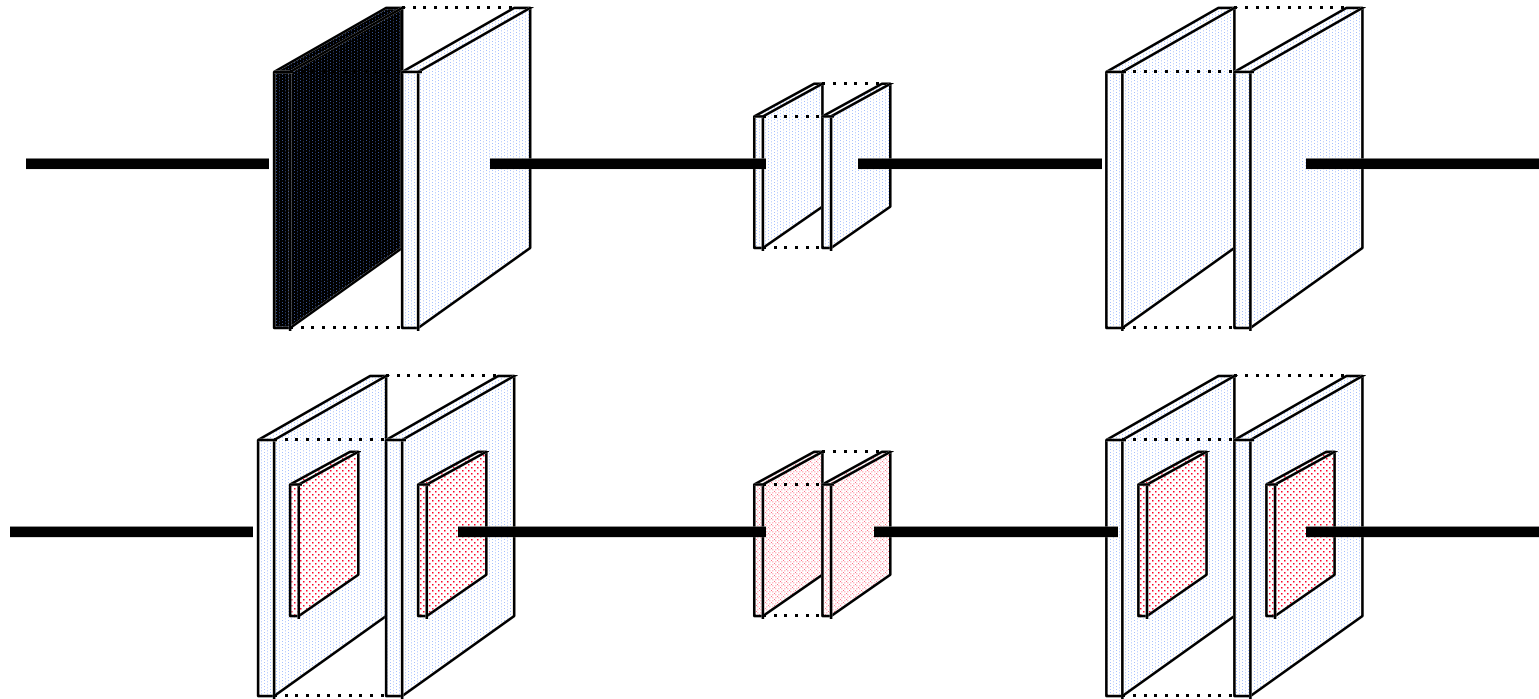


Note: Plate area of all the capacitors becomes effectively the size of the smallest plate and the dielectric distance is the sum of all the widths. Therefore the capacitance of capacitors in series is always smaller than the smallest value.

Capacitors in series

Capacitors.

The Proof

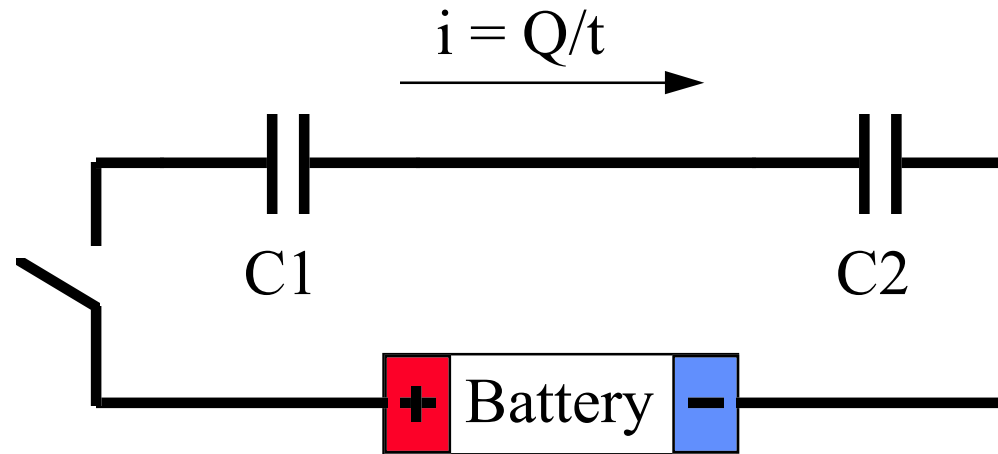

With the switch closed the capacitors charging $I = Q/t$ is same at all points of the circuit.


The total charge Q_t moved through the circuit equals the charge on C1 and is also equal to the charge on C2. $Q_t = Q_1 = Q_2$

Capacitors in series

Capacitors.

The Proof

Note: $V = Q/C$

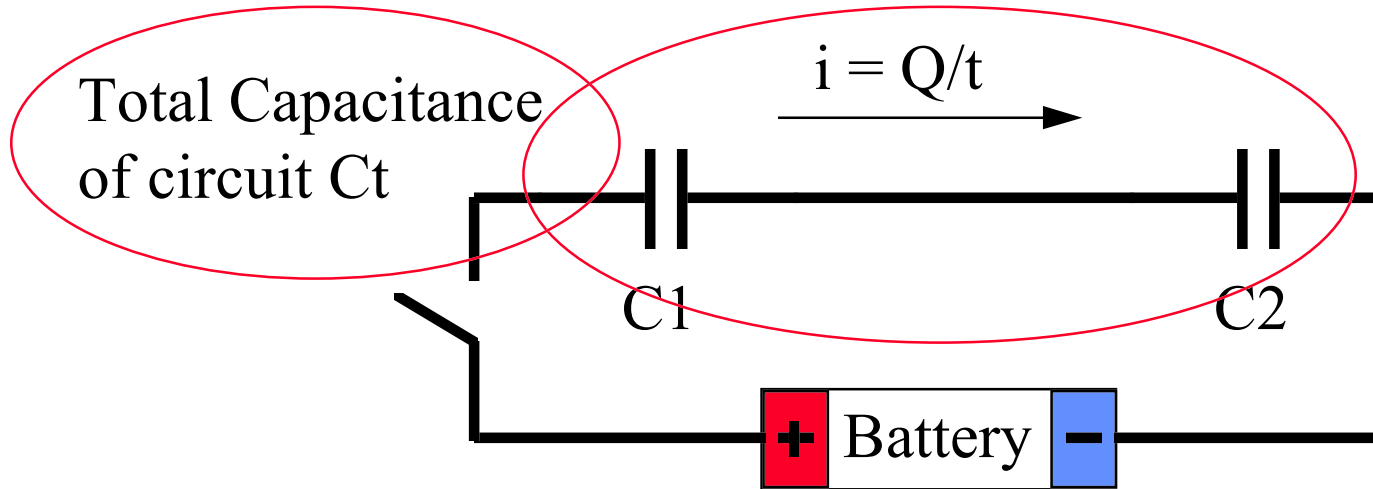

From Kirchhoff's laws . . . $V_{\text{Battery}} = V_{C1} + V_{C2}$

$$\text{or } V_{Ct} = V_{C1} + V_{C2} \quad \text{or} \quad \frac{Qt}{Ct} = \frac{Q1}{C1} + \frac{Q2}{C2}$$


However remember that $Qt = Q1 = Q2 = \text{say just } Q$ then

$$\frac{Q}{Ct} = \frac{Q}{C1} + \frac{Q}{C2}$$

or

$$\frac{1}{Ct} = \frac{1}{C1} + \frac{1}{C2} \dots\dots$$


Capacitors in parallel **Capacitors.**

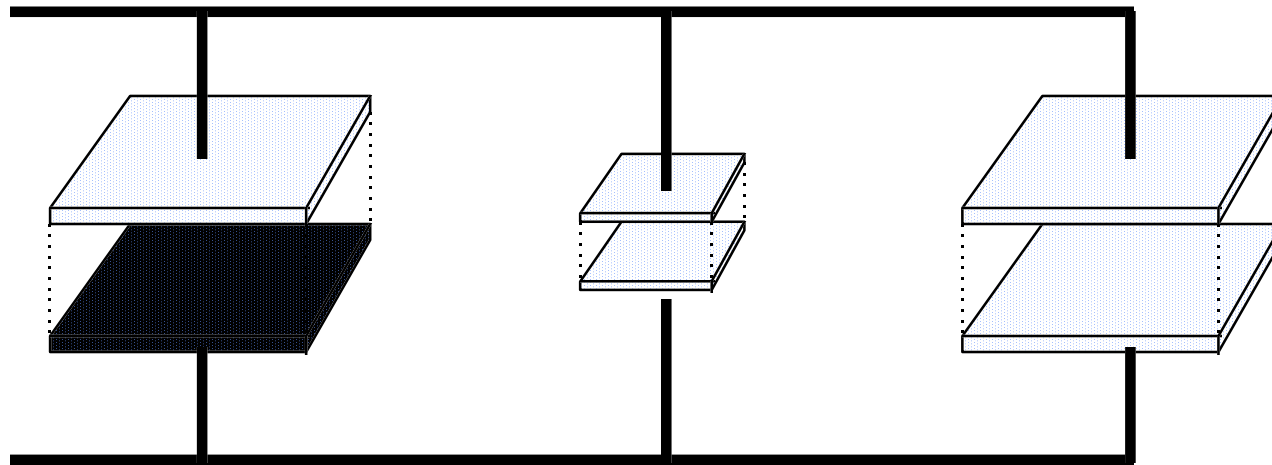

Note: Plate area of all the total capacitance becomes effectively the sum of the sizes of all the plates whilst the dielectric distances remain unchanged. Therefore the capacitance of capacitors in parallel is the sum of their values.

Capacitors in parallel **Capacitors.**


The Proof

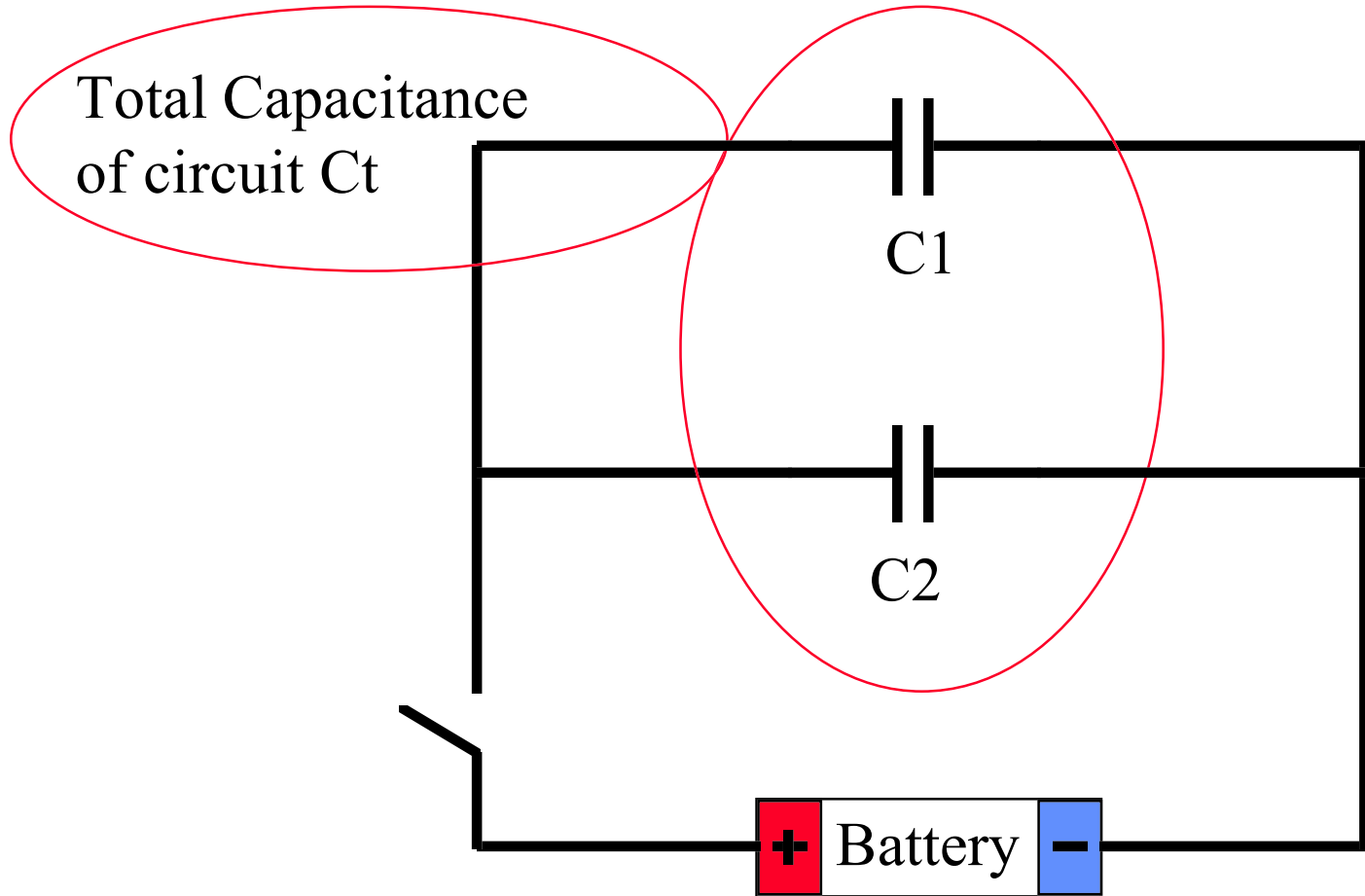

Capacitors in parallel **Capacitors.**

The Proof

Note: $Q = C * V$

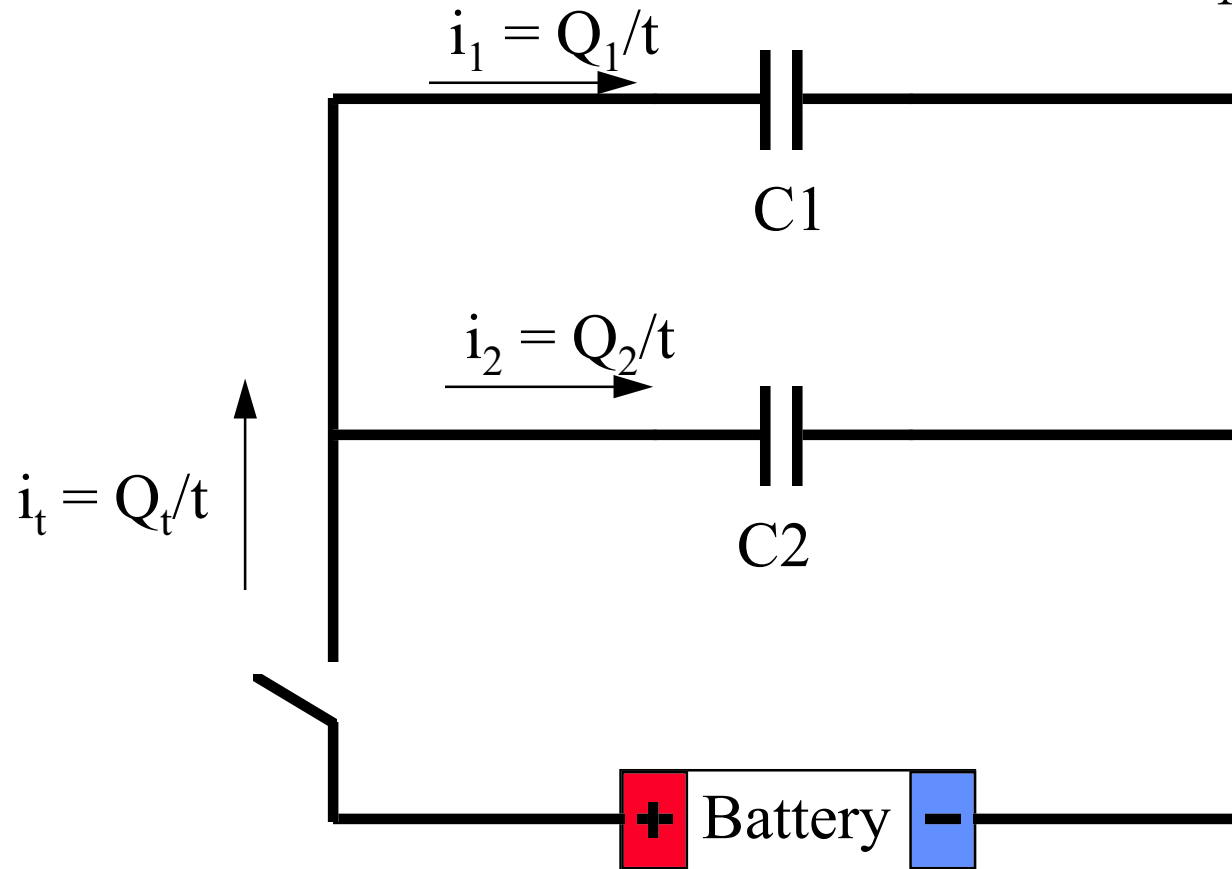

Note: Using Kirchhoff's laws The charge $Q_t = Q_1 + Q_2$

Capacitors in parallel **Capacitors.**

The Proof

So:-

$$C_t * V_{\text{Battery}} = C_1 * V_{\text{Battery}} + C_2 * V_{\text{Battery}}$$

$$(\cancel{C_t}) * \cancel{V_{\text{Battery}}} = (C_1 + C_2) * \cancel{V_{\text{Battery}}}$$

$$C_t = C_1 + C_2$$

The (V Battery) terms can cancel

which gives :-


$$C_t = C_1 + C_2$$

Thinking Exercise

Capacitors.

Initial conditions:

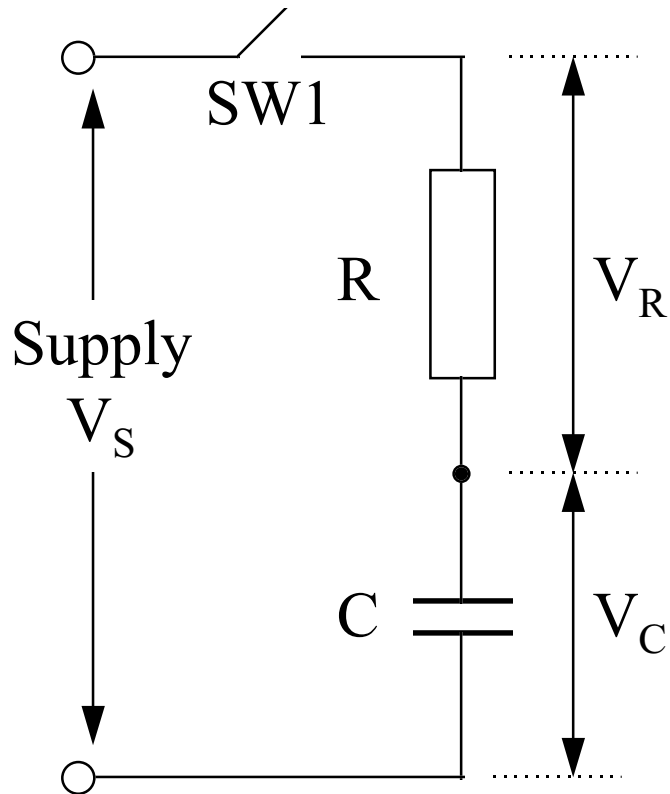Capacitor C contains no charge.
So what voltage is across it?



Solution:

$$Q = CV$$


as $Q = 0$ then

$$V_C = Q/C \text{ or } 0/C = 0 \text{ Volts}$$

Thinking Exercise

Capacitors.

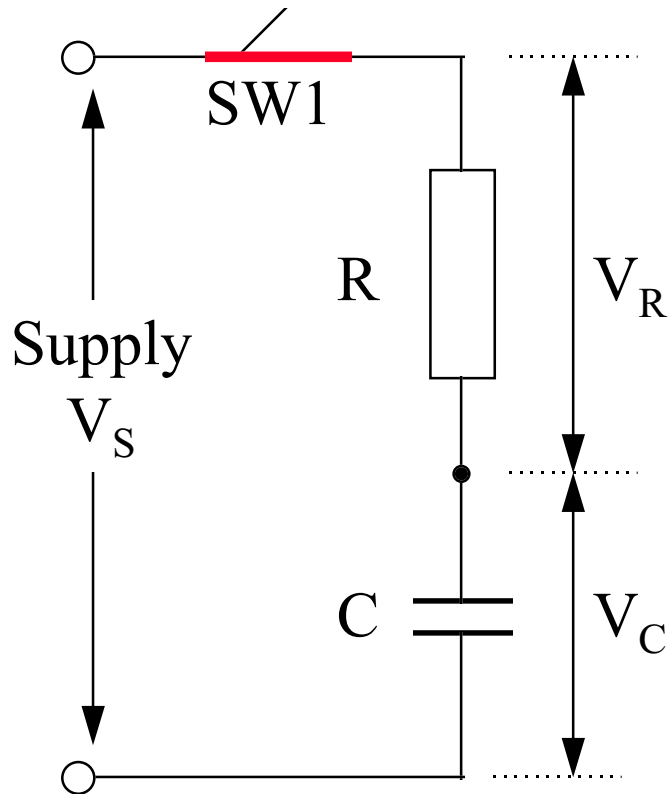The instant that SW1 is closed
what voltage will be present
across V_C and V_R ?



Solution:

$$Q = CV$$

as $Q = 0$ then

$$V_C = Q/C \text{ or } 0/C = 0 \text{ Volts}$$


therefore Voltage across V_R is

$$V_R = V_S - V_C = V_S - 0 = V_S$$

Thinking Exercise

Capacitors.

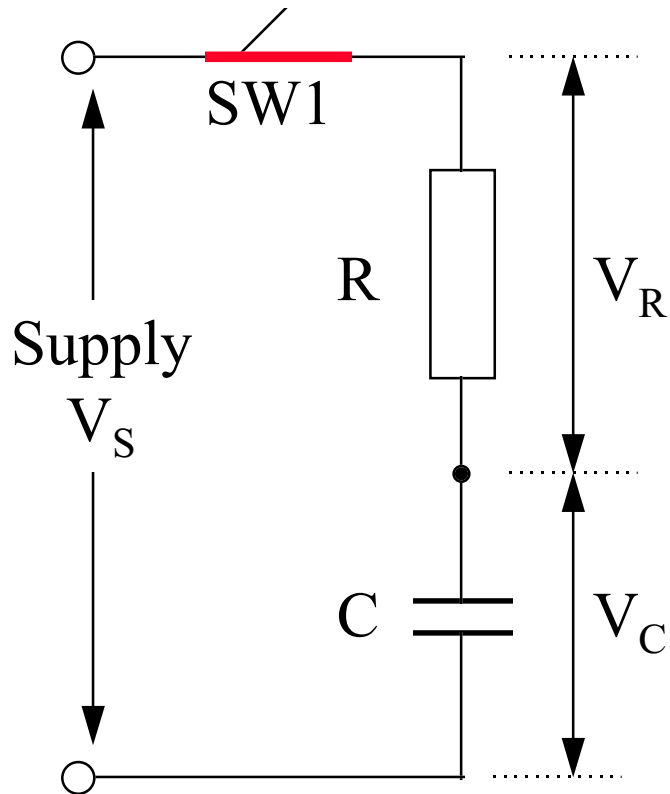After SW1 has been closed for a significant time what voltage will be present across V_C and V_R ?



Solution:


Capacitor becomes full charged
so $V_C = V_S$ Volts

therefore Voltage across V_R is
 $V_R = V_S - V_C = V_S - V_S = 0$

Thinking Exercise

Capacitors.

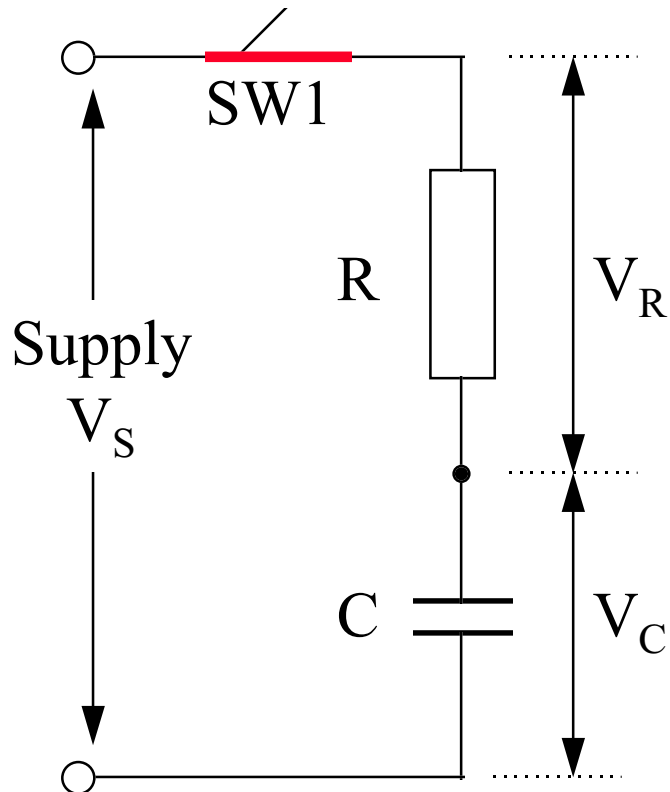After SW1 has been closed for a significant time what voltage will be present across V_C and V_R ?



Solution:

Capacitor becomes full charged
so $V_C = V_S$ Volts

therefore Voltage across V_R is
 $V_R = V_S - V_C = V_S - V_S = 0$

Note: As the capacitor charges the voltage across the capacitor rises and the charge rate slows. Therefore the charge rate is non linear. (1 / Exponential form)

Thinking Exercise

Capacitors.



Summary:

At switch on:

Voltage across Capacitor is minimum
Voltage across Resistor is maximum.

After a long period after switch on:

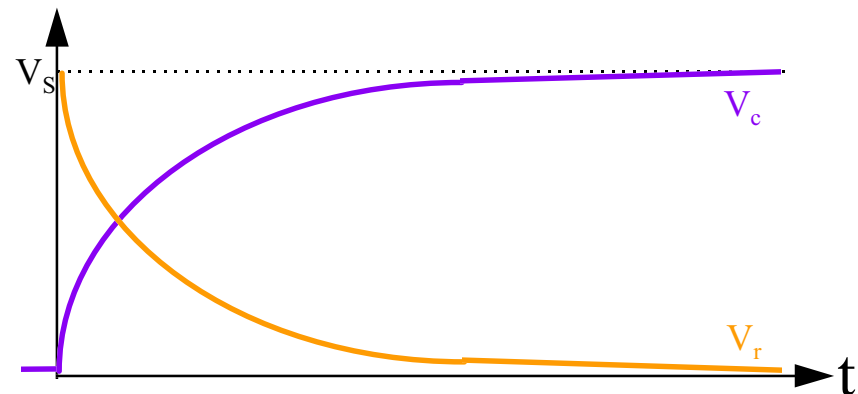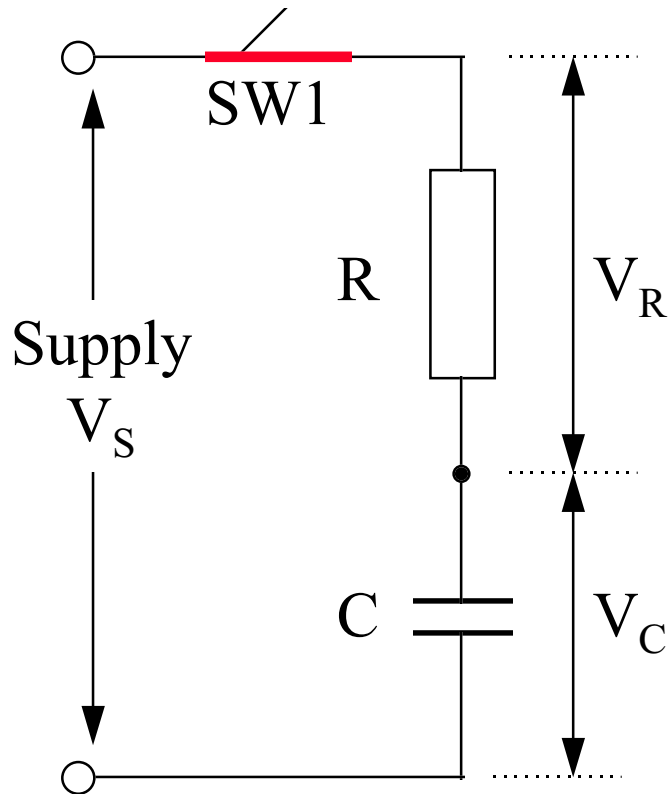
Voltage across Capacitor is maximum
Voltage across Resistor is minimum.



Capacitors.

Charging and Discharging cycles.


τ (tau) is the
The Time Constant.

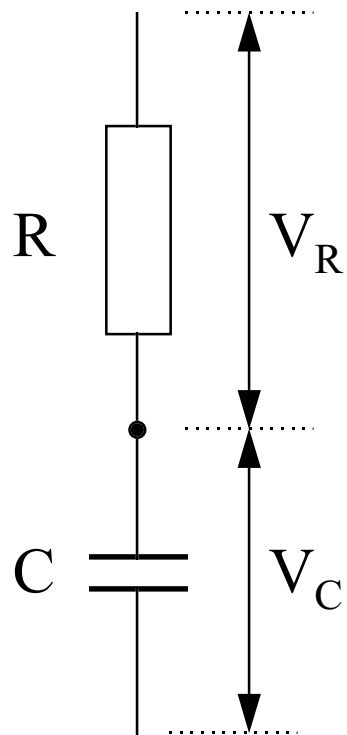

τ (tau) in seconds = C in Farads * R in Ohms

V_i = Voltage Initial

V_f = Voltage Final

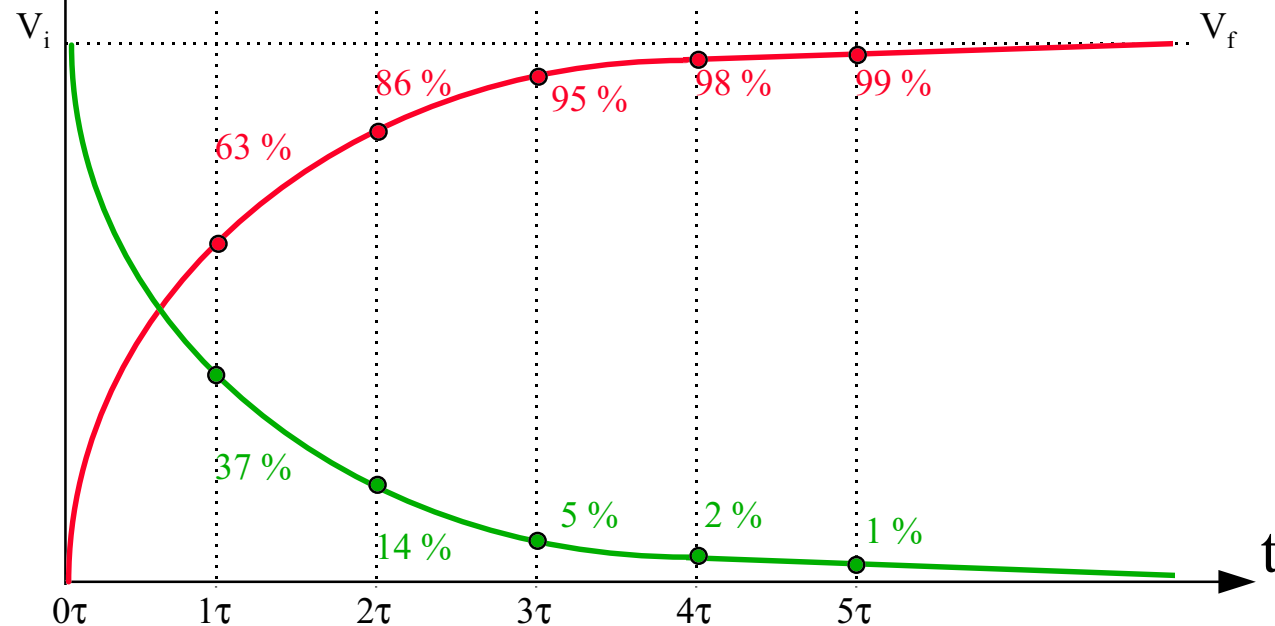

At 5τ the Capacitor is assumed to be **Fully** charged or discharged.

General Formula

Capacitors.

τ (tau) is the
The Time Constant.


$$v = V_f + (V_i - V_f)e^{-t/\tau}$$

$$i = I_f + (I_i - I_f)e^{-t/\tau}$$

t = time τ (tau) in seconds = C in Farads * R in Ohms

V_i / I_i = Voltage/Current Initial V_f / I_f = Voltage/Current Final

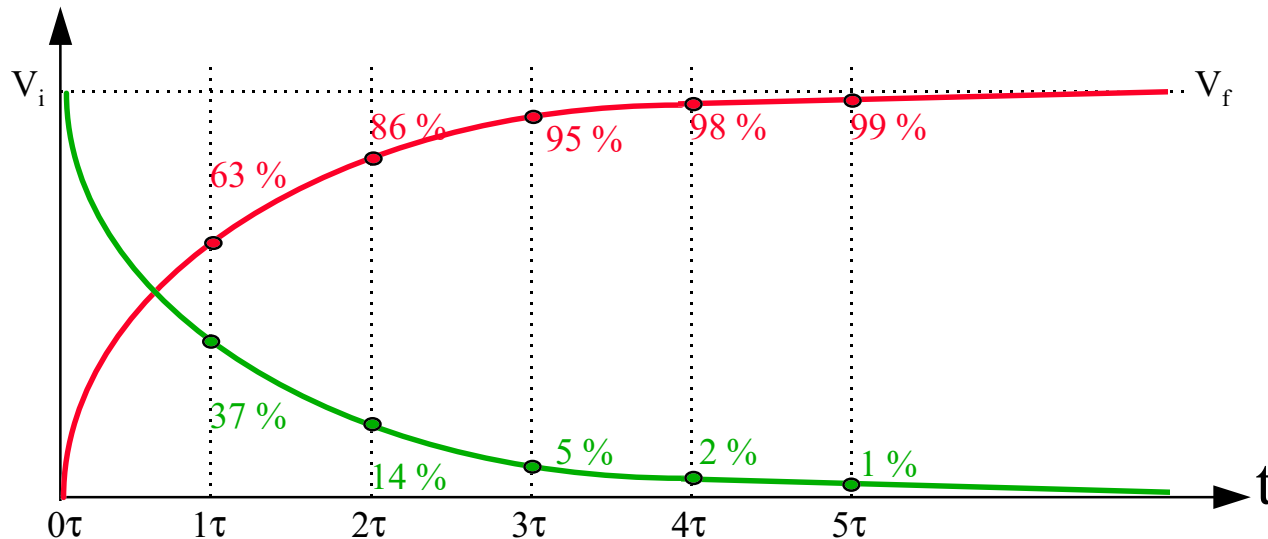v = instantaneous Voltage i = instantaneous Current



At 5τ the Capacitor is assumed to be **Fully** charged or discharged.
Charging and **Discharging** cycles.

Capacitors.


- A $4\mu\text{F}$ Capacitor is completely discharged. It is connected in series with a $6\text{K}8\Omega$ Resistor to a 48V supply through a single pole switch. The switch is closed what voltage will appear across the capacitor after 13.6ms .
 - a) Draw a diagram of the circuit and indicate the polarities of the supply and the capacitor after 13.6ms .
 - b) Determine the voltage across the Capacitor after 13.6ms .
 - c) Calculate how long it will take for the capacitor to be fully charged.

Solution

Capacitors.

- a) Draw a diagram of the circuit and indicate the polarities of the supply and the capacitor after 13.6ms.

SPST
Single Pole
Single Throw

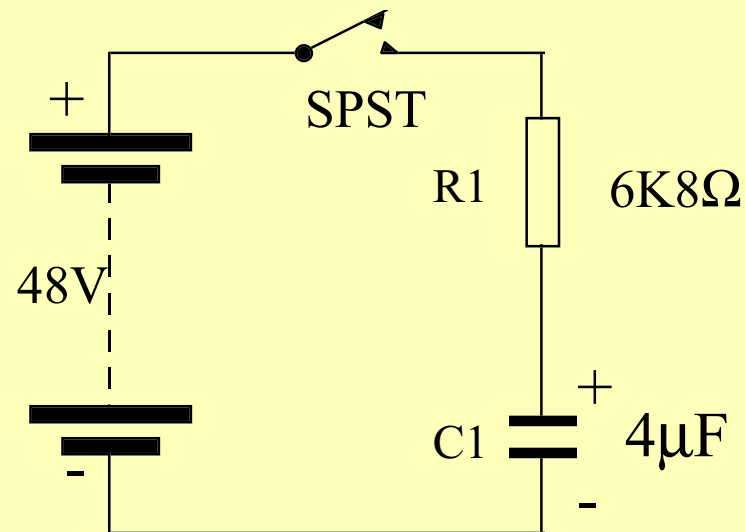

Solution

Capacitors.

- b) Determine the voltage across the Capacitor 13.6ms after the switch has been closed.
- $R = 6K8\Omega$, $C = 4\mu F$,
- $V_f = 48$ Volts, $V_i = 0$ Volts
- $t = 13.6ms$
- Initially Calculate τ (tau)
- $\tau = 4 * 10^{-6} * 6.8 * 10^3 = 27.2 * 10^{-3}$
- $\tau = 27.2 * 10^{-3}$ seconds or 27.2ms

Solution

Capacitors.

- $R = 6K8\Omega$, $C = 4\mu F$, $V_f = 48$ Volts, $V_i = 0$ Volts
- $t = 13.6ms$, τ (tau) = $27.2 * 10^{-3}$ seconds
- Using the formula $v = V_f + (V_i - V_f)e^{-t/\tau}$
- $v = 48 + (0 - 48)e^{-(13.6 * 10^{-3}/27.2 * 10^{-3})}$
- $v = 48 + (0 - 48)e^{-(0.5)}$
- Note: $e^{-(0.5)} = 1/e^{(0.5)}$ or $1/1.64872 = 0.60653$
- $v = 48 + (0 - 48) 0.60653 = 48 + (-48 * 0.60653)$
- $v = 48 + (-29.11347) = 48 - 29.11347 = 18.8865$
- Voltage across capacitor will be 18.8865 Volts

Solution

Capacitors.

- c) Calculate how long it will take for the capacitor to be fully charged.
- $R = 6K8\Omega$, $C = 4\mu F$, $V_f = 48$ Volts, $V_i = 0$ Volts
- $t = 13.6ms$, τ (tau) = $27.2 * 10^{-3}$ seconds
- A capacitor is assumed to be fully charged after 5τ .
- $5\tau = 5 * (27.2 * 10^{-3} \text{ seconds}) = 136 * 10^{-3}$
- Time required for capacitor to be fully charged will be 136 milli seconds.

Capacitors.


- A $20\mu\text{F}$ Capacitor is completely discharged. It is connected in series with a $1\text{M}\Omega$ Resistor to a 20V supply through a single pole switch. The switch is closed and the capacitor becomes fully charged.
 - a) Draw a diagram of the circuit and indicate the polarities of the supply and the capacitor when it is fully charged.
 - b) Determine the final charge on the Capacitor.
 - c) Calculate the energy stored in the capacitor when it is fully charged.
 - d) Calculate the value of the current immediately after the switch is closed.

Solution

Capacitors.

- a) Draw a diagram of the circuit and indicate the polarities of the supply and the capacitor when it is fully charged.

SPST
Single Pole
Single Throw

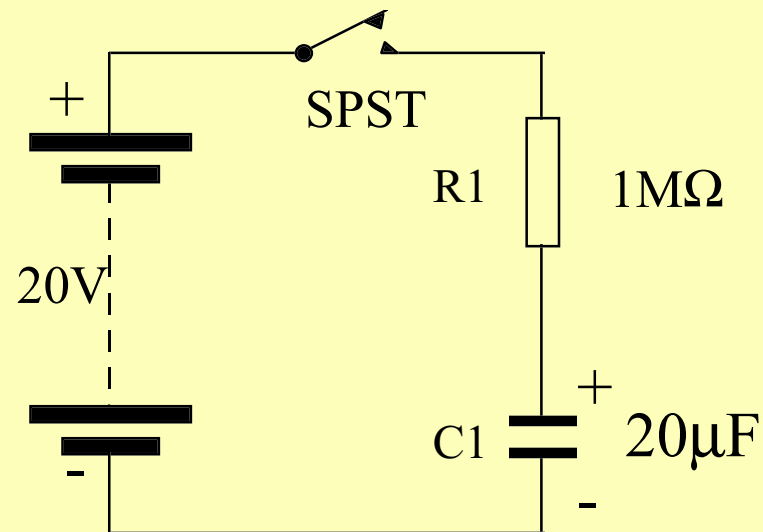

Solution

Capacitors.

- b) Determine the final charge on the Capacitor.
- Charge $Q = CV$ $C = 20\mu\text{F}$, $V = 20$ Volts
- Therefore Charge = $20 * 10^{-6} * 20 = 400\mu\text{C}$

Next Calculation.

- c) Calculate the energy stored in the capacitor when it is fully charged.
- Energy $W = \frac{1}{2}CV^2 = 0.5 * 20 * 10^{-6} * 20^2 = 4\text{mJ}$


Solution

Capacitors.

- d) Calculate the value of the current immediately after the switch is closed.
- Voltage across Capacitor = 0 Volts
- Voltage across Resistor = $V_{\text{Supply}} - 0 = 20\text{Volts}$
- Therefore as Resistor is totally responsible for limiting the current then $I = V/R$
$$= 20\text{V}/1\text{M}\Omega = 20/10^6 \text{ Amps}$$
- Current = $20\mu\text{A}$

Magnetism.

Magnetism.

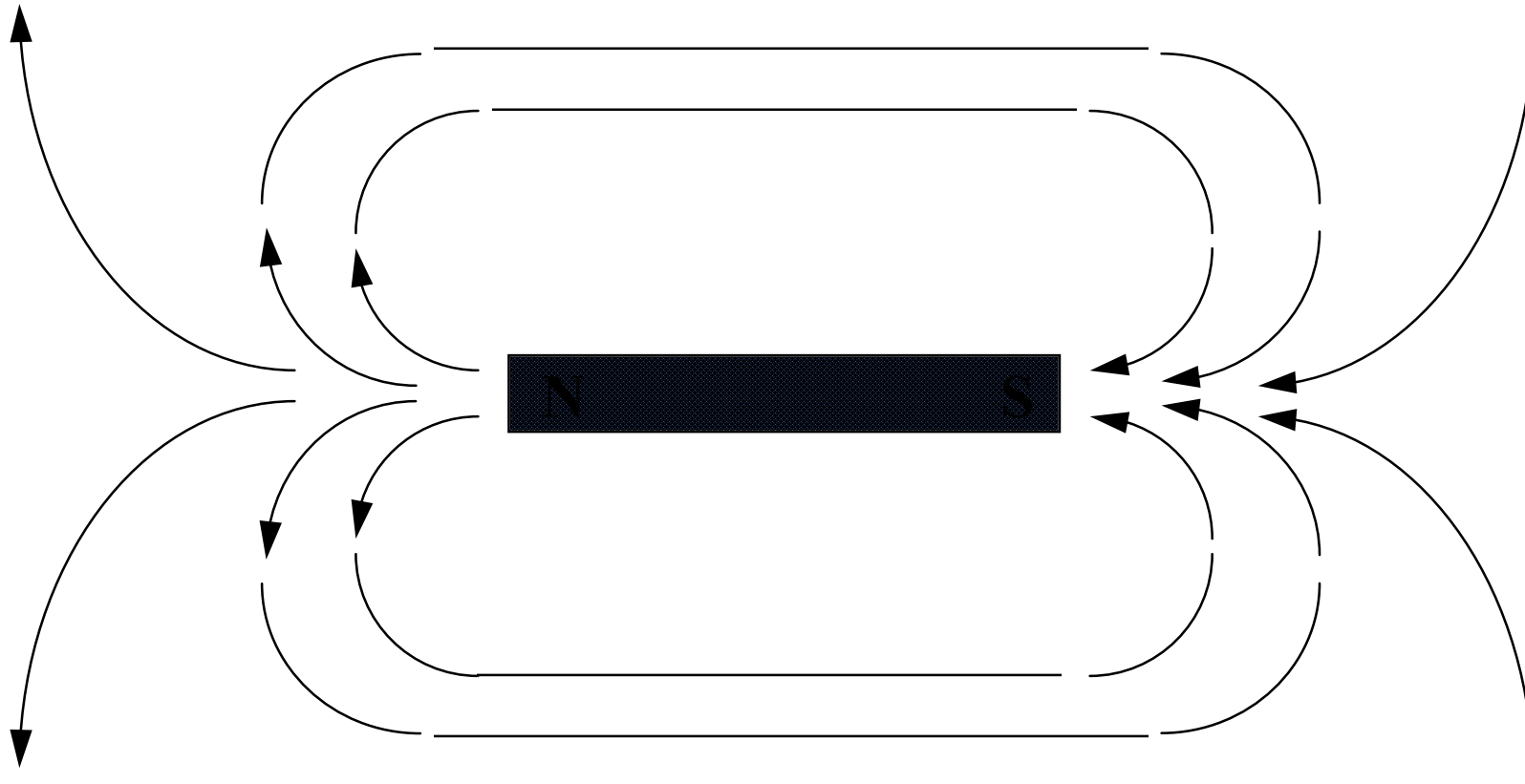


Lines of Flux around a Magnet

Magnetism.

- Terms and Concepts :-
- Magnetic Flux ϕ (phi) measured in Webers Wb
 - $1 \text{ Wb} = 10^8$ lines of Flux
 - or $1 \mu\text{Wb} = 100$ lines of Flux (more common Unit)

Magnetism.

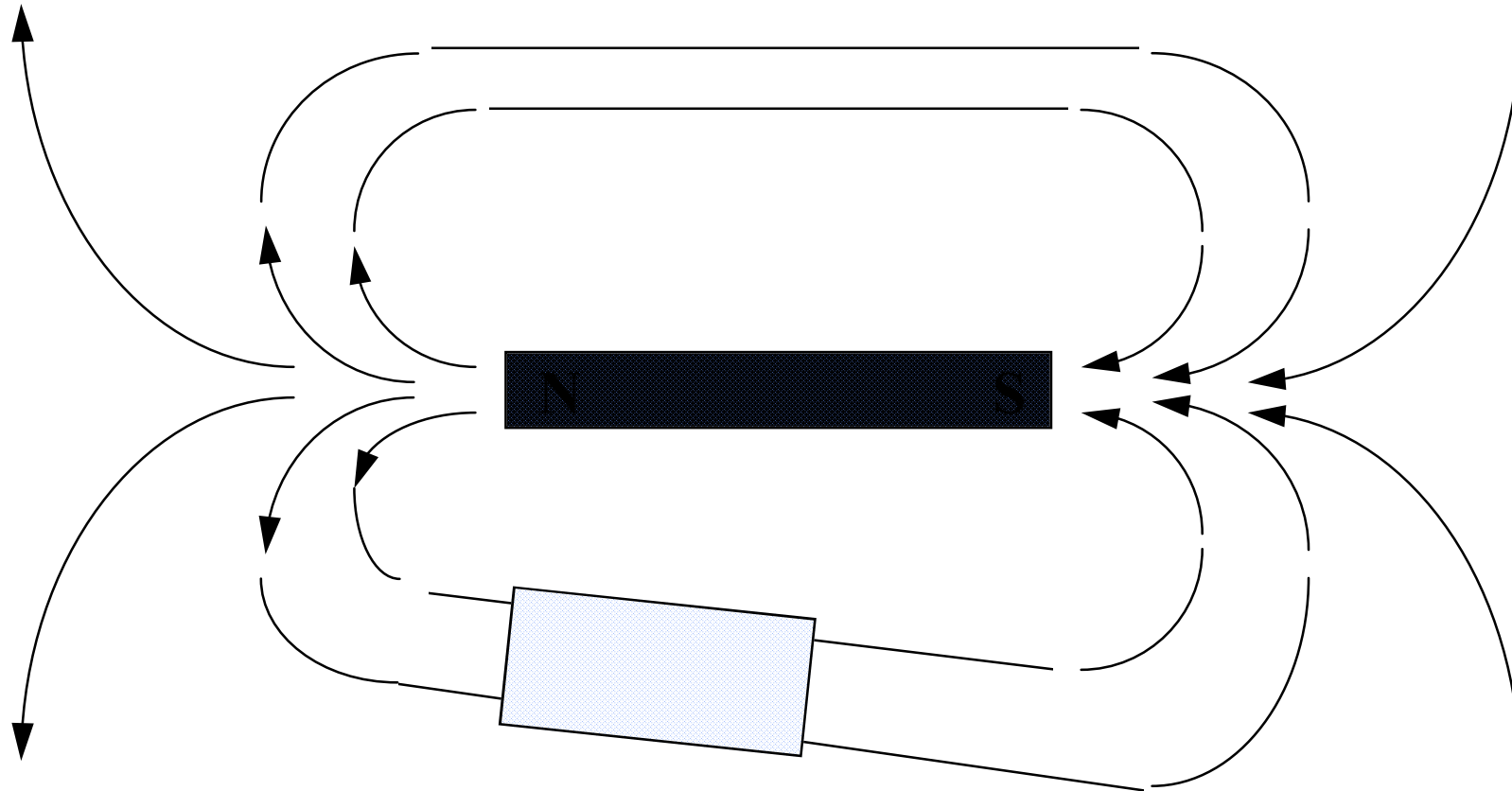


Lines of Flux around a Magnet Distorted by Iron Bar.

Magnetism.

- Terms and Concepts :-
- Magnetic Flux ϕ (phi) measured in Webers Wb
 - 1 Wb = 10^8 lines of Flux
 - or $1\mu\text{Wb} = 100$ lines of Flux (more common Unit)
- The line of flux can have their course changed or focused by the use of an Iron former.

Magnetism.

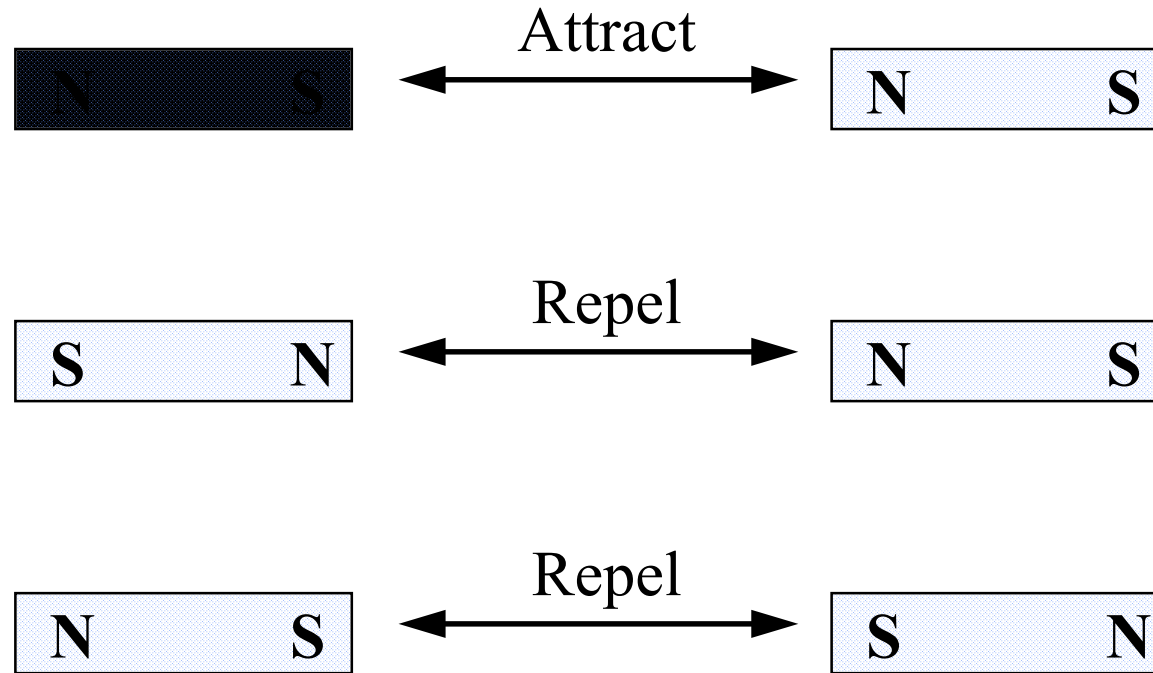

Magnet Attraction and Repulsion


Magnetism.

Strong Attraction



Lines of Force

Same Cross sectional area

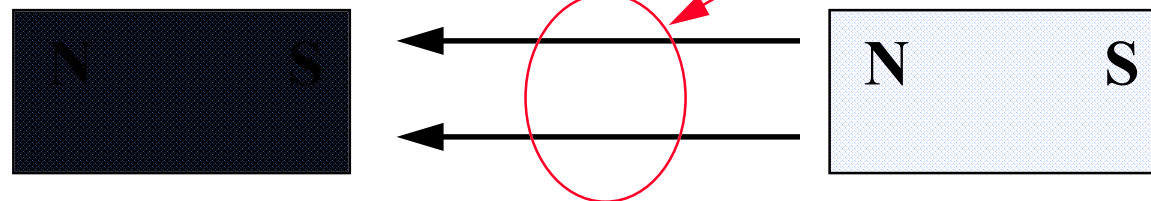

Weak Attraction

Magnet Attraction and Line of Force


Magnetism.

- Terms and Concepts :-
- Magnetic Flux ϕ (phi) measured in Webers Wb
 - 1 Wb = 10^8 lines of Flux
 - or $1\mu\text{Wb} = 100$ lines of Flux (more common Unit)
- The line of flux can have their course changed or focused by the use of an Iron former.
- Flux Density B measured in Wb/m^2 or Tesla (T)

$$\text{Flux Density } \mathbf{B} = \frac{\text{Magnetic Flux } \phi}{\text{Area in Metres}^2 \mathbf{A}}$$


Electromagnetism.

Electromagnetism.

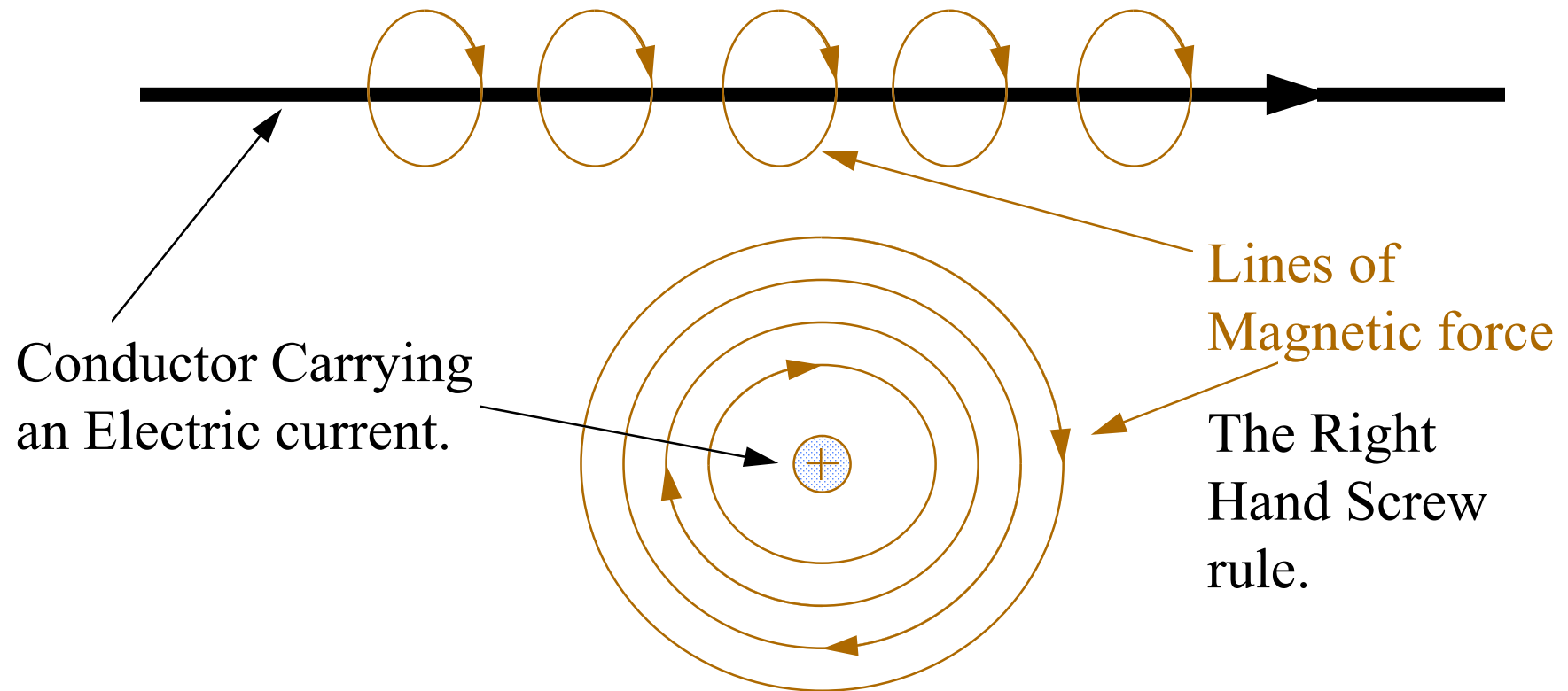

The Magnet effect of current passing through a conductor.


Electromagnetism.

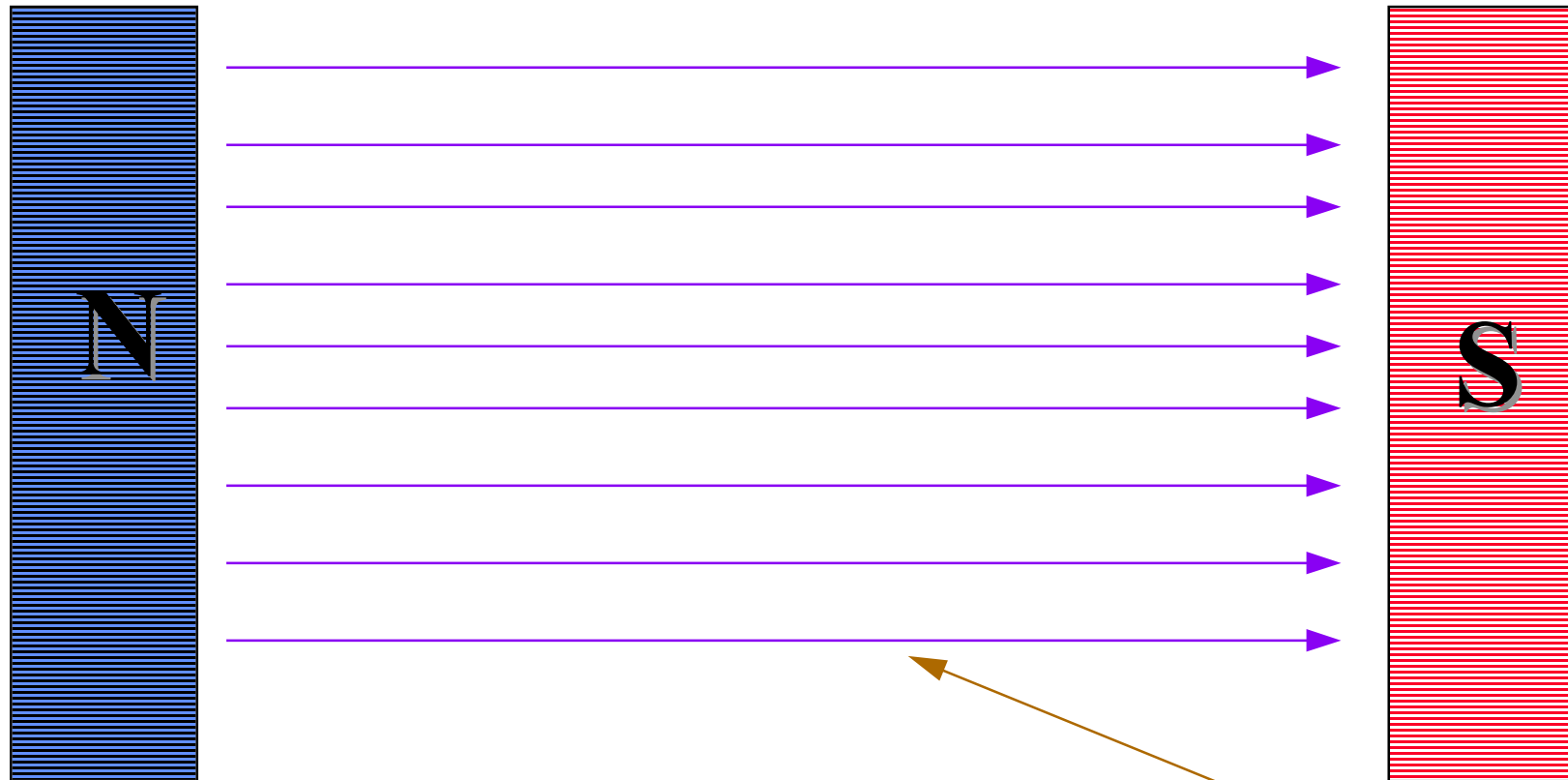

Lines of Magnetic
Force

Lines of Magnetic force.

Electromagnetism.

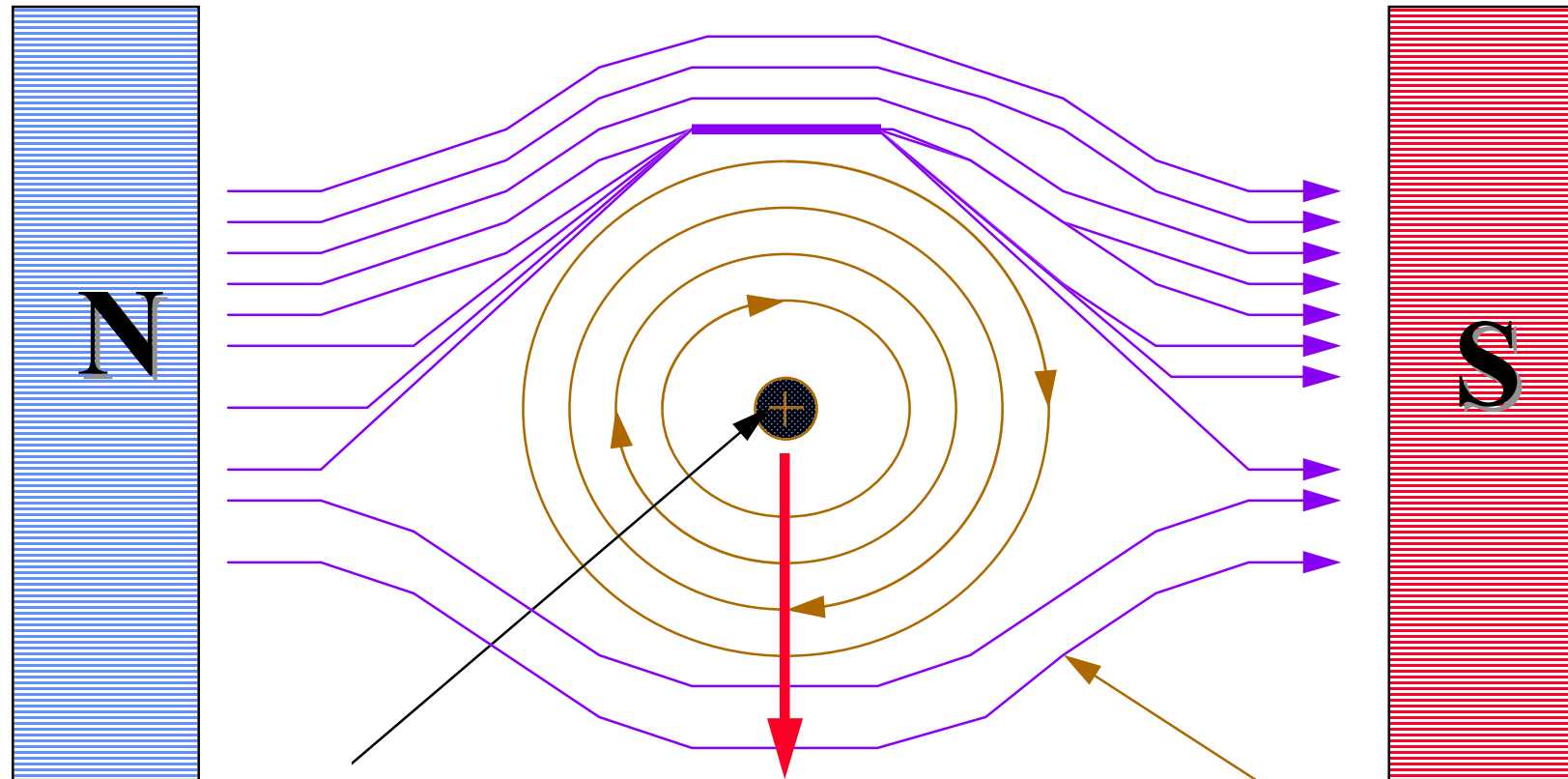

Conductor Carrying
an Electric current.

Direction of Motion
of the Conductor

Lines of Magnetic
Force

The effect of current passing through a conductor in a magnetic field.

Electromagnetism.

- Terms and Concepts :-
- Force on the current - carrying conductor in Newtons is dependent on :-
 - Flux Density B measured in Wb/m^2 or Tesla (T)
 - The Strength of the Current I amperes.
 - The length of the conductor perpendicular to the magnetic field, l metres, and
 - the directions of the field and the current

When Magnetic field and conductor are at right angles then:-
Force in newtons $F = \text{Flux Density } B * \text{Current } I * \text{Length } l$

When Magnetic field and conductor are at θ° to each other then:-
Force in newtons $F = B * I * l * \sin(\theta)$

Electromagnetism.

- Example:-
- Calculate the flux density in a piece of iron of circular cross-section, radius 5 cm, if the flux in the iron is 0.5 Wb.
- Calculate
 - (a) The Flux density.

Electromagnetism.

- Example:-
- Calculate the flux density in a piece of iron of circular cross-section, radius 5 cm, if the flux in the iron is 0.5 Wb.
- Calculations:-
 - Find the cross sectional area of the iron.

$$\text{Area of cross section} = \pi * R^2 = \pi * (5 * 10^{-2})^2 = 78.54 * 10^{-4} \text{ m}^2$$

Electromagnetism.

- Example:-
- Calculate the flux density in a piece of iron of circular cross-section, radius 5 cm, if the flux in the iron is 0.5 Wb.
- Calculations:-
 - Find the flux density.

$$\text{Area of cross section } A = \pi * R^2 = \pi * (5*10^{-2})^2 = 78.54*10^{-4} \text{ m}^2$$

$$\text{Flux density } B = \text{flux } \phi / \text{area } A = 0.5 / 78.54*10^{-4} = 63.66 \text{ Wb/m}^2$$

$$\text{Flux density } B = 63.66 \text{ Tesla}$$

Electromagnetism.

- Example:-
- A 1.5 cm length of wire is placed at right angles to a magnetic field of flux density 0.08T. A current of 2 amps flows. What amount of force is exerted between the wire and the flux?
- Calculate
 - (a) The force on the wire.

Electromagnetism.

- Example:-
- A 1.5 cm length of wire is placed at right angles to a magnetic field of flux density 0.08T. A current of 2 amps flows. What amount of force is exerted between the wire and the flux?
- Calculate
 - (a) The force on the wire.

Force = Flux Density B * Current I * Length of wire in flux L

$$\text{Force} = 0.08 * 2 * 1.5 * 10^{-2} = 2.4 * 10^{-3} \text{ Newtons}$$

Electromagnetism.

- Example:-
- A Flux of 1mWb is present in a square section air gap of 2cm by 2cm . A wire carrying 2 Amps is across the middle of the gap.
- Calculate
 - (a) The Flux density.
 - (b) The force on the wire.

Electromagnetism.

- Example:-
- A Flux of 1mWb is present in a square section air gap of 2cm by 2cm. A wire carrying 2 Amps is across the middle of the gap.
- Identify what we know:-
 - Length $l = 2 * 10^{-2}$
 - Area = $l * l = l^2 = 2 * 10^{-2} * 2 * 10^{-2} = 4 * 10^{-4} \text{ m}^2$
 - Flux $\phi = 10^{-3} \text{ Wb}$
 - Current $I = 2\text{A}$

Electromagnetism.

- Example:-
- The calculations:-
 - Length $l = 2 * 10^{-2}$
 - Area $A = 4 * 10^{-4} \text{ m}^2$
 - Flux $\phi = 10^{-3} \text{ Wb}$
 - Current $I = 2\text{A}$
 - Find Flux Density

$$\text{Flux Density } \mathbf{B} = \frac{\text{Flux } \phi}{\text{Area where the Flux flows}} \quad \text{Wb/m}^2$$

Electromagnetism..

- Example:-
- The calculations:-
 - Length $l = 2 * 10^{-2}$
 - Area $A = 4 * 10^{-4} \text{ m}^2$
 - Flux $\phi = 10^{-3} \text{ Wb}$
 - Current $I = 2\text{A}$
 - Find Flux Density

$$\text{Flux Density } B = \frac{10^{-3}}{4 * 10^{-4}} \text{ Wb/m}^2$$

$$\text{Flux Density } B = 2.5 \text{ Wb/m}^2$$

Electromagnetism.

- Example:-
- The calculations:-
 - Length $l = 2 * 10^{-2}$
 - Current $I = 2A$
 - Flux Density $B = 2.5 \text{ Wb/m}^2$
 - Find Force on wire.

Force **F** in Newtons =

Flux Density **B** * Current **I** * Length of wire in flux l


Electromagnetism.

- Example:-
- The calculations:-
 - Length $l = 2 * 10^{-2}$
 - Current $I = 2A$
 - Flux Density $B = 2.5 \text{ Wb/m}^2$
 - Find Force on wire.

$$\text{Force in Newtons} = 2.5 * 2 * 2 * 10^{-2}$$

$$\text{Force in Newtons} = 0.1 \text{ N}$$

Electromagnetism.

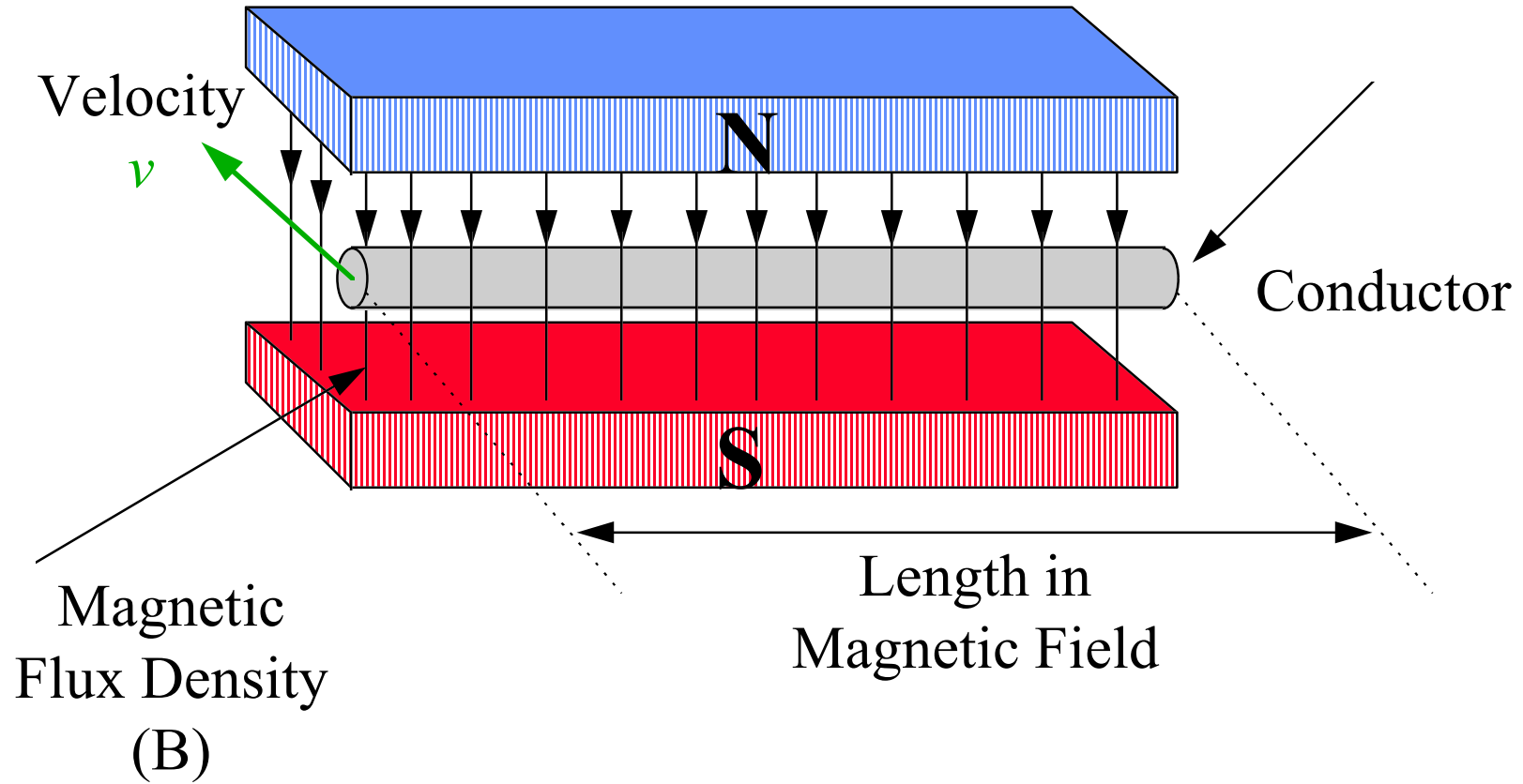

Electromagnetic Induction.

Electromagnetism.

- Terms and Concepts :-
- The induced electro motive force e.m.f. in a conductor in Volts is dependent on :-
 - Flux Density B measured in Wb/m^2 or Tesla (T)
 - The Velocity v that the conductor moves measured in metres per second.
 - The length of the conductor perpendicular to the magnetic field, l metres

When conductor moves at right angles Magnetic field and then:-

Induced e.m.f. $E = \text{Flux Density } B * \text{Length } l * \text{Velocity } v$

When Magnetic field and conductor are at θ° to each other then:-

Induced e.m.f. $E = B * l * v * \sin(\theta)$

Electromagnetism.

- Example:-
- A conductor 300mm long moves at a uniform speed of 4m/s at right angles to a uniform magnetic field of flux density 1.25T
- Calculate
 - The current flowing in the conductor when :-
 - (a) The ends are open circuited.
 - (b) The ends are terminated to a load of 20Ω .

Electromagnetism..

- Example:-
- The calculations:-
 - Length $l = 300 * 10^{-3}$
 - Velocity $v = 4$ metres/second
 - Flux Density $B = 1.25$ Tesla or 1.25 Wb/m^2

Induced e.m.f. $E =$


Flux Density B * Length of wire in flux l * Velocity v

$$E = 1.25 * (300 * 10^{-3}) * 4 = 1.5 \text{ volts}$$

Electromagnetism..


- Example:-
- The calculations:-
 - Length $l = 300 * 10^{-3}$
 - Velocity $v = 4$ metres/second
 - Flux Density $B = 1.25$ Tesla or 1.25Wb/m^2
 - Induced e.m.f $E = 1.5$ volts
- (a) If the ends of the conductor are open circuit no current will flow even though 1.5V has been induced.
- (b) From Ohm's law
$$I = V/R = 1.5/20 = 0.075\text{A or } 75\text{mA}$$

Electromagnetism.

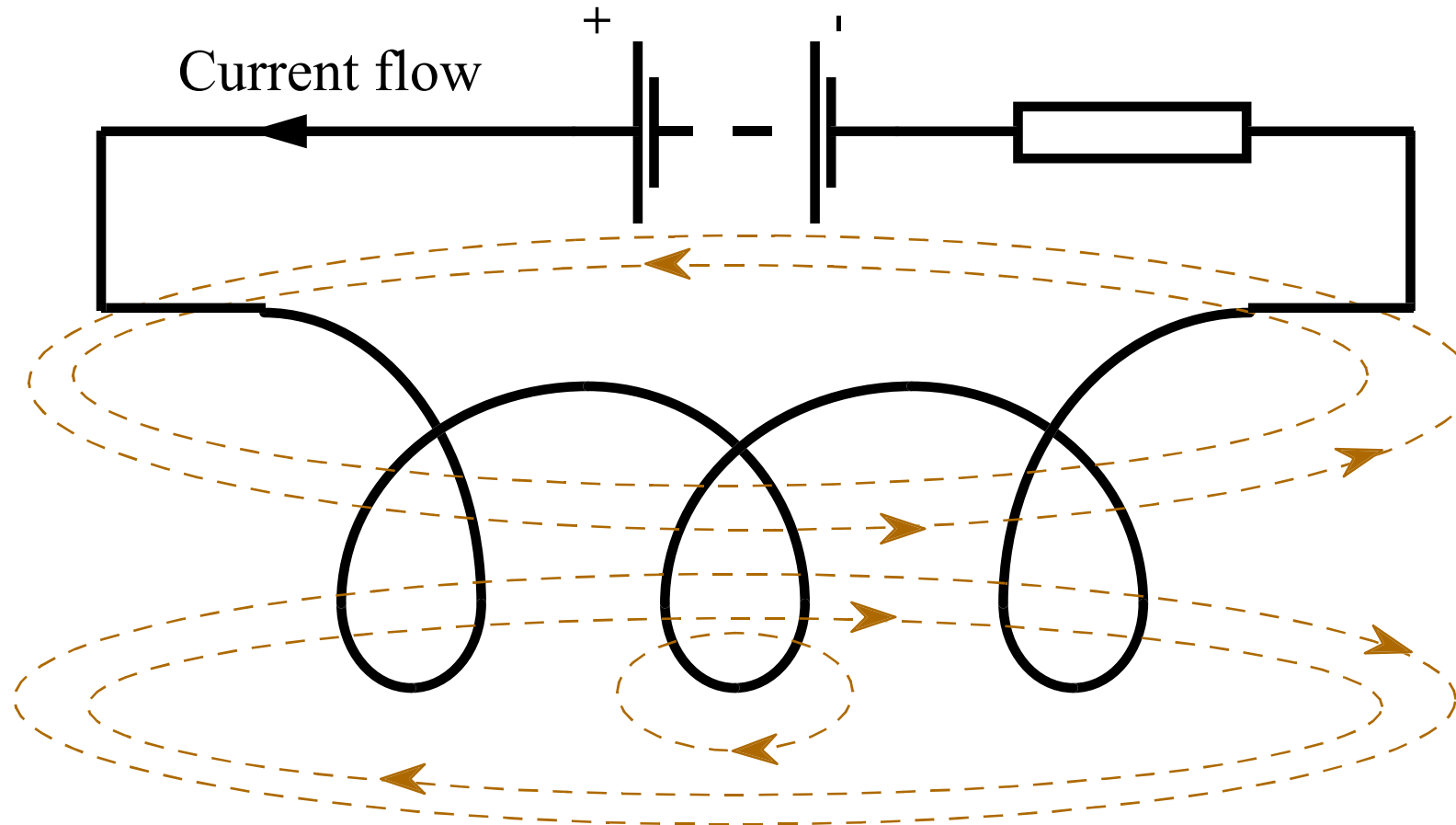

The Magnet effect of current passing through a coil or Solenoid.

Electromagnetism.

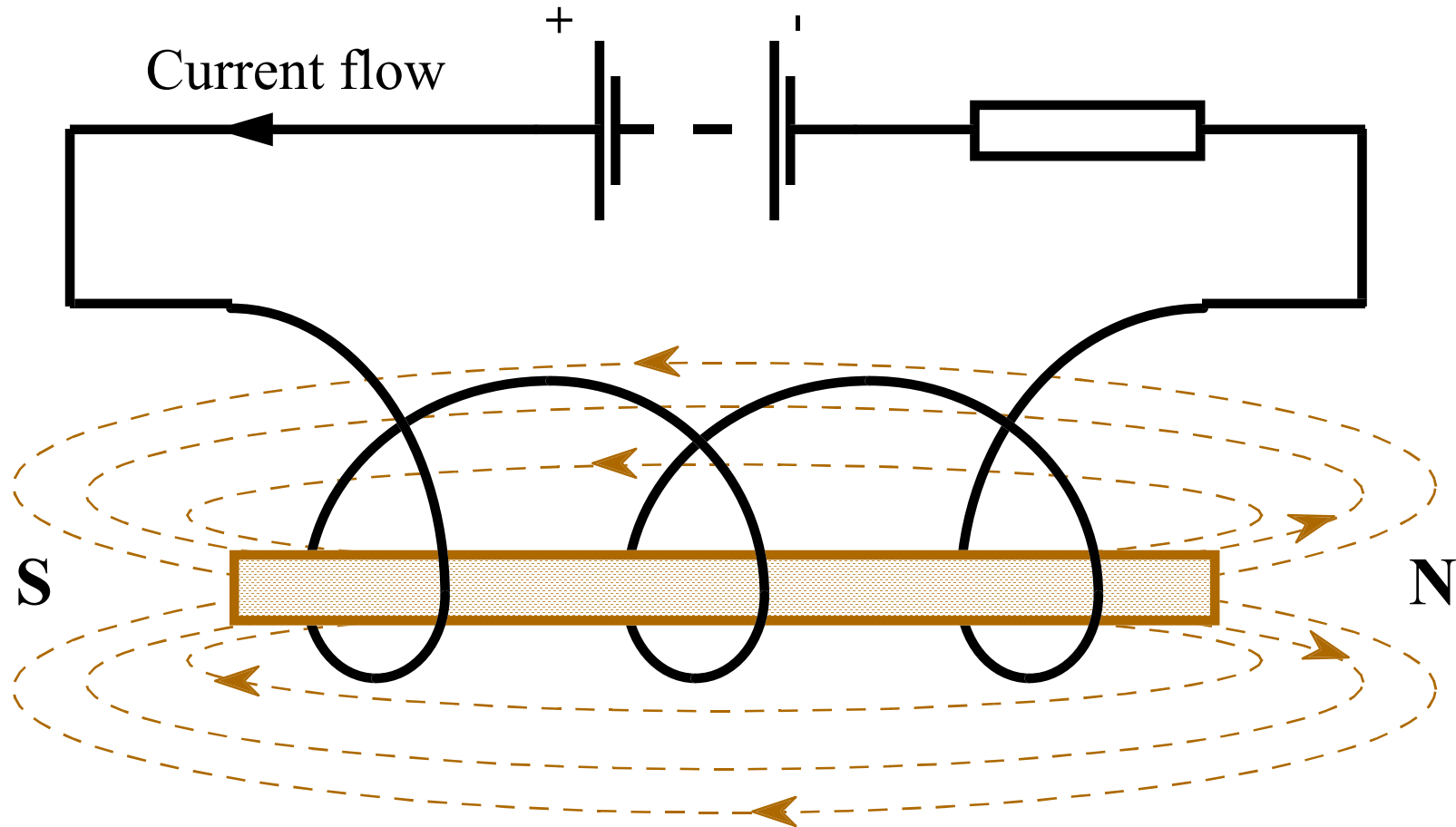

The Magnet effect Intensified due to insertion of an Iron Core.

Electromagnetism.

- You have seen that a current flowing in a wire produces a magnetic field
- The force that produces the magnetic field is the **magnetomotive force (mmf)**
- The unit of **mmf** is the Ampere-turn (**At**) is established on the basis of the current in a single loop(turn) of wire.

$\text{mmf} = \text{Number of Turns} * \text{Current in Amperes}$

$$F_m = N * I$$

Electromagnetism.

- Terms and Concepts :-
- The Magnetising Force (H) depends on three factors:-
 - The number of turns (N) of the coil of wire
 - The current through the coil.
 - The length of the coil
 - It does **NOT** depend on the type of material.
- Magnetising Force H measured in At/m .
 - At/m = Ampere turns per metre.

$$\text{Magnetising Force } \mathbf{H} = \frac{\text{Magnetomotive Force } F_m}{\text{Length in Metres } l}$$

Electromagnetism.

- Permeability (μ):-
- The ease with which a magnetic field can be established in a given material is measured by the **permeability** of the material.
- The higher the permeability, the more easily a magnetic field can be established.
- The symbol of permeability is μ (the Greek letter mu).
- The Permeability value $\mu = \mu_0 * \mu_r$ (in Weber per ampere turn metre (Wb/Atm))
 - where μ_0 = permeability of a vacuum.
 - μ_r = relative permeability of the material.
 - $\mu_0 = 4\pi * 10^{-7}$ Wb/Atm.

Electromagnetism.

- Reluctance (\mathfrak{R}):-
- The opposition to the establishment of a magnetic field in a material is called **reluctance** (\mathfrak{R}).
- The value of reluctance is directly proportional to the length (l) of the magnetic path, and inversely proportional to the permeability (μ) and the cross sectional area (A) of the material and is expressed with the following equation:-

$$\mathfrak{R} = \frac{l}{\mu A}$$

A = Area in square metres.

l = Length in metres.

μ = in Wb/Atm.

\mathfrak{R} = Reluctance in Ampere-turn/Weber.

Electromagnetism.

- Example:-
- What is the reluctance of a material that has :-
- A length of 0.05m,
- A cross sectional area of 0.012 m²,
- and a permeability of 3500 $\mu\text{Wb/Atm}$?

Electromagnetism.

- Example:-
- What is the reluctance of a material that has :-
- A length of 0.05m,
- A cross sectional area of 0.012 m²,
- and a permeability of 3500 μWb/Atm?

$$\mathfrak{R} = \frac{l}{\mu A} = \frac{0.05}{3500 * 10^{-6} * 0.012} = 1190 \text{ At/Wb}$$

Concept. Electromagnetism.

- Ohms law of magnetic circuits :-
- The flux is (ϕ) analogous to current, the mmf (F_m) is analogous to voltage, and the reluctance (\mathcal{R}) is analogous to resistance.

$$\mathcal{R} = \frac{F_m}{\phi}$$

$$F_m = \mathcal{R} * \phi$$

or

$$\phi = \frac{F_m}{\mathcal{R}}$$

F_m = Magnetomotive force (mmf).

ϕ = in Wb.

\mathcal{R} = Reluctance in Ampere-turn/Weber.

Electromagnetism.

- Example:-
- There are two amperes through a wire with five turns :-
- What is the mmf?
- What is the reluctance of the circuit if the flux is $250 \mu\text{Wb}$?

Electromagnetism.

- Example:-
- There are two amperes through a wire with five turns :-
- What is the mmf?
- What is the reluctance of the circuit if the flux is $250 \mu\text{Wb}$?

Solution

$$N = 5 \quad \text{and} \quad I = 2\text{A}$$

$$F_m = NI = (5t) * (2\text{A}) = 10\text{At}$$

Electromagnetism.

- Example:-
- There are two amperes through a wire with five turns :-
- What is the mmf?
- What is the reluctance of the circuit if the flux is $250 \mu\text{Wb}$?

Solution

$$F_m = 10 \quad \text{and} \quad \phi = 250 \mu\text{Wb}$$

$$\mathfrak{R} = 10 \text{At} / 250 * 10^{-6} = 0.04 * 10^6 = 4 * 10^4 \text{ At/Wb}$$

$$\mathfrak{R} = \frac{F_m}{\phi}$$

Electromagnetism.

Relating units B & H

Where

B = Flux Density.

and

H = Magnetising force.

Electromagnetism.


- **Hysteresis** is a characteristic of a magnetic material where a change in magnetisation lags the application of a magnetising force.
- The magnetising force (H) can readily be increased or decreased by varying the current through the coil of wire.
- The magnetising force (H) can readily be reversed by reversing the voltage polarity across the coil of wire.

Electromagnetism.

Initial situation:

Magnetic core is unmagnetised


$$B = 0$$

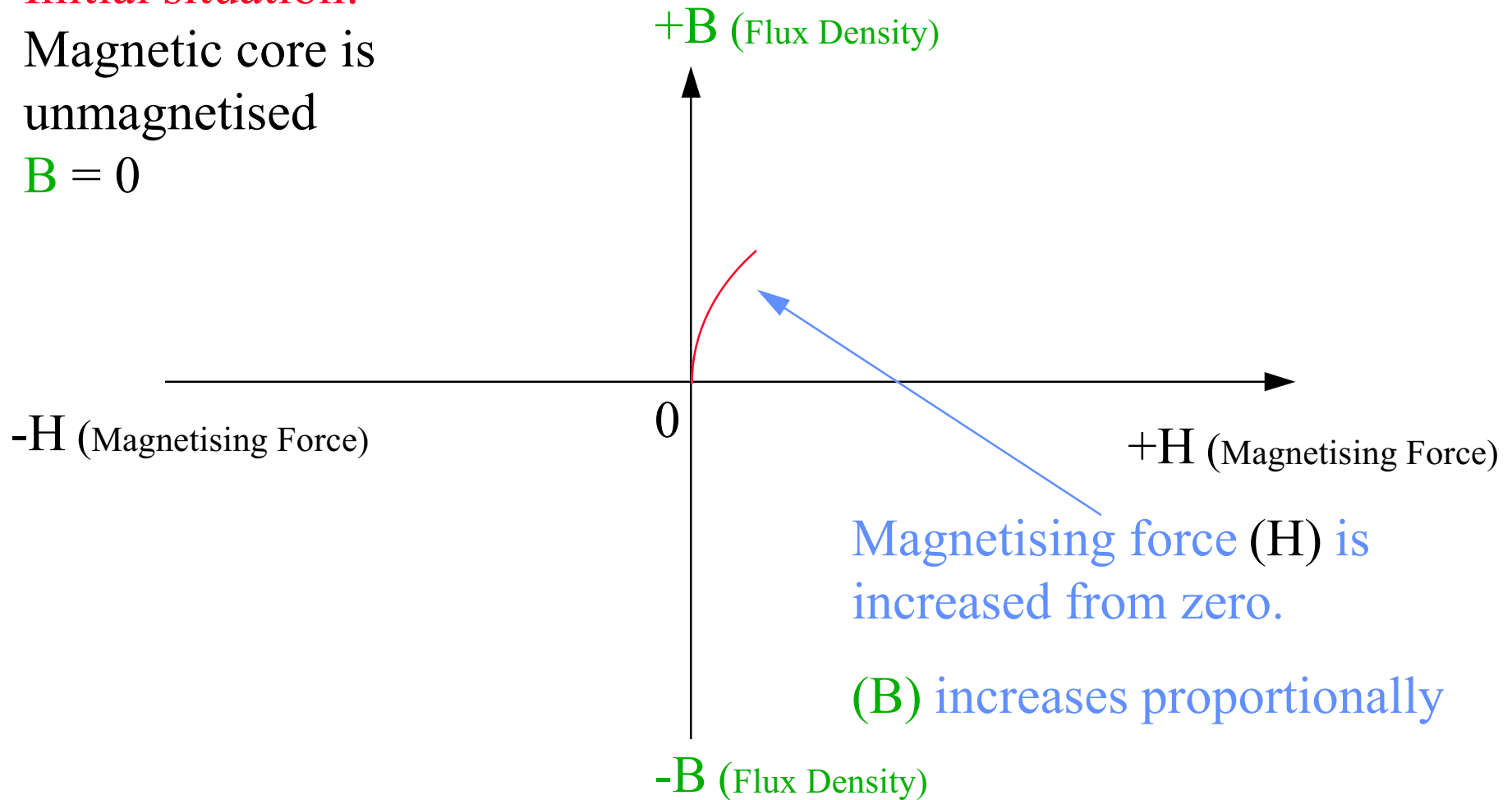

The Hysteresis Curve and Retentivity.

Electromagnetism.

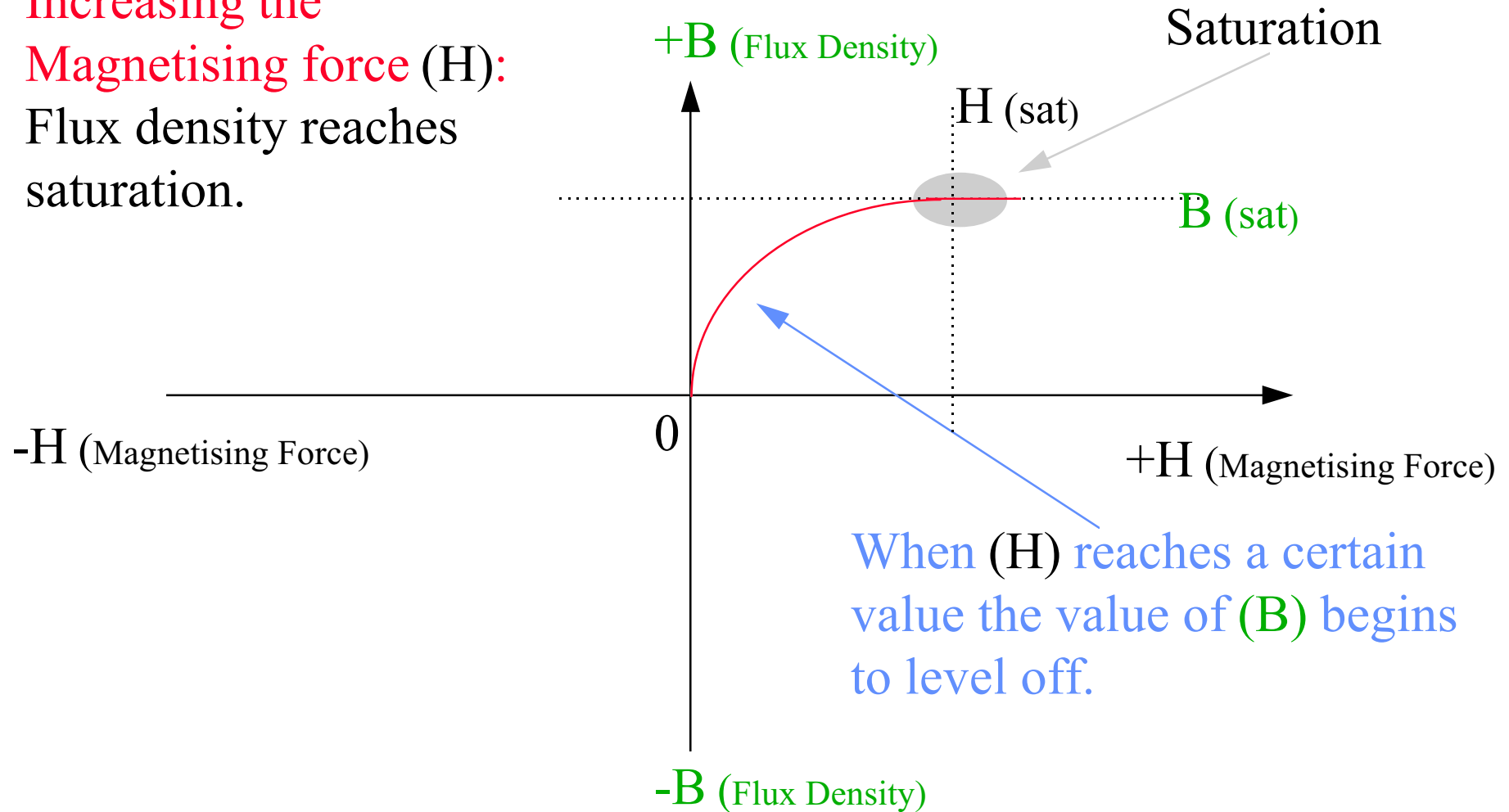Increasing the
Magnetising force (H):
Flux density reaches
saturation.



The Hysteresis Curve and Retentivity.


Electromagnetism.

Reducing the Magnetising force (H): back to zero.

The fact that (B) has not returned to zero indicates that the material is still magnetised

-H (Magnetising Force)

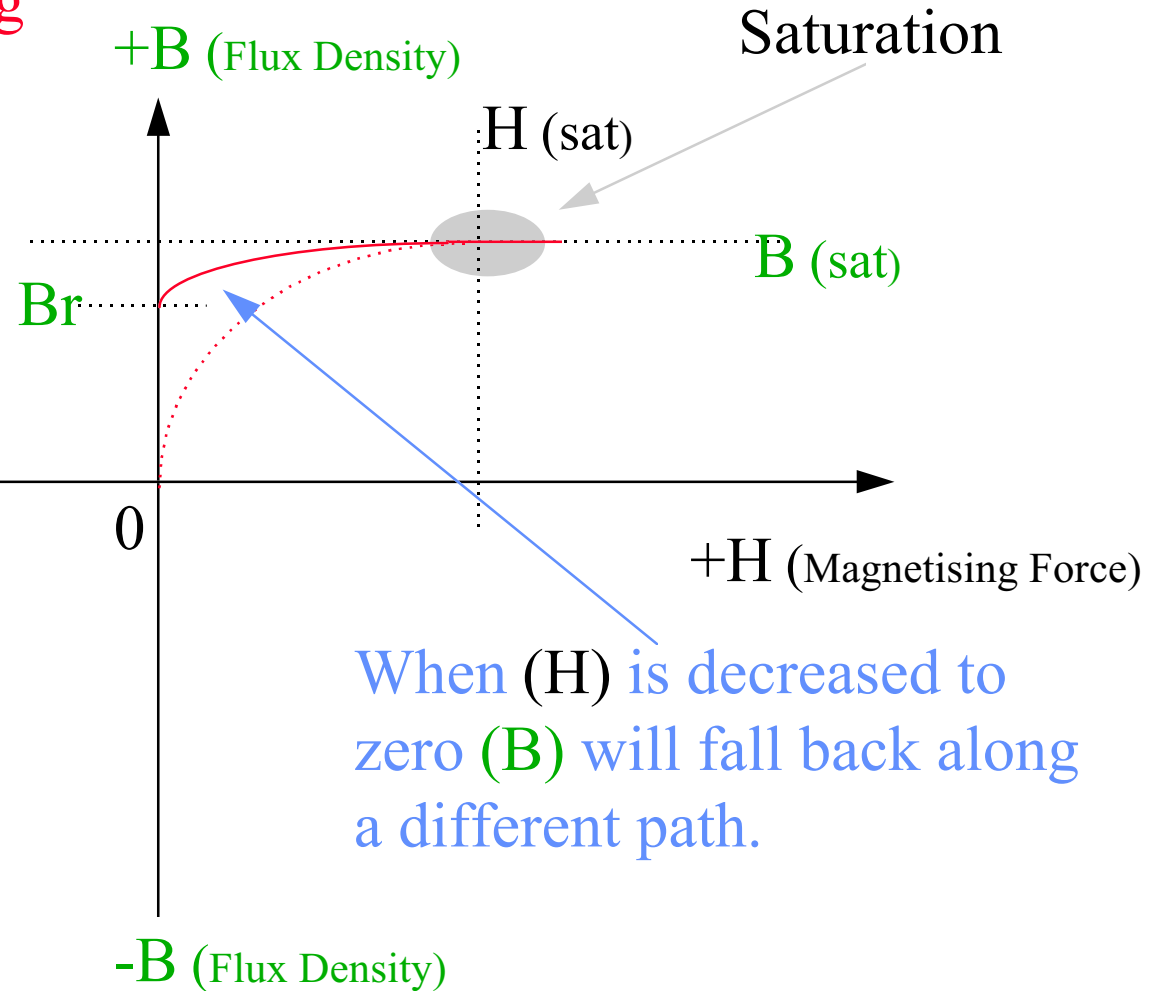The Retentivity of the material is indicated by the ratio of B_r to $B(\text{sat})$.




When (H) is decreased to zero (B) will fall back along a different path.

The Hysteresis Curve and Retentivity.

Electromagnetism.

Reducing the Magnetising force (H): back to zero.

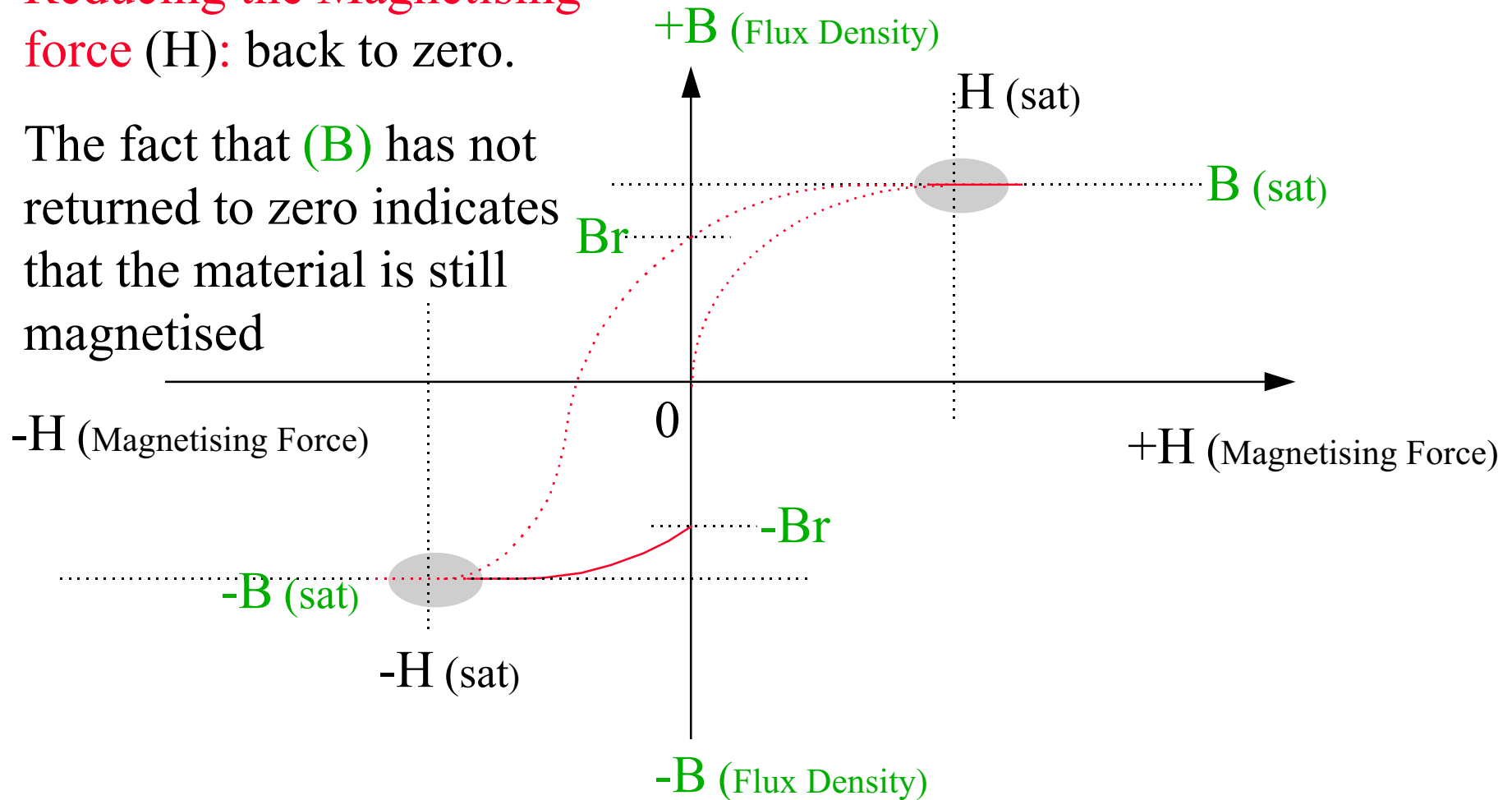The fact that (B) has not returned to zero indicates that the material is still magnetised




The Hysteresis Curve and Retentivity.

Electromagnetism.

Increasing the Magnetising force (H): back to H sat.


This completes the BH curve cycle.

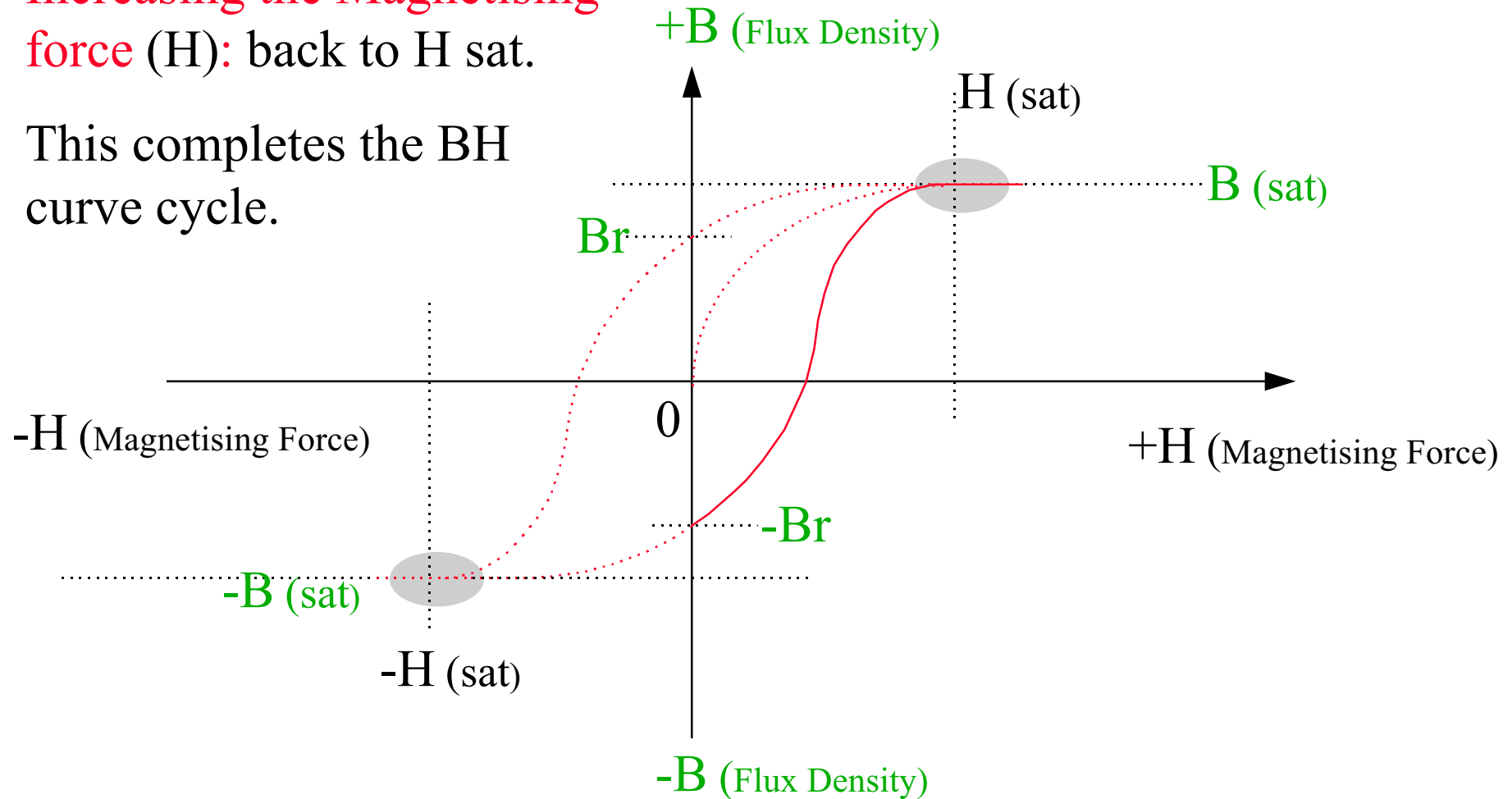

The Hysteresis Curve and Retentivity.

Electromagnetism.

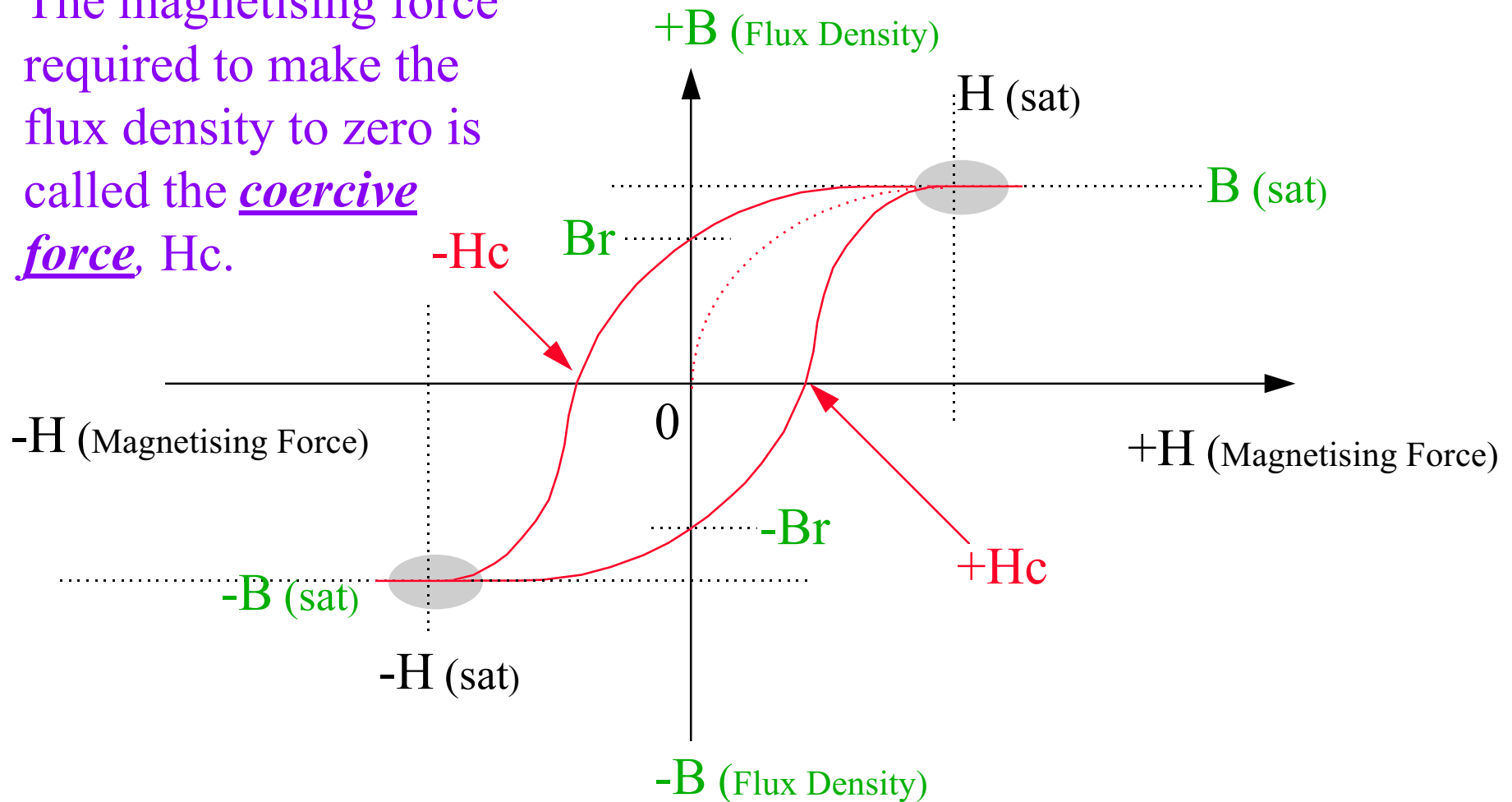The magnetising force required to make the flux density to zero is called the coercive force, H_c .




The Hysteresis Curve and Retentivity.

Electromagnetism.

Summary

- Material with a **Low Retentivity** do not retain magnetic fields very well.
- A permanent magnet requires a material with a **High Retentivity**.
- In AC Motors and Transformers **Retentivity** is undesirable because the residual magnetic field must be overcome each time the current reverses wasting energy.

Electromagnetism.

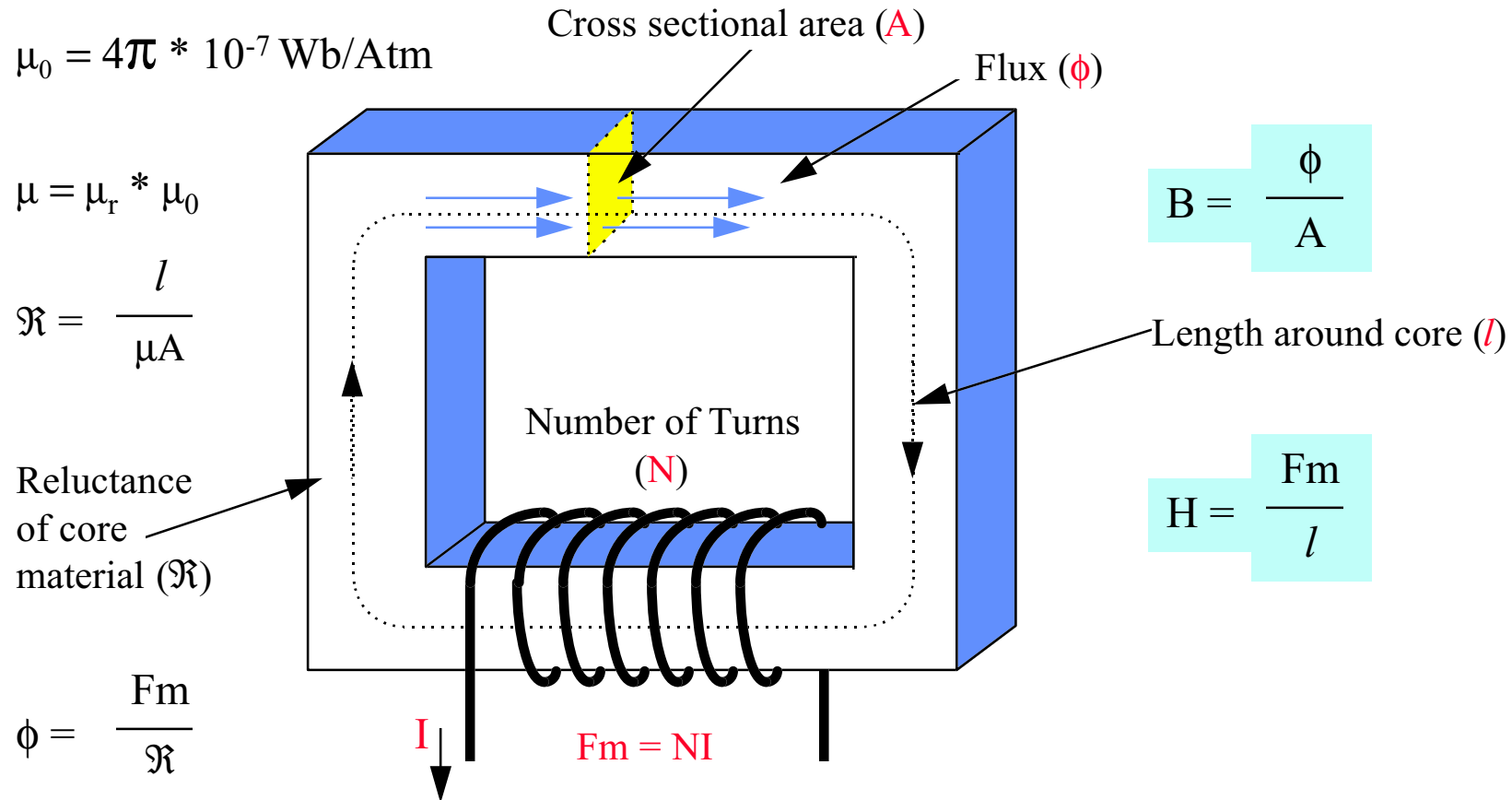

Electromagnetic Relationships.

Electromagnetism.

$$\mu_0 = 4 \pi * 10^{-7} \text{ Wb/Atm}$$

$$\mu = \mu_r * \mu_0$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

Reluctance
of core
material (\mathfrak{R})

$$\phi = \frac{Fm}{\mathfrak{R}}$$

$$\phi * \mathfrak{R} = Fm$$

What we are looking
for now is the
relationship between
B and H

$$H = \frac{Fm}{l}$$

$$B = \frac{\phi}{A}$$

Electromagnetic Relationships.

Electromagnetism.

$$\mu_0 = 4\pi * 10^{-7} \text{ Wb/Atm}$$

$$H = \frac{Fm}{l}$$

$$\mu = \mu_r * \mu_0$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

Reluctance
of core
material (\mathfrak{R})

$$B = \frac{\phi}{A}$$

$$\phi = \frac{Fm}{\mathfrak{R}}$$

$$\phi * \mathfrak{R} = Fm$$

Re-arrange:

To make Cross sectional
Area "A" the focus of the
equation

Electromagnetic Relationships.

Electromagnetism.

$$\mu_0 = 4\pi * 10^{-7} \text{ Wb/Atm}$$

$$\mu = \mu_r * \mu_0$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

$$A = \frac{l}{\mu * \mathfrak{R}}$$

Reluctance
of core
material (\mathfrak{R})

$$\phi = \frac{F_m}{\mathfrak{R}}$$

$$\phi * \mathfrak{R} = F_m$$

Next re-arrange:

Magnetising Force in
terms of Reluctance
and Flux density

$$H = \frac{F_m}{l}$$

$$B = \frac{\phi}{A}$$

Electromagnetic Relationships.

Electromagnetism.

$$\mu \mu_0 = 4\pi * 10^{-7} \text{ Wb/Atm}$$

$$\mu = \mu_r * \mu_0$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

Reluctance
of core
material (\mathfrak{R})

$$\phi = \frac{Fm}{\mathfrak{R}}$$

$$\phi * \mathfrak{R} = Fm$$

$$A = \frac{l}{\mu * \mathfrak{R}}$$

$$H = \frac{\phi * \mathfrak{R}}{l}$$

$$H = \frac{Fm}{l}$$

$$B = \frac{\phi}{A}$$

Next re-arrange so:

Flux density becomes
focus of equation

Electromagnetic Relationships.

Electromagnetism.

$$\mu_0 = 4\pi * 10^{-7} \text{ Wb/Atm}$$

$$\mu = \mu_r * \mu_0$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

Reluctance
of core
material (\mathfrak{R})

$$\phi = \frac{Fm}{\mathfrak{R}}$$

$$\phi * \mathfrak{R} = Fm$$

$$A = \frac{l}{\mu * \mathfrak{R}}$$

$$H = \frac{\phi * \mathfrak{R}}{l}$$

$$H = \frac{Fm}{l}$$

$$\phi = \frac{H * l}{\mathfrak{R}}$$

$$B = \frac{\phi}{A}$$

Next substitute these
equations:
into this **equation**

Electromagnetic Relationships.

Electromagnetism.

$$\mu_0 = 4\pi * 10^{-7} \text{ Wb/Atm}$$

$$\mu = \mu_r * \mu_0$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

Reluctance
of core
material (\mathfrak{R})

$$\phi = \frac{Fm}{\mathfrak{R}}$$

$$\phi * \mathfrak{R} = Fm$$

$$A = \frac{l}{\mu * \mathfrak{R}}$$

$$H = \frac{\phi * \mathfrak{R}}{l}$$

$$H = \frac{Fm}{l}$$

$$\phi = \frac{H * l}{\mathfrak{R}}$$

$$B = \frac{\phi}{A}$$

$$B = \frac{\frac{H * l}{\mathfrak{R}}}{\frac{l}{\mu * \mathfrak{R}}}$$

Simplifying this
equations gives.

Electromagnetic Relationships.

Electromagnetism.

$$\mu_0 = 4\pi * 10^{-7} \text{ Wb/Atm}$$

$$\mu = \mu_r * \mu_0$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

Reluctance
of core
material (\mathfrak{R})

$$\phi = \frac{Fm}{\mathfrak{R}}$$

$$\phi * \mathfrak{R} = Fm$$

$$A = \frac{l}{\mu * \mathfrak{R}}$$

$$H = \frac{\phi * \mathfrak{R}}{l}$$

$$H = \frac{Fm}{l}$$

$$\phi = \frac{H * l}{\mathfrak{R}}$$

$$B = \frac{\phi}{A}$$

$$B = \frac{\frac{H * l}{\mathfrak{R}}}{\frac{l}{\mu * \mathfrak{R}}} \text{ or } \frac{H * l * \mu * \mathfrak{R}}{\mathfrak{R} * l}$$

Electromagnetic Relationships.

Electromagnetism.

$$\mu_0 = 4\pi * 10^{-7} \text{ Wb/Atm}$$

$$\mu = \mu_r * \mu_0$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

Reluctance
of core
material (\mathfrak{R})

$$\phi = \frac{Fm}{\mathfrak{R}}$$

$$\phi * \mathfrak{R} = Fm$$

$$A = \frac{l}{\mu * \mathfrak{R}}$$

$$H = \frac{\phi * \mathfrak{R}}{l}$$

$$H = \frac{Fm}{l}$$

$$\phi = \frac{H * l}{\mathfrak{R}}$$

$$B = \frac{\phi}{A}$$

$$B = \frac{\frac{H * l}{\mathfrak{R}}}{\frac{l}{\mu * \mathfrak{R}}} \text{ or } \frac{H * \cancel{l} * \mu * \mathfrak{R}}{\mathfrak{R} * \cancel{l}}$$

B is proportional to ϕ .
 ϕ is proportional to Fm.
 H is proportional to Fm.
 Therefore
 H is proportional to B.

$$B = \mu H$$

Electromagnetic Relationships.

Electromagnetism.

$$\mu_0 = 4\pi * 10^{-7} \text{ Wb/Atm}$$


$$\mu = \mu_r * \mu_0$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

Reluctance of core material (\mathfrak{R})

$$\phi = \frac{Fm}{\mathfrak{R}}$$

$$\phi * \mathfrak{R} = Fm$$

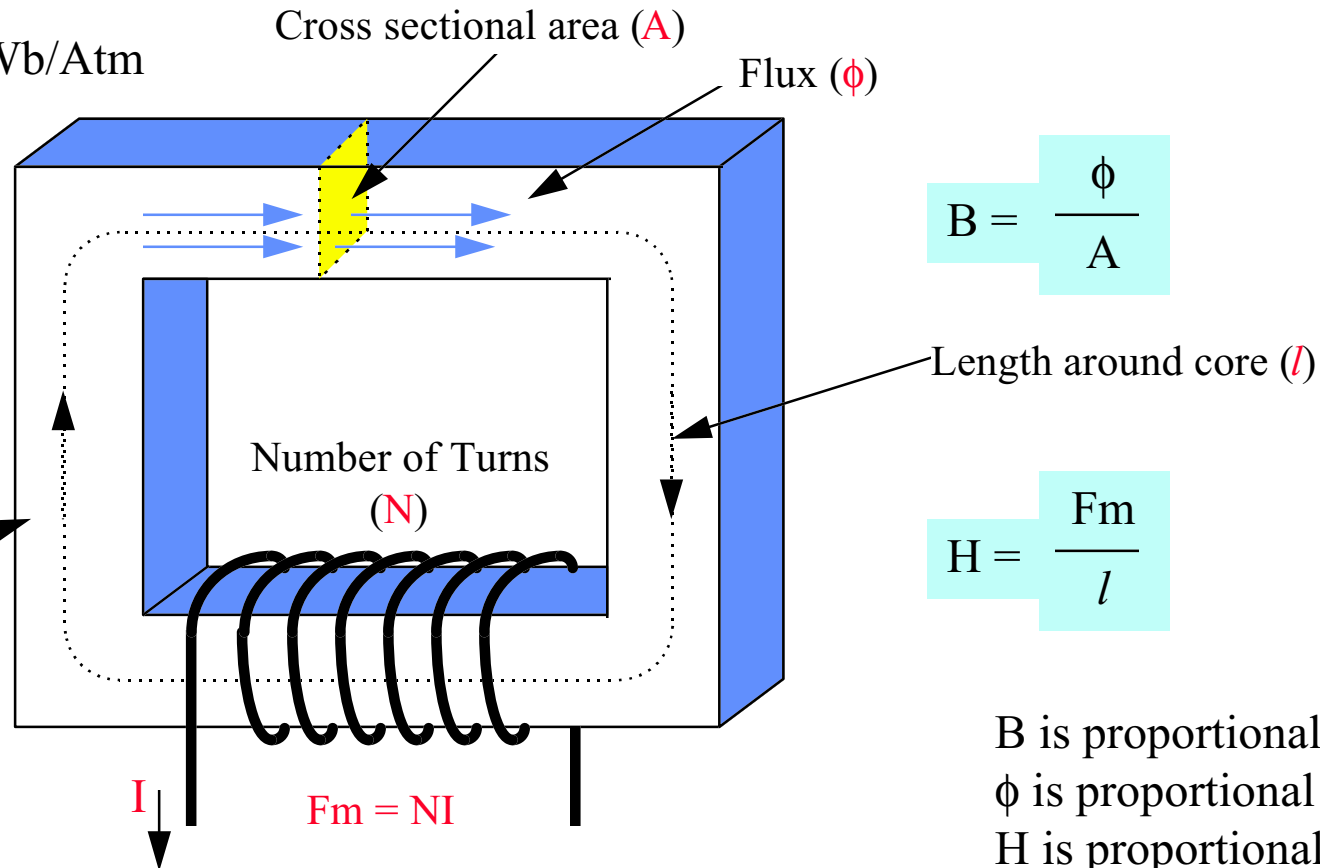

$$B = \frac{\phi}{A}$$

$$H = \frac{Fm}{l}$$


B is proportional to ϕ .
 ϕ is proportional to Fm .
 H is proportional to Fm .
 Therefore
 H is proportional to B.

$$B = \mu H$$

Electromagnetic Relationships.

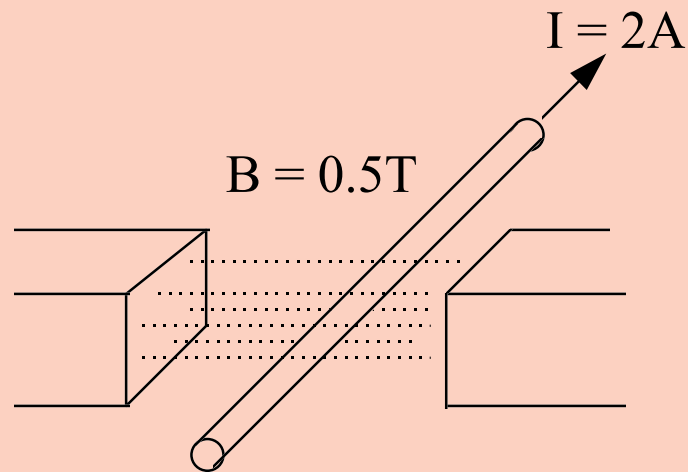
Example Electromagnetism.

- A straight copper conductor of effective length 120mm rests in a magnetic field of flux density 0.5T as shown in diagram.
- a) Calculate the value of force on the conductor when it carries a steady current of 2A.



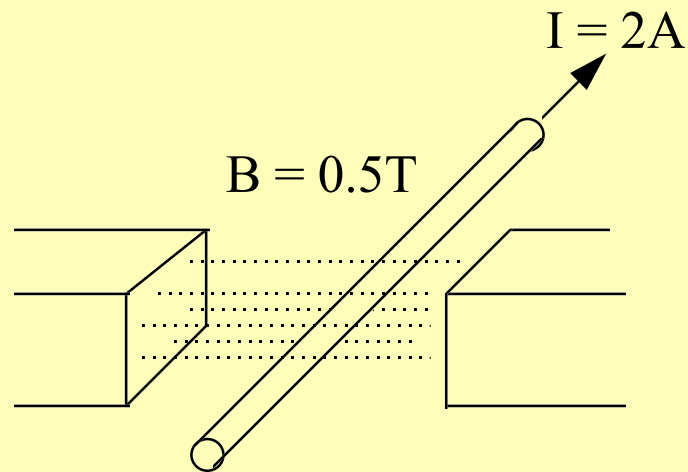Example Electromagnetism.

- Force $F = BI l$
- Where :-
- $B = 0.5\text{T}$, $I = 2\text{A}$, $l = 120\text{mm}$
- Force $F = 0.5 * 2 * 120 * 10^{-3} = 0.12\text{ N}$



Example Electromagnetism.

- b) An electromagnet consists of a coil of wire wound over a cylindrical piece of solid steel. Describe the factors which determine the value of magnetic flux density in the steel core.

Example Electromagnetism.

- Identifying the control factors
- The initial factors we can recognise are:-
 - Flux density in the electromagnet (B).
 - The Magnetizing force (H).
 - What the electromagnet is made from (μ).
 - The relationships between these factors.

Example Electromagnetism.

- The Relationship between factors:-

$$B = \mu * H$$

$$\text{or } B = \mu * (N * I) / l$$


- Where :-
 - B = Flux Density.
 - H = Magnetising Force.
 - μ is the permeability of the material. (or how easy it is to magnetize the material)
 - N = Number of turns on the coil.
 - I = Current flowing in the coil
 - l = Length of the coil

Example Electromagnetism.

- The type of material used
 - High μ (permeability) (Easier to Magnetise) = **More Flux**
 - Low μ (permeability) (Harder to Magnetise) = **Less Flux**
- Number of turn on the coil
 - More turns = **More flux**
 - Less turns = **Less Flux**
- Current flowing
 - More current = **More Flux**
 - Less Current = **Less Flux**
- The Length of the magnetic circuit
 - Longer path = **Less Flux**
 - Shorter path = **More Flux**

Electromagnetism Applications.

Electromagnetism Applications.

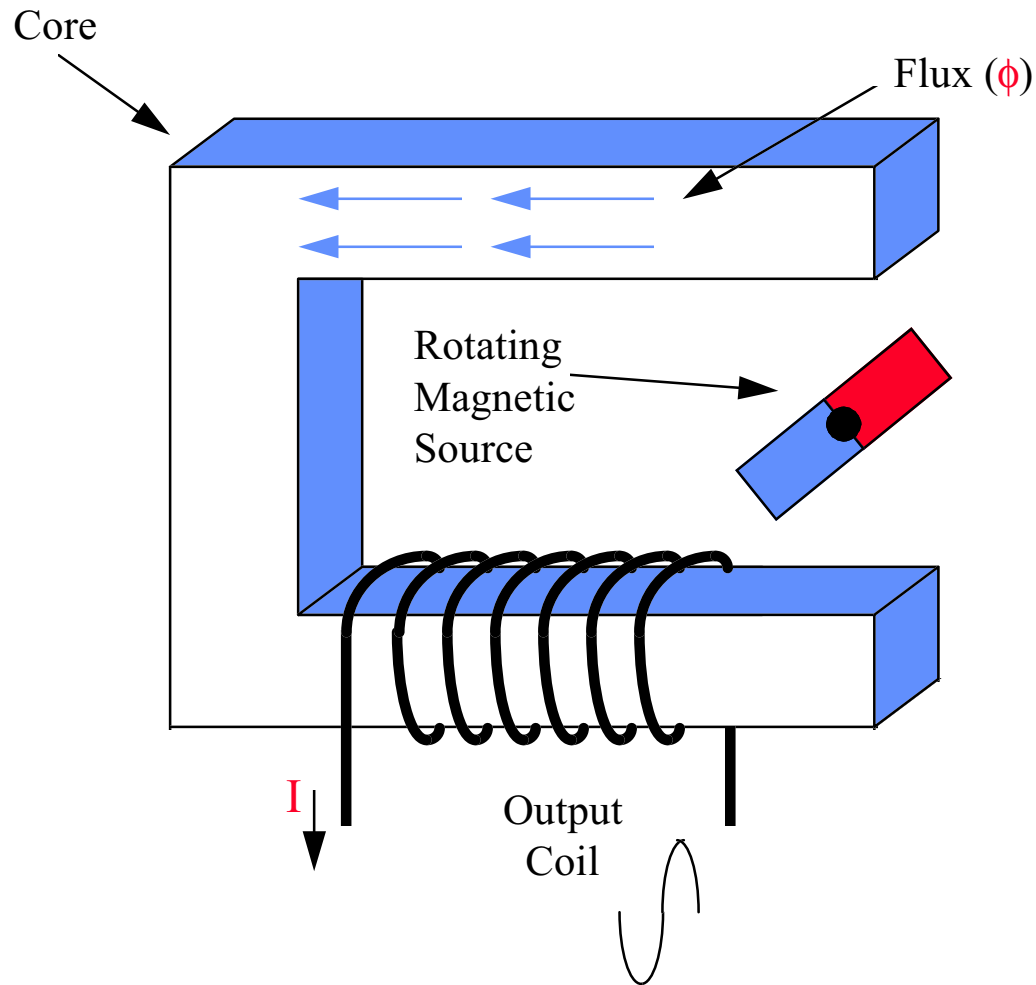

Operation.

- (1) The Magnetic Source rotates and this generates a changing magnetic Flux in the Core.
- (2) Whilst the Flux is changing in the Core this will cause a Voltage to be produced in the Output Coil.

The Basic Generator.


Electromagnetism Applications.

A rotating electro-magnet is called an **Armature**.

A **Commutator** is a connector that can apply power to the Armature.


Operation.

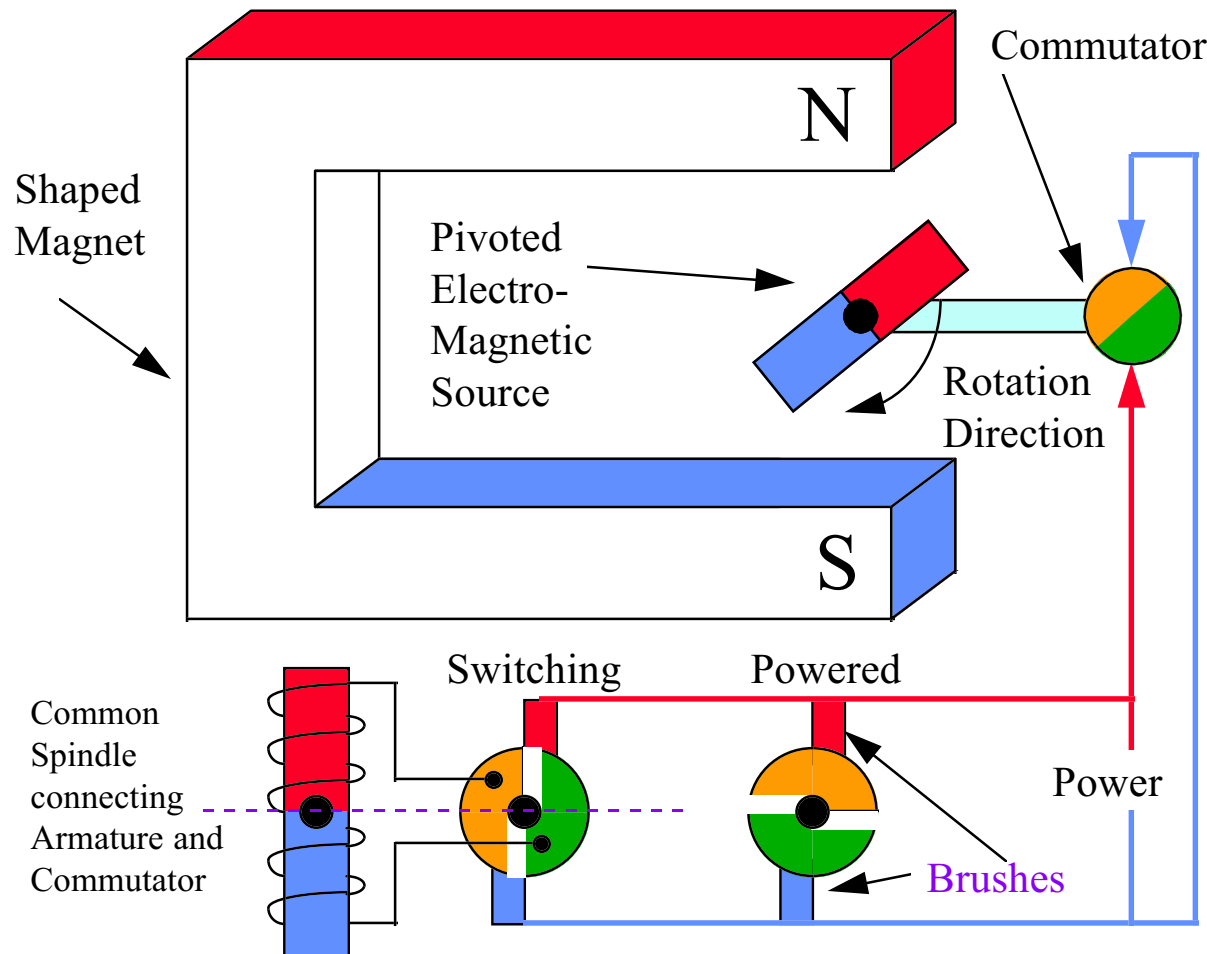- (1) Power is applied through the **Brushes** via **Commutator** to the **Armature**.
- (2) This causes the **Armature** to create a magnetic field.
- (3) The **Armature** will rotate due to the N/S attraction and repulsion of the magnetic forces.
- (4) As the N/S poles become aligned the **Commutator** reverses the current flowing in **Armature** causing its magnetic field to also reverse.
- (5) **Armature** continues to rotate (Back to (3))



The Basic Electric Motor.

Electromagnetism Applications.

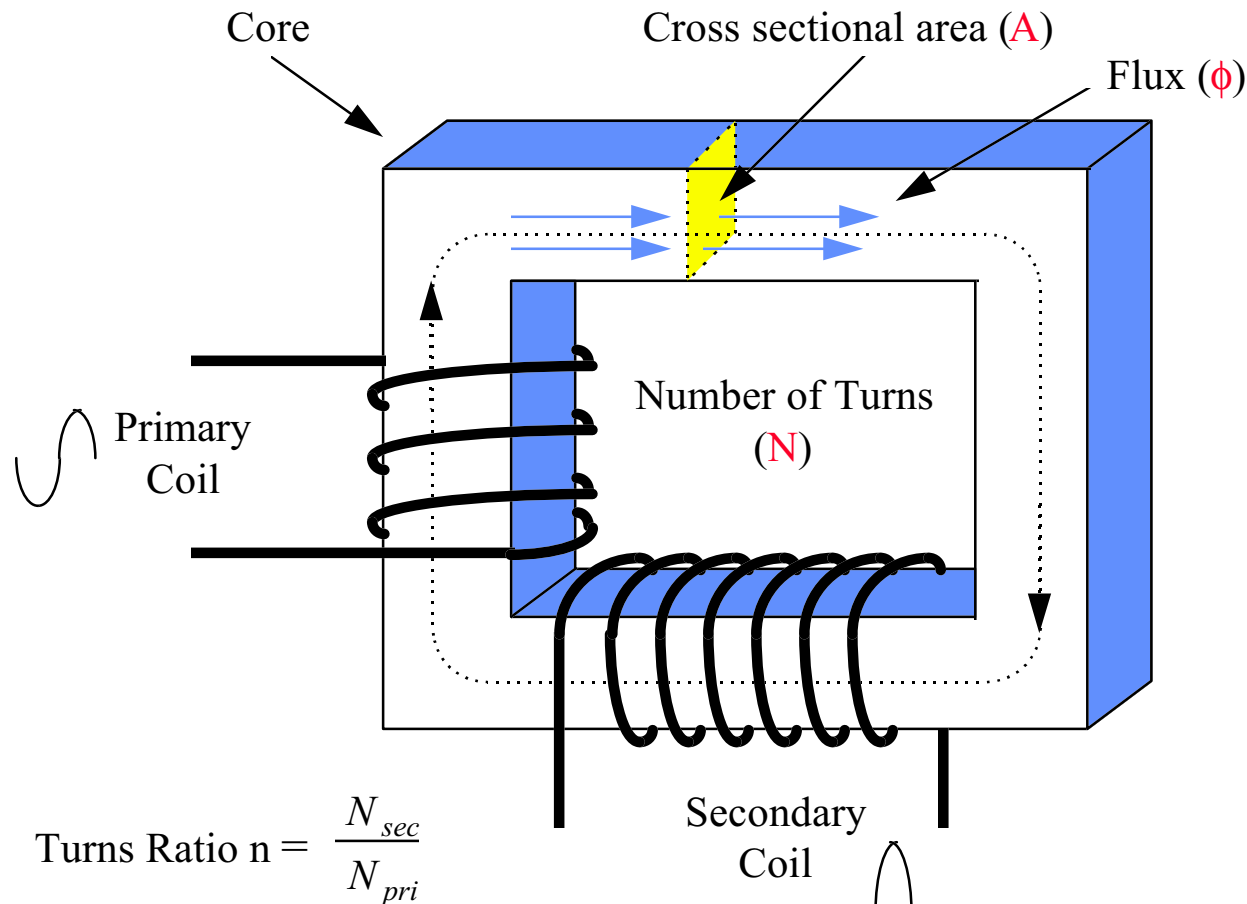

$$\text{Turns Ratio } n = \frac{N_{sec}}{N_{pri}}$$

$$\frac{V_{sec}}{V_{pri}} = \frac{N_{sec}}{N_{pri}}$$

The Basic Transformer.

(1) If a **Voltage** is applied to the **Primary Coil** this will cause a **Flux** to be produced in **Core**.

(2) Whilst the **Flux** is changing in the **Core** this will cause a **Voltage** to be produced in the **Secondary Coil**.

(3) The Transformer's operation is therefore dependent on the Input source being an **Alternating Current (ac)**.

(4) The Output Voltage is dependent on the ratio of the number of turns on Input and Output coils.

Transformers


Transformers.

(1) If a **Voltage** is applied to the **Primary Coil** this will cause a **Flux** to be produced in **Core**.

(2) Whilst the **Flux** is changing in the **Core** this will cause a **Voltage** to be produced in the **Secondary Coil**.

(3) The Transformer's operation is therefore dependent on the Input source being an **Alternating Current (ac)**.

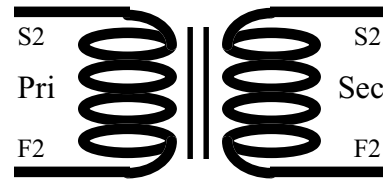(4) The Output Voltage is dependent on the ratio of the number of turns on Input and Output coils.



$$\text{Turns Ratio } n = \frac{N_{sec}}{N_{pri}}$$

$$\frac{V_{sec}}{V_{pri}} = \frac{N_{sec}}{N_{pri}}$$



The Basic Transformer.

Inductors

Inductors.

- **Inductance** is the name given to the property of a circuit where an e.m.f. induced into the circuit by the change of flux linkages produced by a current change.

- When the e.m.f. is induced in the same circuit in which current changing, the property is called :-



Self Inductance, L.

- When the e.m.f. is induced in a circuit by the change of flux due to current changing in adjacent circuit, the property is called :-

Mutual Inductance, M.

Inductors.

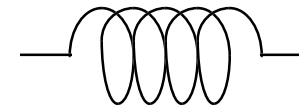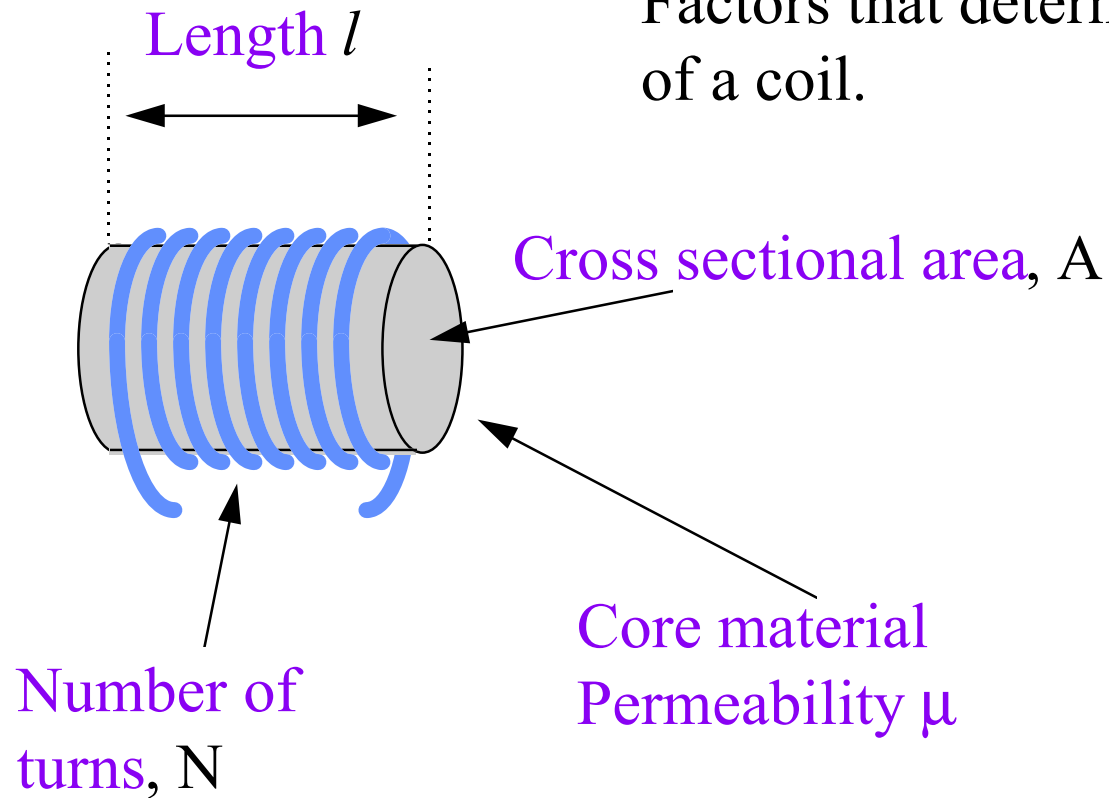Factors that determine the inductance of a coil.



Circuit Symbol for an Inductor.

Physical Construction of an Inductor

Inductors.

- Calculating the Inductance of a Inductor :-
- The Inductance of an inductor is **directly** proportional to:-
 - the number of turns squared,
 - the permeability of the material,
 - the cross sectional area of the core
 - and **inversely** proportional to the length of the core.
- The formula for the Inductance of a Inductor is as follows :-

$$L = \frac{N^2 \mu A}{l}$$

A = Cross sectional area in metres squared.

l = Core length in metres.

μ = permeability in Henries per metre.

L = Inductance in henries (H).

N = Number of turns.

Inductors.

- The Unit of Inductance is the **henry**, H.
- Definition :-
- A circuit has an inductance of one henry when an e.m.f. of one volt is induced in it by a **current changing** at a rate of one ampere per second.
- Most inductors in electronics are measured in (mH) 10^{-3} milli henries.

Inductors.

- The induced e.m.f. in a coil of N turn is:-

$$E = N \frac{\Delta\phi}{\Delta t}$$

Where :-

$\Delta\phi$ = The change in flux in Webers.

Δt = Time taken for flux to change in seconds.

E = The induced e.m.f. in a coil in volts.

N = Number of turns.

- The induced e.m.f. in a coil of Inductance L is:-

$$E = L \frac{\Delta I}{\Delta t}$$

Where :-

ΔI = The change in current in amperes.

Δt = Time taken for current to change in seconds.

E = The induced e.m.f. in a coil in volts.

L = Inductance in henries.

Inductors.

- Example:-
- What is the e.m.f. induced in a coil of 200 turns when there is a change of flux of 25mWb occurs in 50ms :-

Inductors.

- Example:-
- What is the e.m.f. induced in a coil of 200 turns when there is a change of flux of 25mWb occurs in 50ms :-

$$E = N \frac{\Delta\phi}{\Delta t}$$

$$E = 200 * \frac{25 * 10^{-3}}{50 * 10^{-3}} = 100 \text{ Volts}$$

Inductors.

- Example:-
- A flux of $400 \mu\text{Wb}$ passing through a 150 turn coil is reversed in 40ms:-
- Find the average e.m.f. induced.

Inductors.

- Example:-
- A flux of $400 \mu\text{Wb}$ passing through a 150 turn coil is reversed in 40ms:-
- Find the average e.m.f. induced.

Since the flux reverses, the flux changes from $+400\mu\text{Wb}$ to $-400\mu\text{Wb}$ a total change of $800\mu\text{Wb}$.

$$E = N \frac{\Delta\phi}{t} = 150 * \frac{800 * 10^{-6}}{40 * 10^{-3}} = 3 \text{ Volts}$$

Inductors.

- Energy stored in a inductor :-
- An inductor stores energy in the magnetic field created by the current. The energy stored in the inductor is directly proportional to the inductance and the square of the current.
- The formula for the energy stored in an inductor is as follows :-

$$W = \frac{1}{2} LI^2$$

W = energy in joules.

L= inductance in henries.

I = Current in amps.

Summary Inductors.

Inductors in Series

$$L_t = L_1 + L_2 + L_3 \dots \text{etc...}$$

Inductors in Parallel

$$\frac{1}{L_t} = \frac{1}{L_1} + \frac{1}{L_2} \dots \text{etc.}$$

or
$$L_t = \frac{L_1 * L_2}{(L_1 + L_2)}$$
 The two Inductor option.


Thinking Exercise

Inductors.

Initial conditions:

Inductor L has no Current flowing through it.

So what voltage is across it?

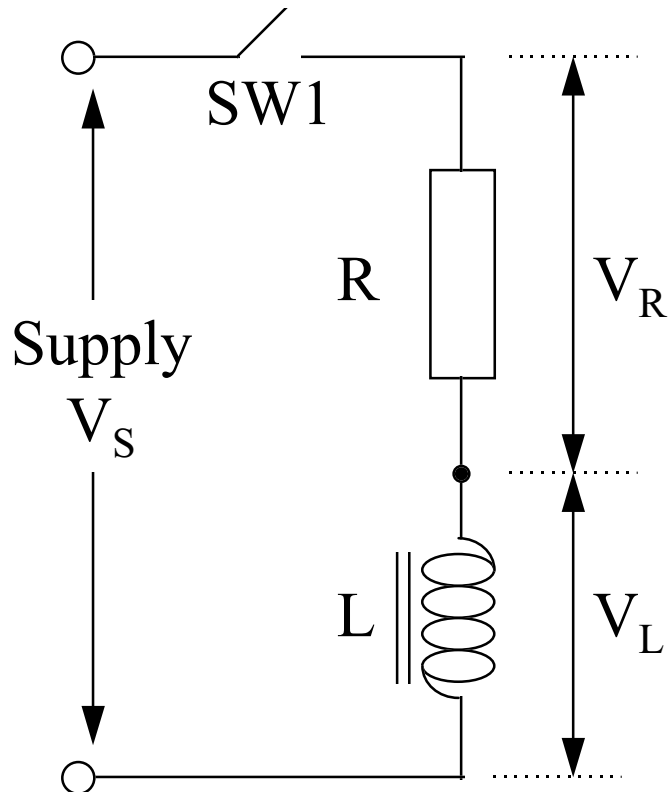

Solution:

Just looking at the Resistance of the Coil windings.

$$V = I * R$$


as $I = 0$ then

$$V_L = I * R_C \text{ or } 0 * R_C = 0 \text{ Volts}$$

Thinking Exercise

Inductors.

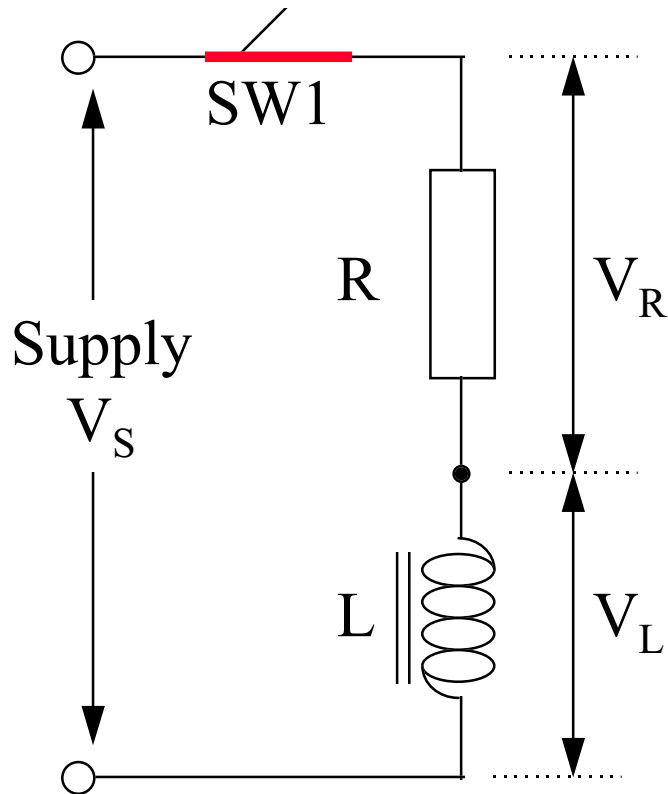The instant that SW1 is closed what voltage will be present across V_L and V_R ?



Solution:

The current will try to change in the coil at a very fast rate in a very short time.

$$V_L = E = L(\Delta I / t) \text{ volts}$$

as ΔI will be large

and t will be small then

V_L will also be large.

By implication if V_L is large the circuit current must be small (0).

$$V_L = V_S - V_R \text{ or}$$


$$V_L = V_S - (I \cdot R) = V_S - (0 \cdot R) \text{ Volts}$$

therefore $V_L = V_S$

Thinking Exercise

Inductors.

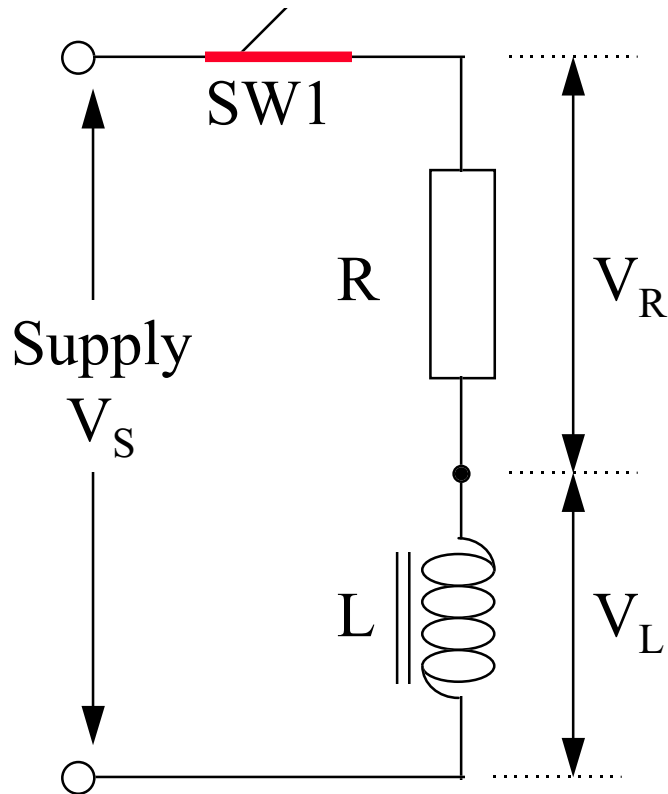After SW1 has been closed for a significant time what voltage will be present across V_L and V_R ?



Solution:

The current will cease to change in the coil.

$$V_L = E = L(\Delta I / t) \text{ volts}$$

as ΔI will be 0

and t will be large then

V_L will also be zero.

By implication if V_L is zero then the circuit current can only be dependent on R.

$$V_L = V_S - V_R \text{ or}$$

$$V_L = V_S - V_R = 0 \text{ Volts}$$

$$0 = V_S - V_R \text{ Volts}$$

therefore $V_R = V_S$

Thinking Exercise

Inductors.



Summary:

At switch on:

Voltage across Inductor is maximum
Voltage across Resistor is minimum.


After a long period after switch on:

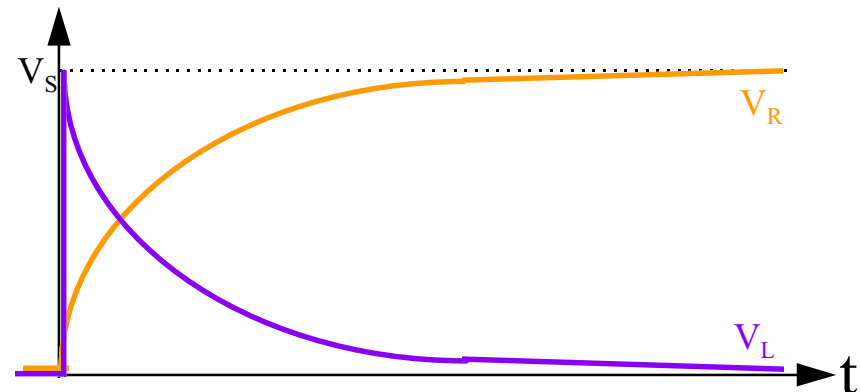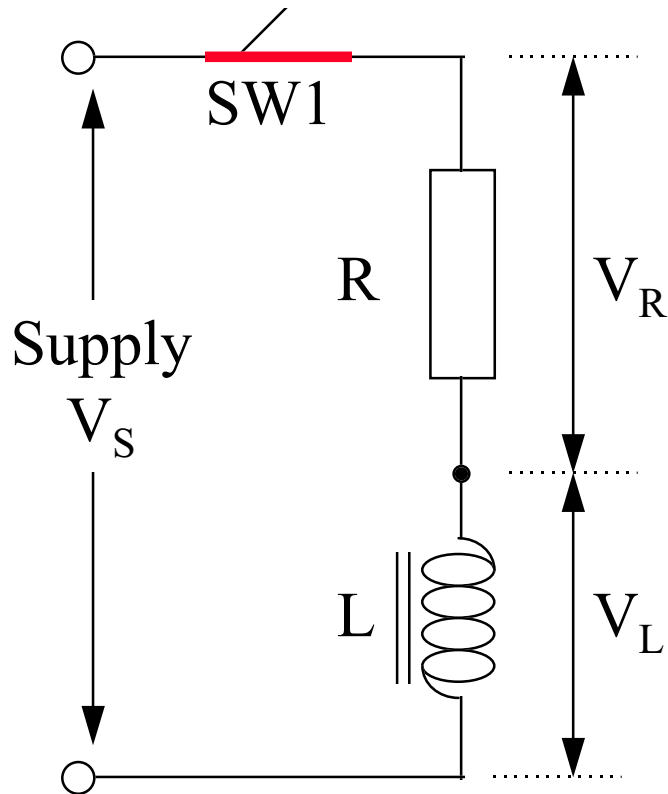Voltage across Inductor is minimum
Voltage across Resistor is maximum.



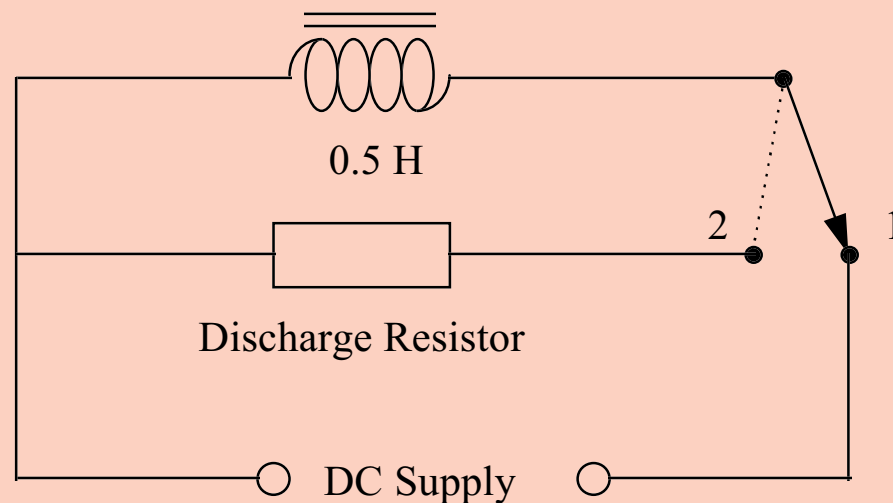
Example Inductors.

- A coil of negligible resistance is connected as shown in the circuit below. The coil carries a steady current of 5 A.
- a) Calculate the energy stored in the coil.
- b) The switch is moved to position 2. Calculate the average value of emf induced in the coil if the current falls to zero in 0.2 seconds.




Example Inductors.

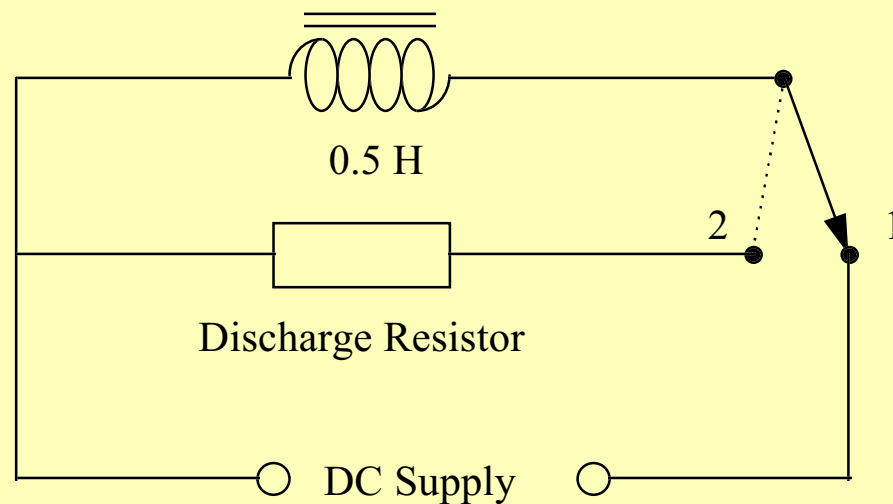- a) Calculate the energy stored in the coil.
- Energy $W = \frac{1}{2}LI^2 = 0.5 * 0.5 * 5^2 = 6.25J$




Example Inductors.

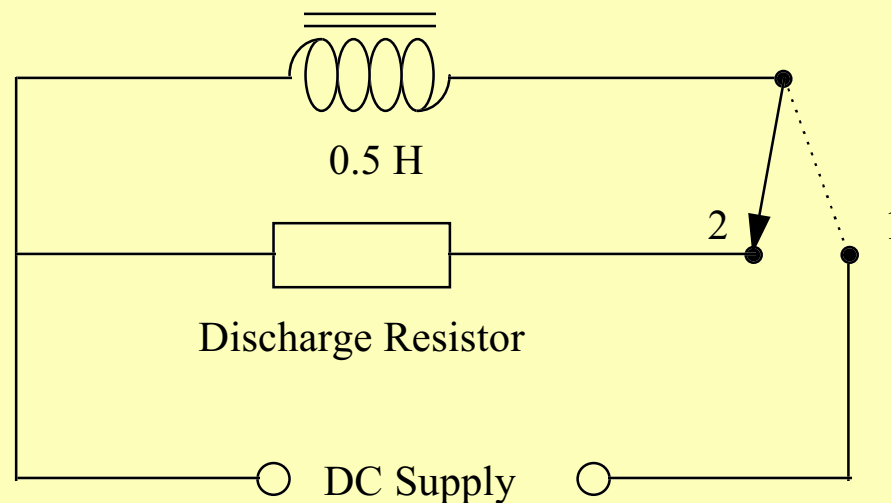- b) The switch is moved to position 2. Calculate the average value of emf induced in the coil if the current falls to zero in 0.2 seconds.
- $e = L \Delta I / \Delta t$ or $e = L dI/dt$
- $dt = 0.2$ Seconds, $dI = 5A$, $L = 0.5H$
- $e = 0.5 * (5 / 0.2) = 12.5$ Volts



AC Theory


AC Theory.

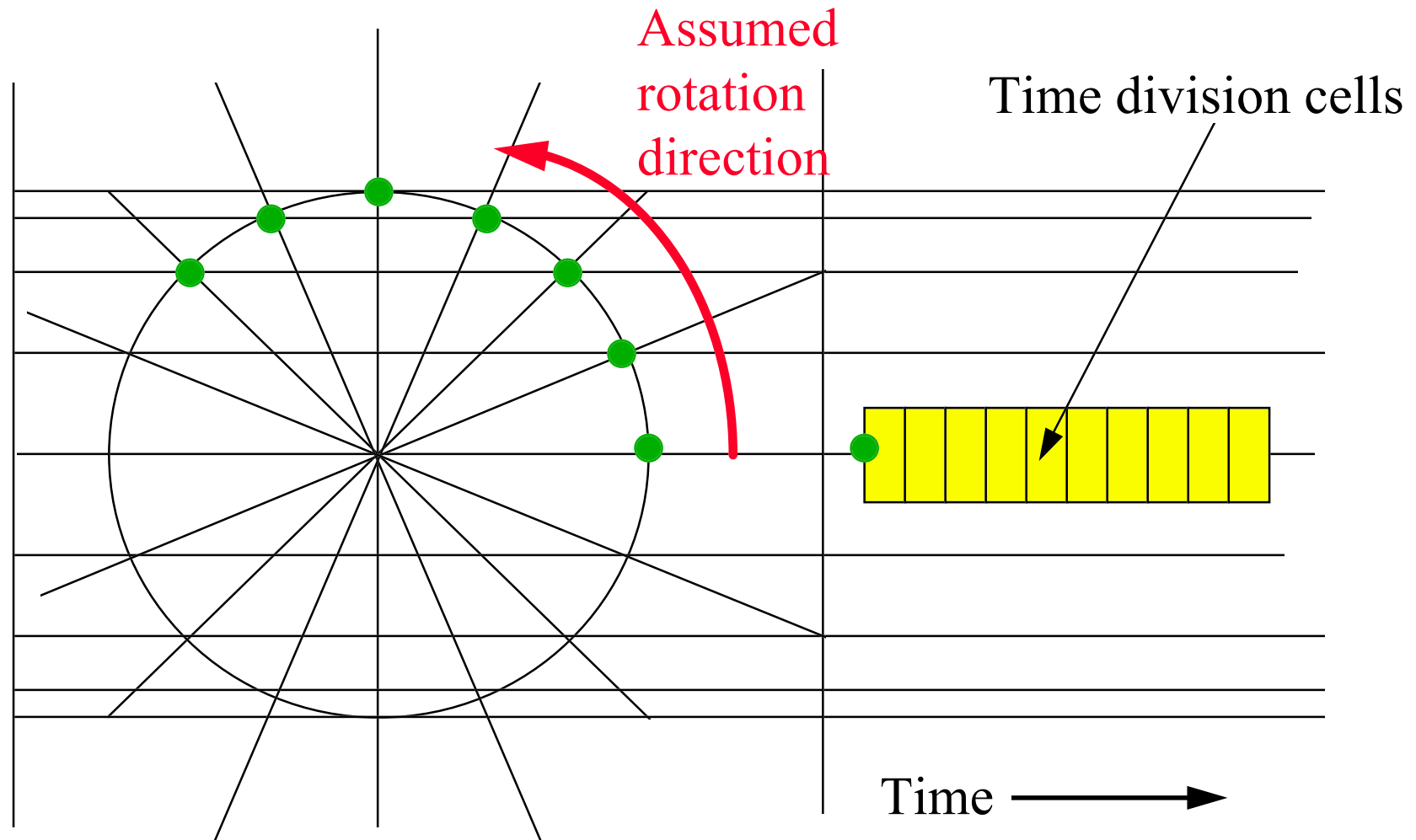

Rotation at 22.5° Steps

Where the Sine Wave comes from.


AC Theory.

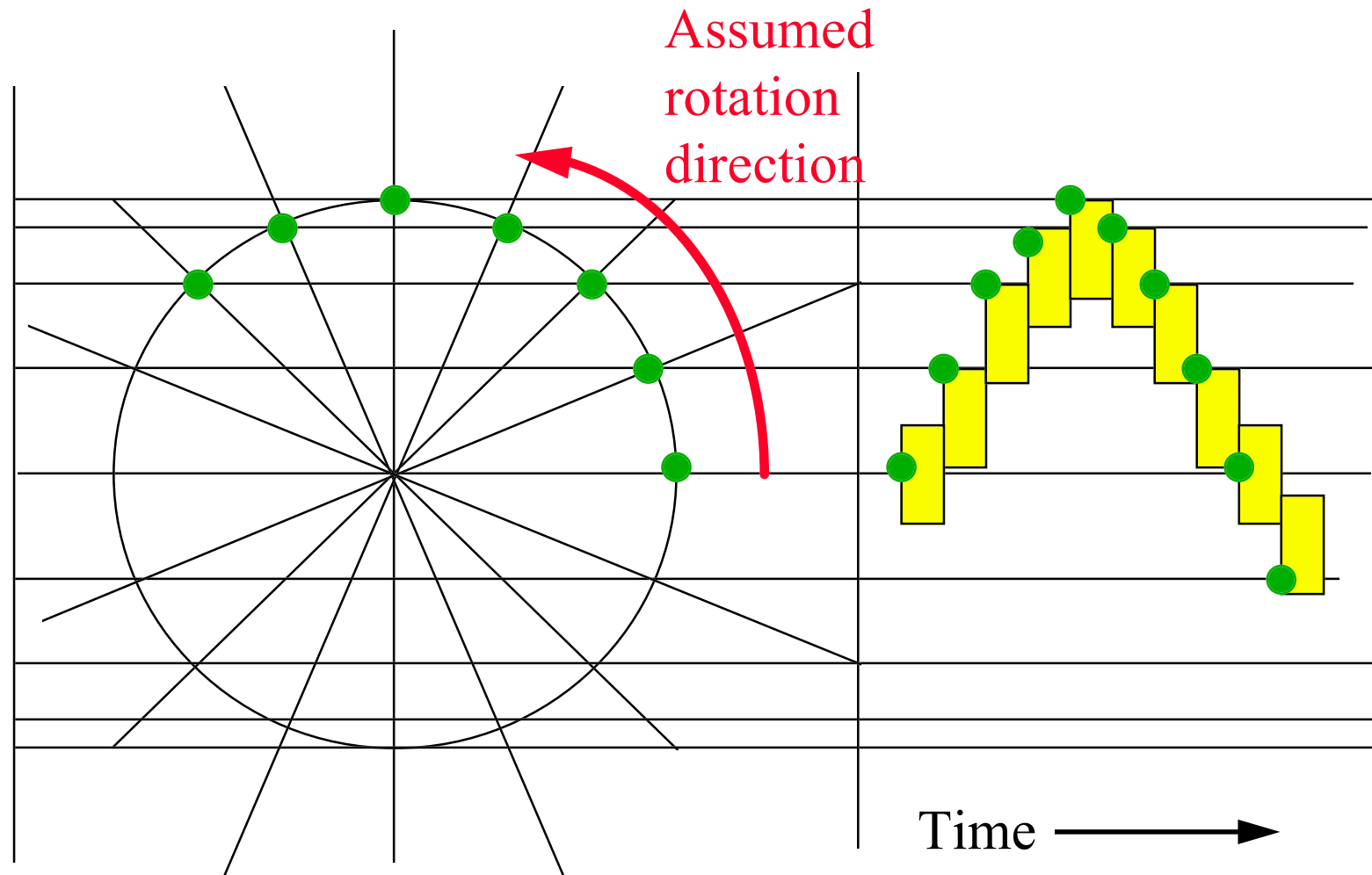

Rotation at 22.5° Steps

Where the Sine Wave comes from.


AC Theory.

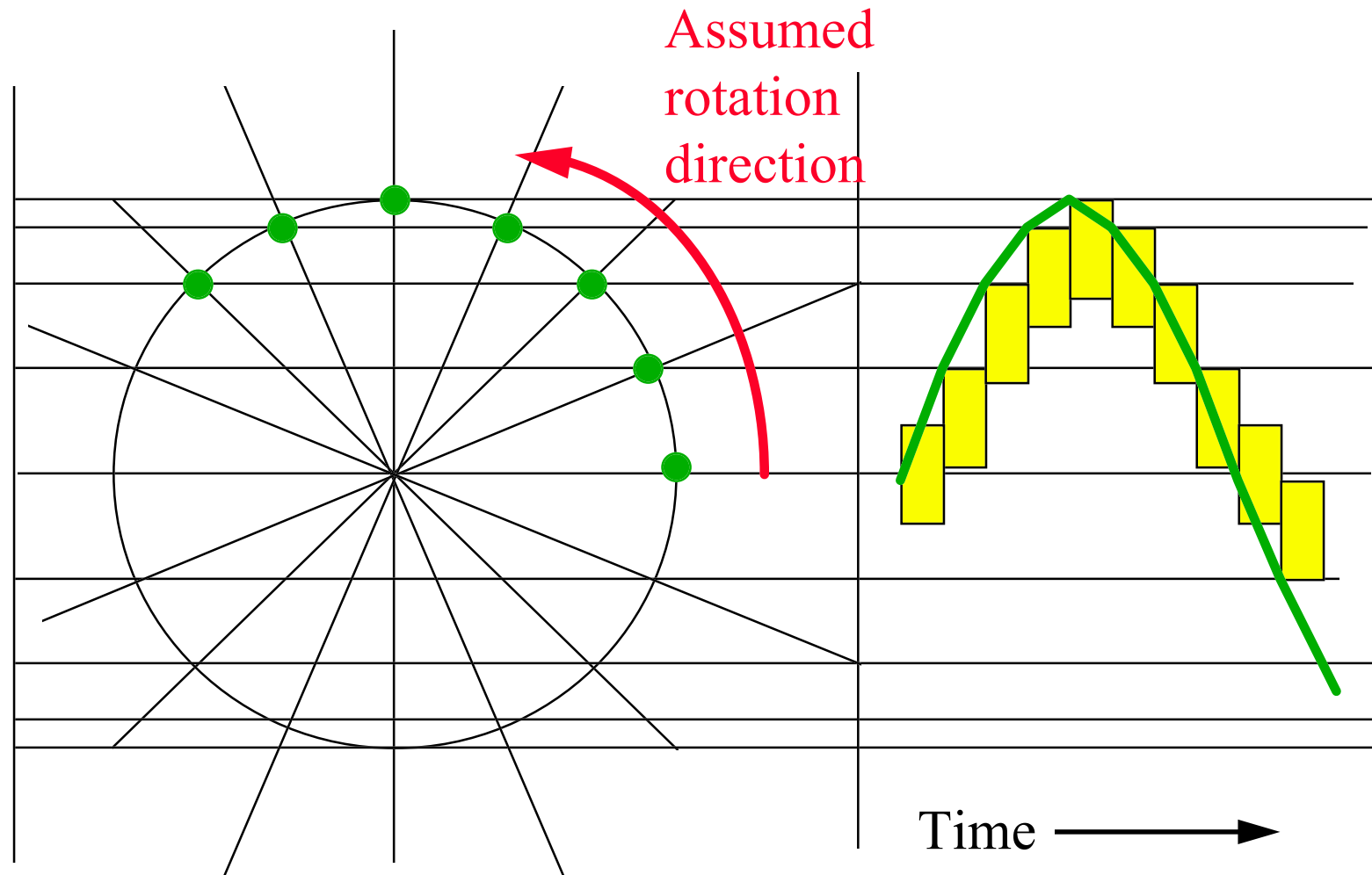

Rotation at 22.5° Steps

Where the Sine Wave comes from.

AC Theory.

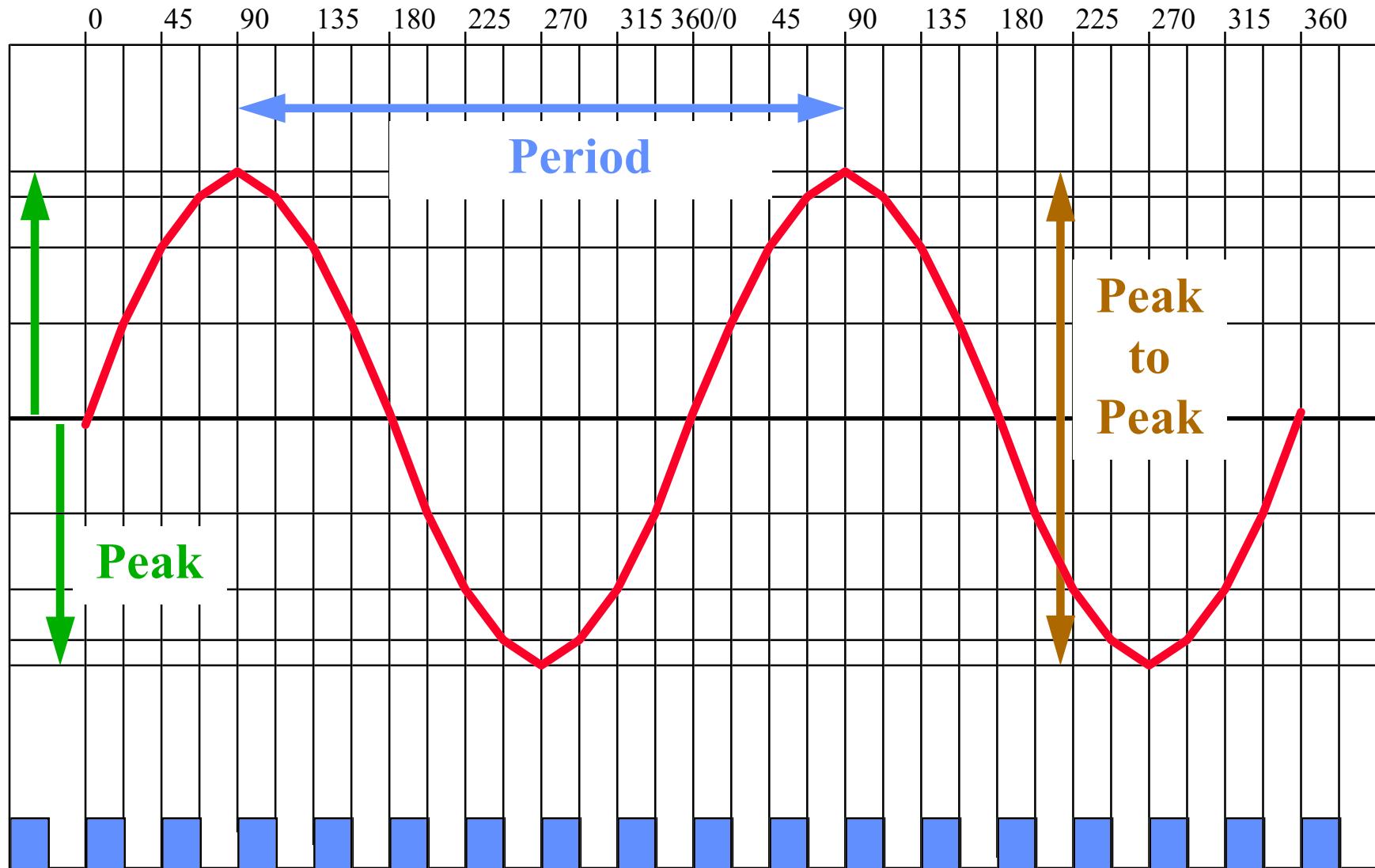

AC Theory.

- Definition 1.
- **Period** is the time taken between two repeated point of a waveform and is measured in seconds.
- **Frequency** is how many times a repeat of a waveform occurs per second and this value is Measured in Hertz (Hz).
- Frequency used to be measured in cycles per second c/s (A cyclic process).

AC Theory.

- Period is the time it takes for one rotation.
- Frequency is how many rotations per unit of time. Measured in Hertz (Hz)
- 1 Hz = 1 Cycle or rotation.
- Therefore the frequency, period relationship is :-

$$\text{Frequency} = \frac{1}{\text{Period}}$$

or

$$\text{Period} = \frac{1}{\text{Frequency}}$$

AC Theory.

- If we know speed we can calculate distance.
- Speed of Light = 186000 miles per second or 299Mms per second (often rounded to 300000Km to ease or speed calculations)
- Therefore the frequency, period , distance relationship is :-

$$\text{Distance} = (\text{Speed of Light}) * \text{Period}$$

or

$$\text{Distance} = \frac{\text{Speed of Light}}{\text{Frequency}}$$

AC Theory.

- Example 1
- Frequency = 2GHz , light = 300000000m/s
- Period =
- Distance =

-
- Example 2
 - Frequency = 50Hz , light = 300000000m/s
 - Period =
 - Distance =

AC Theory.

- Example 1

- Frequency = 2GHz , light = 3000000000m/s

- Period = $1/(2*10^9) = .5 * 10^{-9} = 0.5\text{nSecs}$

- Distance = $3000000000/(2*10^9) = 150*10^{-3} = 150\text{mm} = 15\text{cm}$

- Example 2

- Frequency = 50Hz , light = 3000000000m/s


- Period = $1/(50) = 20 * 10^{-3} = 20\text{mSecs}$

- Distance = $3000000000/(50) = 6000\text{Km}$


AC Theory.

- Implications for modern processors are :-
- The logic in most processors is synchronized by a common clock signal.
- With a 2GHz processor any logic that is say 7.5cms from the clock will be operating 180° out of phase from the master clock.
- This could cause a problem should you need to combine signals from different parts of the circuit. (These phase changes and other delays are a problem known as data skew)

AC Theory.

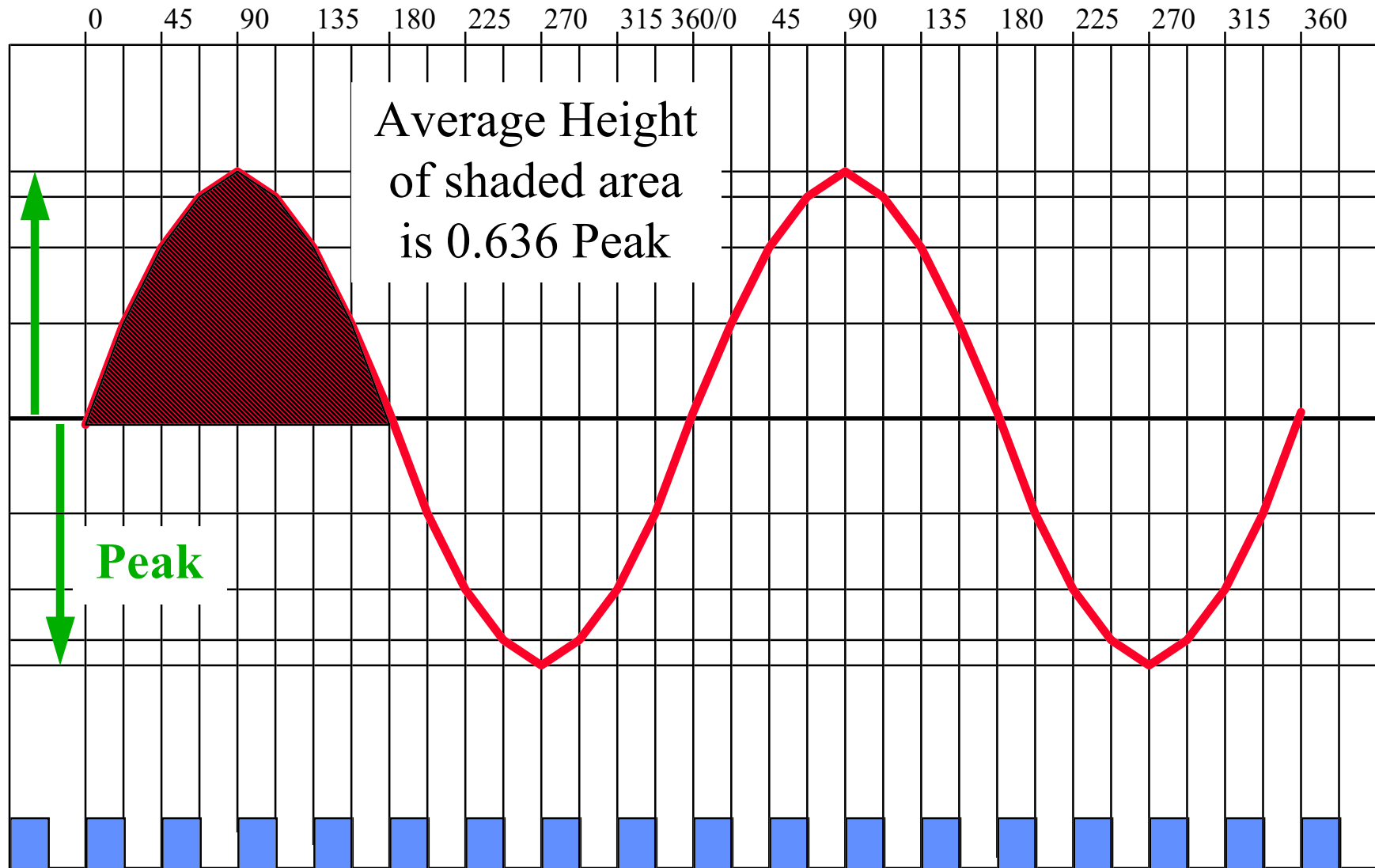

AC Theory.

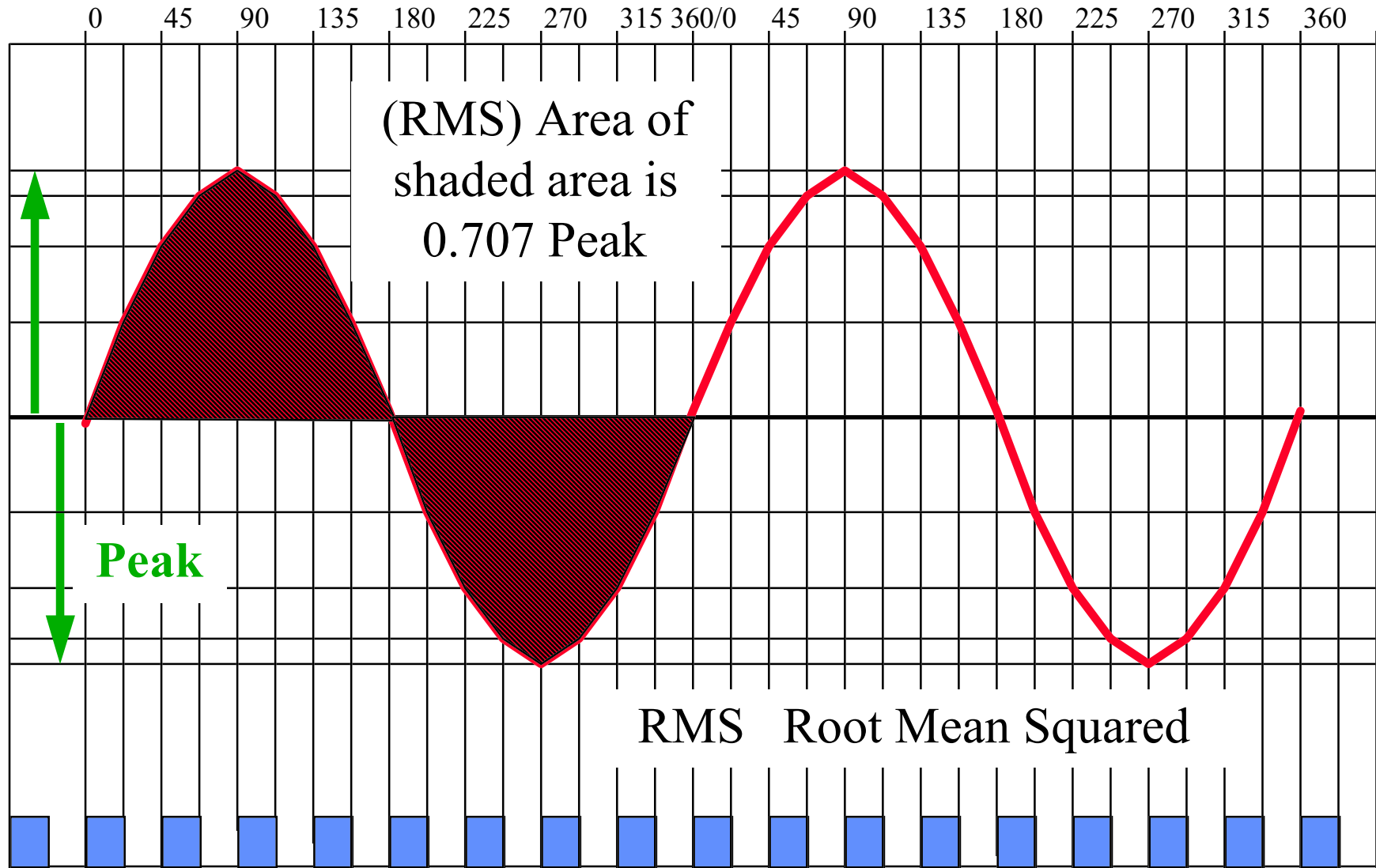

Summary

AC Theory.

$$\text{Peak value} = \text{RMS value} * \sqrt{2}$$

$$\text{RMS value} = \frac{\text{Peak value}}{\sqrt{2}}$$

$$\text{Peak value} = \frac{\text{Average value}}{0.638}$$

$$\text{Average value} = \text{Peak value} * 0.638$$

Note

$$\sqrt{2} = 1.4142$$


AC Theory.

Basic Math's for AC Theory.

AC Theory.

Take a simple square 

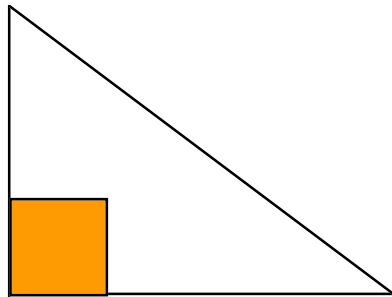
Then build a triangle which is 3 unit high and 4 units wide.



AC Theory.

See how many squares will lie along the sloping axis


3 Units
High

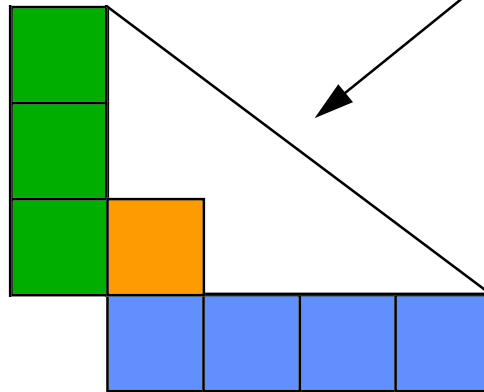

4 Units
Wide


AC Theory.

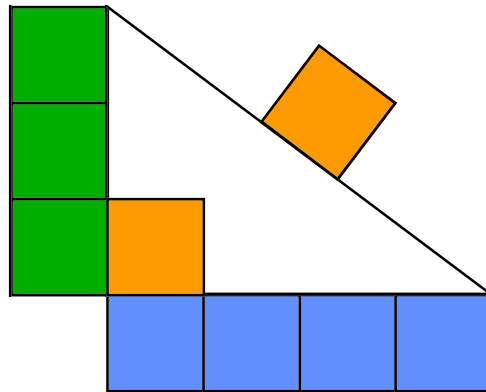You should find that 5 square will lie along the slope



AC Theory.

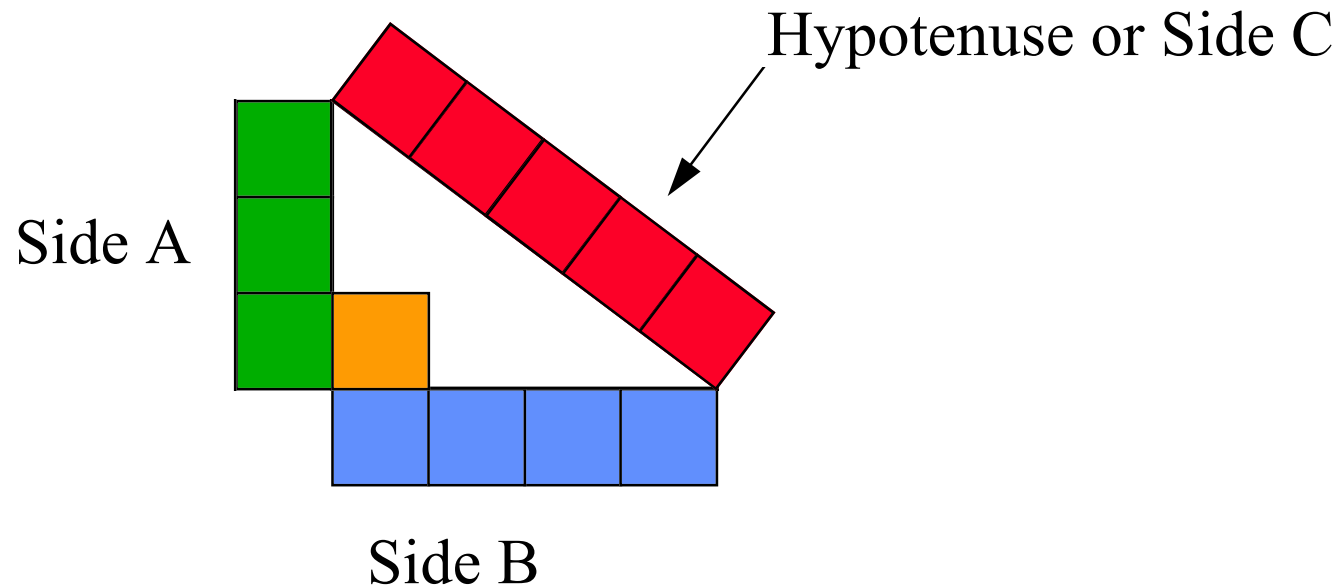Pythagoras identified that the square on the hypotenuse is equal to the sum of the squares on the other sides




AC Theory.

Note: $9 + 16 = 25$


or $A^2 + B^2 = C^2$

or $C = \sqrt{A^2 + B^2}$

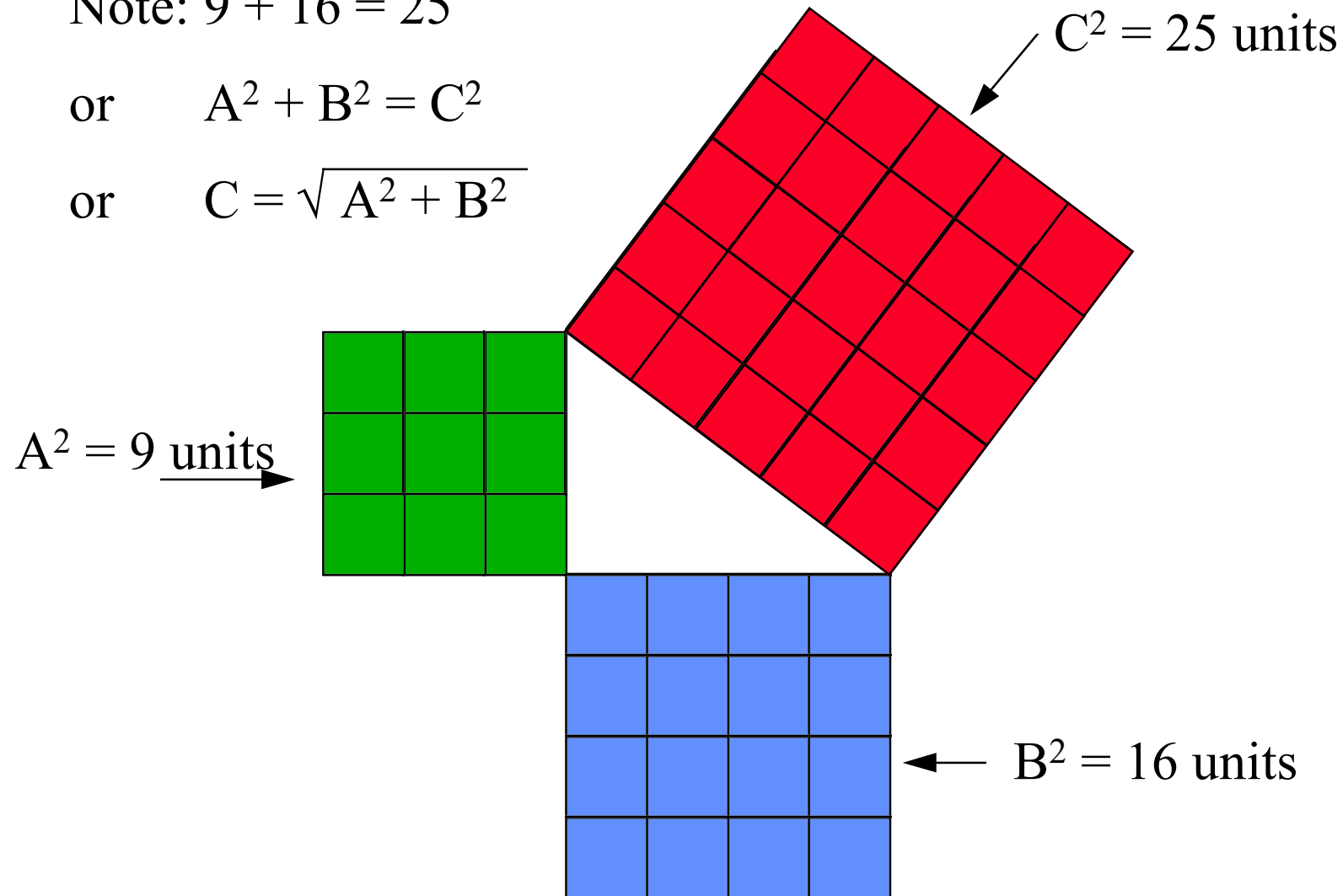

Angular
Measurement


AC Theory.

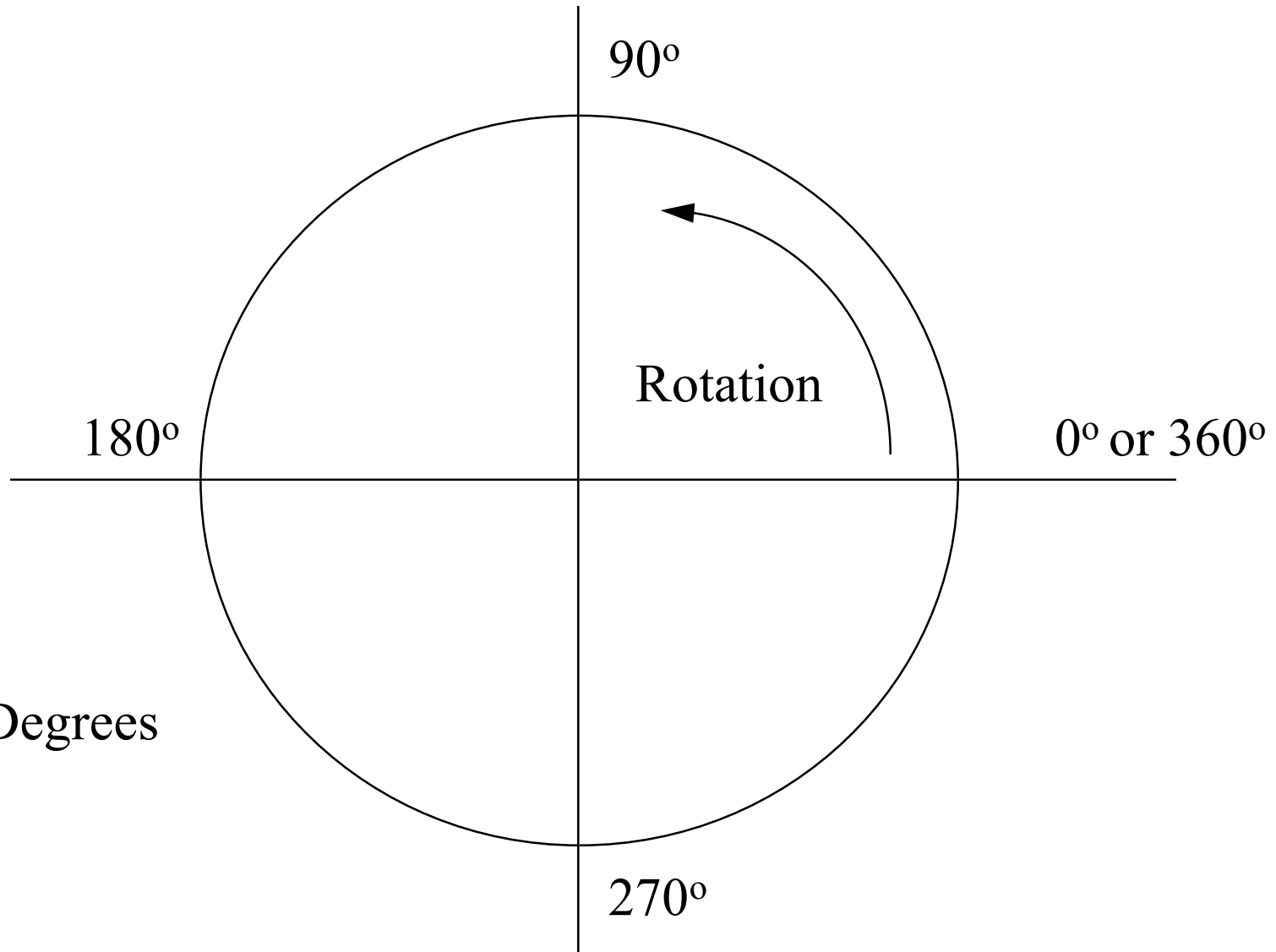

Using Degrees

Angular
Measurement


AC Theory.

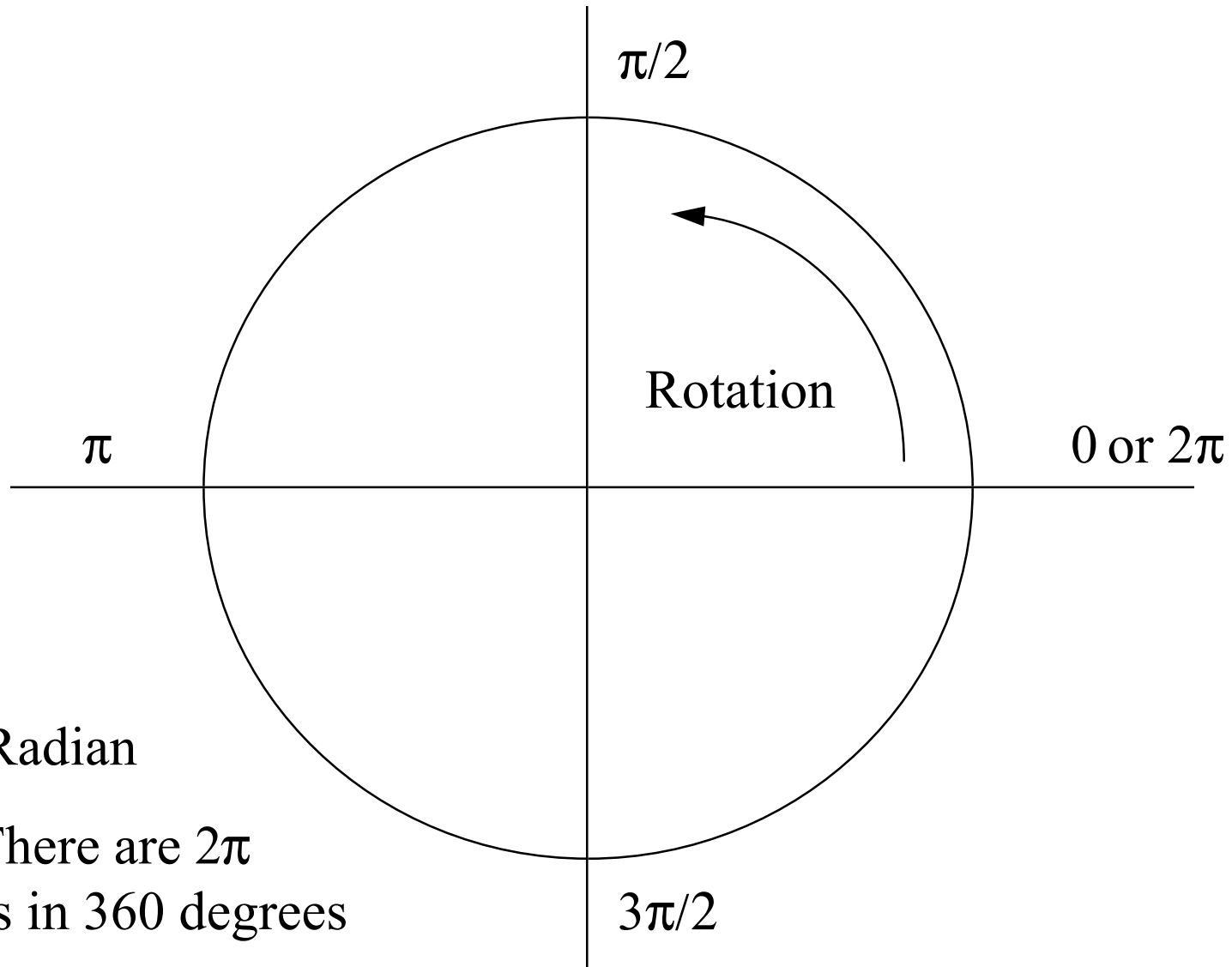

Using Radian

Note: There are 2π
Radians in 360 degrees

AC Theory.

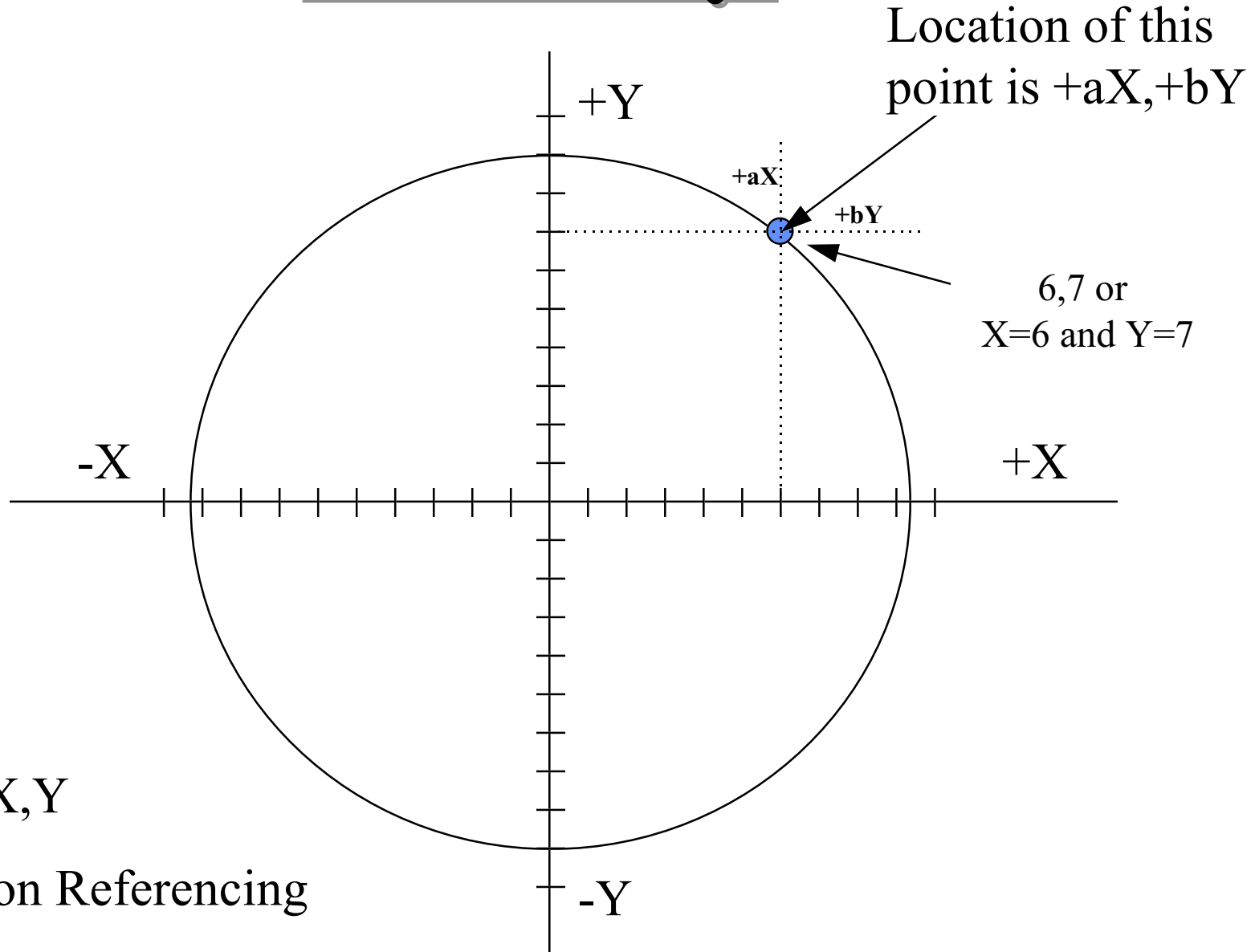


Using X,Y

Location Referencing

Coordinates

AC Theory.

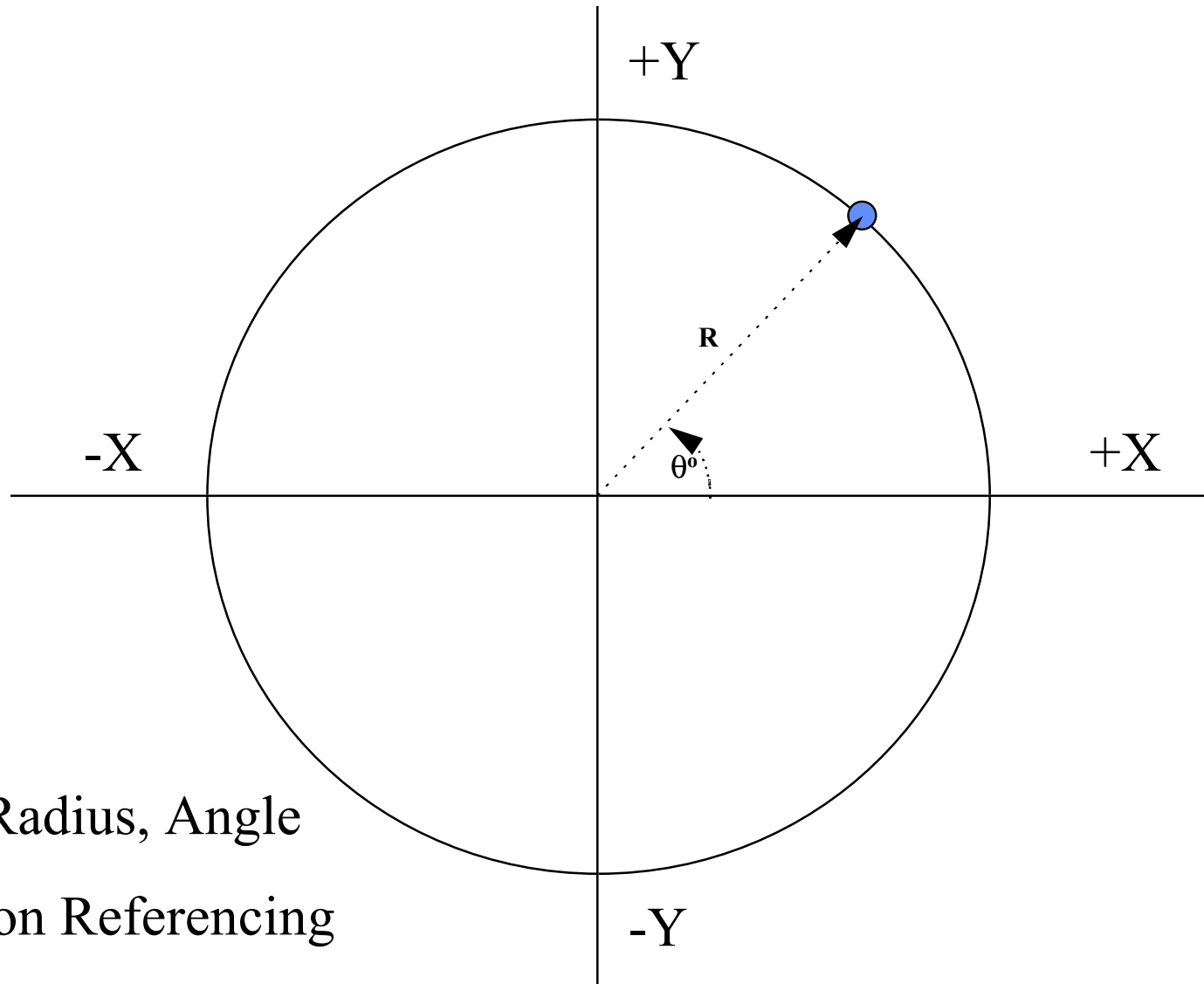


Using Radius, Angle

Location Referencing

Trigonometrical Ratios

AC Theory.

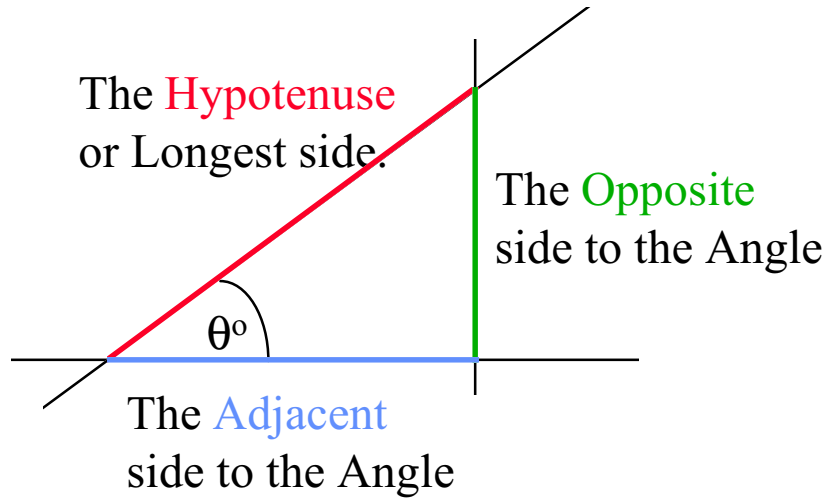

$$\sin \theta = \frac{\text{Opposite}}{\text{Hypotenuse}}$$

$$\cos \theta = \frac{\text{Adjacent}}{\text{Hypotenuse}}$$

$$\tan \theta = \frac{\text{Opposite}}{\text{Adjacent}}$$

These ratios need to be committed to Memory.

AC Theory.

Where do the Ratios come from?

AC Theory.

Where do these ratios come from ?

- pi (π) is the ratio of the circumference of a circle to its diameter. We approximate to $22/7$.
- It can be calculated using the following series:-
- $\text{PI} = 4 - 4/3 + 4/5 - 4/7 + 4/9 - 4/11$

AC Theory.

Where do these ratios come from ?

- The number “e” used in logarithms and exponential growth or decay.
- It can be calculated using the following series:-
- $e = 1/0! + 1/1! + 1/2! + 1/3! + 1/4!$
where ! indicates factorial.
- Note $0!$ is a mathematical quirk and $= 1$
- example $3! = 1 * 2 * 3 \dots 4! = 1 * 2 * 3 * 4$ etc.

AC Theory.

Where do these ratios come from ?


- Sine (x) , Cos (x) and Tan (x)
where x is in radians
- They can be calculated using the following series or formulae:-
- $\text{Sin (x)} = x - x^3/3! + x^5/5! - x^7/7! + x^9/9!$
- $\text{Cos (x)} = 1 - x^2/2! + x^4/4! - x^6/6! + x^8/8!$
- $\text{Tan (x)} = \text{Sin (x)} / \text{Cos (x)}$

AC Theory.

Example of usage.

Trigonometrical Ratios Example

AC Theory.

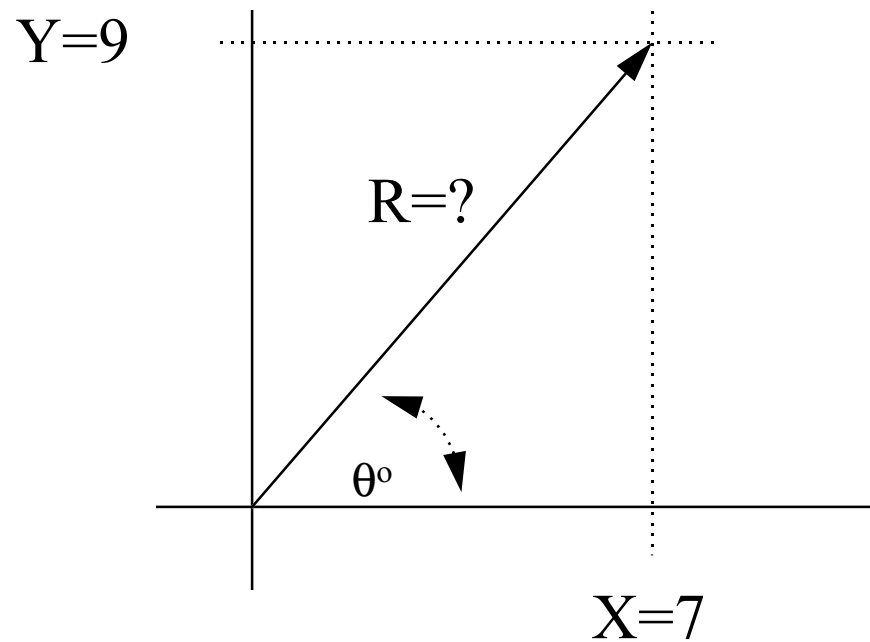

$$\sin \theta = \frac{\text{Opposite}}{\text{Hypotenuse}}$$

$$\cos \theta = \frac{\text{Adjacent}}{\text{Hypotenuse}}$$

$$\tan \theta = \frac{\text{Opposite}}{\text{Adjacent}}$$

Trigonometrical
Ratios Example

AC Theory.

Given that:


$$Y = 9 \text{ and}$$

$$X = 7$$

Calculate:


Length of R and

Angle θ

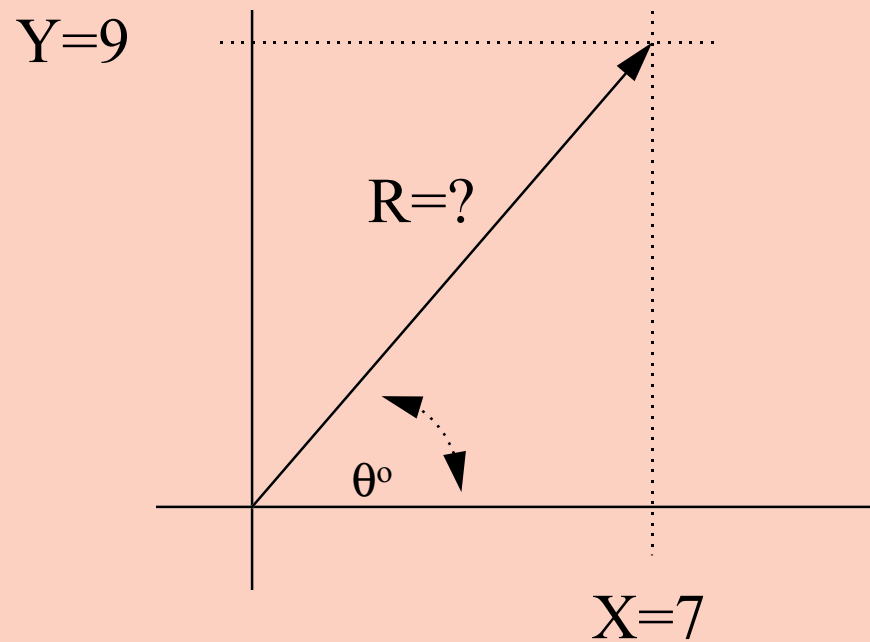

Trigonometrical Ratios Example

AC Theory.

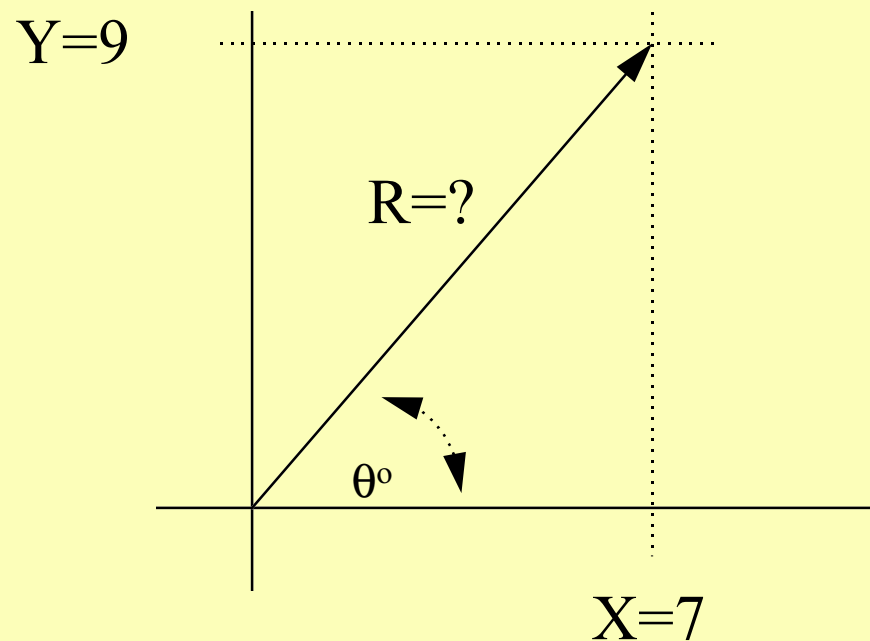

$$\text{Opposite} = Y = 9$$

$$\text{Adjacent} = X = 7$$

Using:-

$$\text{Tan } \theta = \frac{\text{Opposite}}{\text{Adjacent}}$$


$$\text{Tan } \theta = \frac{9}{7} = 1.2857$$

Therefore:

$$\theta = \text{Tan}^{-1}(1.2857) = 52.125^\circ$$

Trigonometrical Ratios Example

AC Theory.

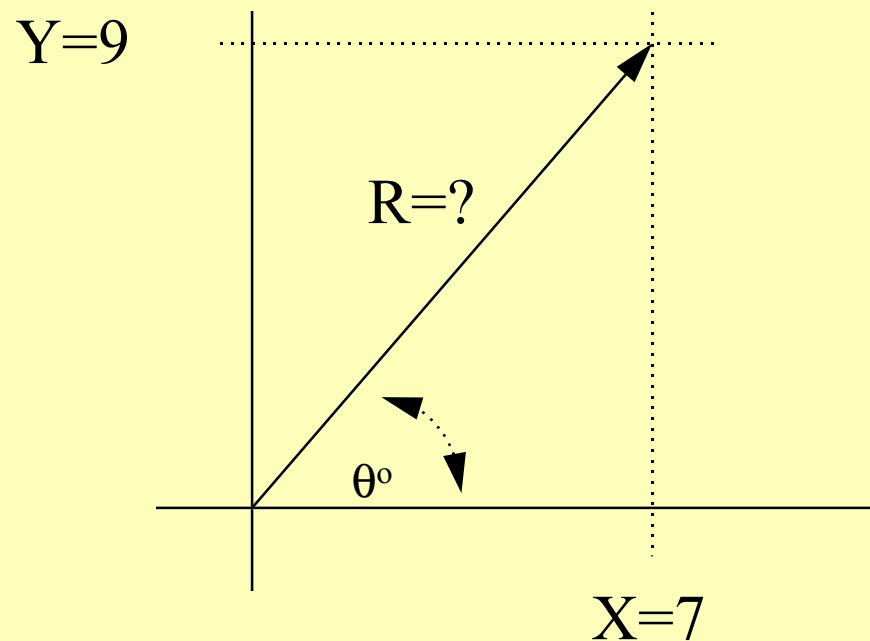

$$\text{Opposite} = Y = 9$$

$$\text{Adjacent} = X = 7$$

Using Pythagoras :-

$$C = \sqrt{A^2 + B^2}$$

$$R^2 = X^2 + Y^2$$

$$R^2 = 7^2 + 9^2 = 49 + 81$$

$$R^2 = 130$$

$$R = \sqrt{130} = 11.4$$

Trigonometrical
Ratios Example

AC Theory.


Given that:

Length of $R = 10$ and

Angle $\theta = 30^\circ$


Calculate:

X and Y

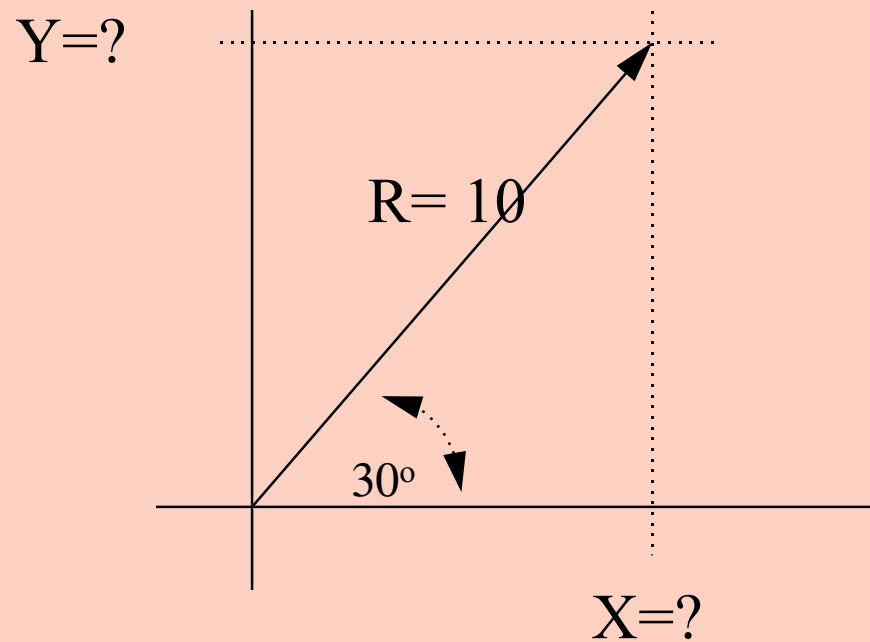

Trigonometrical Ratios Example

AC Theory.

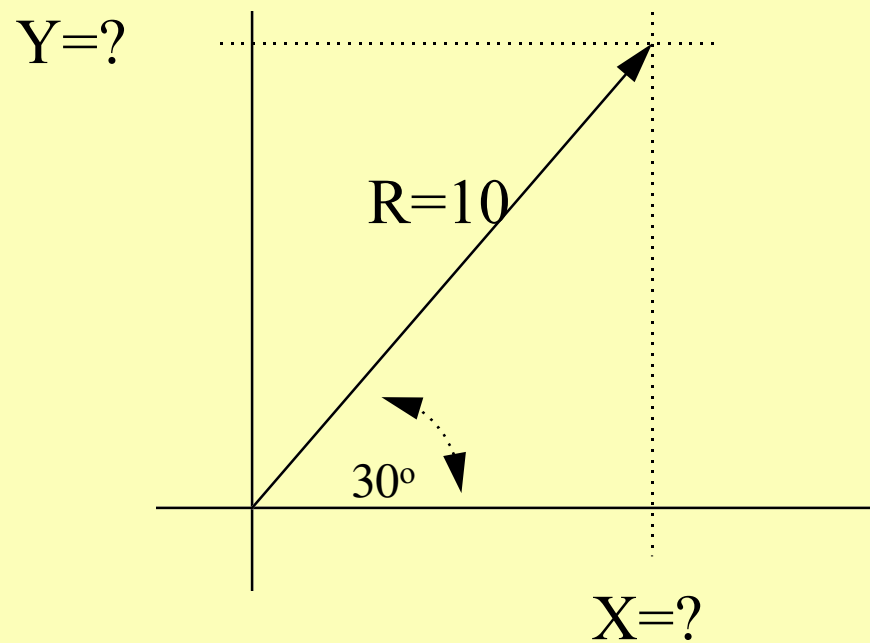

$$\text{Angle} = 30^\circ = \theta$$

$$\text{Radius } R = 10 = \text{Hypotenuse}$$

Using:-

$$\sin \theta * \text{Hypotenuse} = \text{Opposite} = Y$$

Therefore


$$0.5 * 10 = Y = 5$$

$$Y = 5$$

$$\sin \theta = \frac{\text{Opposite}}{\text{Hypotenuse}}$$

Trigonometrical Ratios Example

AC Theory.

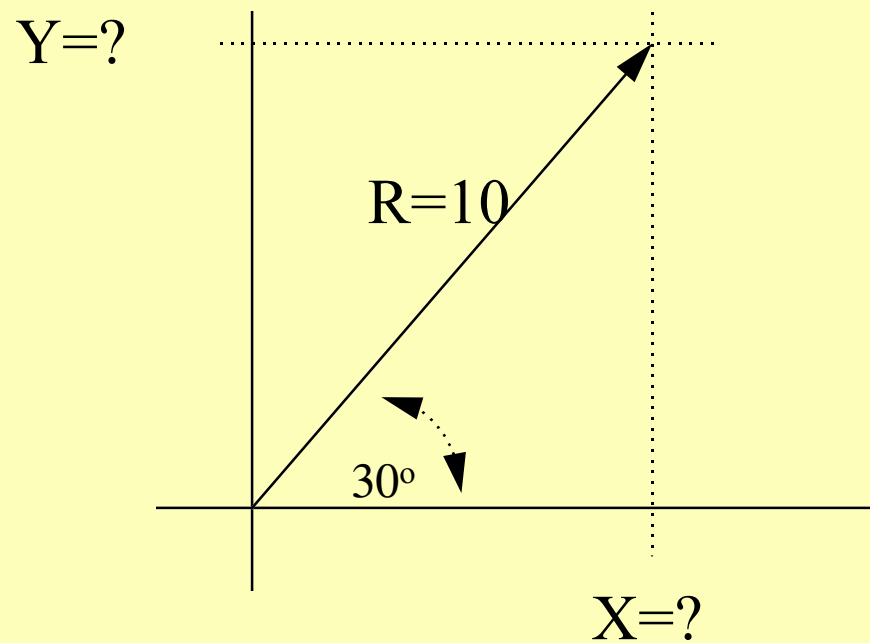

$$\text{Angle} = 30^\circ = \theta$$

$$\text{Radius } R = 10 = \text{Hypotenuse}$$

Using:-

$$\cos \theta * \text{Hypotenuse} = \text{Adjacent} = X$$

Therefore

$$0.866 * 10 = X = 8.66$$


$$X = 8.66$$

$$\cos \theta = \frac{\text{Adjacent}}{\text{Hypotenuse}}$$

AC Theory.

Concepts and Terminology.

AC Theory.

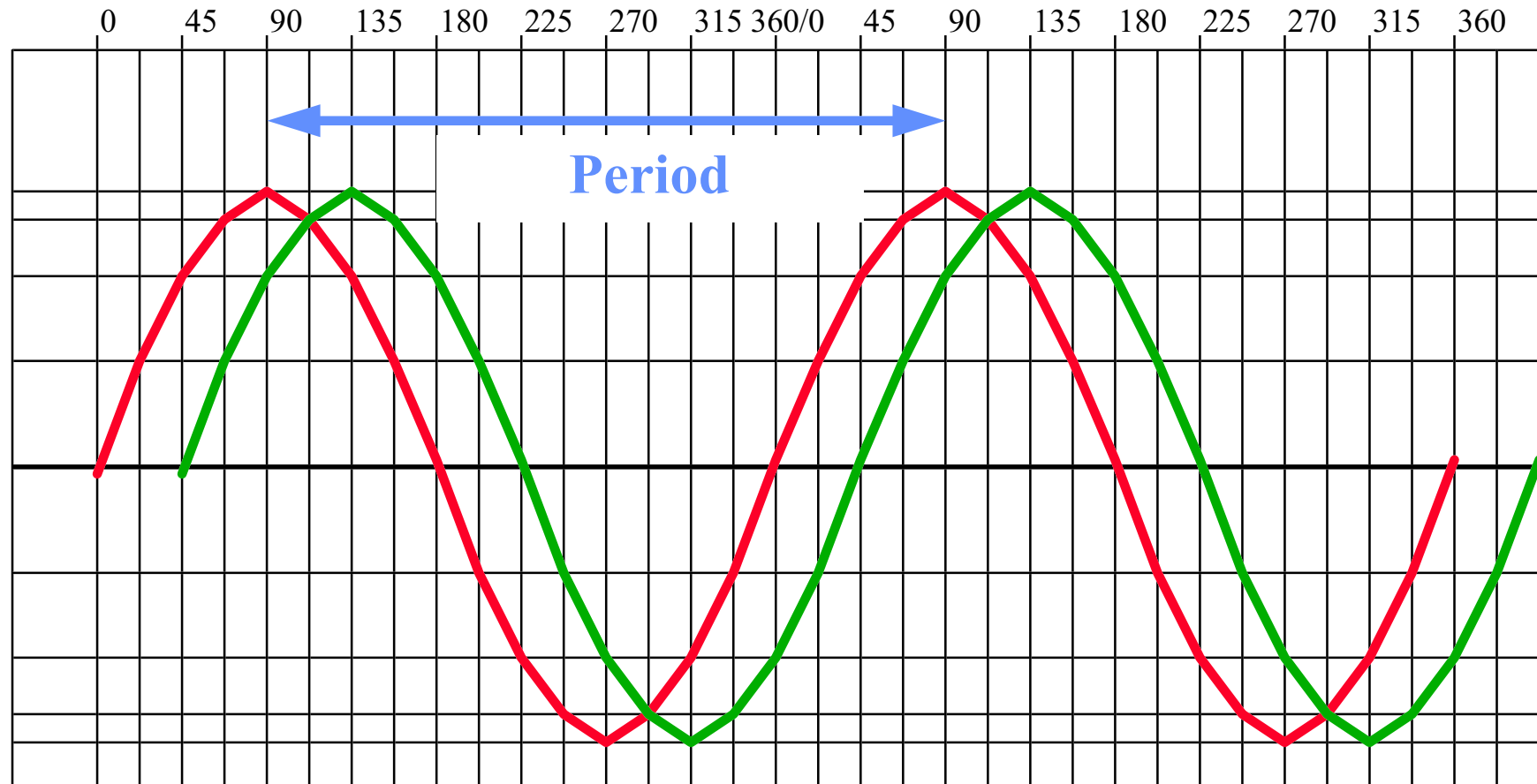


The **Green** Signal “**LAGS**” Reference **Red** Signal by 45°

Signal Phase Difference Measurement

Lag means that it starts after the reference signal.

AC Theory.

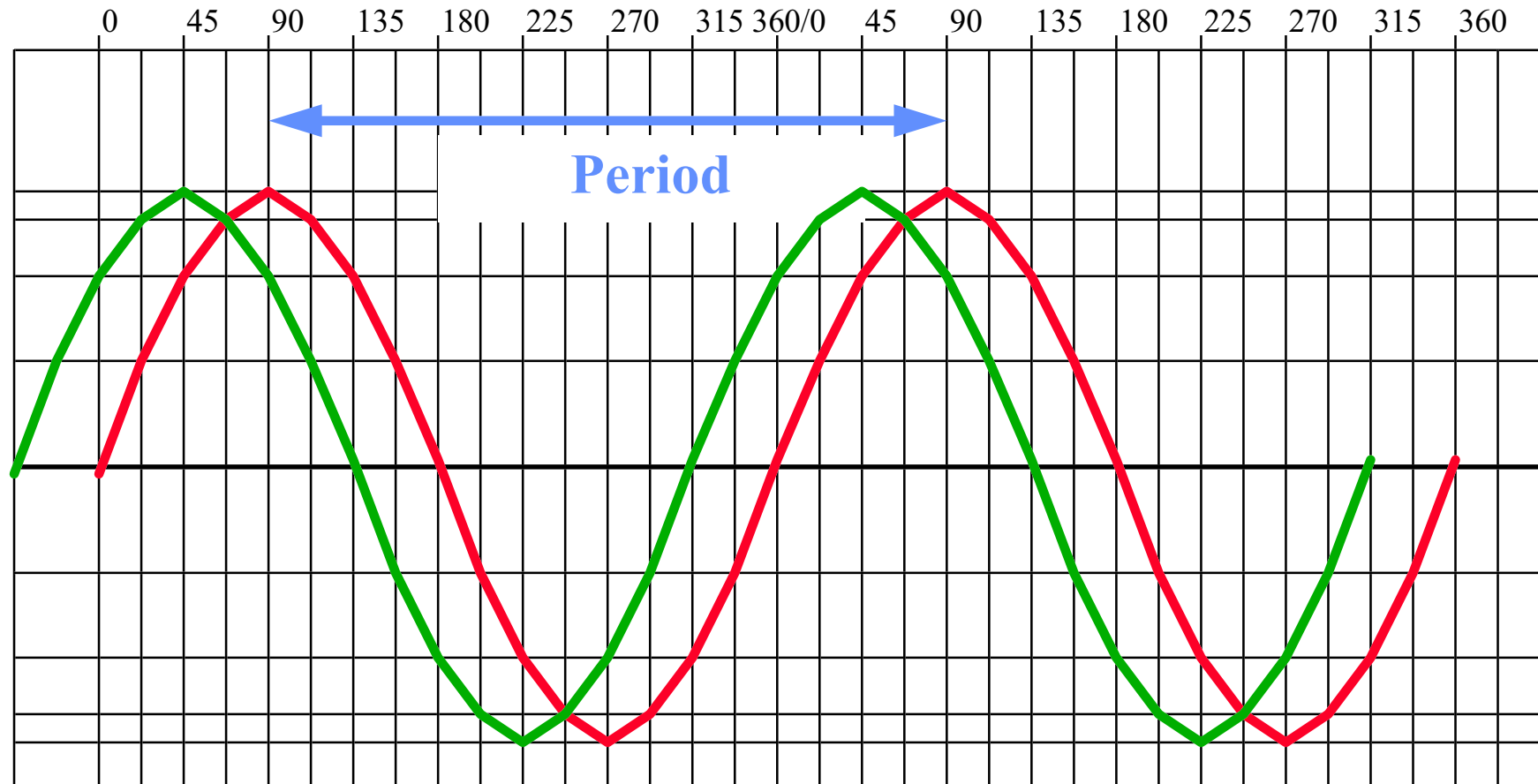


The **Green** Signal **“LEADS”** Reference **Red** Signal by 45°
Signal Phase Difference Measurement

Lead means that it starts before the reference signal.

AC Theory.

Instantaneous Voltages and Current

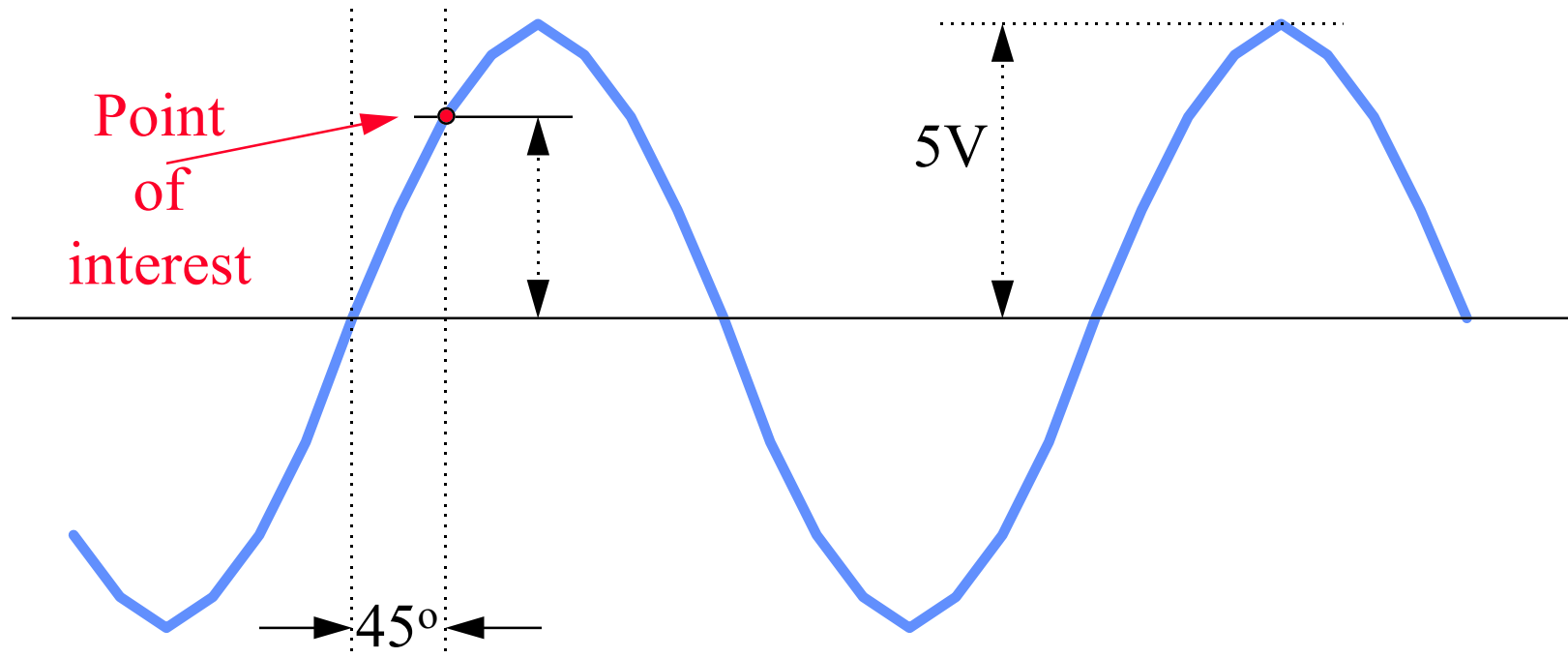

Amplitude of a sine wave = $V_{\text{peak}} \sin (\theta \text{ Angle} \pm \phi \text{ phase shift})$

Amplitude of a sine wave = $5 \sin (45^\circ \pm 0^\circ) = 3.53 \text{ Volts}$

AC Theory.


- Example:-
- A sine wave has a peak value of 20 Volts.
- What is the instantaneous value at $+65^\circ$ from the 0° reference ?
- If the signal lags the reference by 5° what would the new instantaneous value at $+65^\circ$ from the 0° reference be?

AC Theory.

- Example:-
- A sine wave has a peak value of 20 Volts.
- What is the instantaneous value at $+65^\circ$ from the 0° reference?
- Solution
- Amplitude of a sine wave
 - = $20 \sin (65^\circ \pm 0^\circ)$
 - = 18.126 Volts

AC Theory.

Instantaneous Voltages and Current

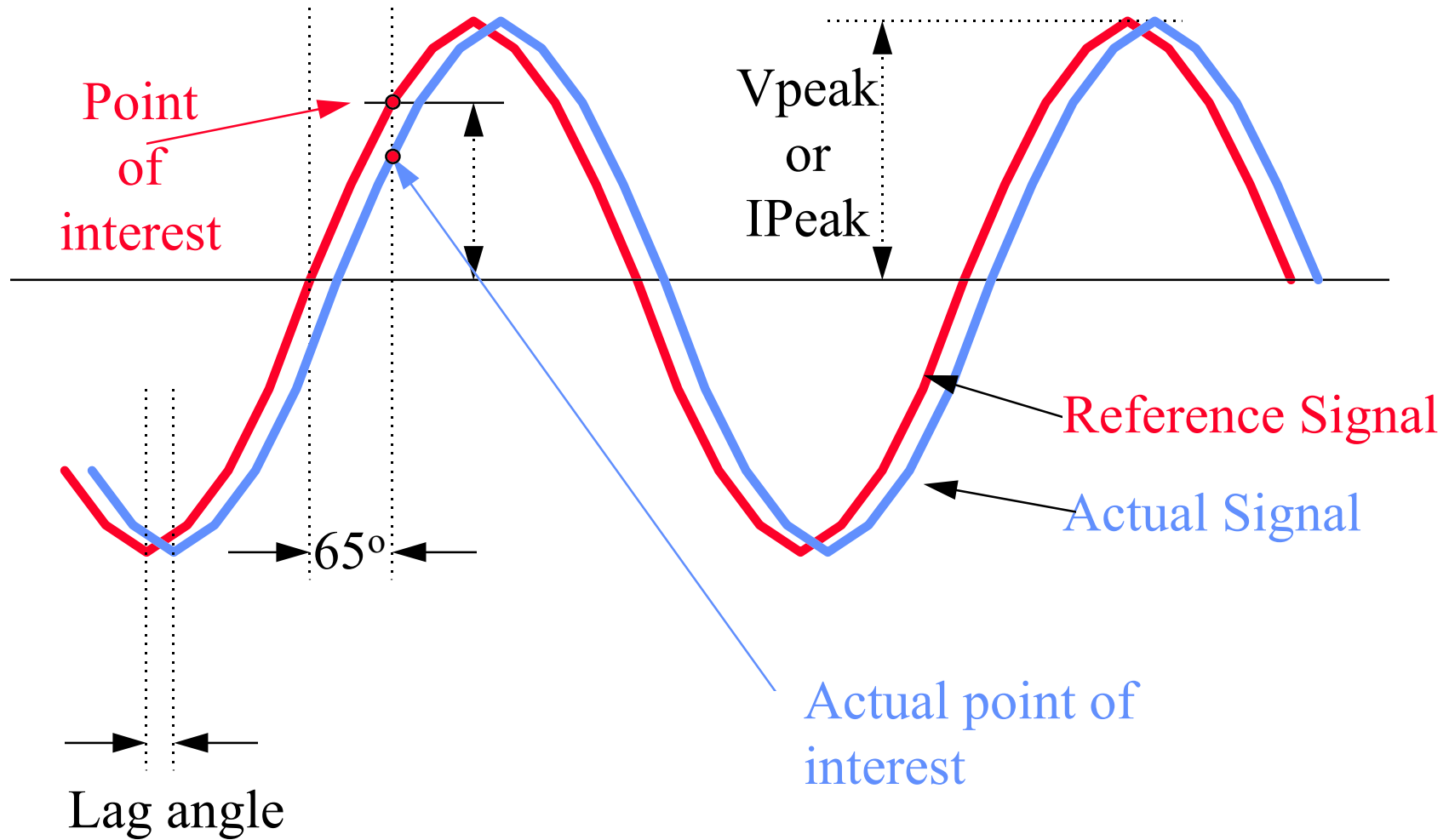


AC Theory.

- Example:-
- A sine wave has a peak value of 20 Volts.
- If the signal lagged the reference by 5° what would the new instantaneous value at $+65^\circ$ from the reference be?
- Solution
- Amplitude of a sine wave with 5° Lag
$$= 20 \sin (65^\circ - 5^\circ) = 20 \sin (60^\circ)$$
$$= 17.32 \text{ Volts}$$


RL or RC Networks

AC Theory.

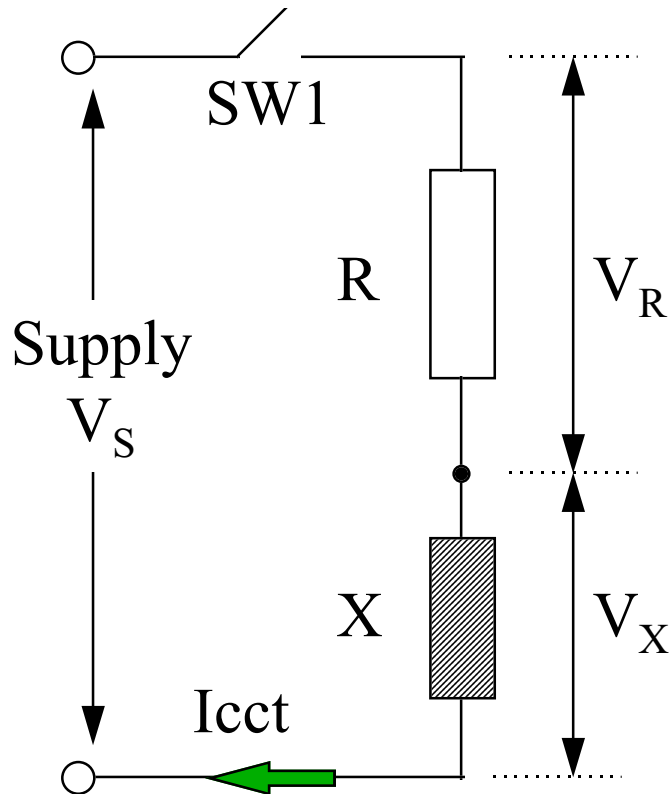
If we consider this circuit below we can observe that Current flowing through the circuit is common to both R and X.



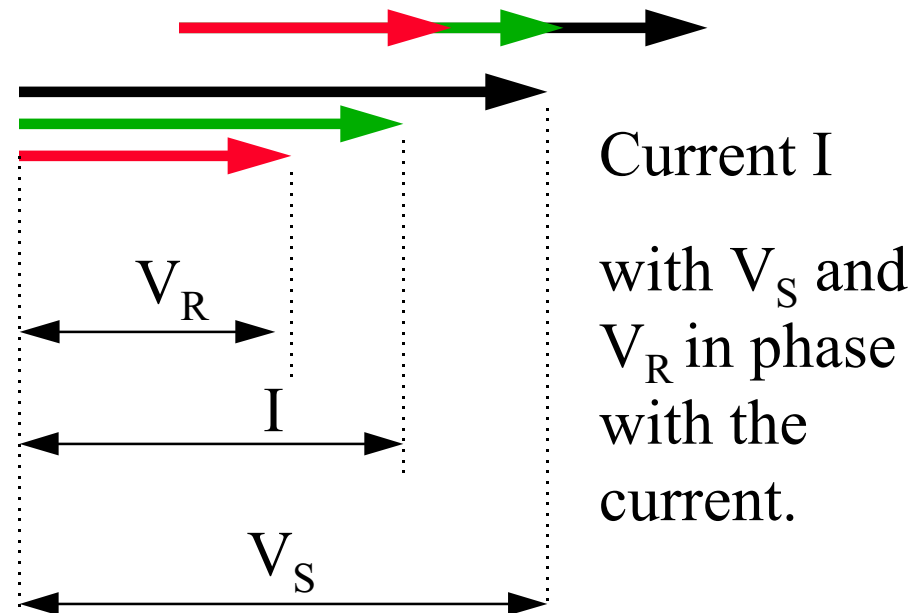Graphically we can represent these amplitudes on a vector diagram with Current I as the reference.




AC Theory.

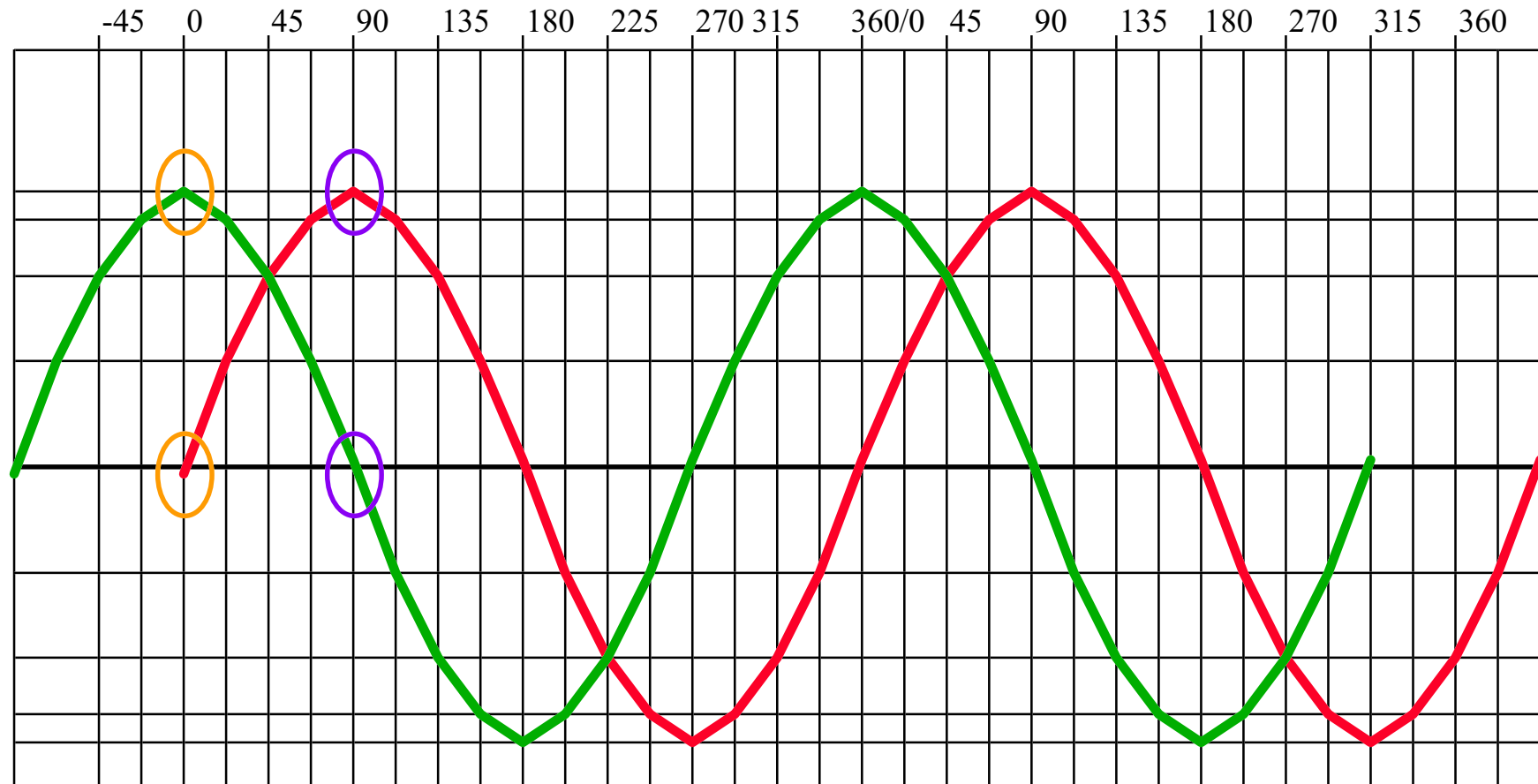

Remember with the Inductor

Point 1: When the voltage across the Resistor was minimum then the voltage across the Inductor was a maximum. **Point 2:** When the voltage across the resistor was maximum then the voltage across the Inductor was a minimum.

AC Theory.

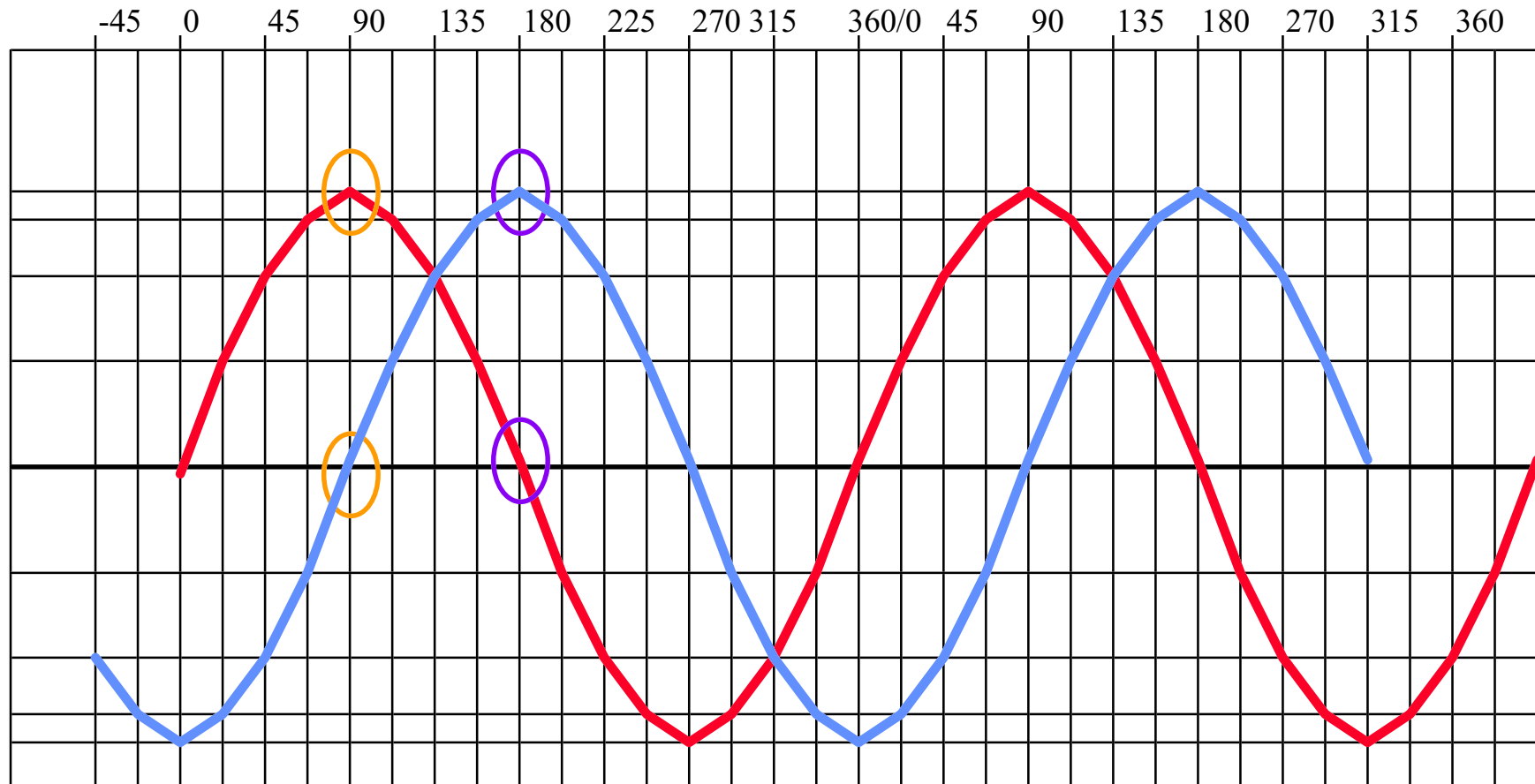


Remember with the Capacitor


Point 1: When the voltage across the Resistor was maximum then the voltage across the Capacitor was a minimum. **Point 2:** When the voltage across the resistor was minimum then the voltage across the Capacitor was a maximum.

AC Theory.

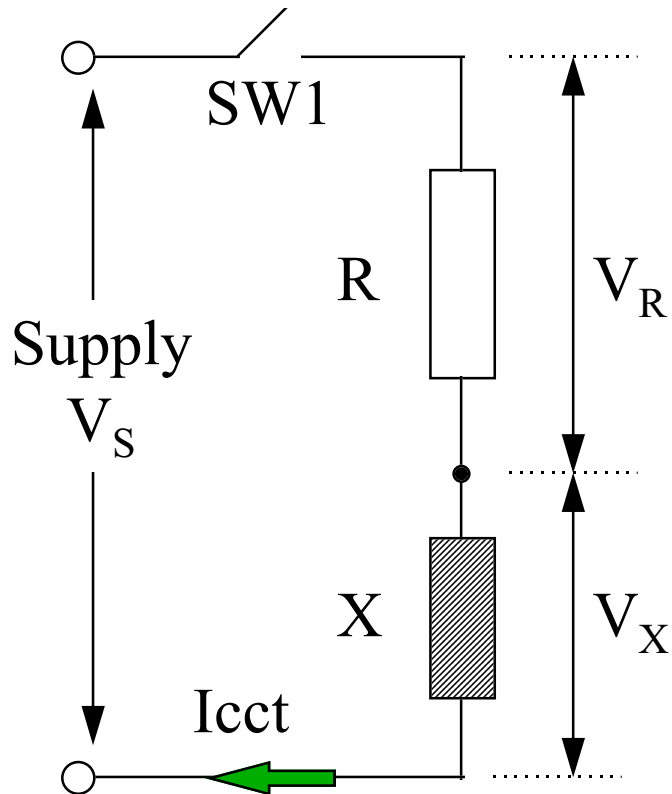If we consider this circuit below we can observe that Current flowing through the circuit is common to both R and X.



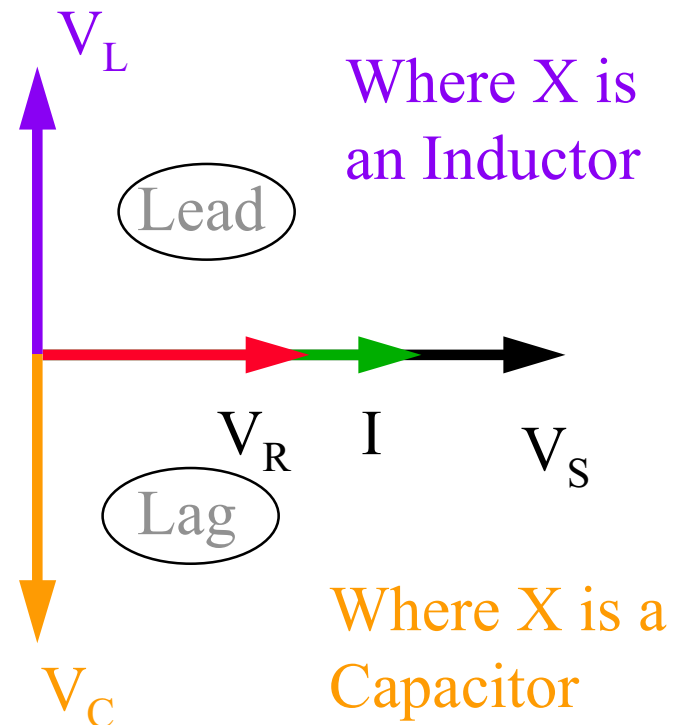Graphically we can represent these amplitudes on a vector diagram with Current I as the reference.



Example

AC Theory.

- Sketch a graph to show the following quantities:-
- A sinusoidal voltage of rms value 10V and frequency 5kHz.
- A sinusoidal current of rms value 2mA and frequency 5kHz lagging the voltage by 45° .
- Use the x-axis for the common time scale and the y-axis for both the voltage and current scales. Show at least two cycles of each waveform.
- Indicate significant values and units on each scale.

Example


AC Theory.

- Step one calculate any appropriate values:-
- $10\text{V rms} = \text{therefore Peak Voltage} = 1.4142 * 10 = 14.142 \text{ Volts.}$
- $2\text{mA rms} = \text{therefore Peak Current} = 1.4142 * 2 = 2.8284 \text{ mA.}$
- $\text{Period} = 1/\text{frequency} = 1/5000 = 200\mu \text{ s}$

14.142 Volts Peak

AC Theory.

2.828 mA Peak

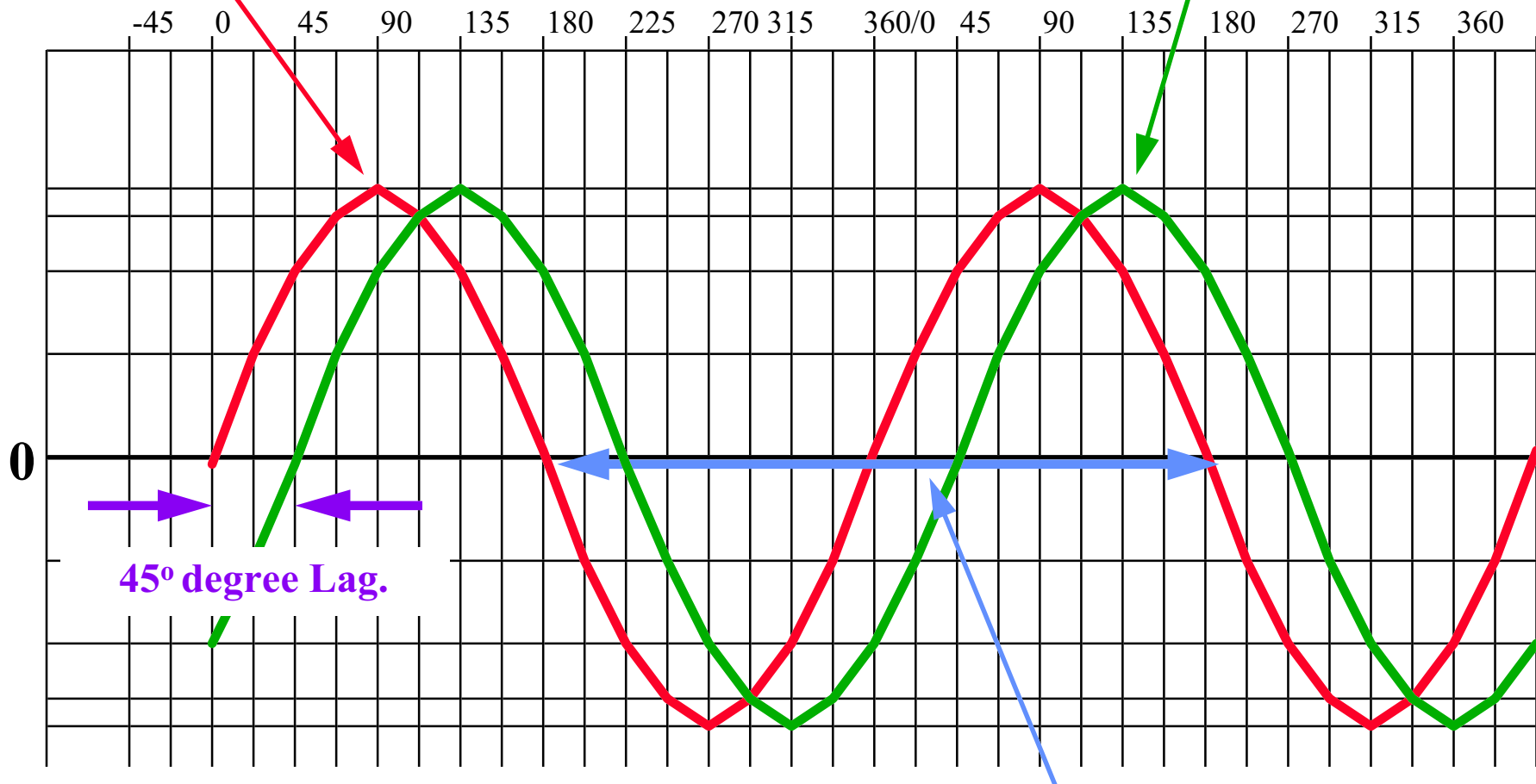

45° degree Lag.

Period 200μS

Signal 1: The voltage waveform

Signal 2: The current waveform lagging the voltage waveform by 45°.

AC Theory.


Power in an AC Circuit.

AC Theory.

- Power in AC Circuits:-
- In a purely **Resistive** AC circuit, **all** the **energy** delivered by the source is **dissipated** in the form of **heat** by the resistance.
- In a purely (**Inductive or Capacitive**) circuit, **all** the **energy** delivered by the source is stored in the (Inductor or Capacitor) during a portion of the voltage cycle and **returned** to the source during another portion of the cycle so that there is **no** net **energy** conversion **to heat**.

AC Theory.

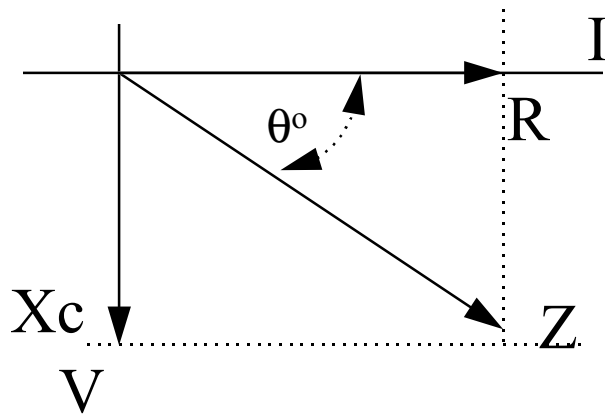- Power in AC Circuits:-
- Apparent power (P_a) = $(I_{\text{tot}})^2 * Z$
 - The unit of apparent power is :-
 - The volt-ampere (VA)
- True Power can be expressed $P_{\text{true}} = P_a * \text{Cos } \theta$



$\text{Cos } \theta = \text{the Power Factor (PF)}$

$$\text{Power Factor} = \frac{\text{Watts}}{\text{VA}}$$

AC Theory.

- Example:-
- An electrical machine powered by 240Volts mains draws 10Amps from the supply. The Phase angle between voltage and current is 30° .
- Calculate the true power.

AC Theory.

- Example:-
- An electrical machine powered by 240Volts mains draws 10Amps from the supply. The Phase angle between voltage and current is 30°.
- Calculate the true power.
 - Power $P = VI \cos \theta$
 - Power $P = 240 * 10 * \cos 30$
 - Power $P = 240 * 10 * 0.87$
 - Power $P = 2088 \text{ Watts}$

Example

AC Theory.

- The following measurements were taken in an inductive ac circuit.
 - Supply Voltage 250V
 - Supply Current 16A
 - Total real power 2400W
- Calculate the circuit impedance.
- Calculate the circuit power factor.

AC Theory.

- Calculate:-
- Circuit impedance
 - $Z = V/I = 250/16 = 15.625\Omega$
- Calculate:-
- Power Factor
 - (PF) $\text{Cos } \phi = \text{True Power/ Apparent power}$
 - $\text{Cos } \phi = 2400/250*16 = 2400/4000 = 0.6$
- Calculate:-
- Phase angle
 - $\text{Cos } \phi = 0.6 = 53.13^\circ$

AC Theory.

Calculating the
Impedance (AC Resistance)
of a Reactive Component
(Capacitor or Inductor)
in an AC Circuit .

AC Theory.

- Impedance of a Capacitor is :-


$$X_c = \frac{1}{2\pi FC}$$

Where :-

X_c = Reactance in Ohms.

F = Frequency in Hertz.

C = Capacitance in Farads.

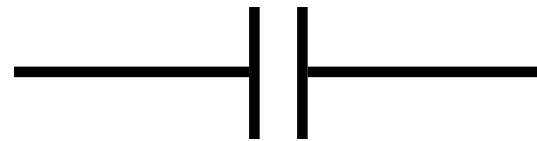

AC Theory.

- Impedance of a Inductor is :-


$$Xl = 2\pi FL$$

Where :-

Xl = Reactance in Ohms.

F = Frequency in Hertz.

L = Inductance in Henries.

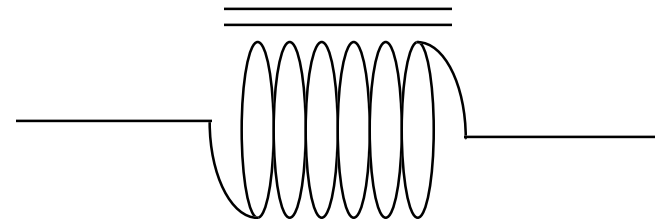

AC Theory.

- Example:-
- What is the impedance of a $10\mu\text{F}$ Capacitor at a frequency of 1KHz .

Solution

AC Theory.

- What is the impedance of a 10 μ F Capacitor at a frequency of 1KHz.
- Solution
- $X_c = 1/2\pi FC = 1/(2 * \pi * (1*10^3) * (10*10^{-6}))$
- $X_c = 1/(6.283 * 10^{-3}) = 159.15\Omega$

AC Theory.

- Example:-
- What is the impedance of a 10H Inductor at a frequency of 1KHz.


Solution

AC Theory.

- What is the impedance of a 10H Inductor at a frequency of 1KHz.
- Solution
- $X_L = 2\pi FL = (2 * \pi * (1 * 10^3) * (10))$
- $X_L = (6.283 * 10^4) = 62.83\text{K}\Omega$

AC Theory.

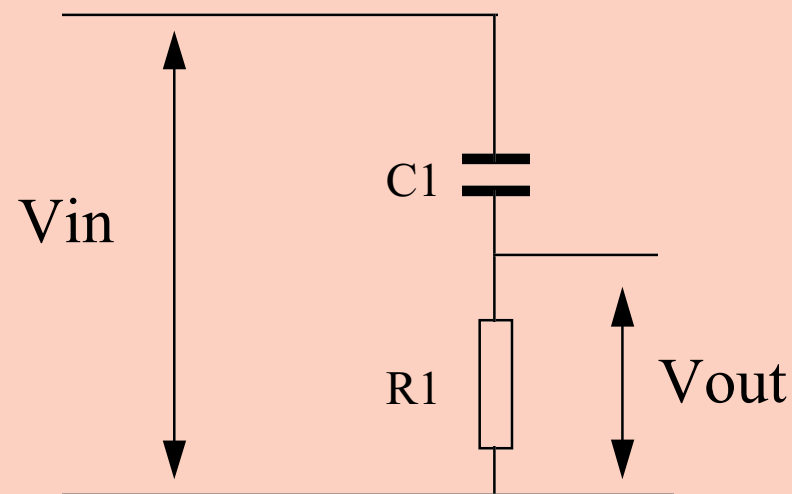
- Example:-
- The Capacitor C1 has a value of 1000nF.
- The Resistor R1 has a value of 1000 Ω .
- When an input signal of 240Volts at a frequency of 50Hz is applied what voltage will be present on the output terminals Vout.



Solution

AC Theory.

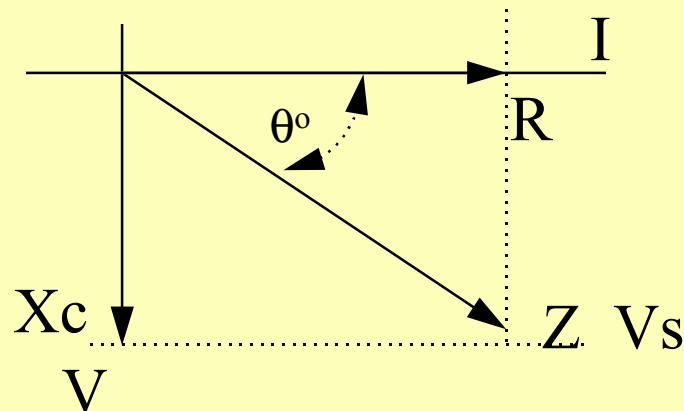- Reactance of Capacitor $X_C = 1/2\pi FC$
 $= 1/(2 * \pi * 50 * (1*10^{-6})) = 3183\Omega$
- Circuit Impedance $= \sqrt{R^2 + X_C^2} = \sqrt{3183^2 + 1000^2}$
 $= \sqrt{11131489} = 3336\Omega$
- Phase angle $\tan \theta = 3182/1000 = 3.182$
- Therefore $\theta = 72.55^\circ$
- Voltage out $= V_s * \sin \theta = 240 * \sin \theta = 228.9$ Volts



AC Theory.

Power Factor Correction in AC Circuits.

AC Theory.

- Why Power correction in AC Circuits ? :-
- In a purely **Resistive** AC circuit, **all the energy** delivered by the source is **dissipated** in the form of **heat/energy** by the Load.
- If the Load is (**Inductive or Capacitive**) it will not use all the raw power effectively.
 - It will need conductors to be thicker because of the higher current requirements.
 - It will need the insulation to be thicker because of the higher voltage requirements.
- It could reduce costs to the consumer if the power factor is corrected.

AC Theory.


- Some advantages of **Power Factor correction** are:-
- Lower voltages \therefore Thinner insulation.
- Lowers current \therefore Thinner conductors.
- Less losses in transmission system / grid.
- Less power regulation needed at the generator station.
- Less power generated at the generator station.
- Reduces costs on industrial tariffs.
- Leading capacitor current cancels lagging current of load.
- Connect Capacitor of appropriate value in parallel.
- Reduces current from supply for inductive load.
- Reduces overall kVA.

AC Theory.

- How do we correct the Power Factor ? :-
- If the load is (Inductive) then we add a (Capacitor) to restore the Power Factor ($\cos \theta$) back to 1.
- If the load is (Capacitive) then we add an (Inductor) to restore the Power Factor back to 1.
- If we are dealing with a series circuit then we could add a Capacitor in series which had the same reactance value as the circuit Inductance.
- The Inductance would cause the current to LAG, the Capacitance would cause the current to LEAD and the overall effect would give a circuit that appears to be purely Resistive.

AC Theory.

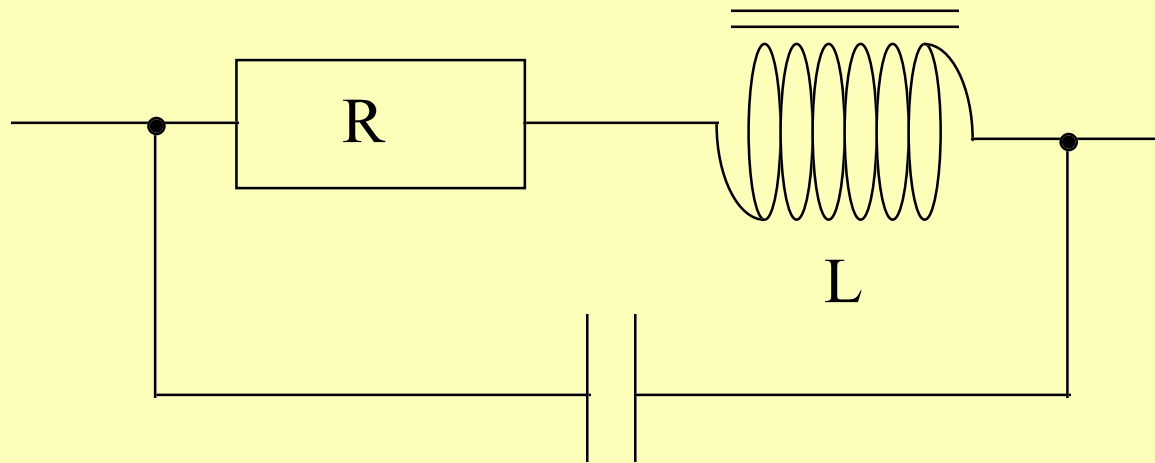- Basic circuit diagram with one method of Power factor correction.



Capacitor

Used to correct power factor

AC Theory.

- A $50\mu\text{F}$ capacitor is connected in series with a $2\text{K}7\Omega$ resistor across a 100V , 50Hz supply calculate.
- The phase angle between voltage and current.
- The Voltage across the capacitor.
- What value of inductance would give the same phase angle?

Solution

AC Theory.

- Phase angle may be obtained from $\tan \theta = X_c/R$
- Reactance of Capacitor $X_C = 1/2\pi FC$
 $= 1/(2 * \pi * 50 * (10*10^{-6})) = 318.3\Omega$
- Phase angle $\tan \theta = 318/2700 = 0.1179 = 6.72^\circ$
- Circuit Impedance $= \sqrt{R^2+X_C^2} = \sqrt{318.3^2+2K7^2}$
 $= \sqrt{7391314.89} = 2718.69\Omega$
- Circuit Current $V/X = 100/2718.7 = 36.78\text{mA}$
- Capacitor voltage $= X_c*I = 318.3*36.78*10^{-3}$
 $= 11.71 \text{ Volts.}$
- Inductive reactance $= 2\pi FL = X_c = 318.3$
- $L = 318.3/2 * \pi * 50 = 1 \text{ Henry}$

AC Theory.

- Part 1
- A circuit with a 230V, 50Hz supply has a $50\mu\text{ F}$ capacitor and 200Ω Resistor in series.
- Calculate reactance of the capacitor.
- Calculate the circuit impedance.
- Part 2
- A series ac circuit has a coil of negligible resistance in series with a resistor. The Voltages measured as follows:-
- Across the coil 160V , Across the resistor 120v
- Draw the phasor diagram of these voltages.
- Determine the supply voltage.

Solution


AC Theory.

- Part 1.
- Reactance of Capacitor $X_C = 1/2\pi fC$
 $= 1/(2 * \pi * 50 * (50 * 10^{-6})) = 63.66\Omega$
- Circuit Impedance $= \sqrt{R^2 + X_C^2} = \sqrt{63.66^2 + 200^2}$
 $= \sqrt{44052.8} = 209.88\Omega$

Solution

AC Theory.

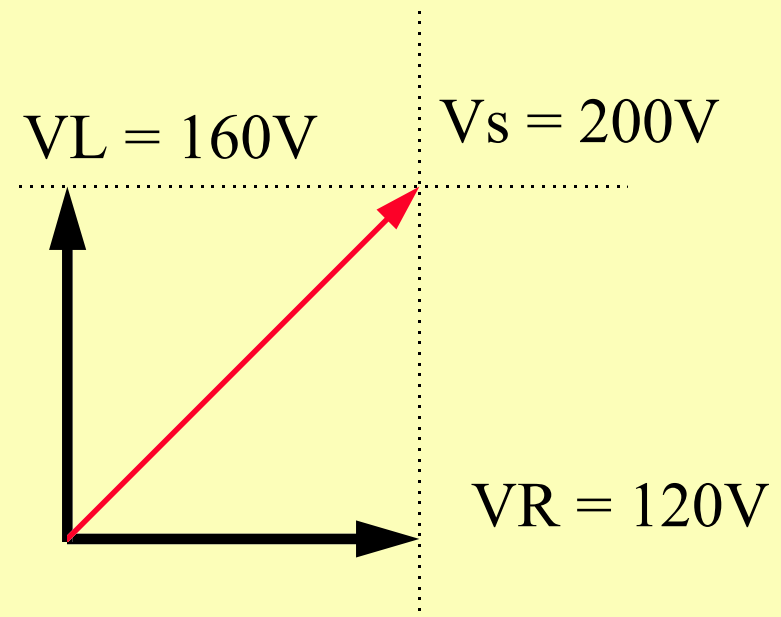
- Part 2.
- $V_S = \sqrt{(V_L)^2 + (V_R)^2}$
- $V_S = \sqrt{(160)^2 + (120)^2}$
- $V_S = \sqrt{25600 + 14400}$
- $V_S = \sqrt{40000}$
- $V_S = 200$



RLC Networks

AC Theory.

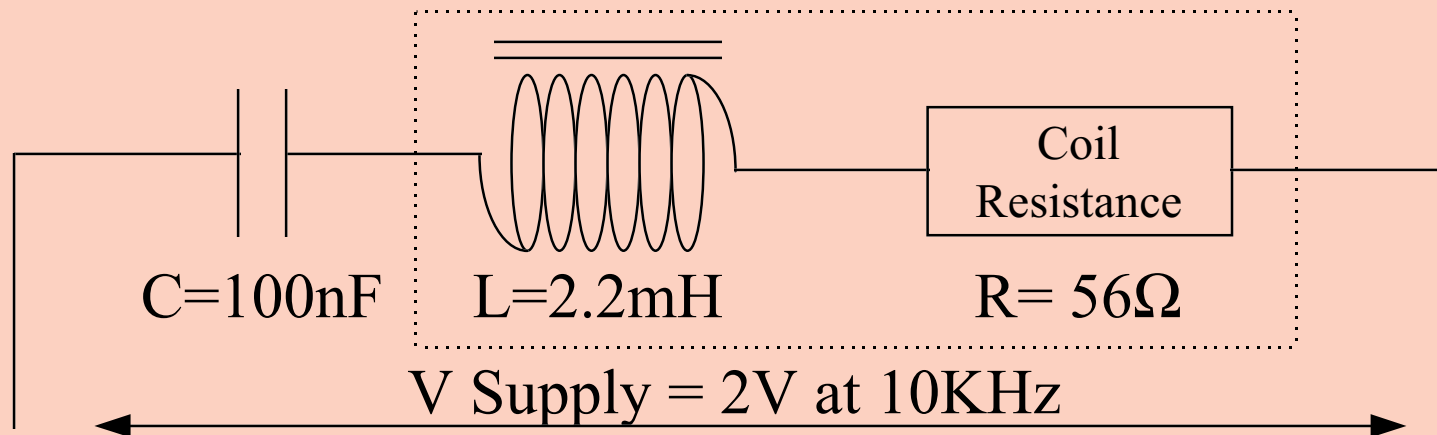- Given the following circuit.
- Calculate the circuit impedance.
- Calculate current flowing in the circuit .
- Calculate and the phase difference between the supply voltage and current.
- Calculate the voltage across the Capacitor
- Calculate the voltage across the Inductor.
- Draw the phasor diagram of these voltages.



AC Theory.

- $X_C = 1/(2 \pi f C)$ Where $C=100\text{nF}$ and $f=10\text{KHz}$
- $X_C = 1/(2 * \pi * 10000 * 100 * 10^{-9}) = 159.15 \Omega$
- $X_L = 2 \pi f L$ Where $L=2.2\text{mH}$ and $f=10\text{KHz}$
- $X_L = 2 \pi f L = 2 * \pi * (1000) * (2.2 * 10^{-3}) = 138.23 \Omega$
- Since X_C is greater than X_L the circuit is capacitive. \therefore Circuit reactance =
- $X_C - X_L = 159.15 - 138.23 = 20.92 \Omega$
- Circuit impedance $Z = \sqrt{[R^2 + (X_L^2 - X_C^2)]}$
 $Z = \sqrt{(56)^2 + (-20.92)^2} = 59.78 \Omega$
- Current $I = I_{cct} = V/Z = 2/59.78 = 33.46\text{mA}$
- Phase angle $\phi = \arctan(X_L - X_C)/R$
- Phase angle $\phi = \arctan -20.92/56 = -20.48^\circ$


AC Theory.

- Impedance of coil (Assume R = Coil Resistance)
- $Z_{\text{coil}} = \sqrt{R^2 + XL^2} = \sqrt{[(56)^2 + (138.23)^2]}$
- $Z_{\text{coil}} = 149.14\Omega$
- Voltage across coil $V_{\text{coil}} = I_{\text{cct}} * Z_{\text{coil}}$
- $V_{\text{coil}} = (0.03346)*(149.14) = 4.989V$
- Coil $\phi = \arctan(XL / R) = 90^\circ$ (Circuit Capacitive)

- Voltage across capacitor VC
- $VC = I * XC = (0.03346)*159.15 = 5.325V$
- Phase angle of the Capacitor = Cap ϕ
- Cap $\phi = \arctan(-XC / R)$
- Cap $\phi = \arctan(-159.15 / 56) = -70.61^\circ$

AC Theory.

- Phasor Diagram

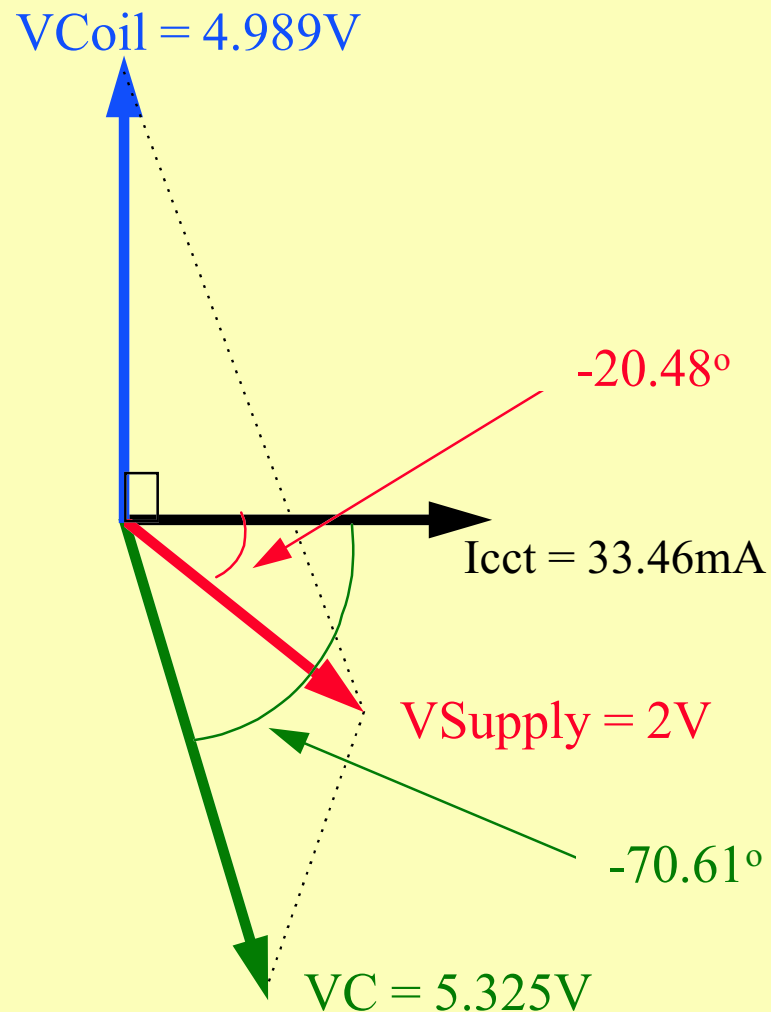


Note:

The supply voltage V is the phasor sum of V_{Coil} and V_{C}

AC Theory.

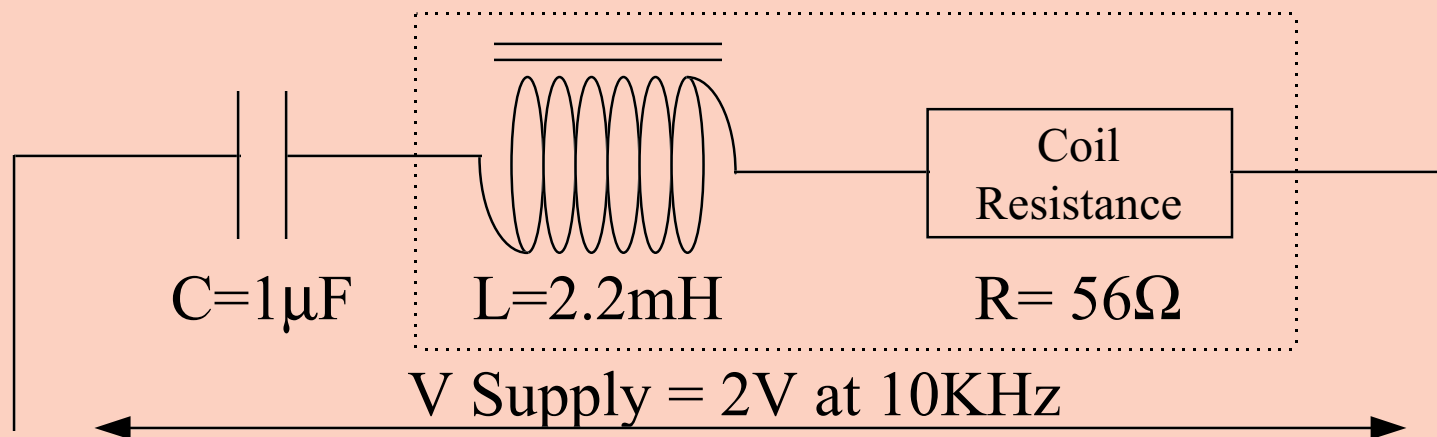- Given the following circuit.
- Calculate the circuit impedance.
- Calculate current flowing in the circuit .
- Calculate and the phase difference between the supply voltage and current.
- Calculate the voltage across the Capacitor
- Calculate the voltage across the Inductor.
- Draw the phasor diagram of these voltages.



AC Theory.

- $X_C = 1/(2 \pi f C)$ Where $C=100\text{nF}$ and $f=10\text{KHz}$
- $X_C = 1/(2 * \pi * 10000 * 1 * 10^{-6}) = 15.915 \Omega$
- $X_L = 2\pi f L$ Where $L=2.2\text{mH}$ and $f=10\text{KHz}$
- $X_L = 2\pi f L = 2 * \pi * (1000) * (2.2 * 10^{-3}) = 138.23 \Omega$
- Since X_L is greater than X_C the circuit is Inductive. \therefore Circuit reactance =
- $X_L - X_C = 138.23 - 15.92 = 122.31 \Omega$
- Circuit impedance $Z = \sqrt{R^2 + (X_L^2 - X_C^2)}$
 $Z = \sqrt{(56)^2 + (122.31)^2} = 134.52 \Omega$
- Current $I = I_{\text{cct}} = V/Z = 2/134.52 = 14.87\text{mA}$
- Phase angle $\phi = \arctan(X_L - X_C)/R$
- Phase angle $\phi = \arctan 122.31/56 = 65.4^\circ$


AC Theory.

- Impedance of coil (Assume R = Coil Resistance)
- $Z_{\text{coil}} = \sqrt{R^2 + XL^2} = \sqrt{[(56)^2 + (138.23)^2]}$
- $Z_{\text{coil}} = 149.14\Omega$
- Voltage across coil $V_{\text{coil}} = I_{\text{cct}} * Z_{\text{coil}}$
- $V_{\text{coil}} = (0.01487)*(149.14) = 2.217V$
- Coil $\phi = \arctan(138.23 / 56) = 67.95^\circ$

- Voltage across capacitor VC
- $VC = I * XC = (0.01487)*15.915 = 0.2366V$
- Phase angle of the Capacitor = Cap ϕ
- Cap $\phi = \arctan (-XC / R) = -90^\circ$ (Circuit Inductive)

AC Theory.

- Phasor Diagram

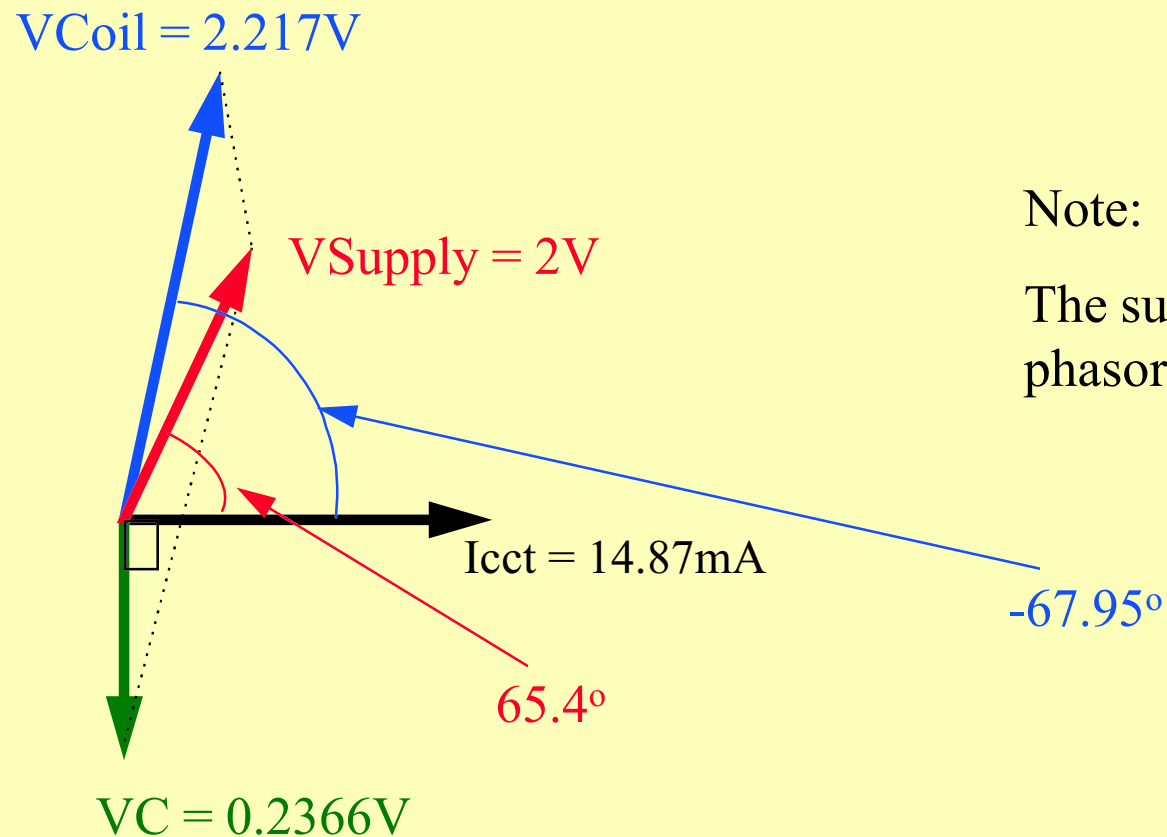


Note:

The supply voltage V is the phasor sum of V_{Coil} and V_{C}

Resonant Networks

AC Theory.

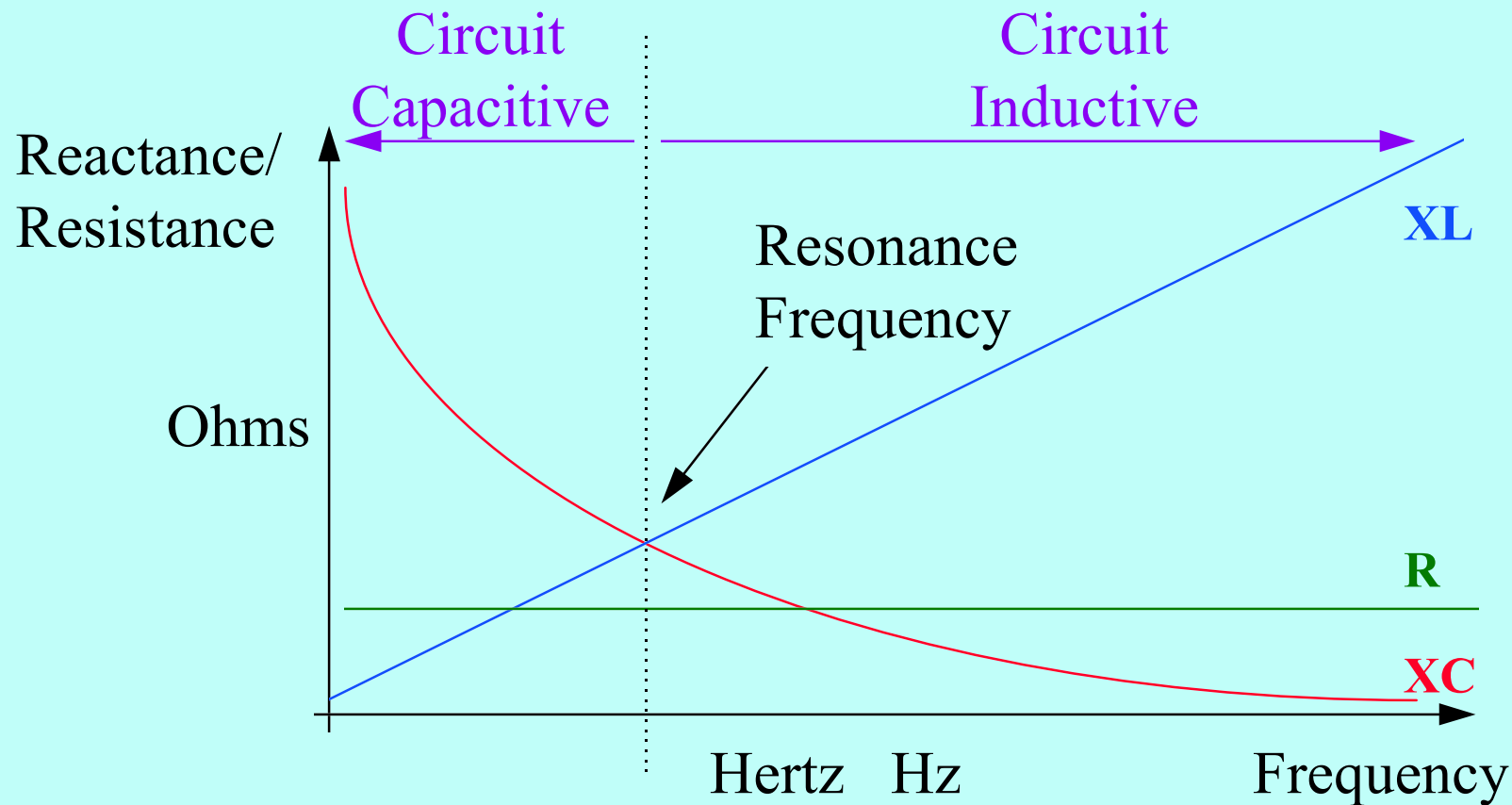- Relationship between R, L and C to Frequency.
- Note: at a frequency $X_L = X_C$ (Resonance)



AC Theory.

- RLC circuits.
- At resonance both X_L and X_C are equal therefore we can calculate the resonant frequency from the component values :-
- Resonant frequency F_0 can be calculated from
- $X_C = 1/2\pi FC = X_L = 2\pi FL$ or
- $(2\pi F)(2\pi F) = 1/LC = (2\pi)^2 * F^2$
- $F^2 = 1 / (2\pi)^2 * LC$
- $F = \sqrt{1 / (2\pi)^2 * LC} = 1 / 2\pi\sqrt{LC}$
- Resonant Frequency = $F_0 = 1 / 2\pi\sqrt{LC}$



AC Theory.

- RLC circuits.
- At resonance both X_L and X_C are equal and opposite therefore depending on the circuit configuration the reactances will either cancel or re-enforce each other.
- Series resonant circuits appear as **Low Impedance**.
- Parallel circuits appear as **High Impedance**.
- A Parallel resonant circuit present an impedance greater than that of either X_C or X_L and is called the Dynamic Impedance Z_0 .
- Z_0 **Dynamic impedance** is calculated by $Z_0 = L/RC$ where R is the DC resistance of the inductor.

AC Theory.

- Relationship between Series RLC and Frequency.
- Note: effect when $X_L = X_C$ (Resonance)

Impedance

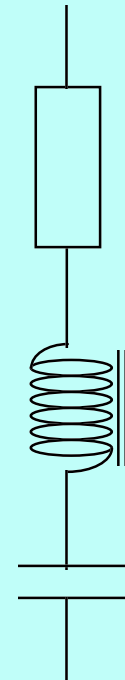
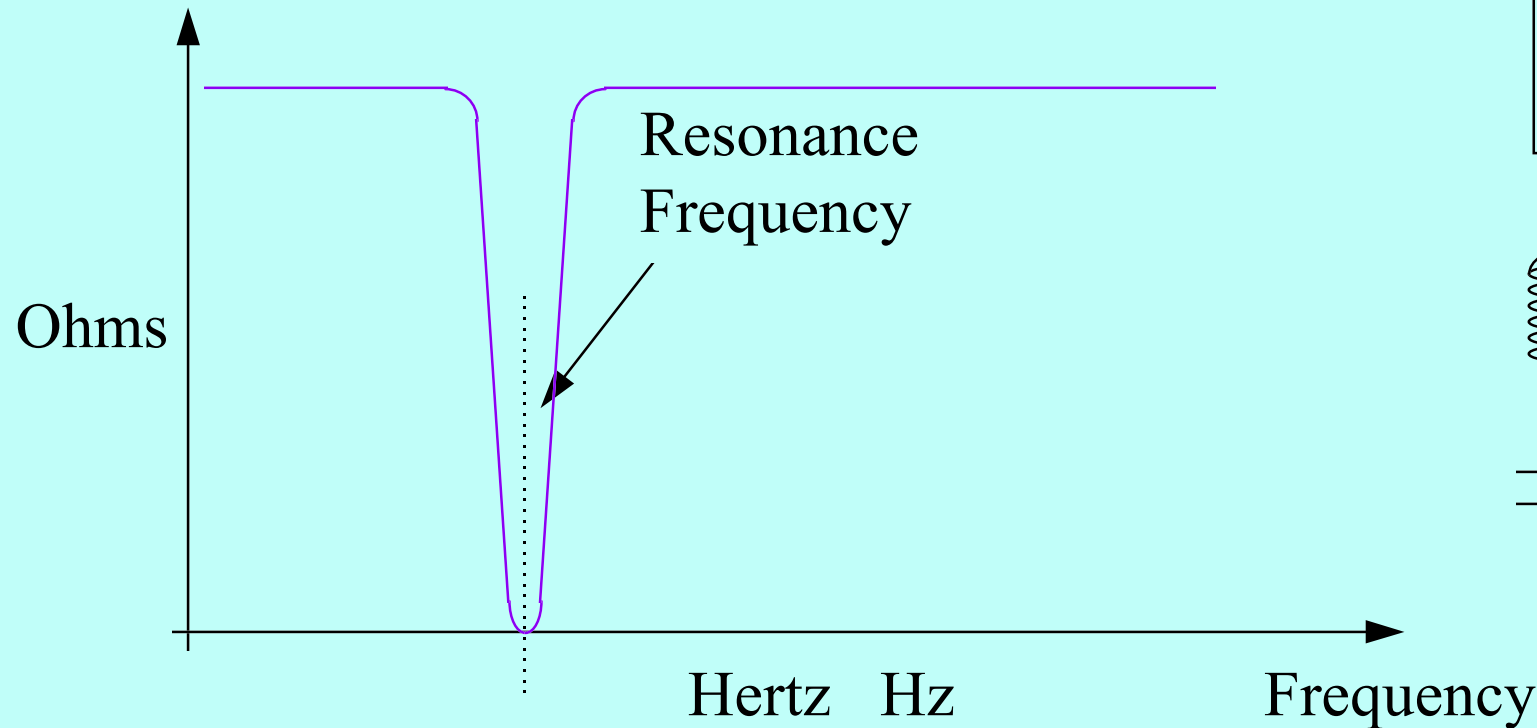


AC Theory.

- Relationship between Parallel RLC and Frequency.
- Note: effect when $X_L = X_C$ (Resonance)

Impedance

Ohms

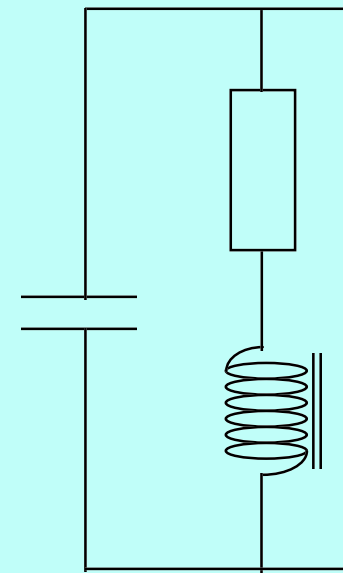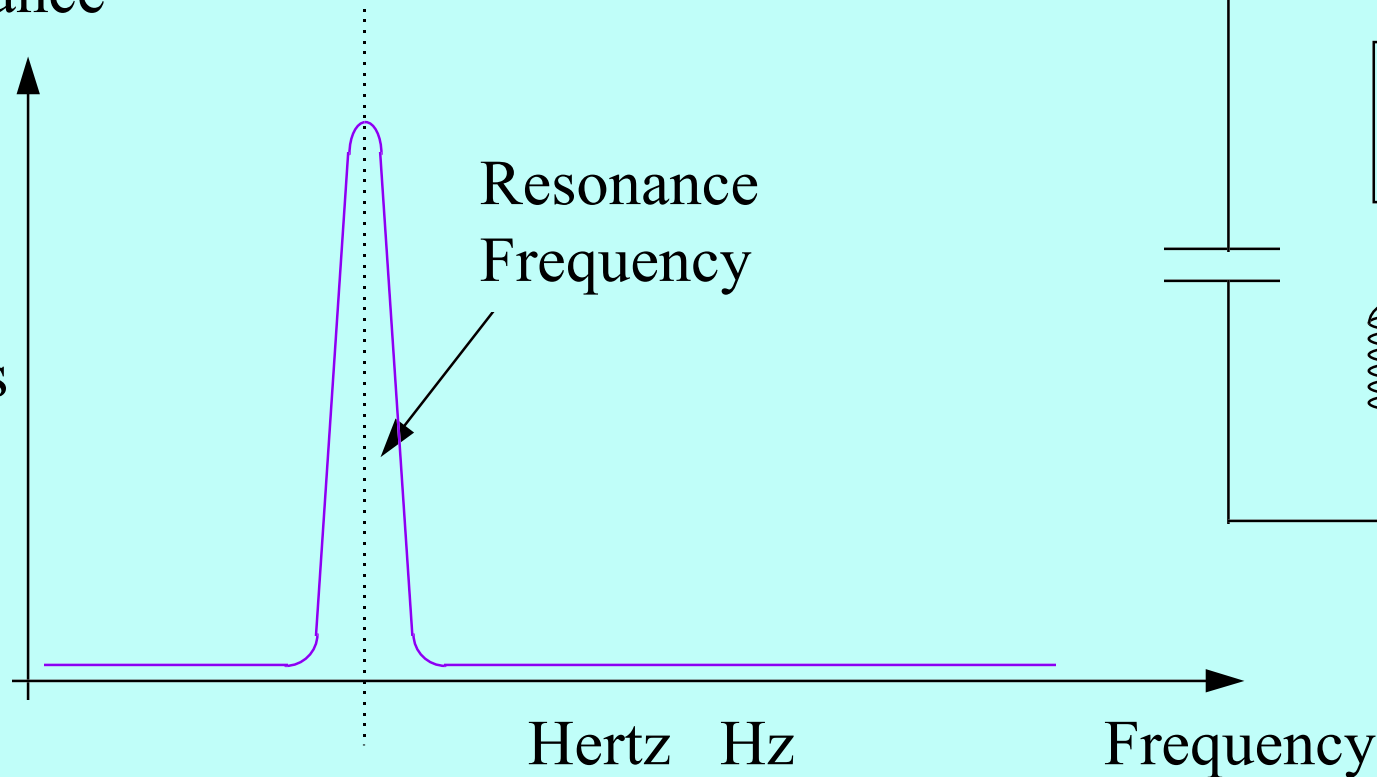


AC Theory.

- Bandwidth of RLC circuits.
- At resonance the RLC circuit will allow a range of frequencies to pass or block around the center frequency f_0 . This range is called the **Bandwidth**.
- The Bandwidth is measured at 70.7% voltage or current output point, (-3db) or half power point
- Bandwidth **$BW = R/2\pi L$ or f_0/Q**
- Quality factor or **Q** is calculated from
- $Q = XL/R$
- A high Q indicates a smaller bandwidth a low Q indicated a larger bandwidth.

AC Theory.

- Bandwidth of a tuned circuit.
- Bandwidth $BW = f_2 - f_1$ or calculated by $R/2\pi L$

Current or
Voltage

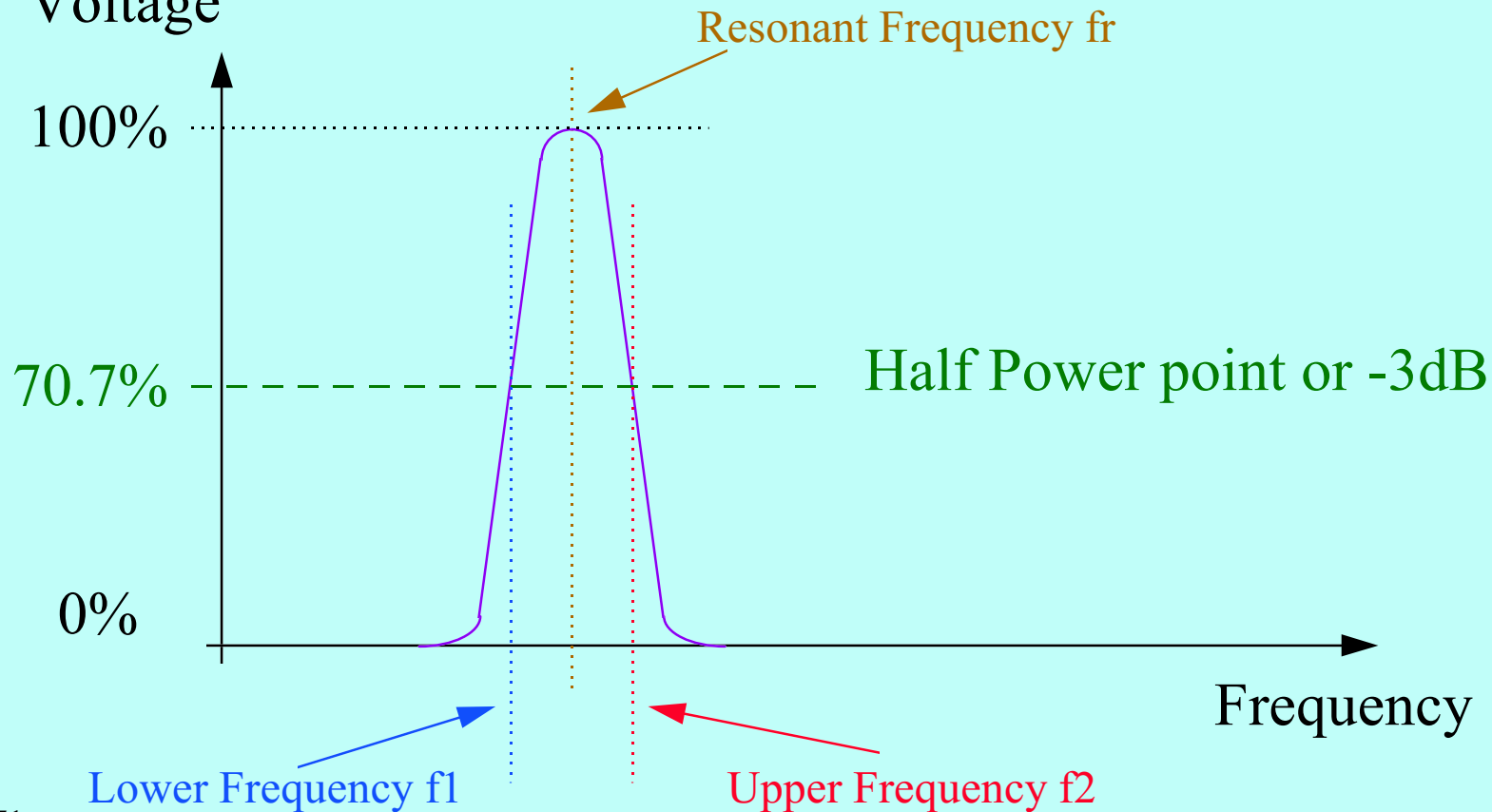

The Decibel

The Decibel.

- Power Gain can be calculated from :-
 - Power Gain = Power Out / Power in
- If we wish to calculate the gain of a system with many sub-modules (some Amplifying {making the signal bigger} and some Attenuating {making the signal smaller}) the process becomes rather tedious because each individual module's Output is calculated by multiplying its Input by its Gain.
- However if we convert the Gain of each module to a logarithmic form (x^n) then the overall Gain of any system can be calculated by just adding the powers of each of the individual Gains.

The Decibel.

- Relationships:-
- Power Gain is calculated from :-
 - Power Gain = (Power Out / Power in)
- Power Gain in Bels is calculated from :-
 - Power Gain = \log_{10} (Power Out / Power in)
- Power Gain in decibels is calculated from :-
 - Power Gain = $10 \log_{10}$ (Power Out / Power in)
- Why use Base 10 Logs? Because our hearing has a Base 10 relationship with respect to sound levels.

The Decibel.

- Gain in decibels (using Current Ratios) =
 - $10 \log_{10} ((I^2_{out} * R_{out}) / (I^2_{in} * R_{in}))$
 - $10 [\log_{10} ((I^2_{out} / I^2_{in}) * (R_{out} / R_{in}))]$
 - $10 [\log_{10} (I^2_{out} / I^2_{in}) + \log_{10} (R_{out} / R_{in})]$
 - $10 [2 \log_{10} (I_{out} / I_{in}) + \log_{10} (R_{out} / R_{in})]$
 - Only if $R_{out} = R_{in}$ then
 - $10 [2 \log_{10} (I_{out} / I_{in}) + \log_{10} 1]$
 - however; note that $\log_{10} 1 = 0$ so
 - Gain = $10 [2 \log_{10} (I_{out} / I_{in})]$
 - or the more common re-written form :-
 - Gain = $20 \log_{10} (I_{out} / I_{in})$

The Decibel.

- Gain in decibels (using Voltage Ratios) =
 - $10 \log_{10} \left(\frac{V^2_{\text{out}} / R_{\text{out}}}{V^2_{\text{in}} / R_{\text{in}}} \right)$
 - $10 \log_{10} \left(\frac{V^2_{\text{out}}}{R_{\text{out}}} * \frac{R_{\text{in}}}{V^2_{\text{in}}} \right)$
 - $10 \left[\log_{10} \left(\frac{V^2_{\text{out}}}{V^2_{\text{in}}} * \frac{R_{\text{in}}}{R_{\text{out}}} \right) \right]$
 - $10 \left[\log_{10} \left(\frac{V^2_{\text{out}}}{V^2_{\text{in}}} \right) + \log_{10} \left(\frac{R_{\text{in}}}{R_{\text{out}}} \right) \right]$
 - $10 \left[2 \log_{10} \left(\frac{V_{\text{out}}}{V_{\text{in}}} \right) + \log_{10} \left(\frac{R_{\text{in}}}{R_{\text{out}}} \right) \right]$
 - Only if $R_{\text{out}} = R_{\text{in}}$ then (Remember $\log_{10} 1=0$)
 - $10 \left[2 \log_{10} \left(\frac{V_{\text{out}}}{V_{\text{in}}} \right) + \log_{10} 1 \right]$
 - Gain = $10 \left[2 \log_{10} \left(\frac{V_{\text{out}}}{V_{\text{in}}} \right) \right]$
 - or the more common re-written form :-
 - Gain = $20 \log_{10} \left(\frac{V_{\text{out}}}{V_{\text{in}}} \right)$

The Decibel.

- The decibel is a ratio and not suitable for specifying an Output unless it is referenced to some defined Input.
- An amplifier with an Output of 30dB means little unless you know what the input is.

$$\text{Output} = *1000$$

- Common Used References :-
 - dBm Output referenced to 1mW
 - dBW Output referenced to 1W
 - dB μ V Output referenced to 1 μ V

Noise

What is Noise?

Noise.

- An unwanted component in an Output signal.
- Sources of Noise
 - Internal (Generated within the equipment itself)
 - External (generated by an External source)
- Types of Noise
 - Thermal Agitation Noise
 - Interference and Crosstalk
 - Semiconductor Noise
 - Shot Noise
 - Partition Noise
 - 1/f noise or Flicker Noise

What is Noise?

Noise.

- Thermal Agitation Noise
 - As temperature rises above -273°C some electrons in the outer shells of the atoms gain sufficient energy to leave their orbits. These electrons drift randomly around the material. If a number of electrons all move in the same direction at the same time then a noise current is developed.
 - r.m.s noise $V_n = \sqrt{4kTBR}$ where :-
 - k = Boltzmann's constant = $1.38 * 10^{-23}$ J/K
 - T = Absolute temperature of conductor
 - B = Bandwidth and R = Resistance in Ohms

What is Noise?

Noise.

- Thermal Agitation Noise

– r.m.s noise $V_n = \sqrt{4kTBR}$ where :-

- k = Boltzmann's constant = $1.38 * 10^{-23}$ J/K
- T = Absolute temperature of conductor
- B = Bandwidth and R = Resistance in Ohms

- Calculate noise voltage produced in a resistance of $68K\Omega$ in a 10MHz bandwidth, temperature = 22°C

What is Noise?

Noise.

- Thermal Agitation Noise

– r.m.s noise $V_n = \sqrt{4kTBR}$ where :-

- k = Boltzmann's constant = $1.38 * 10^{-23}$ J/K
- T = Absolute temperature of conductor
- B = Bandwidth and R = Resistance in Ohms

- Calculate noise voltage produced in a resistance of $68K\Omega$ in a 10MHz bandwidth, temperature = 22°C

- $V_n = \sqrt{4 * (1.38 * 10^{-23}) * (273 + 22) * 10^7 * 68 * 10^3}$

- Noise Voltage = $V_n = 105.2289\mu\text{V}$

What is Noise?

Noise.

- Interference

- Can be split into two types :-

- Electromagnetic interference (e.m.i)

- Radio-frequency interference (r.f.i).

- Where :-

- (e.m.i) is usually low frequency, high energy.

- (r.f.i) is usually high frequency, low energy.

- Typical sources of interference are:- anything that causes electrical sparks (motors , switches, domestic appliances, etc.), fluorescent lights and, some types of power supply (switch mode).

What is Noise?

Noise.

- Crosstalk
 - This is caused when signals in one circuit are unintentionally coupled to another circuit due to their close relative physical proximity.
 - For example PCB tracks or wires in a wire loom coupled through capacitance or inductive effect.
 - Crosstalk interference can also be propagated through common power supplies or power supply connections.

What is Noise?

Noise.

- Semiconductor Noise
 - Shot Noise
 - Noise created in a bipolar transistor as charge carriers cross the PN junction
 - Shot noise current = $I_n = \sqrt{2 e I_{dc} B}$
 - where :-
 - e = the charge of a single electron = $1.6 * 10^{-19}$
 - I_{dc} = the d.c current flowing across the junction.
 - B = Bandwidth (Hz) over which the noise is measured.
 - Shot noise is white (all frequencies.)



What is Noise?

Noise.


- Semiconductor Noise
 - Partition Noise
 - Noise created when the current splits after passing through the emitter junction.
 - Note ($I_e = I_b + I_c$)
 - Flicker Noise
 - Noise caused by fluctuations of conductivity of the semiconductor material. This generated noise is inversely proportional to frequency

Switches

Switches.

- A switch is an electrical device that can enable current to flow into a circuit or can break the flow to a circuit.
- They come in different styles:-
- **Push to Make.** 
- This connection needs activation to enable current to flow into the circuit .
- **Push to Break.** 
- This connection needs mechanical action to disable current flow into the circuit.

Switches.

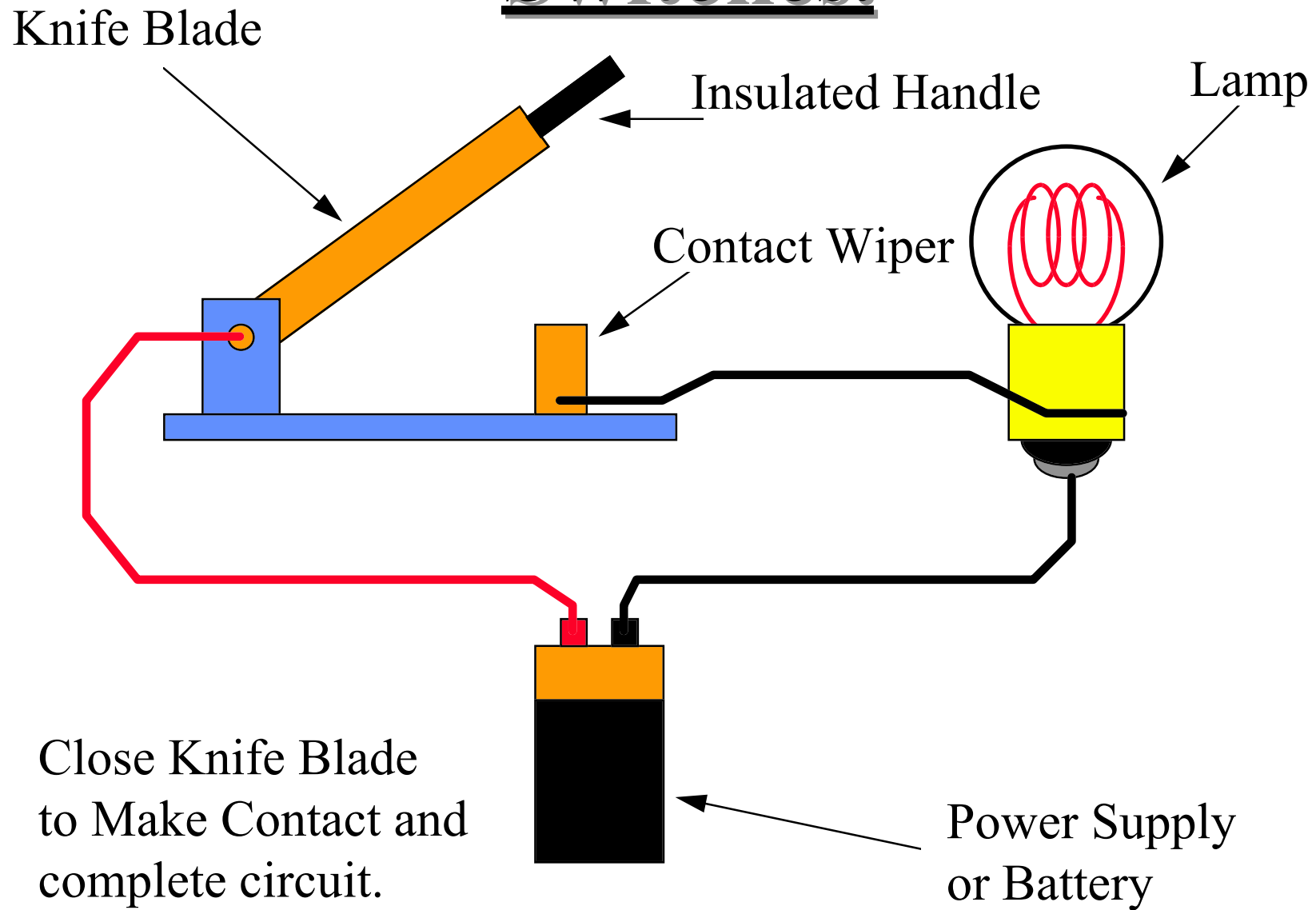

Switches.

Knife Blade


Insulated Handle

Contact Wiper

Knife Blade




Close Knife Blade
to Make Contact and
complete circuit.

End on View of Switch

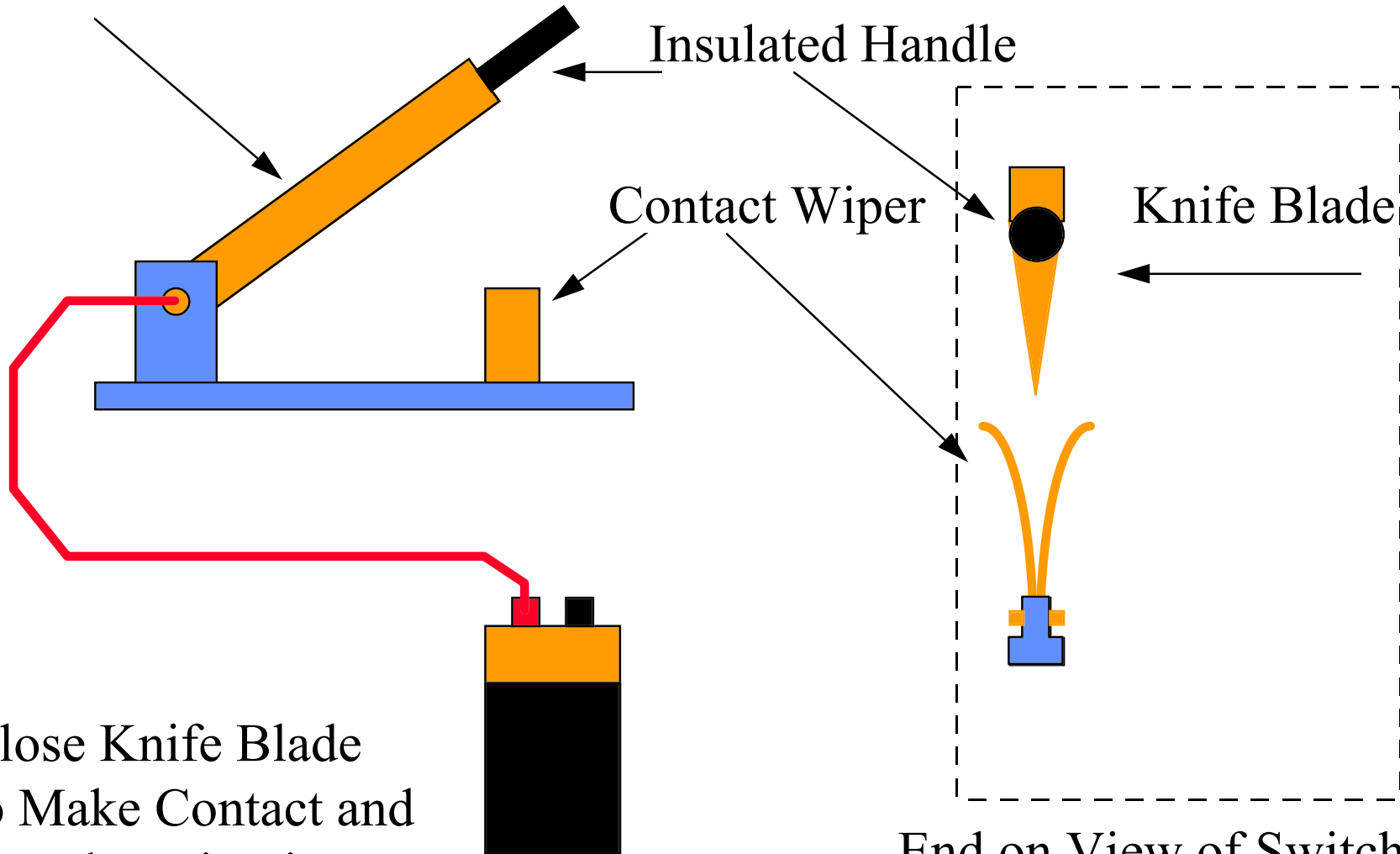

Switches.

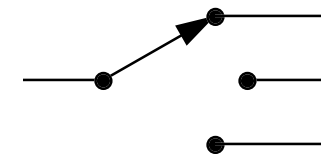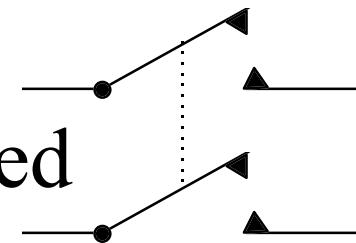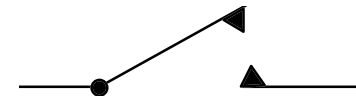- A Switch can also come in different variants.
- Single Pole Single Throw.
- ie one set of connections.
- Double Pole Single Throw.
- Two circuits mechanically connected
- Single Pole Triple Throw.
- ie one connection set with three routing options.




Switches.

- Common codes used:-
- Single Pole Single Throw becomes **SPST**
- Double Pole Single Throw becomes **DPST**
- Single Pole Triple Throw becomes **SPTT**
- It is quite common for the connections of switches to be made up from multiples of twelve i.e. Double Pole Six Way, Triple Pole Four Way, Single Pole Twelve Way.

Switches.


- Other Switching Variants:-
- **Break before Make.**
- This version disconnects a circuit before the next circuit is enabled
- **Make before Break.**
- With this version during the change over period both circuit will be connected for a short period.

Switches.

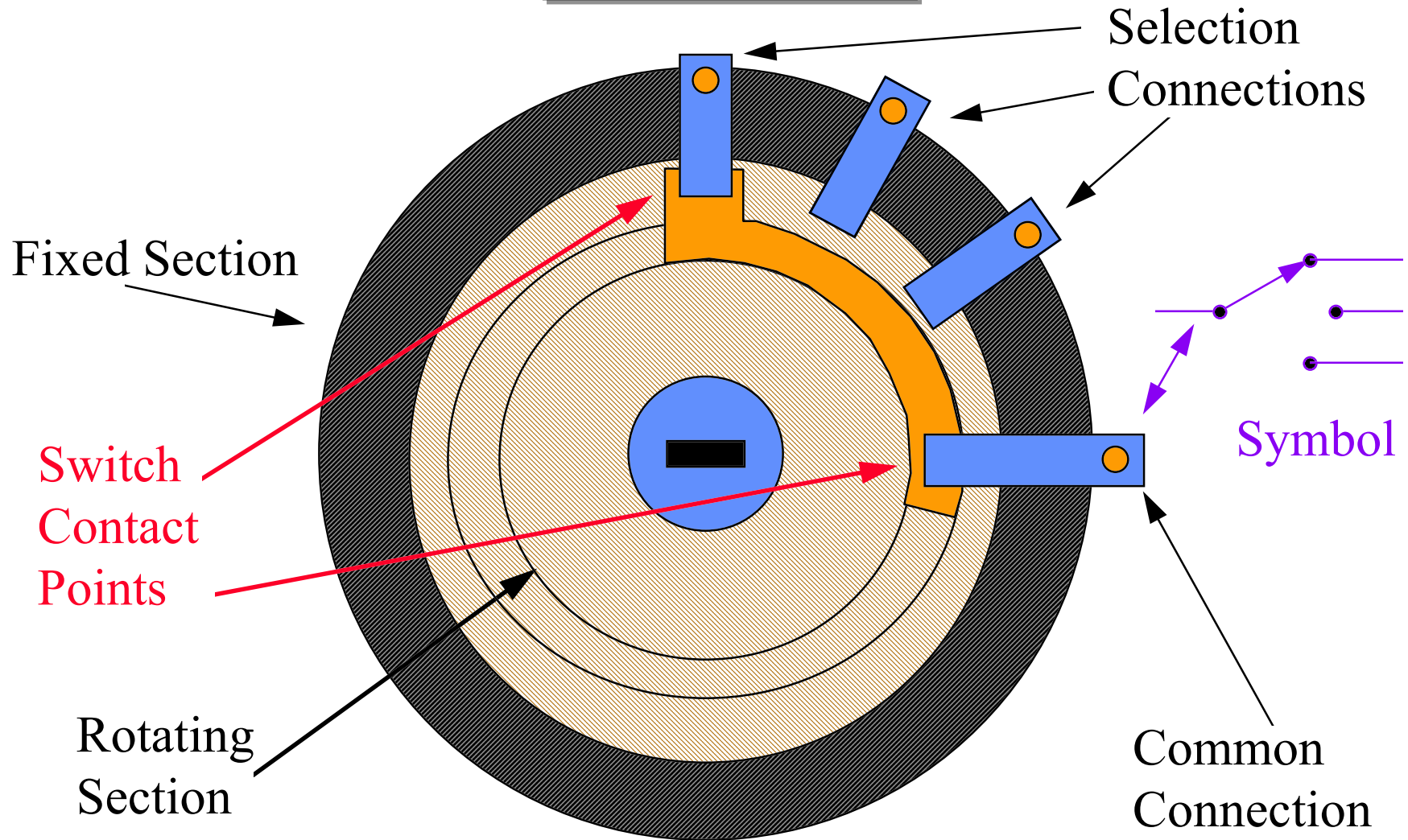

A Basic Wafer Switch Single Pole Three Way (**Break Before Make**)



Switches.

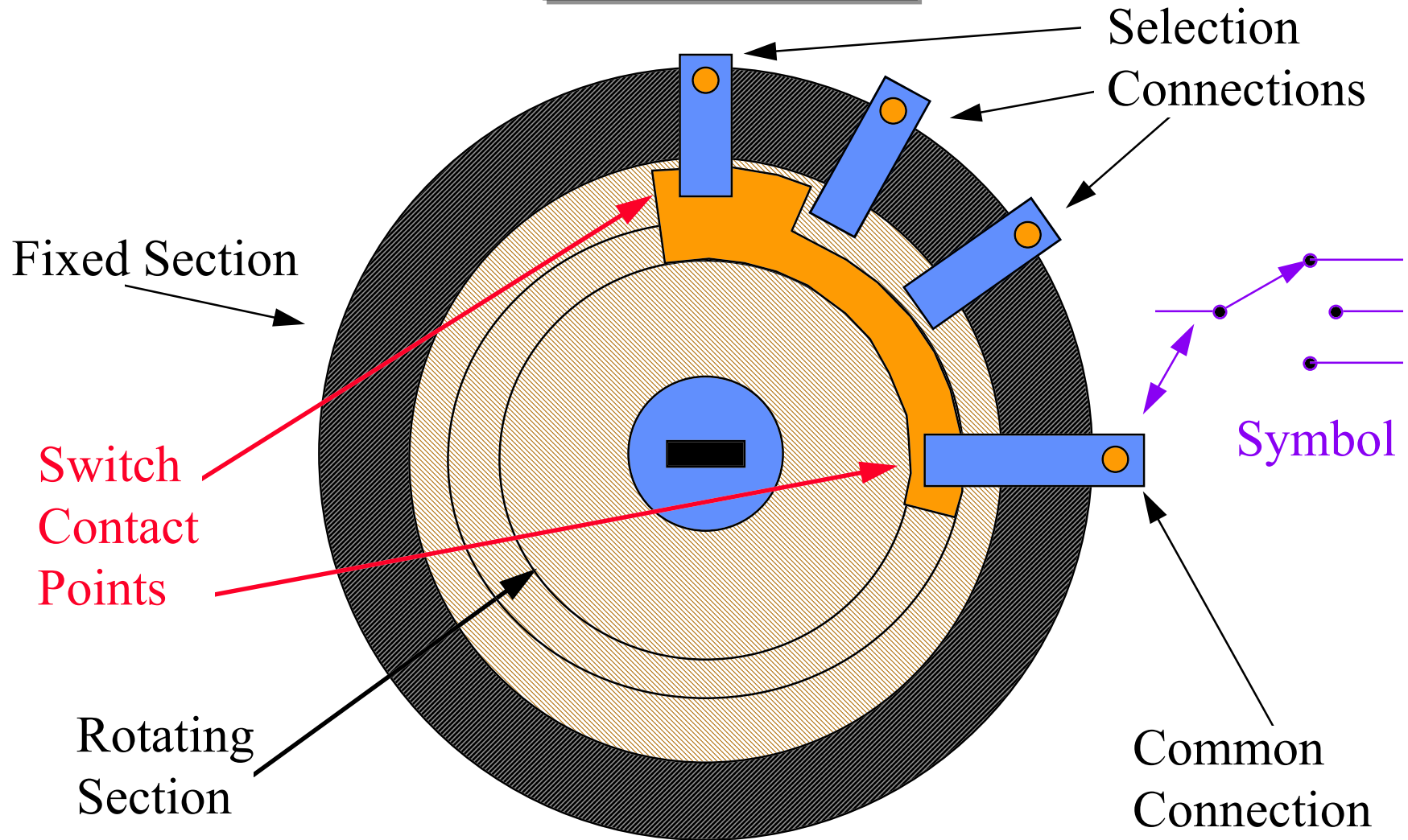



A Basic Wafer Switch Single Pole Three Way (Make Before Break)

Semi- Conductors


Semi-Conductors.

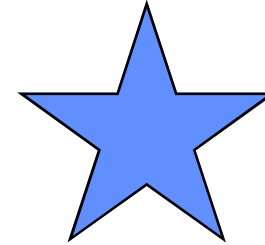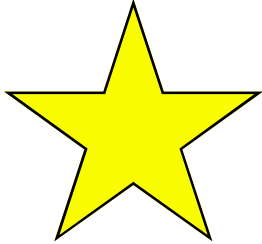

Introduction to Semi-Conductors.

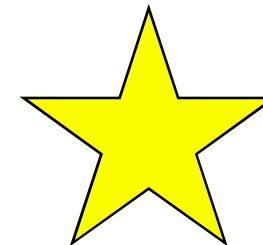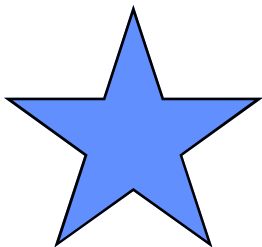


Semi-Conductors.

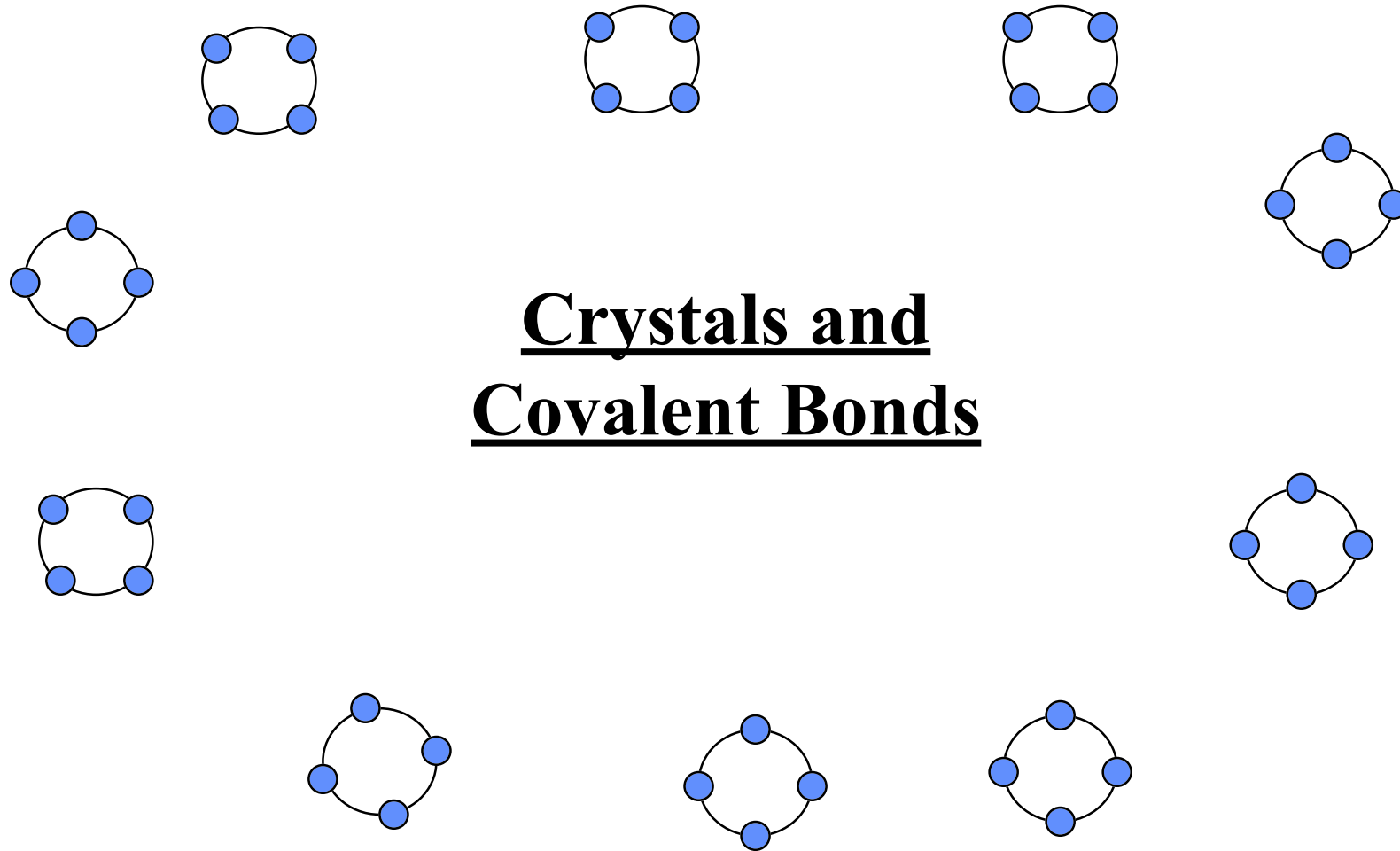


Semi-Conductors.

Covalent Bonds

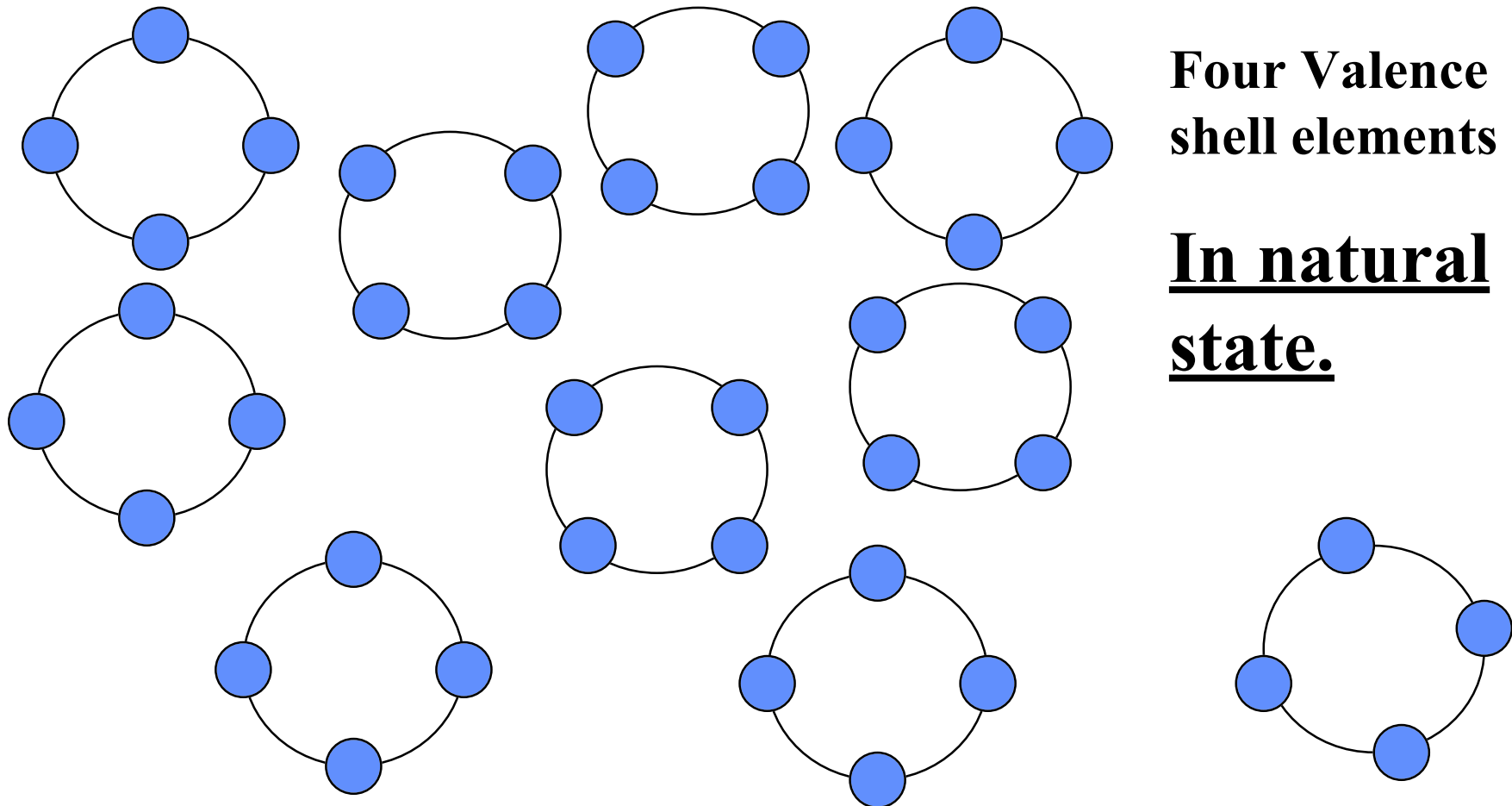

Semi-Conductors.


Covalent Bonds

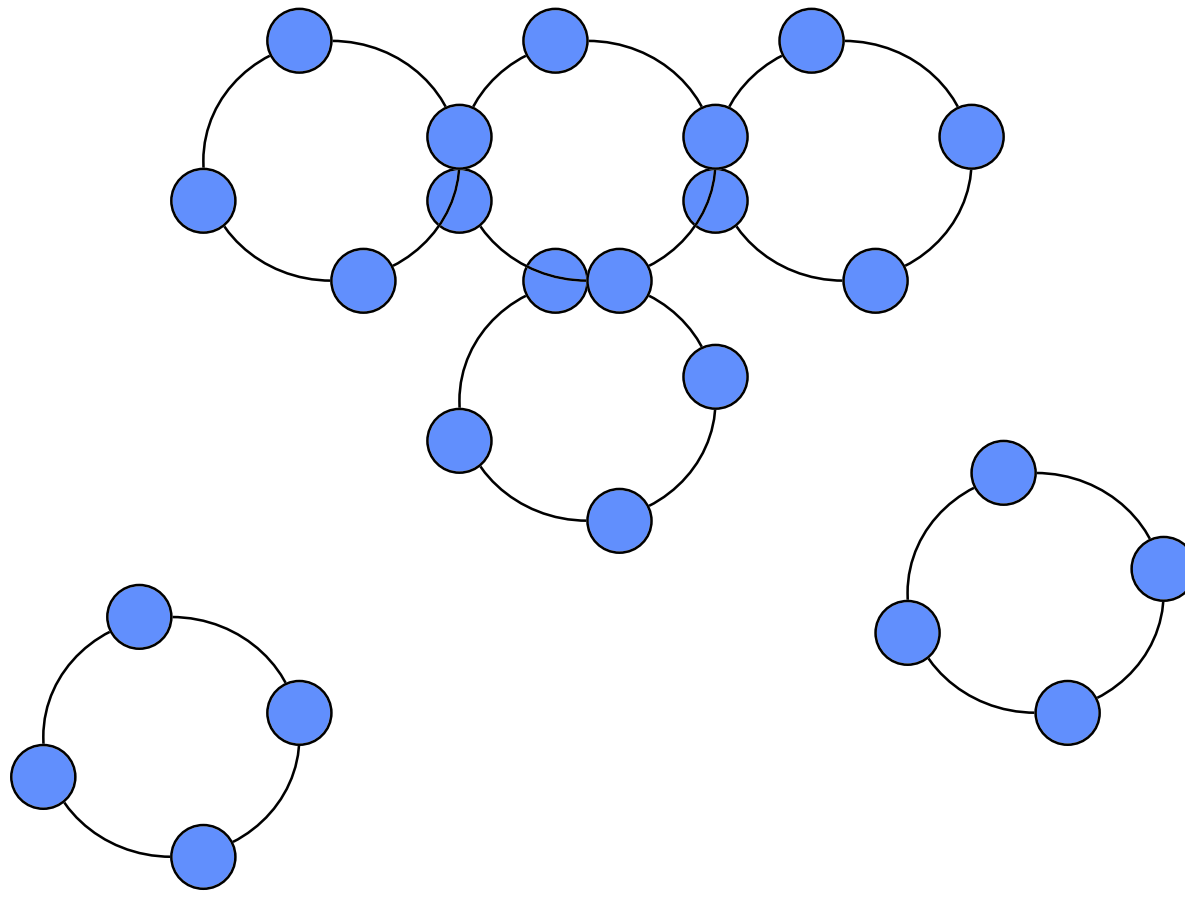

Silicon Si
Germanium Ge
Carbon C


Four Valence
shell elements

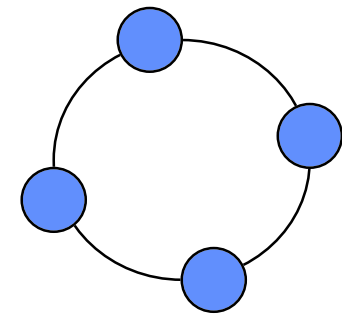Building a
crystal and
sharing valence
electrons




Semi-Conductors.

Covalent Bonds

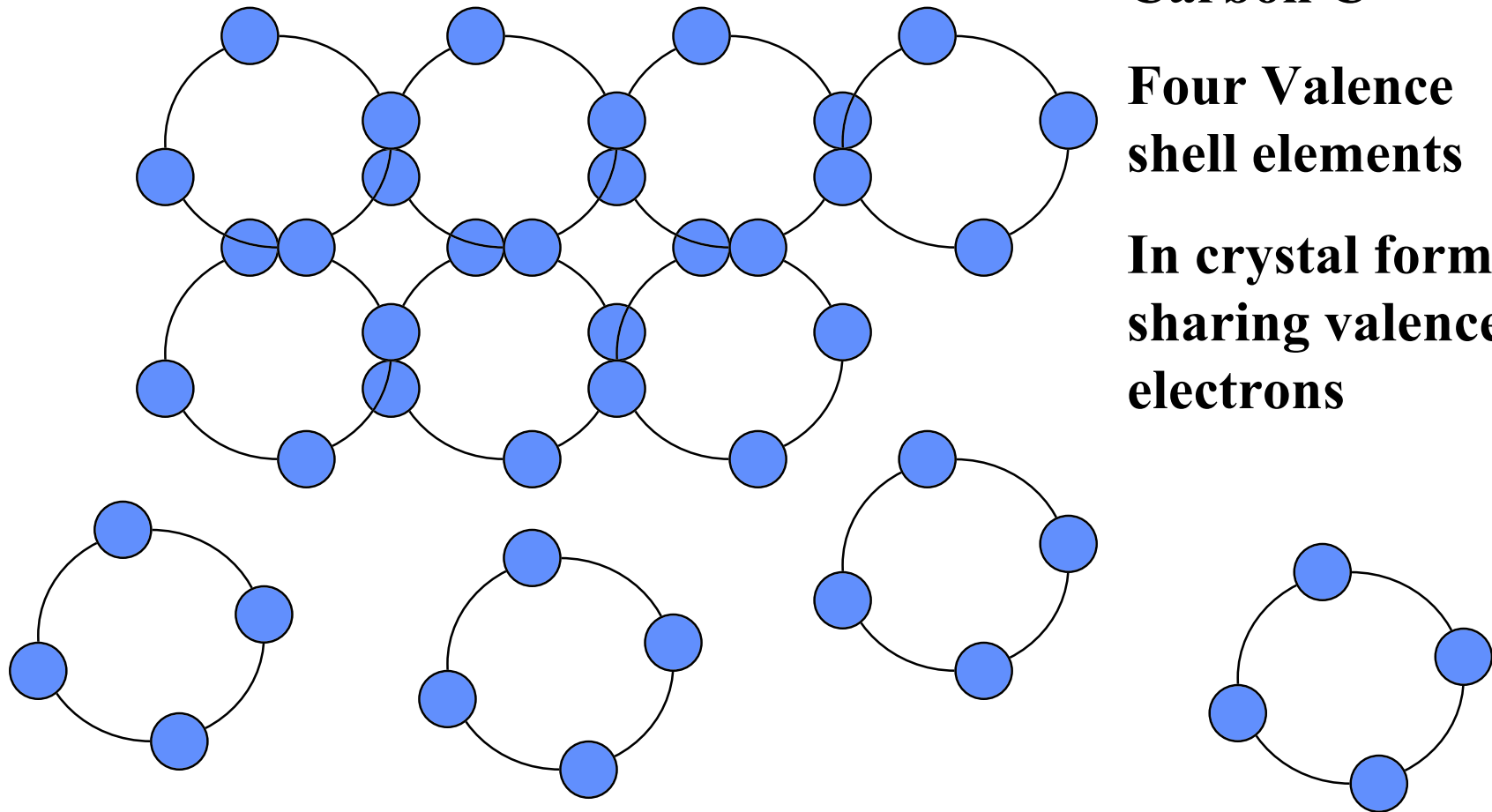

Semi-Conductors.


Covalent Bonds

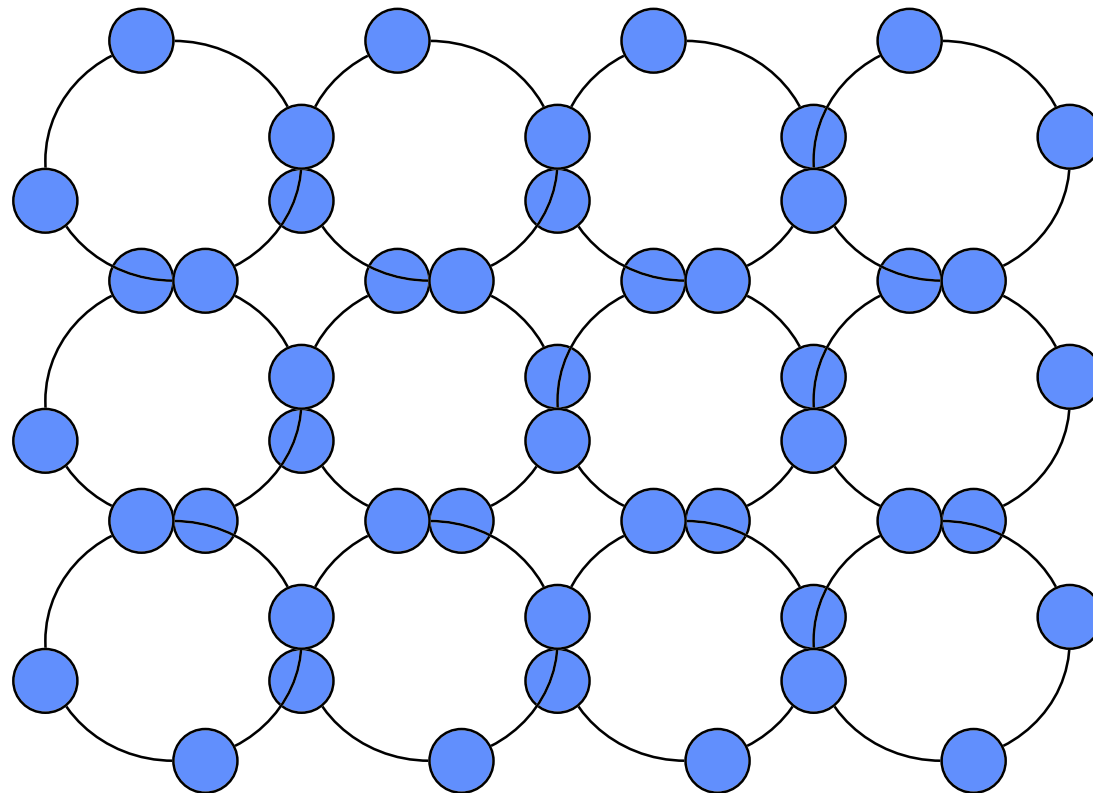

Silicon Si
Germanium Ge
Carbon C

Four Valence
shell elements

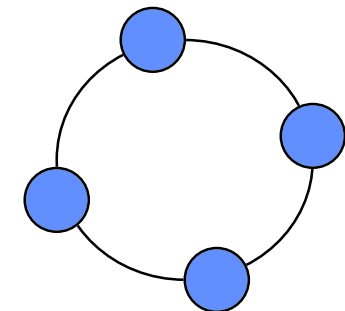
In crystal form
sharing valence
electrons



Note Eight electrons in outer shell . . . type of Insulator.


Semi-Conductors.

Covalent Bonds

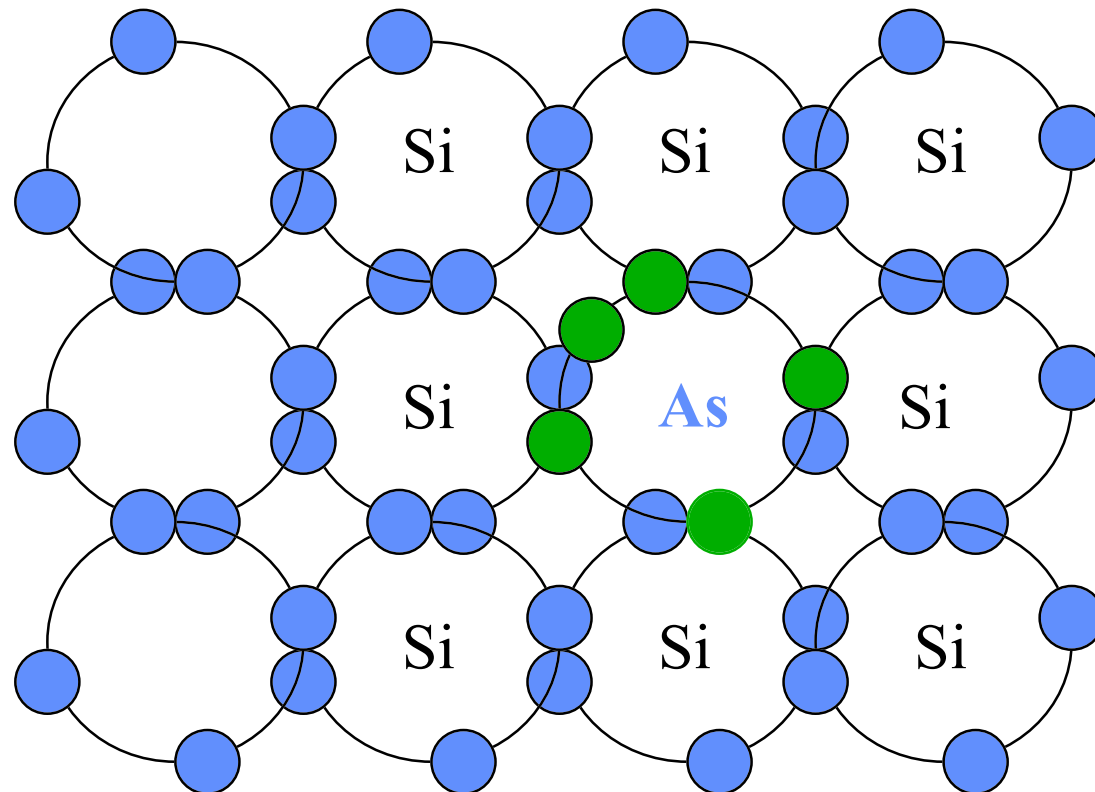

**Doping the
Crystal with a
pentavalent
elements.**


**Arsenic As
Phosphorus P
Antimony Sb**

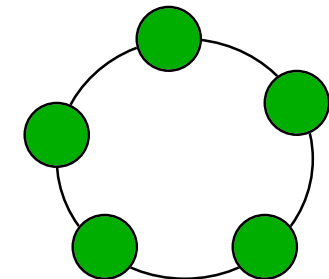

Overall Charge One extra electron more therefore Negative


Semi-Conductors.

Covalent Bonds

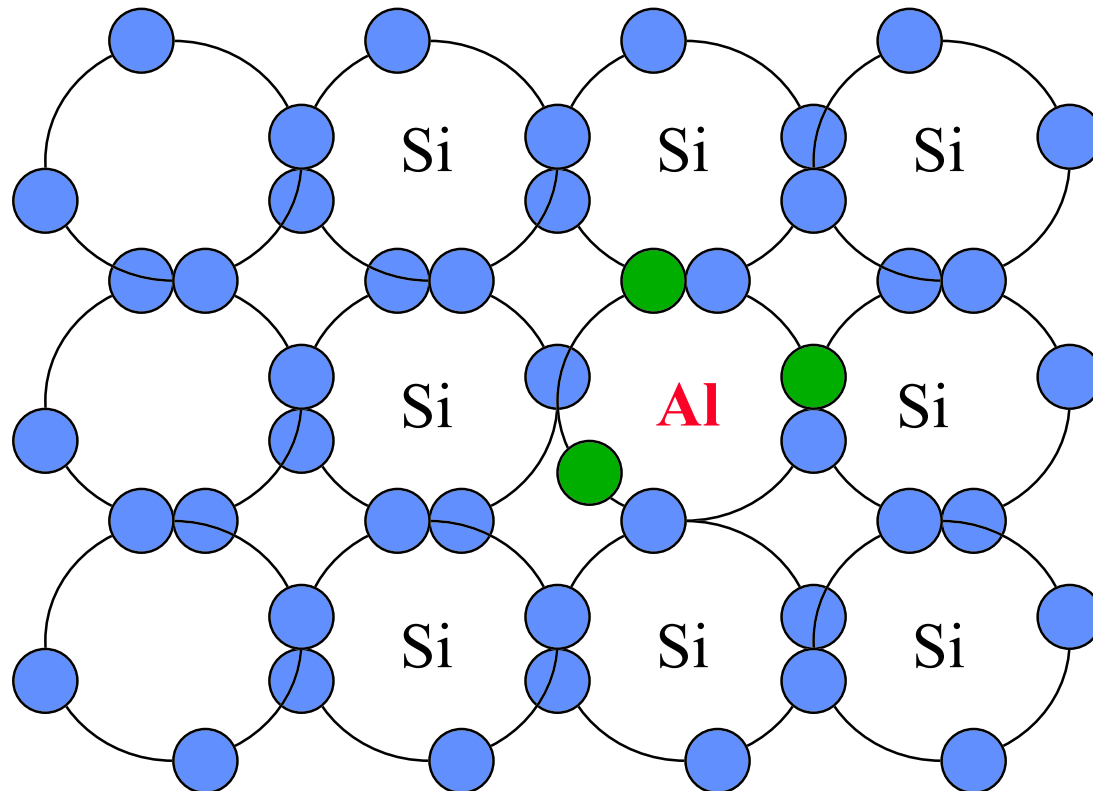

Doping the
Crystal with a
trivalent
elements.

Aluminum Al
Boron B
Gallium Ga

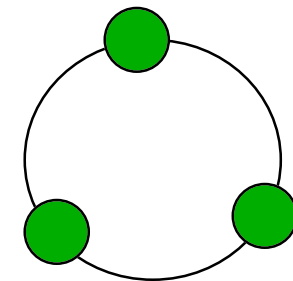

Overall Charge One extra electron less therefore Positive.

Semi-Conductors.

Partial Summary


- Doping can produce two distinct types of Semiconductor.
- One type has an excess of electrons and is called “N” type material. (Why ? .. Because electrons have a (Negative) charge)
- The other type has a shortage of electrons and is called “P” type material. (Positive)
- The electrons in these materials are referred to as the “Majority” Carriers. However

Semi-Conductors.

Covalent Bonds

This part of a Bond Area has one electron less so its overall charge is **Positive**.

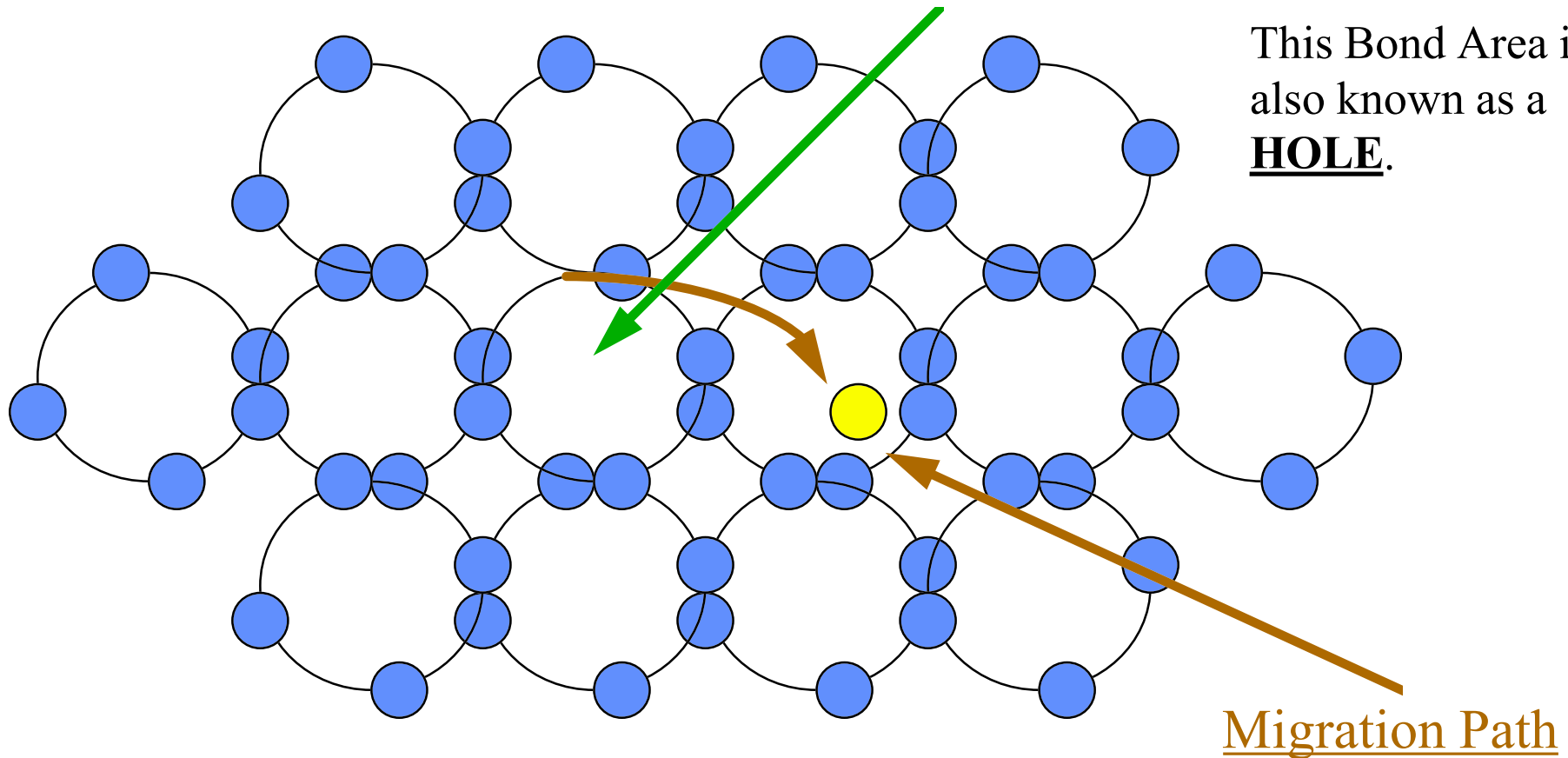This Bond Area is also known as a **HOLE**.




Electron Migration due to Heat (**Minority Carriers**).

Semi-Conductors.

Covalent Bonds

This part of a Bond Area now has one electron more so its overall charge becomes Negative.

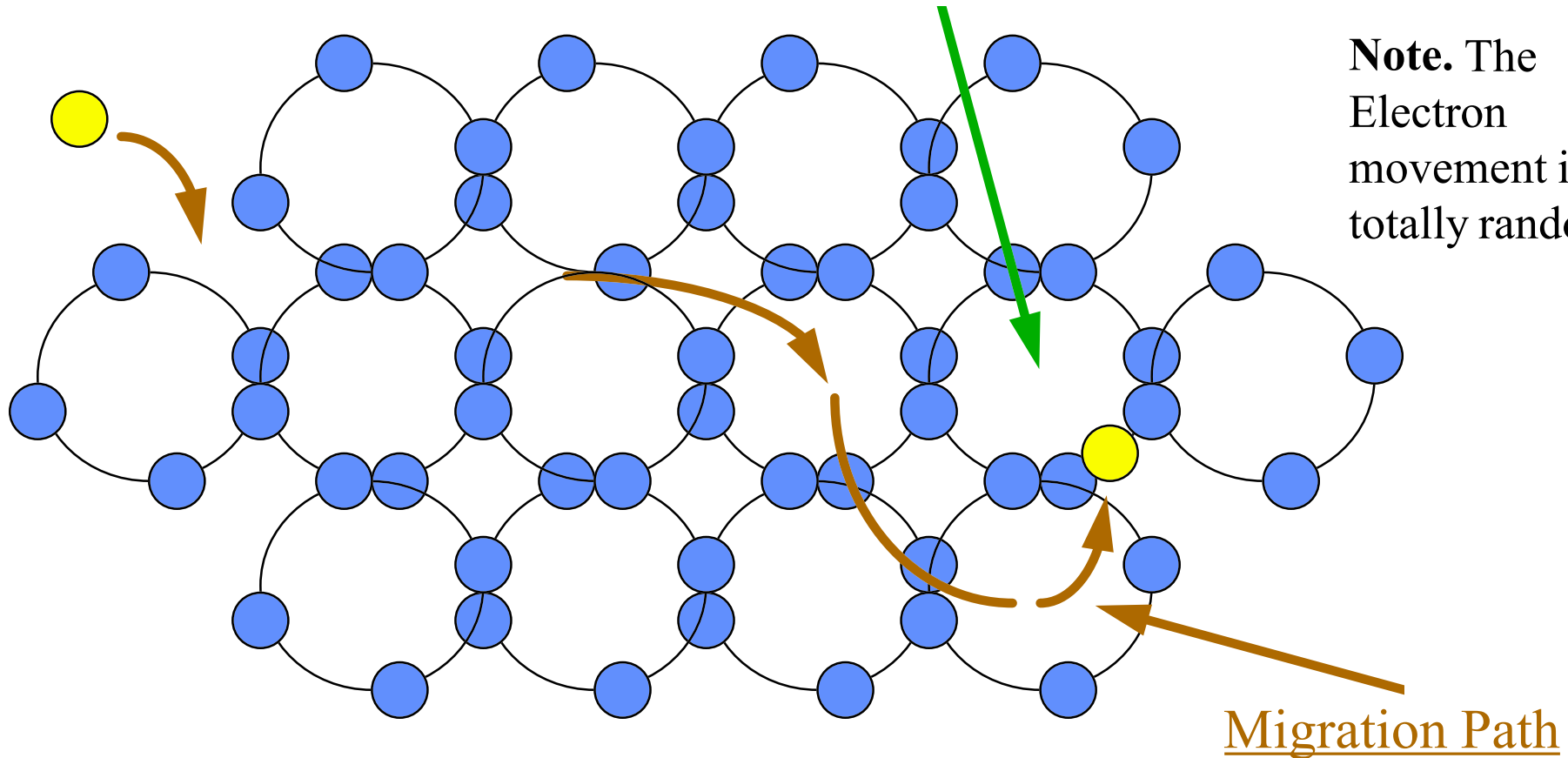Note. The Electron movement is totally random



Electron Migration due to Heat (**Minority Carriers**).

Semi-Conductors.

The Three Semiconductor Material Types

P Type Material

N Type Material

Intrinsic Type Material

The **P** and **N** materials are the MAJORITY carriers of that material, however there will always be a small percentage of MINORITY carriers of the opposite type within the structure caused by movement due to heat etc.


Semi-Conductors.

The PN Junction

P Type Material N Type Material

The majority carriers diffuse across the junction creating a barrier until the potential repels any further diffusion.

This is known as the depletion region.

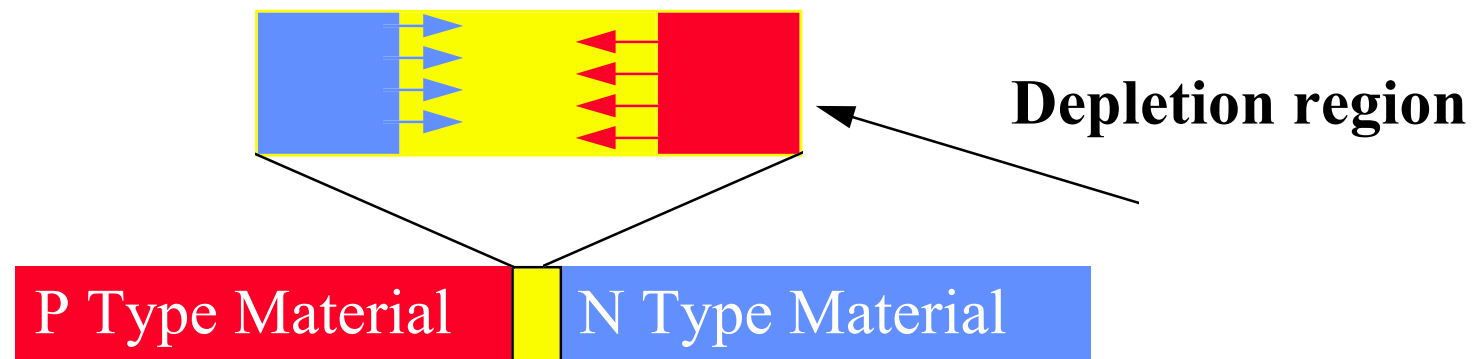

Silicon @25°C is 0.6 to 0.7V , Germanium = 0.3V

Move on to Transistors and Diodes

Transistors and Diodes

Transistors and Diodes.

Junction Diodes


Transistors and Diodes.

The PN Junction review

P Type Material N Type Material


The majority carriers diffuse across the junction creating a barrier until the potential repels any further diffusion.

This is known as the depletion region.

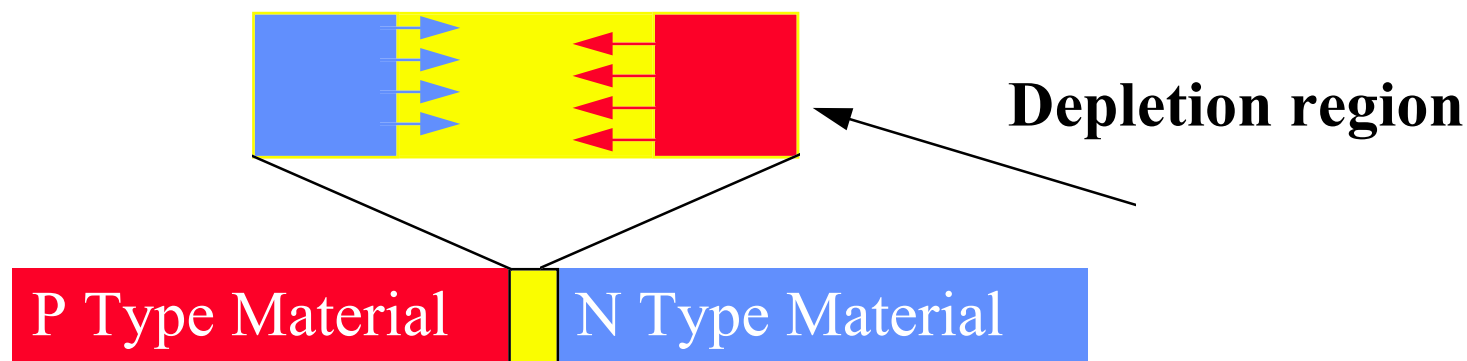

Silicon @25°C is 0.6 to 0.7V , Germanium = 0.3V


Transistors and Diodes.

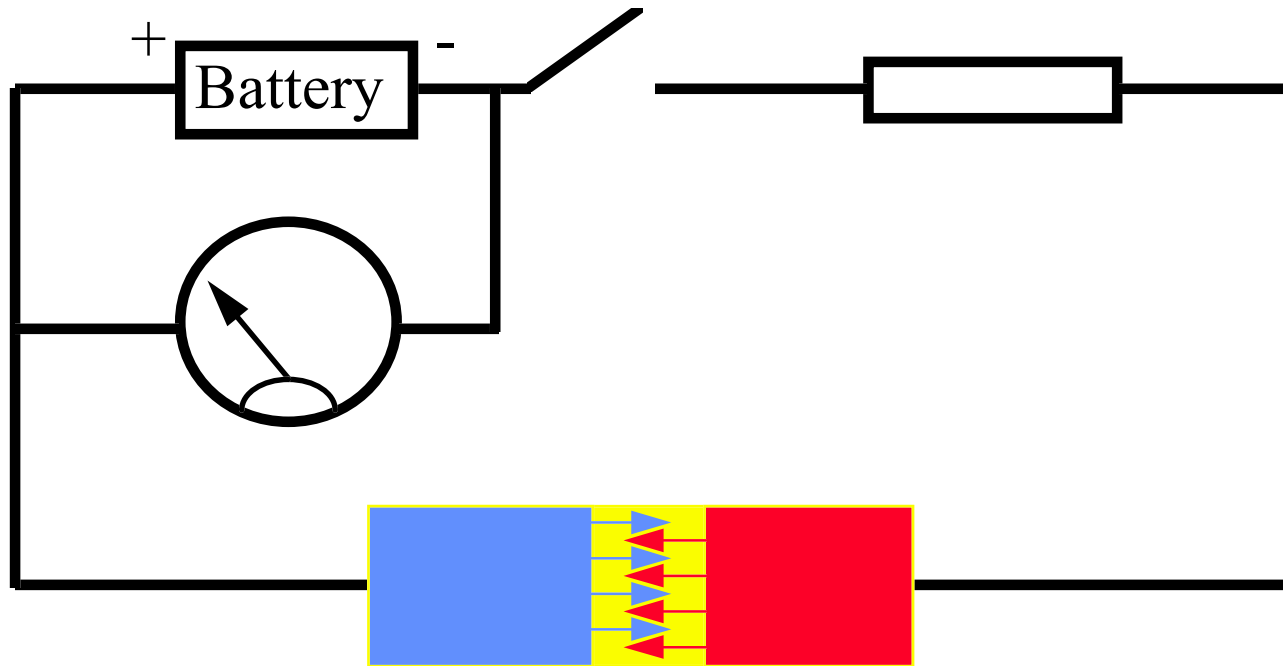

With no applied voltage the depletion barrier will typically be about 0.6 - 0.7 Volts for Silicon. The width is set by the ambient temperature which effects the **Majority Carriers** migration.


594 What happens when a **Reverse Polarity** is applied to a PN junction ?

Transistors and Diodes.

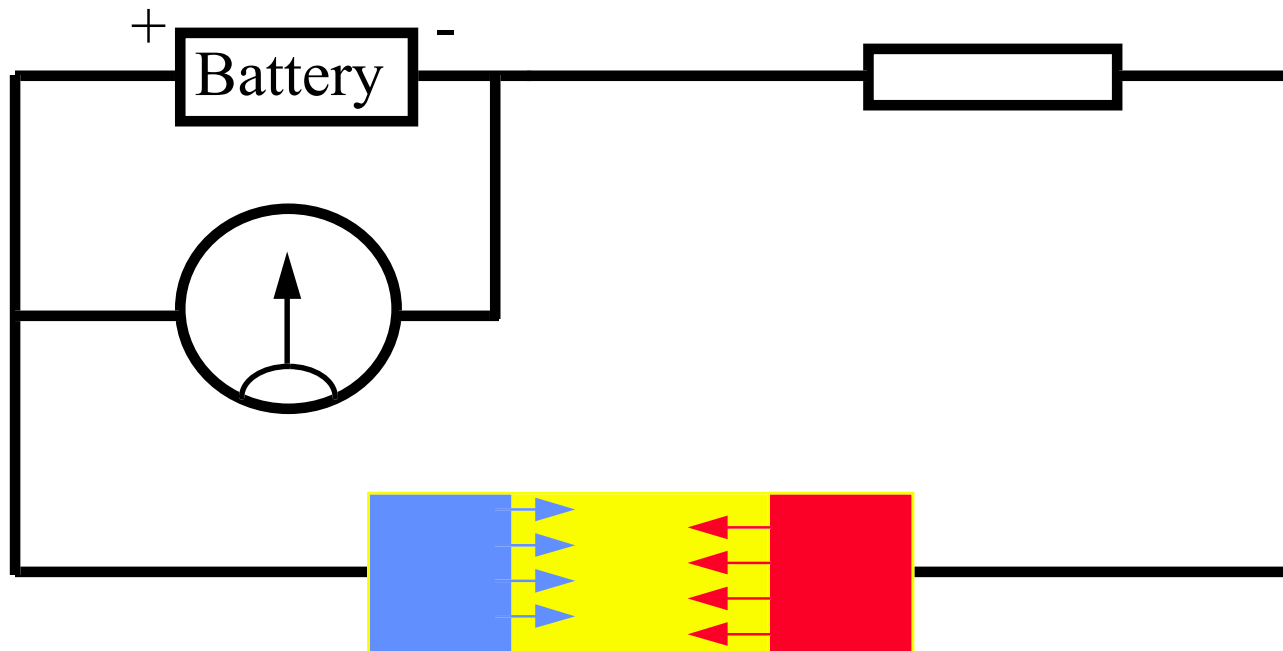


By increasing the **Reverse Polarity** the **Majority** carriers extend the width of the depletion region. This is also known as a **Reversed bias**.

Transistors and Diodes.

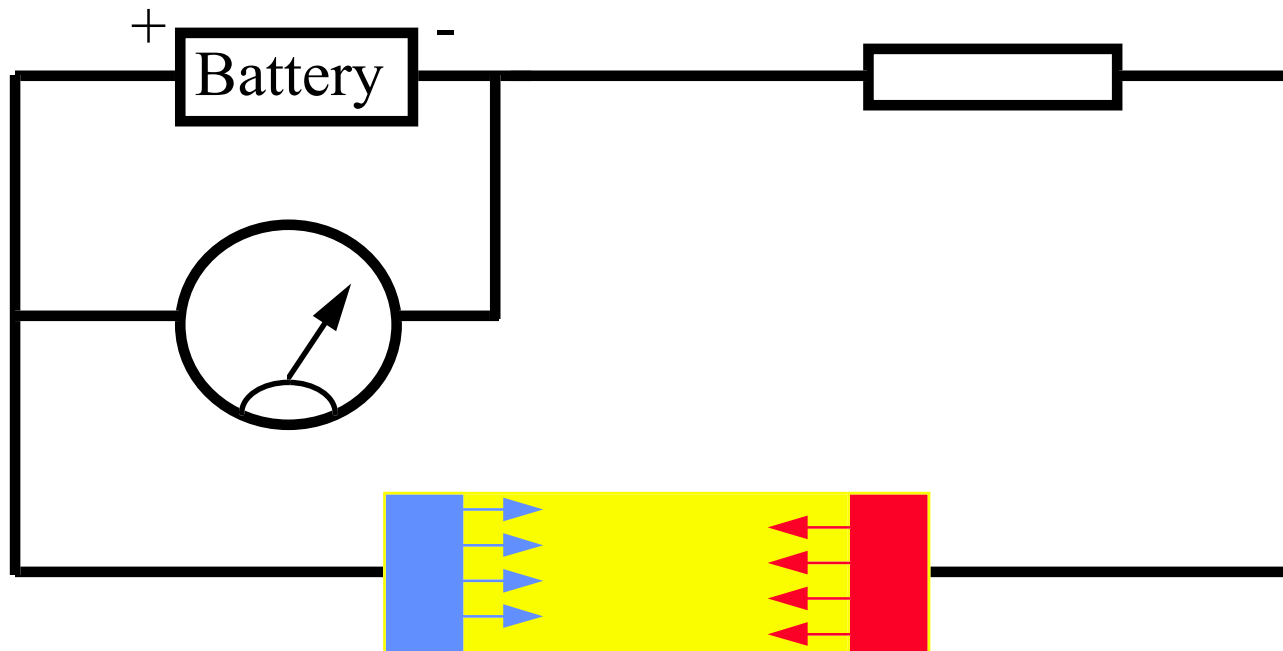


Increasing the **Reverse Polarity** further the **Majority** carriers continue to extend the width of the depletion region. The limit is the Peak Inverse Voltage (PIV) when the device structure breaks down.

Transistors and Diodes.

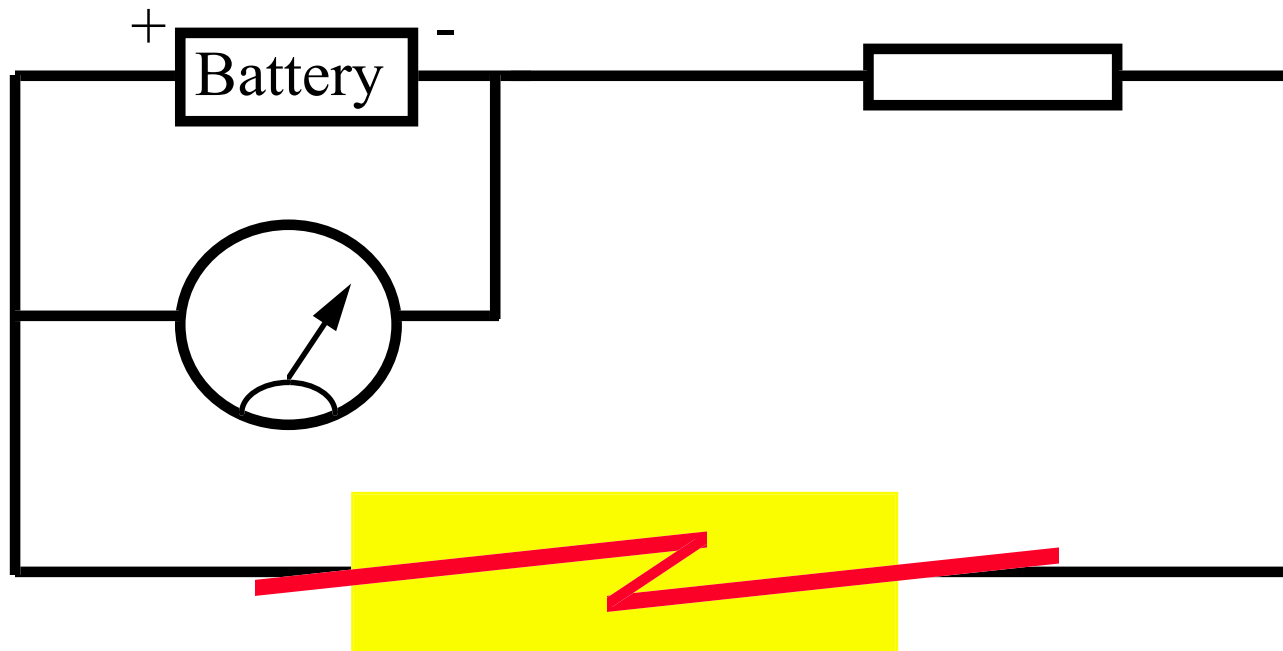


Increasing the **Reverse Polarity** further ($>PIV$) the device structure is destroyed forever (Structure becomes Open or Short Circuit) due to excessive current flowing through the device.

Transistors and Diodes.

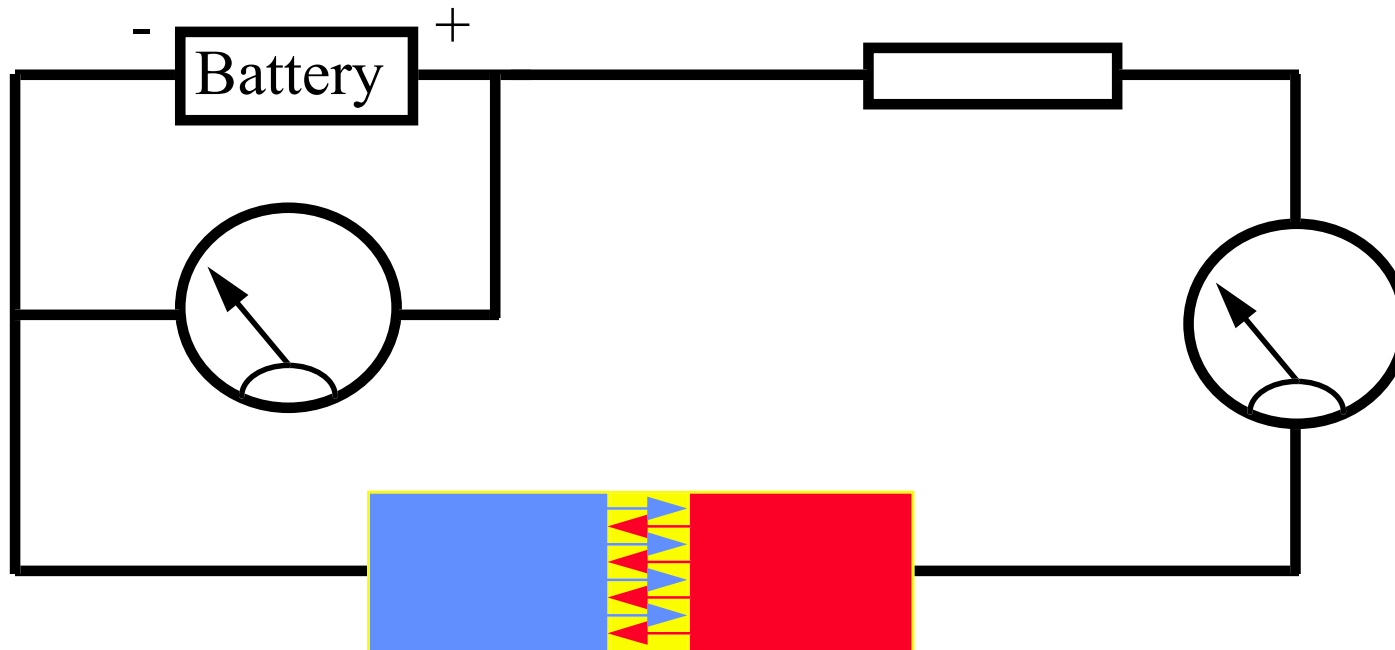


Whilst applied voltage is below the depletion barrier voltage (0.6 - 0.7 Volts for Silicon). The current flow is insignificant however the width of the depletion region will become narrower.

Transistors and Diodes.

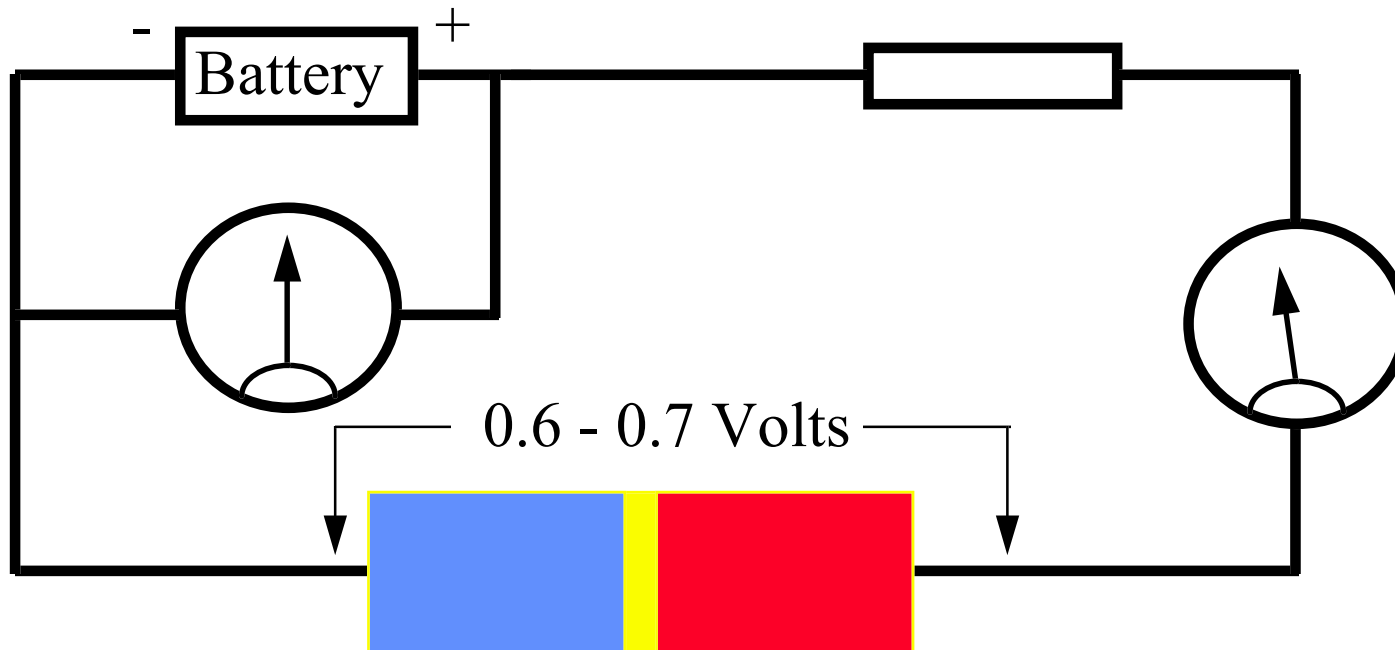

When applied voltage is above the depletion barrier voltage (0.6 - 0.7 Volts for Silicon) current flows. The depletion barrier voltage at this point is now measurable across the device.


Transistors and Diodes.

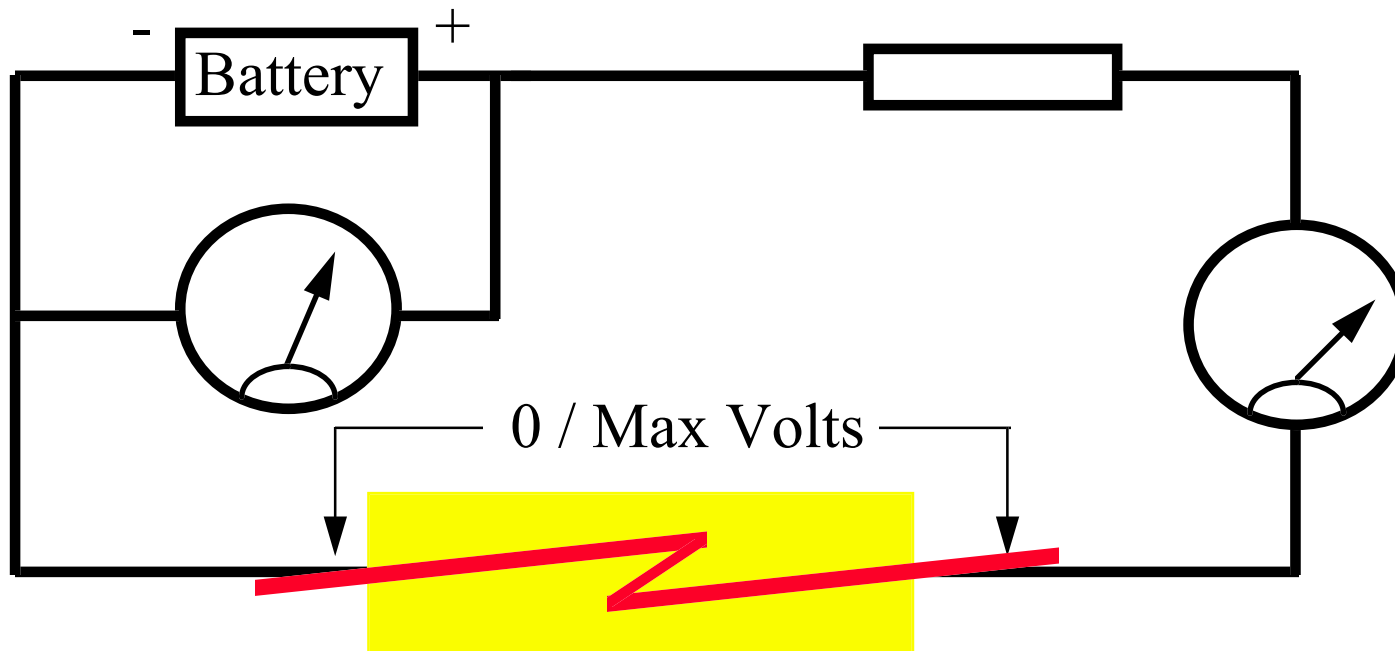


Significantly increasing the **Forward Polarity** can also destroy the device structure (Structure becomes Open or Short Circuit) due to excessive current flowing through the device..

600 The effect when **excessive Forward Polarity** is applied to junction.


Transistors and Diodes.

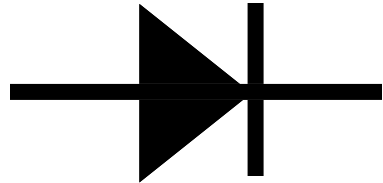


The Symbol for a Diode.

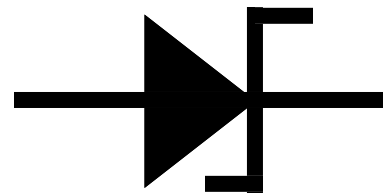

The Symbol for a Zener Diode.

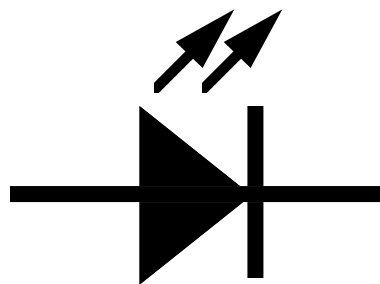

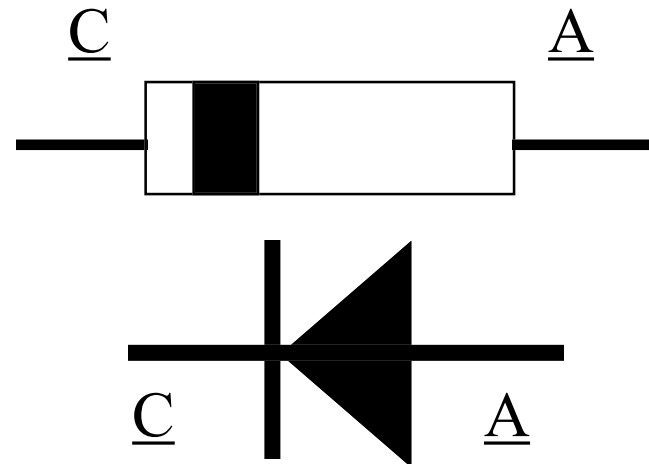
The Symbol for a Light Emitting Diode (LED).



A = Anode the **Positive** + end


C = Cathode the **Negative** -end.

Transistors and Diodes.

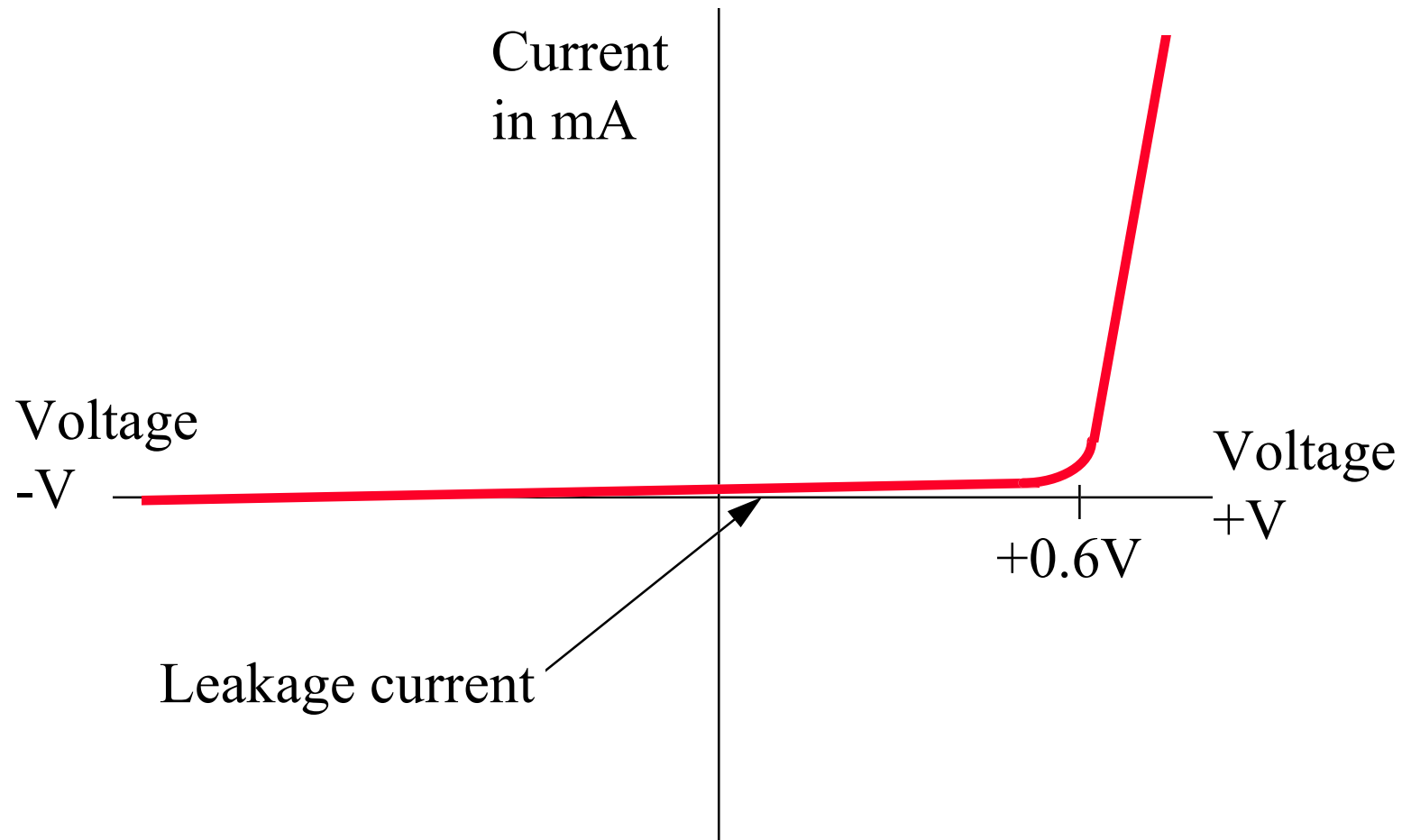


Typical Characteristic of a Silicon Diode

Transistors and Diodes.

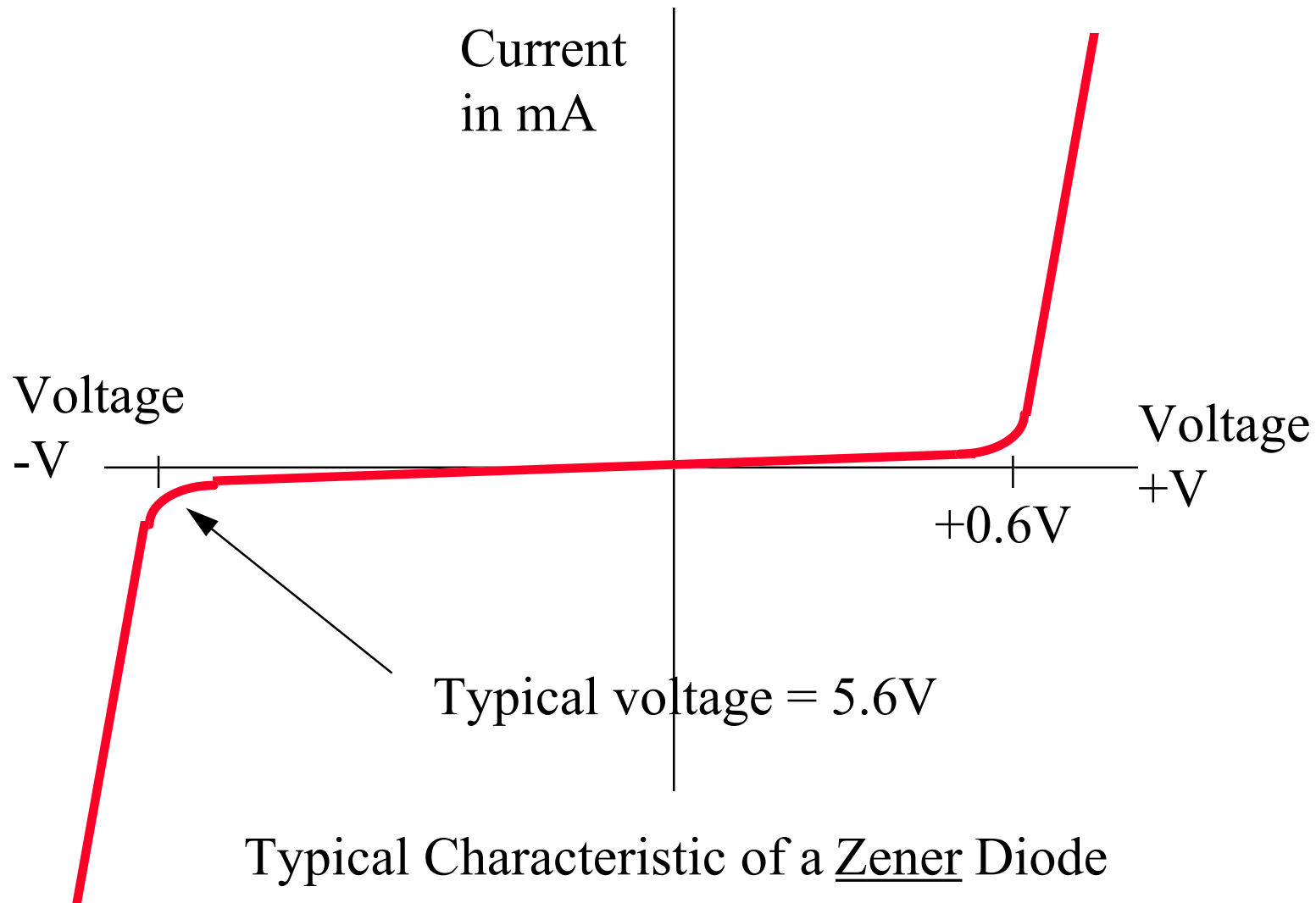

Transistors and Diodes.

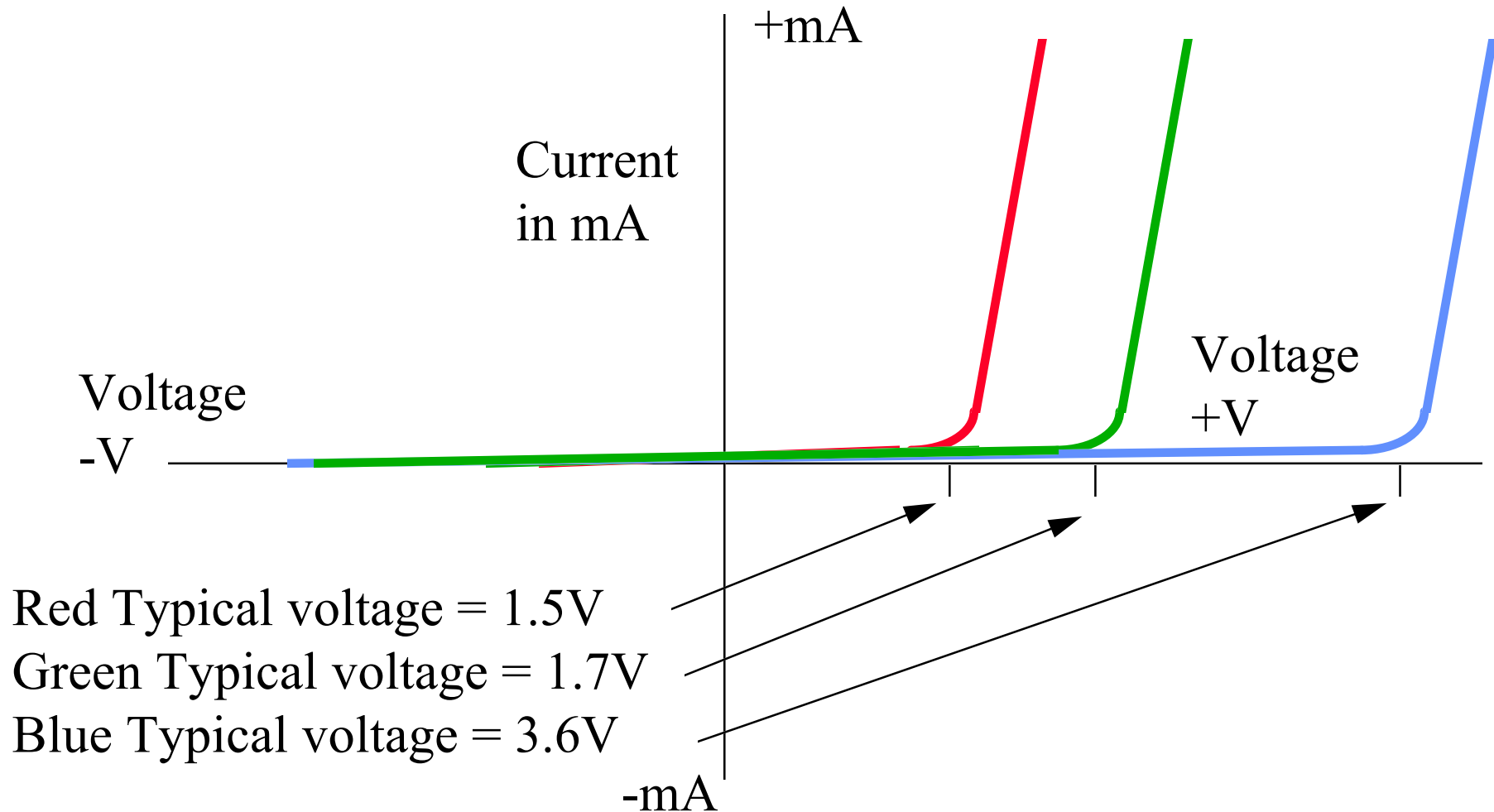

Typical Characteristics of a Light Emitting Diodes

Transistors and Diodes.

Summary



- When a Diode is reversed biased no current will flow.
- If excess Reverse bias is applied to a semiconductor junction the device will breakdown.
- If too much current flows through a junction then the device will be destroyed.

Transistors and Diodes.

Bipolar Junction Transistors


Transistors and Diodes.

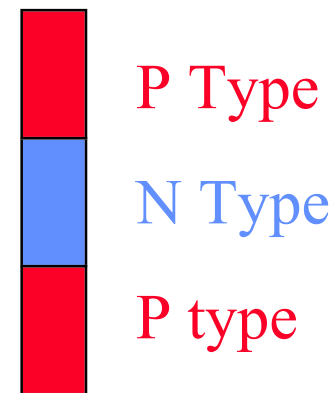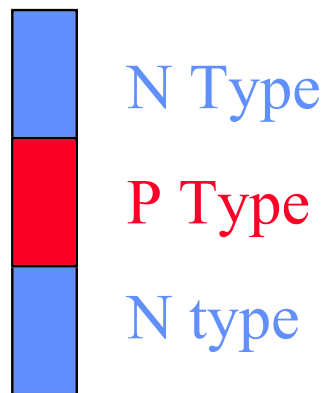- The next development phase was to build three layer semiconductors and this gave the possibility of two variants.
- The variants were identified from their construction i.e. PNP and NPN.




Transistors and Diodes.

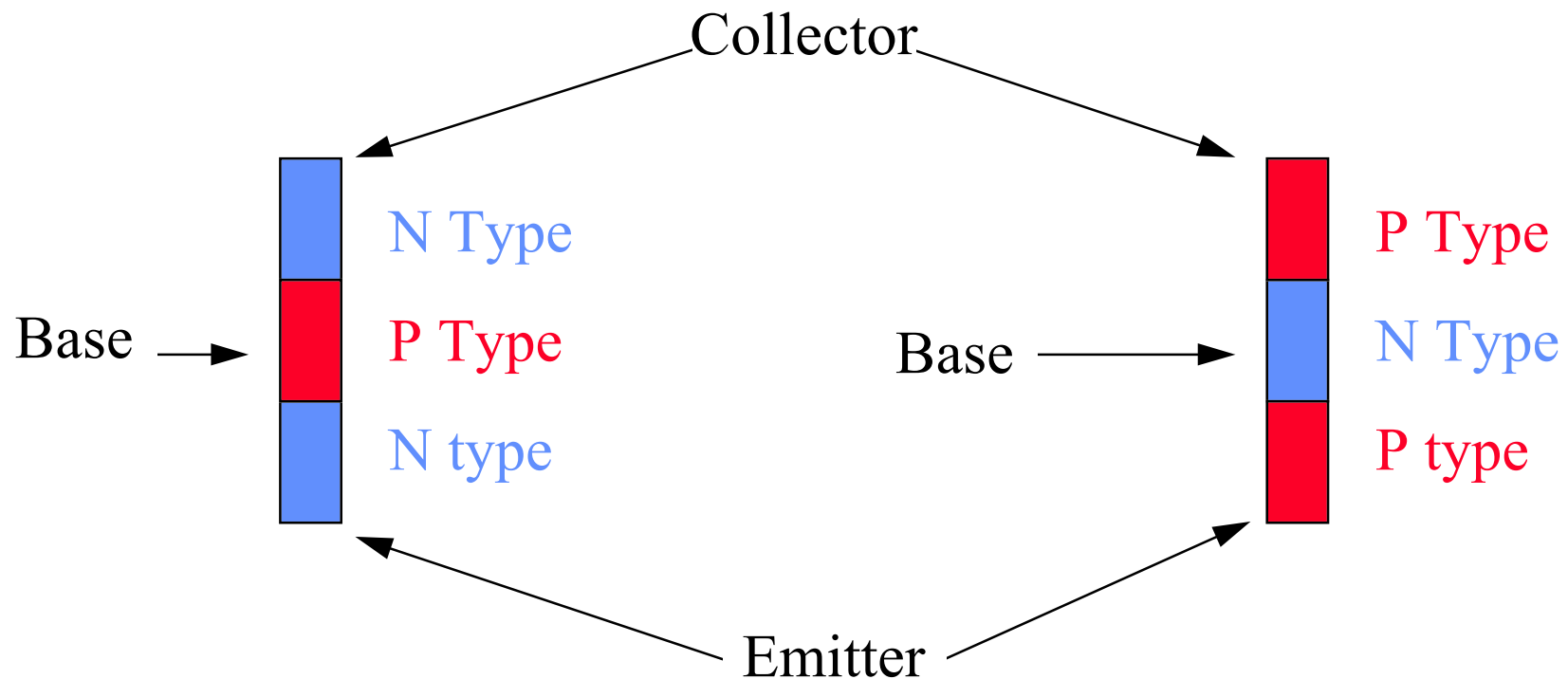- The sections of each construction were also named (based on their function)
i.e. Collector, Base and Emitter.




Transistors and Diodes.

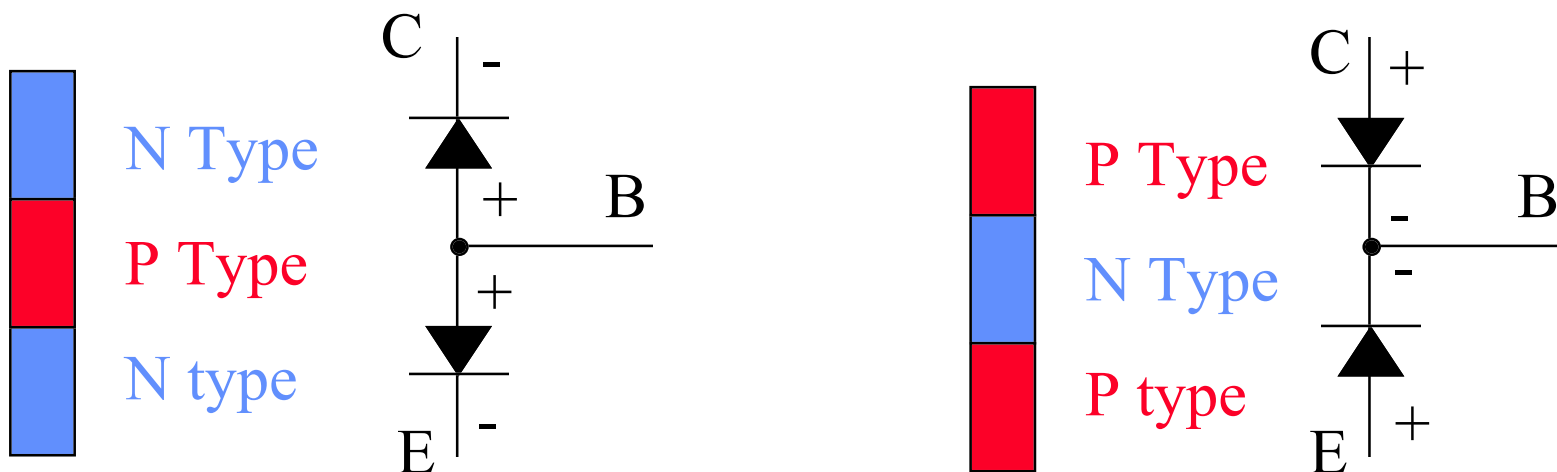- This three layer structure / construction in some ways behaves like two back to back diodes.
- No current can flow between Emitter and Collector when the Base is left floating.




Transistors and Diodes.

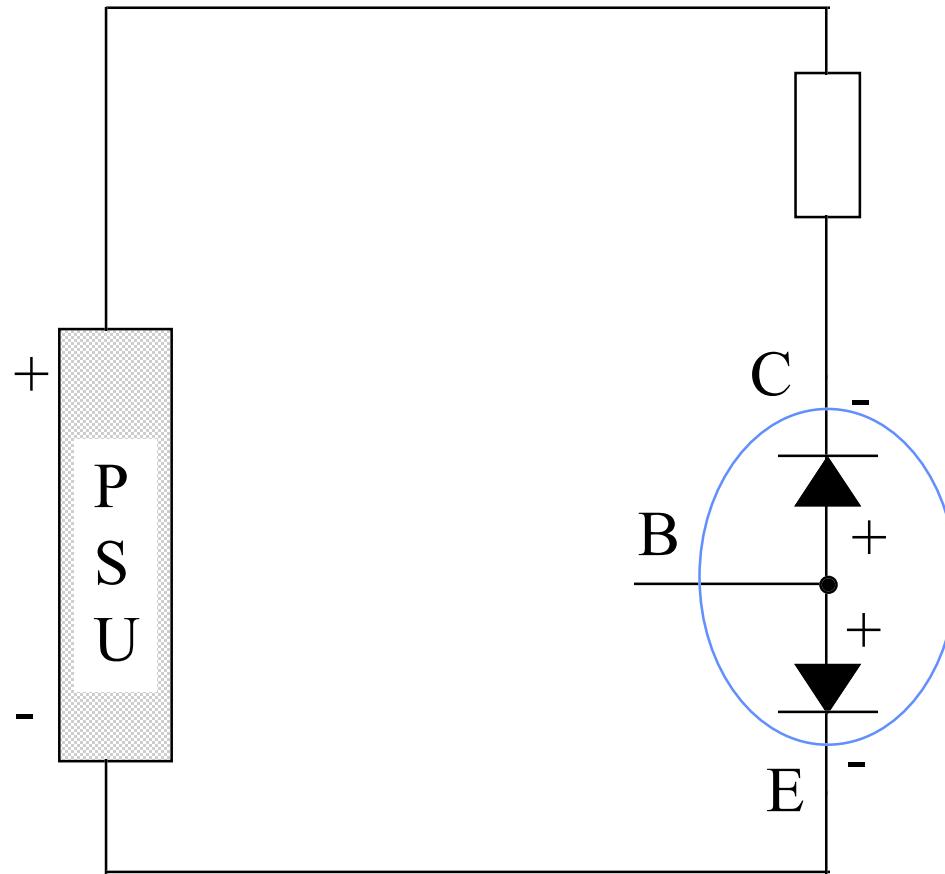

No current flows through the circuit when the Base is left floating.

However


Transistors and Diodes.

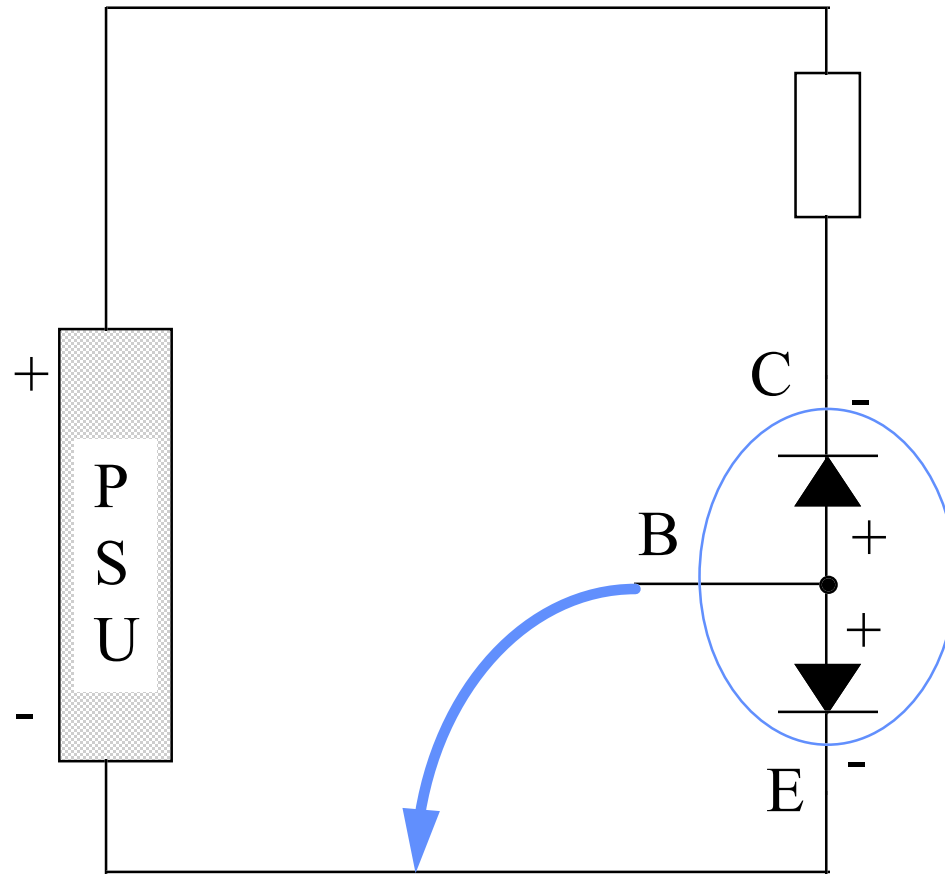

When the Base is connected to the Emitter or to a **Negative** voltage.

The lower diode will remain **Reversed Biased** and **NO current** will flow through the circuit.

Transistors and Diodes.

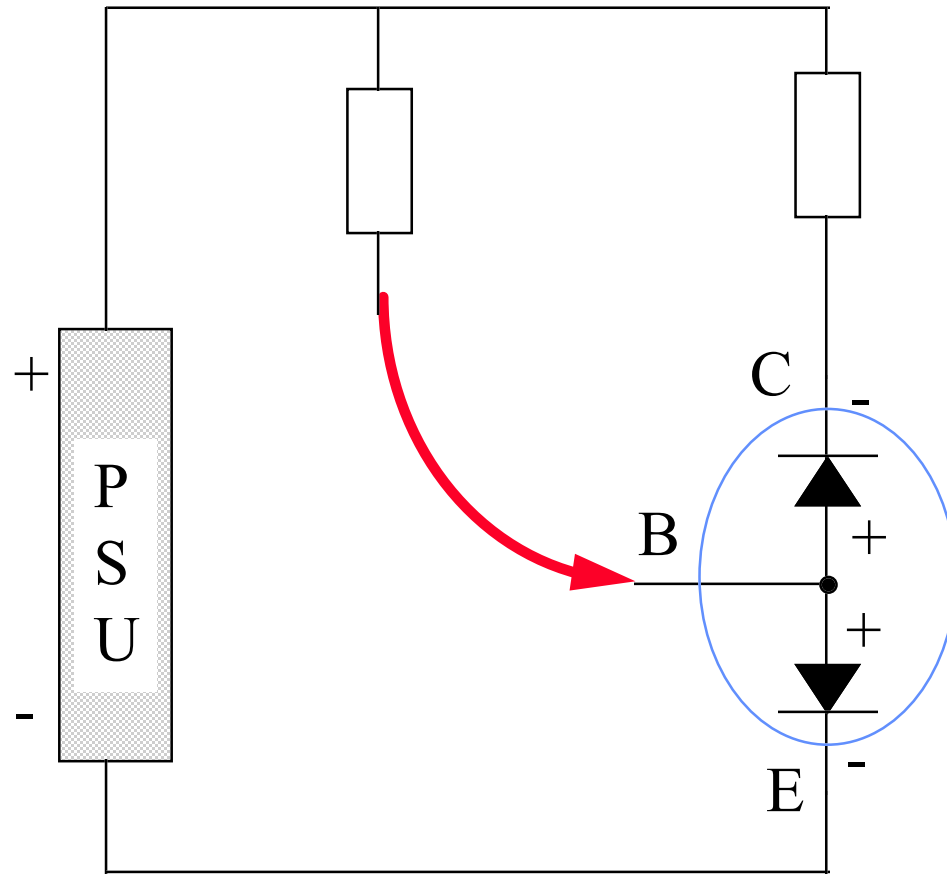


When the Base is connected to the Collector or to a **Positive** voltage.

The lower diode will become **Forward Biased** and **current** will flow from Base to Emitter.

Due to the very close proximity of the upper diode junction (same layer) the two outer **N Type** layers behave as if they are connected.

The NPN Transistor Device.

Transistors and Diodes.

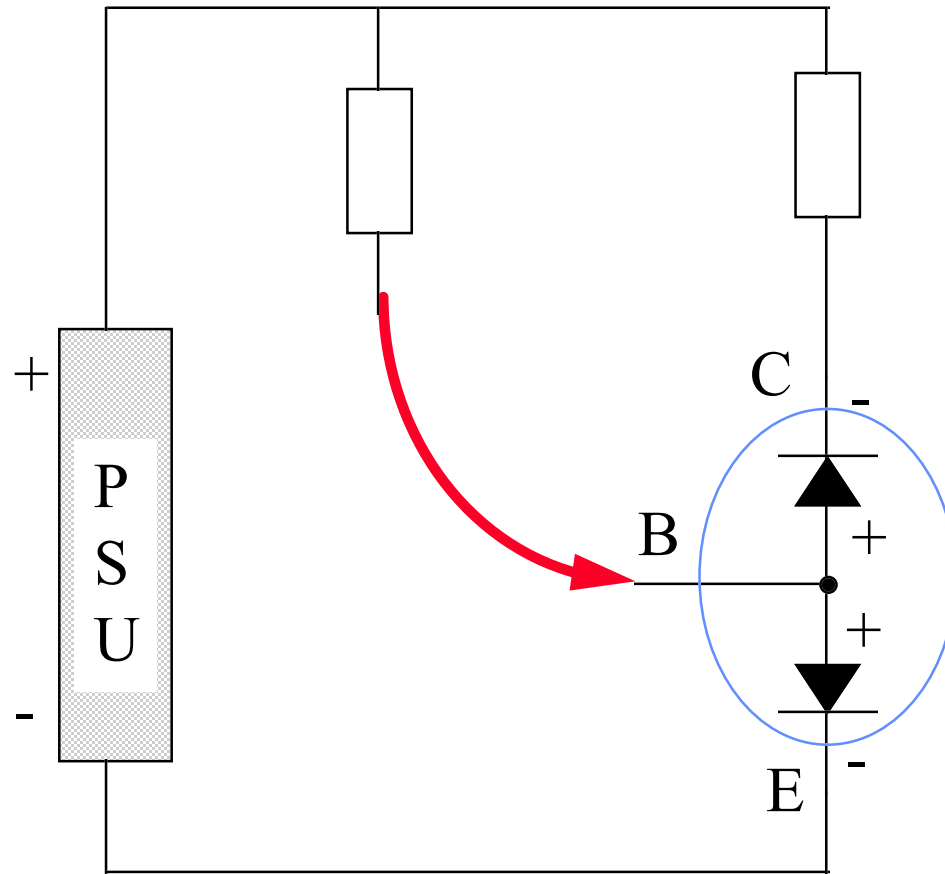


Current can now also flow from Collector through the Base to the Emitter.

It is the amount of current flowing from the Base to the Emitter that controls how much current will flow from Collector to the Emitter.

The **PNP** process is the same except that the **Polarities** applied to the Collector and Emitter are **Reversed**.

The NPN Transistor Device.

Transistors and Diodes.

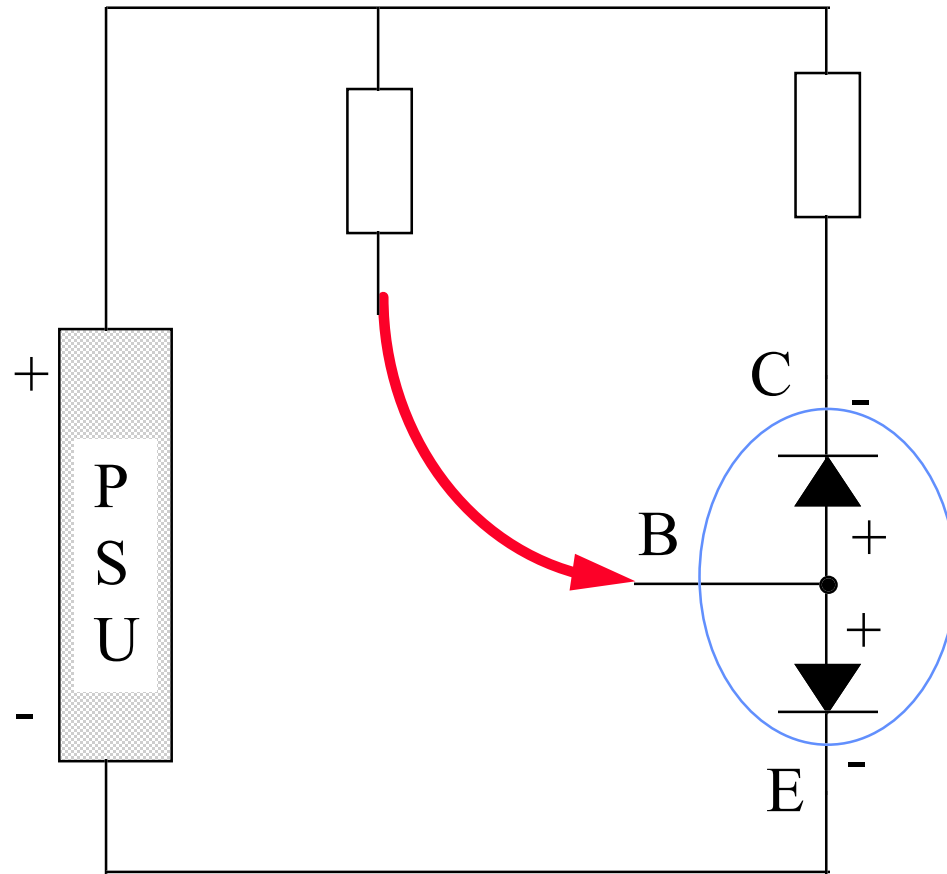

This process leads to the following calculations.

$$I_e = I_c + I_b$$

Where :-

I_e = Emitter Current

I_c = Collector Current

I_b = Base Current


Current gain of Transistor

$$h_{fe} = I_c / I_b$$

The NPN Transistor Device.

Transistors and Diodes.

- The Basic epitaxial planar structure.

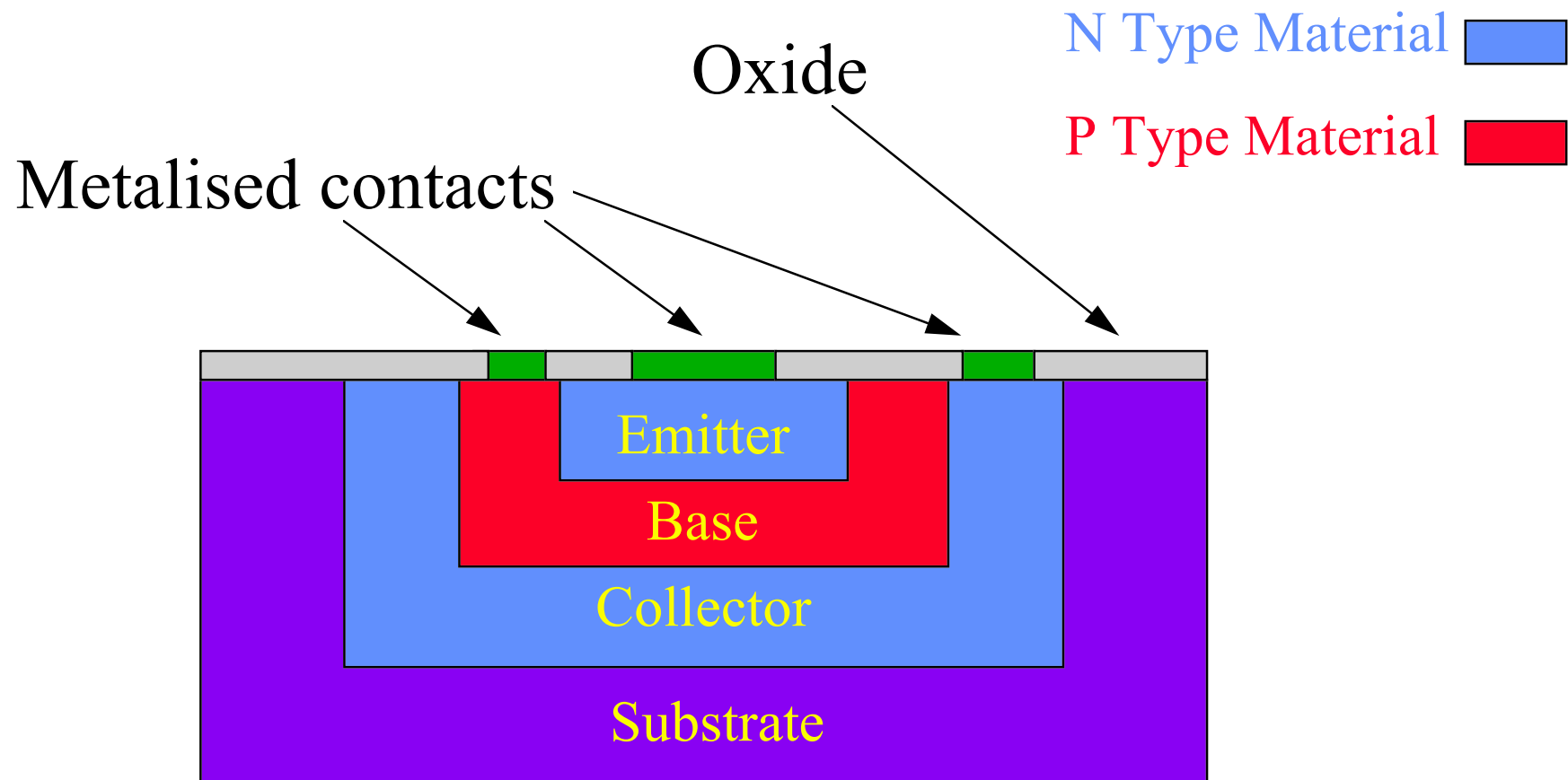


Transistors and Diodes.

Junction Field Effect Transistors (JFET)


Transistors and Diodes.

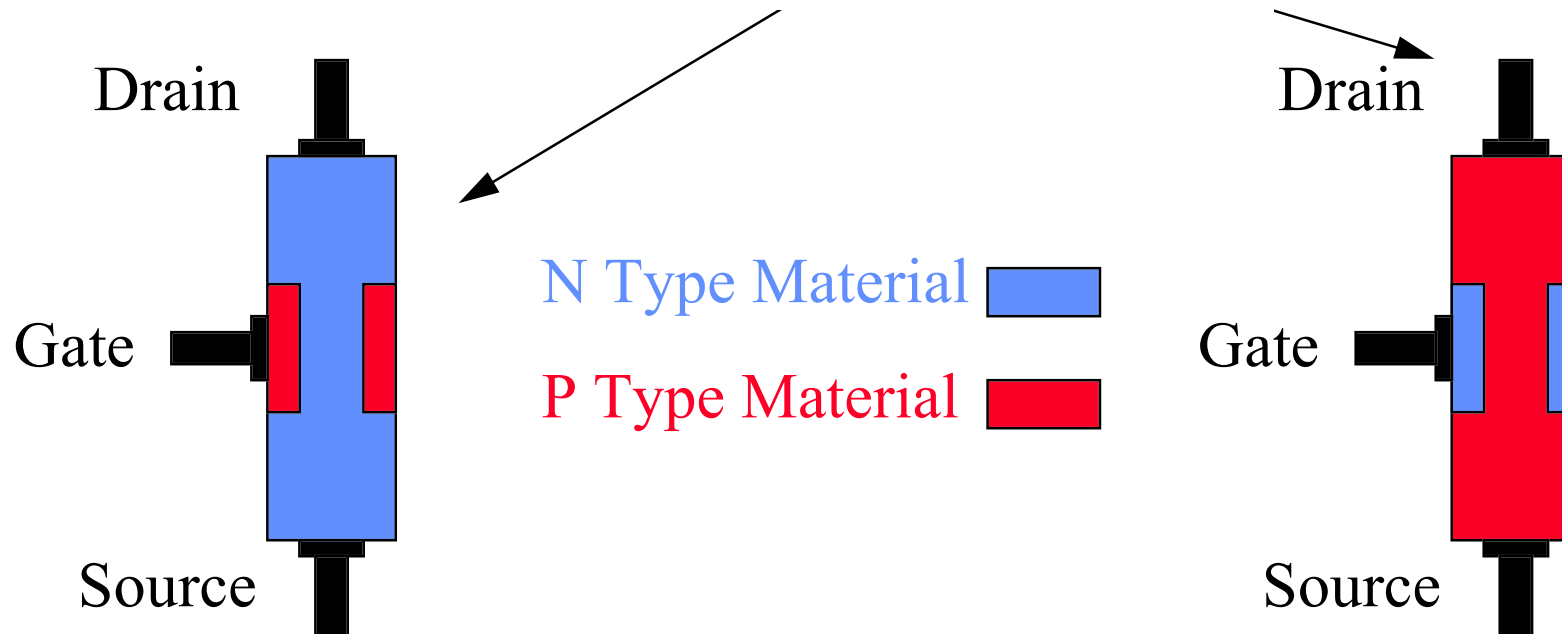- Another development phase was to build single channel device semiconductor and this also gave two the possible variants.
- These variants are identified from their construction i.e. **N Channel** and **P Channel**.




Transistors and Diodes.

Field Effect Transistor (FET).

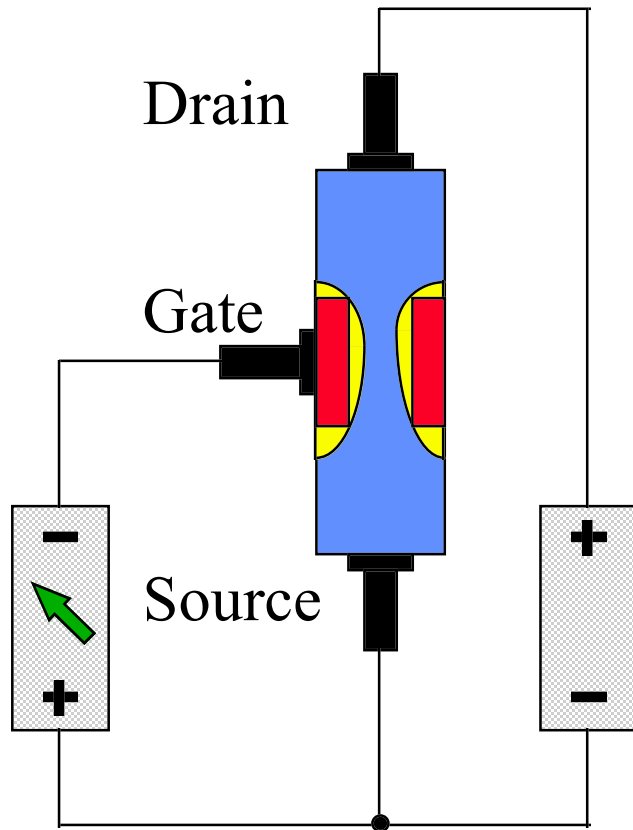

FET Biased for Conduction

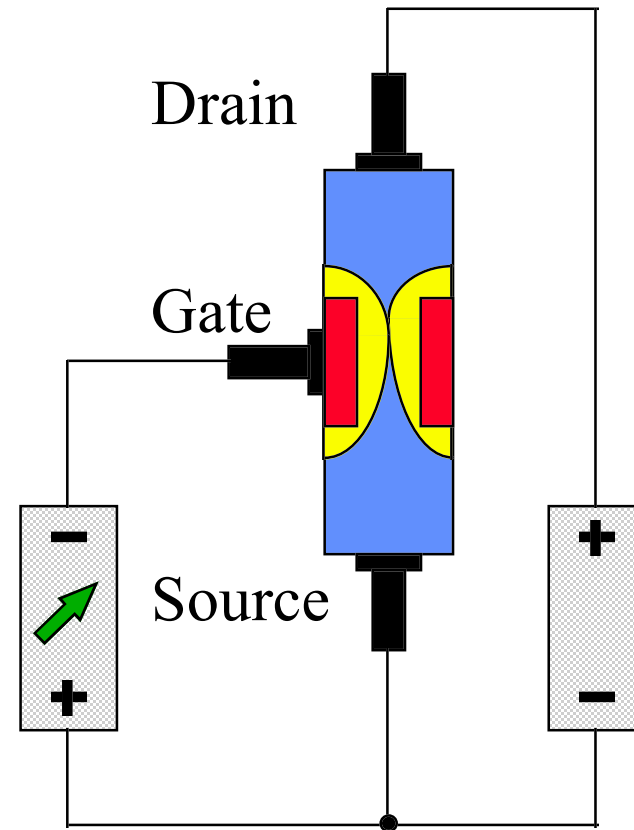

FET Biased for Maximum Resistance

Transistors and Diodes.

Metal Oxide Silicon Field Effect Transistors (MOSFET)


Transistors and Diodes.

MOSFET

Depletion Mode Devices

Transistors and Diodes.

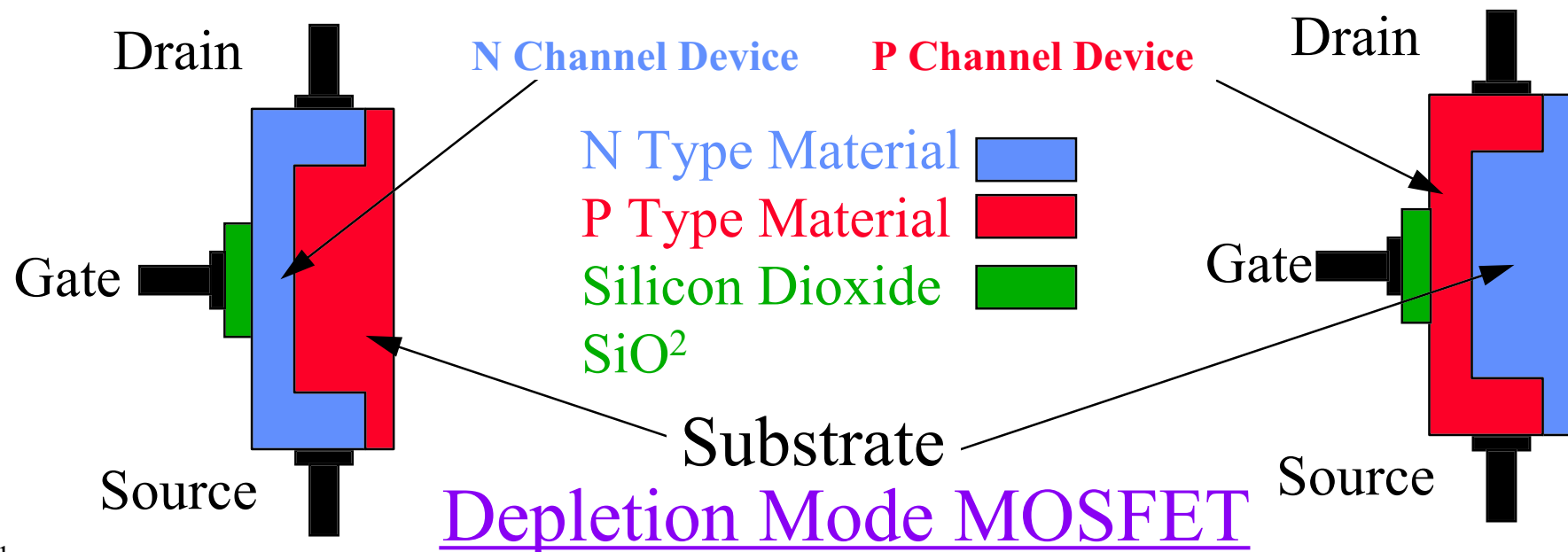
- Another development phase was to build a semiconductor device with no PN junctions giving a number of possible variants.
- These variants are identified again from their construction and Operation.



Transistors and Diodes.

Metal Oxide Silicon Field Effect Transistor (MOSFET).

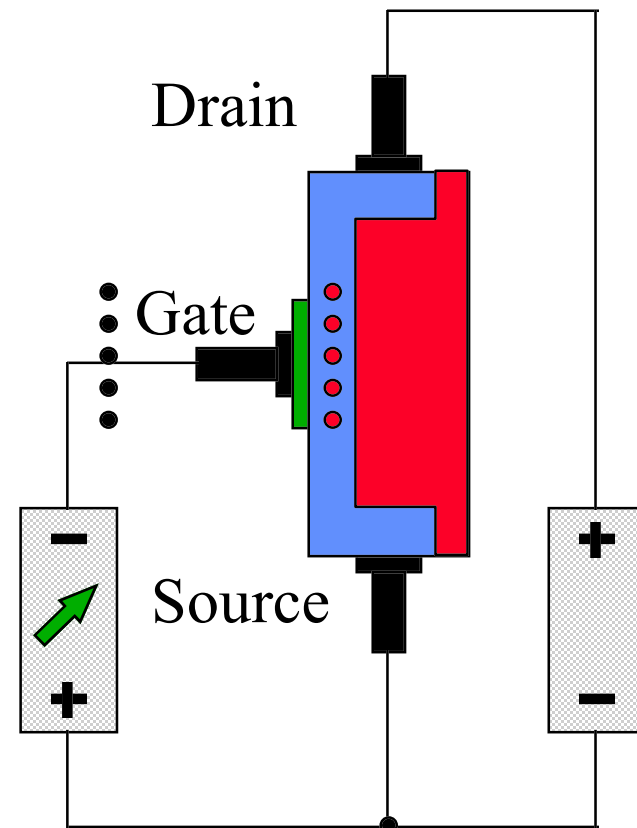- The Insulated Gate behaves in a similar manner to a Capacitor.
- If a **Negative** charge applied on the Gate (Black Dots) presents as a **Positive (Red Dots)** charge in the channel and this charge **Repels Conduction Electrons**.
- A higher Negative Gate voltage will cause MOSFET resistance to increase. (**Depletion Mode**)




MOSFET Biased for Maximum Resistance

Transistors and Diodes.

Metal Oxide Silicon Field Effect Transistor (MOSFET).

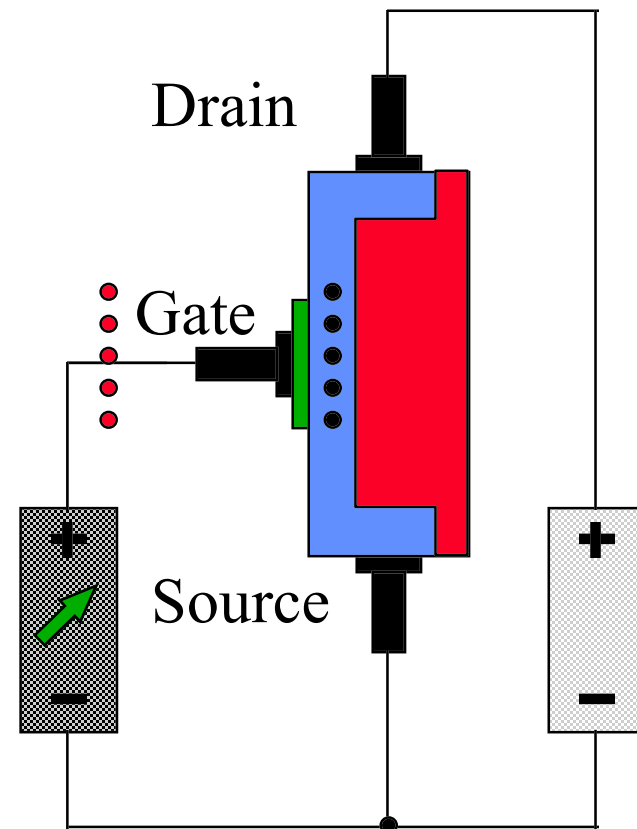- The Insulated Gate behaves in a similar manner to a Capacitor.
- If a **Positive** charge applied on the Gate (**Red Dots**) presents as a **Negative** charge (Black Dots) in the channel and this charge will **Attract Conduction Electrons**.
- A higher Positive Gate voltage will cause MOSFET resistance to reduce. (**Enhancement Mode**)




Transistors and Diodes.

MOSFET

Enhancement Mode Devices

Transistors and Diodes.

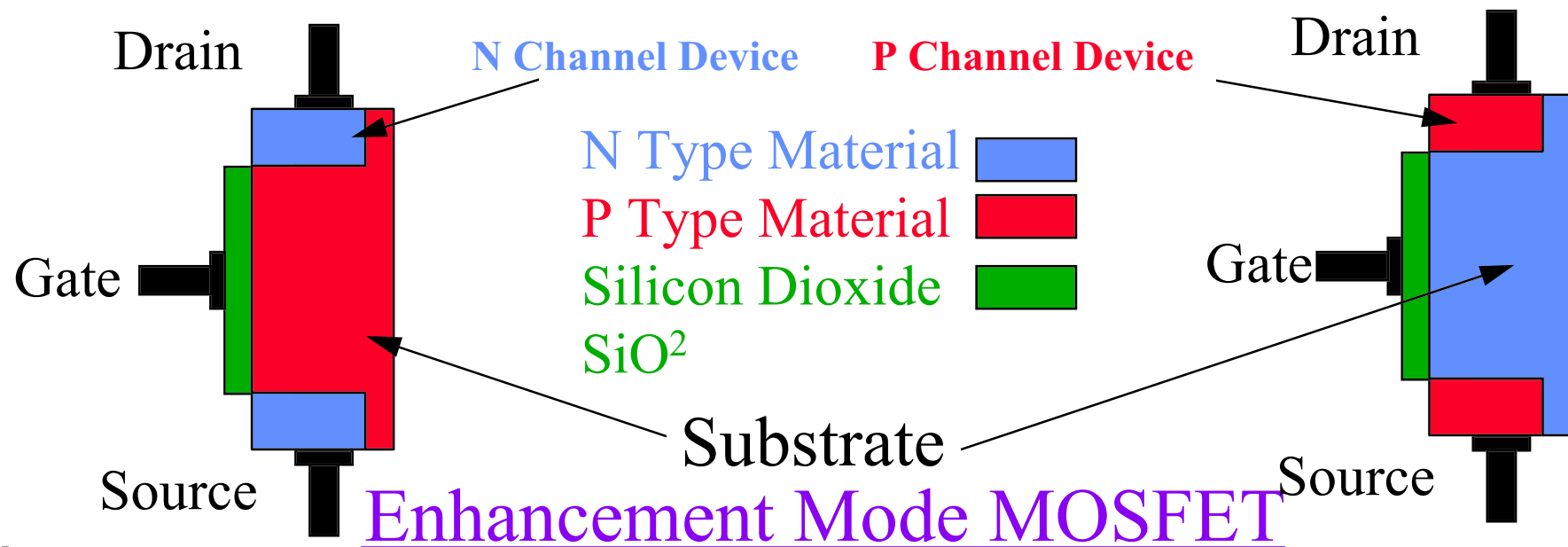
- Another development phase was to build a semiconductor device with no PN junctions giving a number of possible variants.
- These variants are identified again from their construction and Operation.



Transistors and Diodes.

Metal Oxide Silicon Field Effect Transistor (MOSFET).

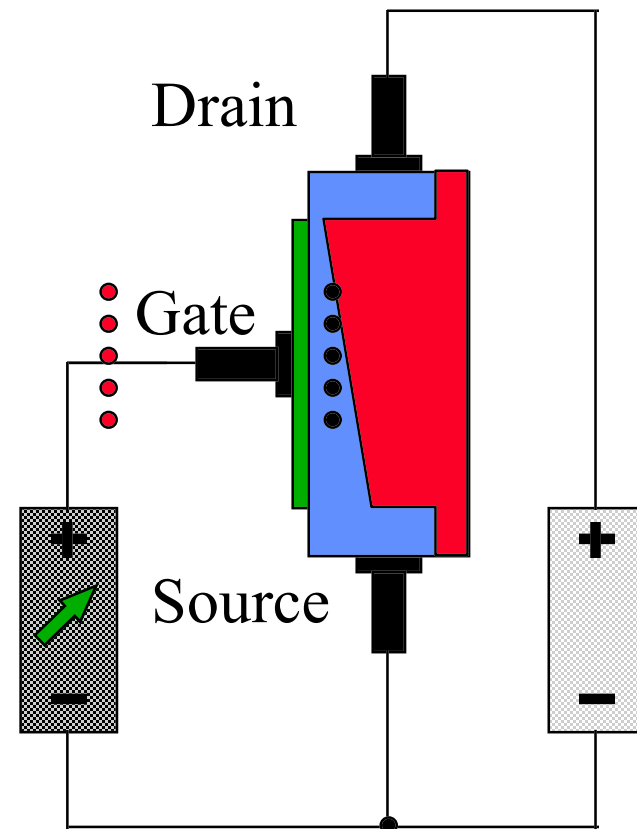- The Insulated Gate behaves in a similar manner to a Capacitor.
- If a **Positive** charge applied on the Gate (**RED Dots**) presents as a **Negative** (Black Dots) charge in the substrate area and this charge will induce a conduction channel through the device.
- A higher Positive Gate voltage will cause MOSFET resistance to reduce. (**Enhancement Mode Only**)




MOSFET Biased for Minimum Resistance

Transistors and Diodes.


BS Circuit Symbols Transistors Bipolar and FET

Transistors and Diodes.


BS Symbols.

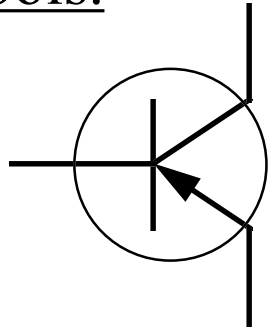


PNP Transistor

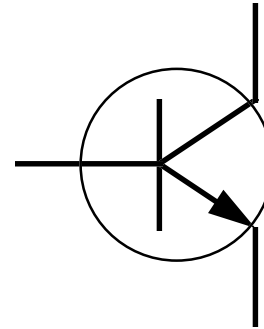

NPN Transistor

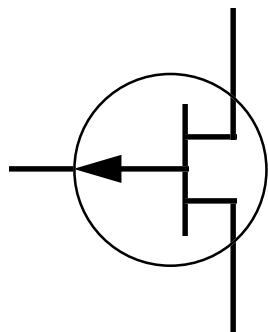

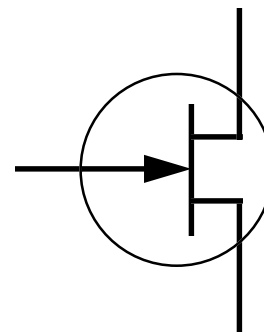
P Channel Junction Field
Effect Transistor JFET




N Channel Junction Field
Effect Transistor JFET

Transistors and Diodes.


BS Symbols.

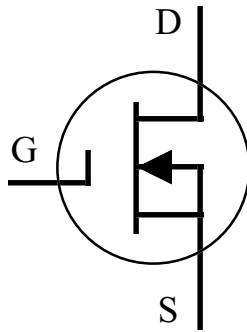


**N Channel Depletion mode
D-MOSFET**

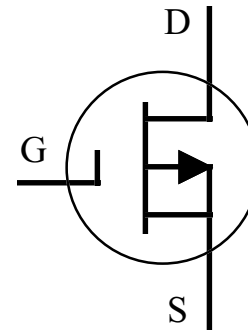

**P Channel Depletion mode
D-MOSFET**

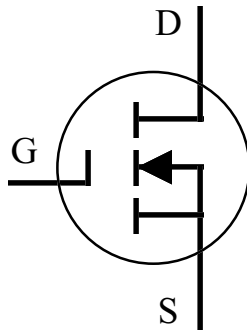

**N Channel Enhancement mode
D-MOSFET**

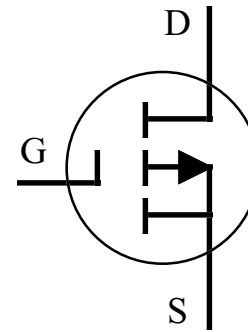


**P Channel Enhancement mode
D-MOSFET**

Metal Oxide Silicon Field Effect Transistors MOSFET


Transistors and Diodes.

Special Circuit Configurations

Transistors and Diodes.

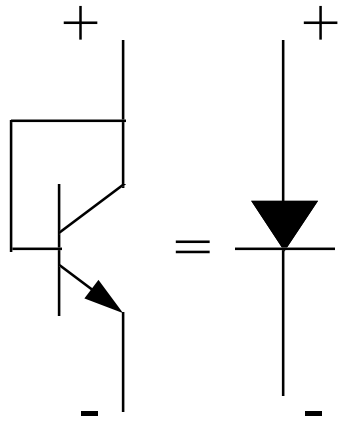


The Transistor
configured as a Diode

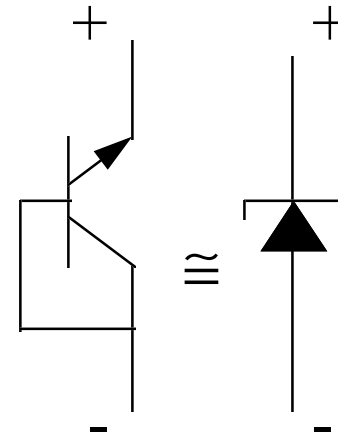

The Transistor
configured as a Zener
Diode

Transistors and Diodes.

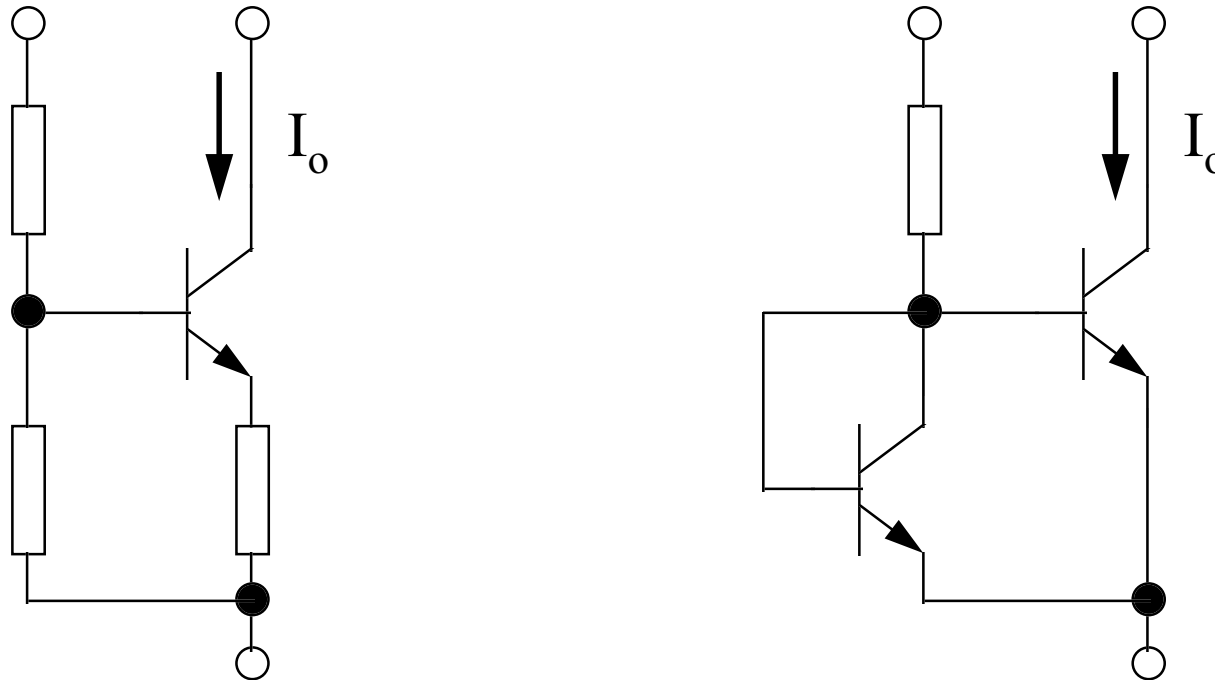

The Transistor/s configured as a
constant current source.

Transistors and Diodes.


**Multi-Layer Devices
Diacs , Thyristors
(SCRs) and Triacs**

Transistors and Diodes.

- General terms related to **Diodes** :-
- Di = two : **ode** from electro**de** (electrical conductor).
- A Diode is a device that usually has two terminals and allows current to flow in one direction only.
- In some applications it can be considered to act like a **Switch** (Power Control and Digital Circuits).
- The diode can be used to produce a voltage **reference**.
- The term **Rectifier** is the generic name used to indicate that a **Diode** is used for **Power** applications.
- The term **Detection** is the generic name used to indicate that a **Diode** is being used in **Low current / High Frequency** applications.

Transistors and Diodes.

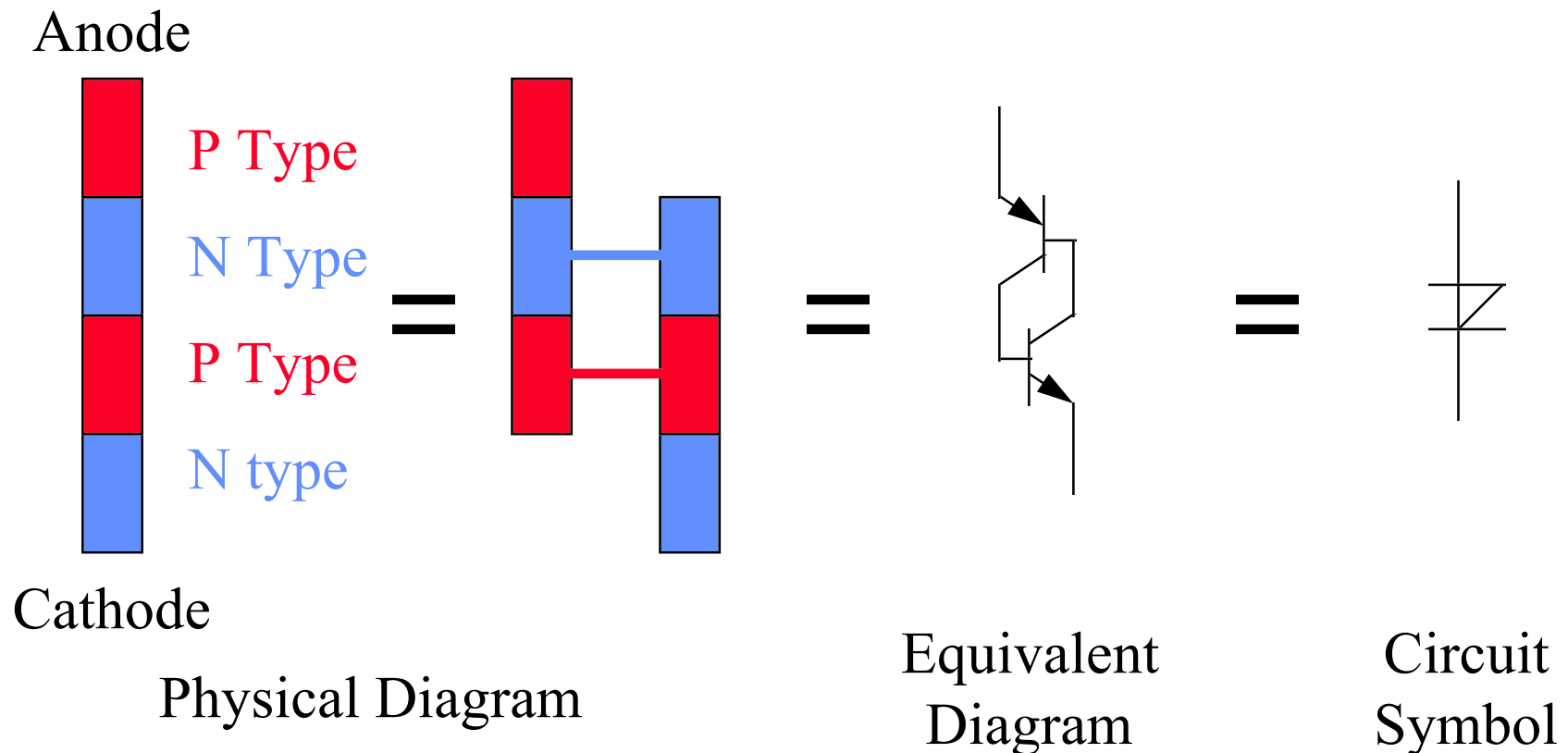- The Shockley Diode is a four layer semiconductor device. The geometry of the device defines the emitters and its operational characteristics.




Transistors and Diodes.

- The Shockley Diode (Unidirectional) :-
- Ideal transistors will not conduct however real devices have defined breakover voltages (Collector/Emitter) and also experience leakage.
- If **one** transistor **starts to conduct**, normal transistor action will then occur switching on the other causing **Positive feedback** and the two **devices** then **latch on**.
- The Shockley Diode will remain switched on until the **current** through the device is **reduced** to a point where one of the transistors reaches the base cutoff point which **breaks** the **Positive feedback** loop.
- Summary : High voltage pulse switches device on.


Transistors and Diodes.

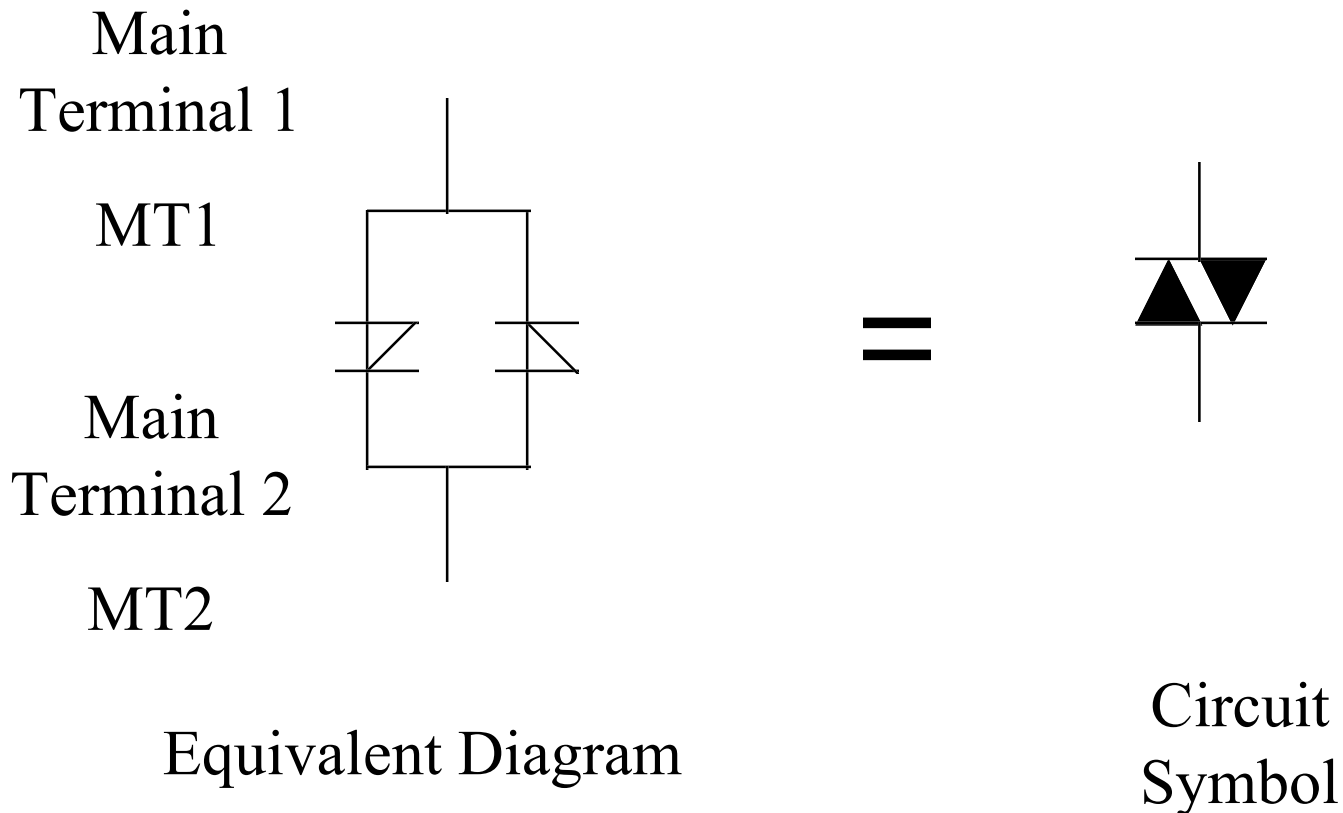- The Diac (Diode for Alternating Current)
- The Diac is built from two Shockley Diodes wired in inverse parallel.




Transistors and Diodes.

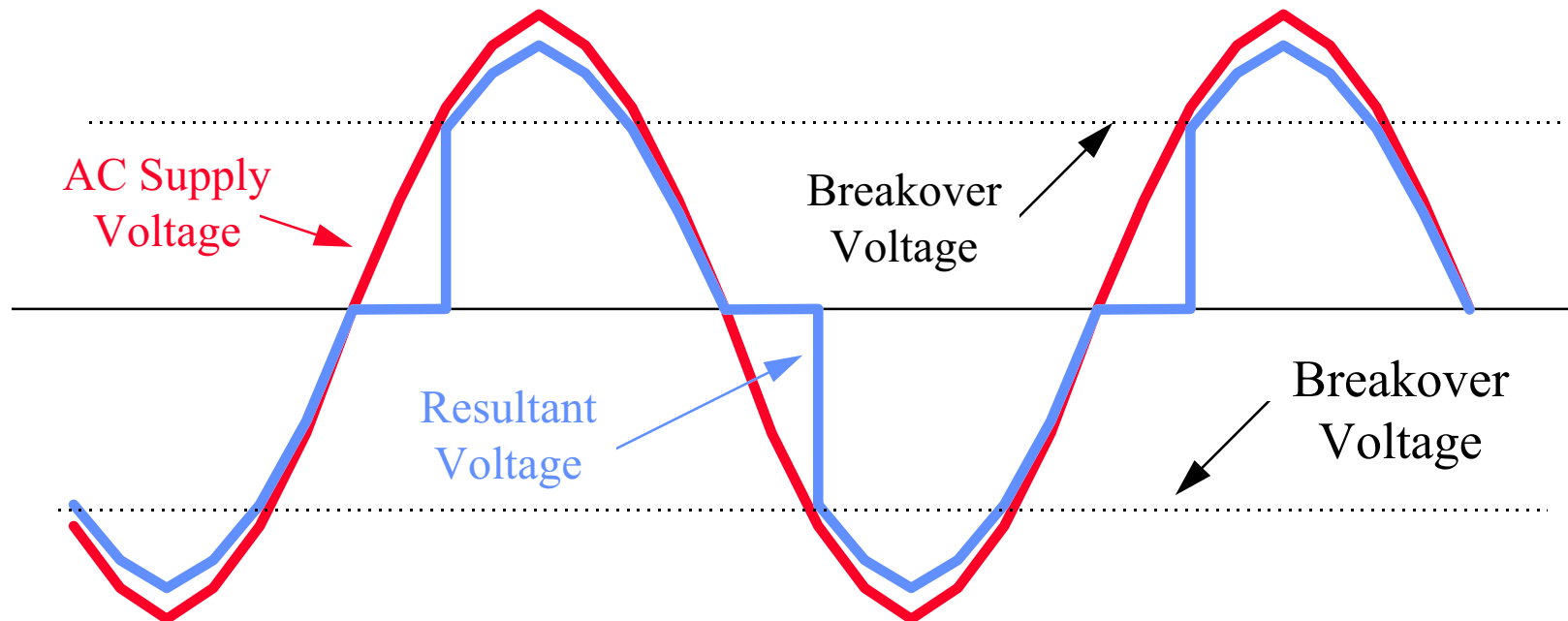- The DIAC (Bi-directional) :-
- With a DC voltage applied the Diac will behave in the same way as a Shockley Diode .
- Summary: AC Operation: effect as shown below.
- Note: This device is rarely used on its own .



Transistors and Diodes.

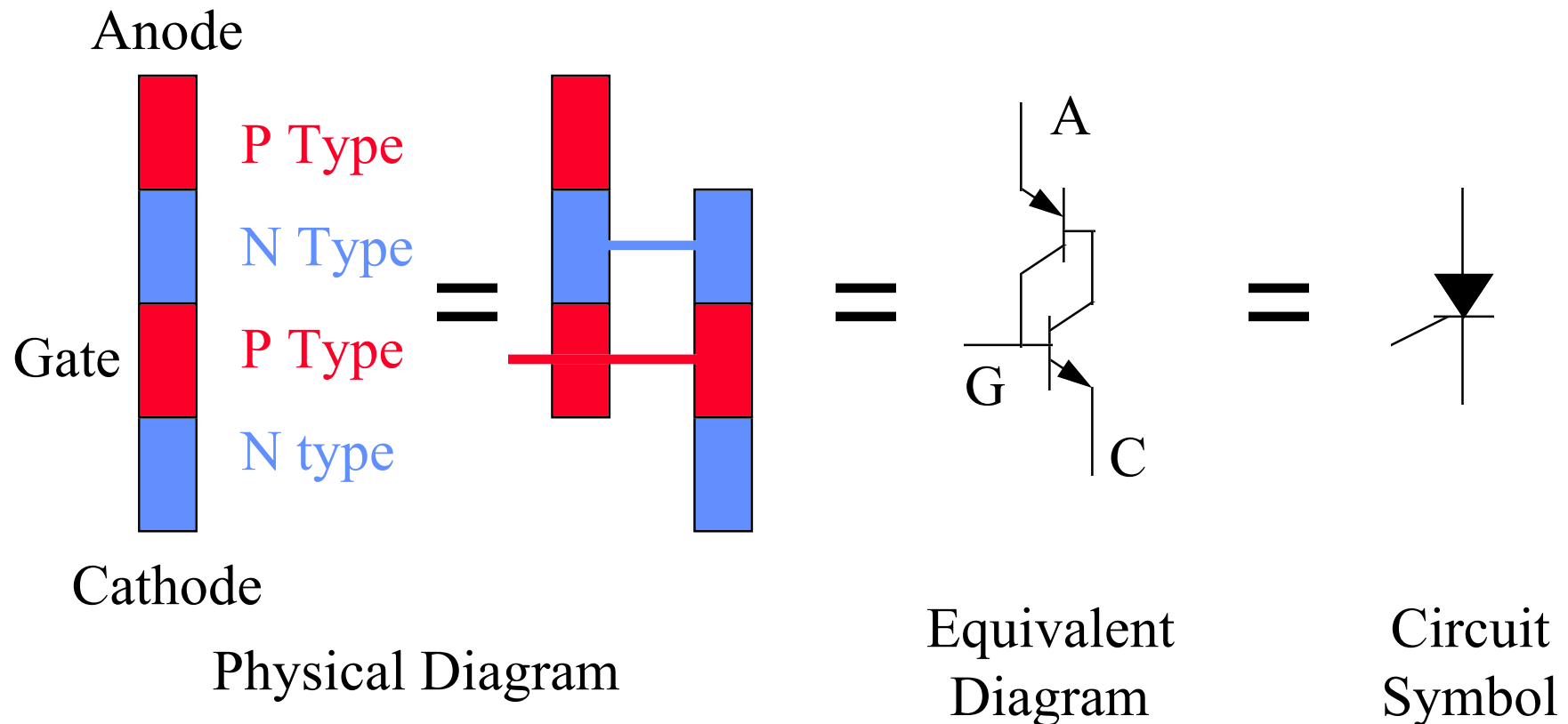- The Silicon-Controlled Rectifier (SCR) is a four layer semiconductor device. The geometry of the device defines its operational characteristics.



Transistors and Diodes.


- The Silicon-Controlled Rectifier (SCR) :-
- The operation is identical to that of a Shockley Diode, however, the gate terminal allows an alternative way of triggering the device.
- The breakover voltage of an SCR is much higher than the expected device operational voltage.
- Summary : A small amount of current applied to the **Gate** of the SCR can **control** significantly higher **current** through the device (Anode to Cathode).
- Note: Some SCRs have a inbuilt resistor connected between Gate and Cathode connections to avoid false triggering of the devices.

Transistors and Diodes.

- The Gate Turn Off Thyristor (GTO) :-
- The operation similar to the SCR, however, the GTO uses the gate current to stop the device conducting.
- The gate current may need to be up to 20% of the Anode (load) current to switch the device off.
- Circuit symbol for a GTO or SCR is the same.
- Summary : The geometry of the device ensures that the gain of the NPN transistor is much higher than the PNP transistor and this allows more control to disable the latched state.
- Note: This device is rarely used in general/common circuit applications.

Transistors and Diodes.

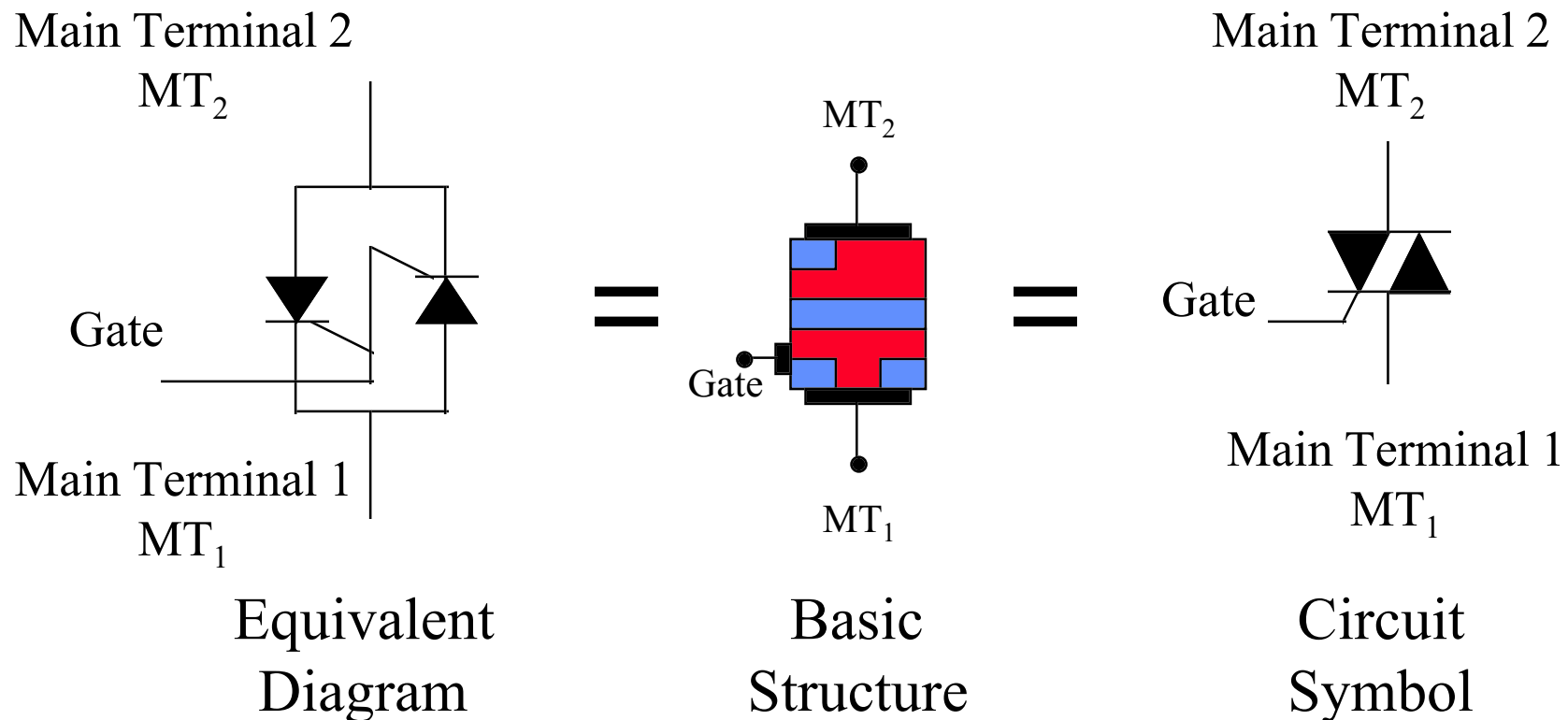- The Triac is built from two SCRs wired in inverse parallel.




Transistors and Diodes.

- The TRIAC (Triode for Alternating Current) :-
- The operation is similar to two back to back SCRs, however, Triacs tend to NOT trigger symmetrically.
- To overcome this problem a DIAC is usually placed in series with the Triac gate.
- Summary : Used to control AC power in relatively low power applications.
- Note :
 - MT1 and MT2 are NOT interchangeable.
 - To trigger successfully the gate current must come from the MT2 side of the device.

Transistors and Diodes.

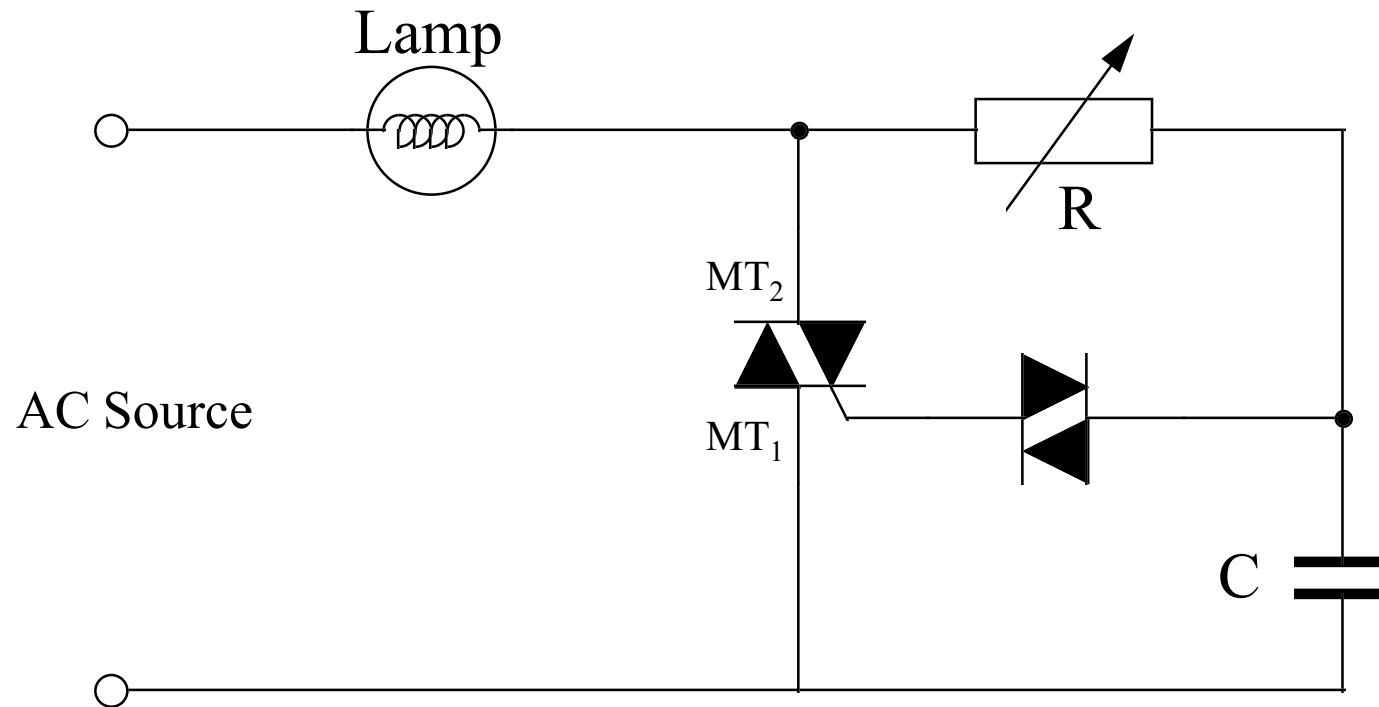
- A typical example of a power control circuit using a Triac.



Note: The quicker the voltage rises across the Capacitor C then the brighter the lamp will become.


Transistors and Diodes.

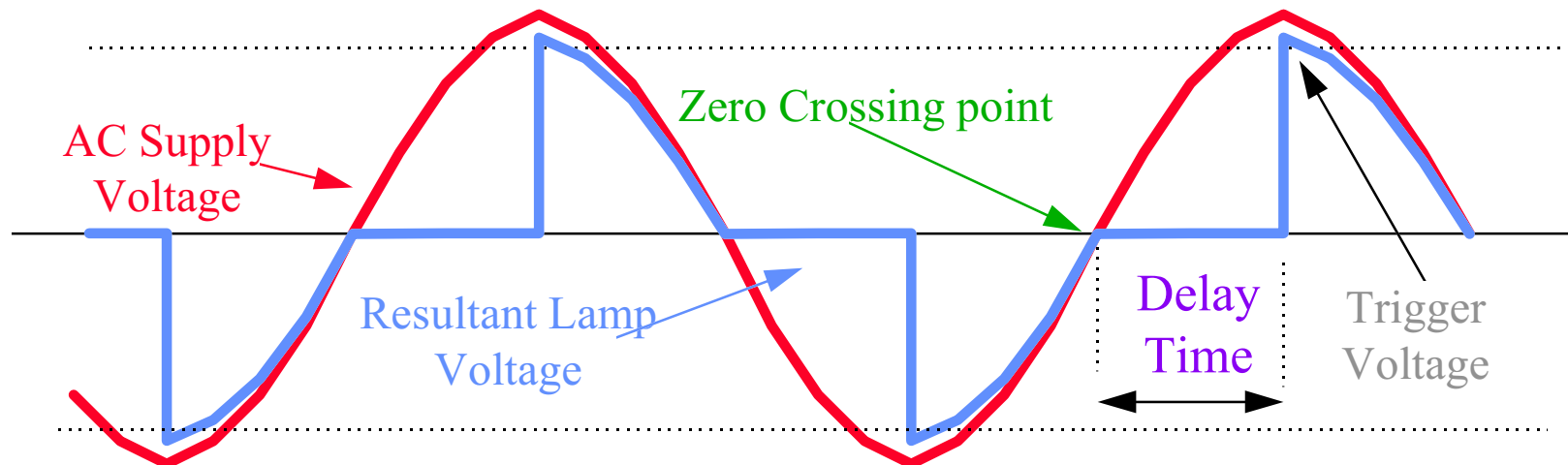- The Capacitor C charges up at a rate determined by the CR Ratio (R is a variable Resistor).
- When the Trigger Voltage across the Capacitor is sufficient to cause the Diac to breakover the Triac will latch on and the lamp will light.
- The level of brightness will depend how long the **Delay Time** is before the trigger occurs after the **Zero Crossing point** of the waveform.




Transistors and Diodes.

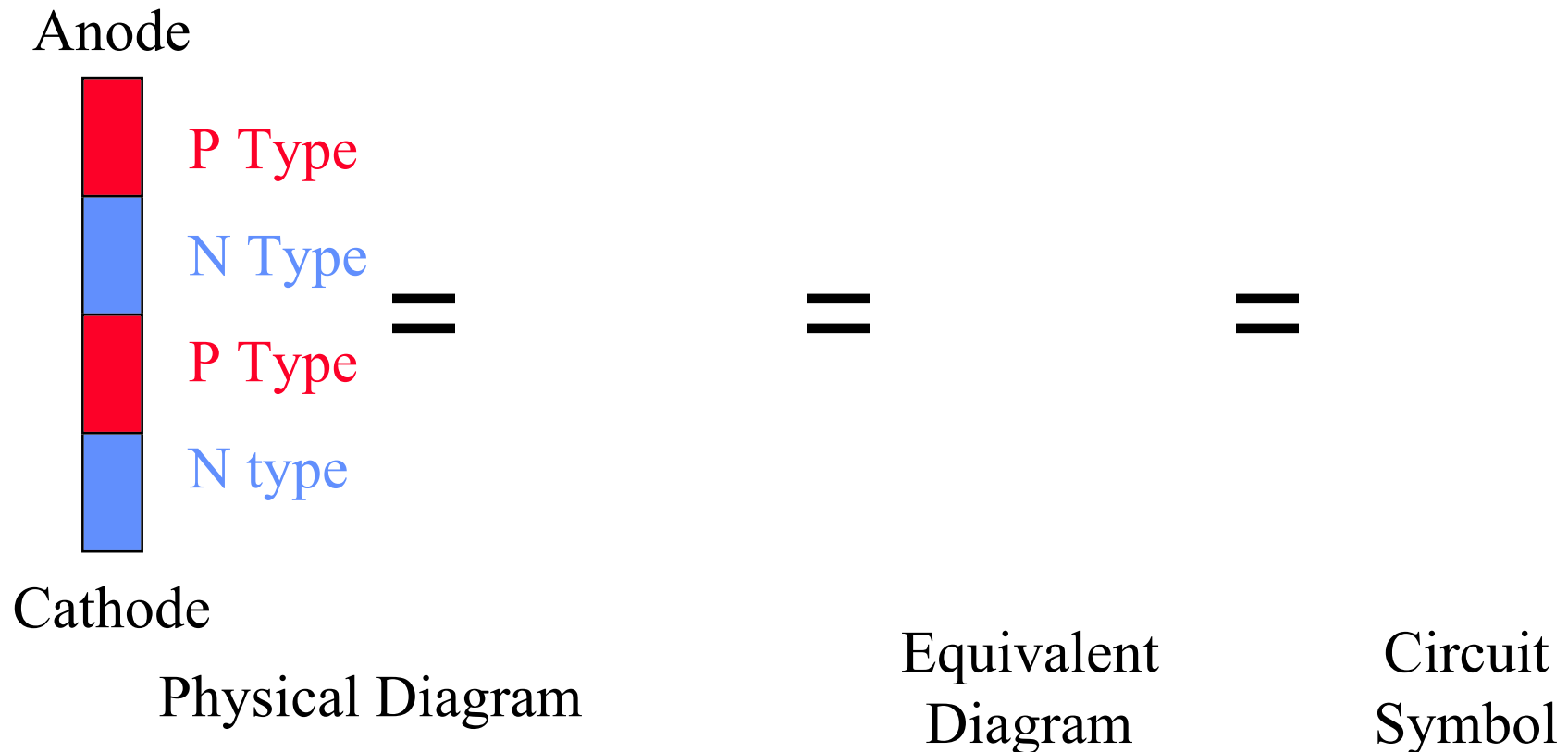- The Shockley Diode is a four layer semiconductor device. The geometry of the device defines the emitters and its operational characteristics.




Transistors and Diodes.

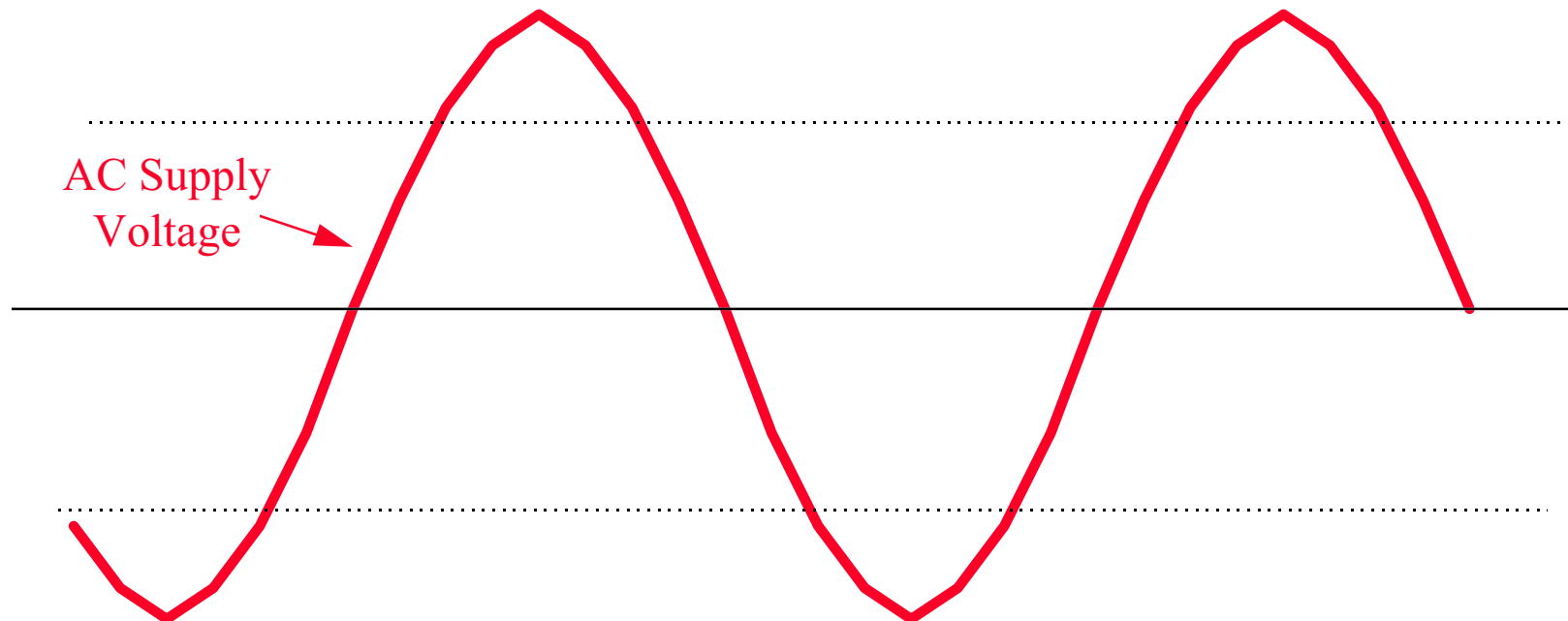- The DIAC (Bi-directional) :-
- With a DC voltage applied the Diac will behave in the same way as a Shockley Diode .
- Summary: AC Operation: effect as shown below.
- Note: This device is rarely used on its own .




Transistors and Diodes.

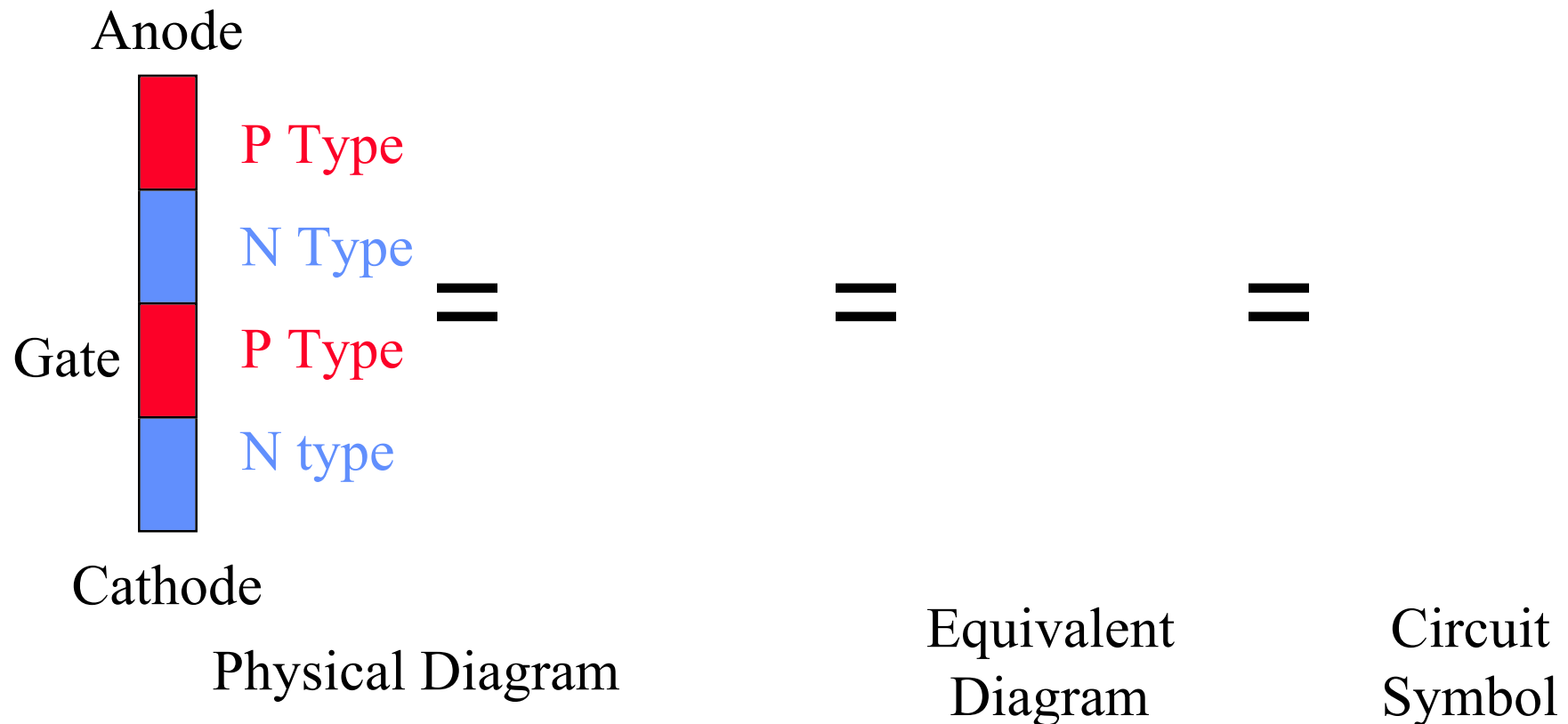- The Silicon-Controlled Rectifier (SCR) is a four layer semiconductor device. The geometry of the device defines its operational characteristics.




Transistors and Diodes.

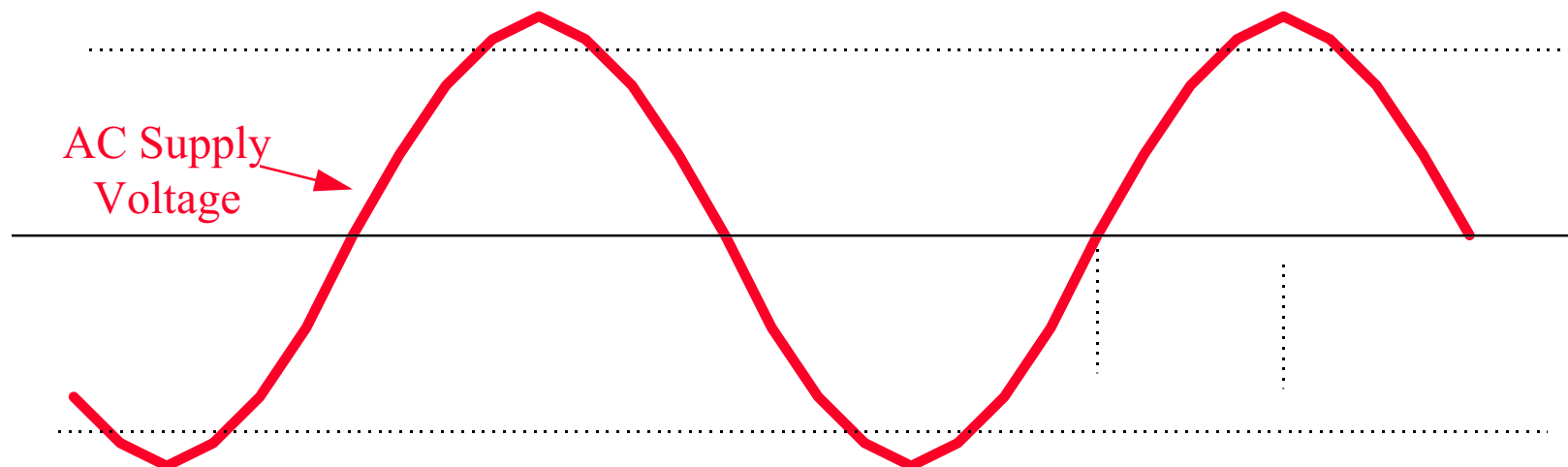- The Capacitor C charges up at a rate determined by the CR Ratio (R is a variable Resistor).
- When the Trigger Voltage across the Capacitor is sufficient to cause the Diac to breakover the Triac will latch on and the lamp will light.
- The level of brightness will depend how long the **Delay Time** is before the trigger occurs after the **Zero Crossing point** of the waveform.



Transistors and Diodes.

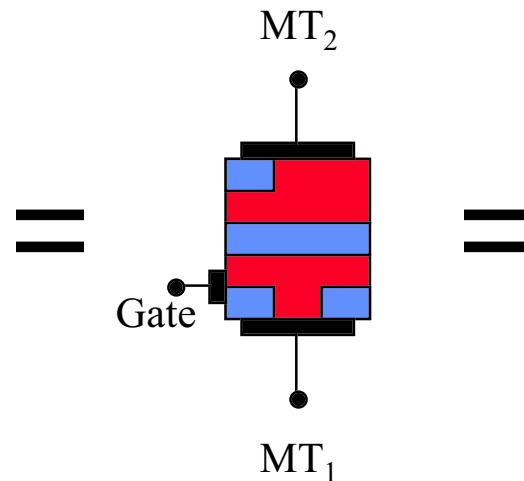- The Triac is built from two SCRs wired in inverse parallel.




Equivalent
Diagram

Basic
Structure

Circuit
Symbol

Transistors and Diodes.

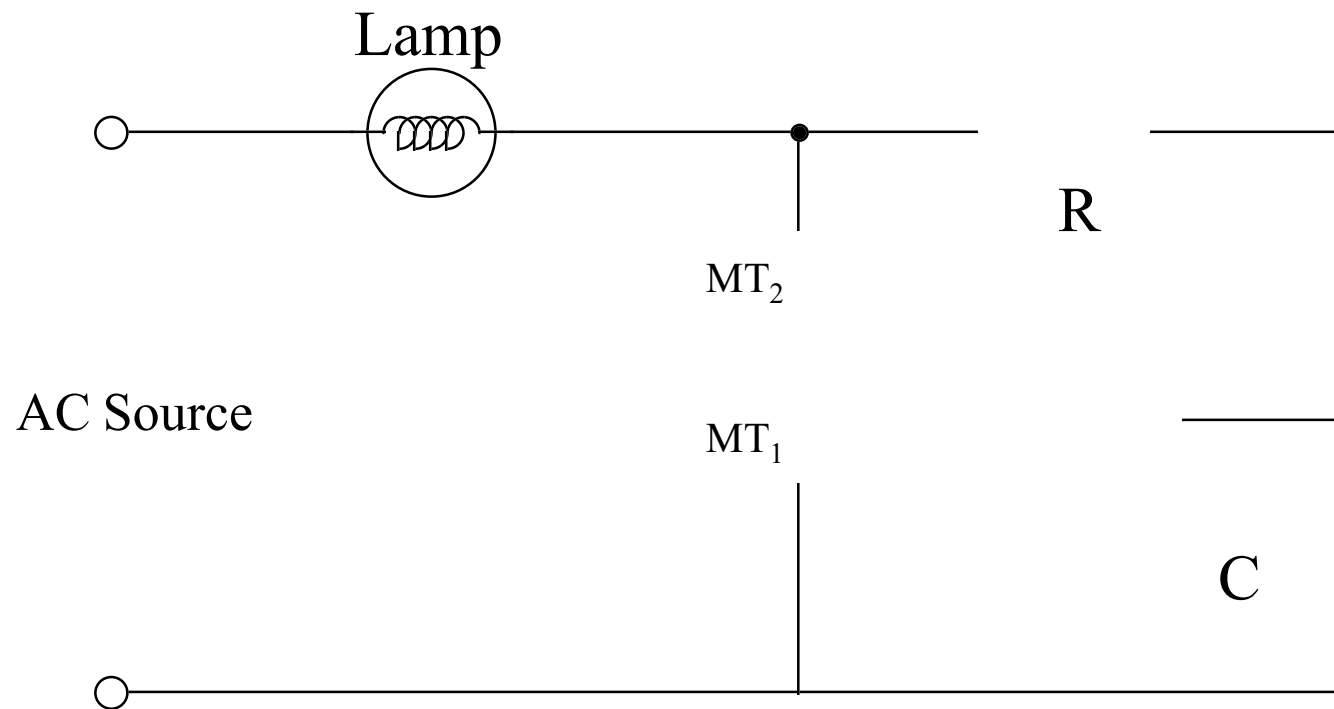- A typical example of a power control circuit using a Triac.



Note: The quicker the voltage rises across the Capacitor C then the brighter the lamp will become.

The 555 Timer

Summary


The 555 Timer.

- A low cost and easy to use component.
- Can be configured as a Monostable using one resistor and one capacitor.
- Can be configured as an Astable using two resistors and one capacitor.
- Can operate up to 2MHz and can be fully compatible with CMOS, TTL and MOS logic.

The 555 Timer.

When Threshold reaches $> 2/3 V_{dd}$ Reset activated and Output is forced Low


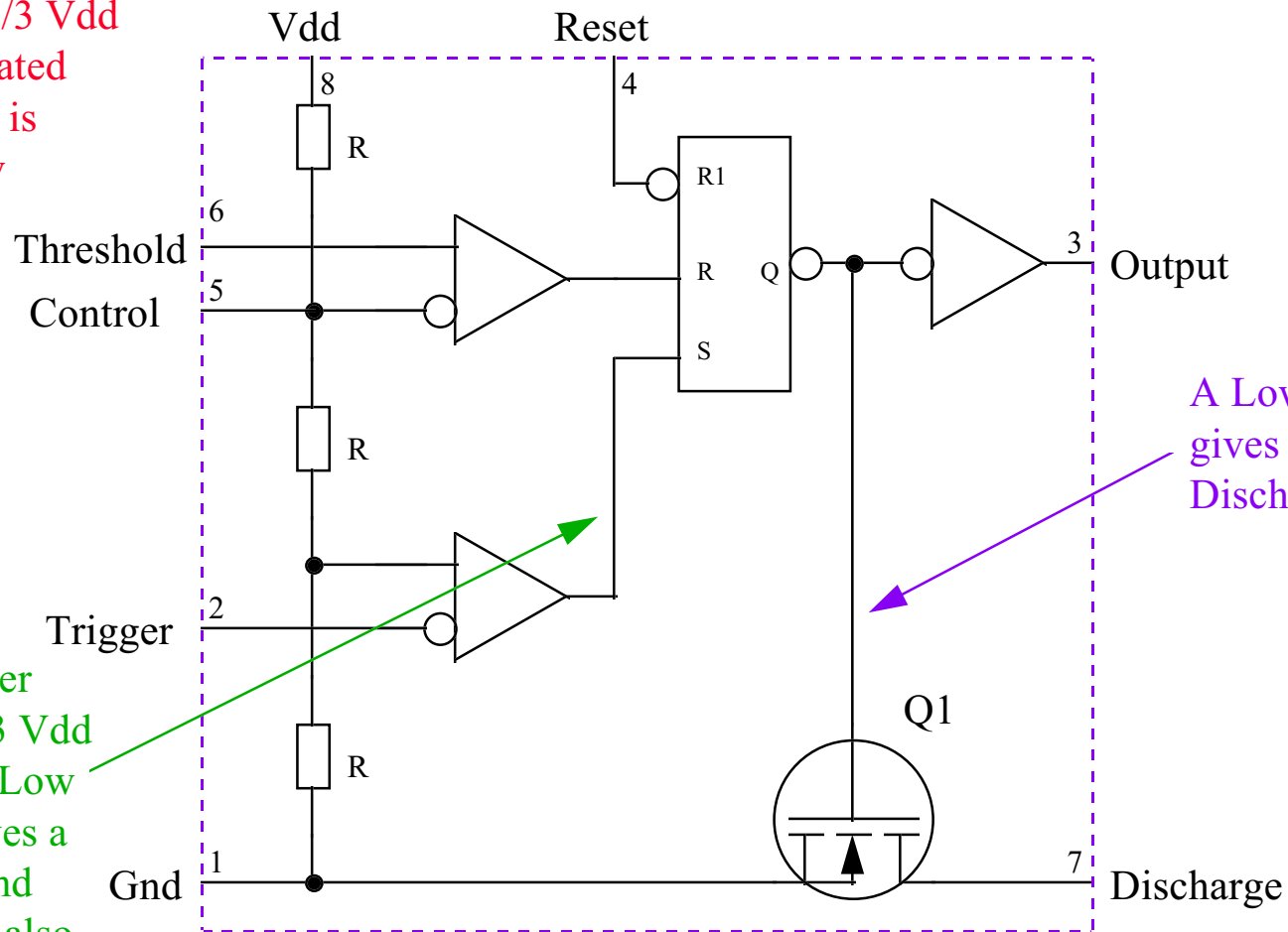
When Trigger reaches $< 1/3 V_{dd}$ or is forced Low then this gives a High here and Output then also goes High.



A Low on the Output gives a High here and Discharge goes Low.

Functional Block Diagram.



The 555 Timer.

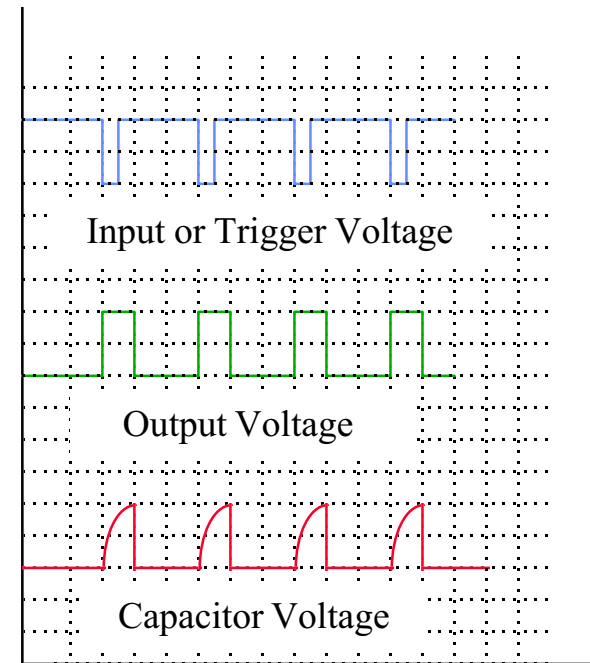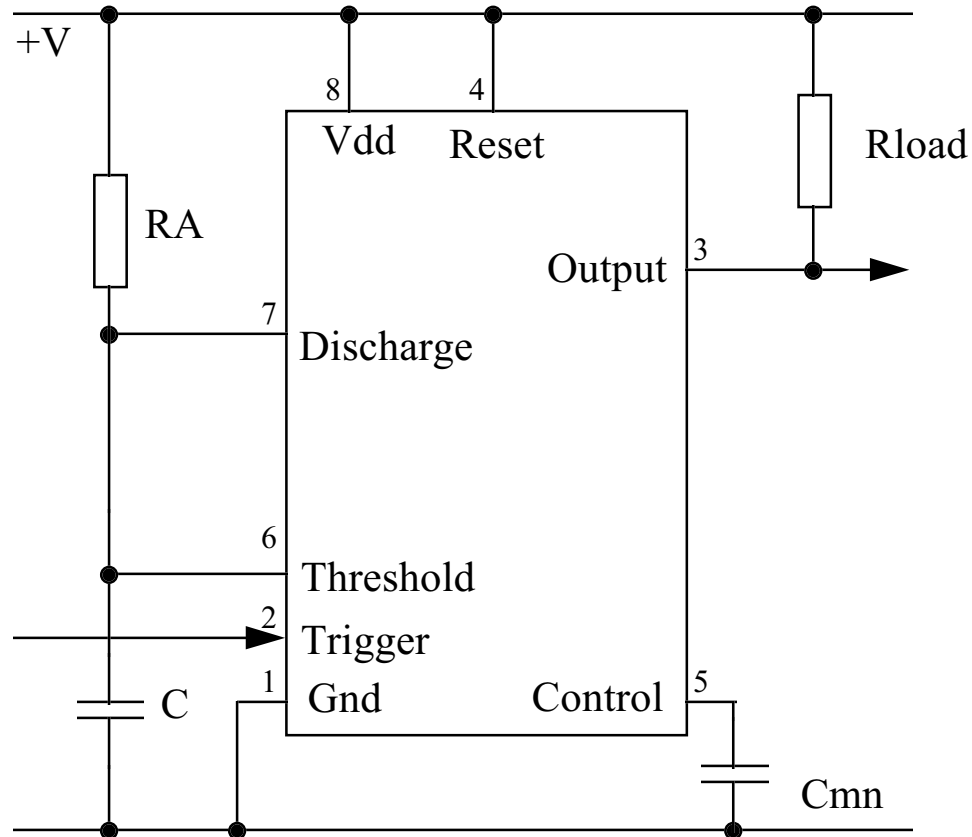

$$\text{Pulse width} = 1.1 * RA * C$$

555 Configured as a Monostable.

The 555 Timer.

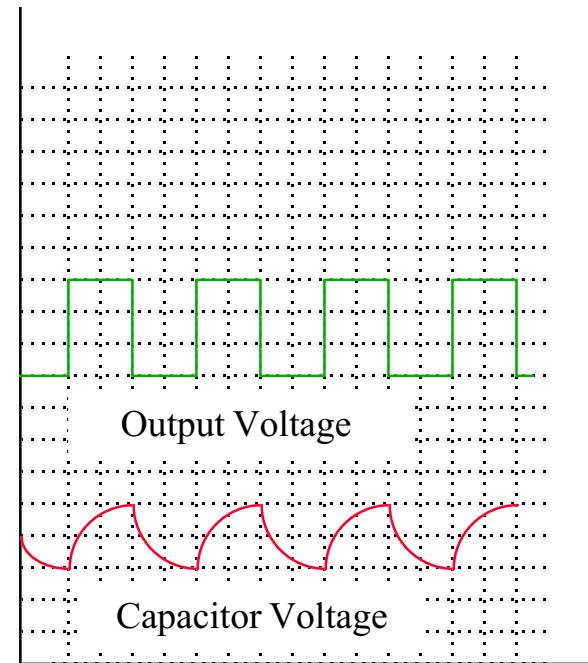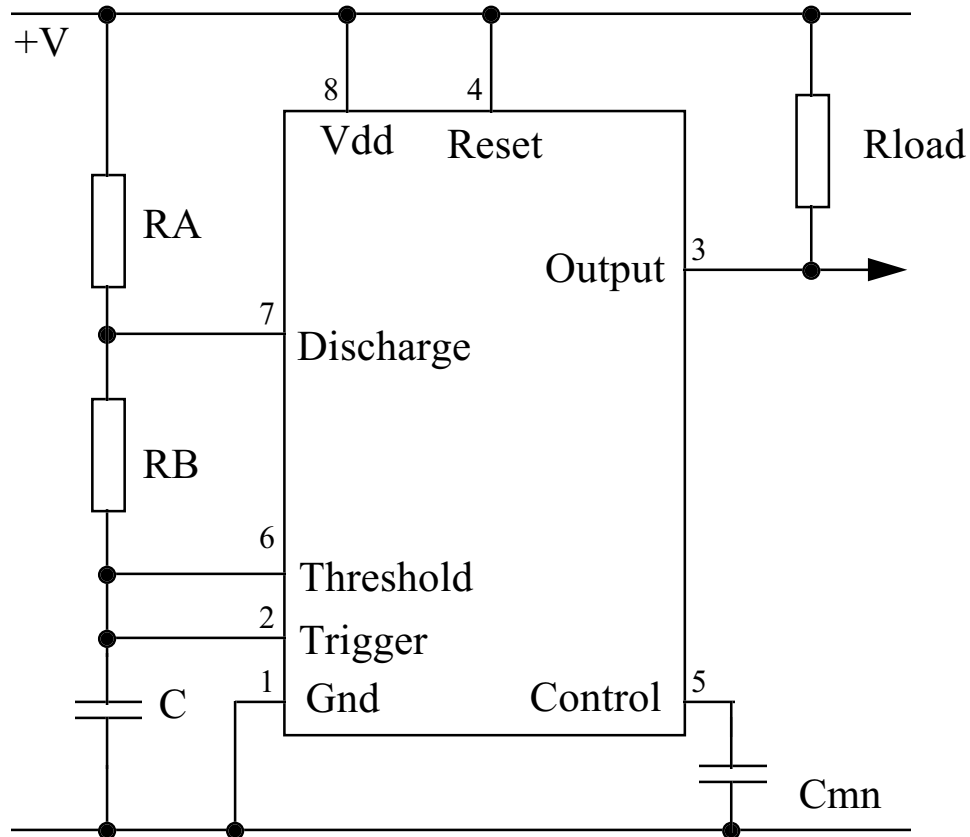


$$\text{Frequency} = 1.44 / (RA + 2RB)C$$

555 Configured as an Astable.

End Slide

Revision Page

<u>Title</u>	BASIC Analogue Electronics.
<u>Author</u>	R. J. Spriggs
<u>Last Update</u>	21/July/2011
<u>Version</u>	4.42
<u>Edit</u>	0373

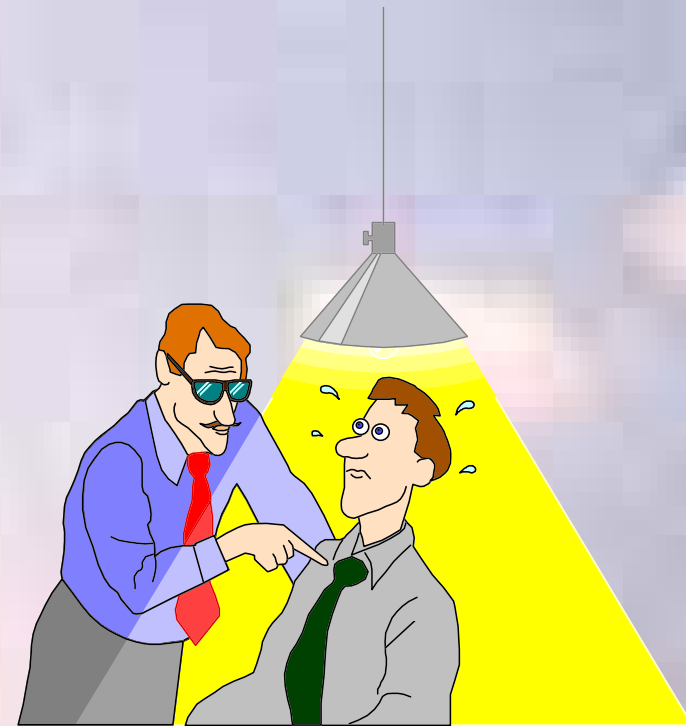

Work in progress