

# BTEC National Coursework.

# Witness Documents

# Witness Statement (Y1).

DICE

- Unit Title
  - ELECTRONICS
- Assignment Reference
  - 2291A
- Title
  - Electronic Dice.
- Task Ref / Description
  - Build/Construct and Test Logic Monitor.
  - Build/Construct and Test Logic Clock/Pulser.
  - Build on Breadboard 1 to 6 Logic Counter.
  - Build on Breadboard Display and Decoder.

# Witness Statement (Y1).

## AMPLIFIER

- Unit Title
  - ELECTRONICS
- Assignment Reference
  - 2291B
- Title
  - Amplifier.
- Task Ref / Description
  - Build/Construct Voltage Amplifier.
  - Build/Construct Power Amplifier.
  - Use of Multimeter.
  - Use of Signal Generator and Oscilloscope.

# Witness Statement (Y1).

## SIMULATION

- Unit Title
  - ELECTRONICS
- Assignment Reference
  - 2291D
- Title
  - Computer Based Electronics.
- Task Ref / Description
  - Simulate Voltage Amplifier.
  - Simulate 1-6 Counter for Dice.
  - TBA.
  - TBA.

# Witness Statement.

## Principles

- Unit Title
  - MICROELECTRONICS
- Assignment Reference
  - 2295A
- Title
  - Micro hardware architecture and principles.
- Task Ref / Description
  - TBA

# Witness Statement (Y1).

Downloading

- Unit Title
  - MICROELECTRONICS
- Assignment Reference
  - 2295B
- Title
  - Micro software/firmware principles.
- Task Ref / Description
  - In and Out (INOUT).
  - Flash (FLASH).
  - Binary Count (BINCO UP/DOWN).
  - Knight Rider (NRIDER).
  - Checkerboard (CHECK)

# Witness Statement.

## Application

- Unit Title
  - MICROELECTRONICS
- Assignment Reference
  - 2295C
- Title
  - Planning, writing, running and testing software.
- Task Ref / Description
  - Produce and document code.
  - Produce efficient compact code.
  - Illustrate code (Selection, Iteration and Modularity).
  - Evaluate code (Report format).



# Witness Statement.

## Interface

- Unit Title
  - MICROELECTRONICS
- Assignment Reference
  - 2295D
- Title
  - Micro hardware interfacing and principles.
- Task Ref / Description
  - TBA

# Witness Statement.

## Interface

- Unit Title
  - Electronics Measurement and Test.
- Assignment Reference
  - 2299B1
- Title
  - Specifications and Test Procedures.
- Task Ref / Description
  - Regulated Power Supply Test Procedure.
  - Split Rail Converter Test Procedure.
  - Fixed Gain Amplifier Test Procedure.
  - Attenuator and Buffer Test Procedure.

**Write ups and**  
**Submission**  
**Documents**

# Write up and Submission Documents.

- Structure of **General/ Formal Report** Submissions :-
  - Title of Submission
  - Introduction
    - What this report's content will identify.
  - Description containing :-
    - What I have done, why and how I did it.
    - What I expected and what happened.
  - Circuit and/or Diagrams (Photographs of constructions).
  - Results
    - in Tabular and/or graphical form(with annotated points of interest).
    - Calculation you may have used.
  - Conclusion / Comments
    - The implication and I have understood from my submission work.

# Write up and Submission Documents.

- Structure of **Laboratory Report** Submissions :-
  - **Experiment Title:** Title and Date.
  - **Objective:** Briefly .. What you intend to do or achieve.
  - **Equipment used:** Record any serial numbers of used equipment.
  - **Method:** Consisting of :-
    - **Circuit and/or Diagrams** (Photographs of constructions etc.).
    - **Description** containing :-
      - What I have done, how I did it.
      - What I expected and what happened.
  - **Results**
    - in Tabular and/or graphical form(with annotated points of interest).
  - **Conclusion / Comments**
    - The implication and I have understood from my experimental work.

# Write up and Submission Documents.

## DICE

- Witness statements for :-
  - Build a 1 to 6 Logic Counter on Breadboard.
  - Build a Display and Decoder on Breadboard.
- Submissions required on Test Equipment
  - Testing the Pulser using a Multimeter.
    - Identify and measure voltages (Table of results)
  - Testing the Clock using an Oscilloscope.
    - Draw precise grid, show waveforms of clock output, record scope settings, Mark key points of interest.
  - Testing the counter/s using your Logic probe.
    - show waveforms of outputs and time relationships.
    - show truth table of expected/actual outputs.

# Write up and Submission Documents.

## AMPLIFIER

- Witness statements for :-
  - Build a Voltage Amplifier on Breadboard.
  - Build a Power Amplifier on Breadboard.
- Submissions required on Test Equipment
  - Testing the Amplifier using a Multimeter.
    - Identify and measure voltages (produce table of results)
  - Testing the Amplifier using both an Oscilloscope and a Signal Generator.
    - Sketch using a precise grid, waveforms of signals, include (inputs , outputs and time) relationships, record scope settings, mark key points of interest on diagrams.

# Write up and Submission Documents.

## SIMULATION

- Witness statements for :-
  - Demonstration Simulation of Voltage Amplifier.
  - Demonstration Simulation of 1-6 Counter for Dice.
- Hardcopy Submissions required
  - Screen shots of Simulations and Calculations.
    - Identify and measure voltages etc... tables of results.
    - Record Digital waveforms/levels showing state table.
    - Plot Voltage and Frequency graph of the Amplifier.
    - As above when gain is changed \* 3.
    - Mini Report relating Simulated and Practical results for voltage amplifier.



# Write up and Submission Documents.


## DOWNLOAD

- Witness statements for :-
  - Demonstration of Download of all programmes.
- Hardcopy Submissions required
  - Source code fully commented.
    - Fully commented source codes that you have downloaded.
    - Flowcharts of programme operation.
    - Structured walk through of programme code (**fully annotated** (show principle register and memory locations and how they change)).

# **Build and Test LOGIC Probe**

# Logic Probe Board.

IC1 = CMOS 4049

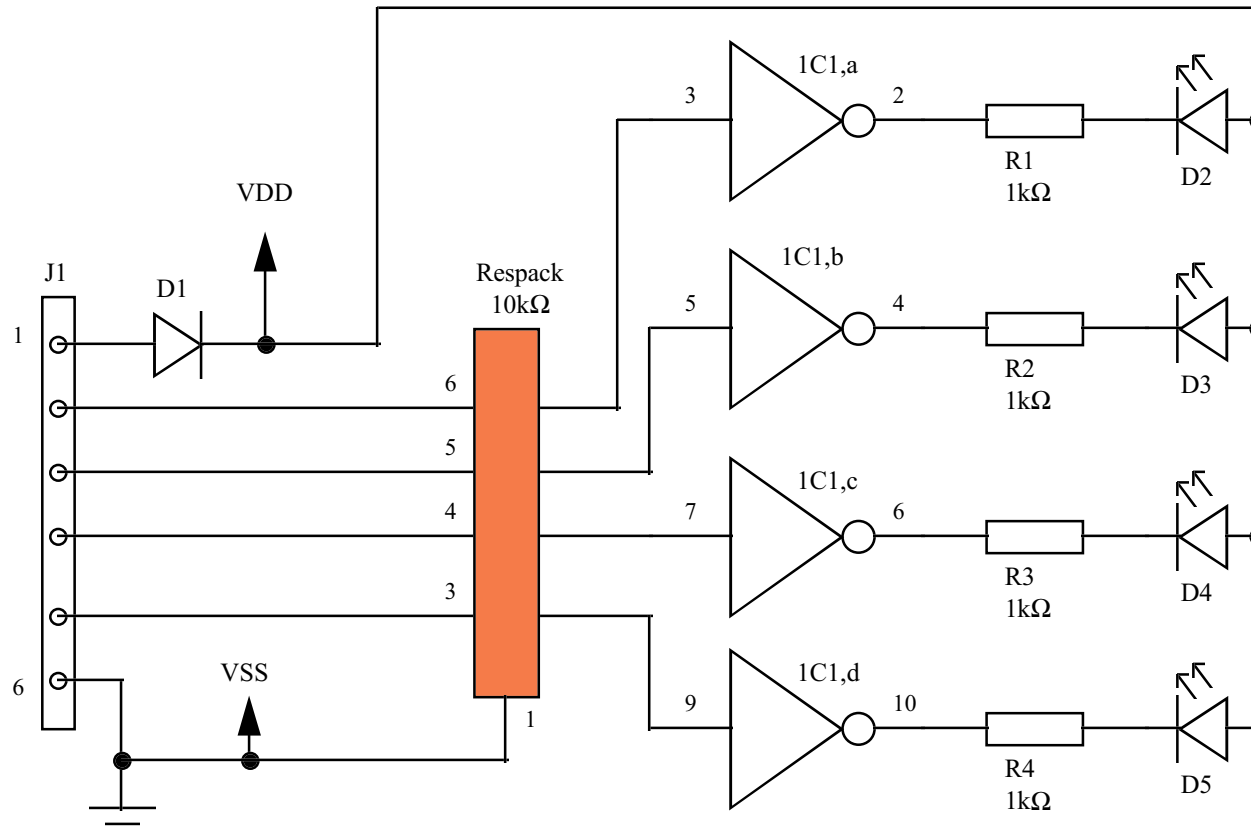


Circuit of  
Logic Probe  
Board

IC1,8 = VSS

IC1,1 = VDD

# Logic Probe Board.

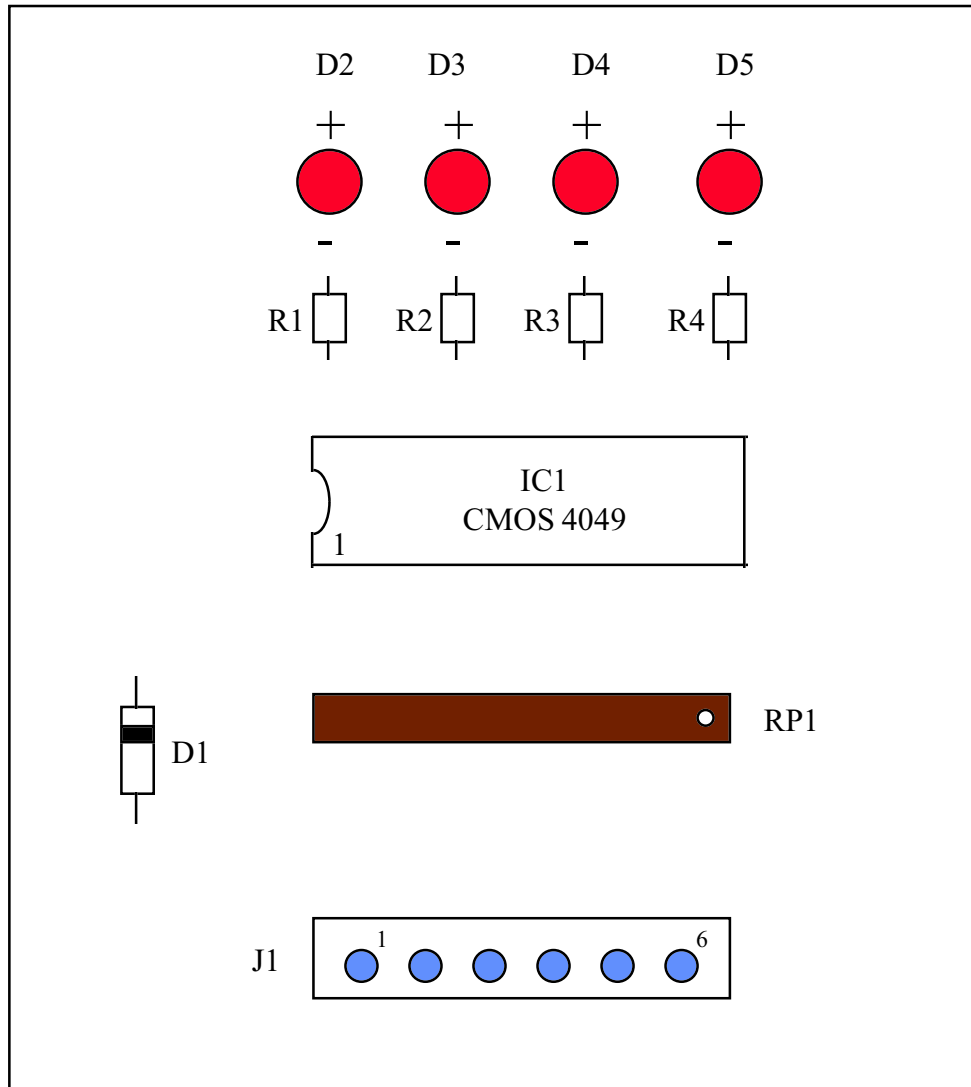

Layout of  
Probe Board

# Testing Logic Probe.

- Check all solder connections (Shiny, Concave, No lumps bumps holes)
- Have all links and Components been made/located in the correct place the right way round.
- Verify that all tracks connect to the correct place and no additional short circuits added.
- Ensure IC1 is **NOT** yet fitted.

# Testing Logic Probe.


- Track checking Verify
- S/C checks
- J1,6 → IC1,8
- IC1,1 → D1,- → D2,+ → D3,+ → D4,+ → D5,+
- IC1,3 → J1,2
- IC1,5 → J1,3
- IC1,7 → J1,4
- IC1,9 → J1,5
- O/C Checks
- D1,+ → D1,- (also check D2,D3,D4 and D5 same way)
- IC1,1 → IC1,8

# Testing Logic Probe.

- Resistance Checks (No Power applied).
- Resistance Checks
- Verify J1,2  $\rightarrow$  J1,6 = 10k $\Omega$
- Verify J1,3  $\rightarrow$  J1,6 = 10k $\Omega$
- Verify J1,4  $\rightarrow$  J1,6 = 10k $\Omega$
- Verify J1,5  $\rightarrow$  J1,6 = 10k $\Omega$
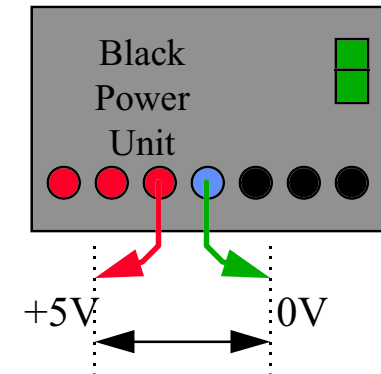
# Testing Logic Probe.


- Apply power to board if previous tests OK.
  - Pin J1,1 = +5V , Pin J1,6 = 0V
- S/C checks
- Short J1,6 → IC1,2 (LED D2 should Light)
- Short J1,6 → IC1,4 (LED D3 should Light)
- Short J1,6 → IC1,6 (LED D4 should Light)
- Short J1,6 → IC1,10 (LED D5 should Light)
- Remove Power from board
- If all previous tests OK insert IC1 into board.




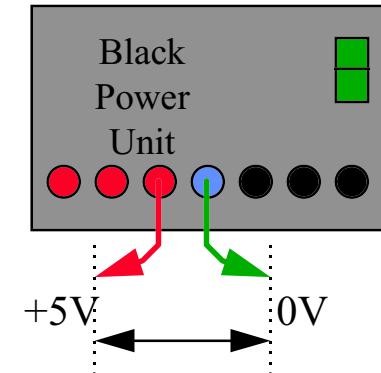
# Testing Logic Probe.


- Verify full functionality.
- Apply power to board +5V.
  - Pin J1,1 = +5V , Pin J1,6 = 0V
- All LEDs should be **OFF**.
- **S/C checks**
- Short J1,1 → J1,2 (LED D2 should Light)
- Short J1,1 → J1,3 (LED D3 should Light)
- Short J1,1 → J1,4 (LED D4 should Light)
- Short J1,1 → J1,5 (LED D5 should Light)
- If all LEDs light with above tests the board is fully functional.



# Build and Test a Debounced Switch and Clock Board


# Level and Clock Board.

IC1 = CMOS 4093

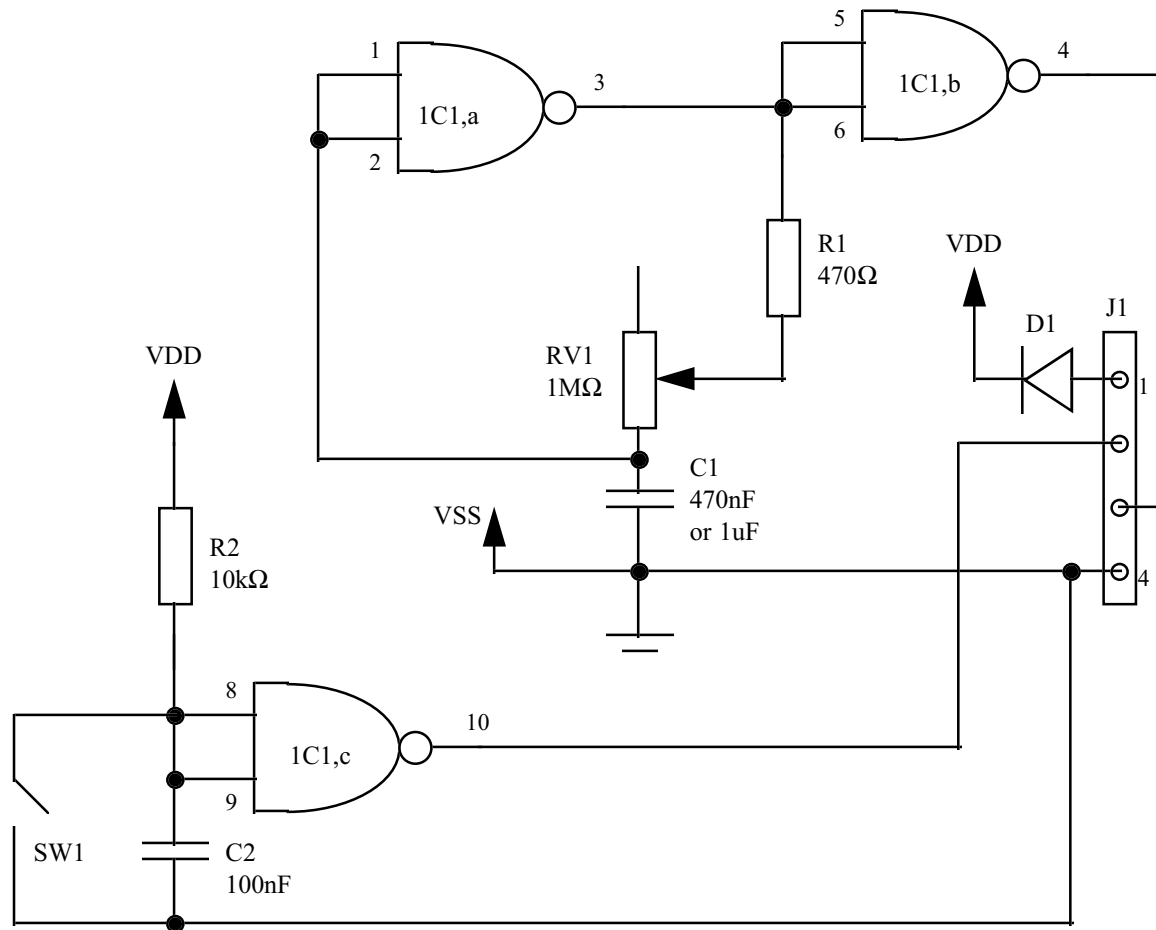

Circuit of  
Level and Clock  
Board

# Level and Clock Board.

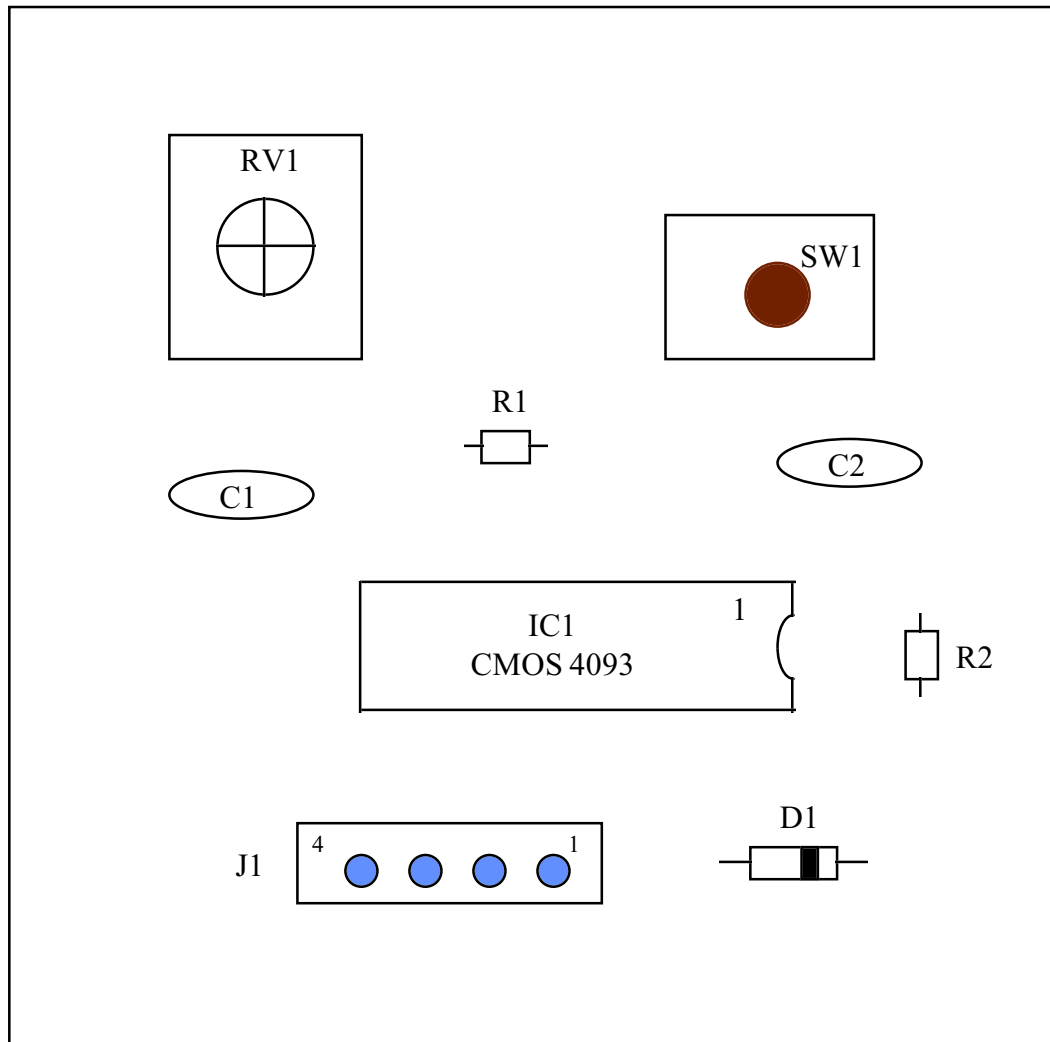

Layout of  
Level and Clock  
Board

# Level and Clock Board.

- Track checking Verify
- S/C checks
- J1,4 → IC1,7
- IC1,1 → IC1,2
- IC1,5 → IC1,6
- IC1,8 → IC1,9
- IC1,4 → J1,3
- IC1,10 → J1,2
- O/C Checks
- IC1,7 → IC1,14

# Level and Clock Board.

- Resistance Checks (No Power applied).
- Resistance Checks
- Verify J1,4 → IC1,8 = S/C when Switch Pressed
- Verify IC1,14 → IC1,8 = 10kΩ
- If all previous tests OK insert IC1 into board.


# Level and Clock Board.

- Functional Checks (Power applied).
- Power Applied Checks
- Connect +5V to J1,1 and Ground / 0V to J1,4
- Connect using your Logic probe : J1,2 to one channel and J1,3 to another channel. (Remember to Power your Probe).
- Press Switch and the selected channel should come on.
- Rotate RV1 until other channel flashes about once a second. Other extreme end RV1, LED appears always on
- Check Maximum frequency and waveshape of clock signal [Use Scope] (Sketch Waveforms) {Calculate Frequency}
- If LEDs light correctly with above tests and waveforms are square then the Level and Clock board is fully functional.

# Digital Dice Assignment




# Digital Dice Block Diagram.

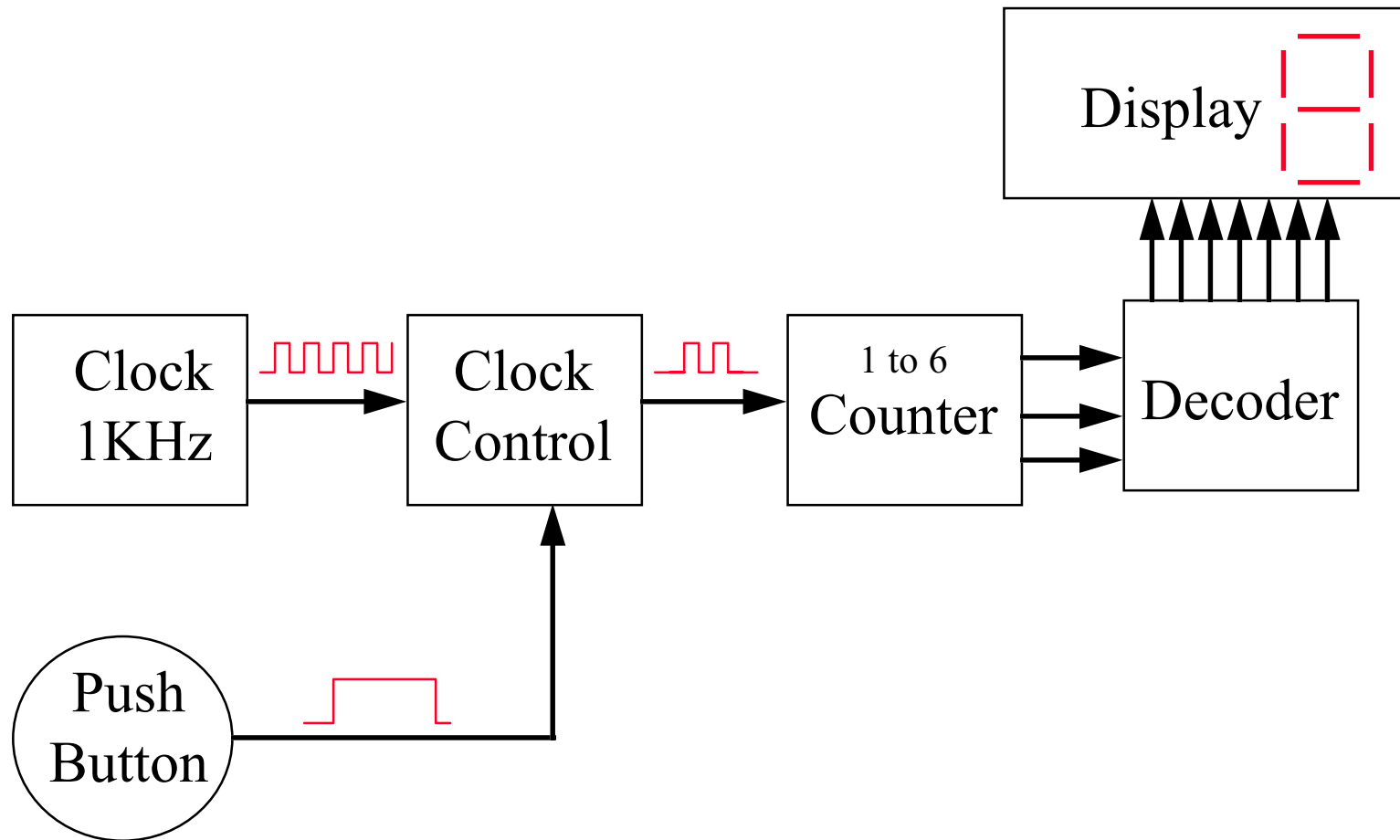

# **Build and Test a 0 to 7 Counter**
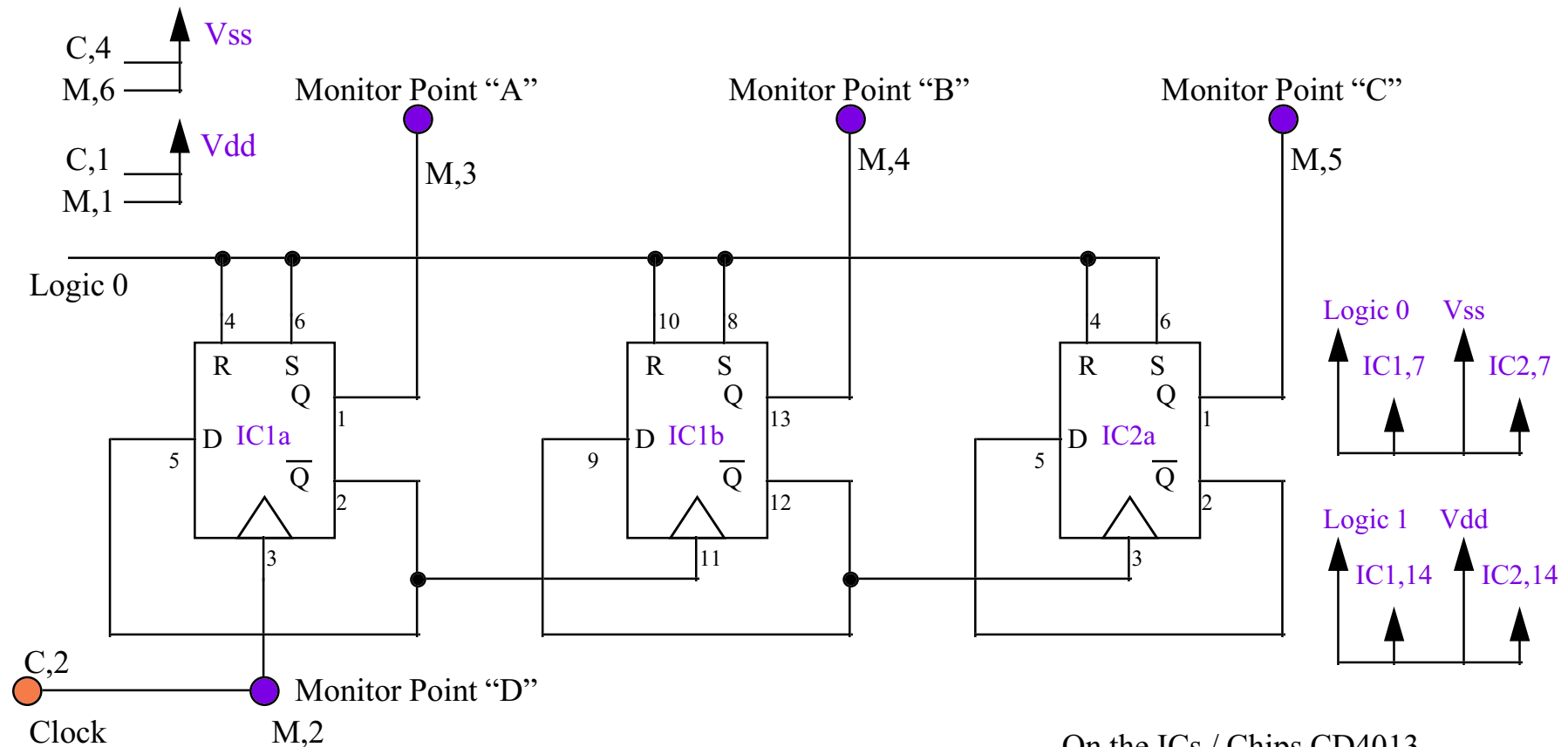
# Digital Dice Counter Circuit.

Monitor and Record what happens at the monitor points.




## Basic Counter Circuit

On the ICs / Chips CD4013  
 Connect **VSS** to Ground/0V  
 Connect **VDD** to +5V

# Digital Dice Counter Circuit.

Record/Indicate what happens at the monitor points.

Typical example of waveform recording.

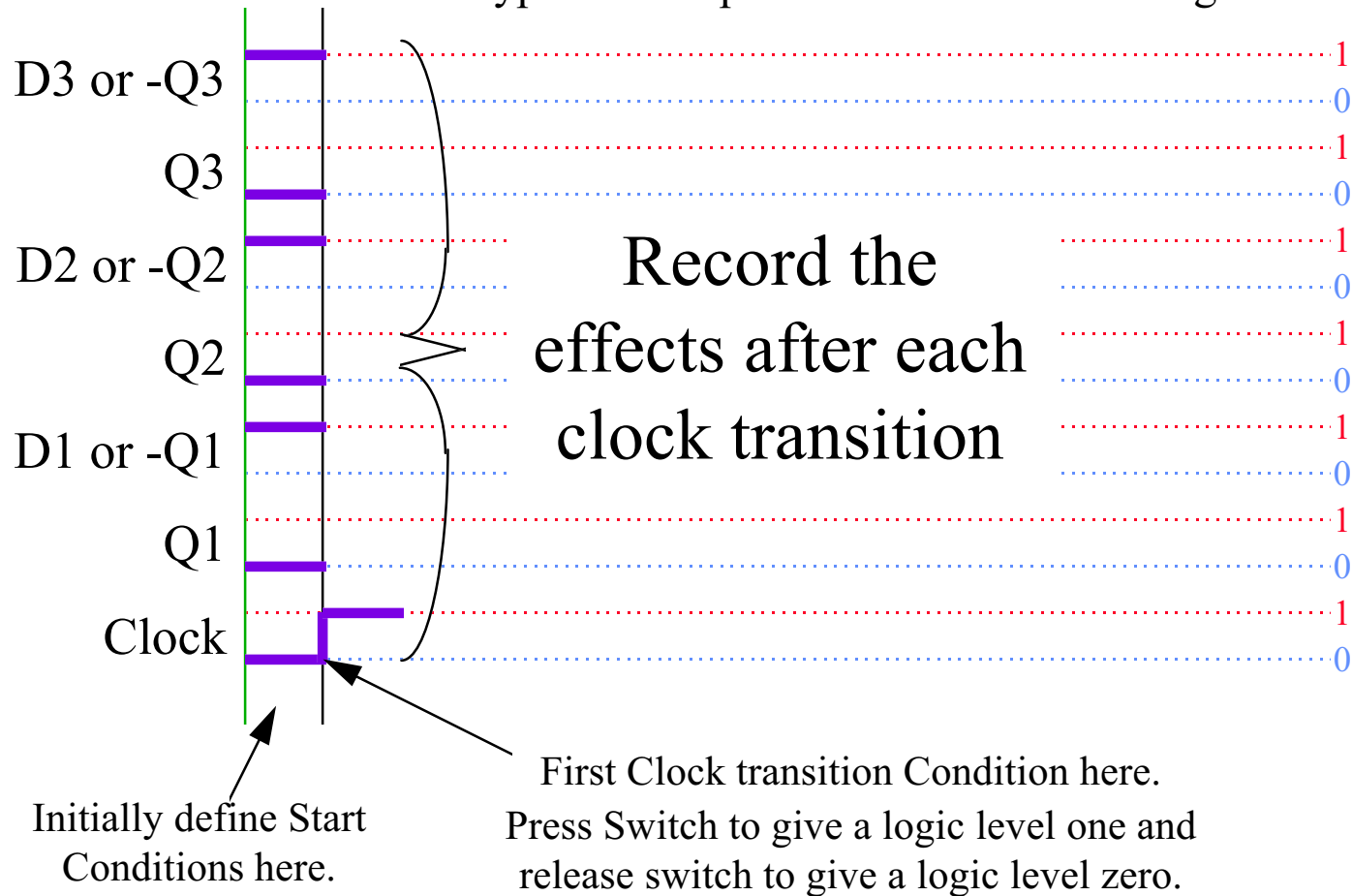


# Formal Method to Create Bread Board Layouts

# General Construction Concepts.

- Draw circuit diagram.
- Allocate names to all devices.
- Use Data sheets to identify pins of devices.
- Build a Resource list.
- Use Circuit Diagram to build NET List.
- Use NET list to wire up Breadboard.

**Process complete**

# Digital Dice Counter Circuit.

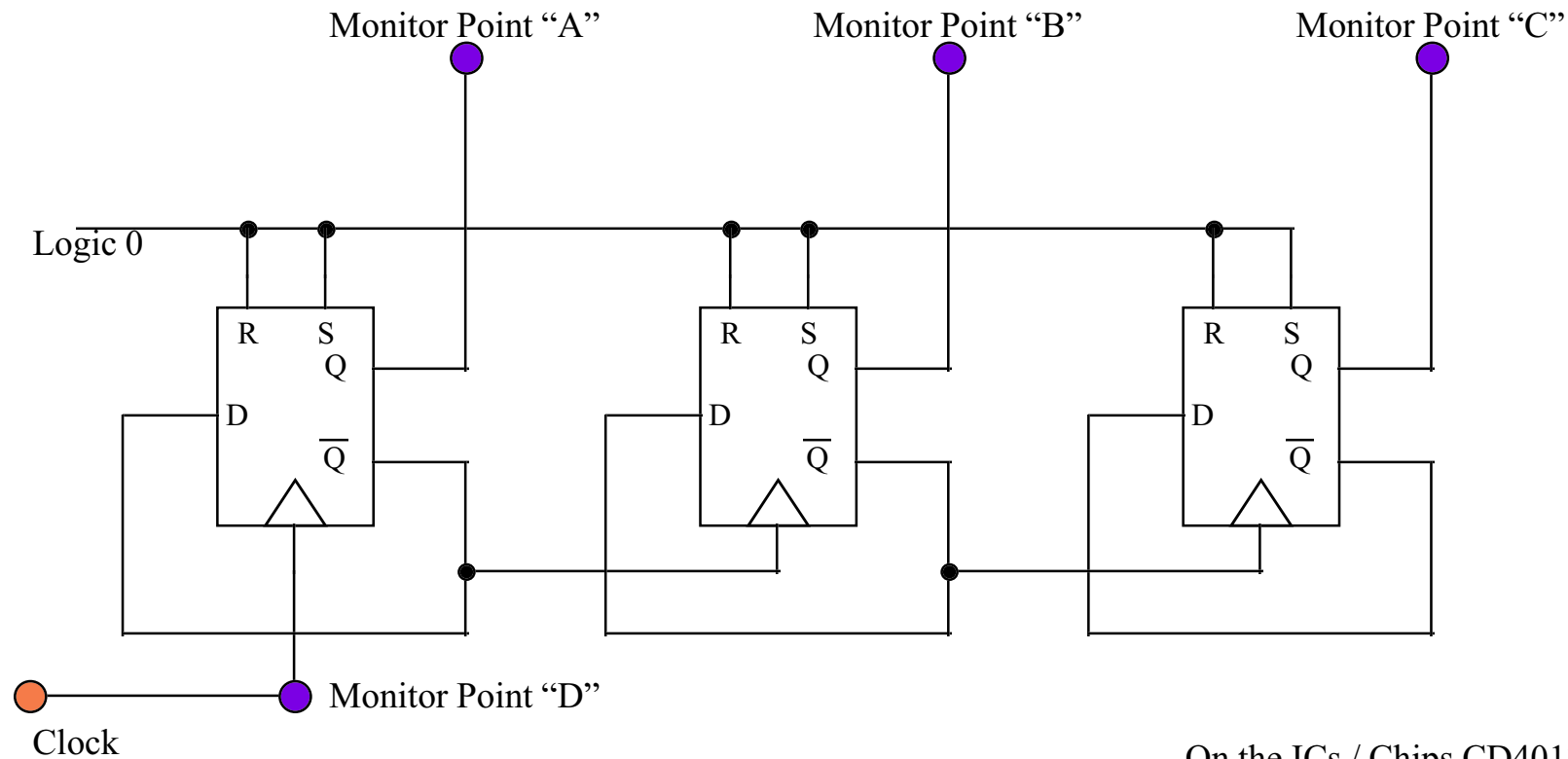

## Basic Counter Circuit


On the ICs / Chips CD4013  
Connect **VSS** to Ground/0V Logic 0  
Connect **VDD** to +5V Logic 1

# General Construction Concepts.

- Draw circuit diagram.
- Allocate Names to all devices.
- Use Data sheets to identify pins of devices.
- Build a Resource list.
- Use Circuit Diagram to build NET List.
- Use NET list to wire up Breadboard.



# Digital Dice Counter Circuit.

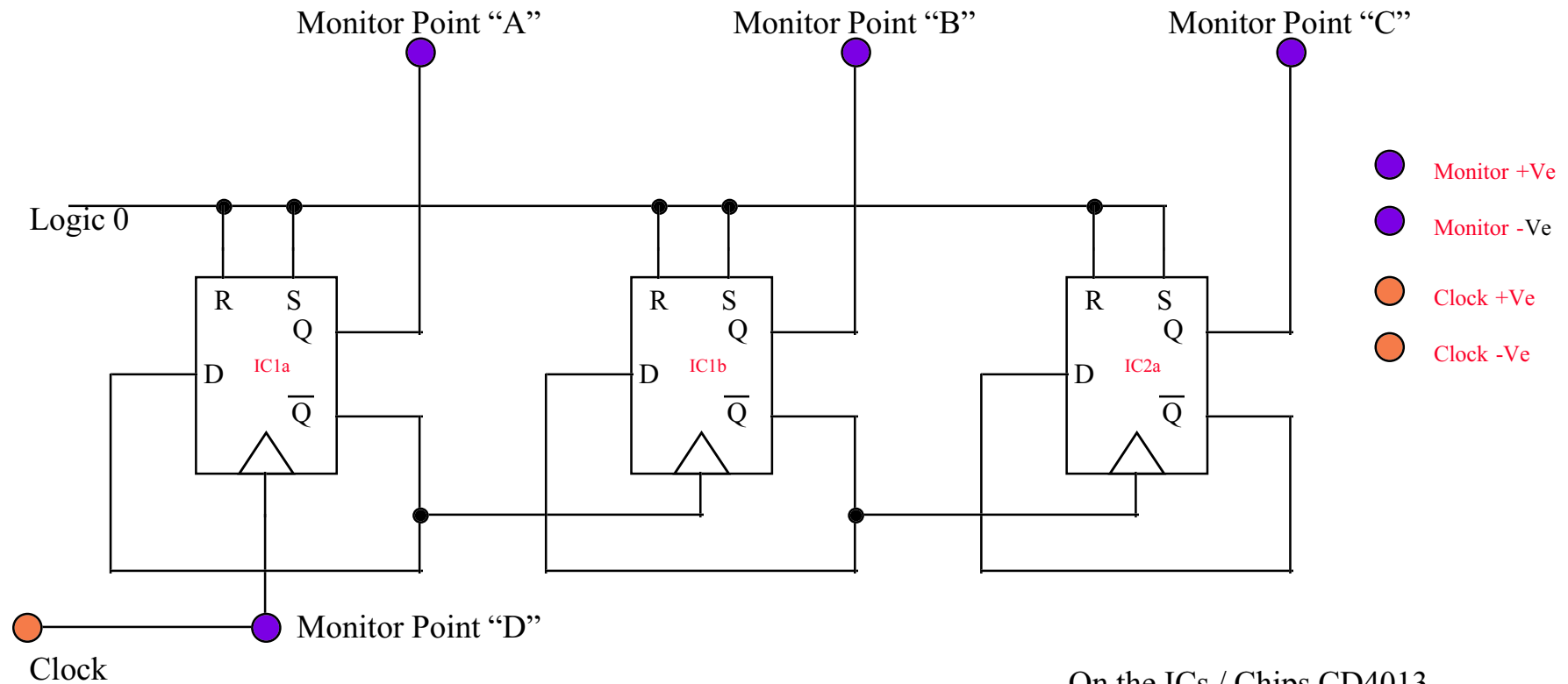

## Basic Counter Circuit


On the ICs / Chips CD4013  
 Connect **VSS** to Ground/0V Logic 0  
 Connect **VDD** to +5V Logic 1

# General Construction Concepts.

- Draw circuit diagram.
- Allocate Names to all devices.
- Use Data sheets to identify pins of devices.
- Build a Resource list.
- Use Circuit Diagram to build NET List.
- Use NET list to wire up Breadboard.
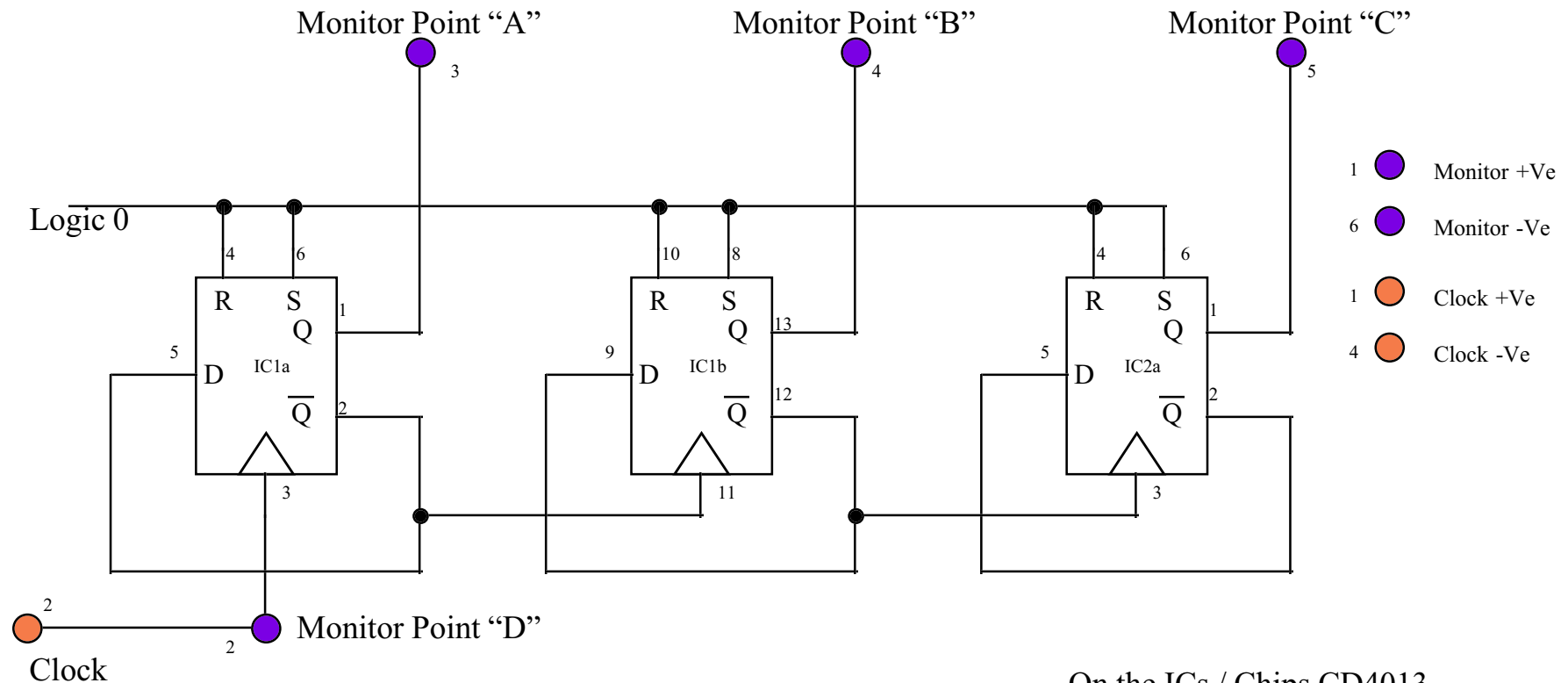
# Digital Dice Counter Circuit.

Monitor and Record what happens at the monitor points.



## Basic Counter Circuit

On the ICs / Chips CD4013  
 7 7 Connect VSS to Ground/0V Logic 0  
 14 14 Connect VDD to +5V Logic 1

# General Construction Concepts.

- Draw circuit diagram.
- Allocate Names to all devices.
- Use Data sheets to identify pins of devices.
- Build a Resource list.
- Use Circuit Diagram to build NET List.
- Use NET list to wire up Breadboard.

# Resource List.

- | <u>Name</u>    | <u>ID</u> | <u>Pins</u> | → | →  |   |   |    |    |
|----------------|-----------|-------------|---|----|---|---|----|----|
| • Count 1,2    |           | IC1         | 1 | 2  | 3 | 4 | 5  |    |
|                |           |             | 6 | 7  | 8 | 9 | 10 | 11 |
|                |           |             |   |    |   |   |    | 12 |
|                |           |             |   |    |   |   |    | 13 |
|                |           |             |   |    |   |   |    | 14 |
| • Count 3      |           | IC2         | 1 | 2  | 3 | 4 | 5  | 6  |
|                |           |             | 7 | 14 |   |   |    |    |
| • Monitor      | M         |             | 1 | 2  | 3 | 4 | 5  | 6  |
| • Clock        | C         |             | 1 | 2  | 4 |   |    |    |
| • Power +      | +5V       |             | 1 |    |   |   |    |    |
| • Power/Ground | 0V        |             | 1 |    |   |   |    |    |

# General Construction Concepts.

- Draw circuit diagram.
- Allocated names to all devices.
- Use Data sheets to identify pin of devices.
- Build a Resource list.
- Use Circuit Diagram to build NET List.
- Use NET list to wire up Breadboard.

# NET List.

- Name                      ID      Pins and Connections
- Power +V                      +5V      +5V,1 →      IC1,14 →      IC2,14 →  
    C,1      →      M,1
- Ground/Logic 0              0V      0V,1 →      IC1,7 →      IC2,7 →  
    M,6      →      C,4      →      IC1,4      →      IC1,6      →      IC1,10  
    →      IC1,8      →      IC2,4      →      IC2,6
- Clock                              CLK      C,2      →      IC1,3      →      M,2
- Net                                      #1      IC1,5 →      IC1,2 →      IC1,11
- Net                                      #2      IC1,9 →      IC1,12 →      IC2,3
- Net                                      #3      IC1,1 →      M,3
- Net                                      #4      IC1,13 →      M,4
- Net                                      #5      IC2,1 →      M5
- Net                                      #6      IC2,2 →      IC2,5


# General Construction Concepts.

- Draw circuit diagram.
- Allocated names to all devices.
- Use Data sheets to identify pin of devices.
- Build a Resource list.
- Use Circuit Diagram to build NET List.
- Use NET list to wire up Breadboard.




# Circuit Notes

# Circuit Notes.

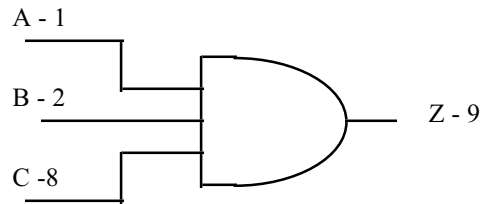

CD4073

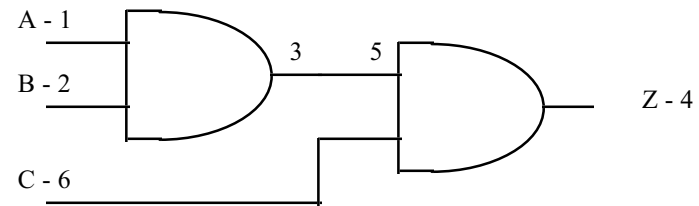


CD4081

Converting Two 2 Input AND gates  
into a 3 Input AND Gate

# **Build and Test a 1 to 6 Counter**
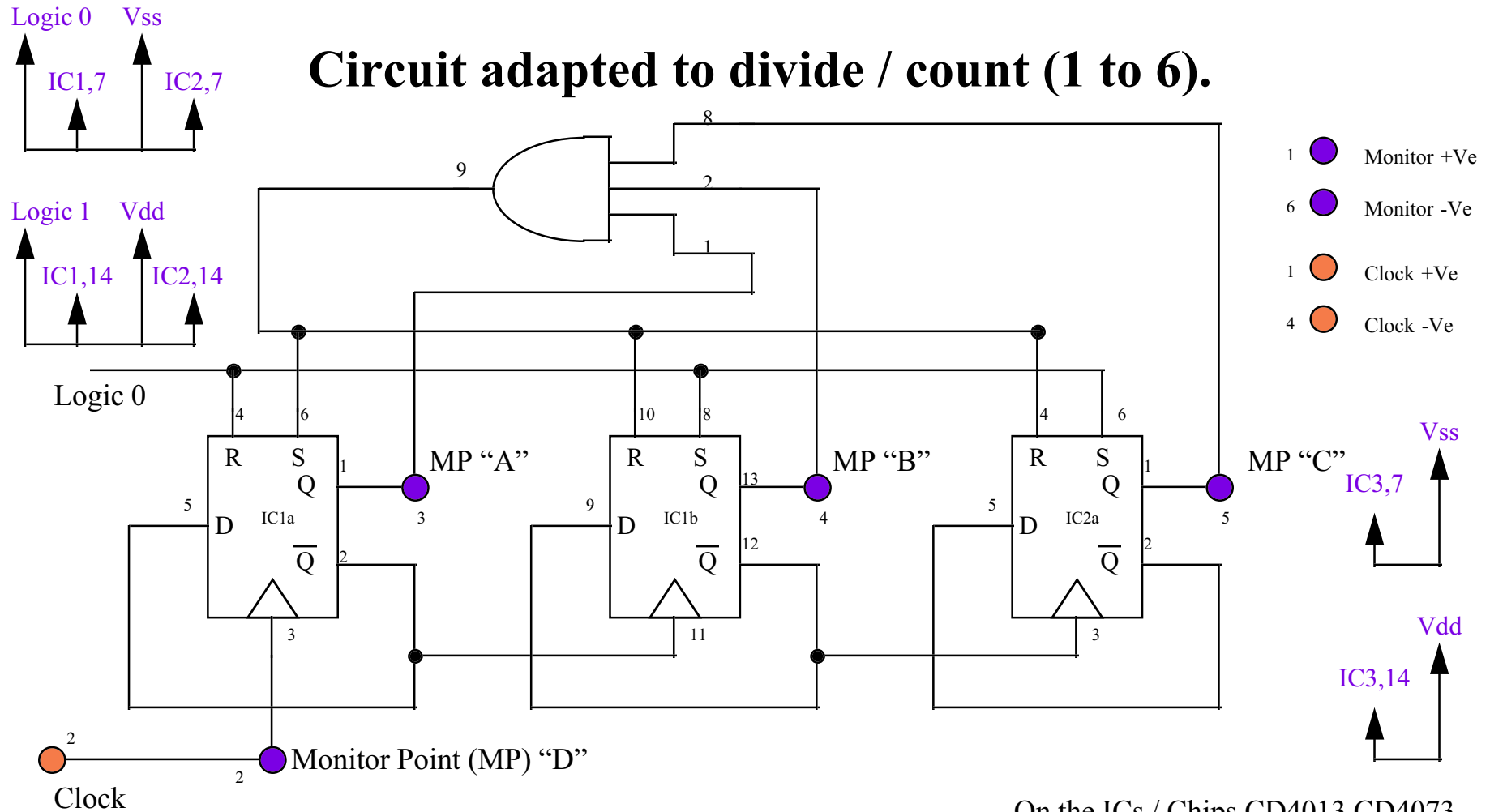
# Digital Dice Counter Circuit.

Circuit adapted to divide / count (1 to 6).



## Modified Counter Circuit


On the ICs / Chips CD4013 CD4073  
Connect **VSS** to Ground/0V Logic 0  
Connect **VDD** to +5V Logic 1

# Circuit Notes.

- 1 to 6 Counter Board
  - Connection on U1:A,Q will go to your Logic Monitor pin M3.
  - Connection on U1:B,Q will go to your Logic Monitor pin M4.
  - Connection on U2:A,Q will go to your Logic Monitor pin M5.
  - Note U3:A may be constructed from 2 separate AND gates.
  - $VDD = +5V$  and  $VSS = 0V$

**Build and describe**  
**Operation of a**  
**Display / Decoder**

# Display / Decoder.

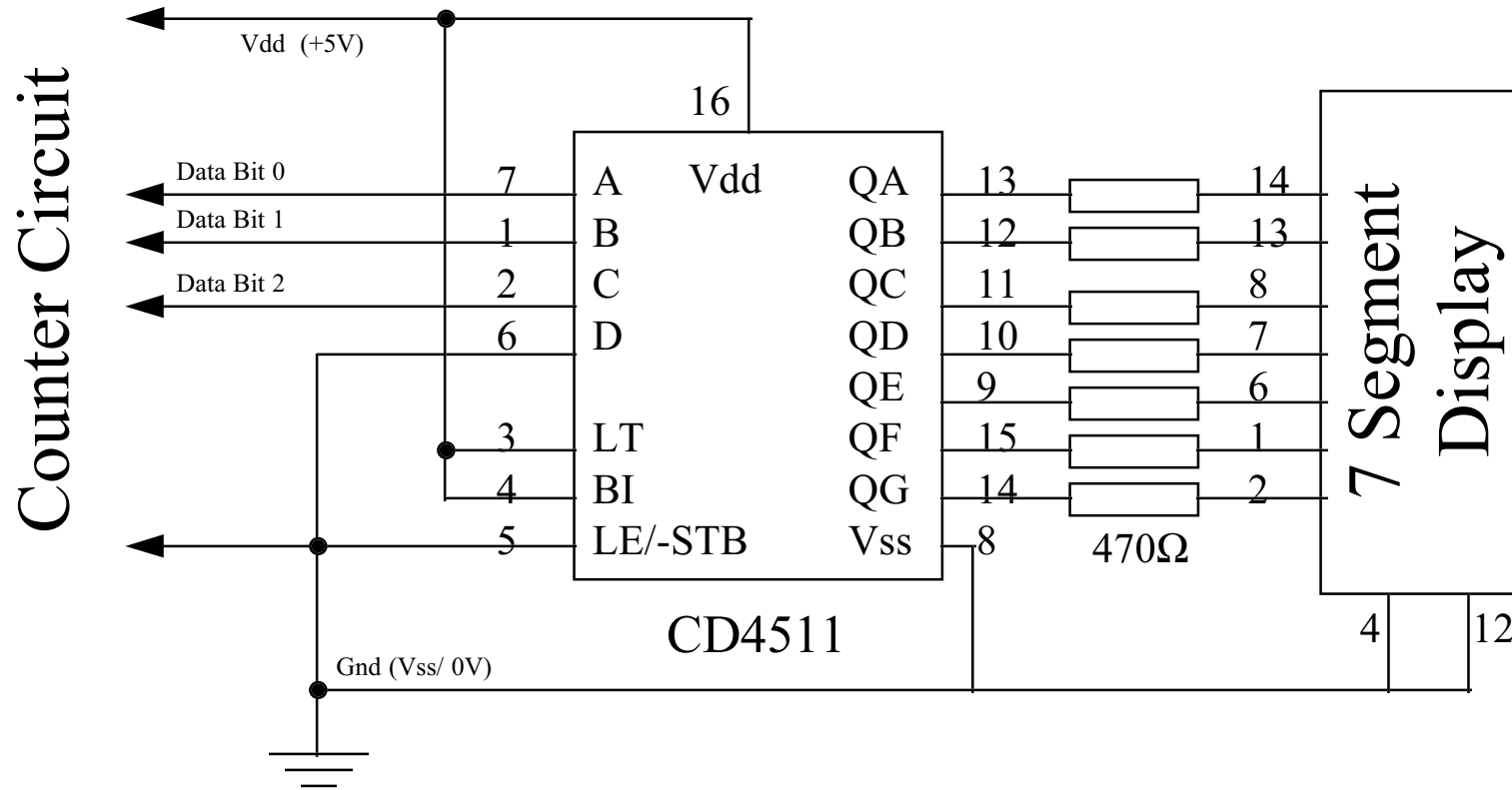



Circuit diagram for the Decoder - Display

# Circuit Notes.

- Decoder / Display Board
  - Data Bit 0 will link to Q1 or QA on your counter.
  - Data Bit 1 will link to Q2 or QB on your counter.
  - Data Bit 2 will link to Q3 or QC on your counter.
  - U1,Pin 5 (LE/-STB) connects to Ground Vss.
  - U1,Pin 3 (LT) and U1,Pin 4 (BI) connect to Vdd.
  - Vdd = +5V and Vss = 0V



# Display / Decoder.

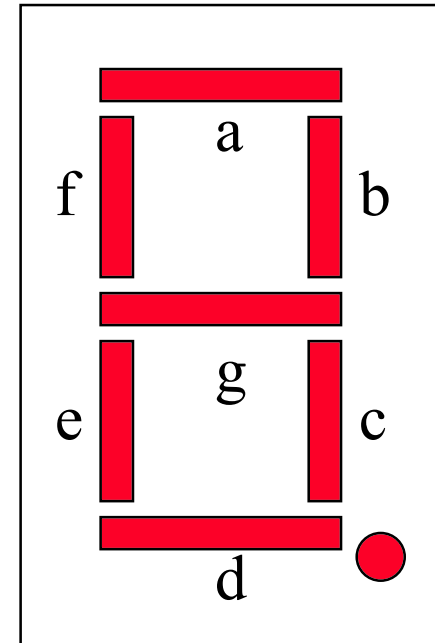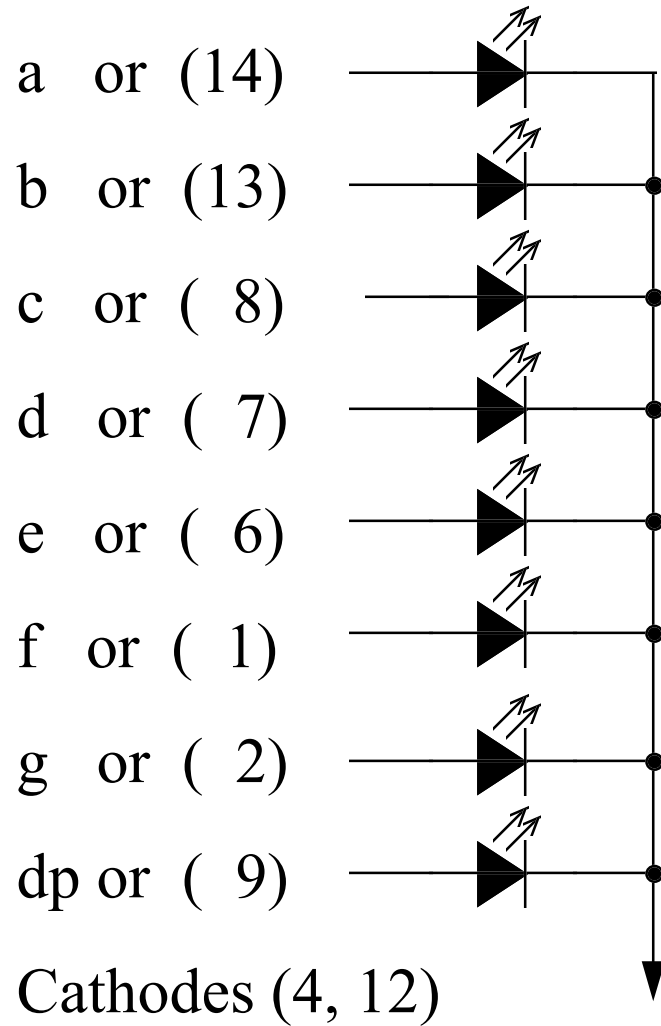


N/c Pins are (3,5,10 and 11)

**(The Common Cathode) Seven Segment Display.**

**Build and describe  
Operation of a  
Roll Dice Circuit**


# Circuit Notes.

## Theory

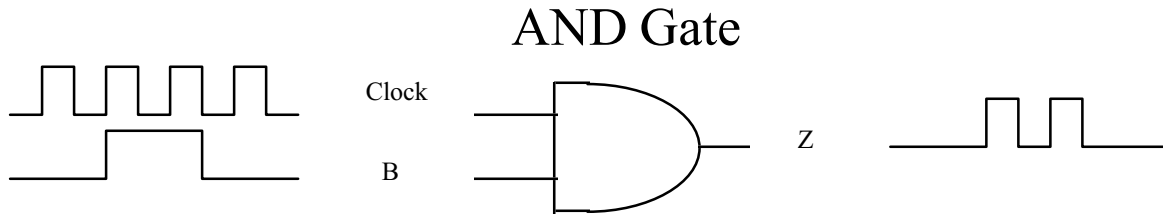



A	B	Z
0	0	0
1	0	0
0	1	0
1	1	1

A	B	Z
Clock	0	0
Clock	1	Clock

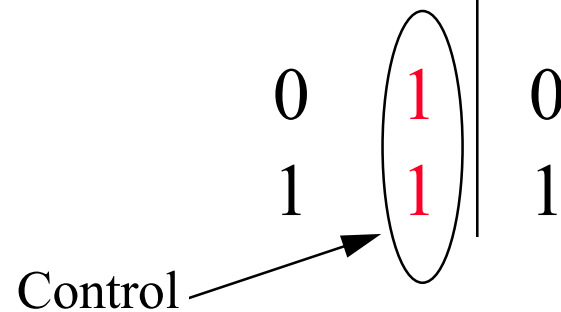

Circuit to Gate  
or control the  
flow of pulses.


# Circuit Notes.

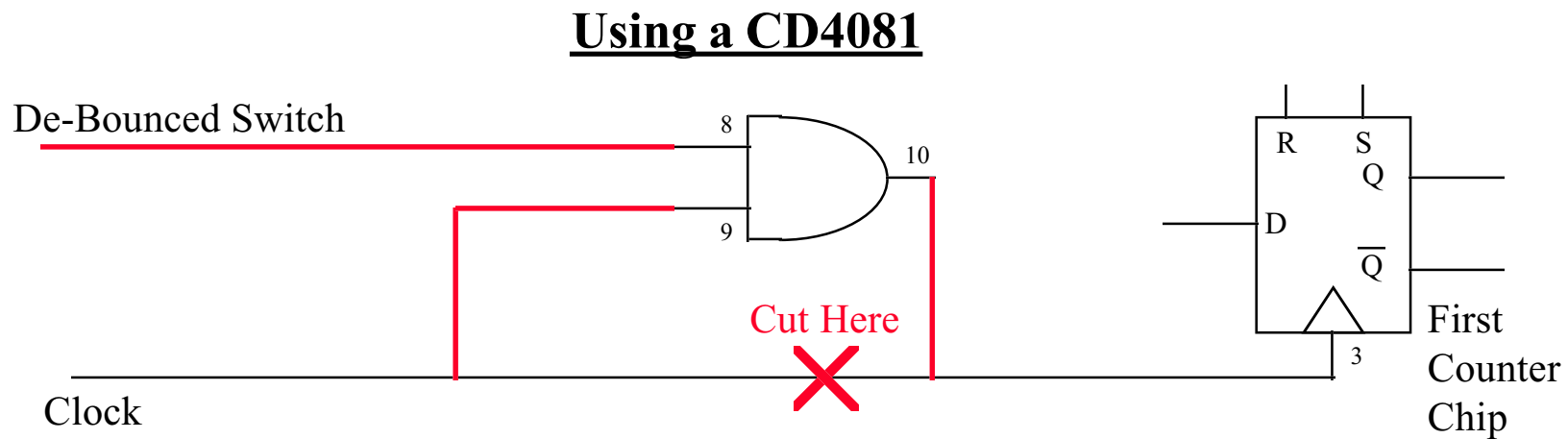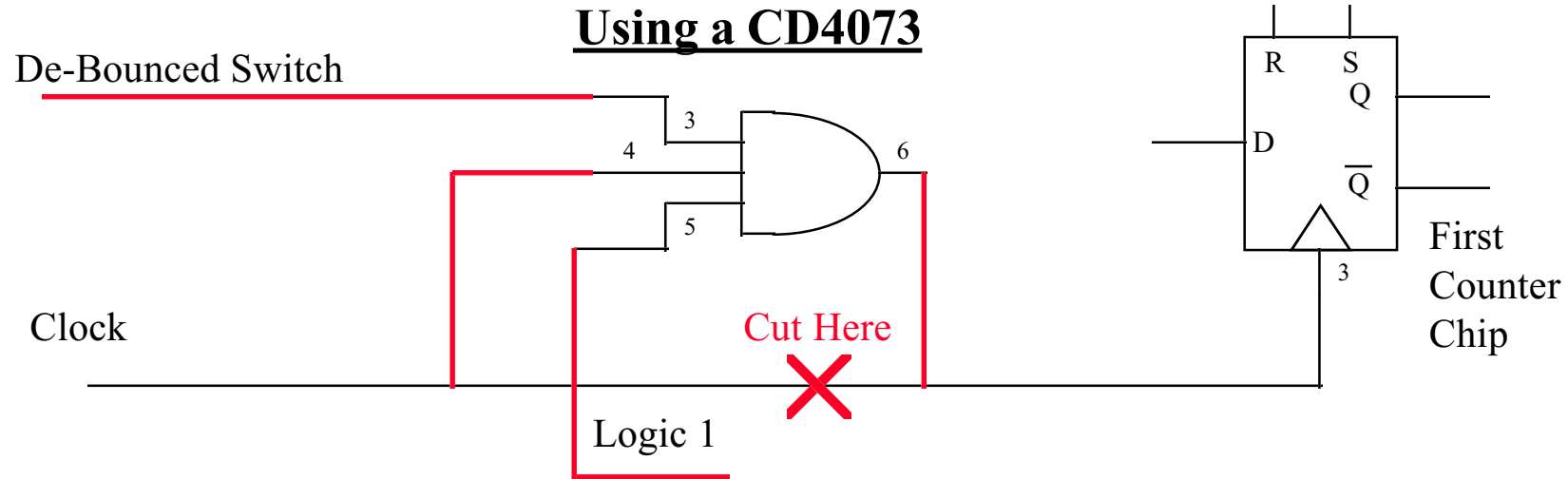

Adding the Roll Dice function.


# Amplifier

# The Amplifier.

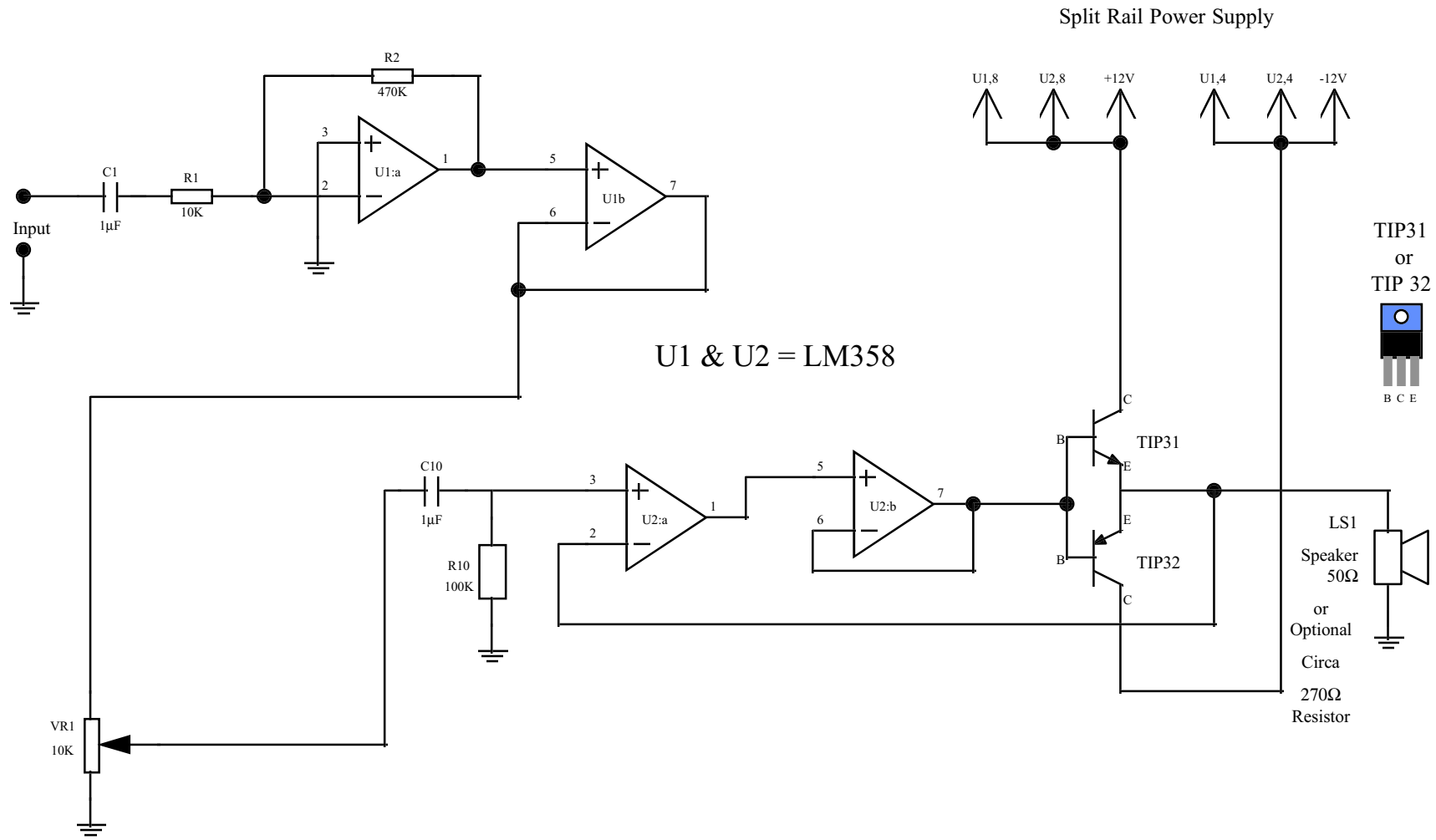


# The Amplifier (Final Design).

# The Amplifier.

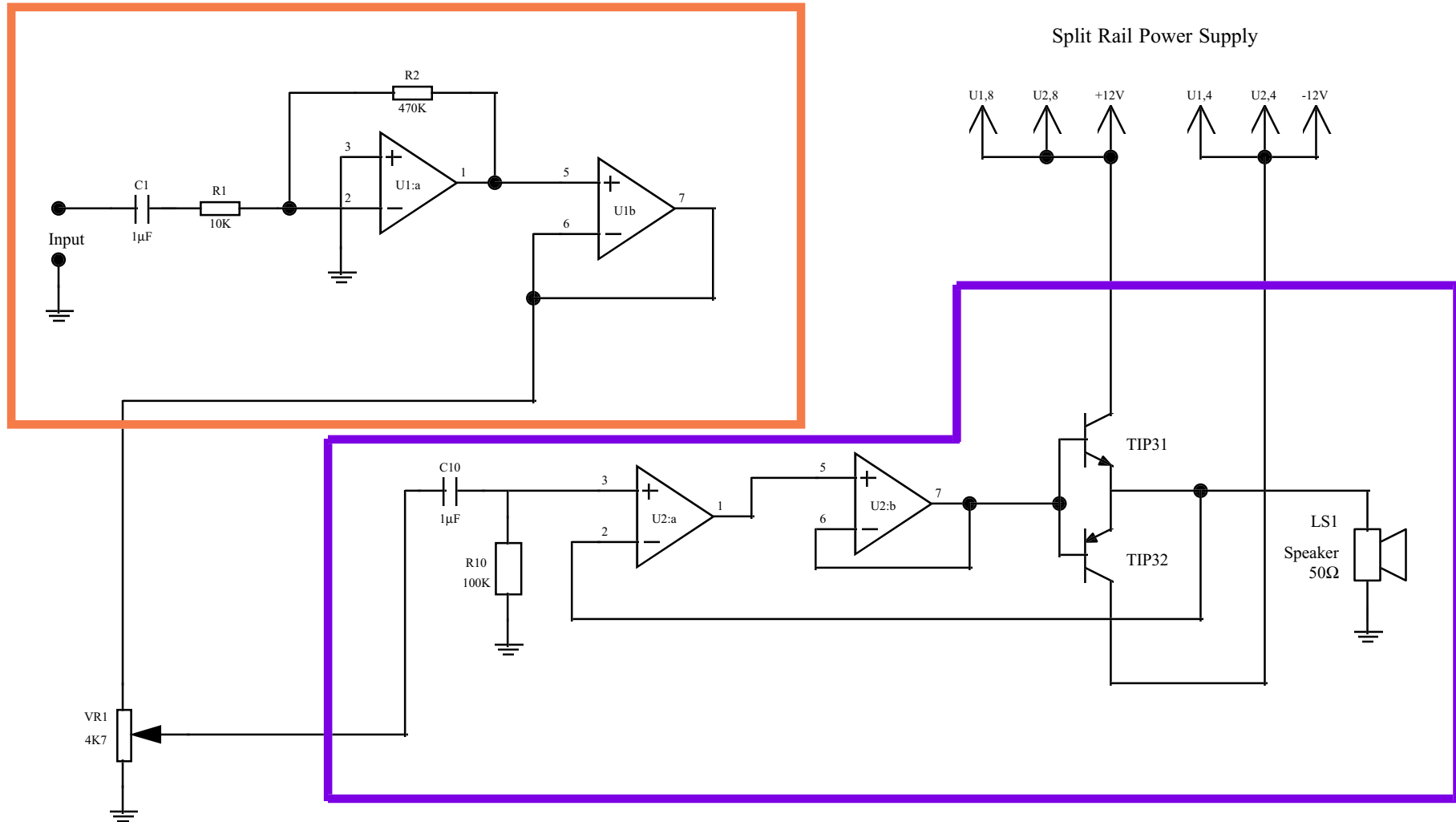

## The Amplifier (Module Design).


# Amplifier Theory.

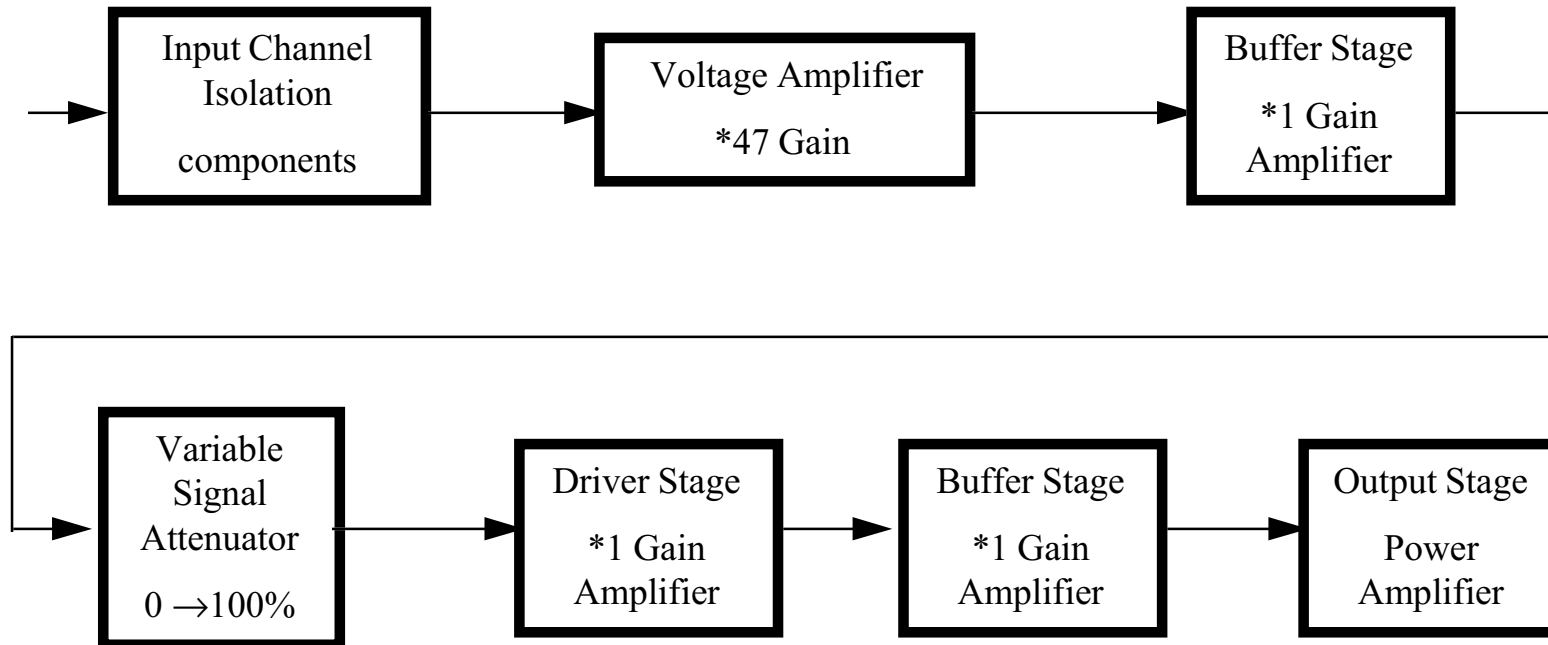

Block Diagram.




# The Amplifier.

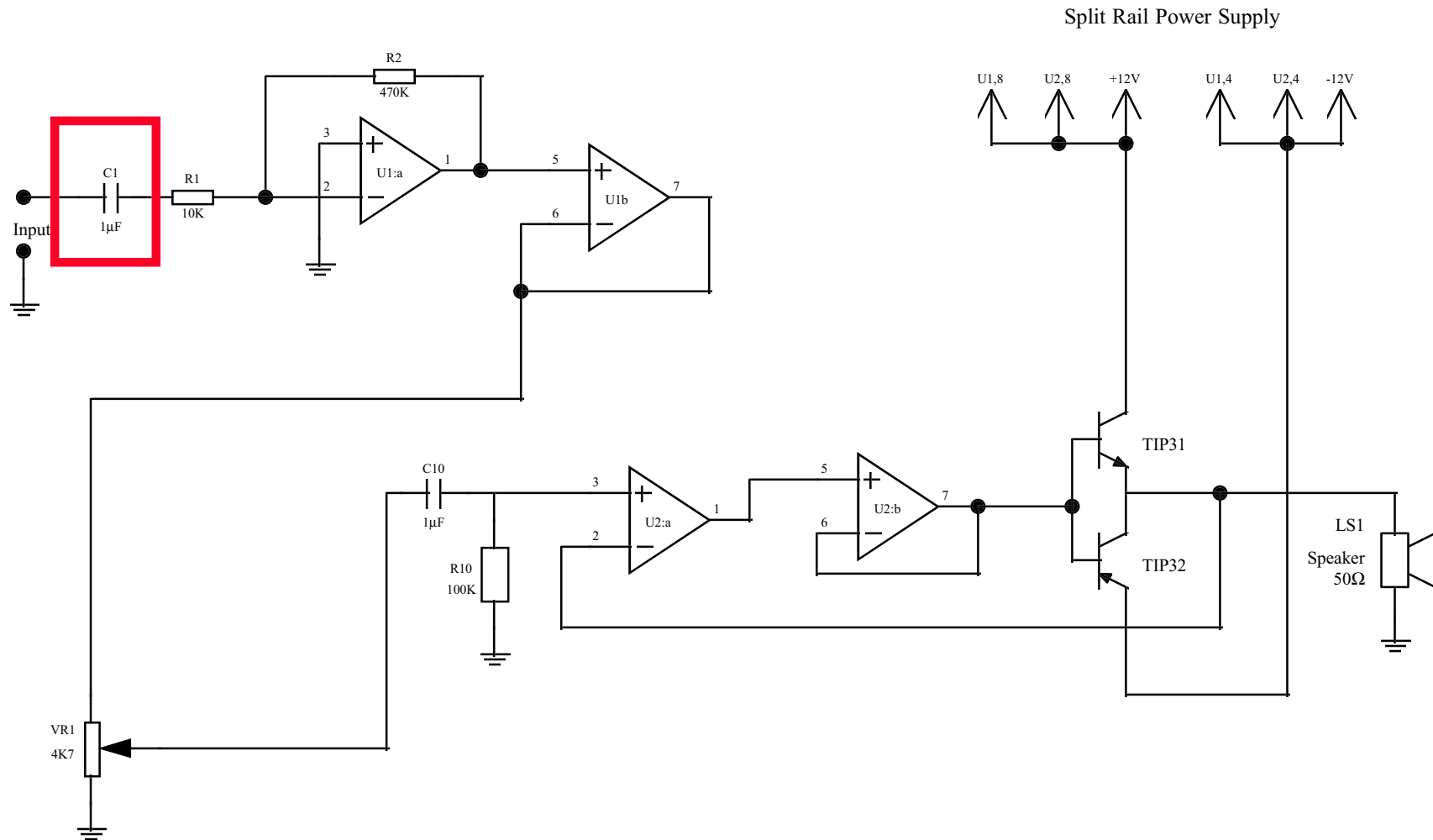

**Capacitor coupling (DC Block).**

# The Amplifier.

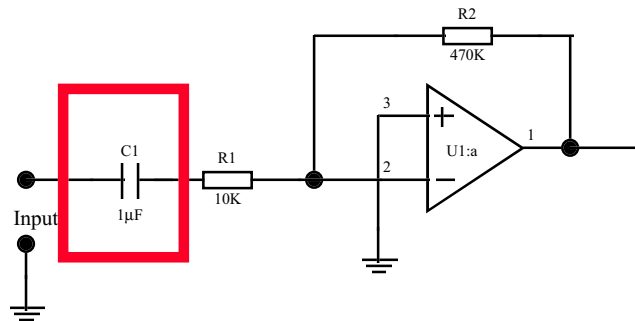

The Coupling Capacitor reactance


$$X_c = \frac{1}{2\pi FC}$$

$$F = 100\text{Hz and } C = 1\mu\text{F}$$

$$X_c = \frac{1}{2 * \pi * 100 * 10^{-6}} = \frac{10^6}{2 * \pi * 100} = ?$$

**Capacitor coupling (DC Block).**

# The Amplifier.

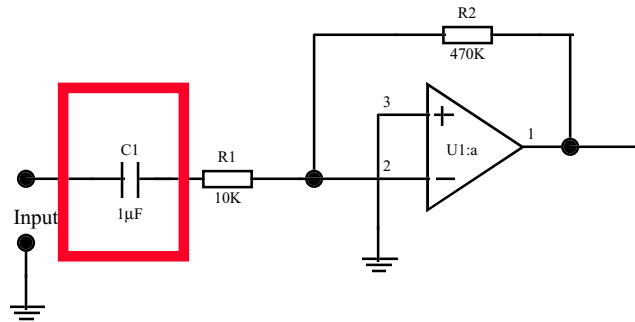

The Coupling Capacitor reactance

$$X_c = \frac{1}{2\pi FC}$$


$$F = 100\text{Hz and } C = 1\mu\text{F}$$

$$X_c = \frac{1}{2 * \pi * 100 * 10^{-6}} = \frac{10^6}{2 * \pi * 100} = 1591\Omega$$

**So what if  $F = 10\text{KHz}$ .**

**Capacitor coupling (DC Block).**

# The Amplifier.

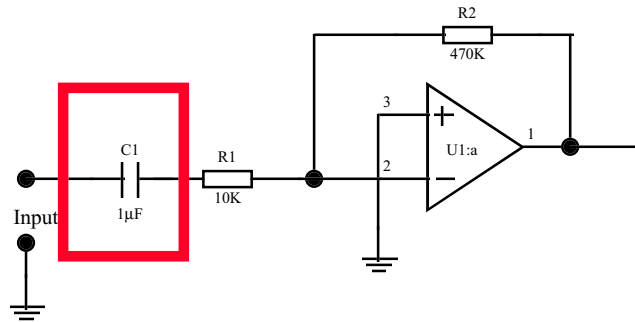

The Coupling Capacitor reactance


$$X_c = \frac{1}{2\pi FC}$$

$$F = 100\text{Hz and } C = 1\mu\text{F}$$

$$X_c = \frac{1}{2 * \pi * 100 * 10^{-6}} = \frac{10^6}{2 * \pi * 100} = 15.91\Omega$$


**Capacitor coupling (DC Block).**

# Amplifier Theory.

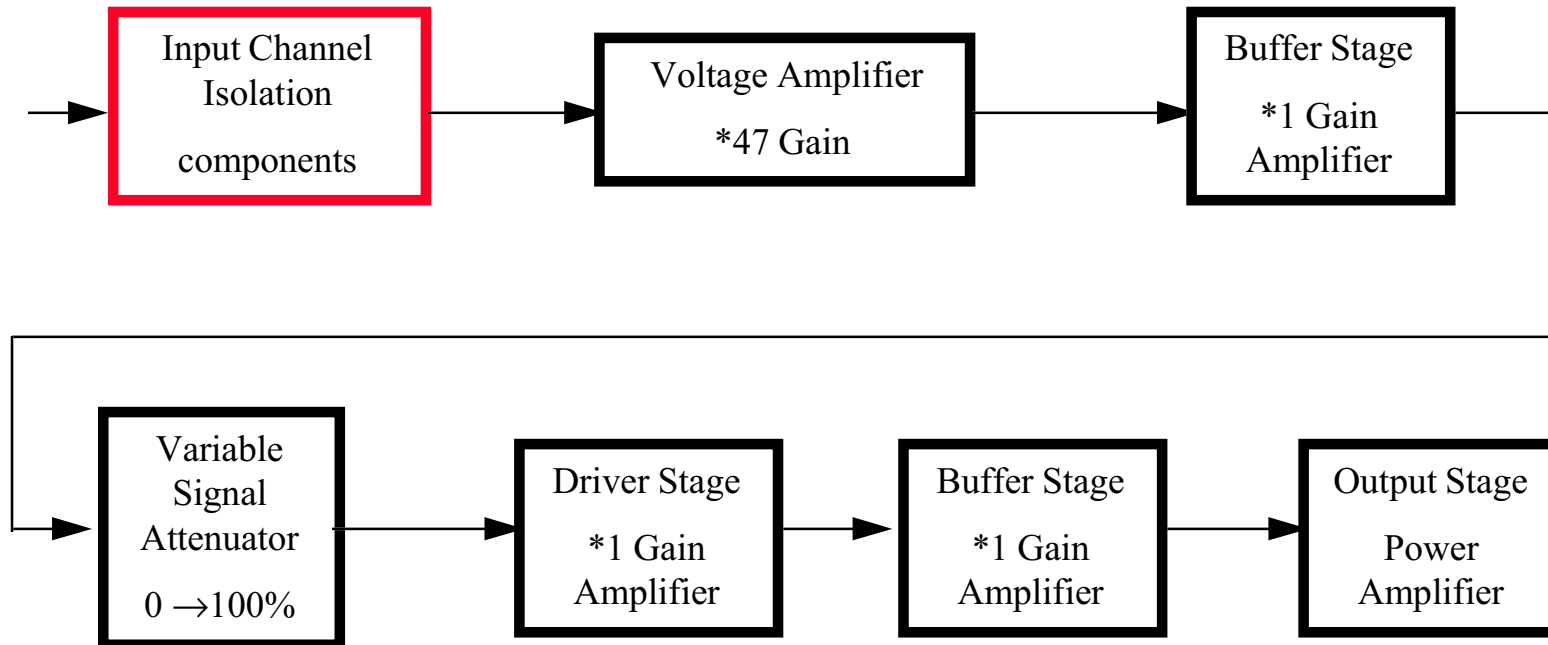

Block Diagram.


# The Amplifier.

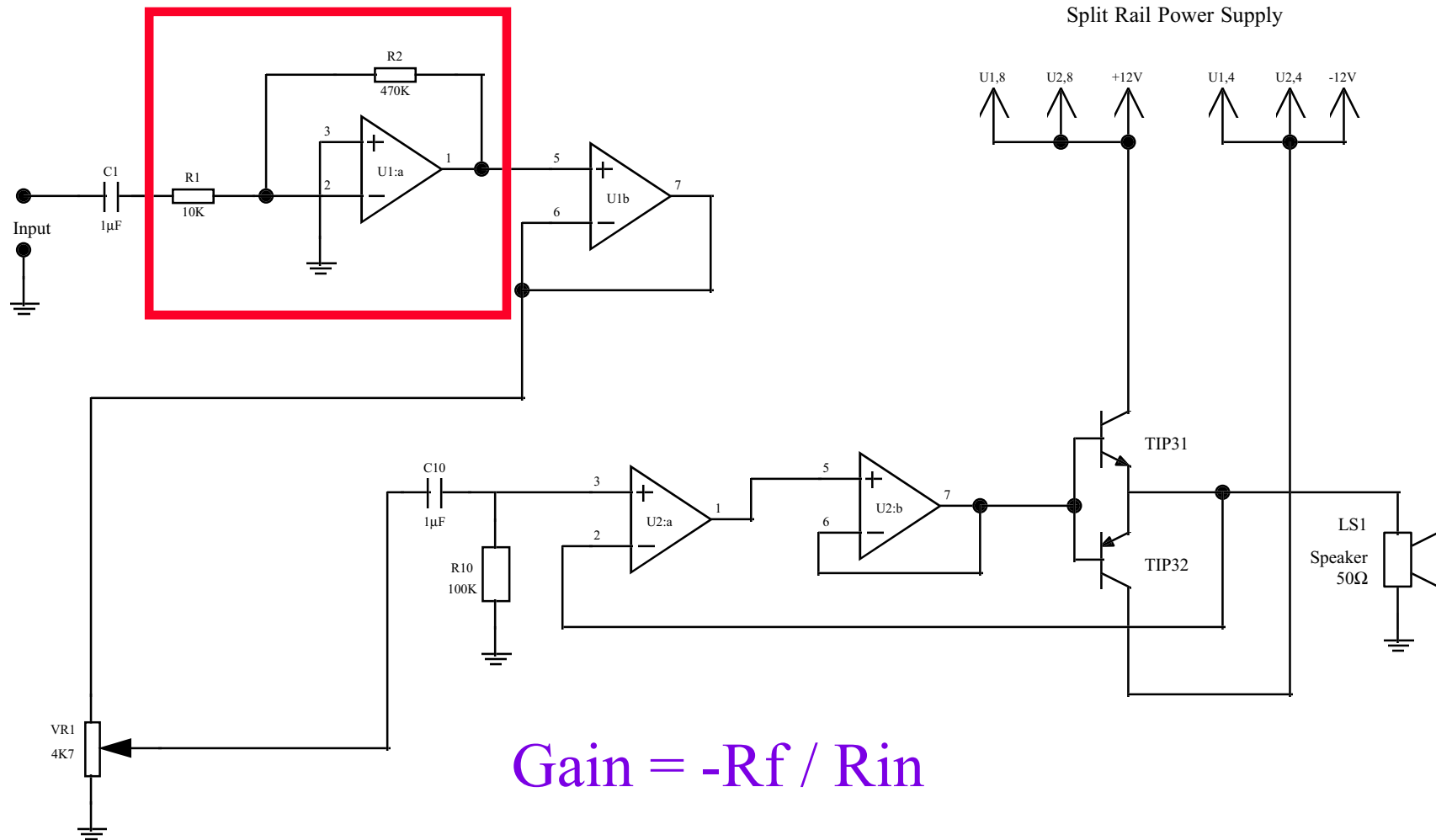

$$\text{Gain} = -R_f / R_{in}$$


**Signal Amplifier circuit.**

# Amplifier Theory.

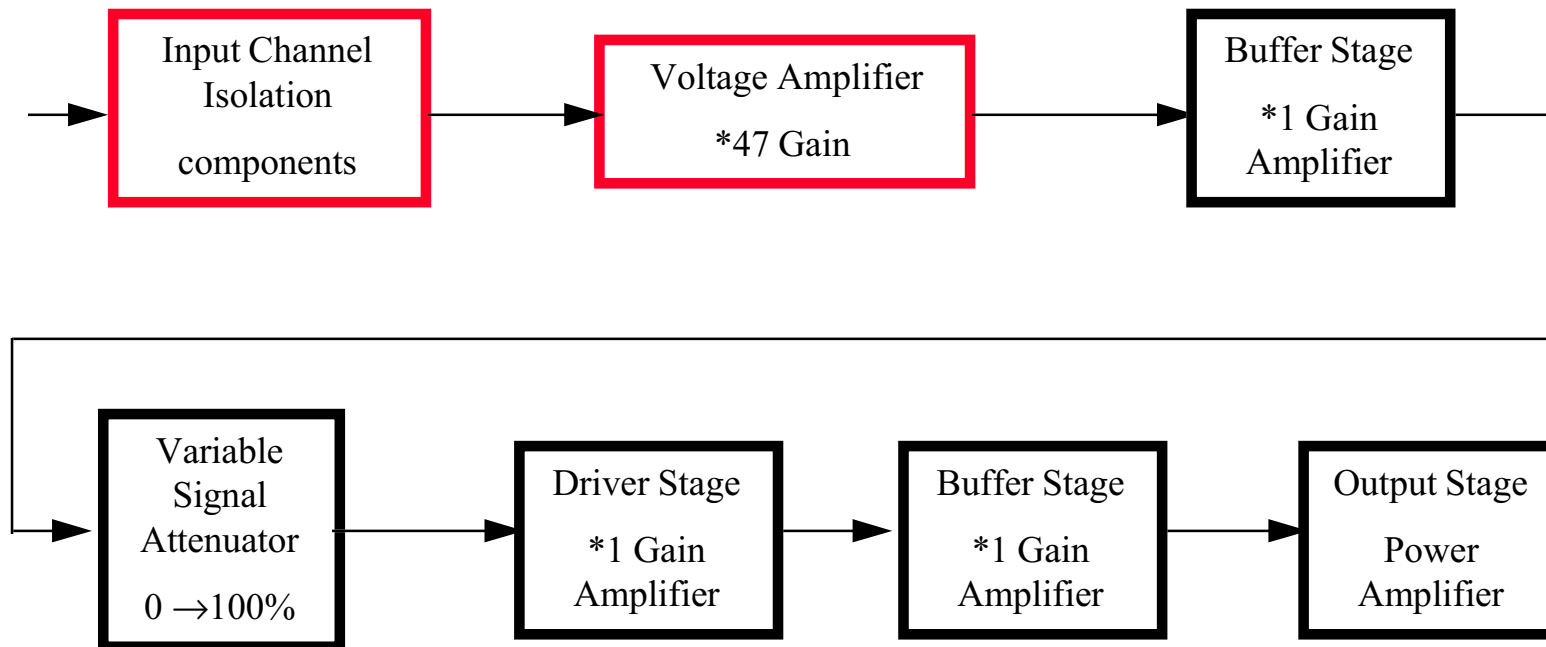

Block Diagram.


# The Amplifier.

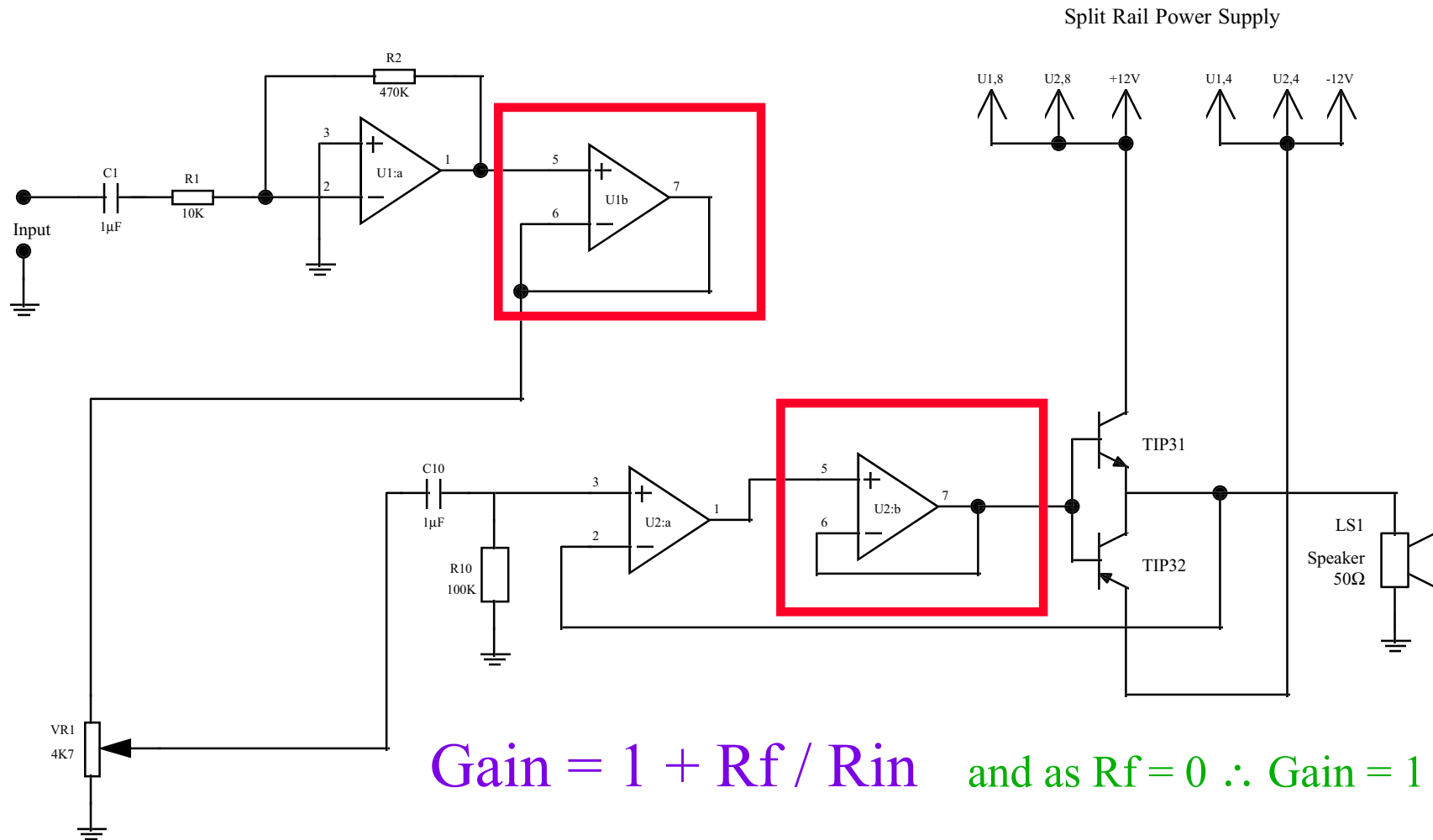

**Buffer Stage (Signal Amplifier \*1 Gain) circuit.**




# Amplifier Theory.

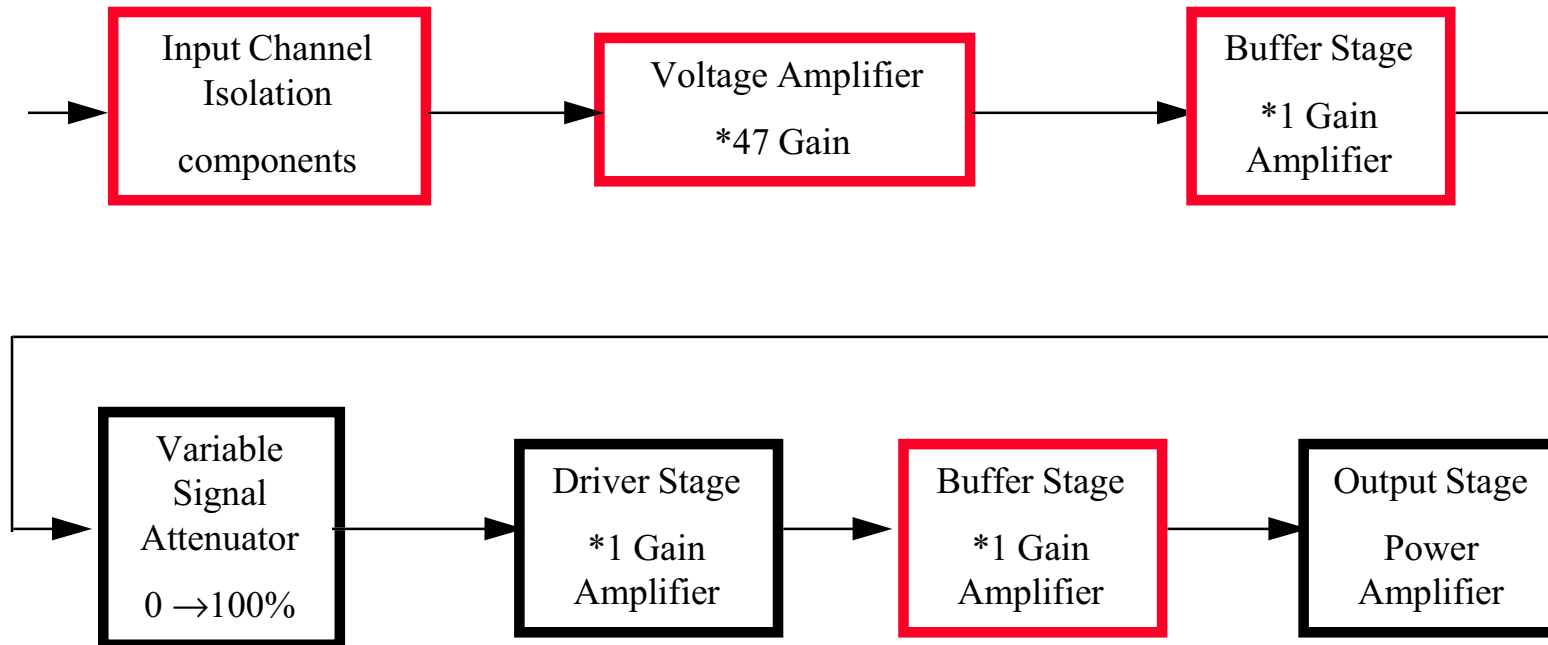


Block Diagram.

# The Amplifier.

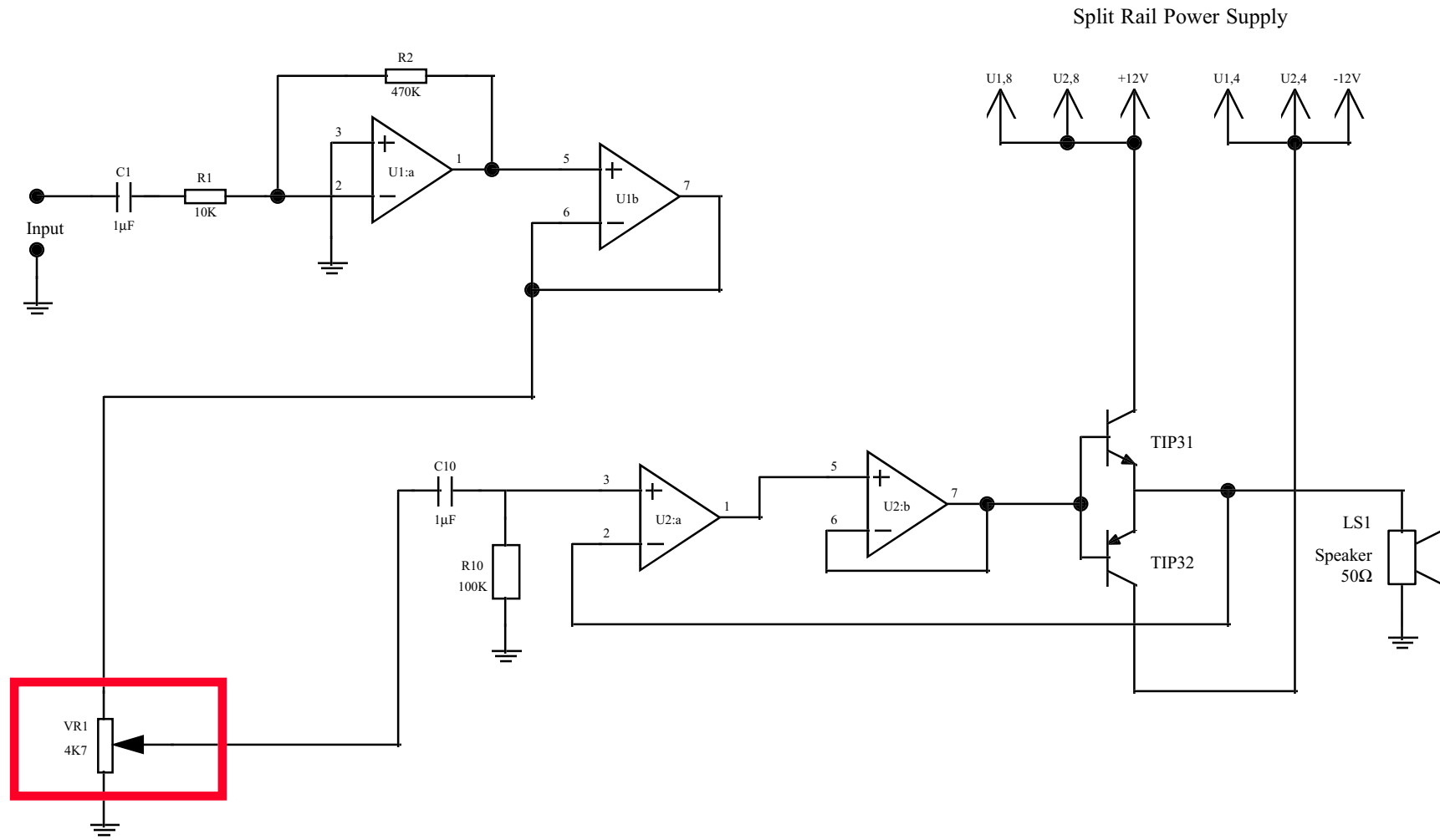


**Signal Attenuator (Volume Control).**

# Amplifier Theory.

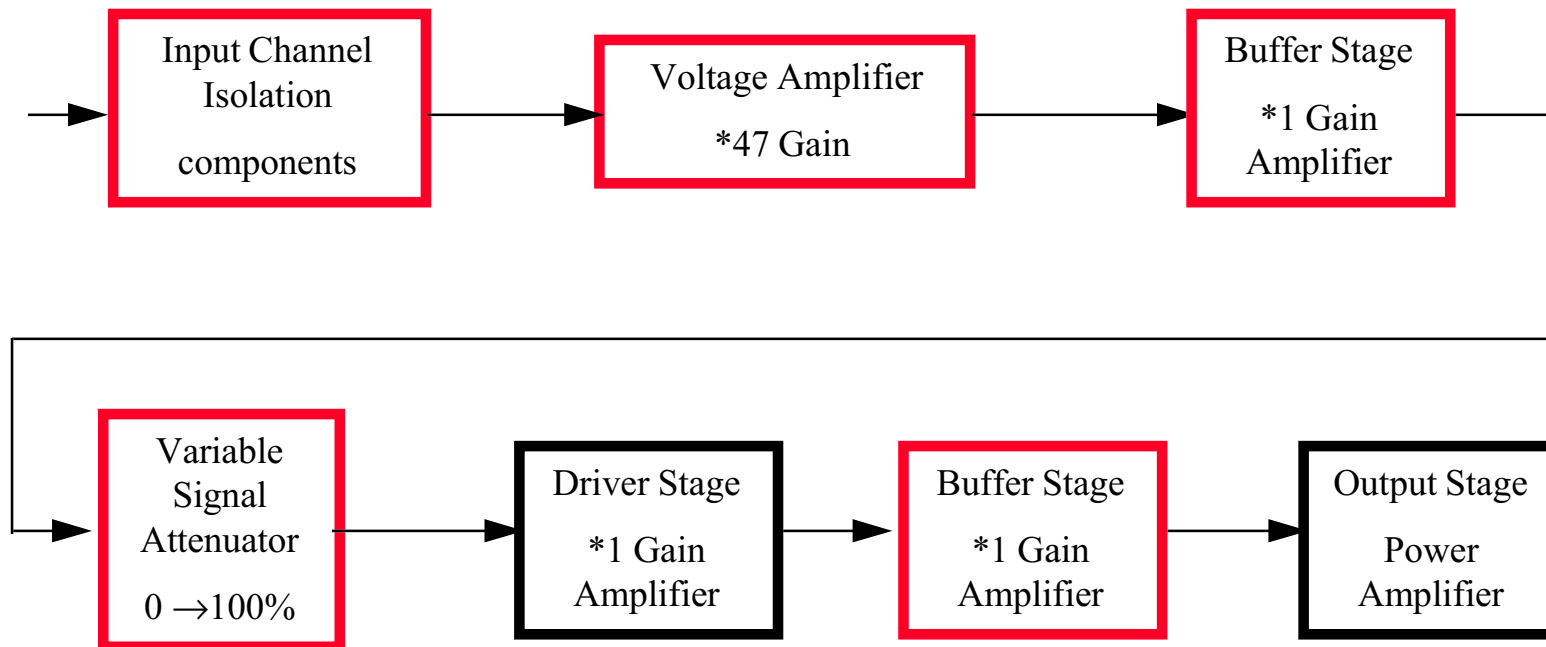

Block Diagram.


# The Amplifier.

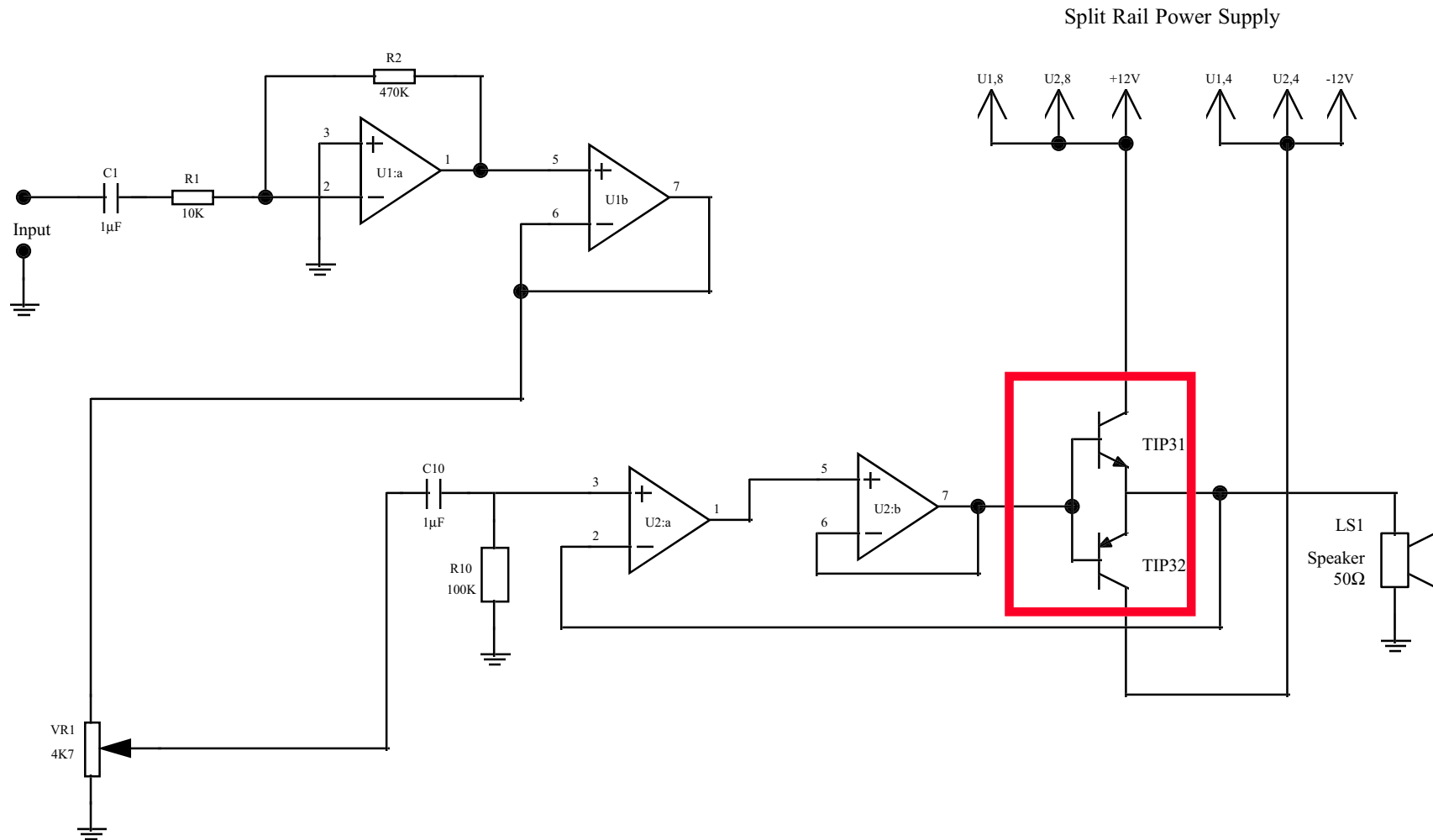

**Power Driver circuit.**

# The Amplifier.

Split Rail Power Supply

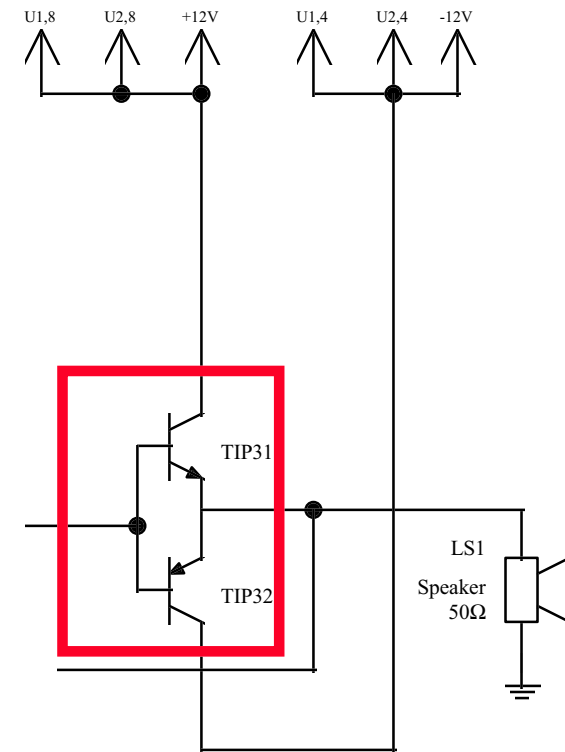

Power Driver circuit.

# Amplifier Theory.

If Base connection is held at mid rail voltage then


TIP32 is Switched Off. (Will appear as O/C)

TIP31 is Switched Off. (Will appear as O/C)

The Load Speaker Cone will remain in neutral position as no voltage will be present across it.

**Remember** that you need a voltage about **0.6 volts** to switch a silicon transistor into a conducting state (**Switched on**).

Split Rail Power Supply

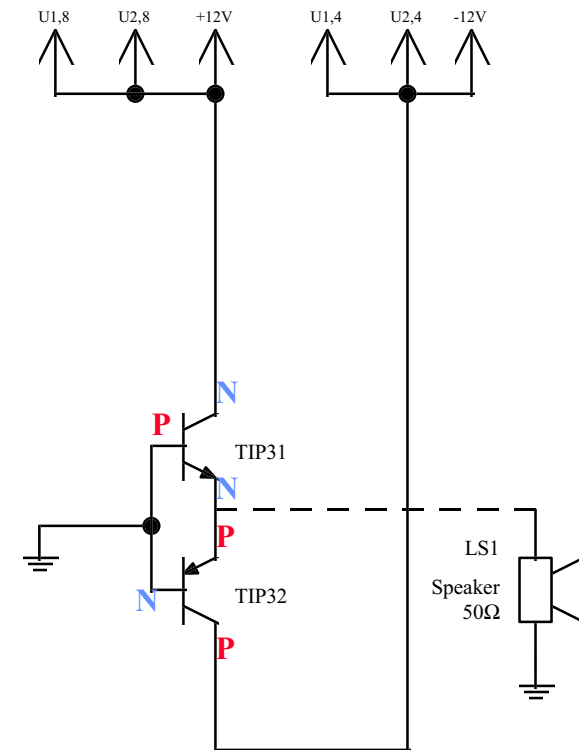


**Power Driver circuit.**

# Amplifier Theory.

As Base connection goes more  
**Positive**  
TIP31 Conducts.  
TIP32 is Switched Off.  
Load Speaker Cone Pushes Forward.

Split Rail Power Supply

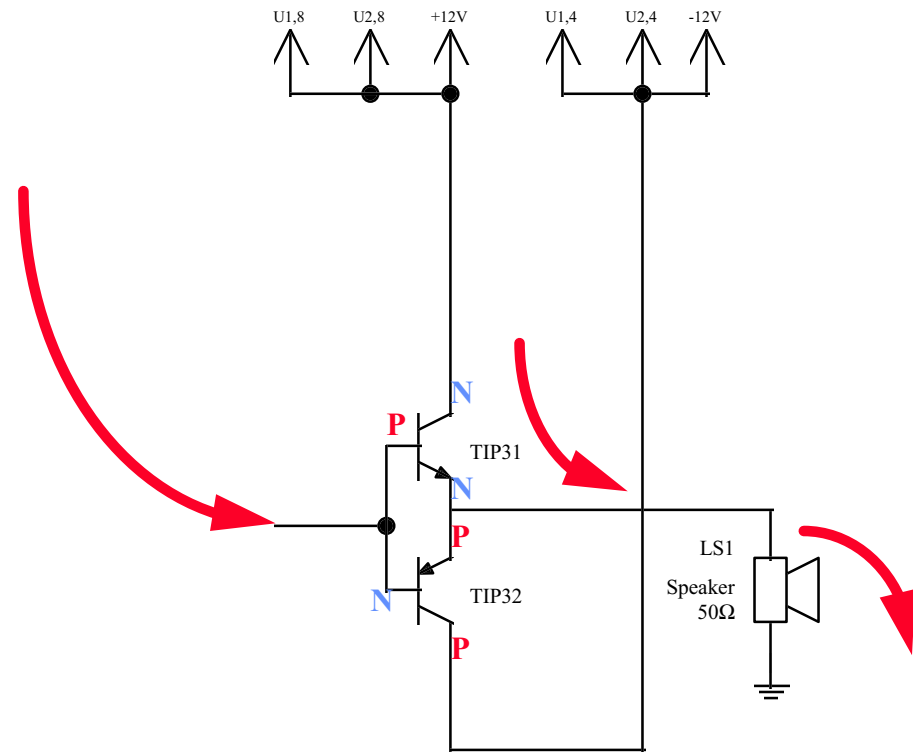


Power Driver circuit.

# Amplifier Theory.

As Base connection goes more **Negative**  
TIP32 Conducts.  
TIP31 is Switched Off.  
Load Speaker Cone Pulls Back.


Split Rail Power Supply

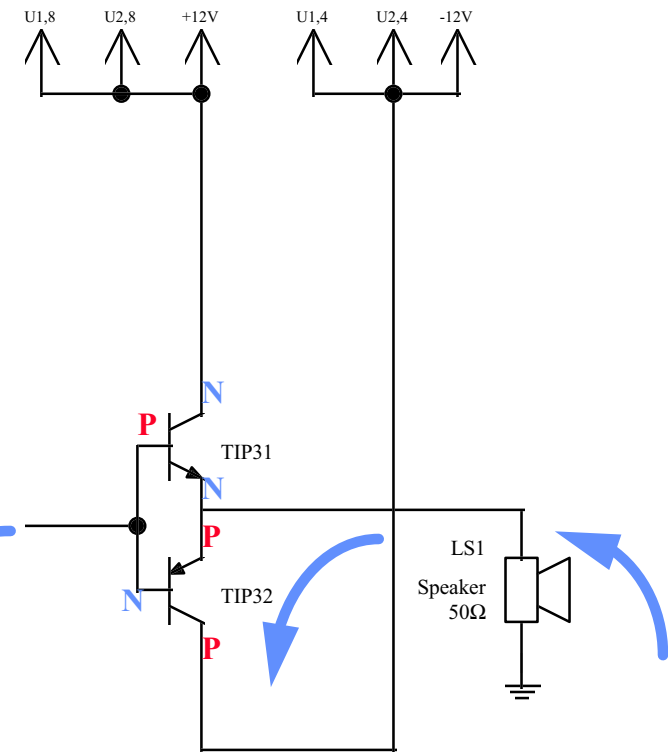

**Power Driver circuit.**




# Amplifier Theory.

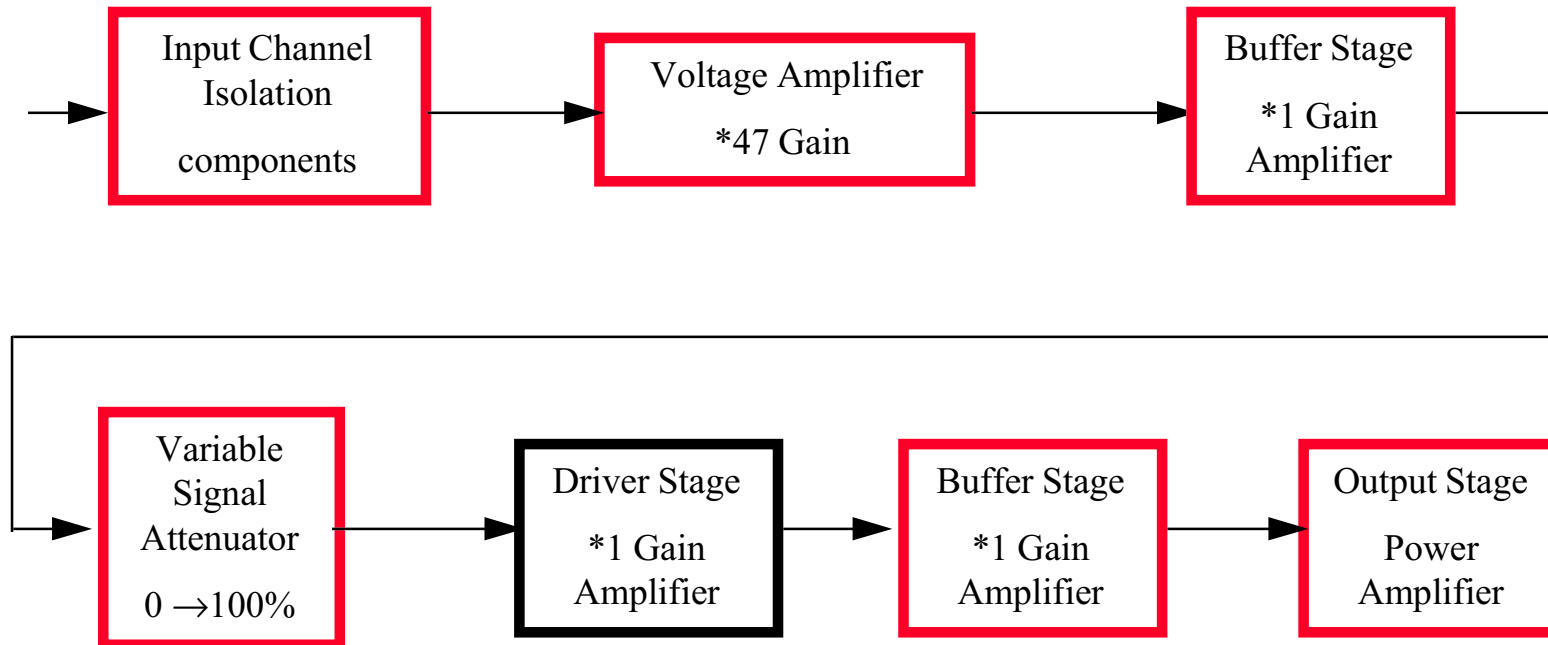


Block Diagram.

# The Amplifier.

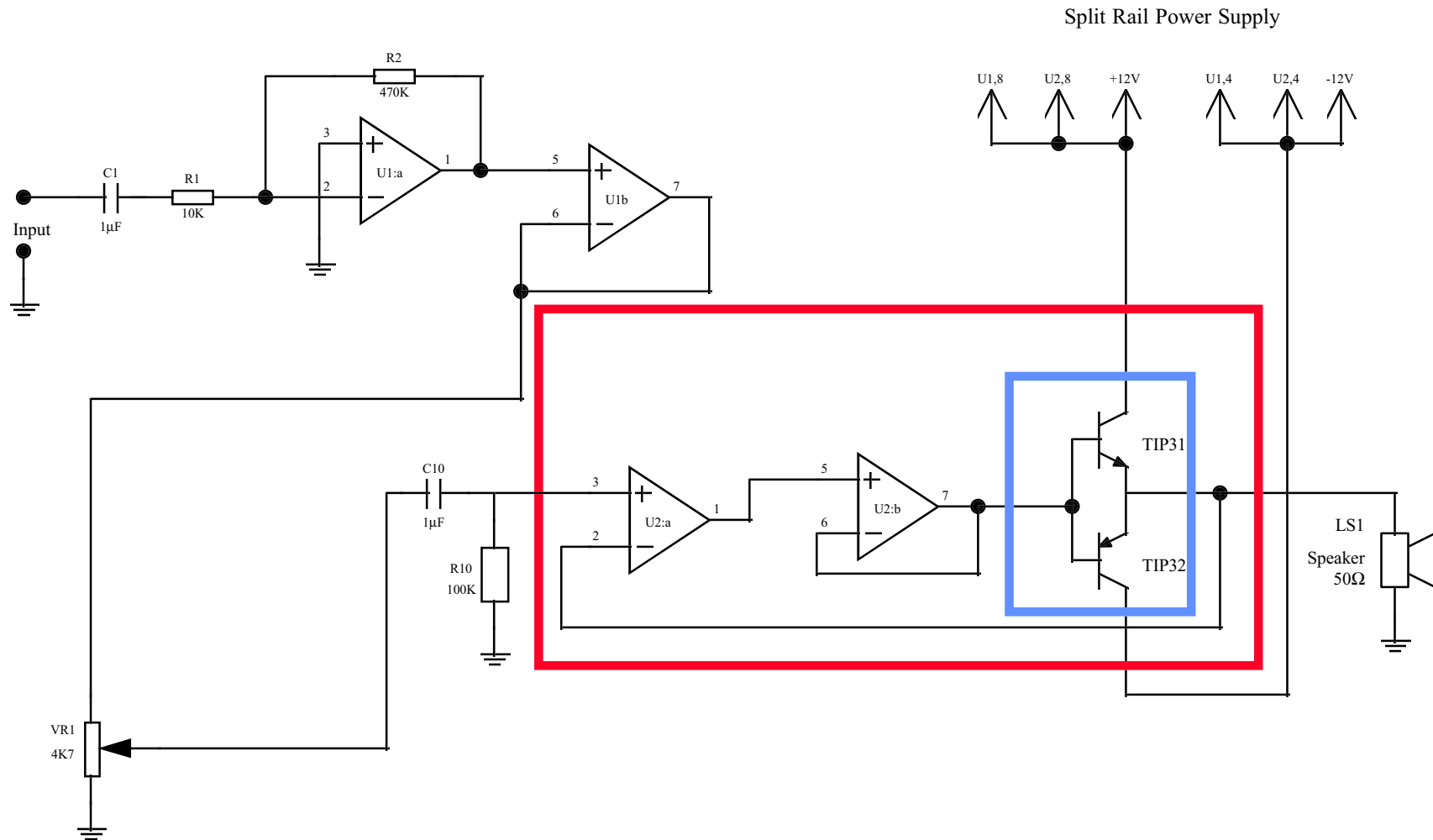


Voltage Follower "Driver" & Power Amplifier circuit.

# The Amplifier.

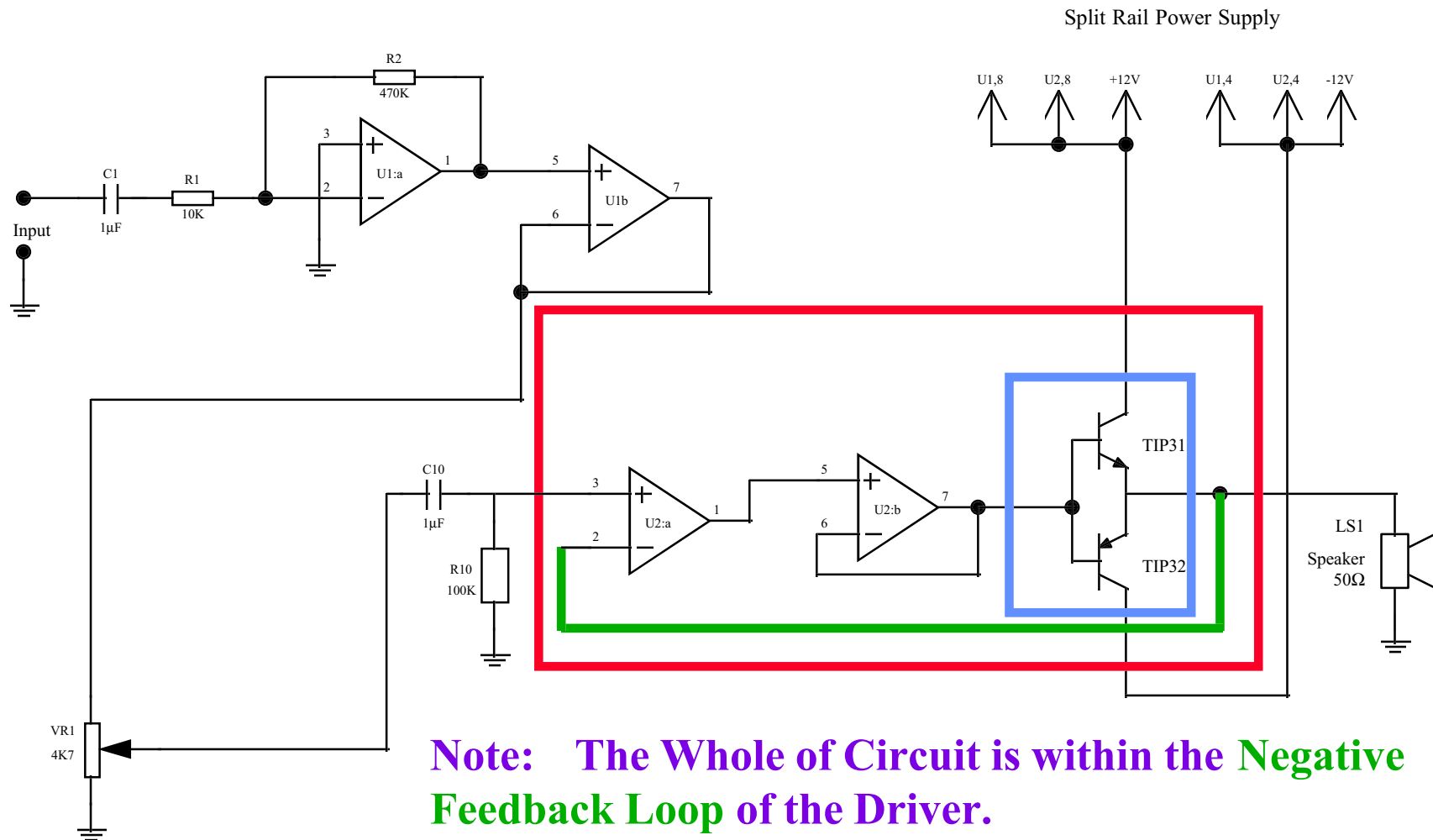

**Voltage Follower "Driver" & Power Amplifier circuit.**

# Amplifier Theory.

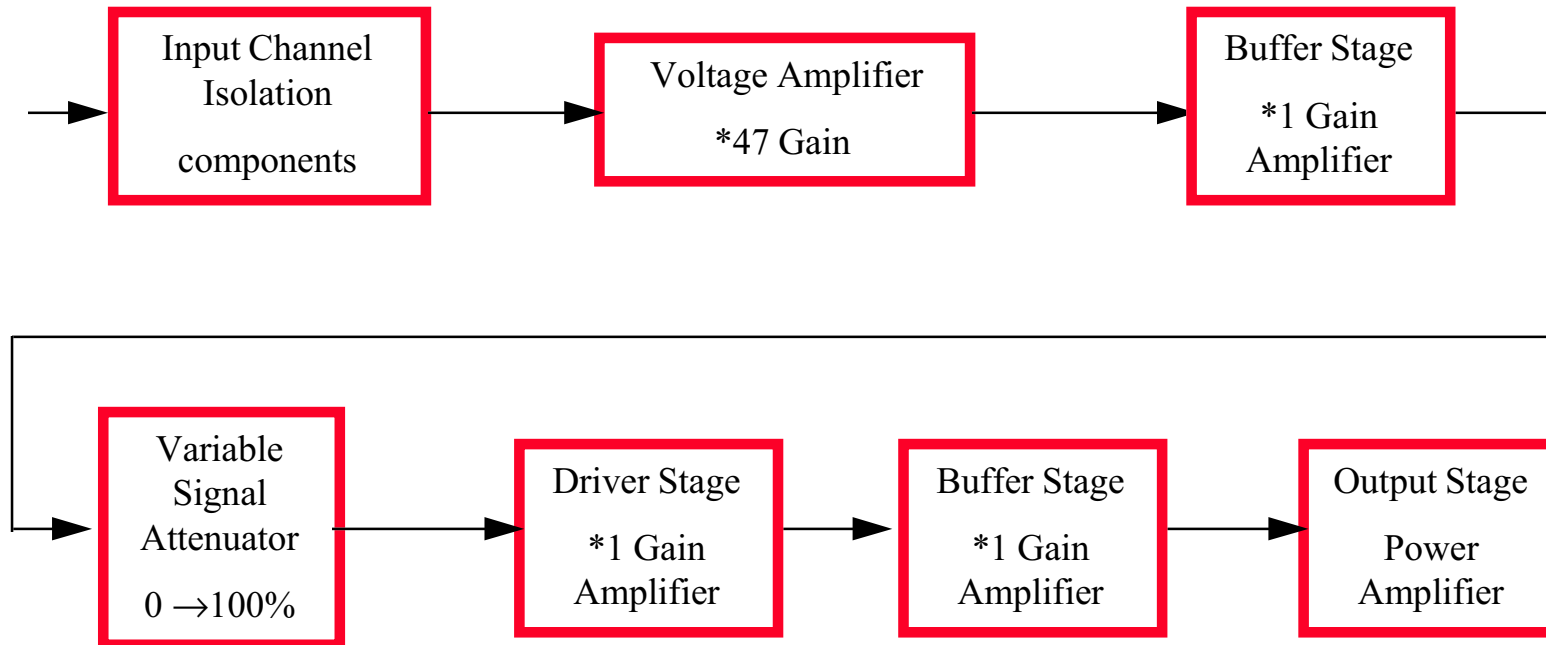


Block Diagram.

# Amplifier Building


# Amplifier Circuit checking.

- Check that ICs are correct way round and in the correct place.
- Check that Transistors are correct way round and in the correct place.
- Verify all resistor are in correct place and correct value.
- Verify all capacitors are in correct place and correct value.
- Verify that your “NET” list matches your Breadboard construction.

# The Amplifier.

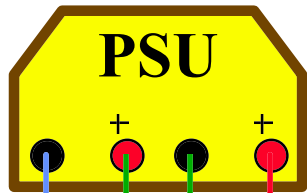

Set both PSU voltages to 12V

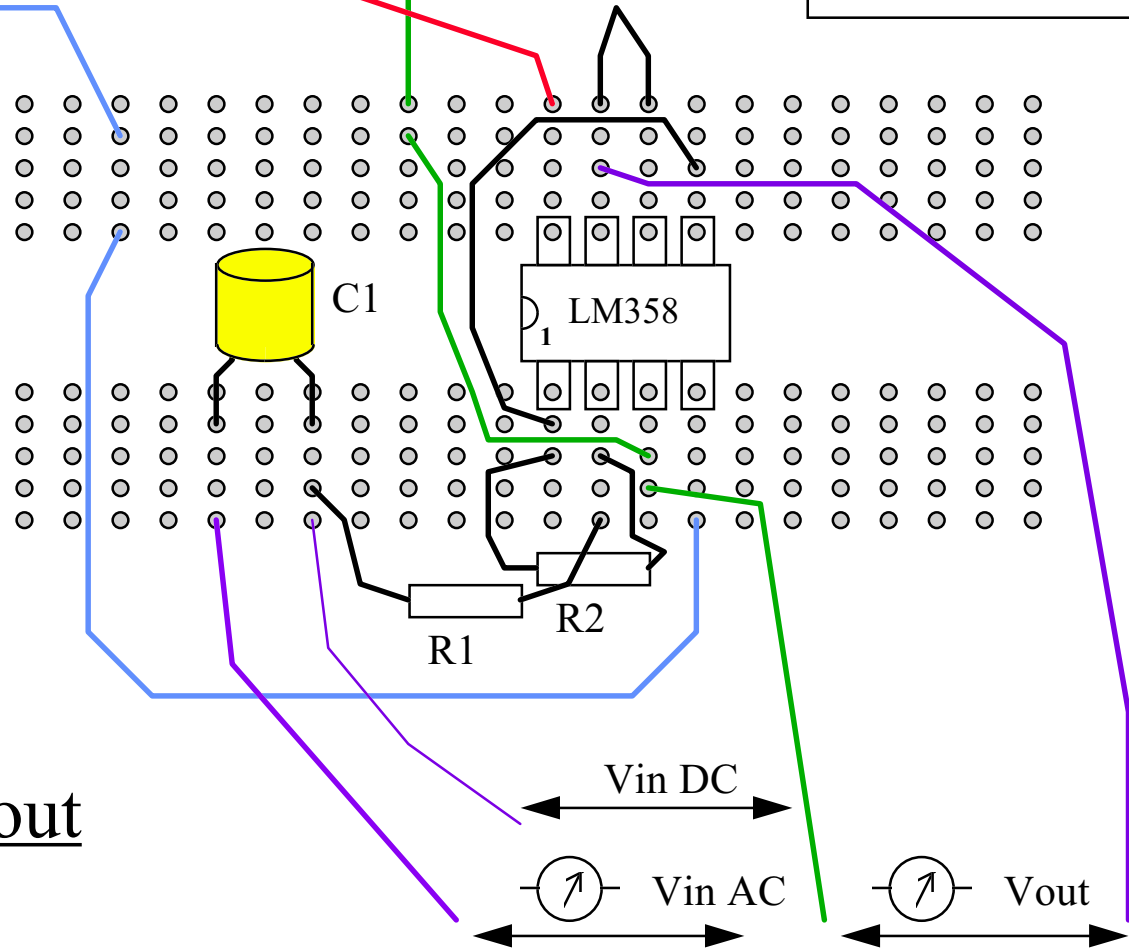


Voltage  
Amplifier

Physical Layout  
Diagram

# The Amplifier.

Set both PSU voltages to 12V

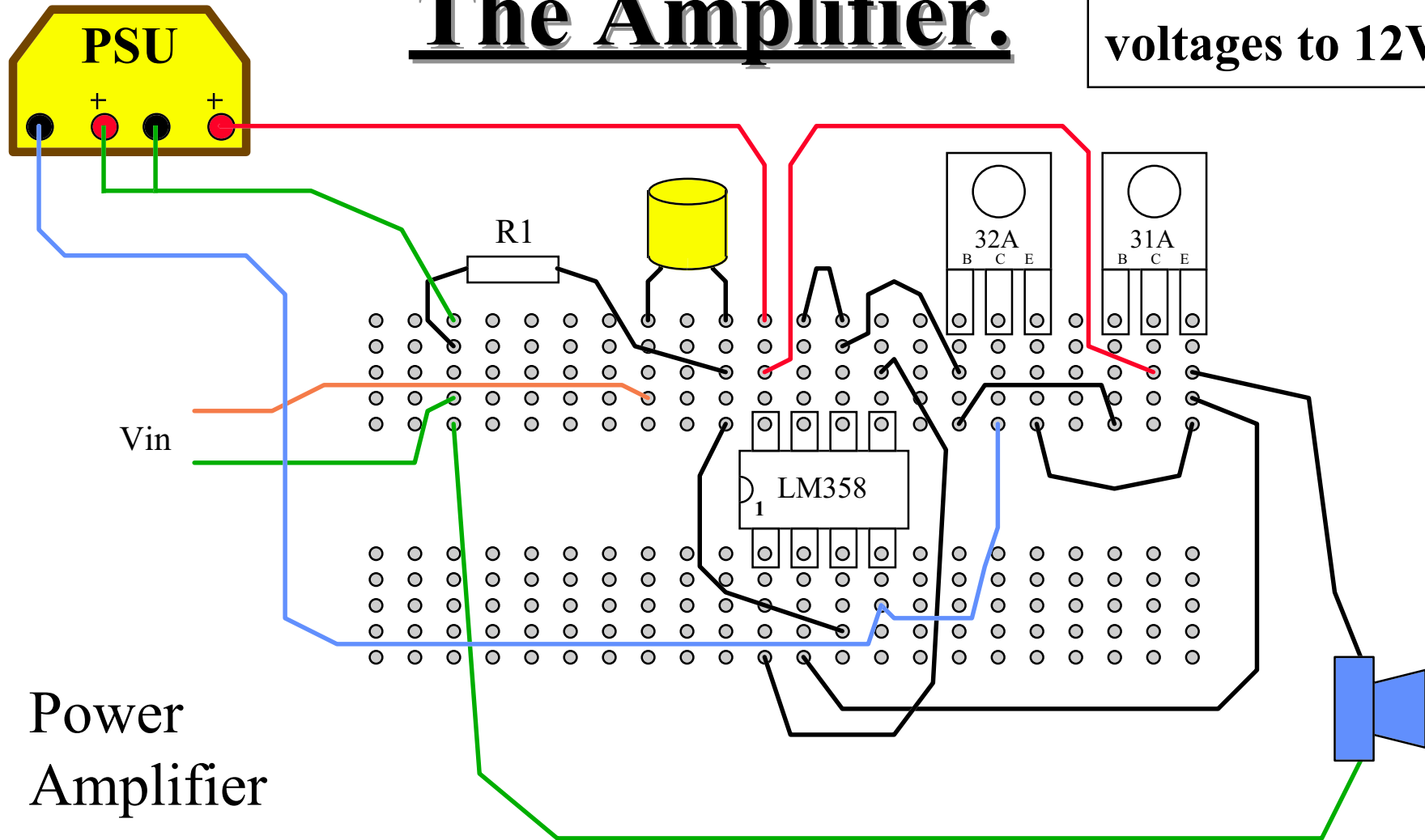


Power  
Amplifier

Physical Layout  
Diagram



# Amplifier Testing

# The Amplifier Testing (AC).

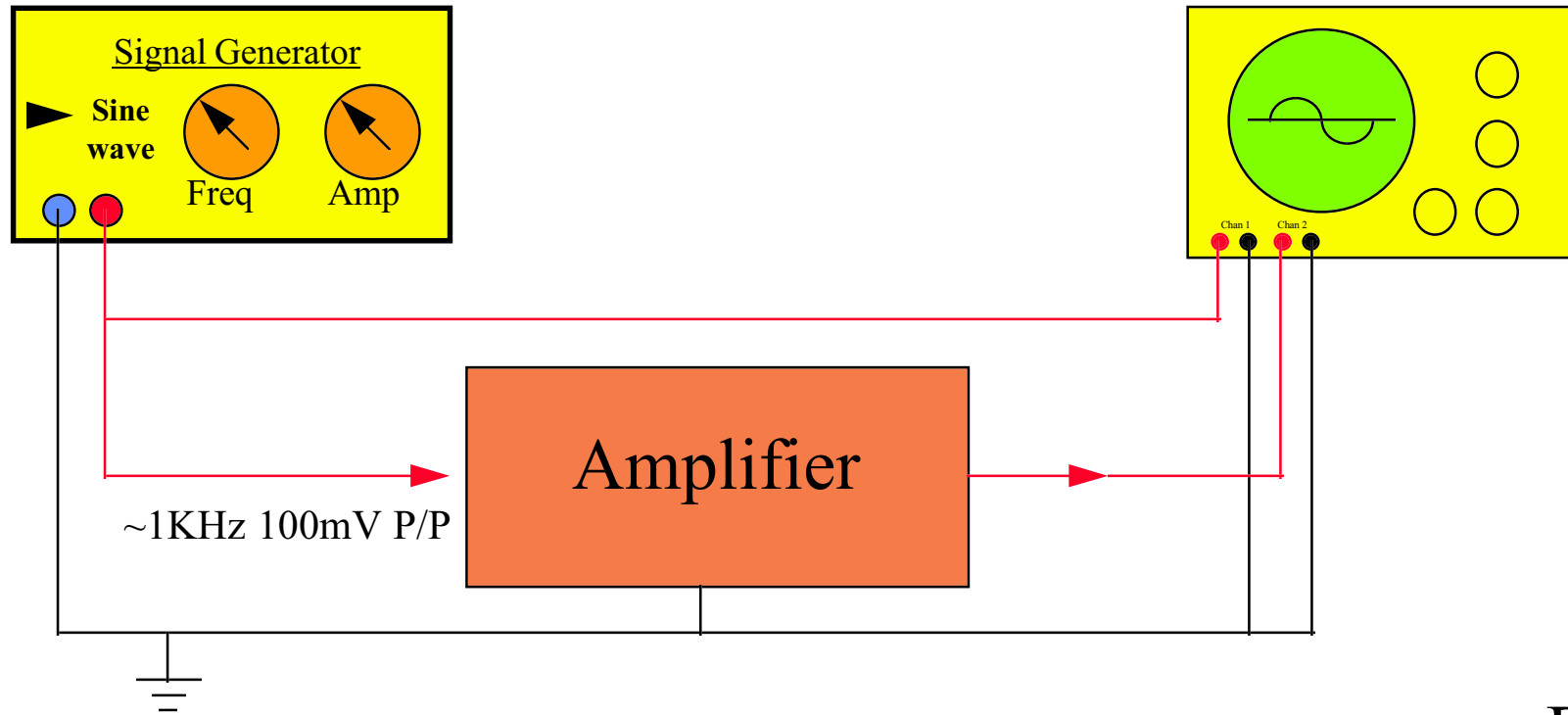

Calculate Gain.


Measure Gain.

Compare Results (Do they match) ?

$$\text{Gain} = \frac{V_{\text{Output}}}{V_{\text{Input}}} = \frac{-R_f}{R_{in}}$$

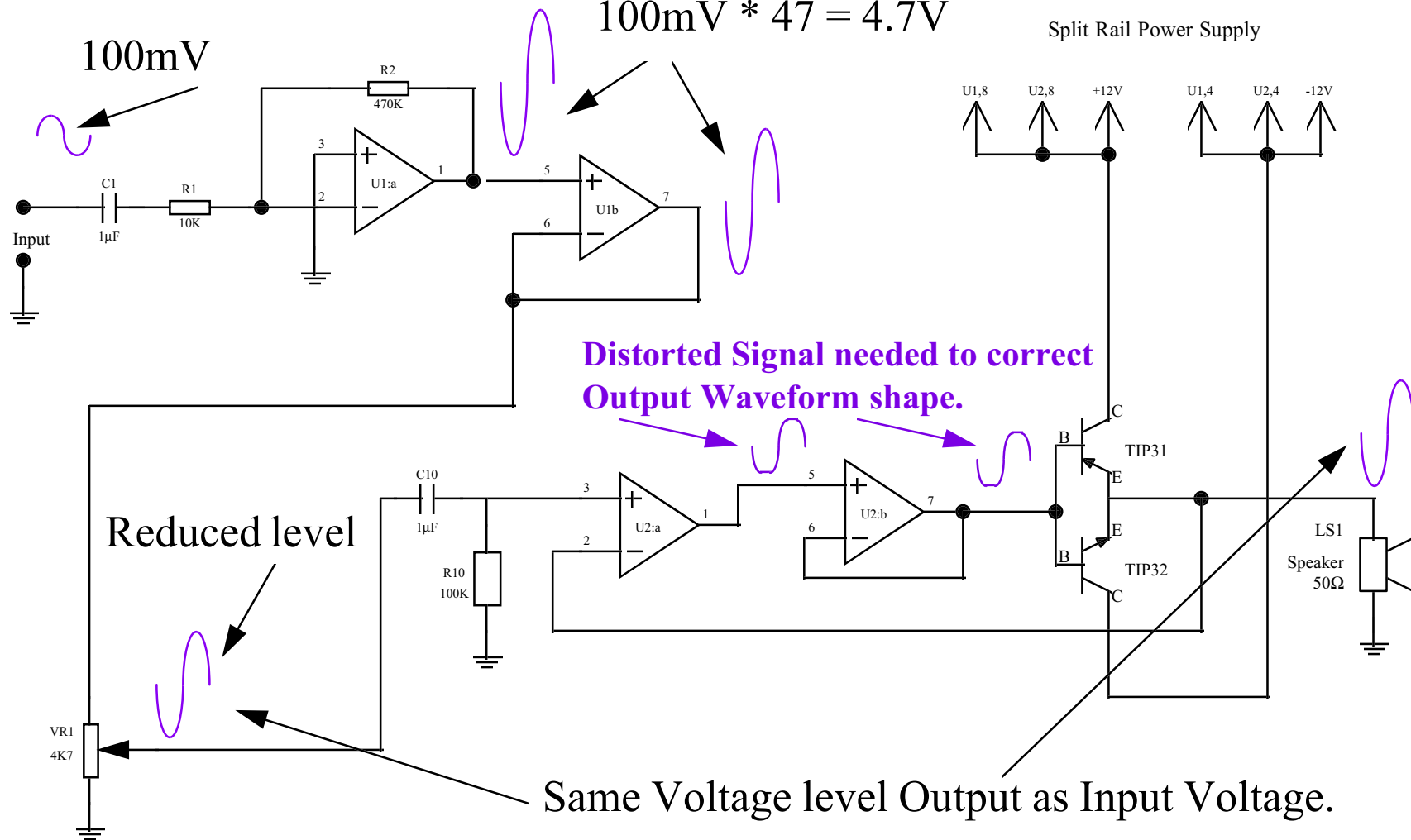
# The Amplifier.

$$\text{(Input) * Gain}$$
$$100\text{mV} * 47 = 4.7\text{V}$$



**Signals through the Amplifier circuit.**


# The Amplifier Testing (DC).

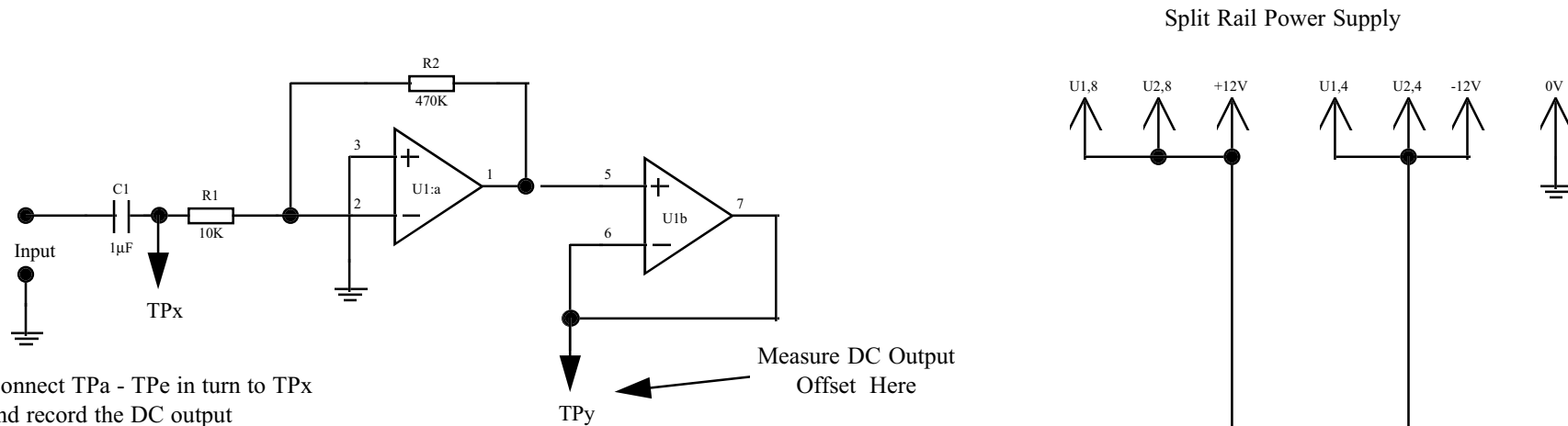

Connect TPa - TPe in turn to TPx and record the DC output resulting from the connection.

Record the voltages presented at TPa through to TPe

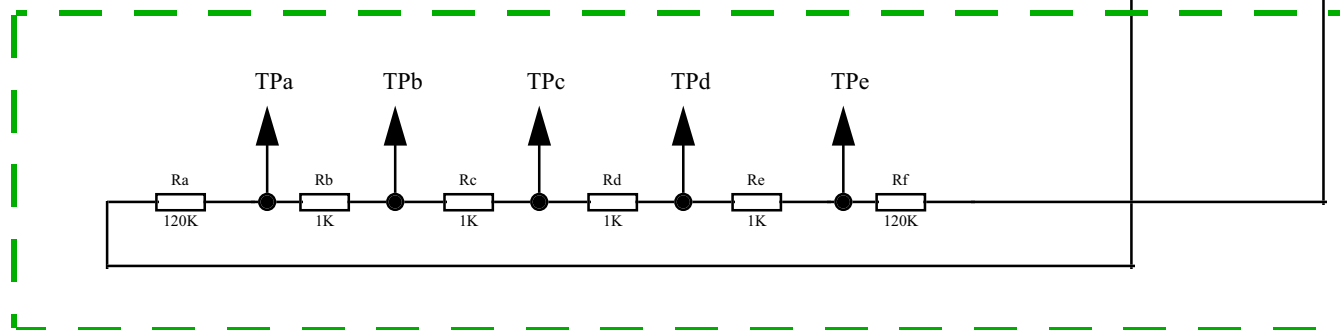
Additional Circuit required for these tests only.



**DC Voltage Tests for Voltage amplifier circuit.**

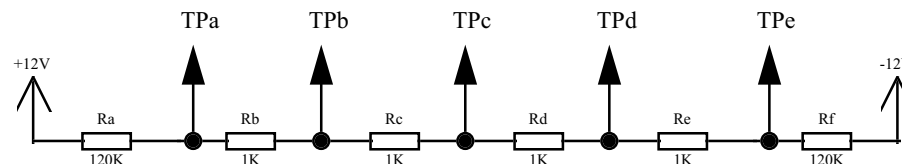
# The Amplifier Testing (DC).

- Calculate total voltage across resistor circuit.
- Left hand side = +12V : Right hand side = -12V
- Difference = +12V - (-12V) = 24V
- Calculate total resistance of circuit
- $R_{Ts} = R1 + R2 + R3 \dots$
- $R_{Ts} = 120K + 1K + 1K + 1K + 1K + 120K = 244K$
- Calculate current in circuit ie.  $I = V/R$
- $I_{cct} = 24V / 244K = 24/244000 \text{ A}$



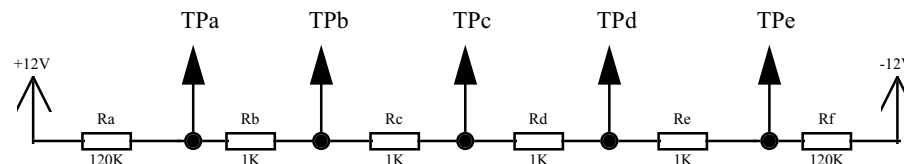
# The Amplifier Testing (DC).

- Calculate voltage across resistors Ra or Rf.
- $V = I * R \therefore V_{R_{(a,f)}} = 24/244000 * 120000 = (24 * 120)/244 = 2880/244 \text{ Volts} \quad 11.803V$
- Calculate voltage across resistors Rb,Rc,Rd or Re.
- $V = I * R \therefore V_{R_{(b-e)}} = 24/244000 * 1000 = (24 * 1)/244 = 24/244 \text{ Volts} \quad 0.0984V$
- Note: Sum of the voltages is  $2 * (2880/244) + 4 * (24/244) = (5760 + 96)/244 = 5856/244 = 24$


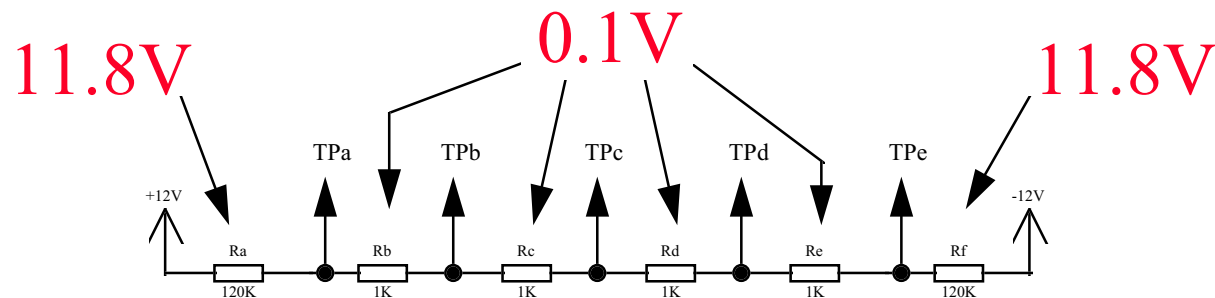
# The Amplifier Testing (DC).

- Calculate voltage across resistors Ra or Rf.
- $V = I * R \therefore V_{R_{(a,f)}} = 24/244000 * 120000 = (24*120)/244 = 2880/244 \text{ Volts} \quad 11.803V$
- Calculate voltage across resistors Rb,Rc,Rd or Re.
- $V = I * R \therefore V_{R_{(b-e)}} = 24/244000 * 1000 = (24*1)/244 = 24/244 \text{ Volts} \quad 0.0984V$
- Note: Sum of the voltages is  $2*(2880/244) + 4*(24/244) = (5760+96)/244 = 5856/244 = 24$




# Simulation



# Digital Dice Counter Circuit.


Button is a push to make switch.

## 1 to 6 Count Circuit.

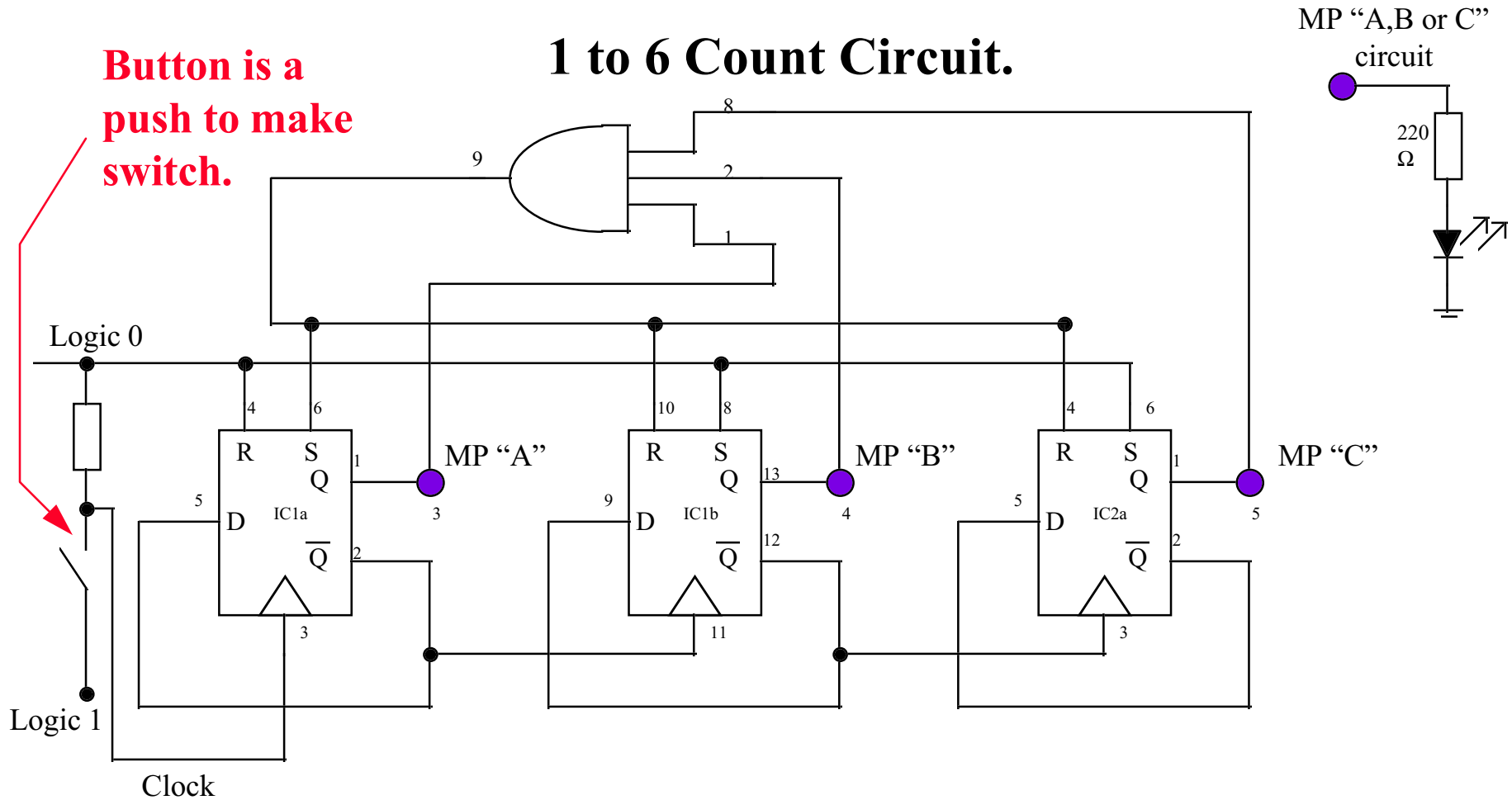

On the ICs / Chips CD4013 CD4073  
 7 7 7 Connect **VSS** to Ground/0V Logic 0  
 14 14 14 Connect **VDD** to +5V Logic 1

# Digital Dice Counter Circuit.

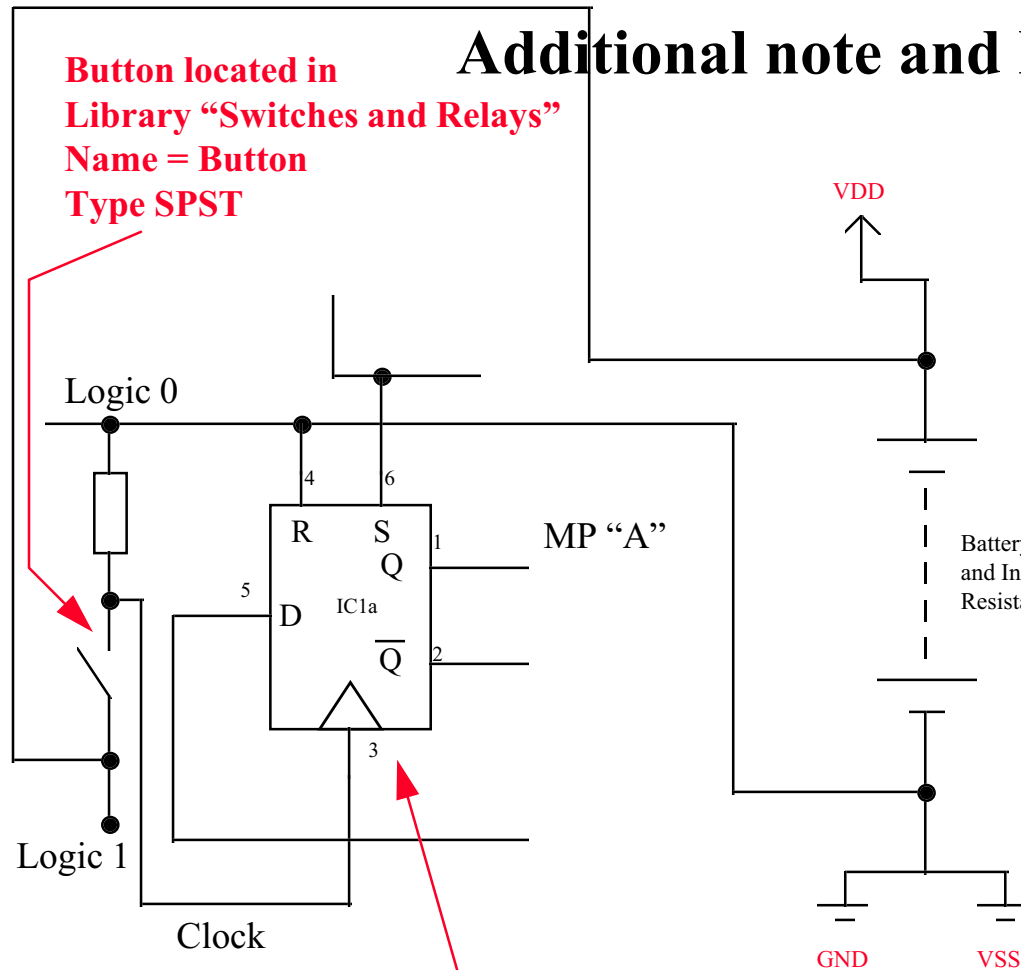


**Additional note and labels required.**

**Button located in Library "Switches and Relays" Name = Button Type SPST**

**LED located in Library "Optoelectronics" Name = LED-RED, LED-GREEN, LED-YELLOW, LED-BLUE**

MP "A,B or C" circuit

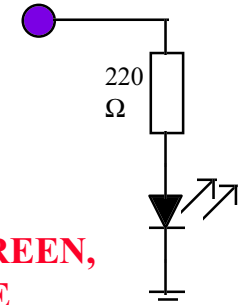


**Battery located in Library "Simulator Primitives" Name = BATTERY**

**Resistor located in Library "Modelling Primitives" Name = RESISTOR**

**Devices located in Library "CMOS 4000 series" Name = 40... etc.**

On the ICs / Chips CD4013 CD4073  
 7 7 7 Connect **VSS** to Ground/0V Logic 0  
 14 14 14 Connect **VDD** to +5V Logic 1

# The Amplifier.

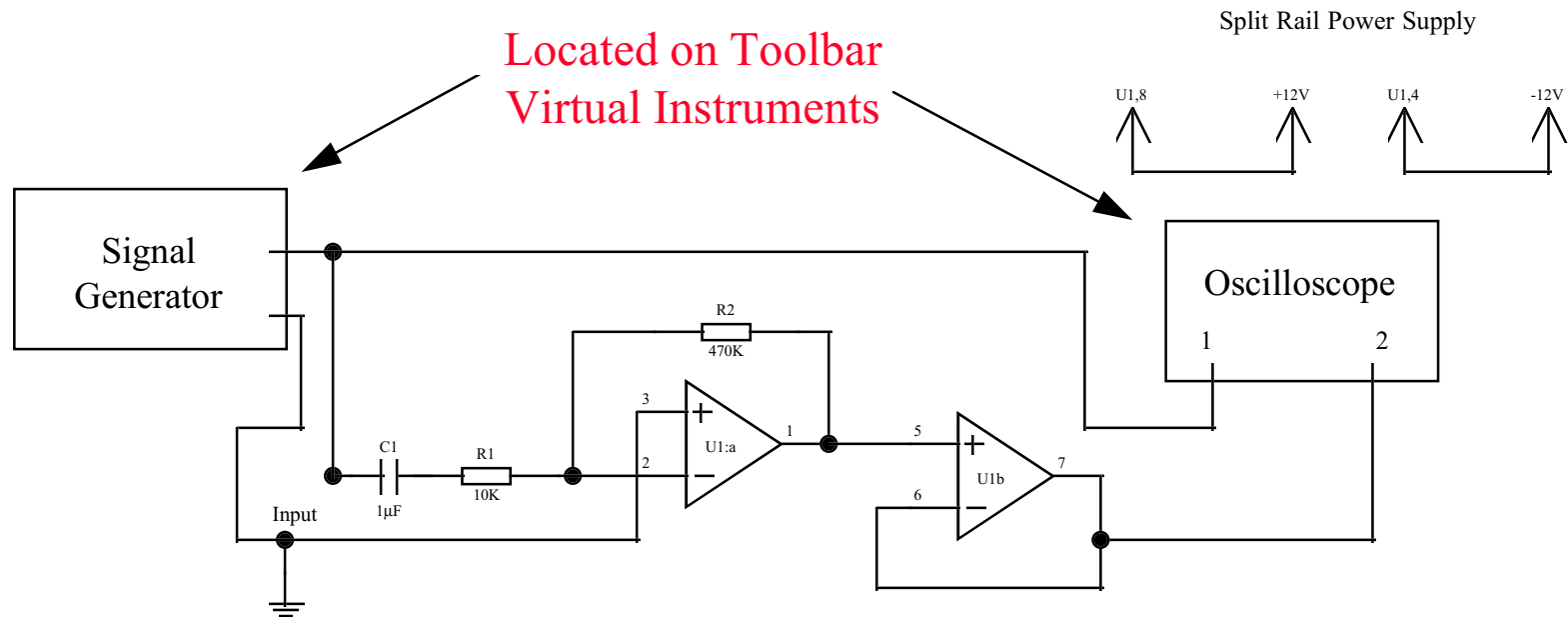

Device located in  
Library “Operational Amplifiers”  
Name = LM358.

Look for the Chip with a Spice model


Resistor and Capacitor located in  
Library “Modelling Primitives”  
Name = RESISTOR , CAPACITOR

Voltage Amplifier circuit.

# Microprocessors.


# LED Display Board

# LED Display Board.

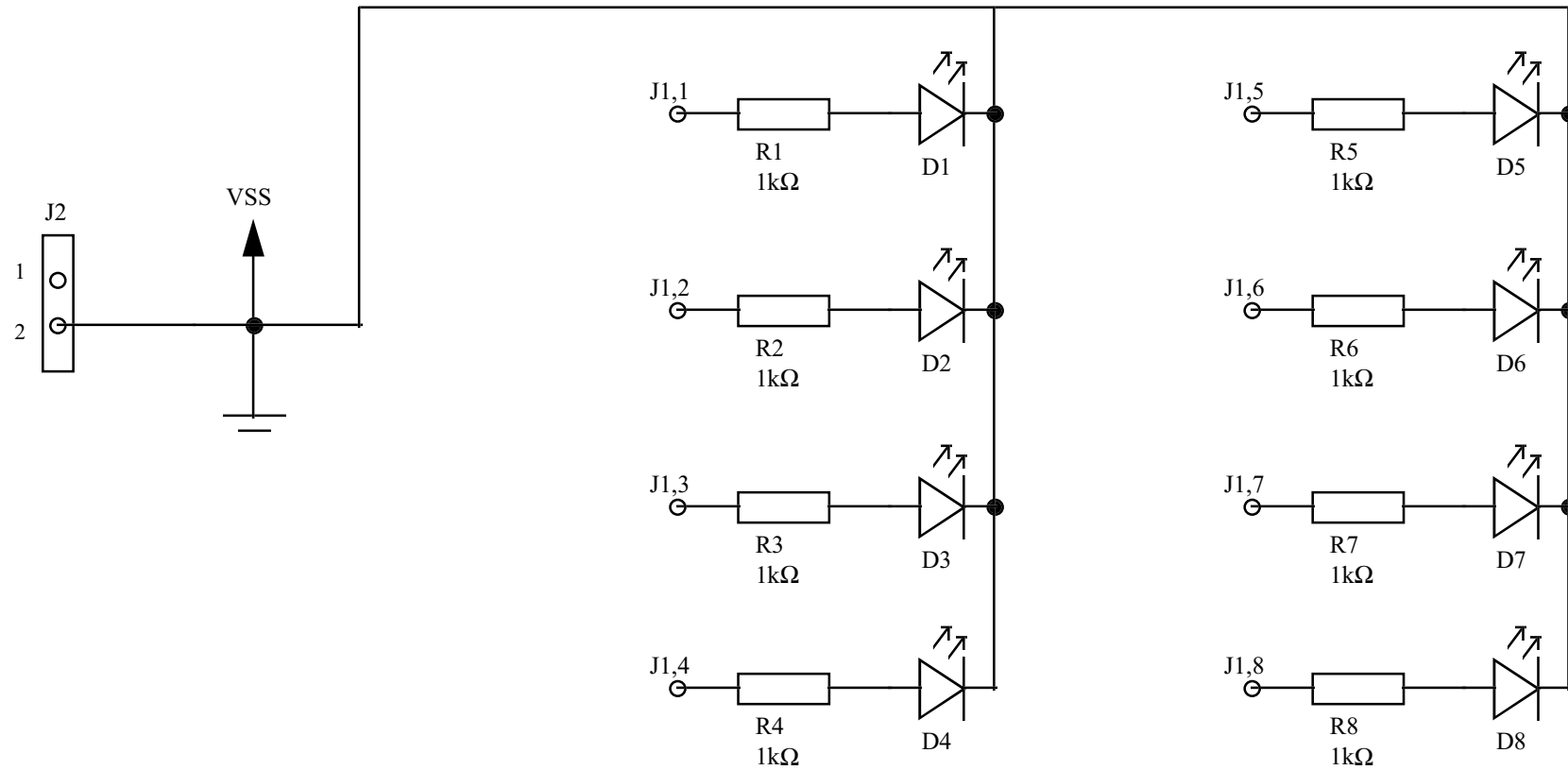

Circuit of LED Display Board.

# LED Display Board.

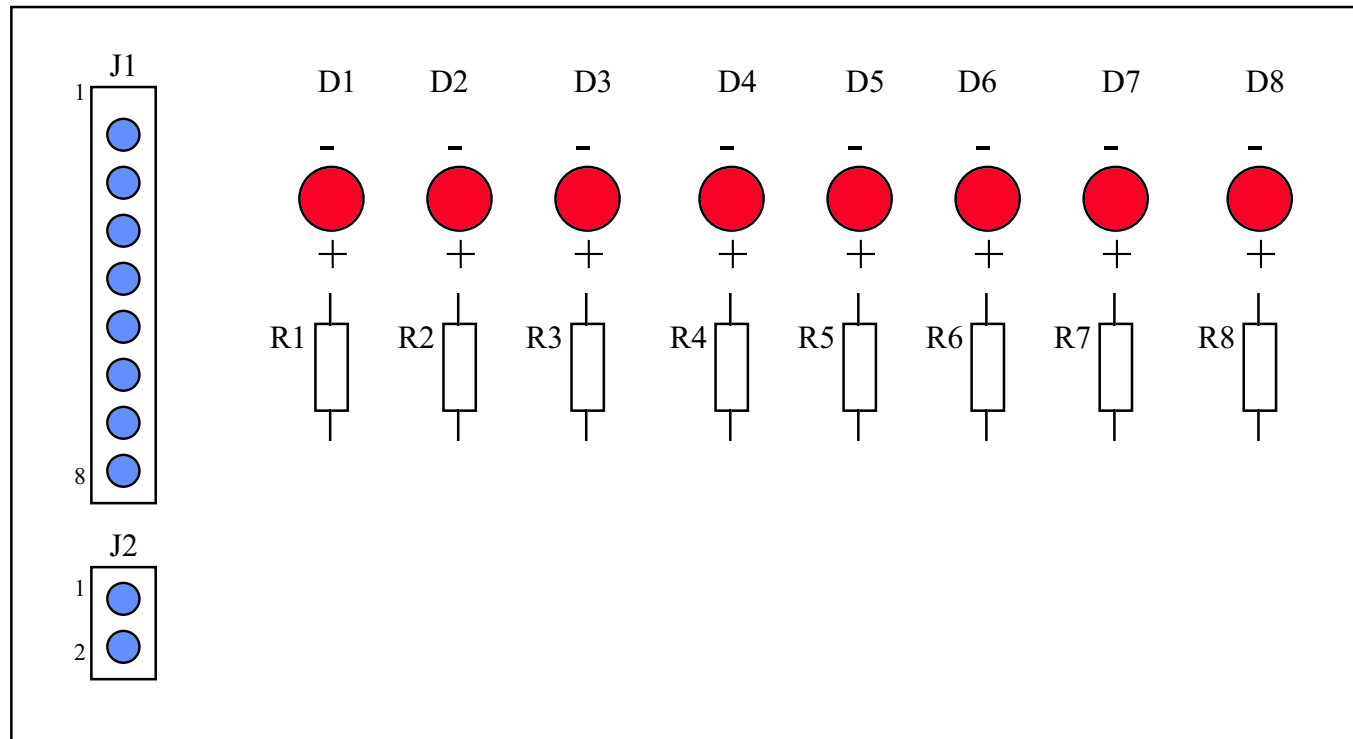

Layout of LED Display Board.


# Testing LED Display Board.

- Check all solder connections (Shiny, Concave, No lumps bumps holes)
- Have all Components been located in the correct place the right way round.
- Verify that all tracks connect to the correct place and no additional short circuits added.
- Connect J2,2 to Ground
- and apply +5V to J1,1 and D1 should light.
- Repeat J1,2 ... ,8 → and D2...,D8 should light.




# Push Button Array

# Push Button Array Board.

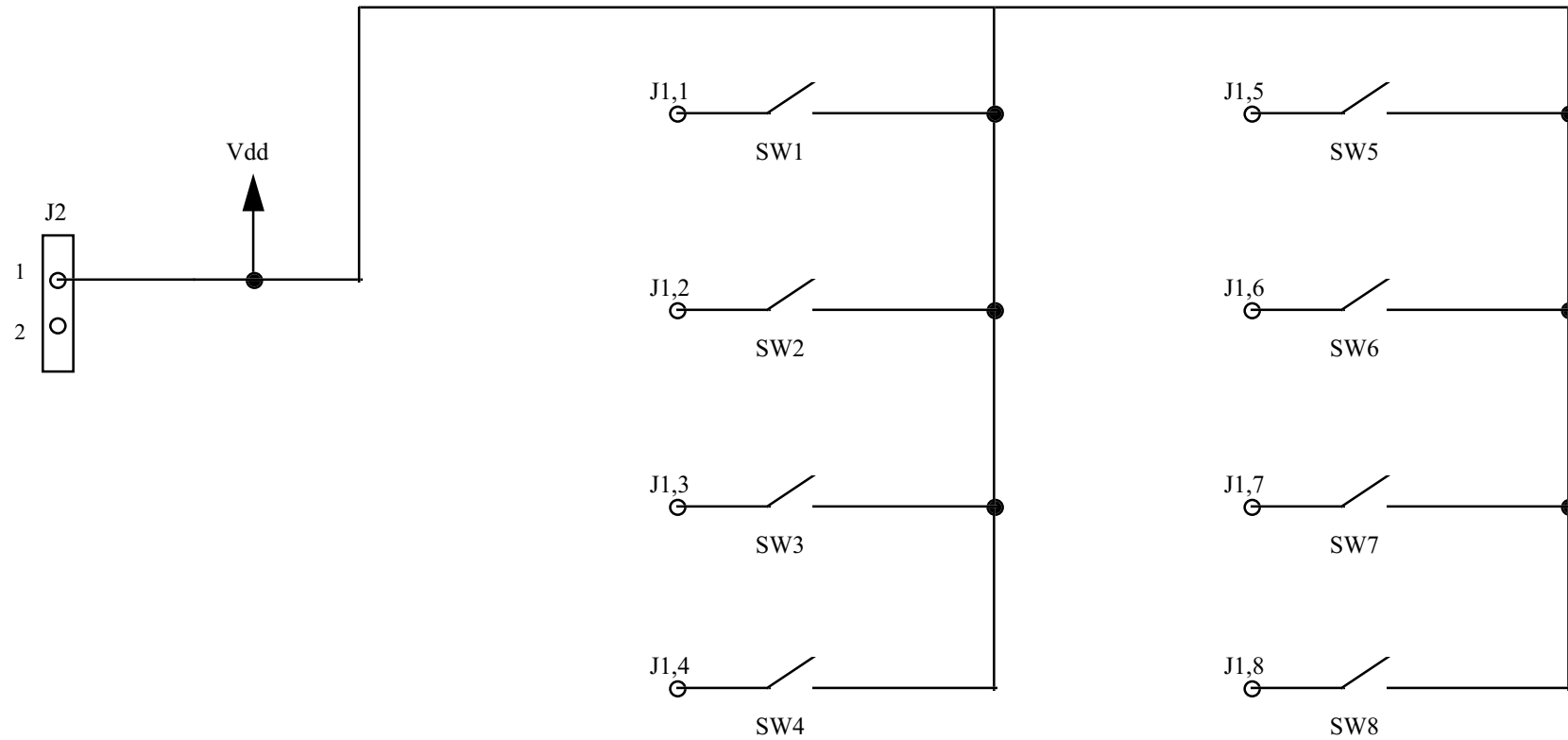

Circuit of Push Button Array Board.

# Push Button Array Board.

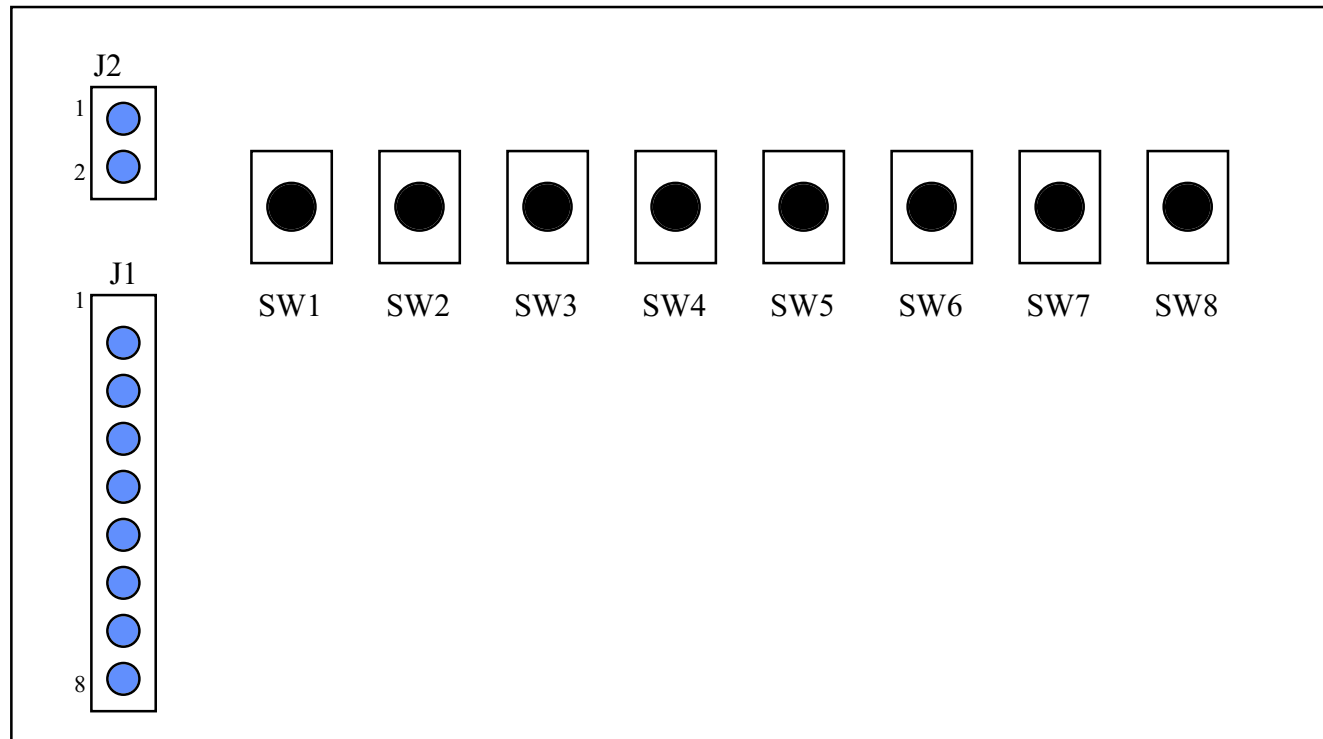

Layout of LED Push Button Array Board.

# **Testing Push Button Array Board.**


- Check all solder connections (Shiny, Concave, No lumps bumps holes)
- Check all Components been located in the correct place the right way round.
- Verify that all tracks connect to the correct place and no additional short circuits added.

# Testing Push Button Array Board.

- Connect J2,1 of the Switch array board to +5V.
- Connect J2,2 of the Display Board to Ground.
- Connect **J1,1** of the Switch array board to **J1,1** of the Display Board.
- Repeat process for **J1,2 ... ,8** as above.
- Press SW1 and D1 should light.
- Repeat process for SW2 ... ,8 and D2 ..,8 and the appropriate LED should light.

# Processor

# Processor Board.

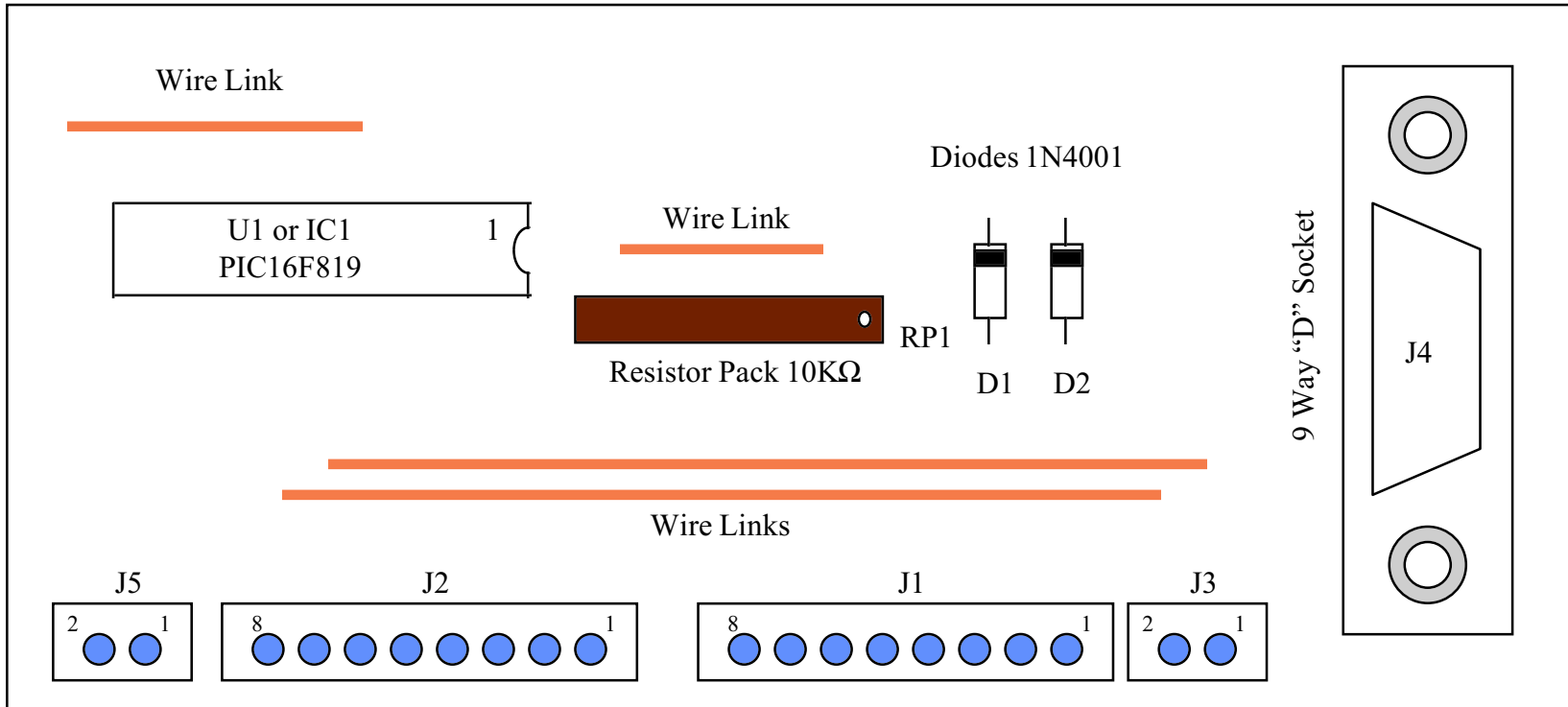

Layout of Processor Board.

# Testing Processor Board.

- Check all solder connections (Shiny, Concave, No lumps bumps holes)
- Check all Components been located in the correct place the right way round.
- Verify that all tracks connect to the correct place and no additional short circuits added.
- Before you insert the processor chip complete the following checks.
- **DO NOT** Proceed unless all checks OK.



# Testing Processor Board.

- S/C checks
- J5,1 → IC1,14
- IC1,5 → J4,4 → J3,2 → J5,2
- IC1,17 → J1,1      IC1,18 → J1,2      IC1,1 → J1,3
- IC1,2 → J1,4      IC1,3 → J1,5      IC1,4 → J1,6
- IC1,15 → J1,7      IC1,16 → J1,8
- IC1,6 → J2,1      IC1,7 → J2,2      IC1,8 → J2,3
- IC1,9 → J2,4      IC1,10 → J2,5      IC1,11 → J2,6
- IC1,12 → J2,7      IC1,13 → J2,8
- IC1,4 → J4,5      IC1,12 → J4,7      IC1,13 → J4,8

# Testing Processor Board.

- 10K $\Omega$  Resistance checks
- IC1,5  $\rightarrow$  J1,1            IC1,5  $\rightarrow$  J1,2            IC1,5  $\rightarrow$  J1,3
- IC1,5  $\rightarrow$  J1,4            IC1,5  $\rightarrow$  J1,5            IC1,5  $\rightarrow$  J1,6
- IC1,5  $\rightarrow$  J1,7            IC1,5  $\rightarrow$  J1,8
- O/C Checks
- IC1,5  $\rightarrow$  IC1,14
- J3,1  $\rightarrow$  J4,9
- Diode checks (Circa 0.6V) (Cmn Test Lead to IC1,14)
- J3,1  $\rightarrow$  IC1,14
- J4,9  $\rightarrow$  IC1,14

# Electronic Measurement and Testing.

# Test Equipment Characteristics.

## Volt Meter (Reads Voltage)

- Two Forms of Meter
  - Analogue
    - Should be High Impedance.
    - Direct Low Frequency/Jitters reading possible.
    - Interpreted reading, Parallax on a background scale.
  - Digital
    - Should be High Impedance.
    - Subject to Quantization errors.
    - Advantage Direct reading display.
    - Can record RMS, Peak and Average readings.

See Document [labwork.pdf](#) section Experiment 1(Connections)

# Test Equipment Characteristics.

## Ammeter (Reads Current)

- Two Forms of Meter
  - Analogue
    - Should be Low Impedance.
    - Direct Low Frequency/Jitters reading possible.
    - Interpreted reading, Parallax on a background scale.
  - Digital
    - Should be Low Impedance.
    - Subject to Quantization errors.
    - Direct reading display.
    - Can record RMS, Peak and Average readings.

See Document [labwork.pdf](#) section Experiment 1(Connections)

# Test Equipment Characteristics.

## Multi-Meter (Reads Many Units)

- Two Forms of Meter
  - Analogue or Digital
    - Usually uses a switch to select Measurement type or measurement range.
    - Impedance should match the selected settings.
    - Main Readings Volts, Amps and Ohms.
    - Additional options that may also be available: Hfe, Diode Tests, Capacitance, Transistor checks, Frequency and Power measured in decibels dB.
  - Digital
    - May also record RMS, Peak and Average readings.

# Test Equipment Characteristics.

## Frequency Counter.

- Basic system will only measure frequency.
  - Will measure Frequency of a Signal.
    - Usually has a direct Digital Readout.
    - Input Impedance is high or will match source.
    - Connections BNC, N Type or Laboratory Terminal.
  - Can measure Period of a Signal.
    - May also record PRF Pulse Repetition Frequency, Time between Pulses, Direct count of pulses and other advanced features.

# Test Equipment Characteristics.

## Signal Generators.

- Create an alternating voltage with the ability to adjust both its Frequency and Amplitude.
  - Additional Features.
    - Usually has Variable Frequency control, Frequency Range control and can Vary the signal Amplitude.
    - Can generate different wave shapes (Sine, Square).
    - Can generate Logic Pulses (TTL , CMOS levels)
    - Can Modulate the primary signal (**Amplitude** AM , **Frequency** FM or **Pulse width** for logic systems)
    - Output Impedance is low or will match sink eg 50Ω.
    - Connections BNC, N Type or Laboratory Terminal.



# Test Equipment Characteristics.

## Oscilloscope.


- Measures voltage with respect to Time.
  - Additional Features.
    - Can display on screen one or two independent signals.
    - Has a graticule to enable measurements to be made of signal Height (Voltage) and Width (Time).
    - Can be use to measure signal Phase relationships or modulation depths.
    - May have storage capability and PC interconnect.
    - Input Impedance is very High  $1M\Omega$ .
    - Connections BNC, N Type or Laboratory Terminal.

See Document [labwork.pdf](#) section Experiment 1(Connections)

# Test Equipment Characteristics.

## Wheatstone Bridge.

- Measures Unknown Resistors.

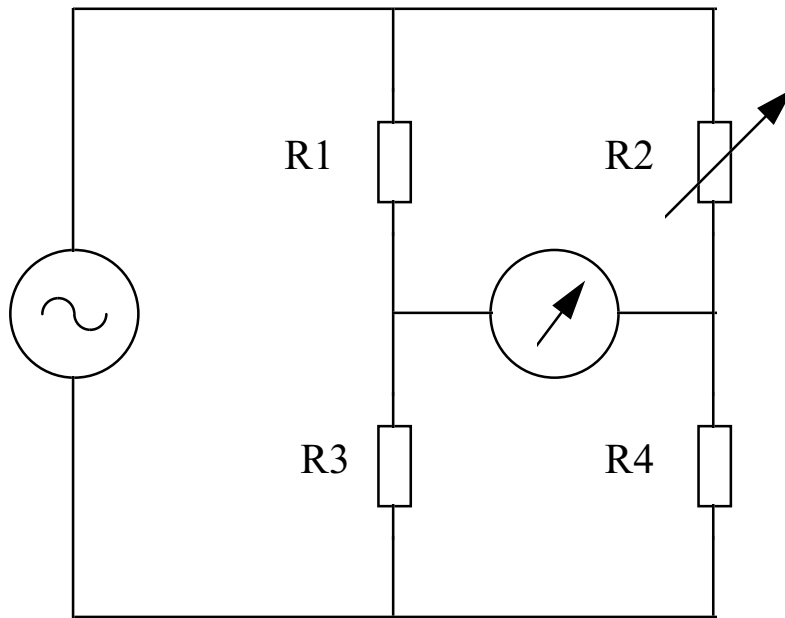

Measurement of  
Resistance by the  
Wheatstone Bridge  
Method


When Bridge Balanced

$$\frac{R1}{R3} = \frac{R2}{R4}$$

# Test Equipment Characteristics.
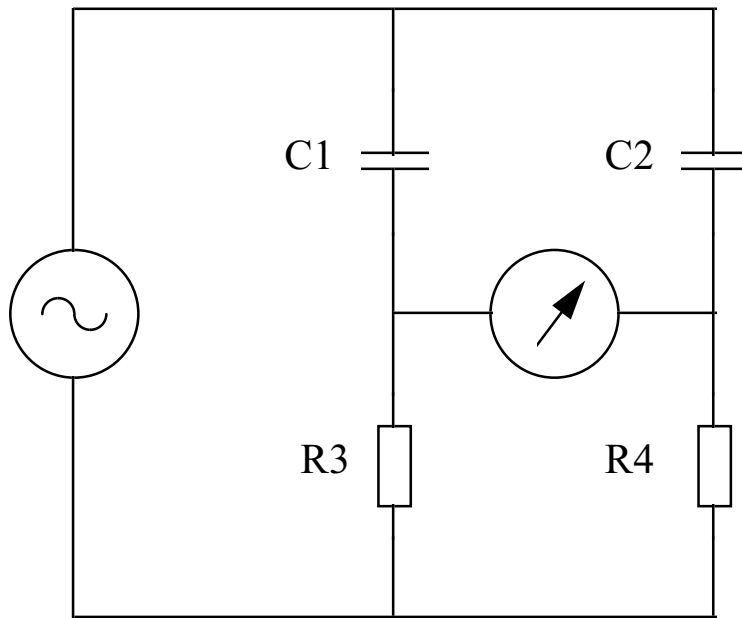
## AC Bridge.

- Measures Unknown Capacitors or Inductors.



Note:  $X_c = 1/2\pi fC$  or  $X_c \propto 1/C$

Measurement of  
Capacitance by the  
De Sauty's Method

When Bridge Balanced

$$\frac{X_{c1}}{R3} = \frac{X_{c2}}{R4} \quad \text{or} \quad \frac{R4}{R3} = \frac{X_{c2}}{X_{c1}}$$

$$\frac{X_{c2}}{X_{c1}} \cong \frac{1/C2}{1/C1} = \frac{C1}{C2}$$

So When the is Bridge Balanced

$$\frac{R4}{R3} = \frac{C1}{C2} \quad \text{or} \quad C1 = \frac{R4 * C2}{R3}$$

# Test Equipment Characteristics.

## AC Bridge.

- Measures Resistors, Capacitors or Inductors
  - Additional Features, observations.
    - Hardware can be configured to give a direct reading.
    - In practice you may need to adjust variables to give a minimum as phase differences may not allow a null to occur naturally.
    - Can be time consuming to take measurement and sometimes calculations are required.
    - Capacitor polarisation may cause bridge imbalance.
    - Connections Screw or Laboratory Terminal.

# Test Equipment Characteristics.

## Voltage Testers and Tracers.

- Indicate the presence of a Voltage
  - Additional Features, observations.
    - Often contain a Neon Lamp indicating a voltage present from about 80Volts up to 500Volts.
    - Neon lamp sometimes embedded in a Screw driver handle in series with a very high value resistor.
    - Specialist versions detect an electric field and amplify to give an audio output (Used in Telecommunications cable tracking and tracing activities)
    - Plug testers to indicate if wiring is correct.
- Proving Units are used to verify correct operation of Voltage Testers.

# Test Equipment Characteristics.

## Signal Tracers.

- Used to track Audio/RF signal in circuits.
  - Additional Features, observations.
    - Often contain RF (Radio Frequency) detector (simple diode Circuit) and low pass filter plus a variable gain Audio Amp to drive a speaker or similar device.
    - They allow you to track the path of a signal through a radio receiver, audio amplifier or similar system to identify a stage failure or fault conditions.
    - Some specialist tracers are used to monitor Network or Serial line communication wiring.

# Test Equipment Characteristics.

## Earth Loop Impedance Tester.

- Specialist Equipment for Electricians.
  - Additional Features, observations.
    - Used to measure the resistance of the Phase and Protective conductors in an Installation.
    - Modern equipment will apply appropriate test conditions and calculate cable impedance.
    - A fault condition circuit may draw a current in excess of 20 Amps.

# Test Equipment Characteristics.

## Signal Strength Meter.

- Used to measure Amplitude of radio Signals.
  - Additional Features, observations.
    - Used for checking transmitters, alignment of antenna and similar activities.
    - Consists of an untuned RF (Radio Frequency) detector (simple diode Circuit), low pass filter and a meter calibrated to indicate signal amplitude.
    - Connections BNC, N Type or F Type .



# Test Equipment Characteristics.

## Logic Probe/Pulser/Checker.

- Used to monitor signal levels or inject signals into Digital circuits.
  - Additional Features, observations.
    - Usually the probes take its power from the digital circuit under examination via fly leads.
    - The Probes usually have a test lead spike to connect to the digital circuit. The probe will indicate a logic **High** or Logic **Low** with coloured LEDs.
    - Sometime an additional sounder is available to indicate logic state being monitored.
    - A switch if often available on the probe to inject a Logic **High** into the circuit under test.

# Reliability.

# Reliability.

- **Definition**
  - Reliability is the ability of a component, equipment, or system to perform a required function under specified conditions for a specified period of time. (Woolard 1974)
- **Reporting Results of reliability test**
  - Identification of component - type, number, ratings, manufacture, date and place, sample selection, test description, department responsible for testing, test conditions, recorded results, accuracy of measurement, duration, failure criteria ....presentation of data etc ...

Barry G Woolard (1974) *Electrical Principles and Testing Methods*. McGraw-Hill Book Company (UK) Limited.

# Reliability.

- What is it ?
- The characteristic of an item expressed by the probability that it will perform a required function under stated conditions for a stated period of time.
- Why are we interested in this ?
- So we can predict and plan for potential problems in systems and develop strategies to cope with the implications, such as :-
  - Cost , Safety , Maintenance , Etc.

# Reliability.

- **What is Failure Rate?**
- Failure Rate is the average frequency with which something fails. Failure rate, often denoted by the Greek letter  $\lambda$  (Lambda)
- An alternative way of expressing Failure rate is the Mean Time Between Failure (MTBF) which is the average time between failures.
- **What are the control factors ?**
- Failure rate depends on the failure distribution, which describes the probability of failure prior to a specified time.


*<http://en.wikipedia.org/wiki/MTBF> accessed 28/March/2006*

# Reliability.

- What does this involve ?
- Introduction to Statistical methods
  - Graphical representations.
  - Using Calculations.
- Identify M.T.B.F  
Mean Time Between Failure.
- Identify probability of events.
  - With the simple models the average failure rate would be the same as the failure rate, this corresponds to an exponential distribution.

# Reliability.


$\lambda = \text{Lambda}$

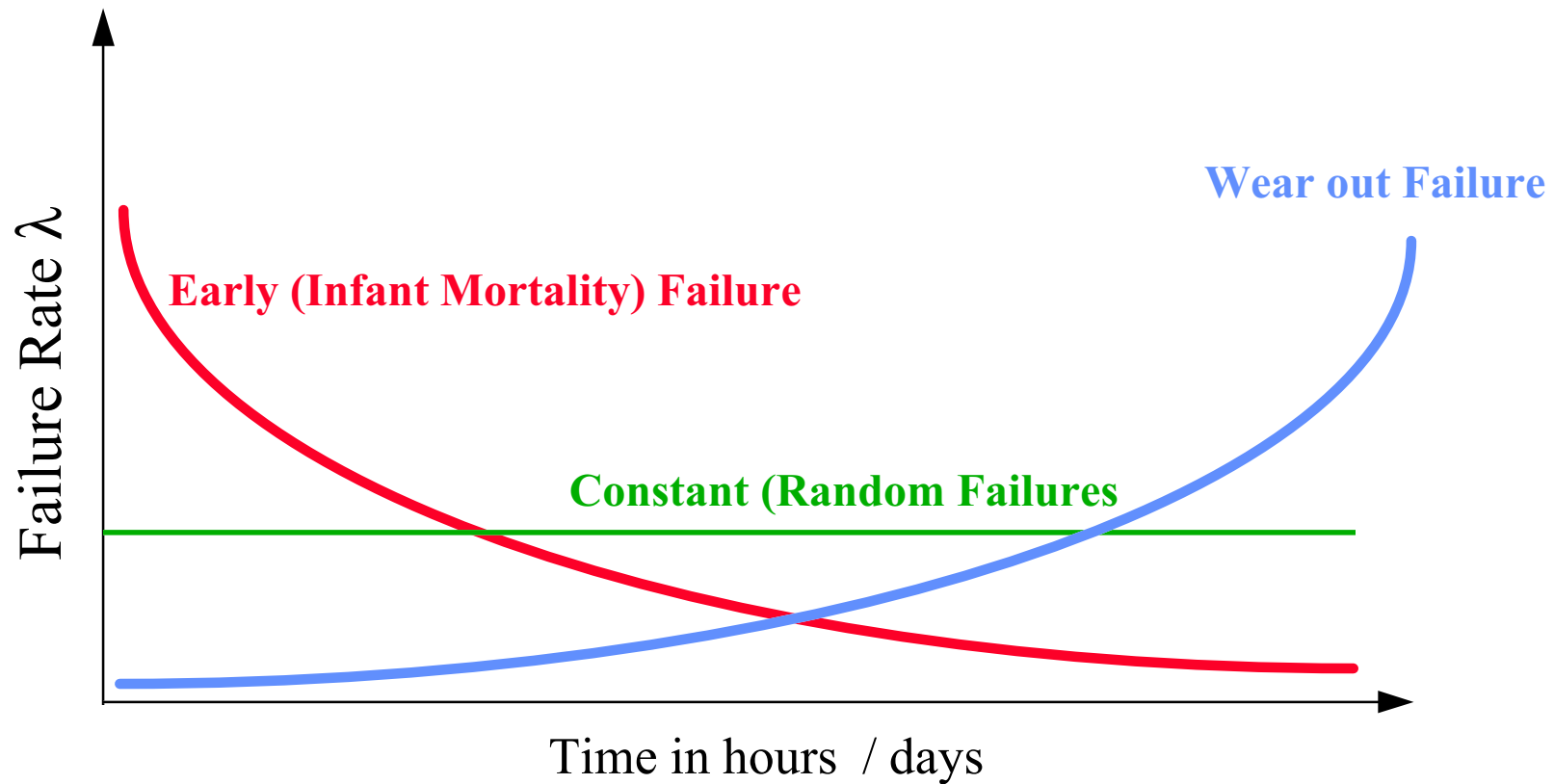

Failure rate-time curve (Factors)

# Reliability.

$\lambda = \text{Lambda}$

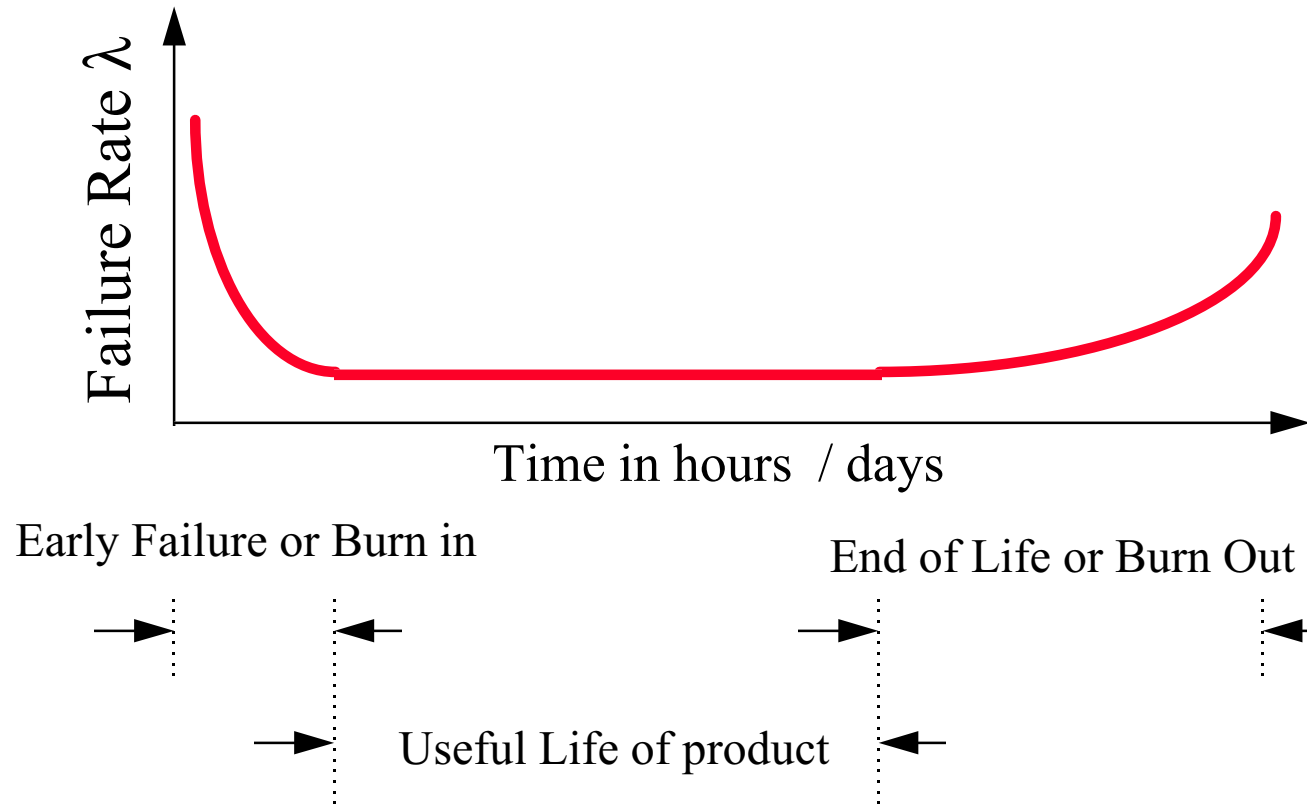


Failure rate-time curve (Bath tub diagram)


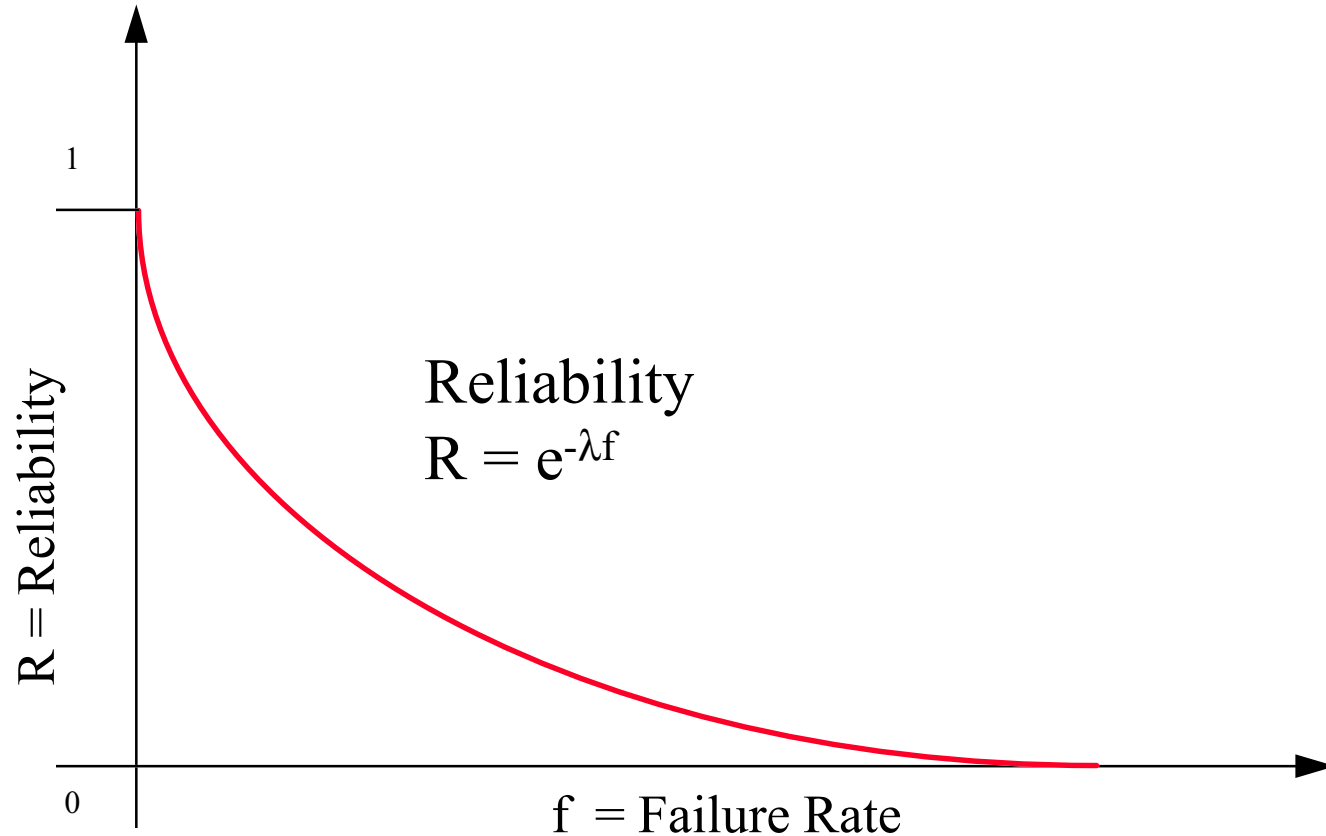
# Reliability.

$$\lambda = \text{Lambda}$$
$$e = 2.7182818$$




Exponential reliability function  
(for constant failure rate)

Reliability represented graphically.
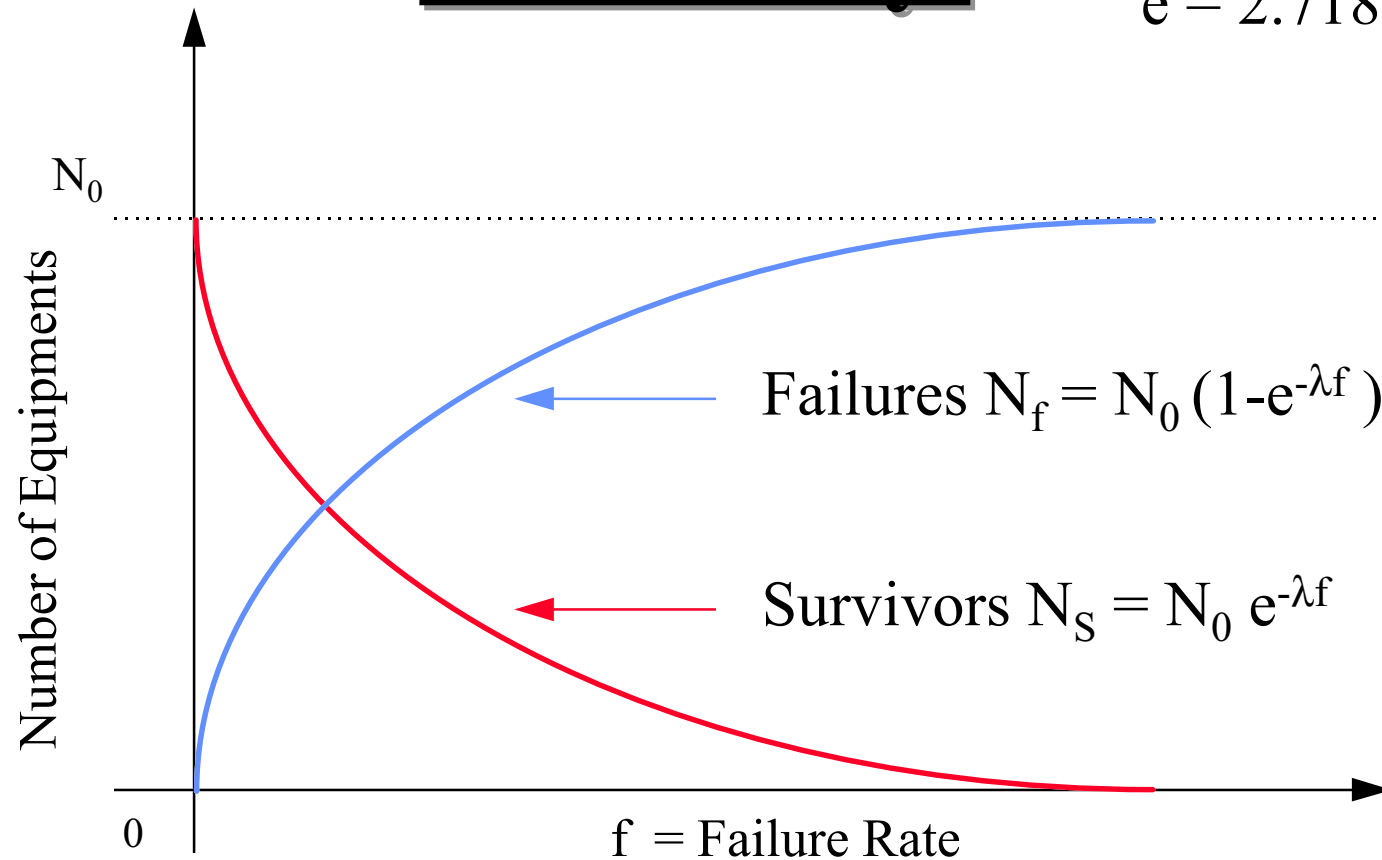
# Reliability.

$\lambda = \text{Lambda}$   
 $e = 2.7182818$



Survival and failure curves.

Reliability represented graphically.

# Reliability.

- Calculations
- Proportional Failure rate  $\lambda =$
- (Number of Failures  $\div$  Population )  $\div$  Period
- M.T.B.F Calculations.
  - M.T.B.F is Mean Time Between Failure.
  - $m =$  M.T.B.F calculated by :-
- $m =$  Total Survival Hours  $\div$  Total Population
  - where  $m = 1 \div \lambda$  or  $1 / \lambda$
- Calculate Reliability R
- $R = e^{-t/m}$  or  $R = e^{-t \lambda}$ 
  - where  $\lambda = 1 \div m$  or  $1/m$

Example

# Reliability.

Solution 1.

- What is the probable number of Failures from a batch of 600 items after 350 hours if the failure rate = 0.0027%/hour
- Proportional Failure rate  $\lambda =$   
(Number of Failures  $\div$  Population )  $\div$  Period
- Failure rate  $\lambda = 0.0027 / 100 = 0.000027$
- so  $\lambda = 0.000027 = (\text{NoF} / 600) / 350$
- or  $0.000027 * 350 = (\text{NoF} / 600) = 0.00945$
- or  $0.00945 * 600 = \text{NoF} = 5.67 \cong \underline{\underline{6 \text{ Failures.}}}$
- By implication we have  $600 - 6 = 594$  Survivors.

Example

# Reliability.

Solution 2.

- What is the probable number of Failures from a batch of **600** items after **350** hours if the failure rate = 0.0027%/hour
- Proportional Failure rate  $\lambda =$   
(Number of Failures  $\div$  Population )  $\div$  Period
- 1 hour Failure rate  $\lambda = 0.0027 / 100 = 0.000027$
- 350 hour Failure rate =  $\lambda * 350 = 0.00945 = \lambda f$
- Failures  $N_f = N_0 (1 - e^{-\lambda f}) = 600 (1 - e^{-0.00945})$
- or  $600 * 0.009405 = \text{NoF} = 5.64 \cong \underline{\underline{6 \text{ Failures.}}}$
- Survivors  $N_s = N_0 e^{-\lambda f} = 600 e^{-0.00945}$
- or  $600 * 0.99059 = 594.3 \cong \underline{\underline{594 \text{ Survivors.}}}$

## Example

# Reliability.

- Calculate the failure rate of a batch of lamps if there are 62 failures from a population of 950 items over a period of 5000 hours.
- Calculate failure rate factor (Failures/Population)
- Calculate proportional failure rate  $\lambda$
- $\lambda = (62/950) / 5000 = 13.05 * 10^{-6}$  failures / hour
- Percentage failure rate =  $13.05 * 10^{-6} * 100\%$
- Percentage failure rate =  $0.001305\%$  / hour
- The **Normal Failure Rate** expressed as a percentage per 1000 hours therefore the failure rate is :-
- failure rate =  $0.001305 * 1000 = 1.305 \rightarrow \rightarrow$
- failure rate =  $1.305\%$  / 1000 hours

## Example

# Reliability.

- The M.T.B.F of an equipment is 7500 hours.  
Calculate the reliability of the equipment during a period of 150 hours.
- $R = e^{-t/m}$
- $R = e^{-150/7500}$
- $R = e^{-0.02}$
- therefore  $R = 0.980198$
- or R as a percentage  $0.980198 * 100\% = 98.0198\%$
- Summary :-
- This means that the probability of 150 failure free running hours is circa 98.02%.

Example

# Reliability.

Note:  $\log_n n = 1$

- Calculate the failure rate of an electronic component over a period of 620 hours if the reliability is 96.5%.
- Convert Percentage to a Reliability value.  
 $96.5\% / 100\% = 0.965$
- Reliability  $R = e^{-t\lambda}$
- $\therefore 0.965 = e^{-620\lambda}$        $\therefore 0.965 = 1 / e^{620\lambda}$
- $\therefore e^{620\lambda} = 1 / 0.965$       (Take Logs on both sides)
- $\therefore \log_e e^{620\lambda} = 620\lambda \log_e e = 620\lambda = \log_e (1/0.965)$
- $\therefore \lambda = (1/620) \log_e (1/0.965)$
- $\therefore \lambda = (0.0016129) \log_e (1.0362694) = 0.000057463$
- $\therefore$  Failure rate = 0.057463% / hour
- $\therefore$  Failure rate = 5.7463% / 1000 hours



## Example

# Reliability.

- Using the table shown on the right calculate the failure rate.
- Ten identical components were tested until they failed or operated correctly for 1000 hours.
- Failure Rate = Failures/Time(hours)
- 6 Failures / 6779 hours which gives = 0.000885 failures per hour
- or 0.00885% / Hour
- or 8.85% / 1000 Hours

Component	Hours	Status
Lamp 1	1000	No Failure
Lamp 2	104	Failure
Lamp 3	523	Failure
Lamp 4	1000	No Failure
Lamp 5	769	Failure
Lamp 6	356	Failure
Lamp 7	1000	No Failure
Lamp 8	215	Failure
Lamp 9	1000	No Failure
Lamp 10	812	Failure
Totals	6779	6

# Testing.

# Power Supply Unit.

- Reference voltage set by Zener Diode.
- Testing:
- Use the following load resistors to identify the regulation characteristics of the power supply.
  - 2200, 1000, 680, 470, 330, 270, 220, 100, 47, 33, 22, 10 Ohms
- Compare Calculated and measured values.

# The EMT Amplifier Construction.

- Remember **DO NOT** insert the Input, Output or Power connectors (Not Needed for Testing).
- Insert fixed value Resistors.
  - (Read values Top to Bottom or Left to Right)
- Insert Chip Socket. (Ensure correct way round)
  - Look for the notch (the pin one mark)
- Insert Diode (Ensure polarity correct)
  - The mark/ring indicates the Cathode (Negative)
- Insert Test Point connector (Only)      Ensure R1 ( $33\Omega$ )
- Insert Capacitor      is raised about
- Insert Variable Resistor      8mm above PCB


# Year 2 Work.

# TTL or CMOS Gates.

<u>Device Type</u>	<u>TTL 74 LS Series</u>	<u>CMOS 4000</u>
2 input AND	74LS08	4081
3 Input AND	74LS15	4073
4 Input AND	74LS21	4082
2 input OR	74LS32	4071
3 Input OR	Convert	4075
4 Input OR	Convert	4072
2 input NAND	74LS00	4011
3 Input NAND	74LS10	4023
4 Input NAND	74LS20	4012
2 input NOR	74LS02	4001
3 Input NOR	74LS27	4025
4 Input NOR	74LS25	4002
Dual D Type	74LS74	4013
4 to 1 Multiplexer	74LS153	4052
8 to 1 Multiplexer	74LS151	4051
16 to 1 Multiplexer	74LS150	4067

# Revision Page

<b><u>Title</u></b>	BTEC National Coursework
<b><u>Author</u></b>	R. J. Spriggs
<b><u>Last Update</u></b>	14/May/2007
<b><u>Version</u></b>	1.42
<b><u>Edit</u></b>	0101

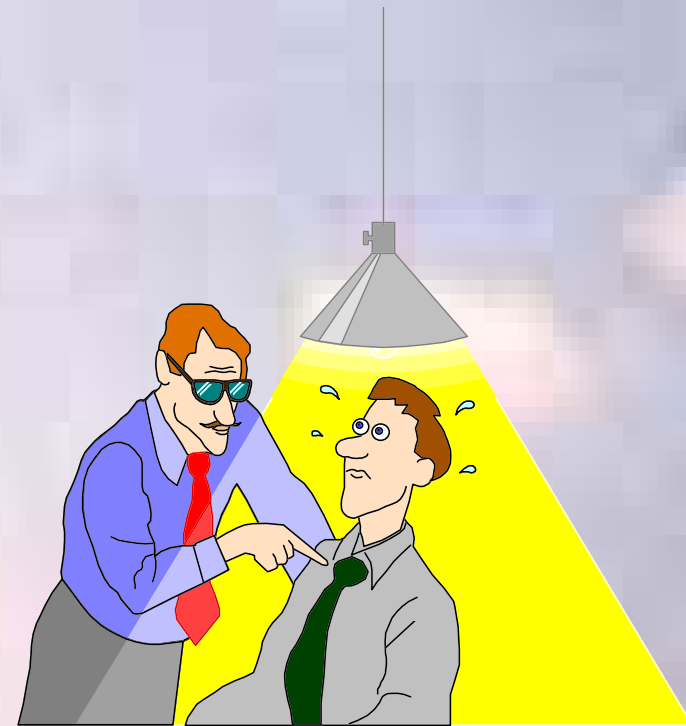

**End Slide**