

# ELECTRONICS


## Practical

# Experiment 1.



# The Test Equipment.

## Digital Meter

## Analogue Meter

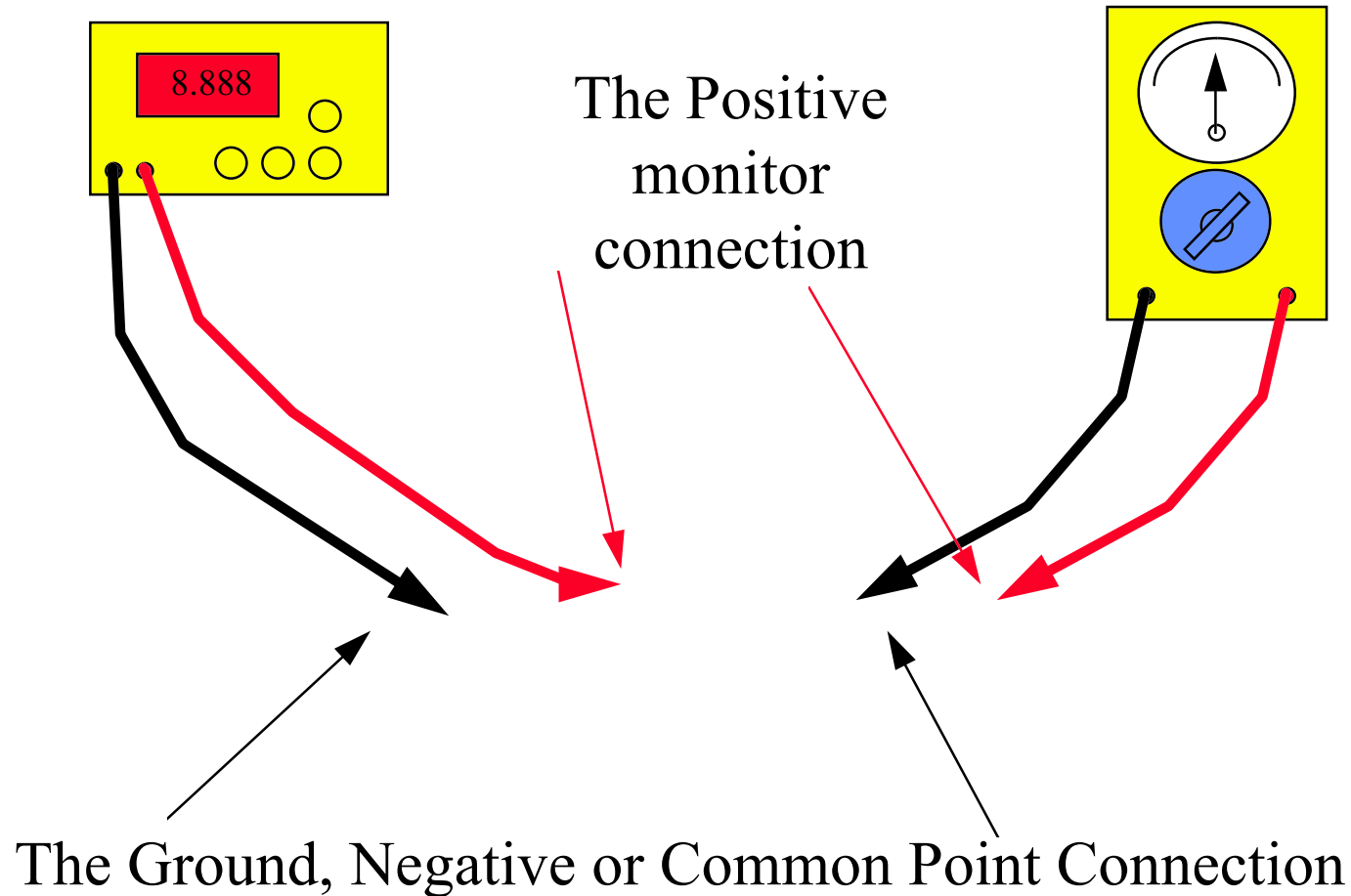

# The Test Equipment.

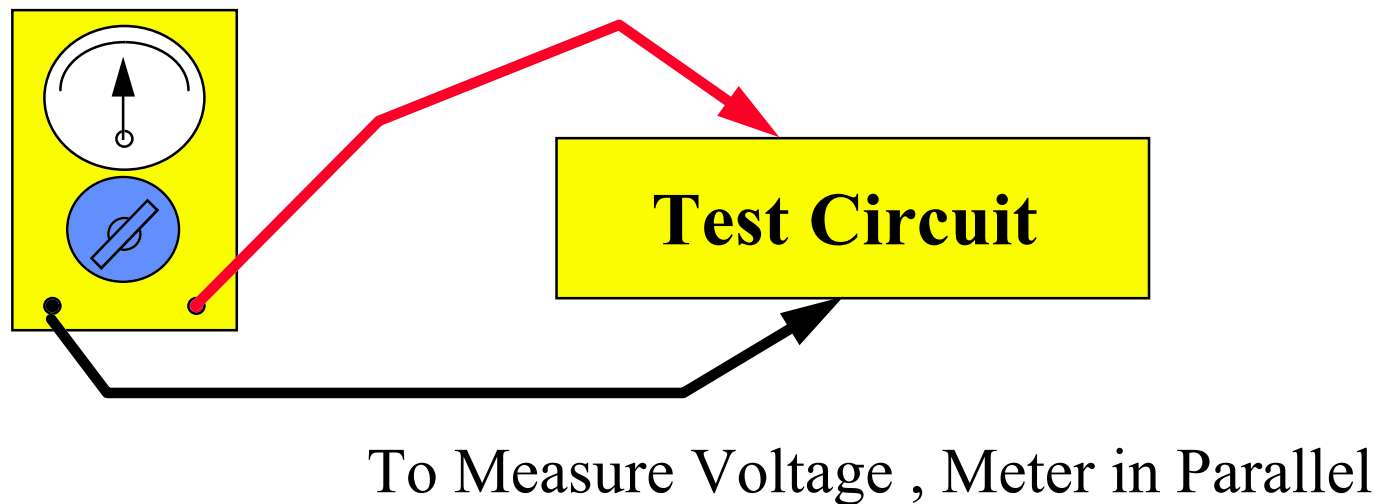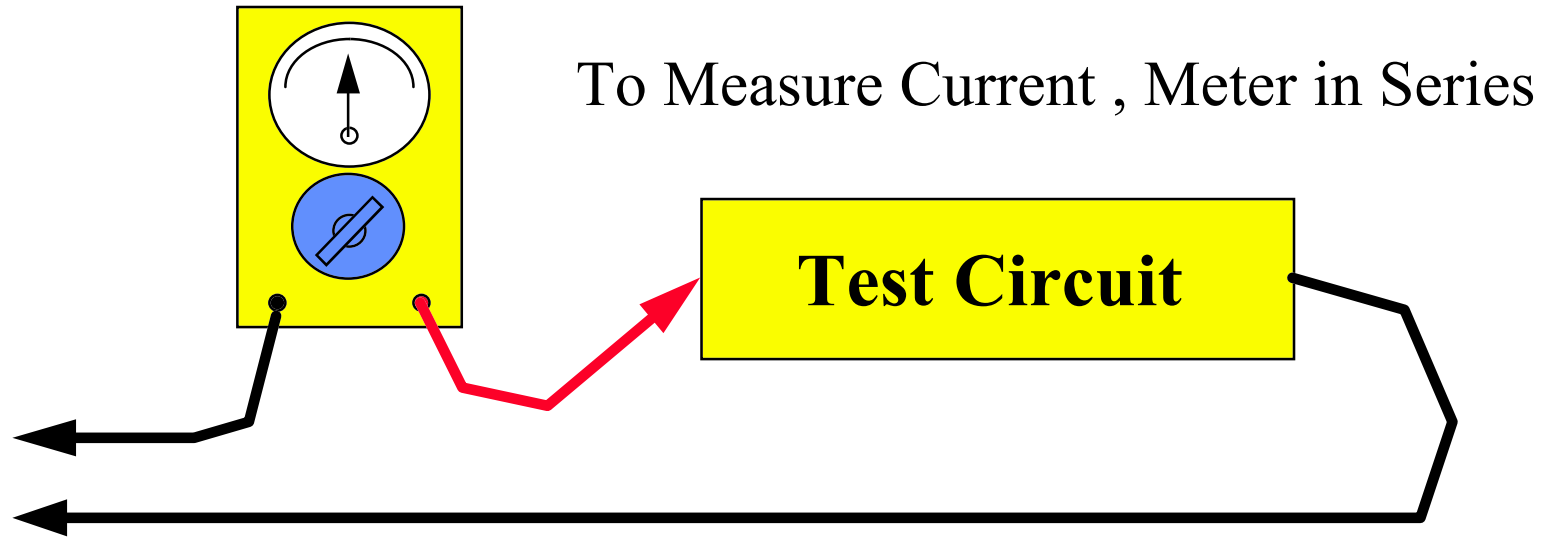


# The Test Equipment.

- Measuring an **Unknown** Current or Voltage Set meter to maximum value first. Then reduce settings until you get a valid reading.
- Current measurement in Series.
- Voltage measurement are in parallel with circuit/component.
- Always Check - AC setting for AC readings and DC settings for DC readings.


# The Test Equipment.

## The Oscilloscope

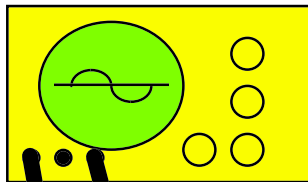

Channel 1 = Your Reference Signal  
or the signal you want to measure.

Channel 2 = The Compare Signal.

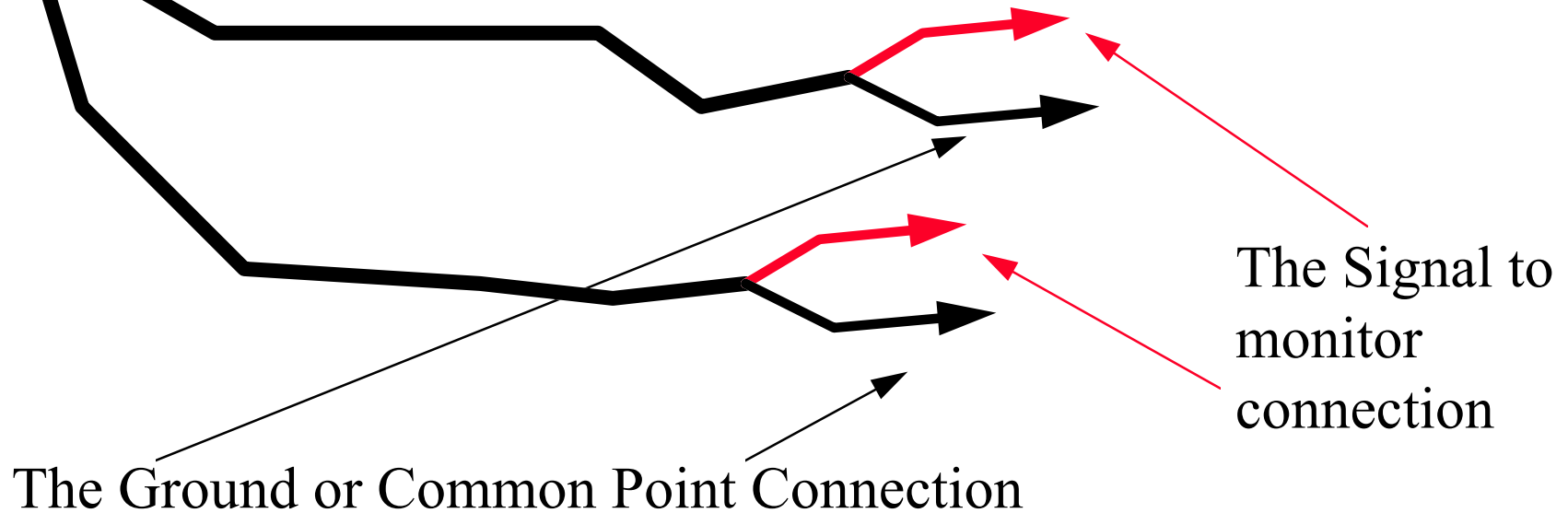

# The Test Equipment.

- The Cathode Ray Oscilloscope  
(CRO pronounced “crow”).
- Measures Voltage with respect to Time.
- The Timebase set the speed that the beams moves across the screen (One Screen unit per unit of time {the period} )
- The trigger control help set a stable display.
- Voltage is measured by using the vertical amplifier settings so many screen units/Volt.


# LED and Resistors.

- Build “Circuit 1”. Did LED light up ?
- What happens when LED is reversed ?
- What differences and problems did you notice when measuring voltages using the Analogue meter, Digital Meter, and the Cathode Ray Oscilloscope (CRO pronounced “crow”).
- How did you measure the current in the circuit. (Draw a diagram)



# LED and Resistors.

Measure Current  
in the circuit

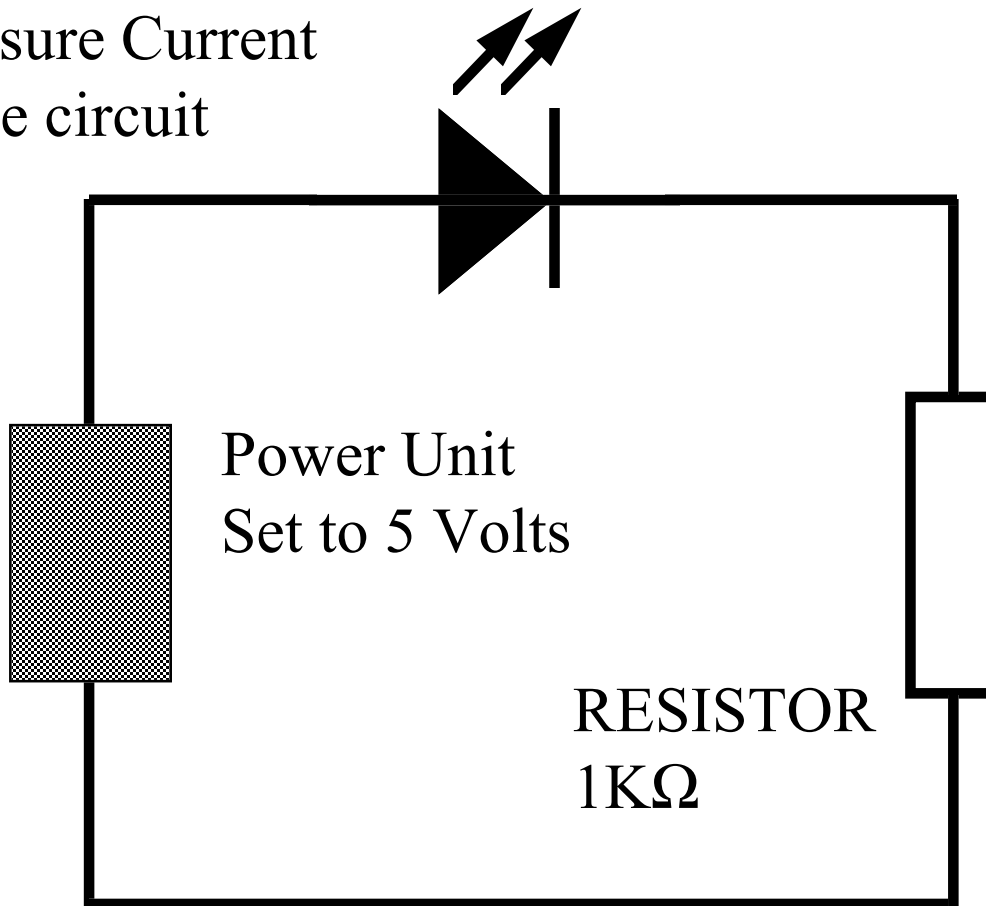

Measure Voltage  
across every  
component in  
circuit.

Mark Polarity of  
voltages around  
circuit when LED  
is lit up

**Circuit 1**


# **LED and Resistors.**

- Modify your board to “Circuit 2”.
- What happened to LED brightness ?
- Record the Voltages around the circuit.
- Record the current used by the circuit.

# LED and Resistors.

Measure Current  
through the LED

Measure Voltage across every  
component in circuit.

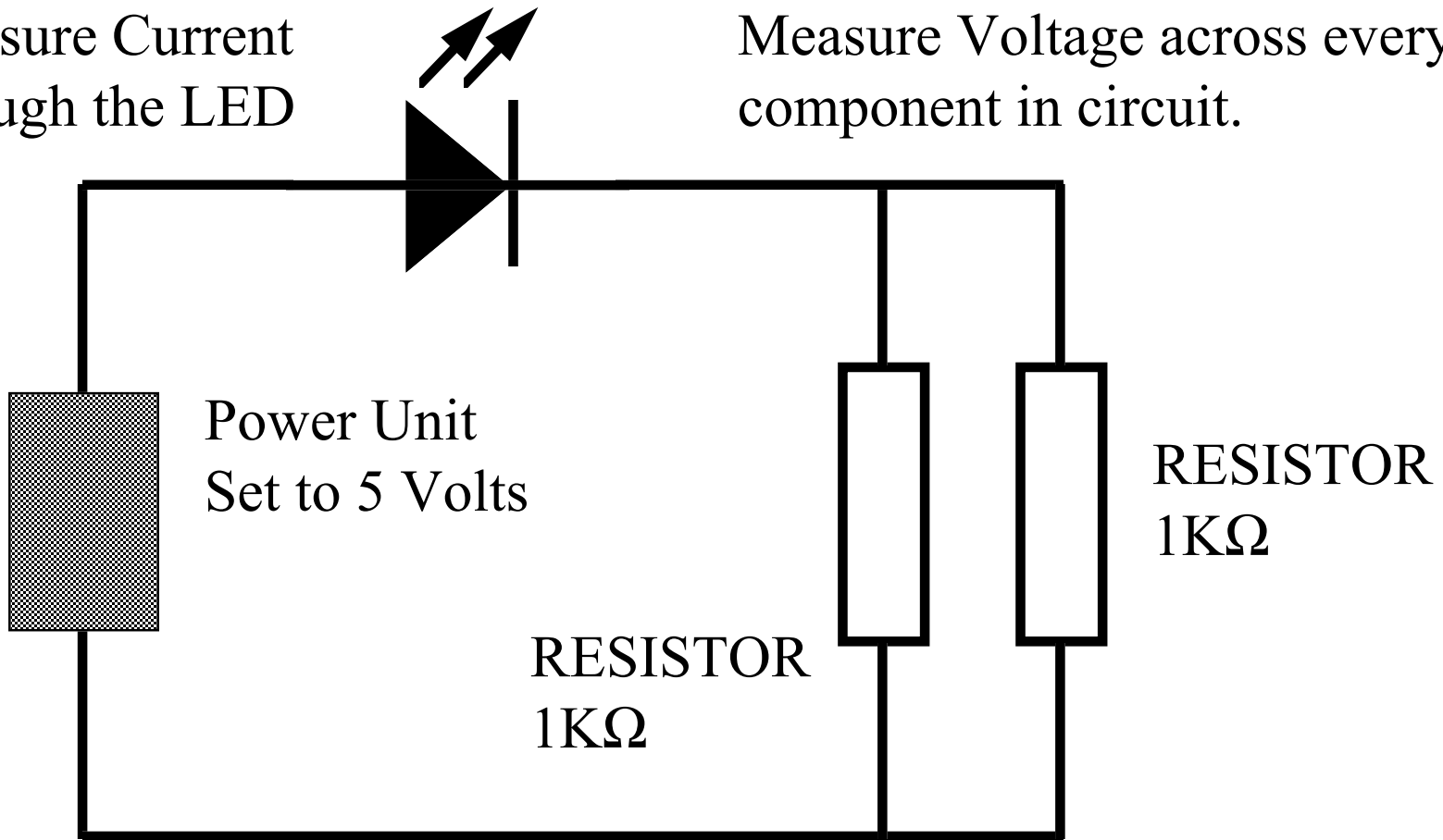

Circuit 2


# **LED and Resistors.**

- Modify your board to “Circuit 3”.
- What happened to LED brightness ?
- Record the Voltages around the circuit.
- Record the current used by the circuit.

# LED and Resistors.

Measure Current  
through the LED


Measure Voltage across every  
component in circuit.

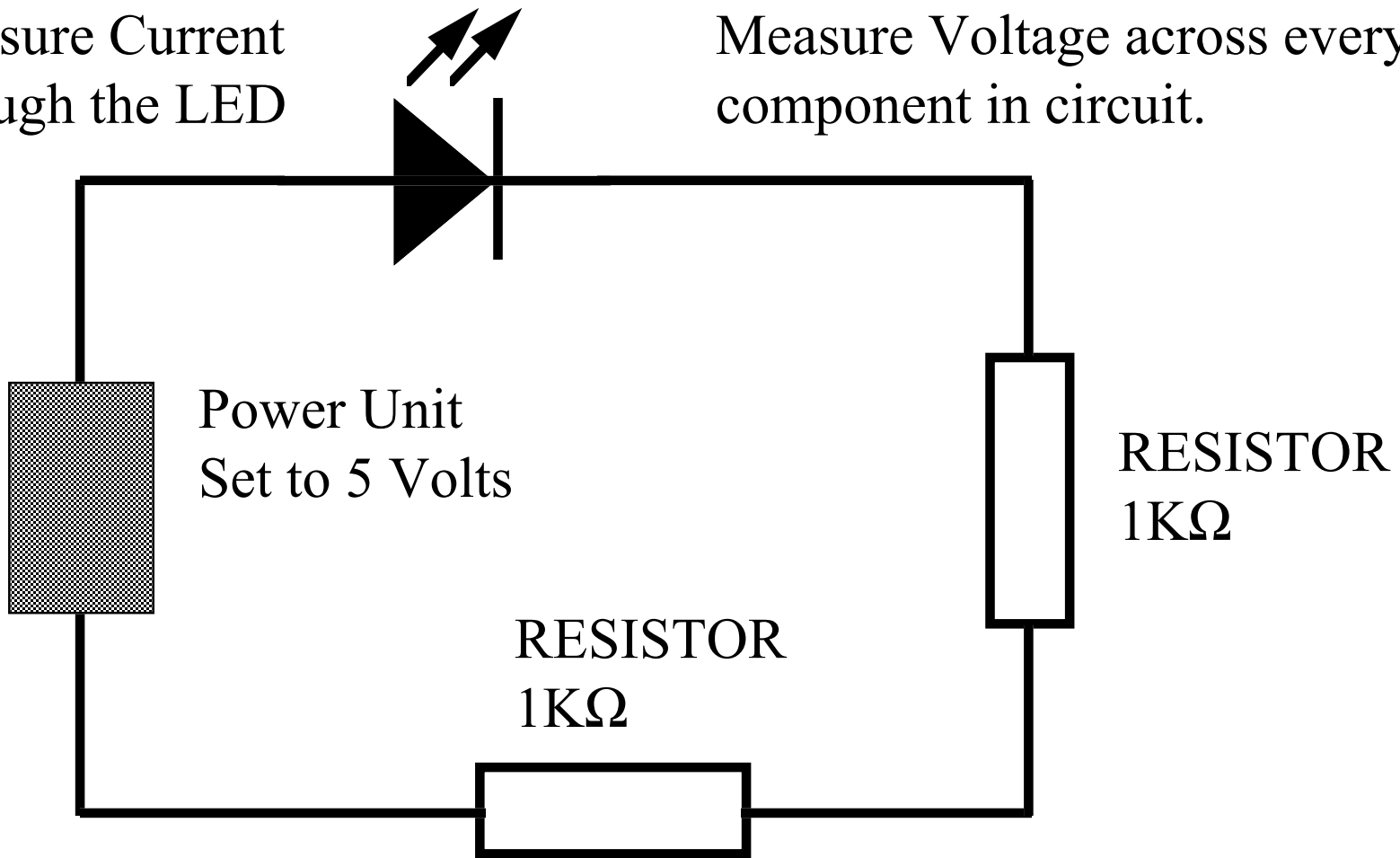


Circuit 3

# Experiment 2.


# The Test Equipment.

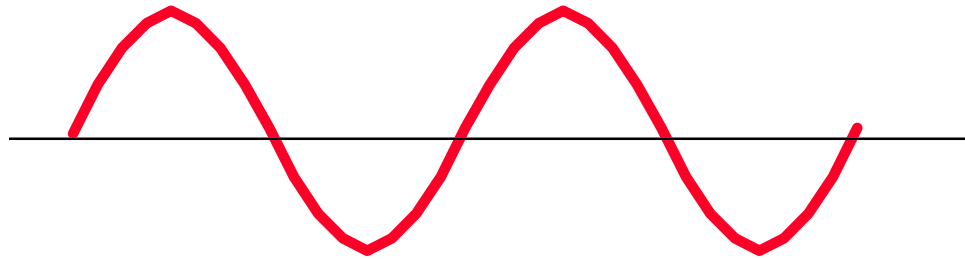

Sine Wave

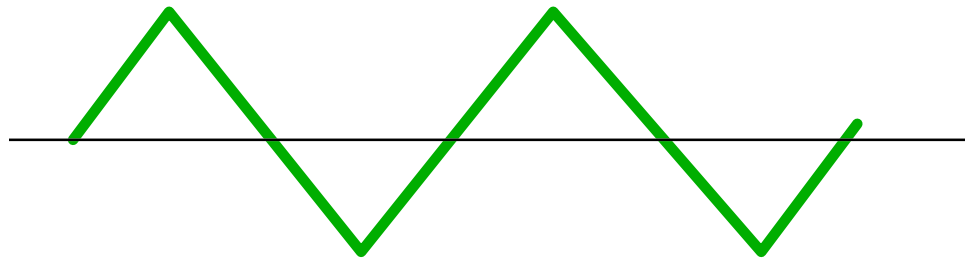


Triangle Wave

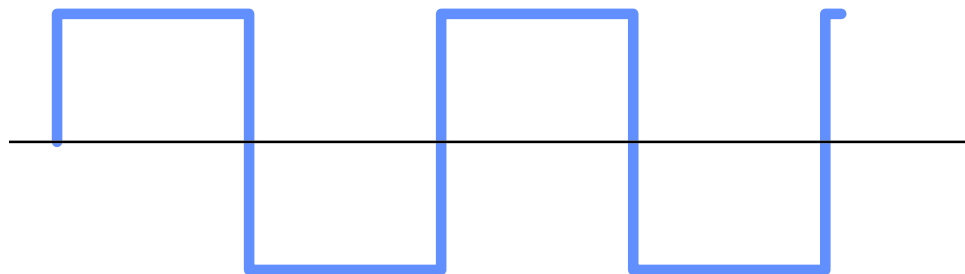

Square Wave

## Typical Signal Generator Waveshapes.

# The Test Equipment.

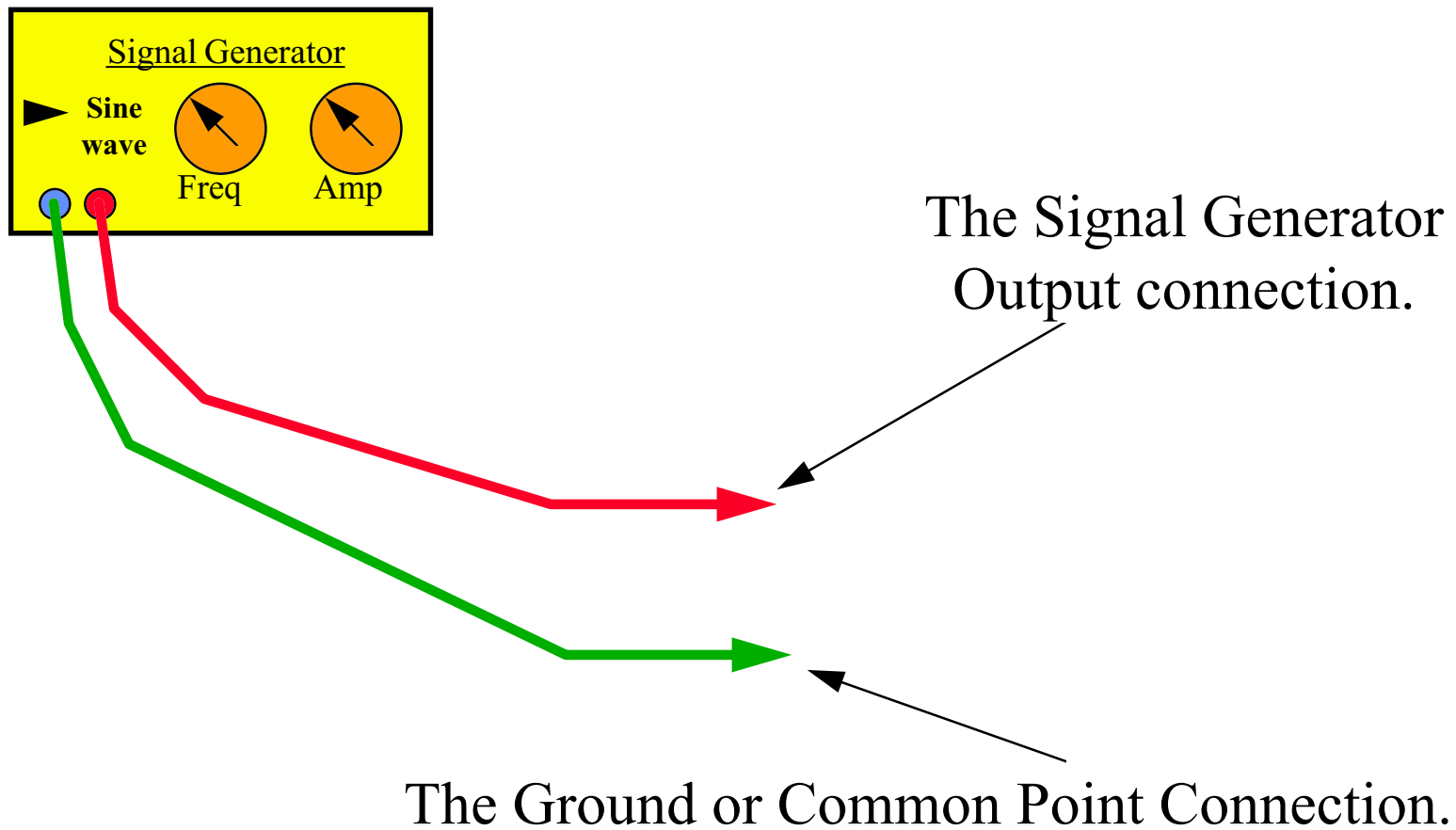



# The Test Equipment.

- The Signal Generator.
- Used to produce various waveshapes  
Sine, Square and Triangle waves .
- Frequency of waveshapes can be adjusted  
from Hz to KHz.
- Amplitude (height of signal) can be  
adjusted. The attenuator is used to extend  
the range of the amplitude adjustment.

# Frequency and Amplitude.

- Amplitude (Measure height of Signal).
- Frequency, Period Conversion.
- Period measure time units between two repeating points of a waveform.


$$\text{Frequency} = \frac{1}{\text{Period}}$$

or

$$\text{Period} = \frac{1}{\text{Frequency}}$$

# Frequency and Amplitude.

Set Signal generator to Sine wave with a frequency to 1000Hz and amplitude to 200mV

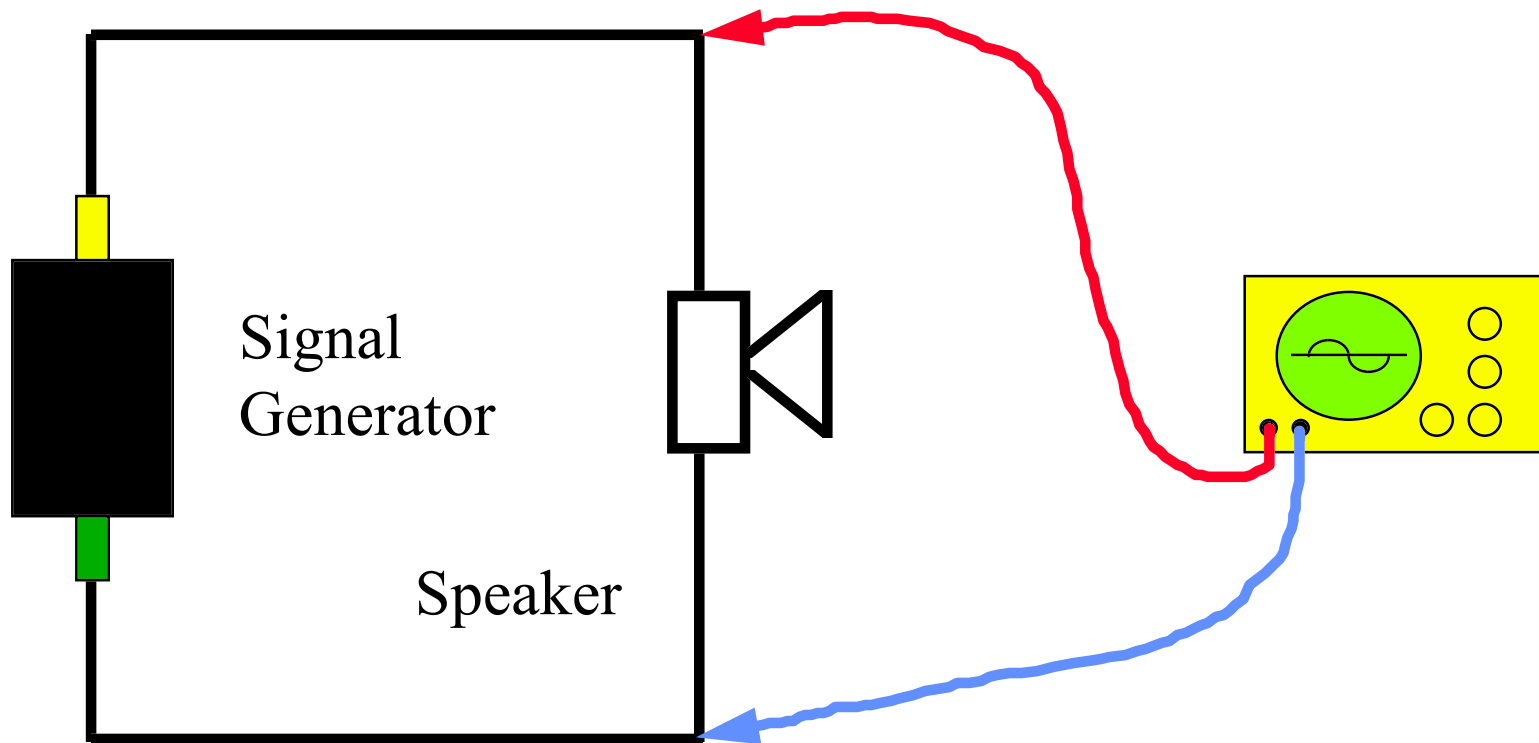

Circuit 1

# Frequency and Amplitude.

- Build “Circuit 1”.
- With initial setting sketch CRO display.
- Increase Amplitude what is the effect on volume ?
- What is the lowest level of amplitude you can hear ?
- If you double the amplitude does volume double ?

# Frequency and Amplitude.

- Adjust amplitude to comfortable level.
- Set frequency to 100Hz keeping amplitude the constant. What effect is noticed ?
- Set frequency to 10KHz keeping amplitude the constant. What effect is noticed ?
- What is lowest frequency you can hear.
- What is highest frequency you can hear.
- Change wave shape. What effect did this have ?

# Frequency and Amplitude.

- On one or more diagrams.
- Mark where peak voltages occur.
- Mark where zero crossing occurs.
- Measure a Peak Voltage.
- Measure a Peak to Peak Voltage.
- Measure waveshape period.
- Relate waveshape period to frequency.
- Calculate an RMS and Average voltage from a peak value.

# Experiment 3.


# Voltage dividers 1.

- Build “Circuit 1”.
- Measure and record voltages across R1 & R2 with CRO then confirm readings using Digital meter then Analogue meter.
- Are readings consistent ?
- Change R1 & R2 to  $1\text{K}\Omega$
- Repeat measurements and record voltages using CRO, Digital and Analogue meters.
- Are readings consistent ? (Explain)



# Voltage dividers 1.

Set Power unit to 5V

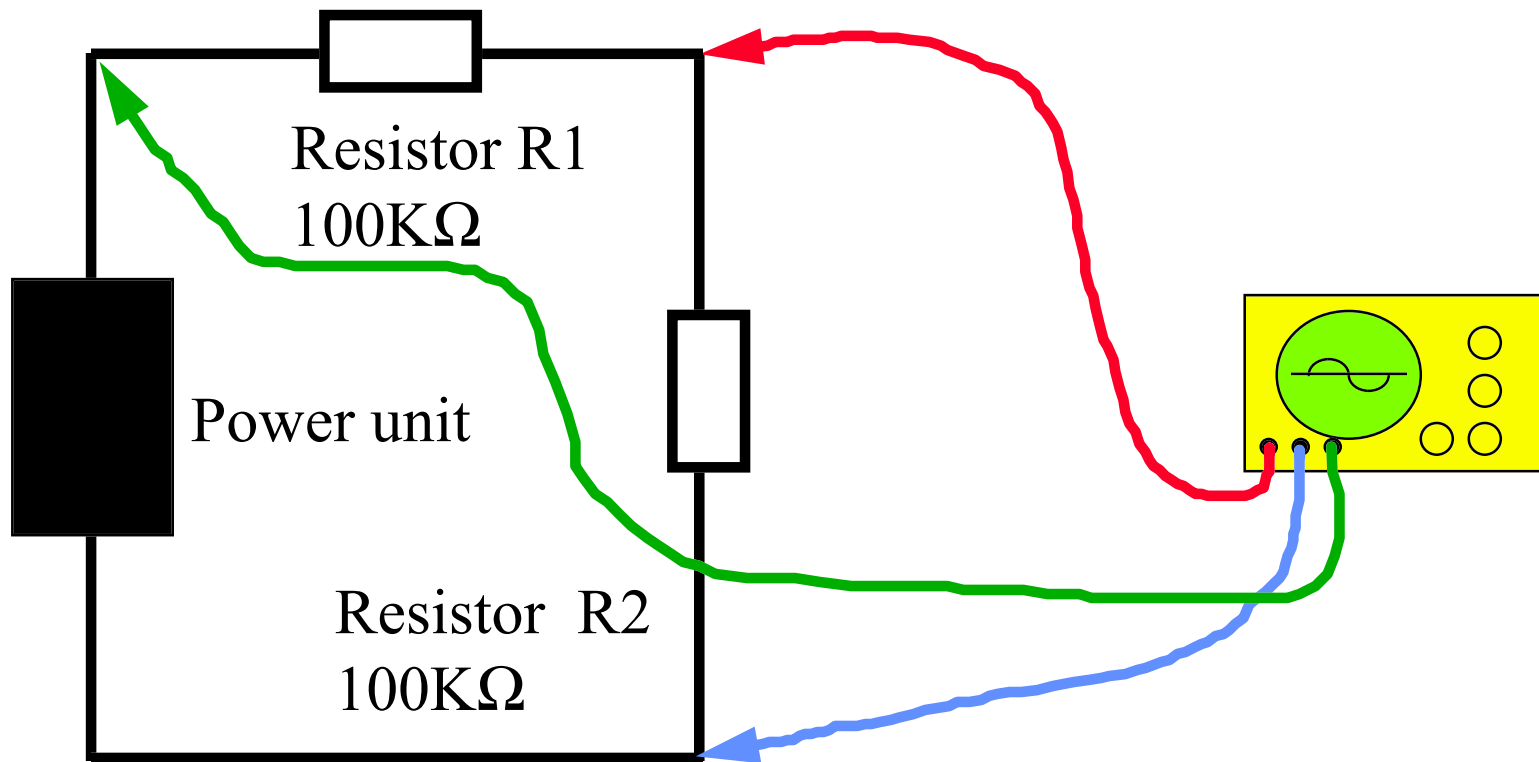

Circuit 1

# Voltage dividers 1.

- Calculate expected voltages and compare with actual readings.
- Change R1 to  $10\text{K}\Omega$
- Calculate expected voltages and compare with actual DVM readings.
- Change R1 to  $1\text{K}\Omega$  and R2 to  $10\text{K}\Omega$  .
- Calculate expected voltages and compare with actual DVM readings.


# Voltage dividers 1.

- Calculation method :-
  - $R_T$  = Resistance Total,      $R_n$  = Resistor 'n'
  - $V$  = Volts,      $I$  = current.
- 1. Calculate total circuit resistance ( $R_T$ ).
- 2. Calculate current flowing in  $R_T$ .      $\{V/R_T\}$
- 3. Calculate voltage across  $R_n$ .      $\{I * R_n\}$

# Experiment 4.

# Capacitors and Resistors.

Set Both Power Units to 5V

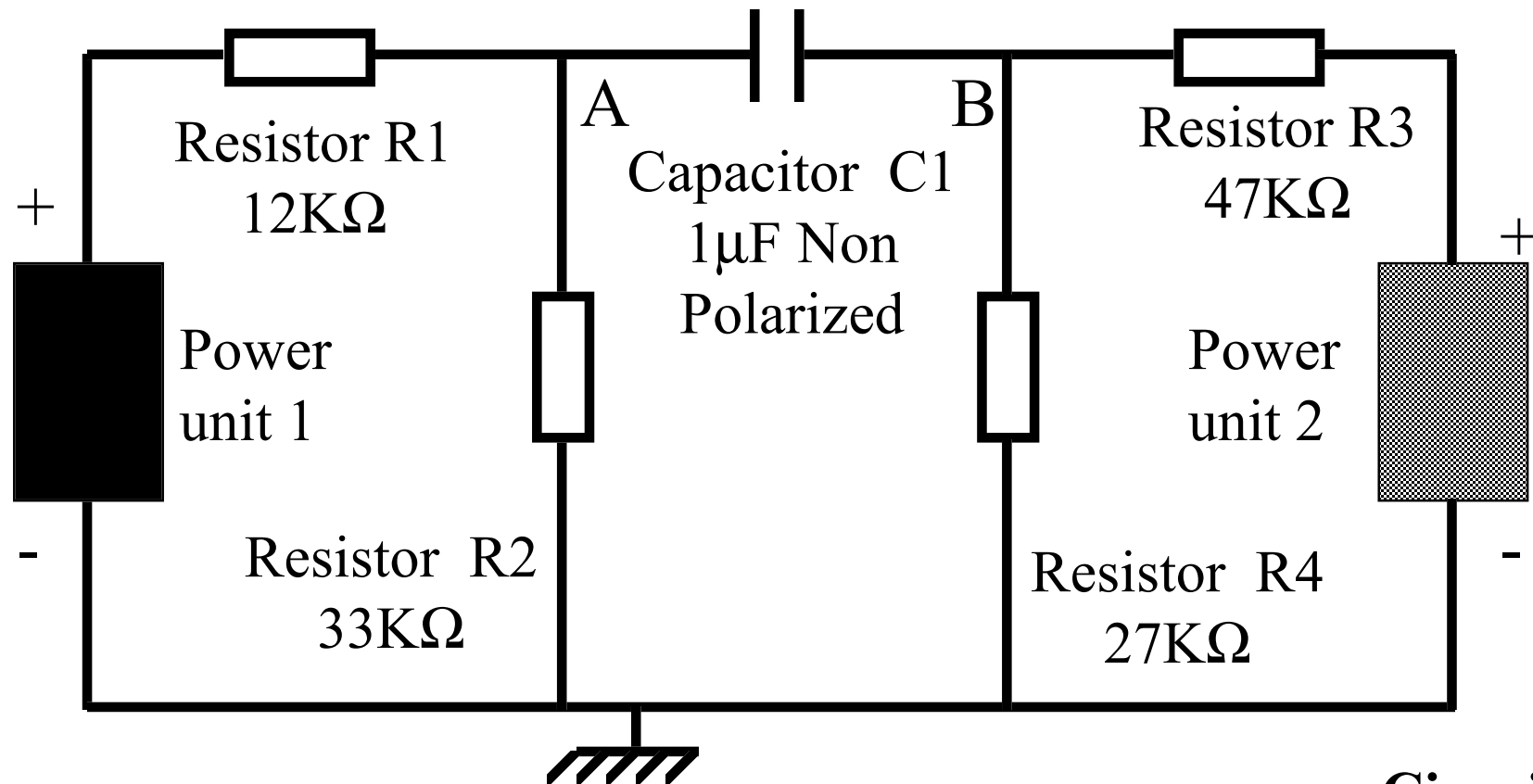


Circuit 1

# Capacitors and Resistors.

- Build “Circuit 1”.
- Measure Voltage across all resistors using a DVM (Digital Volt Meter).
- Calculated expected voltages at points ‘A’ and ‘B’.
- Conclusion.
- Do Voltages agree with your calculations?
- Did capacitor effect the DC levels?

# Capacitors and Resistors.

Set Signal generator to Sine wave with a frequency of 1000Hz and the amplitude set to 1 Volt peak to peak.

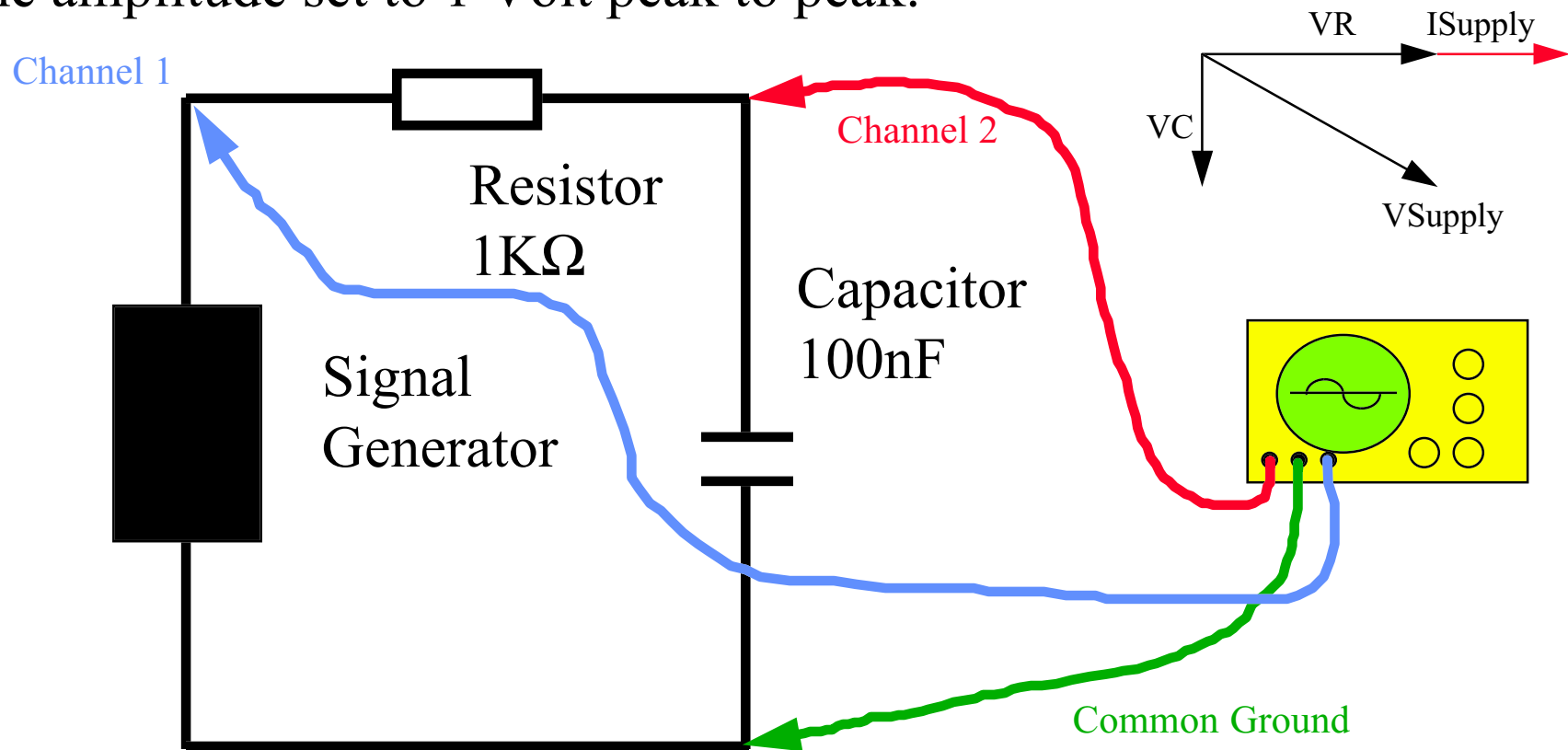

**Circuit 2**

# Capacitors and Resistors.

- Build “Circuit 2”.
- With initial setting sketch the CRO display.
- Increase frequency to 10KHz what is the effect on the voltage across the resistor ?
- Decrease frequency to 100Hz what is the effect on the voltage across the resistor ?
- Sketch the changes for all settings.



# Capacitors and Resistors.

- Calculate value of Capacitor using the measurements taken with 1KHz Signal.
  - Calculate Voltage across resistor:-
    - $V_{\text{Resistor}} = \sqrt{V_{\text{source}}^2 - V_{\text{Capacitor}}^2}$ .
  - Calculate Current through the Resistor and the Capacitor (they are in series):-
    - $I_{\text{Resistor}} = I_{\text{Capacitor}} = V_{\text{Resistor}} / \text{Resistance}$ .
  - Calculate Reactance of the Capacitor:-
    - Capacitor Reactance  $X_c = V_{\text{Capacitor}} / I_{\text{Capacitor}}$ .
  - Calculate Capacitance of the Capacitor:-
    - Capacitance  $C = 1 / (2 * \pi * f (\text{frequency} = 1\text{KHz}) X_c)$ .

# Capacitors and Resistors.

- Change capacitor in “Circuit 2” to 1 $\mu$ F.
- With initial setting sketch CRO display.
- Increase frequency to 10KHz what is the effect on the voltage across the resistor ?
- Decrease frequency to 100Hz what is the effect on the voltage across the resistor ?
- Sketch the changes for all settings.

# Capacitors and Resistors.

- Conclusion:
- How do the measured results compare with the calculated values.
- How did the frequency effect the impedance of the CR network circuit.
- When a DC voltage was applied to the capacitor what impedance / resistance did it present.

# Experiment 5.

# Amplifiers.


Using the LM324

Pin 4 is +ve Supply

Pin 11 is -ve Supply

$$R1 = R2 = 100K\Omega$$

$$VR1 = 10K\Omega$$


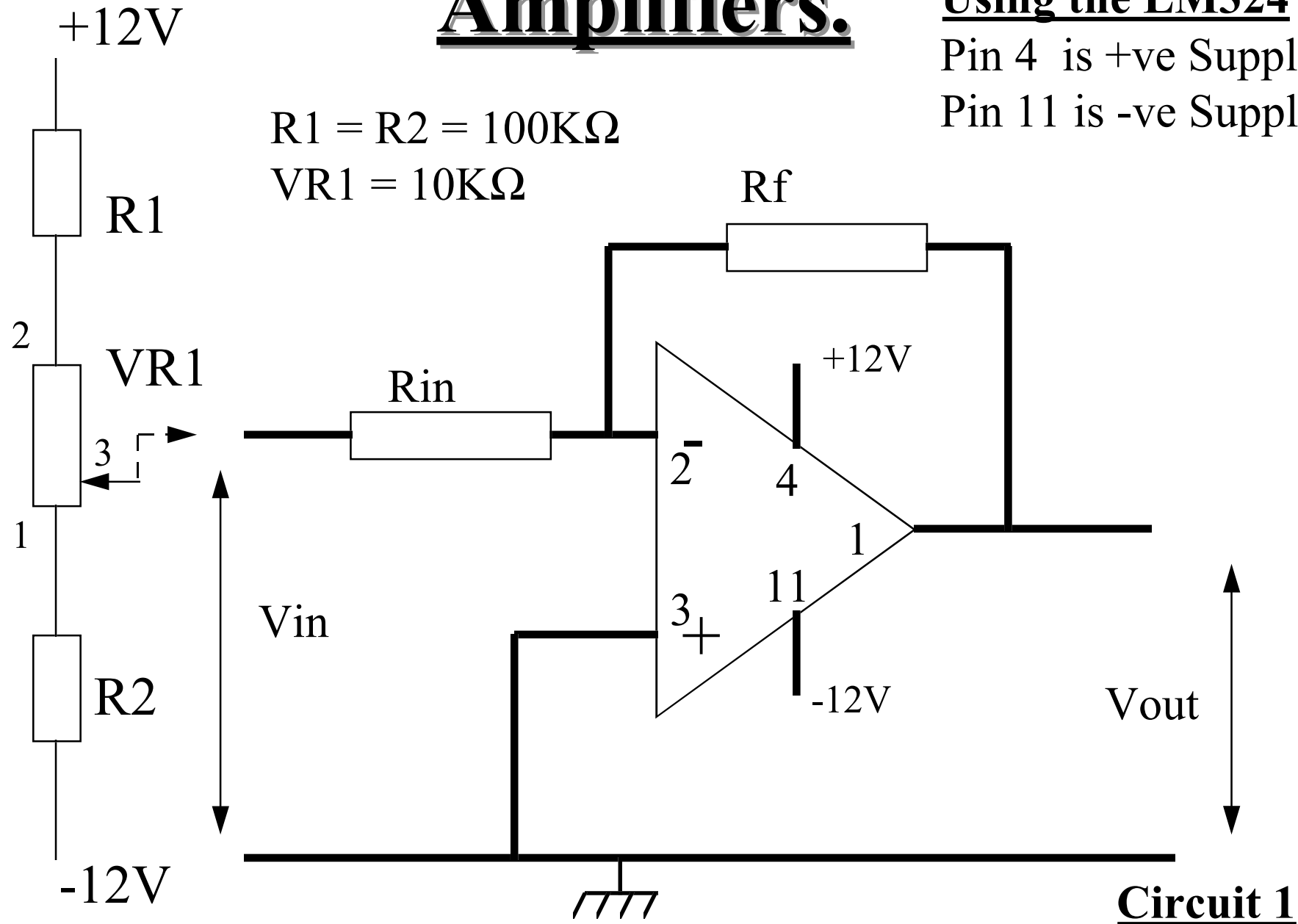


# Amplifiers.

- DC **Test 1**      Build “Circuit 1”.
- Set  $R_{in} = 1\text{K}\Omega$  and  $R_f = 10\text{K}\Omega$
- Adjust  $V_{in}$  from  $+10\text{mV}$  to  $-10\text{mV}$  in  $1\text{mV}$  steps. (or as near as possible, record actual values)
- Monitor and record  $V_{out}$ .
- Set to  $R_f = 100\text{K}\Omega$ , Repeat  $V_{in}$  changes.
- Monitor and record  $V_{out}$ .
- Set to  $R_f = 1\text{M}\Omega$ , Repeat  $V_{in}$  changes.
- Monitor and record  $V_{out}$ .


# Amplifiers.

## LM358

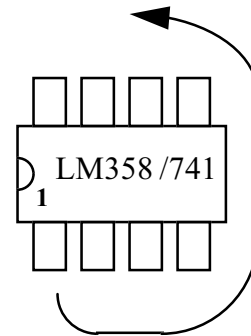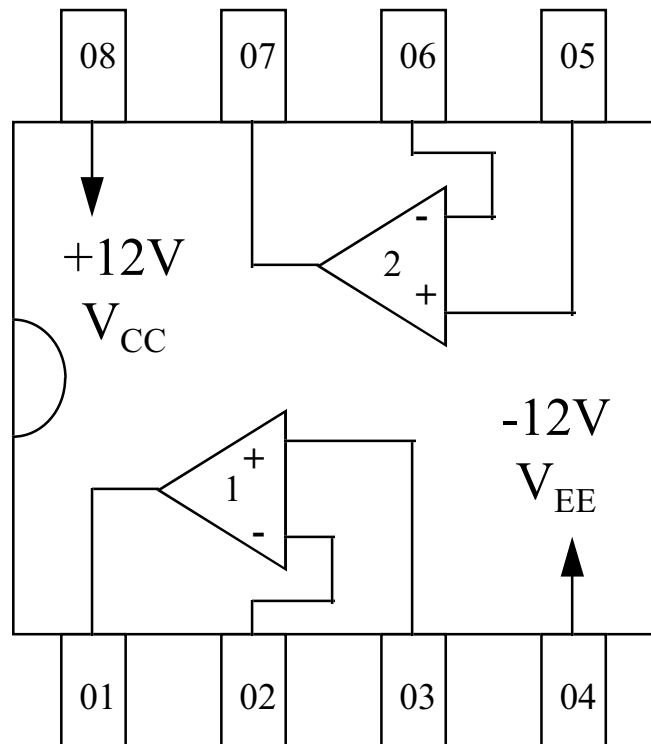



Count Pins in  
this direction

## LM741

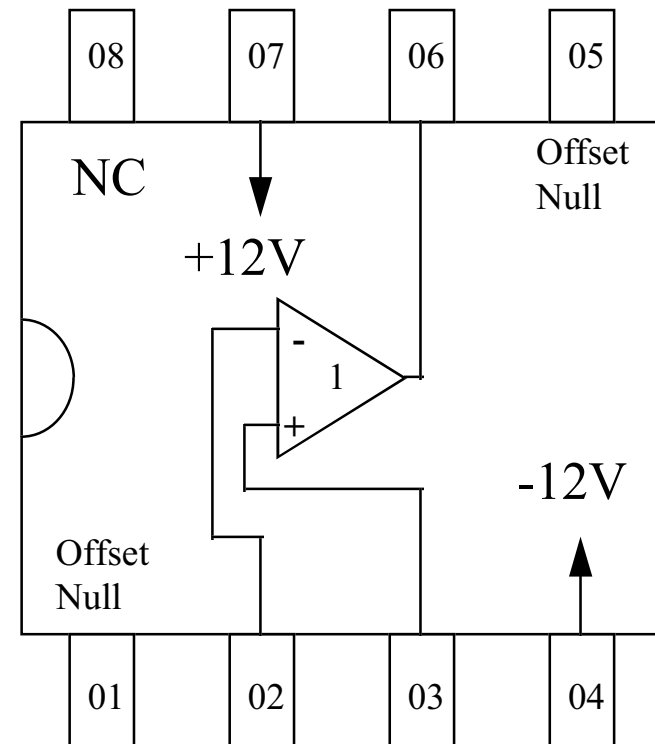

## Physical Layout Diagrams for LM358 and LM741

# Amplifiers.

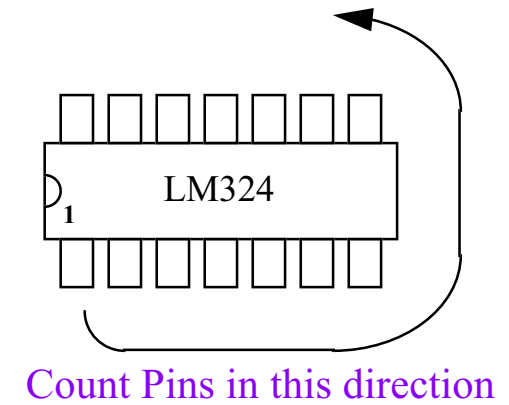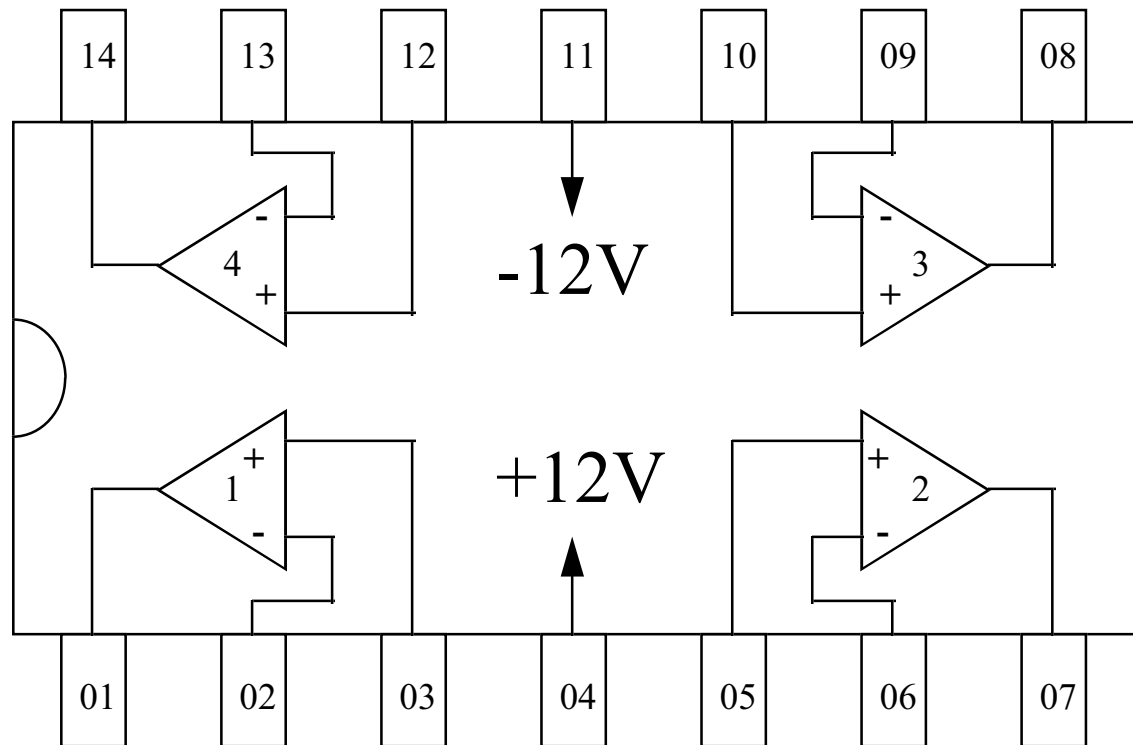


Physical Layout Diagram for LM324



# Amplifiers.

Set both PSU voltages to 12V

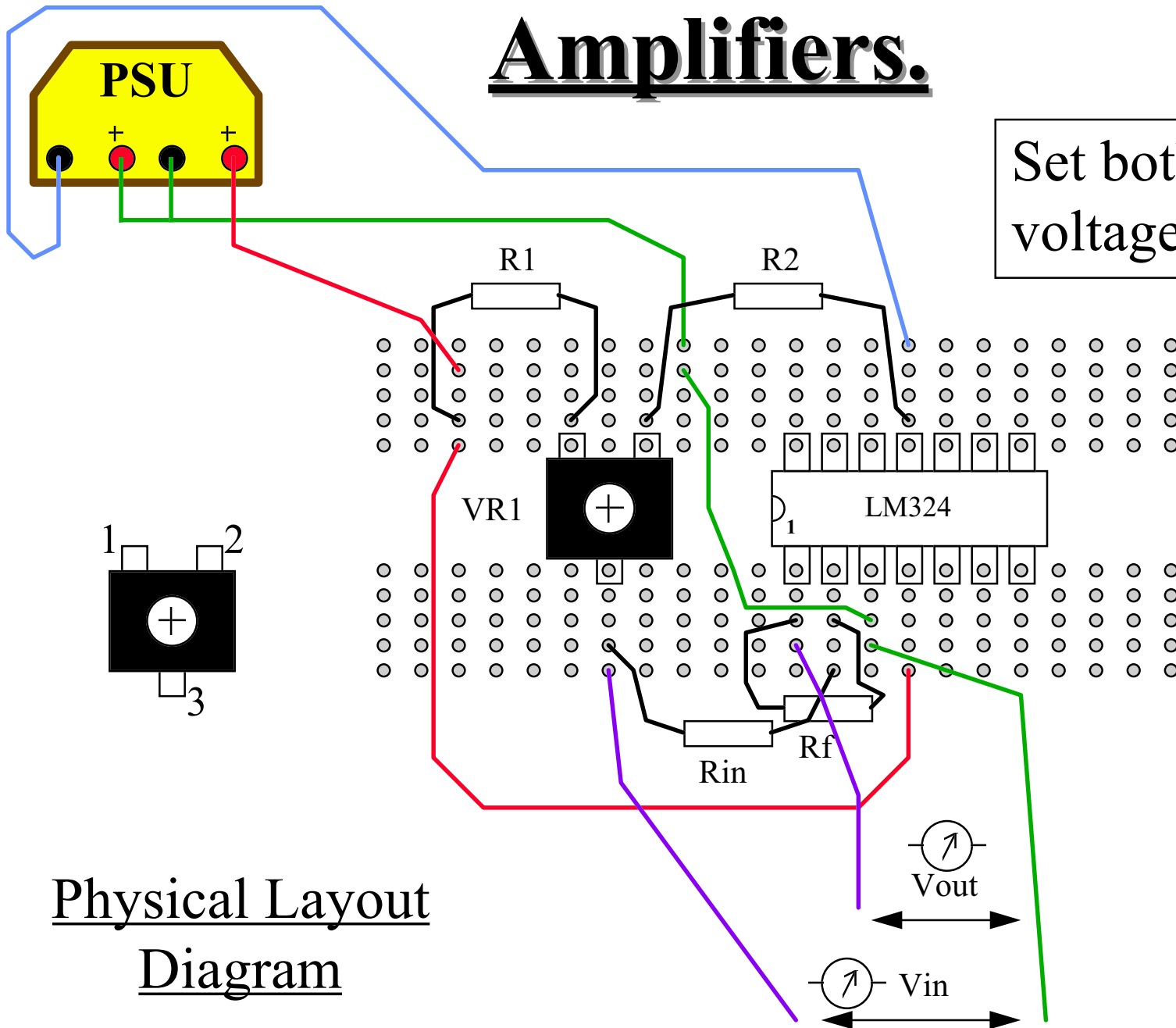

Physical Layout  
Diagram

Circuit 1

# Amplifiers.

## Recording Results Example


Vin (mV) Target	Vin (mV) Actual	Vout(mV) Actual
+10	+10.3	nnn
+9	+8.74	nnn
..	..	nnn
0	Not Possible to Adjust VR1 to get an exact reading.	
...	...	nnn
-5	-4.63	nnn
-10	-9.82	nnn

# Amplifiers.

Using the LM324

Pin 4 is +ve Supply

Pin 11 is -ve Supply

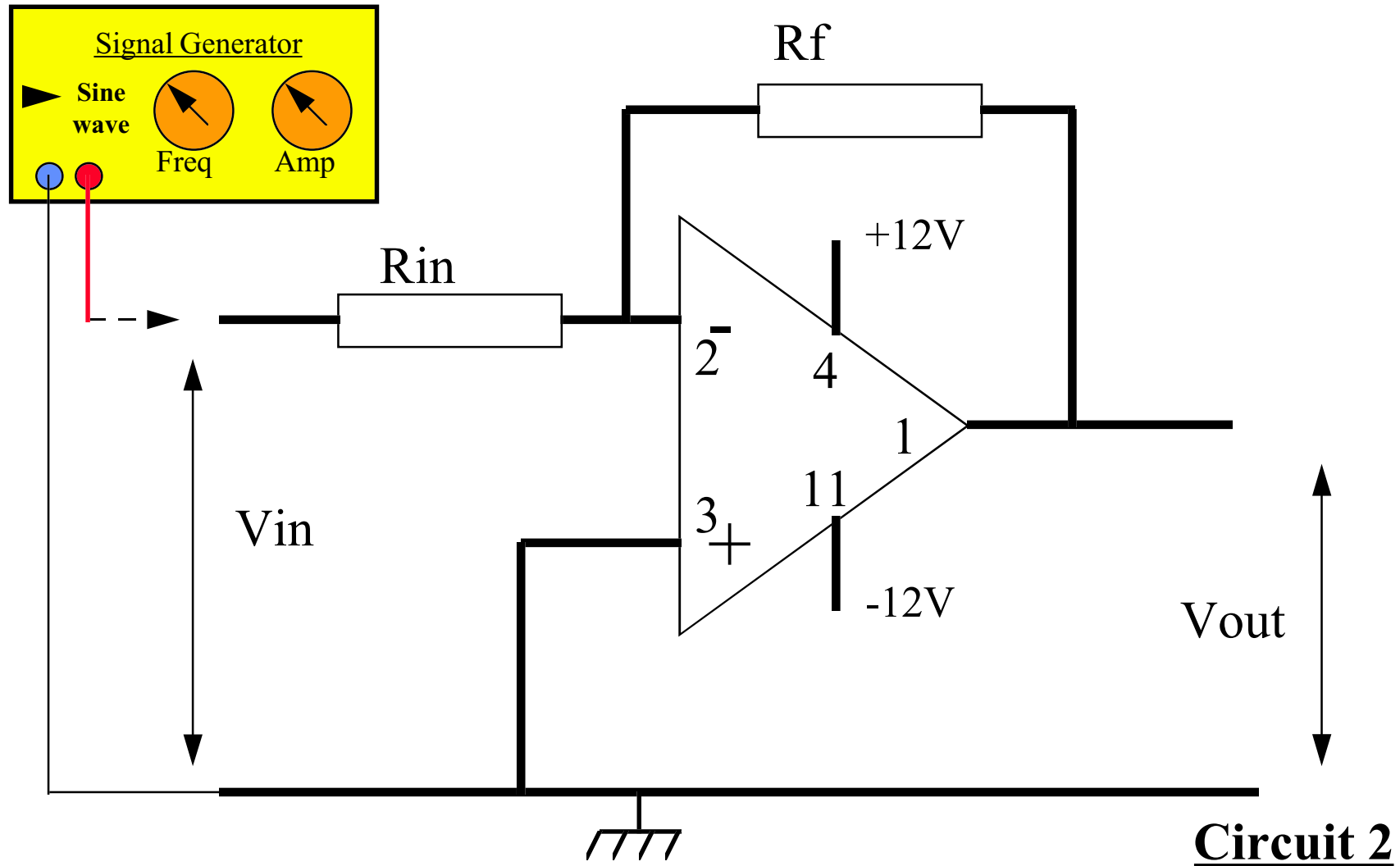

# Amplifiers.

- AC Test 1            Build “Circuit 2”.
- Set  $R_{in} = 1K\Omega$  and  $R_f = 1K\Omega$
- Set  $V_{in}$  to Sine wave with a frequency to 100Hz and amplitude to 100mV
- Monitor  $V_{out}$  and sketch CRO display.
- Change Frequency to 1000Hz
- Monitor  $V_{out}$  and sketch CRO display.
- Change Frequency to 10KHz
- Monitor  $V_{out}$  and sketch CRO display.

# Amplifiers.

- AC Test 2 Using “Circuit 2”.
- Set  $R_{in} = 1K\Omega$  and  $R_f = 10K\Omega$
- Set  $V_{in}$  to Sine wave with a frequency to 100Hz and amplitude to 100mV
- Monitor  $V_{out}$  and sketch CRO display.
- Change Frequency to 1000Hz
- Monitor  $V_{out}$  and sketch CRO display.
- Change Frequency to 10KHz
- Monitor  $V_{out}$  and sketch CRO display.

# Amplifiers.

- AC Test 3 Using “Circuit 2”.
- Set  $R_{in} = 1K\Omega$  and  $R_f = 100K\Omega$
- Set  $V_{in}$  to Sine wave with a frequency to 100Hz and amplitude to 100mV
- Monitor  $V_{out}$  and sketch CRO display.
- Change Frequency to 1000Hz
- Monitor  $V_{out}$  and sketch CRO display.
- Change Frequency to 10KHz
- Monitor  $V_{out}$  and sketch CRO display.

# Amplifiers.


Using the LM324

Pin 4 is +ve Supply

Pin 11 is -ve Supply

$R1, R2, R3, R4 = 100K\Omega$

$VR1, VR2 = 10K\Omega$

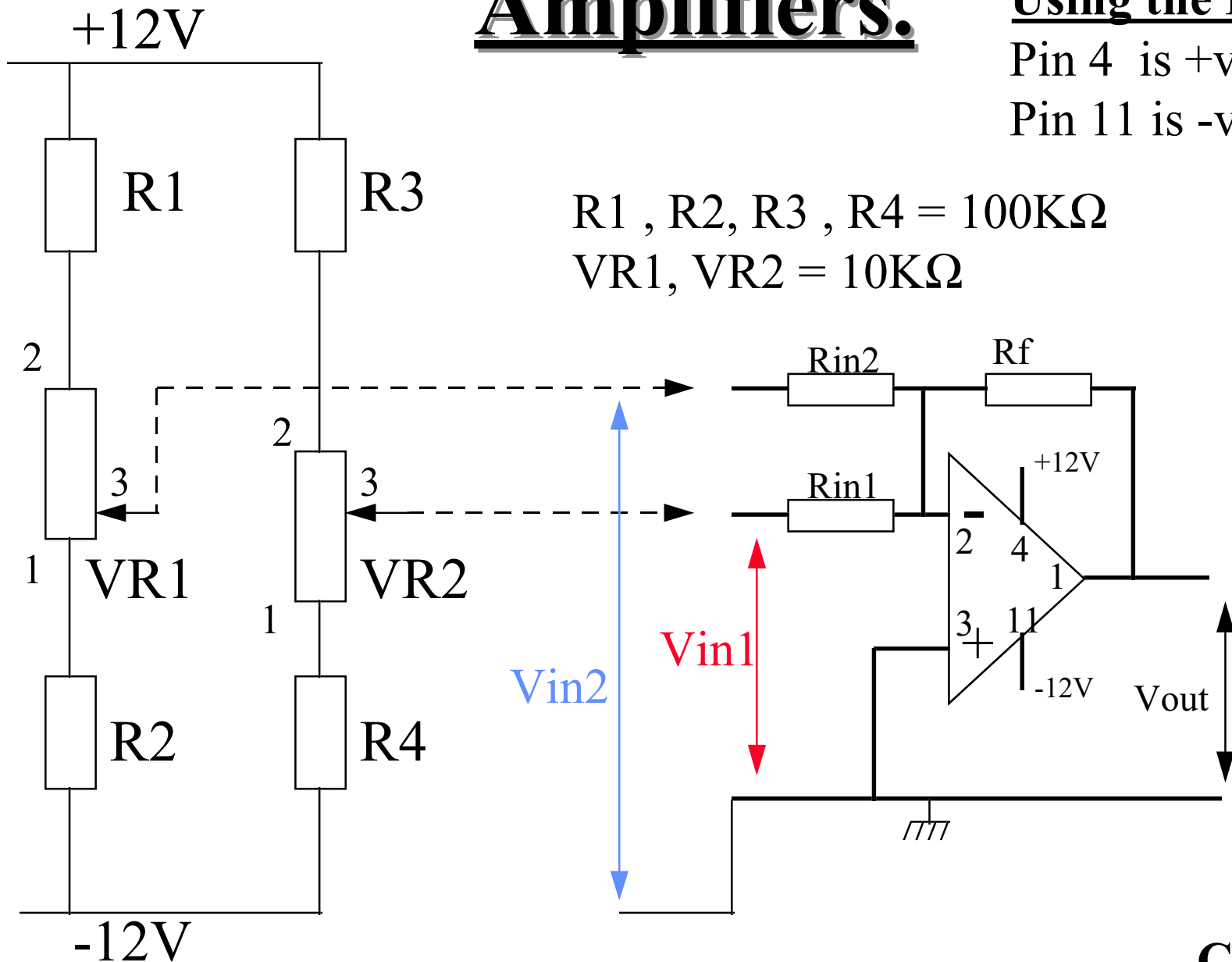

Circuit 4

# Amplifiers.

- DC **Test 2**      Build Circuit 4.
- Set  $R_{in1}$  &  $R_{in2} = 10K\Omega$  and  $R_f = 100K\Omega$
- Adjust  $V_{in1}$  from  $+10mV$  to  $-10mV$  in  $2mV$  steps. (or as near as possible, record actual values)
- Adjust  $V_{in2}$  from  $+10mV$  to  $-10mV$  in  $5mV$  steps. (or as near as possible, record actual values) for each setting of  $V_{in1}$ .
- Monitor and record  $V_{out}$ .
- Note This will result in you taking about 55 readings.



# Amplifiers.

Using the LM324


Pin 4 is +ve Supply

Pin 11 is -ve Supply

$R1, R2 = 100K\Omega$

$VR2 = 10K\Omega$

$R_{in} = 10K\Omega$

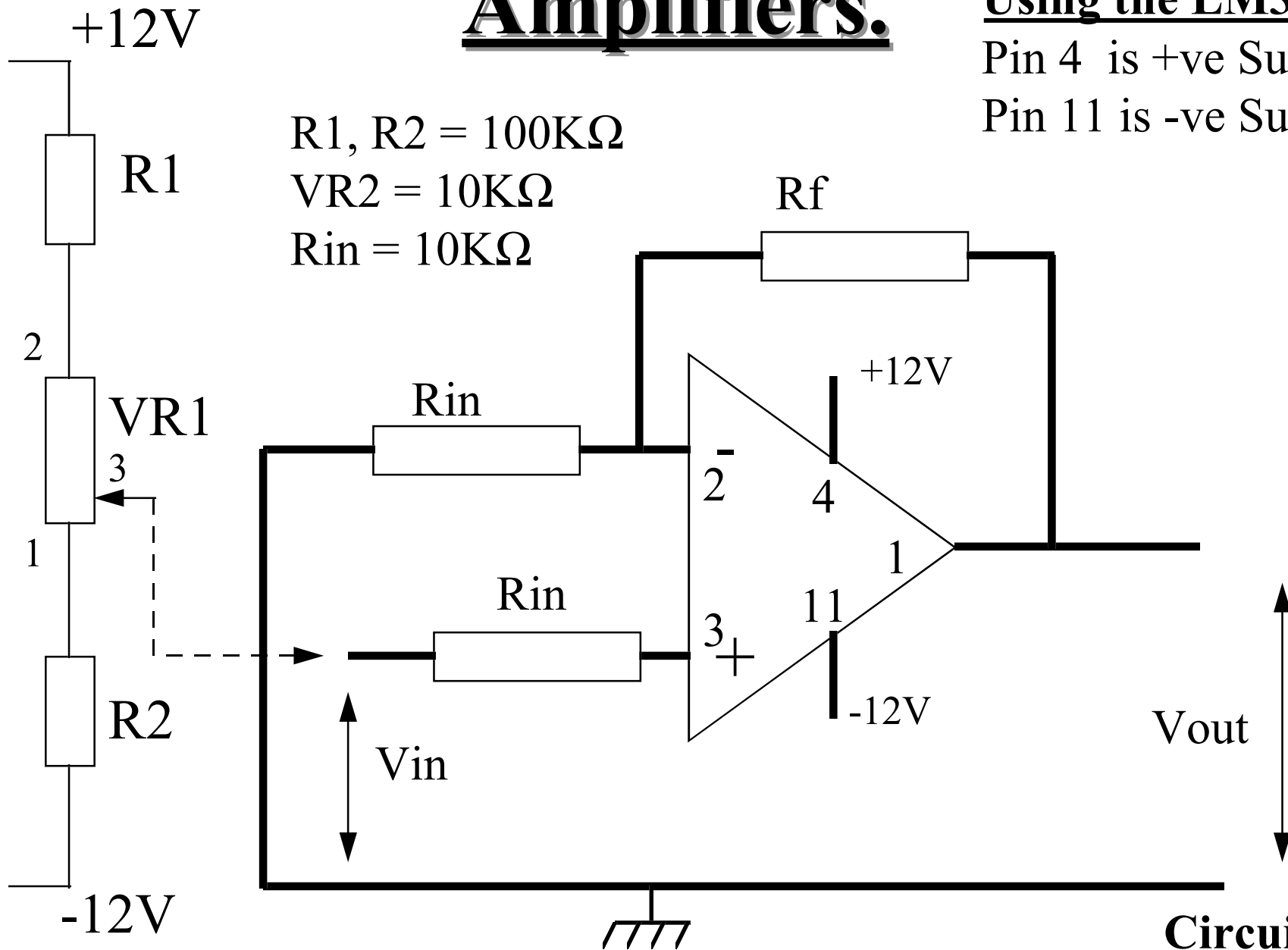

Circuit 5

# Amplifiers.

- DC Test 3            Build “Circuit 5”.
- **Warning** Check the Pin numbers. . .
- Set  $R_{in} = 1K\Omega$  and  $R_f = 10K\Omega$
- Adjust  $V_{in}$  from +10mV to -10mV in 1mV steps. (or as near as possible, record actual values)
- Monitor and record  $V_{out}$ .
- Set to  $R_f = 100K\Omega$  , Repeat  $V_{in}$  changes.
- Monitor and record  $V_{out}$ .

# Amplifiers.

Using the LM324

Pin 4 is +ve Supply


Pin 11 is -ve Supply

$R1, R2 = 100K\Omega$

$VR2 = 10K\Omega$

$R3 = 10K\Omega$

$R_{in} = 1K\Omega$

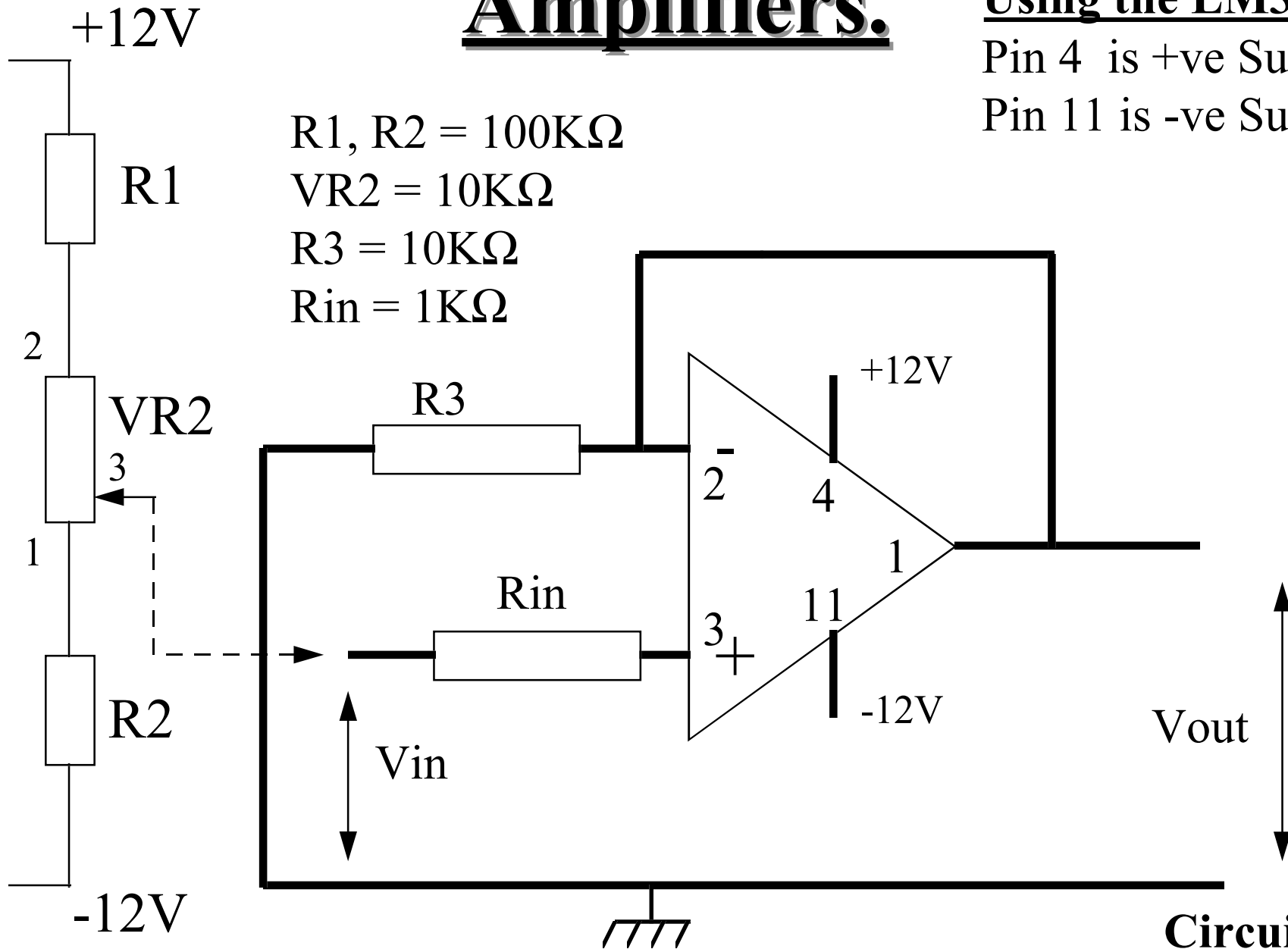

Circuit 6

# Amplifiers.

- DC **Test 4**      Build “Circuit 6”.
- Set  $R_{in} = 1\text{K}\Omega$
- Adjust  $V_{in}$  from  $+10\text{mV}$  to  $-10\text{mV}$  in  $1\text{mV}$  steps. (or as near as possible, record actual values)
- Monitor and record  $V_{out}$ .
- Set  $R_{in} = 10\text{K}\Omega$
- Adjust  $V_{in}$  from  $+10\text{mV}$  to  $-10\text{mV}$  in  $1\text{mV}$  steps. (or as near as possible, record actual values)
- Monitor and record  $V_{out}$ .

# Amplifiers.

Using the LM324

Pin 4 is +ve Supply


Pin 11 is -ve Supply

Amp 1    + = 2 , - = 3 , O/P = 1

Amp 2    + = 5 , - = 6 , O/P = 7

Amp 3    + = 10 , - = 9 , O/P = 8

Amp 4    + = 12 , - = 13 , O/P = 14

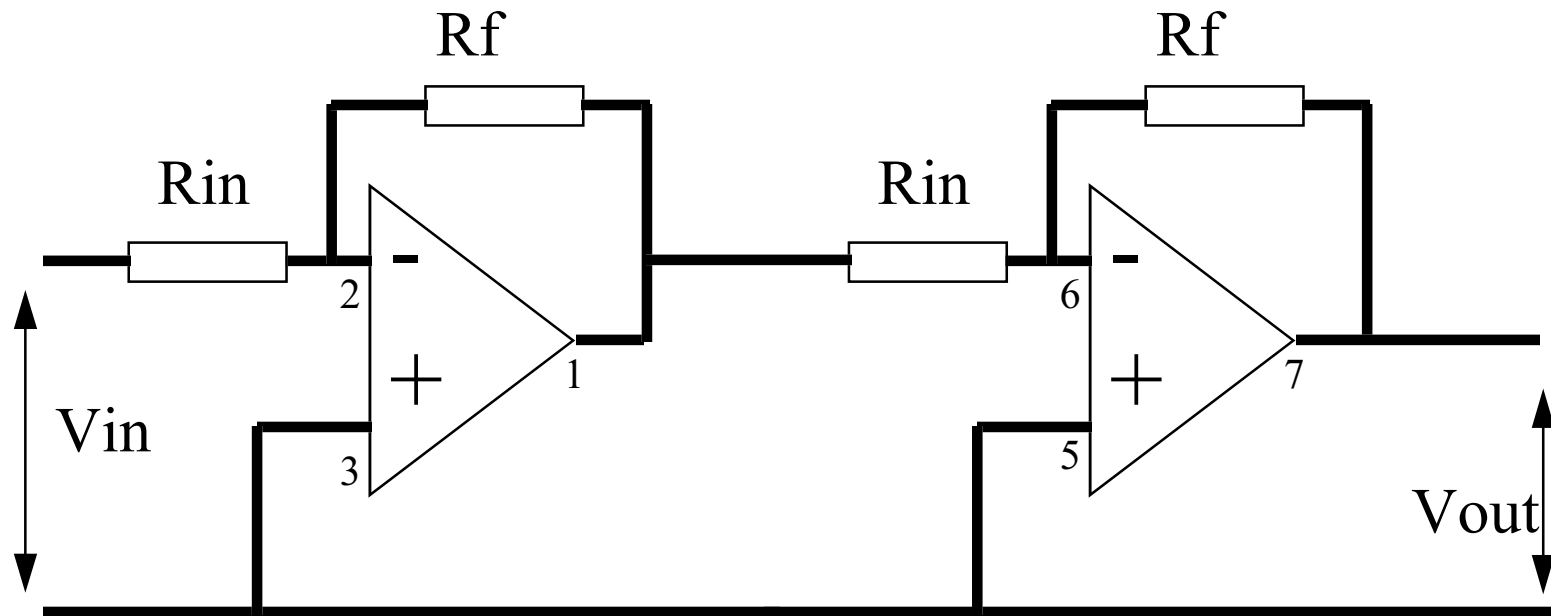

Circuit 3

# Amplifiers.

- AC Test 4            Build Circuit 3.
- Set  $R_{in} = 1K\Omega$  and  $R_f = 10K\Omega$
- Set  $V_{in}$  to Sine wave with a frequency to 100Hz and amplitude to 100mV
- Monitor  $V_{out}$  and sketch CRO display.
- Change Frequency to 1000Hz
- Monitor  $V_{out}$  and sketch CRO display.
- Change Frequency to 10KHz
- Monitor  $V_{out}$  and sketch CRO display.

# Amplifiers.

- Order to complete Activities :-
  - DC Test 1
  - AC Test 1
  - AC Test 2
  - AC Test 3
  - DC Test 2
  - DC Test 3
  - DC Test 4
  - AC Test 4 (Optional if time allows)

# Experiment 6.




# **Diode Circuits.**

- Build “Circuit 1”.
- With initial setting sketch CRO display.
- Reverse Diode D1
- Sketch CRO display.

# Diode Circuits.

Set Signal generator to Sine wave with a frequency to 1000Hz and amplitude to 2 Volts

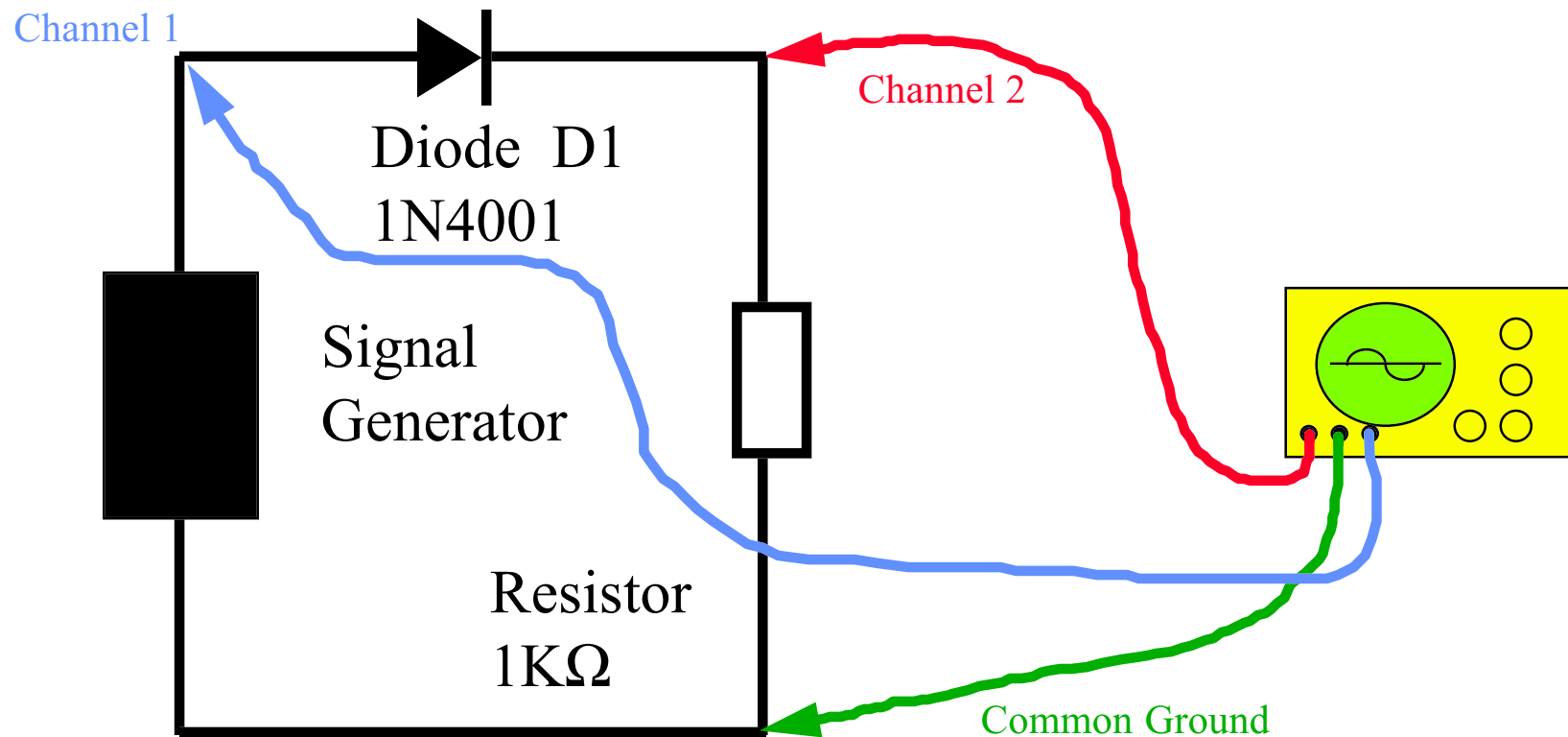


**Circuit 1**

# Experiment 7.

# Capacitors and Resistors.

Initially discharge the capacitor (SwC Open and SwD Closed)

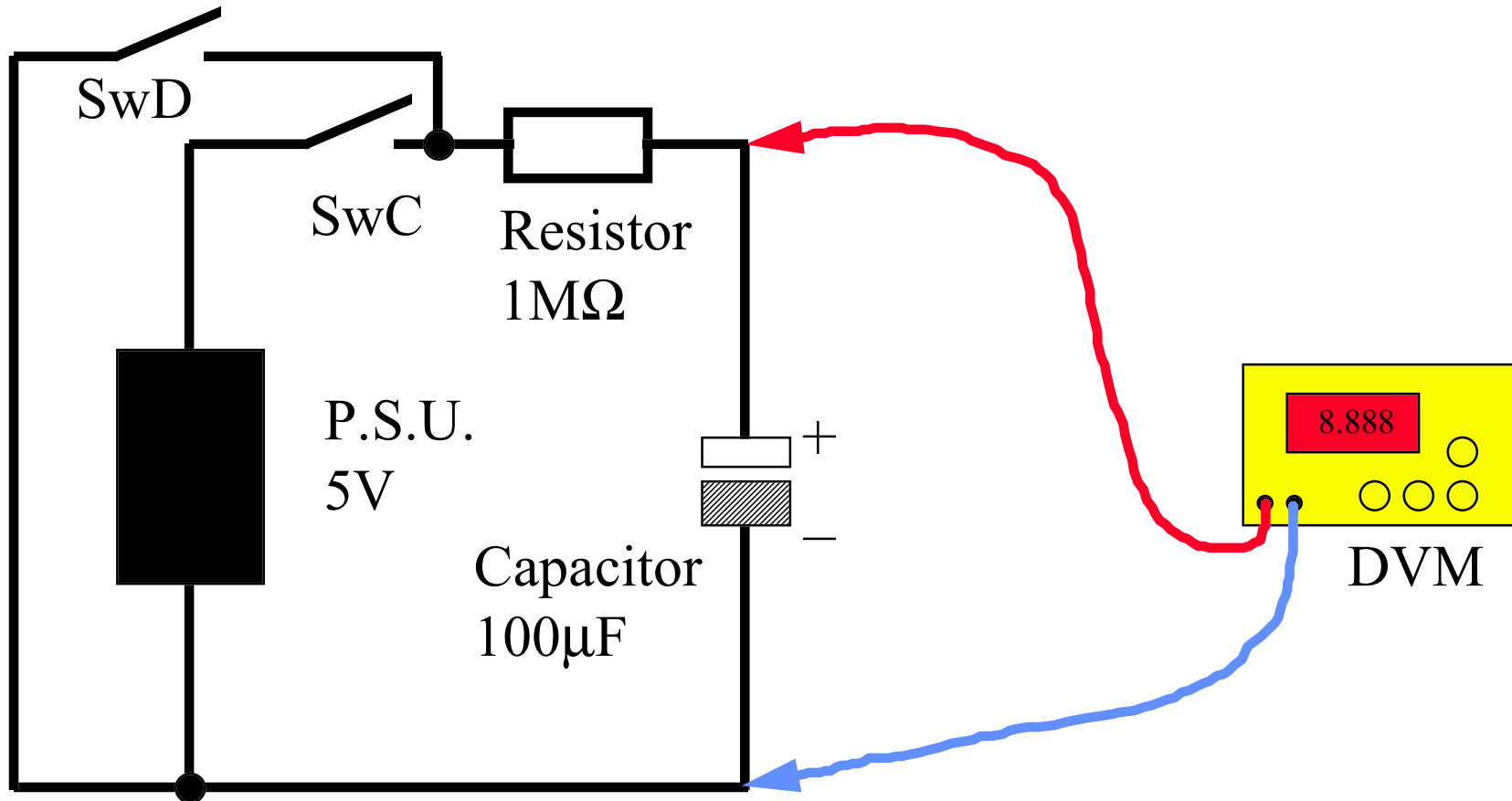

**Circuit 1**

# Capacitors and Resistors.

- Build “Circuit 1” and Discharge Capacitor.
- Open SwD when capacitor fully discharged.
- Close SwC and record voltage across the capacitor at the following time intervals.
- 0, 10, 20, 30, 40, 50, 60, 80, 100, 120, 140, 160 seconds , 3, 3.5, 4, 5, 6, 7 minutes.
- Open SwC , Close SwD and record voltage across the capacitor at the following time intervals.
- 0, 10, 20, 30, 40, 50, 60, 80, 100, 120, 140, 160 seconds , 3, 3.5, 4, 5, 6, 7 minutes.

# Capacitors and Resistors.

- Change capacitor to  $22\mu\text{F}$  and discharge it.
- Open SwD when capacitor fully discharged.
- Close SwC and record voltage across the capacitor at the following time intervals.
- 0, 5, 10, 15, 20, 25, 30, 35, 40, 45, 50, 55, 60, 80, 100 seconds, 2, 3, 5 minutes.
- Open SwC , Close SwD and record voltage across the capacitor at the following time intervals.
- 0, 5, 10, 15, 20, 25, 30, 35, 40, 45, 50, 55, 60, 80, 100 seconds, 2, 3, 5 minutes.

# Capacitors and Resistors.

- Change capacitor to  $10\mu\text{F}$  and discharge it.
- Open SwD when capacitor fully discharged.
- Close SwC and record voltage across the capacitor at the following time intervals.
- 0, 5, 10, 15, 20, 25, 30, 35, 40, 45, 50, 55, 60, 80, 100 seconds, 2, 3, 5 minutes.
- Open SwC , Close SwD and record voltage across the capacitor at the following time intervals.
- 0, 5, 10, 15, 20, 25, 30, 35, 40, 45, 50, 55, 60, 80, 100 seconds, 2, 3, 5 minutes.


# Capacitors and Resistors.

- Plot the family of curves of the reading.
- Calculate then mark on each curve the 63% point of the final steady state voltage.
- Calculate the time constant (  $\tau$  {tor} )
- $\tau = R * C$  seconds where  $R=1M$  &  $C=100\mu F$
- Therefore  $\tau = 1 * 10^6 * 100 * 10^{-6} = 100\text{secs}$
- Repeat for the  $10\mu F$  and  $22\mu F$  capacitors.
- How do the theory and practical values match?



# Experiment 8.

# Amplifier AC and DC Tests.

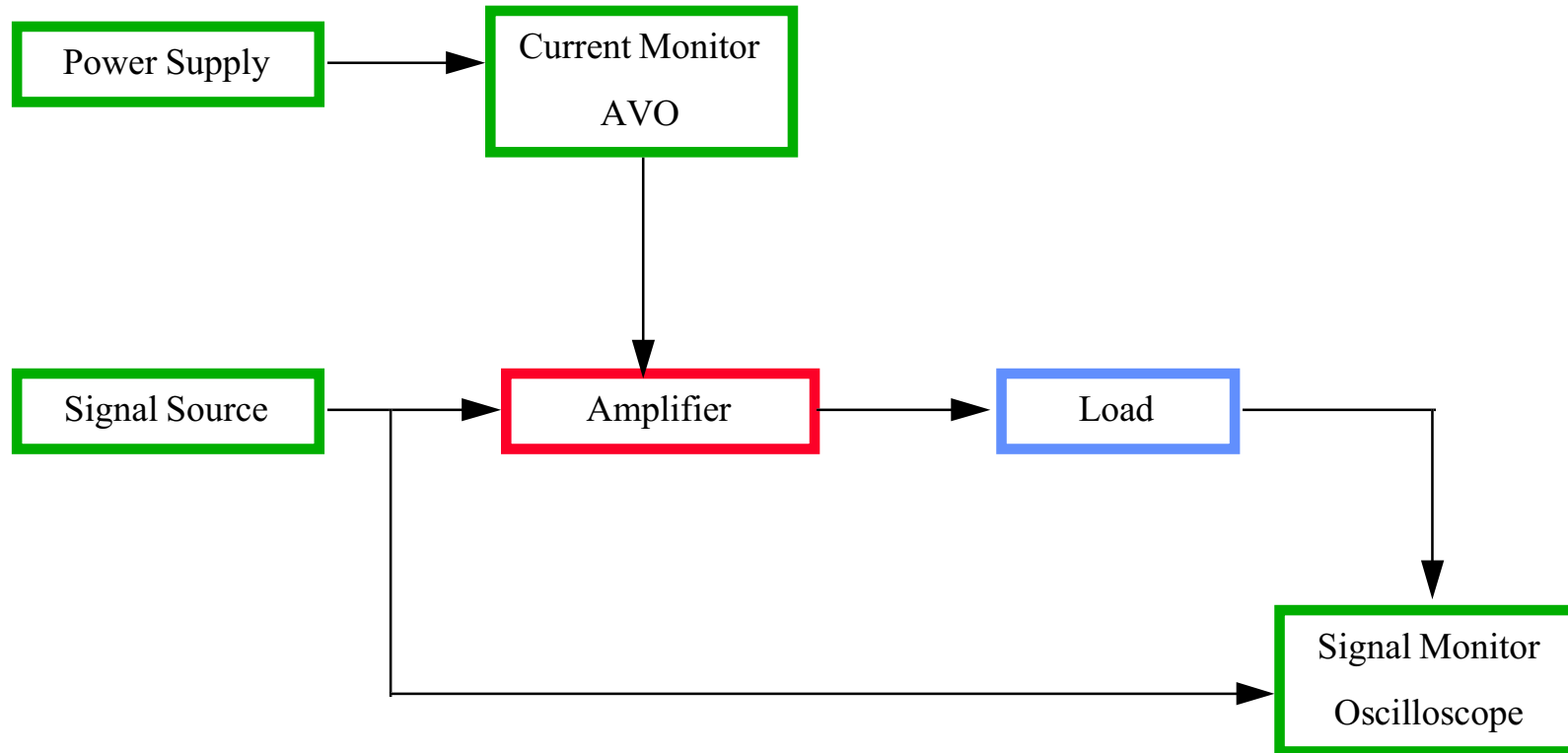

Block Diagram.

# Amplifier Input Power Test.

## Control Conditions

Load  $50\Omega$

Input Signal 1KHz

Supply +/-9V

Volume control set to minimum attenuation.

Input current in mA	Input Signal in mV P/P	Output Signal % Undistorted	Output Voltage in Volts P/P
40 mA	520 mV P/P	Max or 100%	13 Volts P/P
29mA	400 mV P/P	75% Undistorted	10 Volts P/P
22mA	300 mV P/P	50% Undistorted	6.5 Volts P/P
12.5mA	250 mV P/P	25% Undistorted	3.25 Volts P/P
6 mA	0 mV P/P	0 % Undistorted	0 Volts P/P


Quiescent , Standing or Bias Current

# Amplifier AC Frequency Test.

## Control Conditions

AC Input Signal Amplitude 200mV P/P per channel.


Input Frequency in Hz	Output Voltage Volts P/P
100 Hz	10V P/P
500 Hz	10V P/P
1000 Hz	10V P/P
2000 Hz	10V P/P
10000 Hz	10V P/P
20000 Hz	9V P/P
30000 Hz	6V P/P

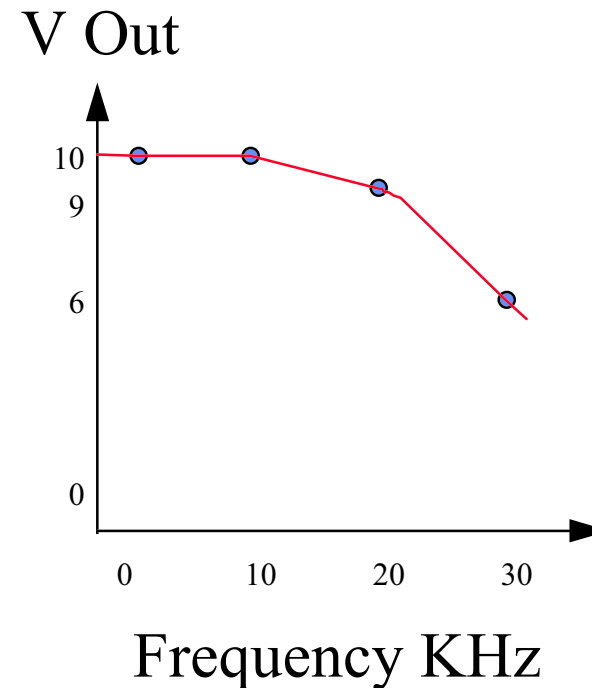
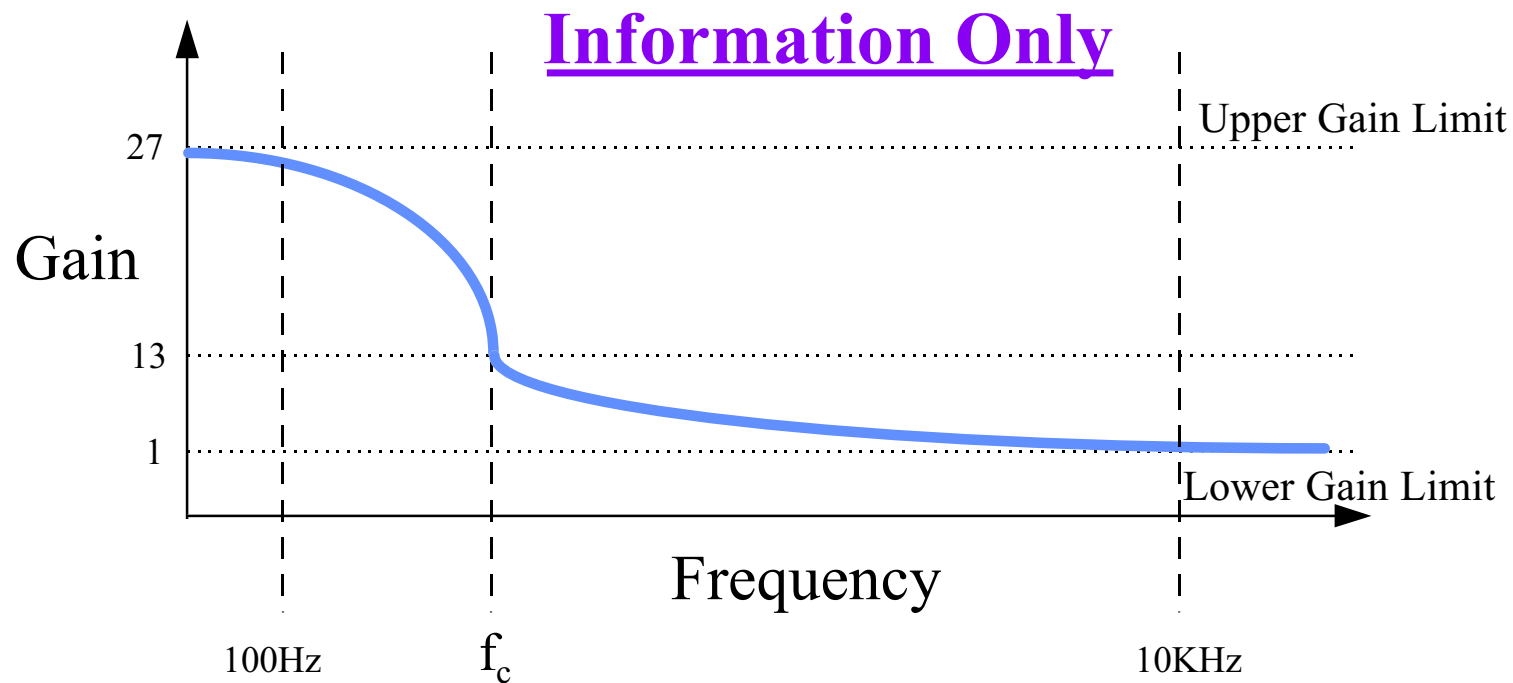
# Amplifier Theory.


The Gain / frequency relationship graph of the Base Boost Circuit.

**Note** That the cutoff frequency of a simple filter is the point where Impedance and resistance are the same.




**Base Boost (Gain Modifier) Calculations.**

# Amplifier Theory.

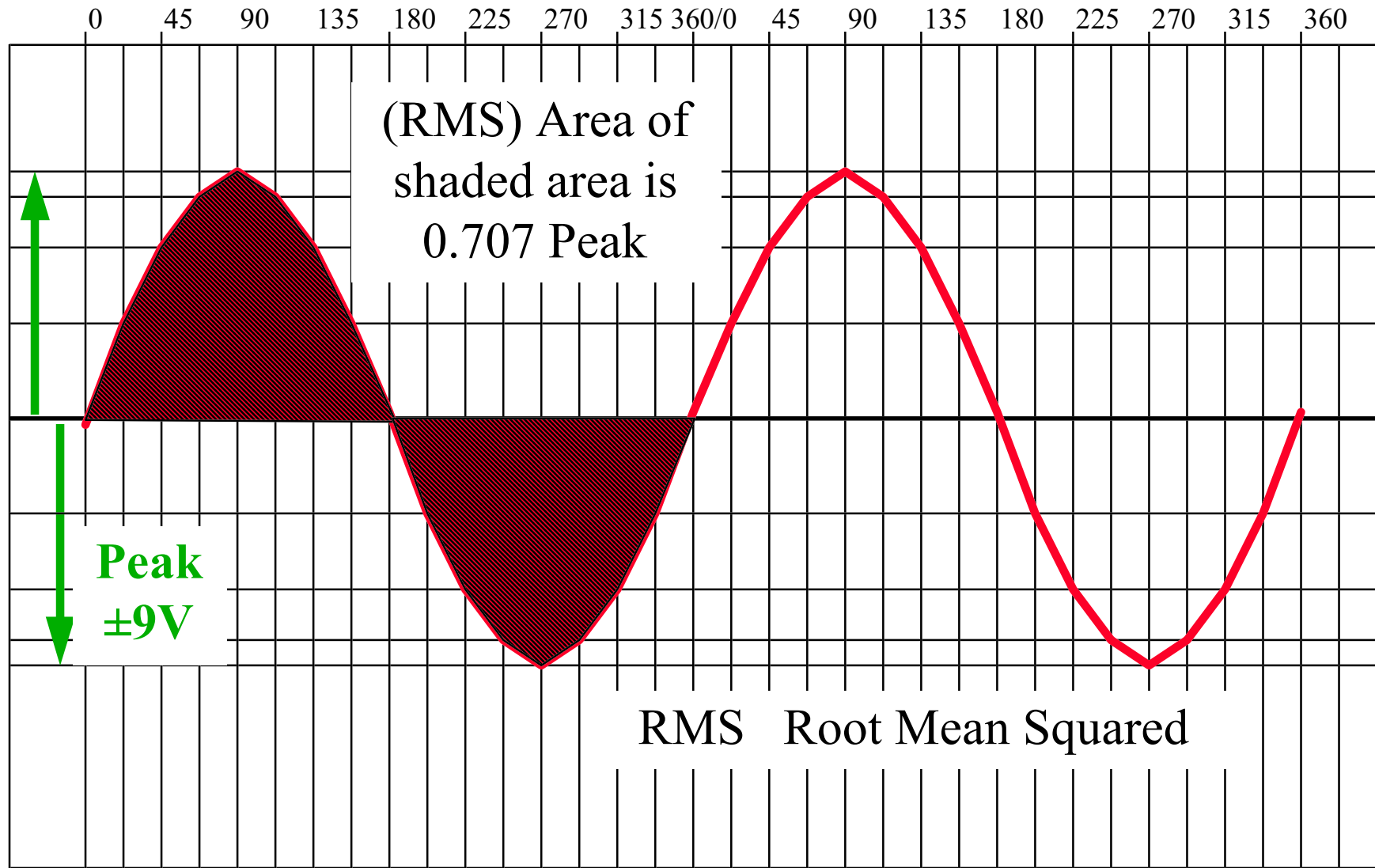
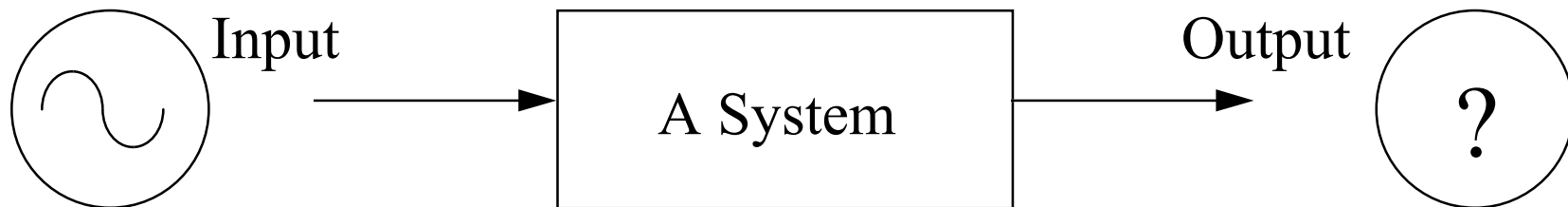
# Amplifier Theory.

- When we analyze a System we often look at it as a block or series of independent blocks
- We are often quite interested what would happen to the system :-
  - If we applied a particular control to the Input ?
  - What Output would result if that control was applied ?
- The “Transfer characteristic” is a graphical representation of a system showing the relationship between Input and Output




# Amplifier Theory.

Graph of Transfer Equation.

Produced from the values in results table.

Results	
Input	Output
0.5V	-5V
0.4V	-4V
0V	0V
-0.3V	+3V
-0.5V	+5V

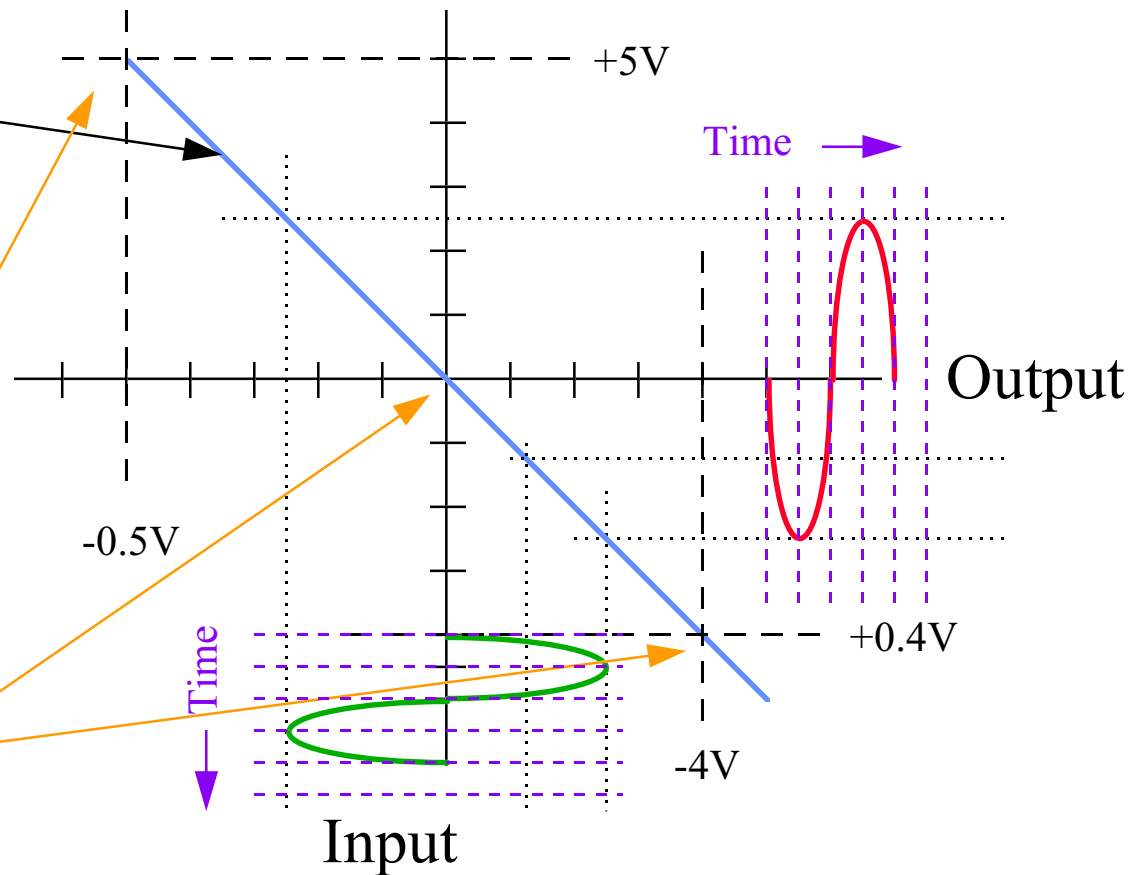

A times ten gain Inverter Amplifier  
“Transfer Characteristic”.


**The Transfer Characteristic.**



# Amplifier Theory.

Graph of Transfer Equation

Results	
Input	Output
0.5V	+5V
0.3V	+3V
0V	0V
-0.3V	-0.3V
-0.5V	-0.5V

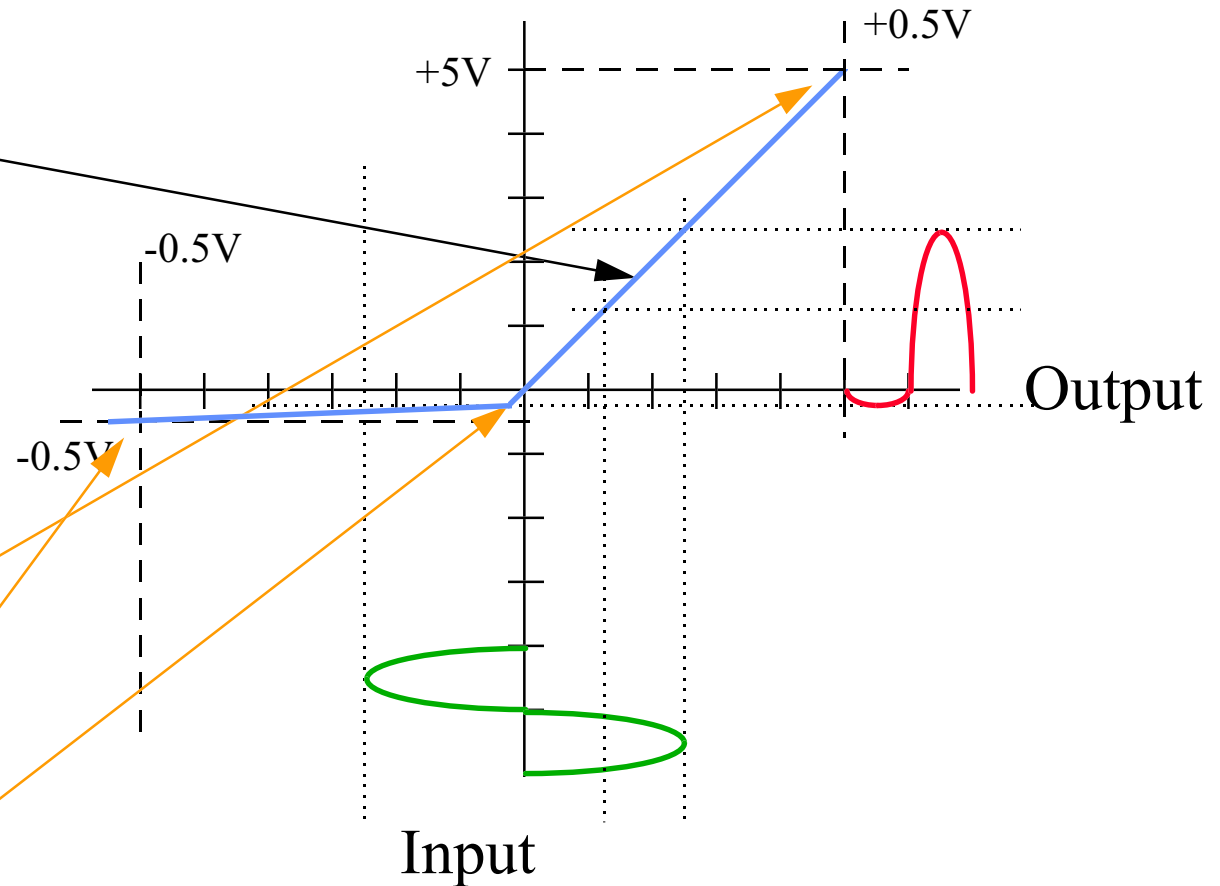


An example of an asymmetrical  
“Transfer Characteristic”.

**The Transfer Characteristic.**

# Experiment 9.

# Inductors and Resistors.

Set Signal generator to a Sine wave with a frequency of 600KHz and an amplitude of 2 Volts peak to peak.

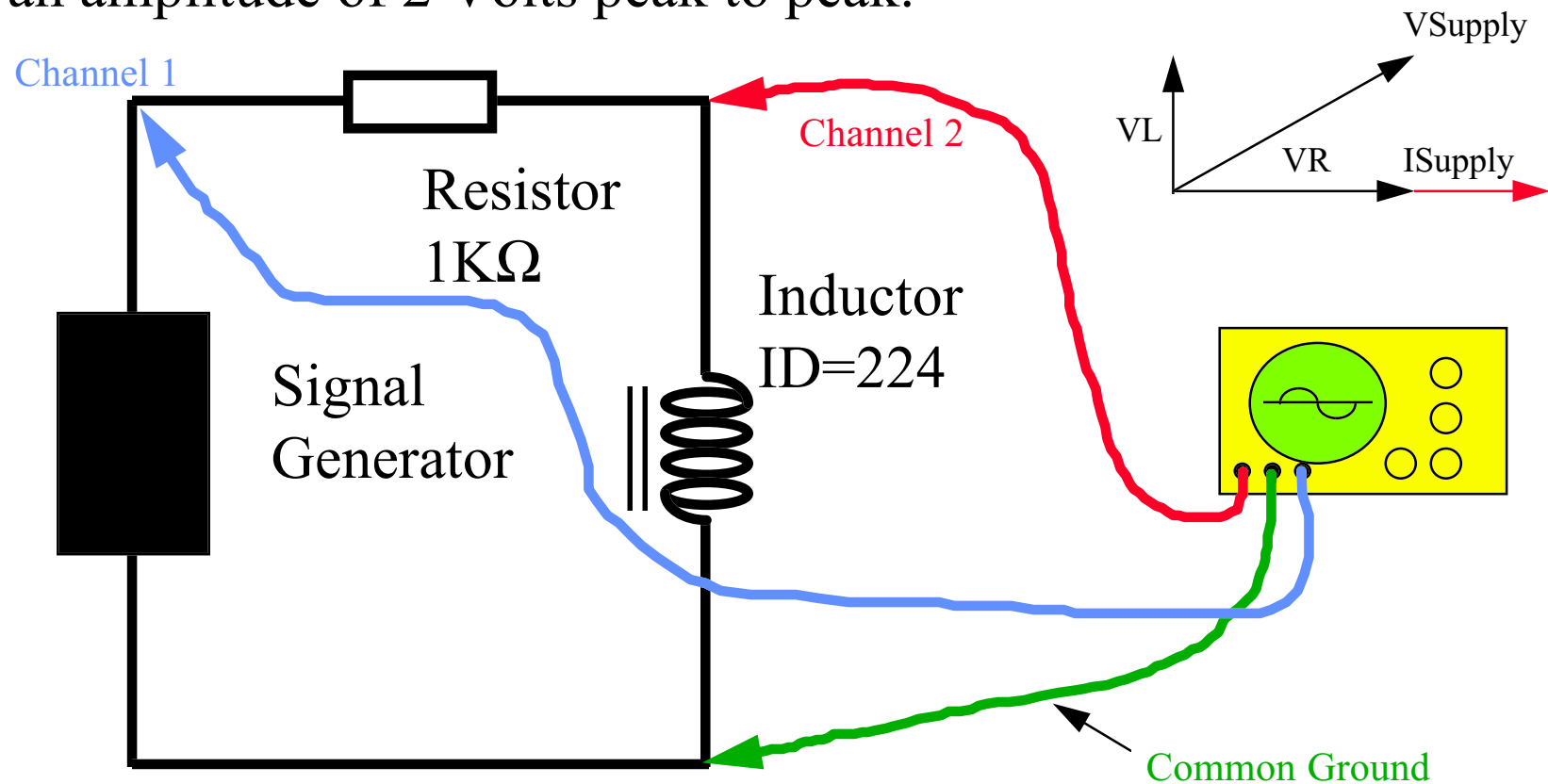

**Circuit 1**

# Inductors and Resistors.

- Build “Circuit 1”.
- With initial settings sketch the CRO display.
- Increase frequency to 900KHz what is the effect on the voltage across the Inductor ?
- Decrease frequency to 200KHz what is the effect on the voltage across the Inductor ?
- Sketch the changes for all settings.
- Create a table of your measurements.
- Add to the table the value of the Inductors reactance at the different frequencies.

# Inductors and Resistors.



- Calculate value of Inductance using the measurements taken with 200KHz Signal.
  - Calculate Voltage across resistor:-
    - $V_{\text{Resistor}} = \sqrt{V_{\text{source}}^2 - V_{\text{Inductor}}^2}$ .
  - Calculate Current through the Resistor and the Inductor (they are in series):-
    - $I_{\text{Resistor}} = I_{\text{Inductor}} = V_{\text{resistor}} / \text{Resistance}$ .
  - Calculate Reactance of the Inductor:-
    - Inductor Reactance  $X_l = V_{\text{Inductor}} / I_{\text{Inductance}}$ .
  - Calculate Inductance of the Inductor:-
    - Inductance  $l = X_l / (2 * \pi * f \text{ (frequency = 200KHz)})$ .

# Inductors and Resistors.

- Conclusion:-
- What did you notice about the position of the Source Voltage with respect to the Voltage across the Inductor?
  - Did frequency effect this position/phase and if so how did it effect it?
- In what way did the frequency have an effect on the reactance of the Inductor?
- What was the resistance rather than the reactance of the Inductor (Measure it)?

# Experiment 10.

# Digital Logic.

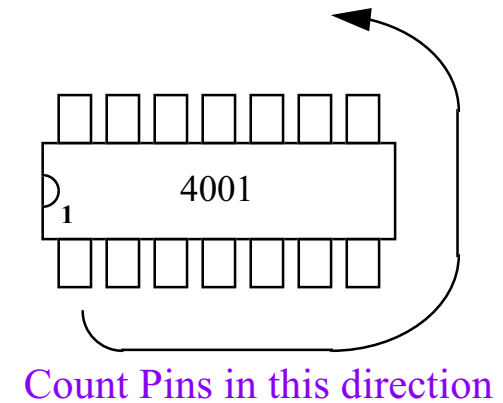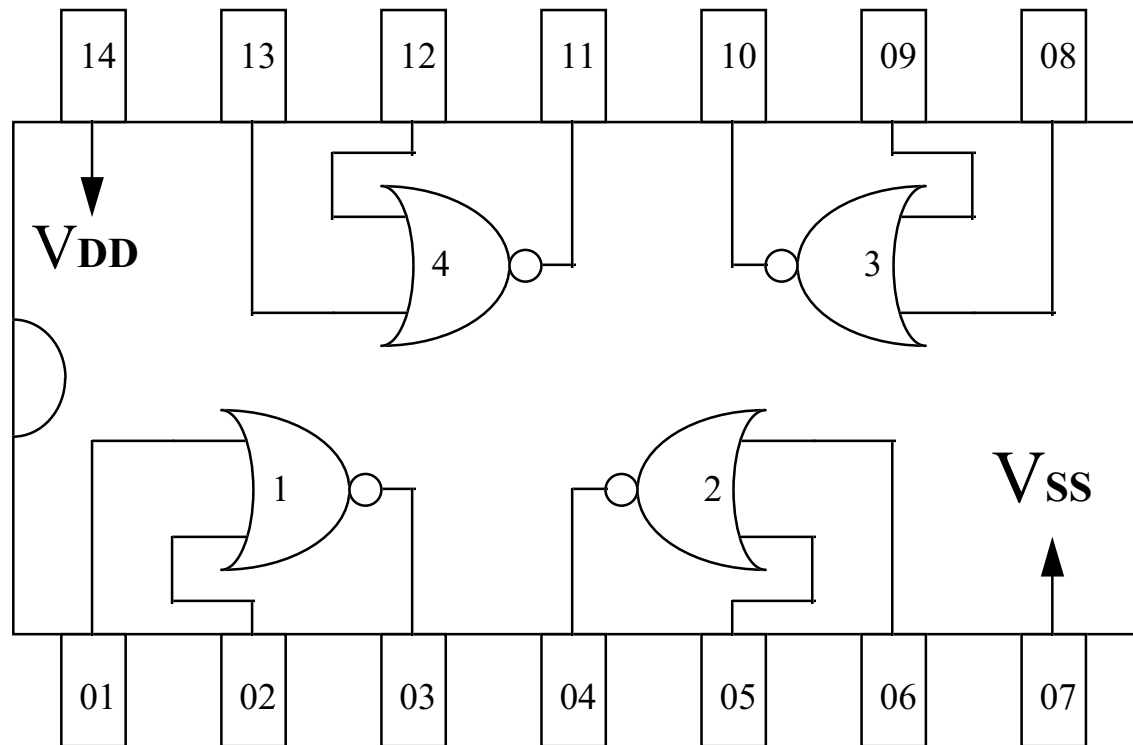



$V_{DD} = +5V$

$V_{SS} = \text{Ground} / 0V$

## Physical Layout Diagram for 4001



# Digital Logic.

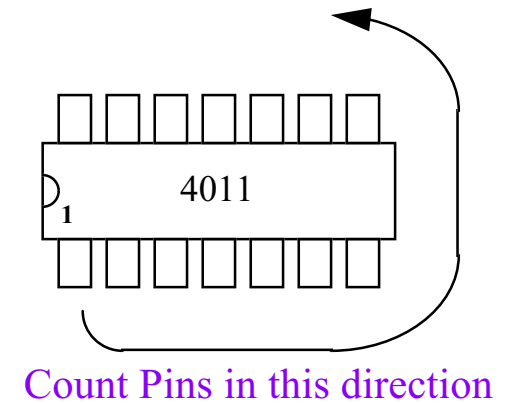
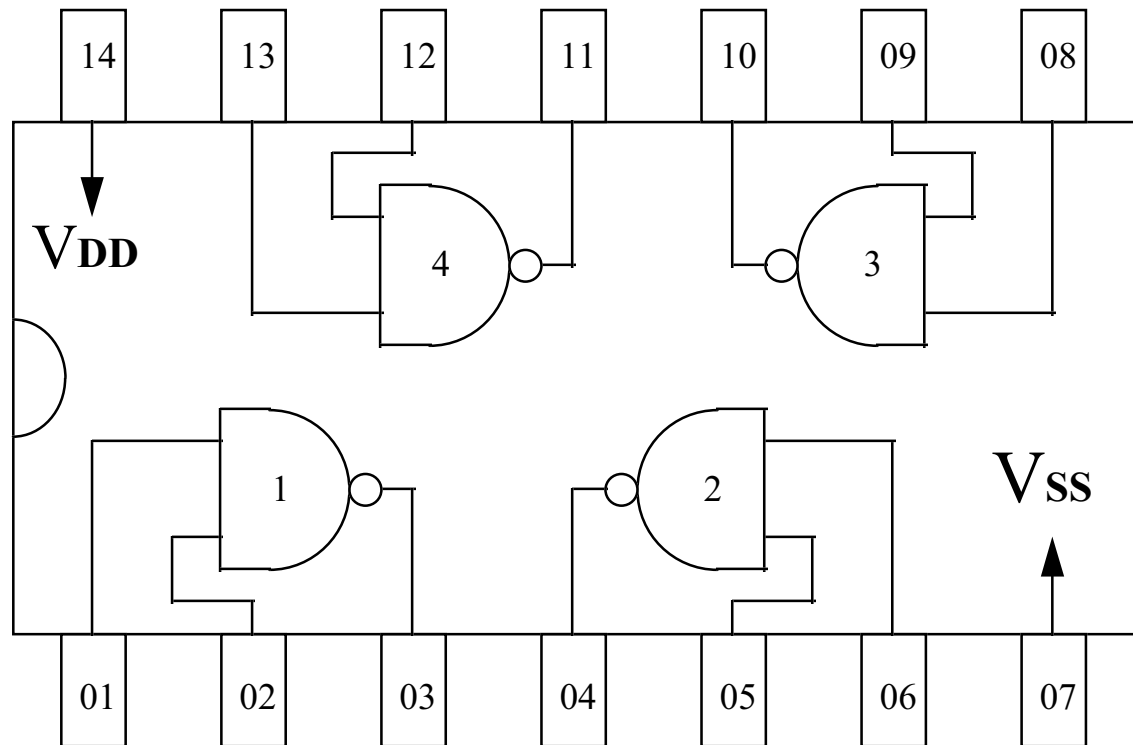


$V_{DD} = +5V$

$V_{SS} = \text{Ground} / 0V$

## Physical Layout Diagram for 4011

# Digital Logic.

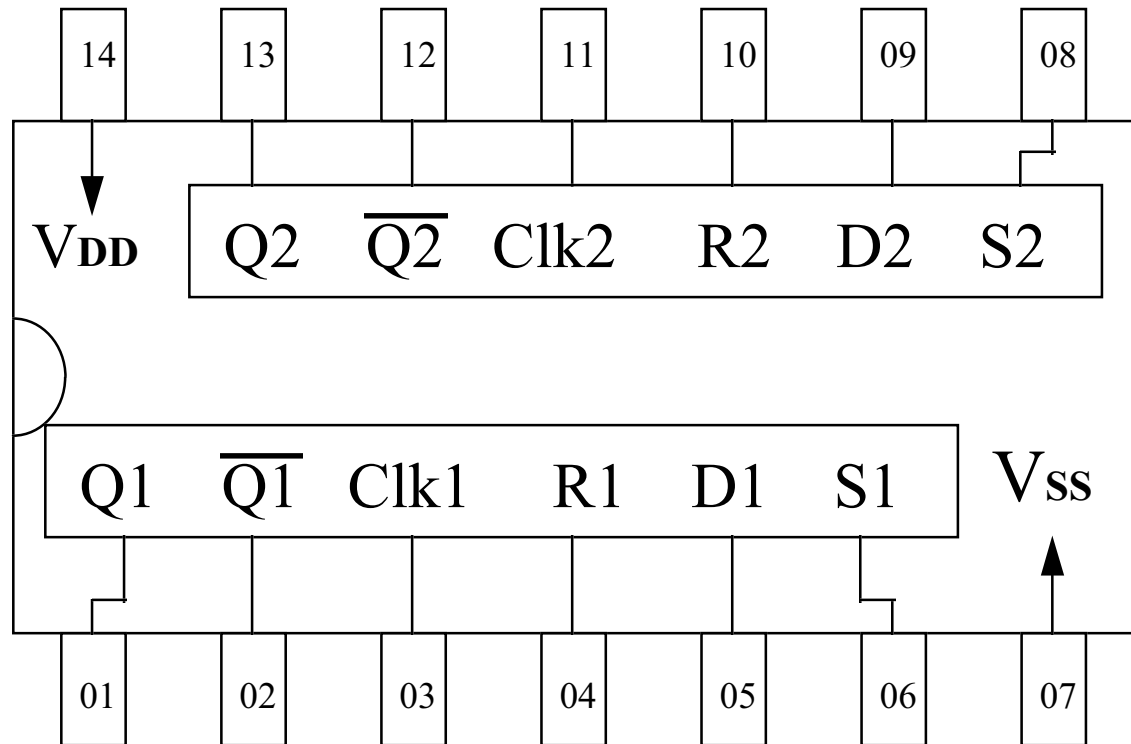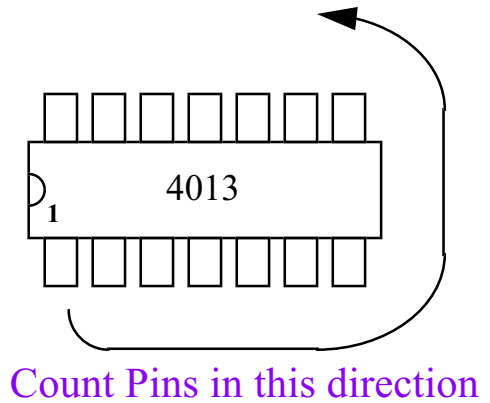

Q = Output

R = Reset

S = Set

D = Input



Clk = Clock

V<sub>DD</sub> = +5V

V<sub>ss</sub> = Ground / 0V

## Physical Layout Diagram for 4013

# Digital Logic.

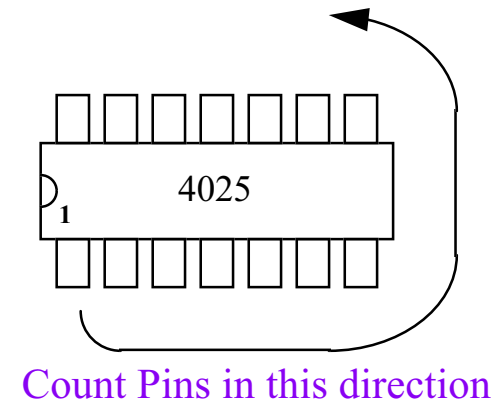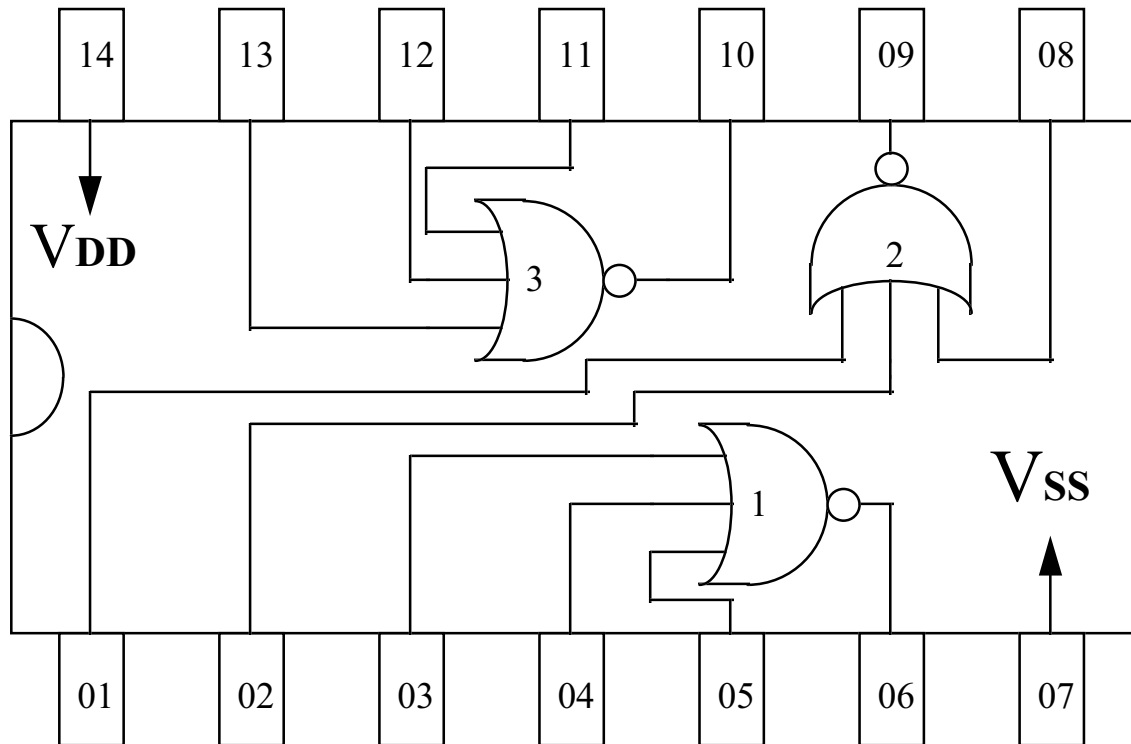


$V_{DD} = +5V$

$V_{SS} = \text{Ground} / 0V$

## Physical Layout Diagram for 4025


# Digital Logic.

Example Layout of a Truth Tables that will be entered in Log Book.
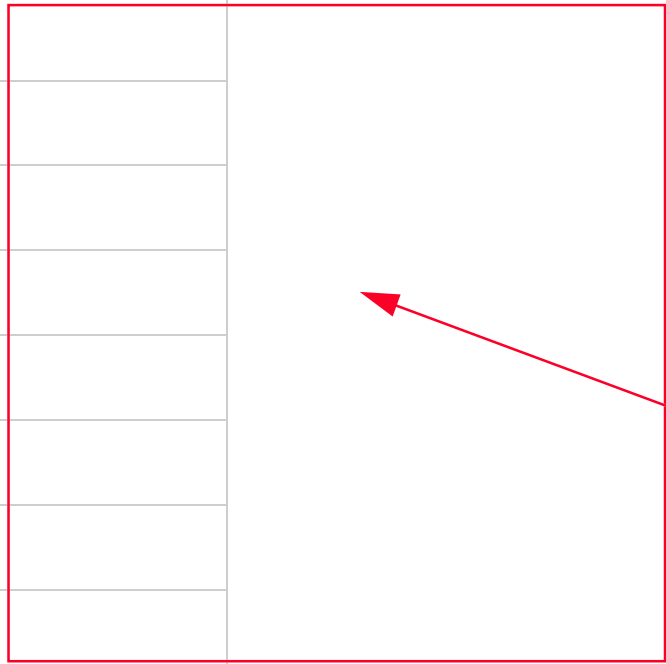
<u>Inputs</u>			<u>Output</u>	<u>Comments</u>
A	B	C	O/P	
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

You fill  
in this  
area

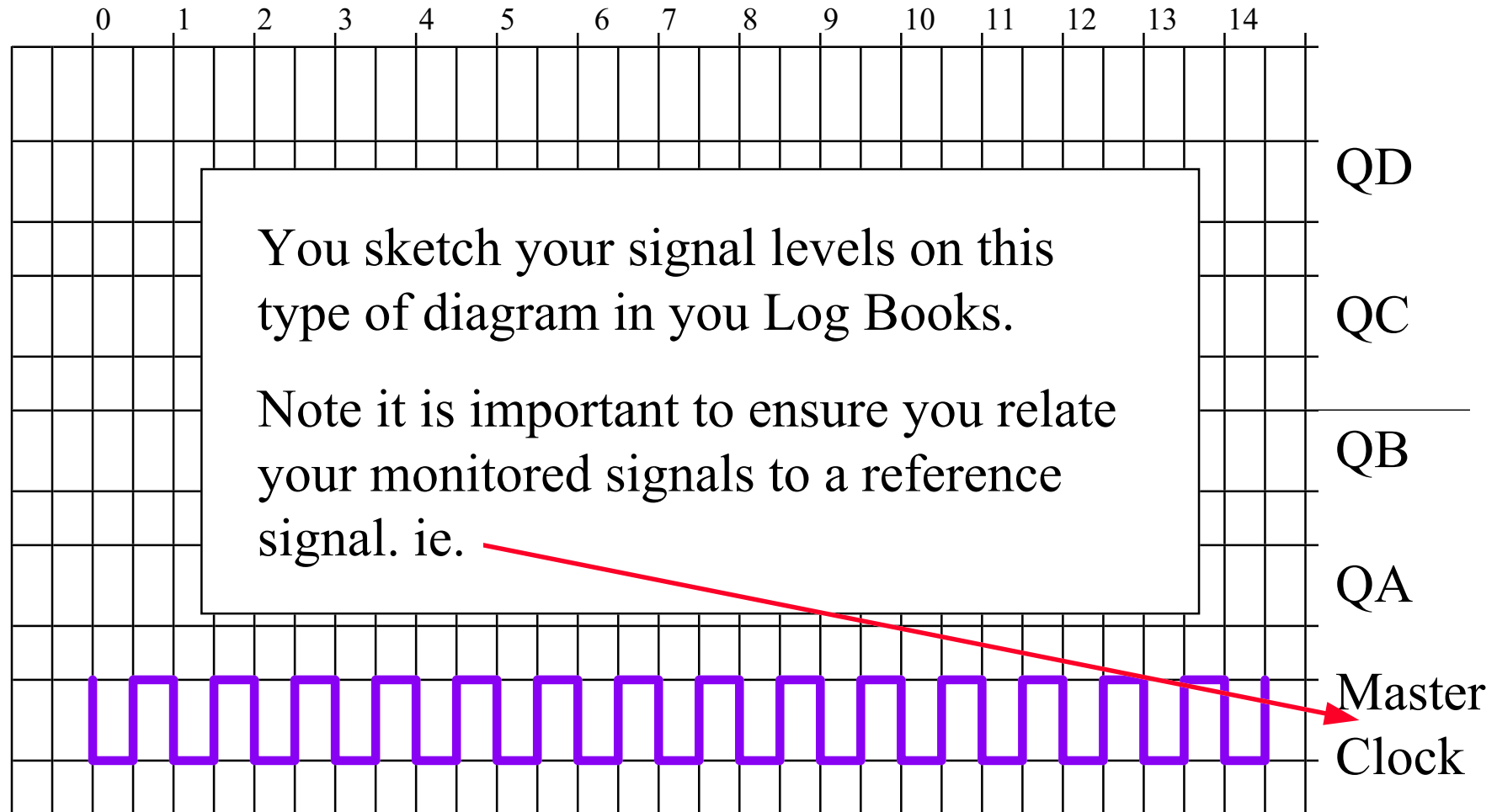


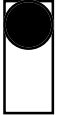
# Logic Functions.



A Example of a Signal Level or State Diagram.




# Digital Logic.

- Using the Logic Box. See Circuit 1.
- Connect Logic State Input Switches to the LED Logic State Output Monitor Points.
- Note Switch **up**  indicates a LOGIC “1”  
the Switch **down**  is a LOGIC “0”
- Monitor and record on a truth table in your Log Book the Output state for all combinations of Logic Inputs.
- Note LED **on**  indicates a LOGIC “1” the LED **off**  is a LOGIC “0”

Circuit 1

# Digital Logic.

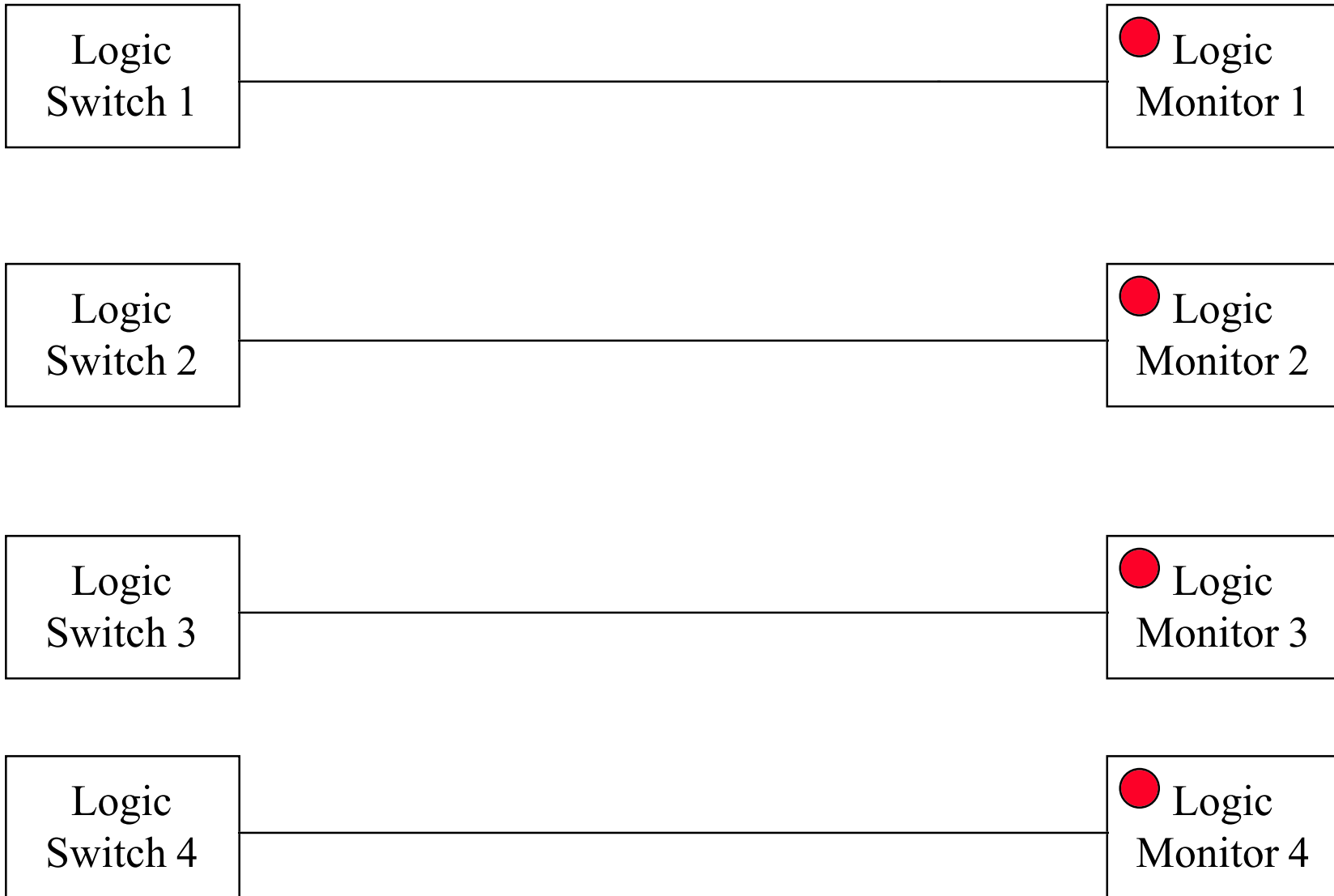


# Digital Logic.

- Gates **Test 1** Use Chip 4011.
- Using Circuit 2 as an example Connect Switch Logic levels to Pins 1 and 2 of the 4011 Integrated circuit chip.
- Monitor and record on a truth table the output state for all combinations of Logic Input.
- Conclusion Does the truth table you have drawn match the expected results ?



## Circuit 2

# Digital Logic.

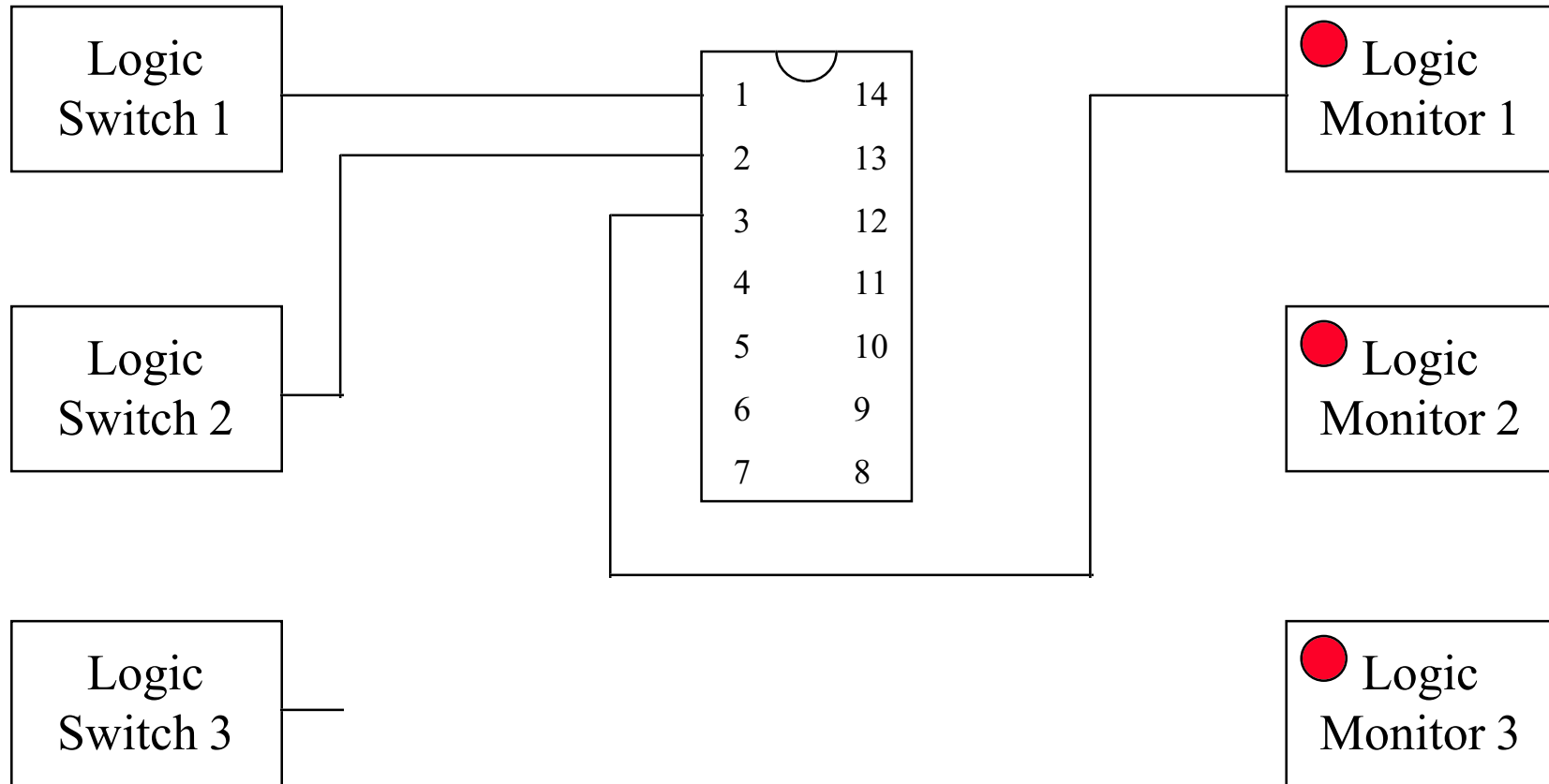


Apply +5V to Pin 14 and 0V or Ground to Pin 7

# Digital Logic.

- Gates **Test 2** Use Chip 4025.
- Using Circuit 3 as an example Connect Switch Logic levels to Pins 1, 2 and 3 of the 4025 Integrated circuit chip.
- Monitor and record on a truth table the output state for all combinations of Logic Input.
- Conclusion Does the truth table you have drawn match the expected results ?

### Circuit 3

# Digital Logic.

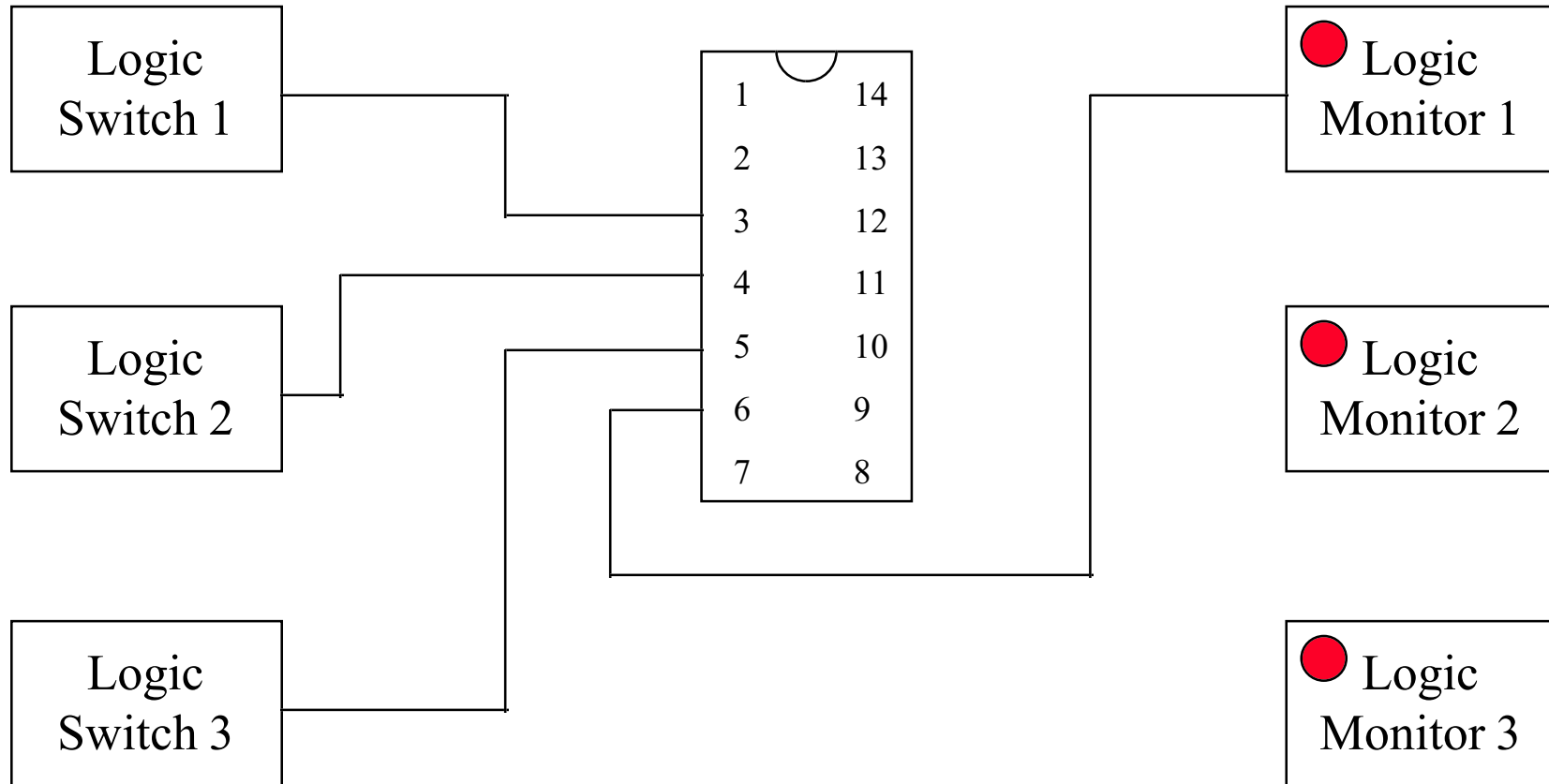


Apply +5V to Pin 14 and 0V or Ground to Pin 7

# Digital Logic.

- Gates **Test 3** Use Chip 4011.
- Build the circuit shown in Circuit 4.
- Monitor and record on a truth table the output state for all combinations of Logic Input.
- Conclusion Does the truth table you have drawn match the expected results ?
- What logic functions has been created by this gate combination.

## Circuit 4

# Digital Logic.

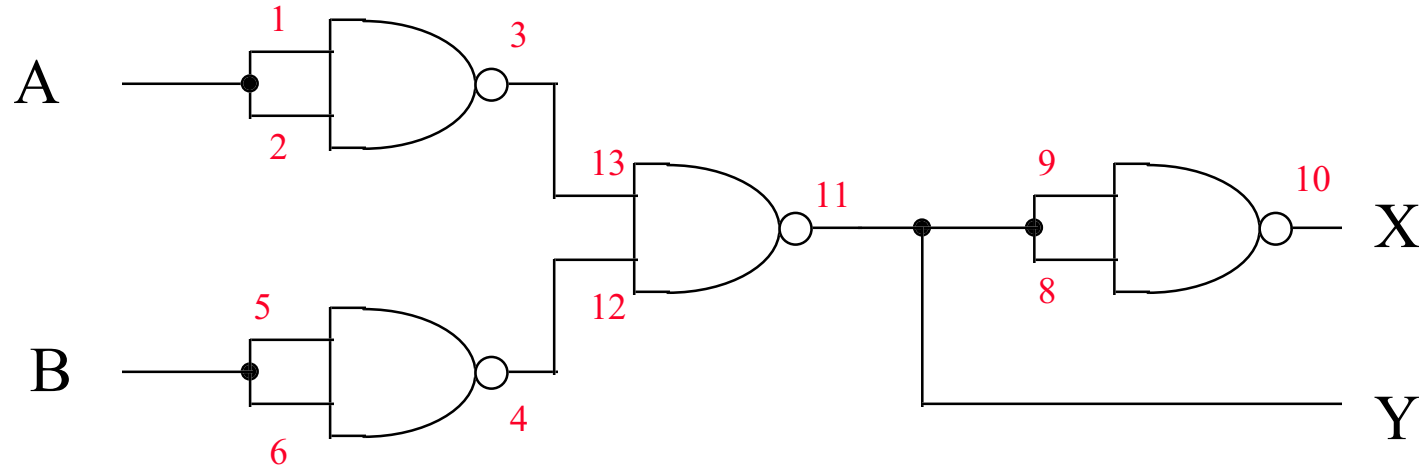

Use Chip 4011

Apply +5V to Pin 14 and 0V or Ground to Pin 7


Suggested Pin  
configuration

# Digital Logic.

- Gates **Test 4** Use Chip 4001.
- Build the circuit shown in Circuit 5.
- Monitor and record on a truth table the output state for all combinations of Logic Input.
- Conclusion Does the truth table you have drawn match the expected results ?
- What logic functions has been created by this gate combination.

## Circuit 5

# Digital Logic.

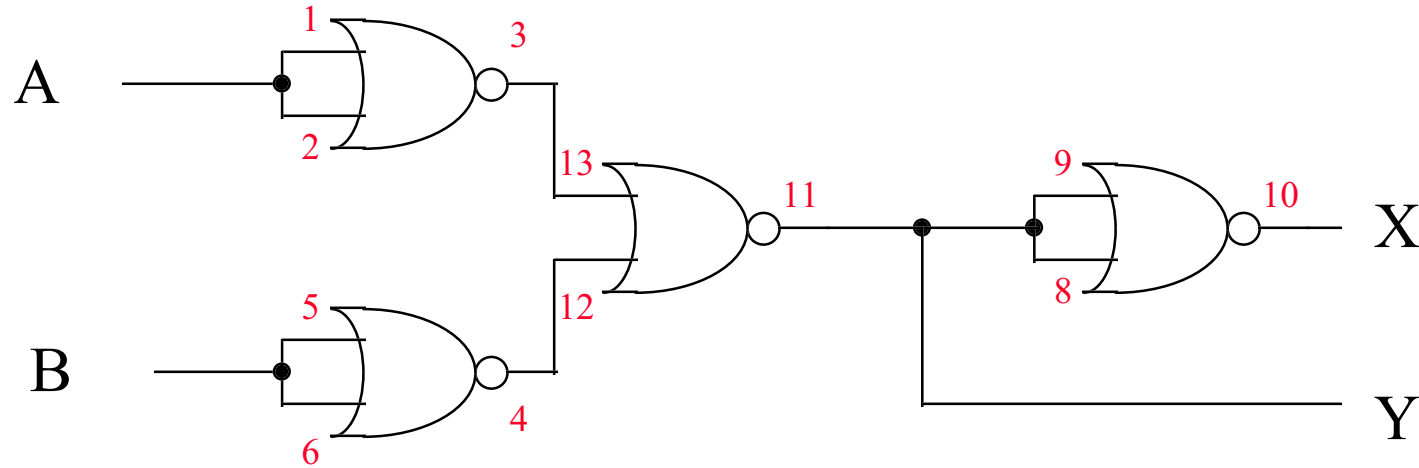

Use Chip 4001

Apply +5V to Pin 14 and 0V or Ground to Pin 7

Suggested Pin  
configuration


# Digital Logic.

- Counters **Test 1** Use Chip 4013.
- Build the circuit shown in Circuit 6.
- Monitor and record on a Signal State Diagram the Output state of all the indicated monitor points.
- Conclusion What does the Signal State Diagram indicate to you ?



## Circuit 6

# Logic Functions.

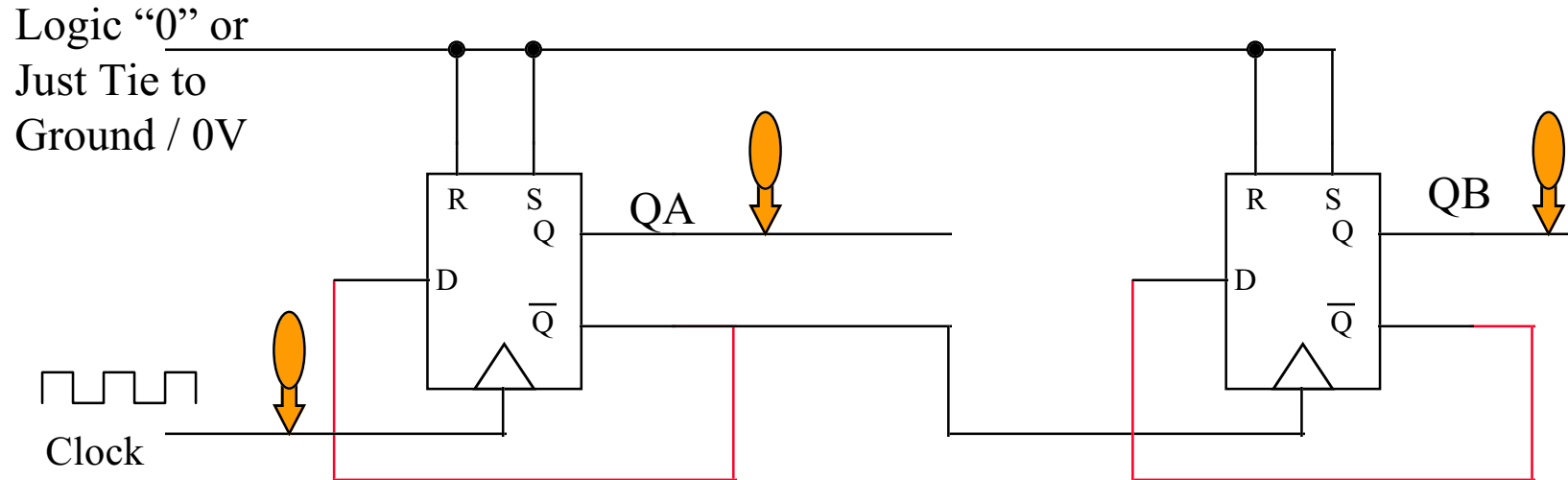

Set Clock to 1Hz, If speed too fast to see what is happening then create a manual Clock using a Debounce Logic Switch. Toggle it at an appropriate speed to record results.

Apply +5V to Pin 14 and 0V or Ground to Pin 7


Use Chip 4013

# Digital Logic.

- Counters **Test 2** Use Chip 4013.
- Build the circuit shown in Circuit 7.
- Toggle the R and S logic inputs. Monitor and record on a Signal State Diagram or truth table the Output state of the indicated monitor points.
- Conclusion What effect do the R & S inputs have on the circuit ?

## Circuit 7

# Logic Functions.

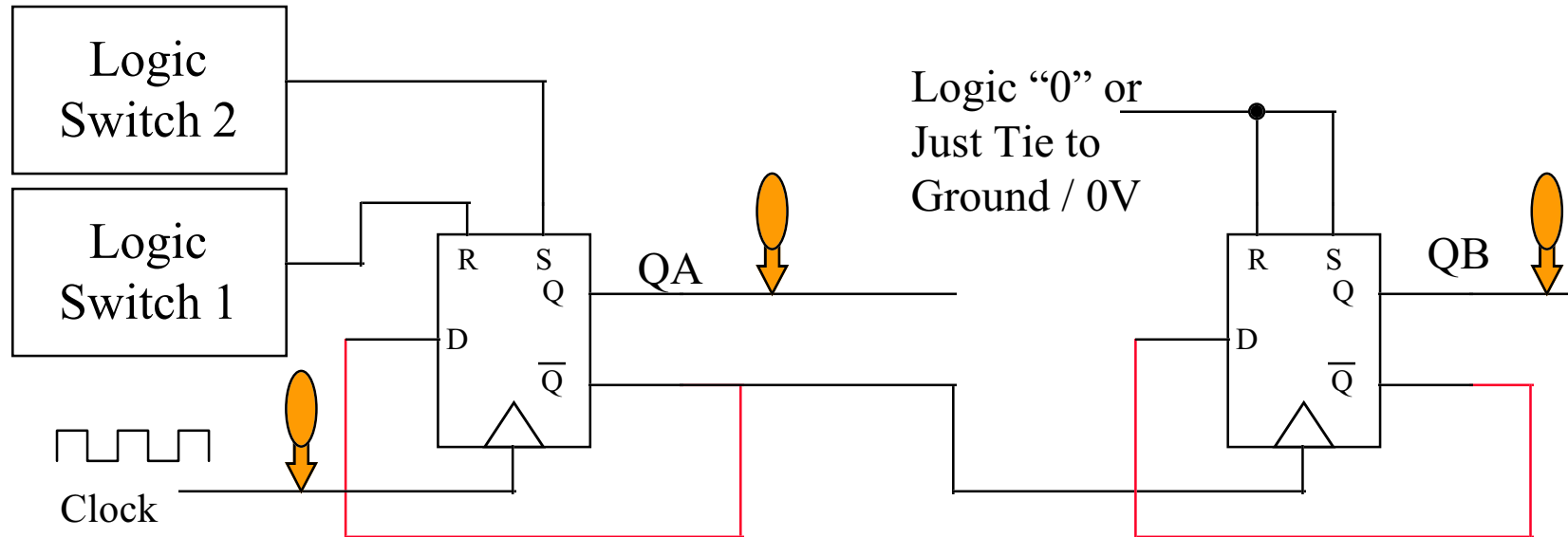

Set Clock to 1Hz.

Apply +5V to Pin 14 and 0V or Ground to Pin 7

Use Chip 4013



# Digital Logic.

- Counters **Test 3** Use Chip 4013.
- Build two copies of the the circuit shown in Circuit 6. Chain the two circuits together.
- Monitor and record on a Signal State Diagram the Output state of all the indicated monitor points.
- With the information gained in this circuit and Circuit 7. Create a counter that divides an input clock by TEN.

# Digital Logic.

- Decoder Test 1 Use Seven Segment LED.
- Use a Switch Logic “1” to display a “1” on a Seven Segment Display.
- Use a Switch Logic “0” to display a “0” on a Seven Segment Display.
- Note You need to define what Segments need to be lit for each logic state before you attempt to wire up circuit.
- Note Some segments are not connected.

# Digital Logic.

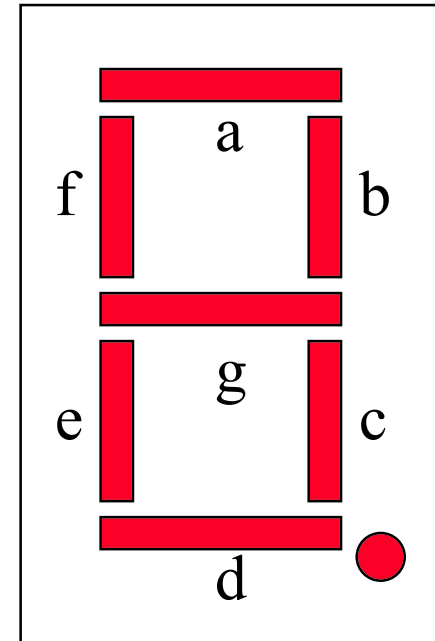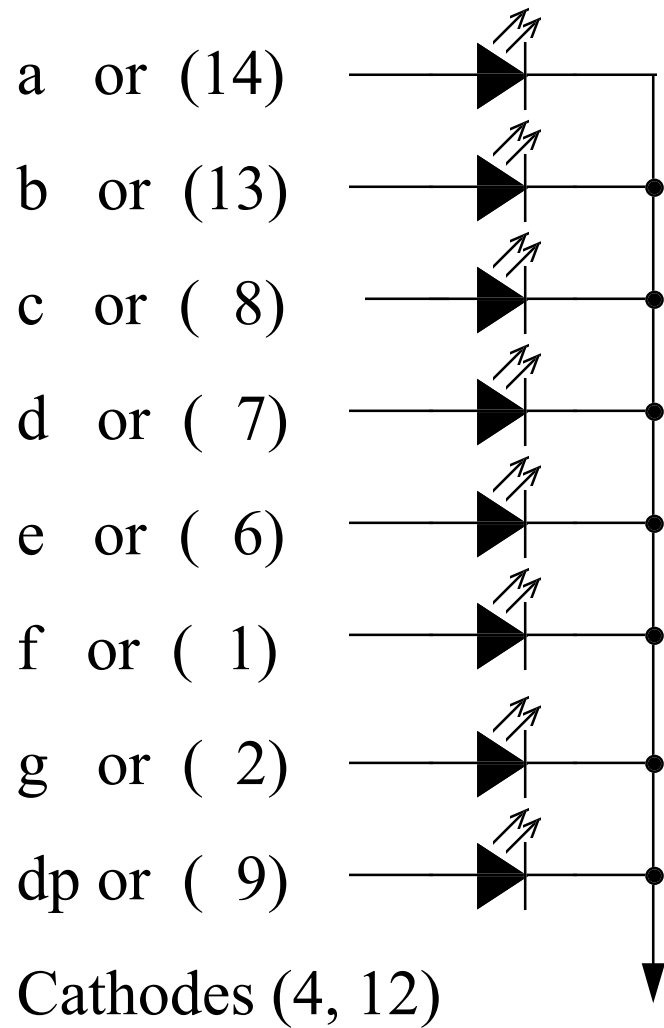


N/c Pins are (3,5,10 and 11)

**(The Common Cathode) Seven Segment Display.**
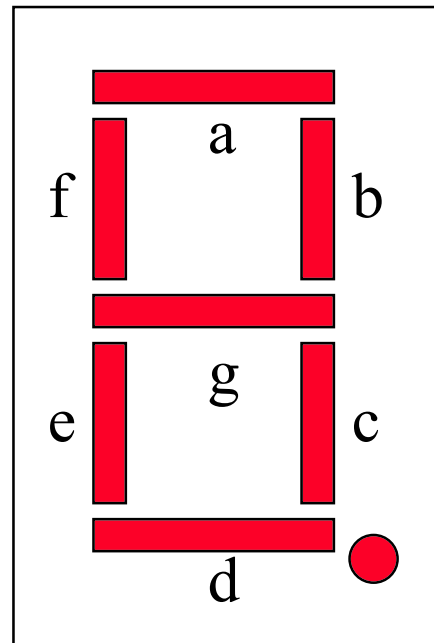
# Digital Logic.

Pin 1 is at  
the Top  
Left hand  
Corner.


Count pins around  
the device in an  
anti-clockwise  
direction.



N/c Pins are (3,5,10 and 11)

**(The Common Cathode) Seven Segment Display.**


# Digital Logic.

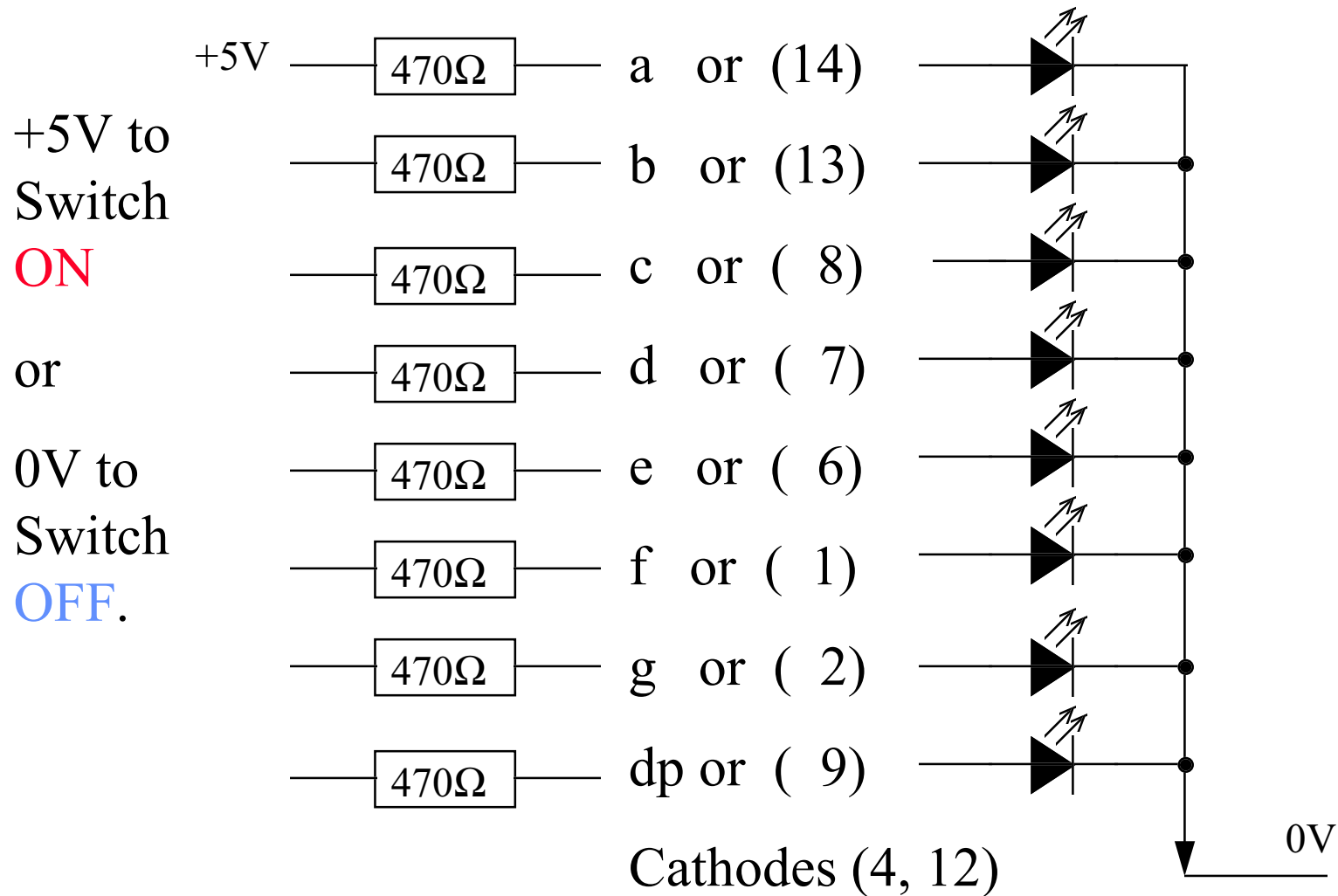

**(The Common Cathode) Seven Segment Display.**




# Digital Logic.

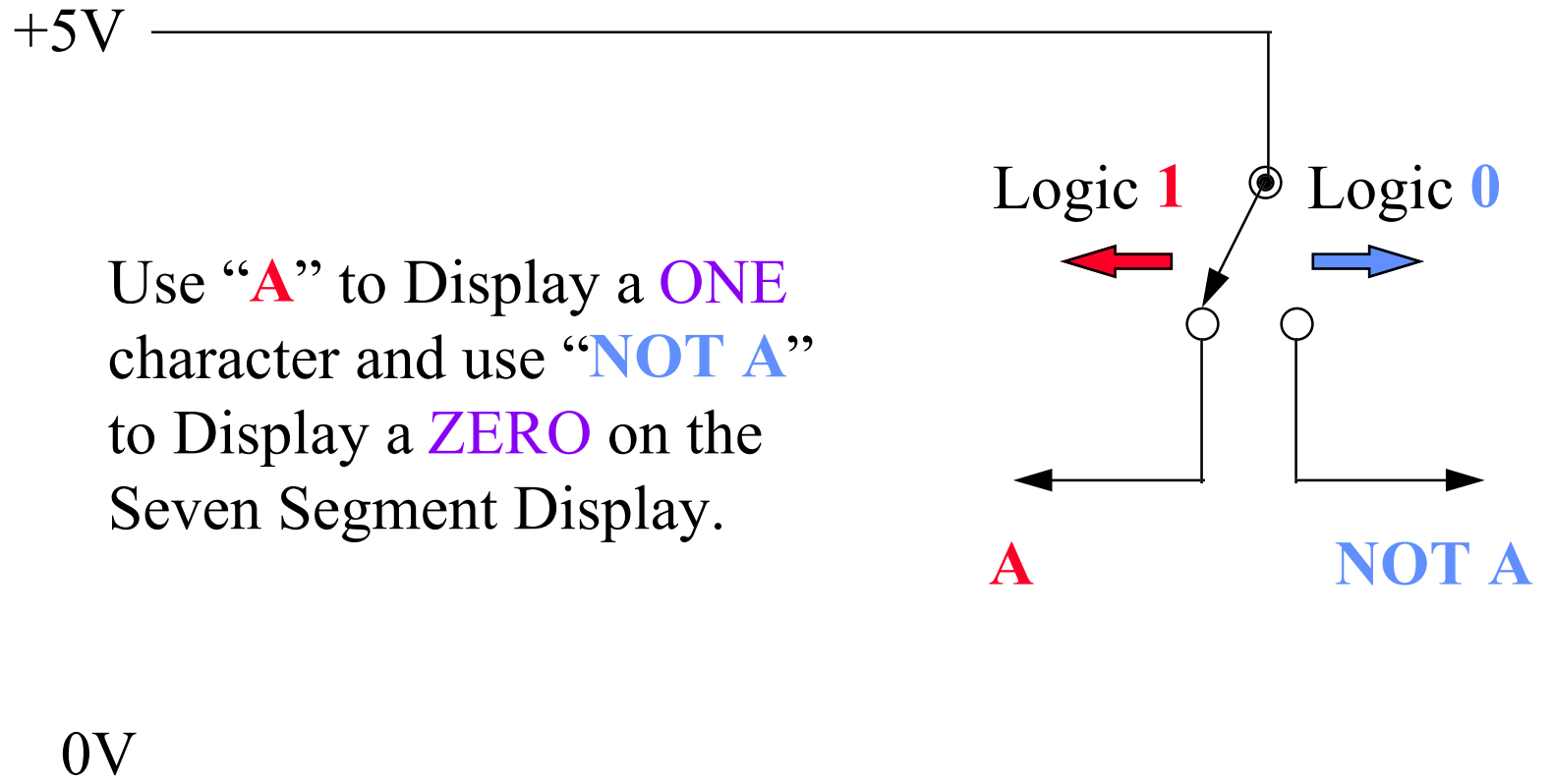

## Switch Logic Options.

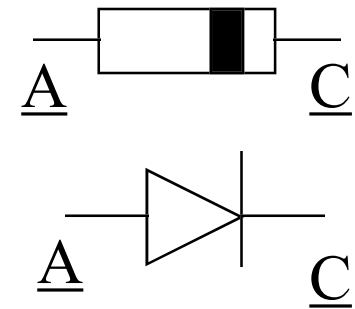
# Digital Logic.

Repeat these circuit elements as required.



Segment Choice “0”  
if required.

Segment Choice “1”  
if required.

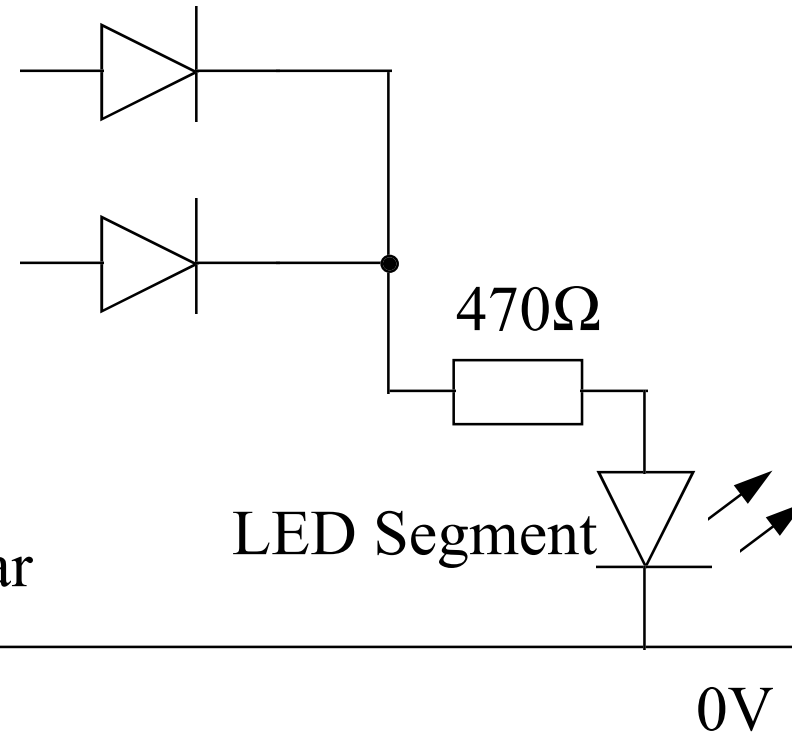



Diodes are 1N4001 or similar

# Digital Logic.


- One Shot **Test 1** Use Chip 4013.
- Build the circuit shown in Circuit 8.
- Monitor and record on a Signal State Diagram the Output state of all the indicated monitor points.
- Conclusion How might this circuit be used to control a 4026 chip ? What would happen if the following clock signal was applied to this circuit after a Reset signal.




# Logic Functions.

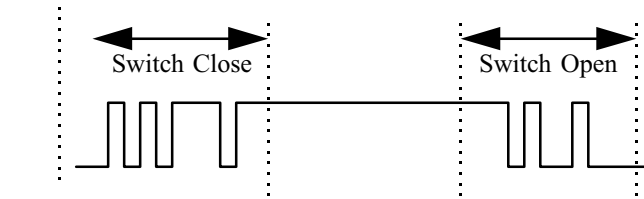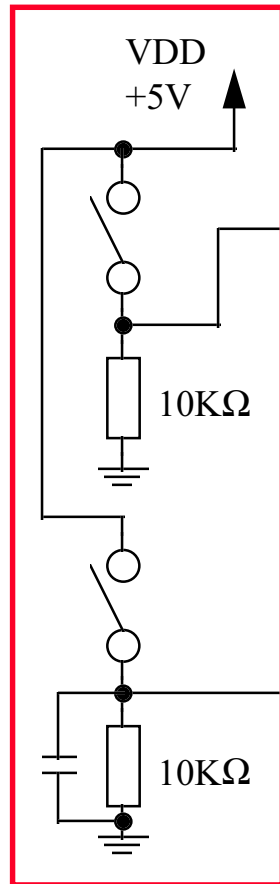

**Switch without Debounce.**

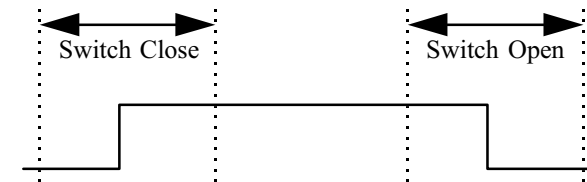

**Ideal Debounce Output.**

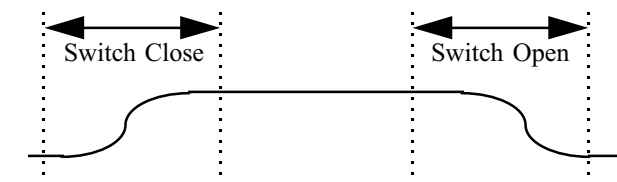


**Switch with Capacitor Debounce.**

## Debounce Switches on Logic Box.

## Circuit 8

# Logic Functions.

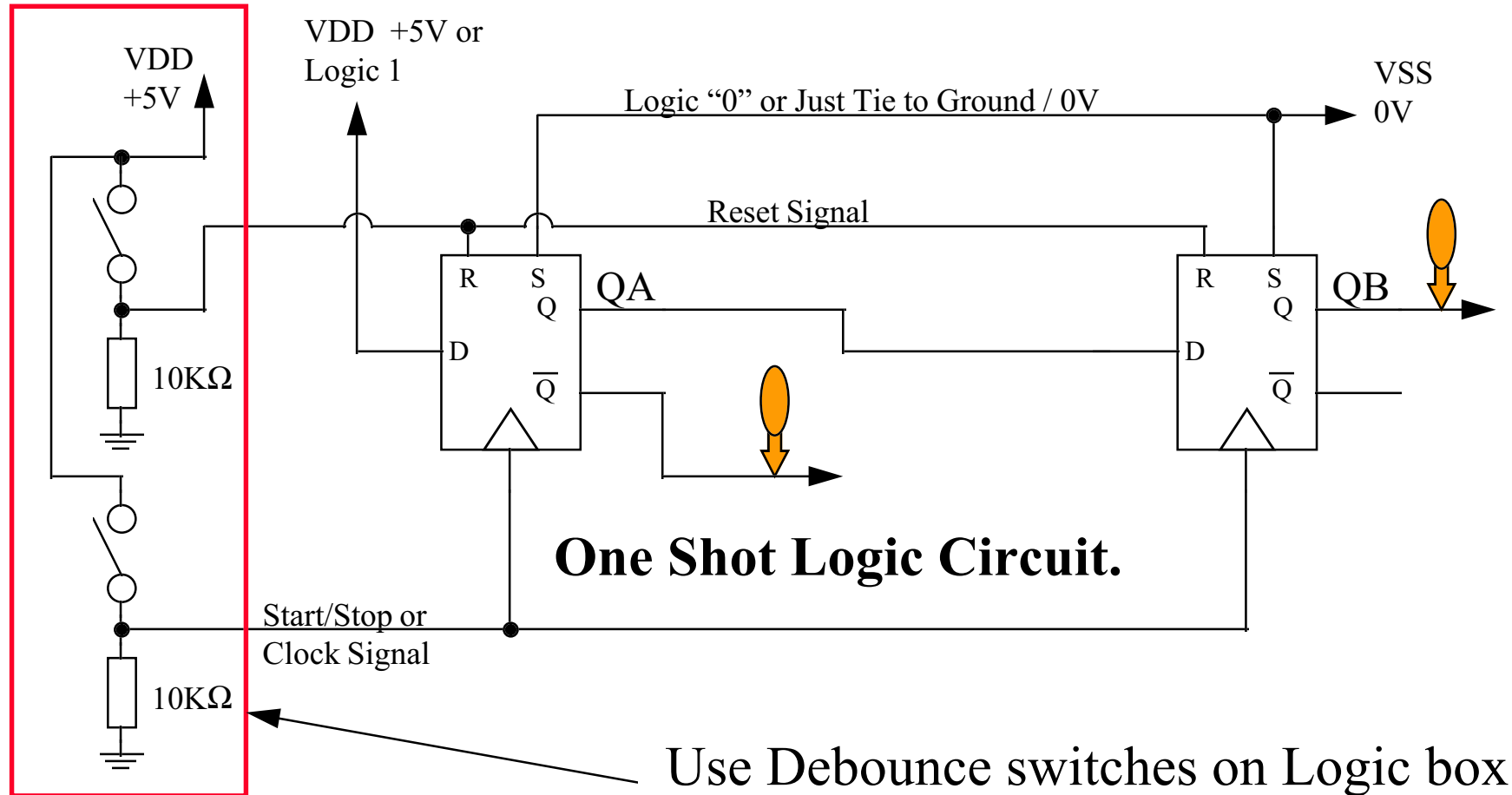


Use Debounce switches on Logic box to simulate these circuits

Use Chip 4013

Remember to Apply +5V to Pin 14 and 0V or Ground to Pin 7

# Digital Logic.

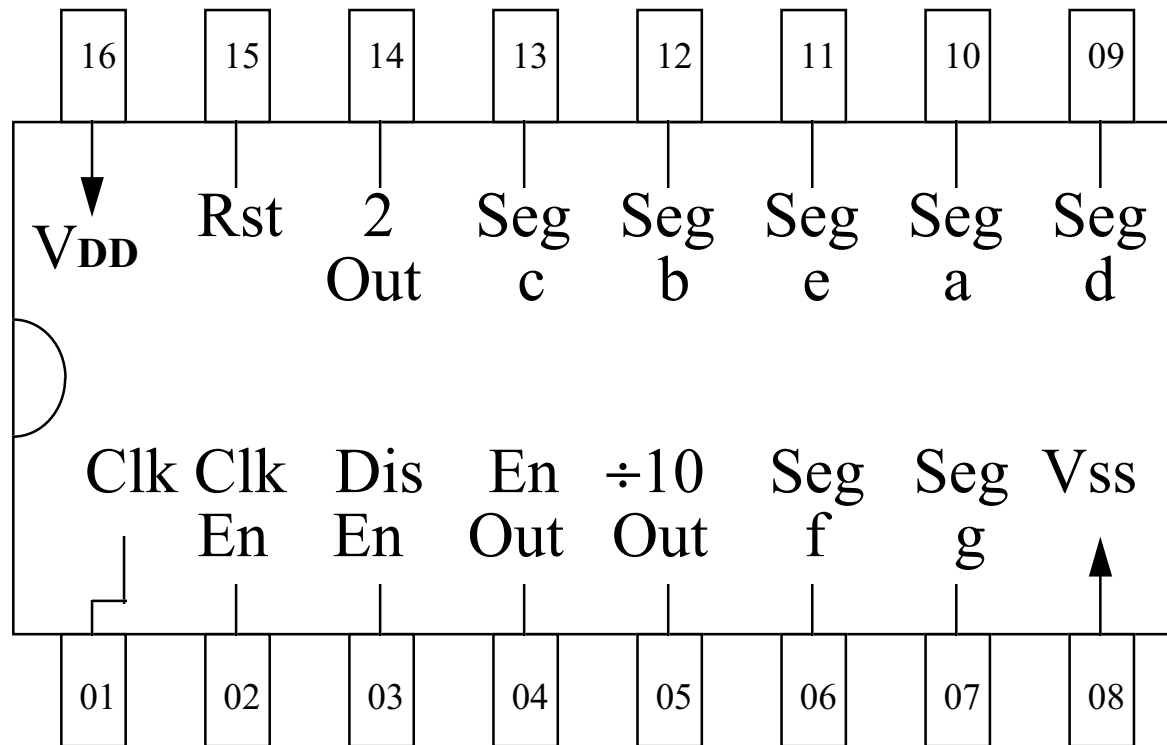

Seg = Segment

Rst = Reset

÷10 = Clk/10

Dis = Display

En = Enable

Clk = Clock

V<sub>DD</sub> = +5V

V<sub>SS</sub> = Ground / 0V

## Physical Layout Diagram for 4026

# Digital Logic.


## Control Signals of the 4026 Chip.

Reset	Count Enable	Effect
1	Dont Care	Chip Reset, Count=0
0	1	Counting Inhibited
0	0	Counting Permitted

Display Enable = 0 = Display off

Display Enable = 1 = Display on

# Digital Logic.

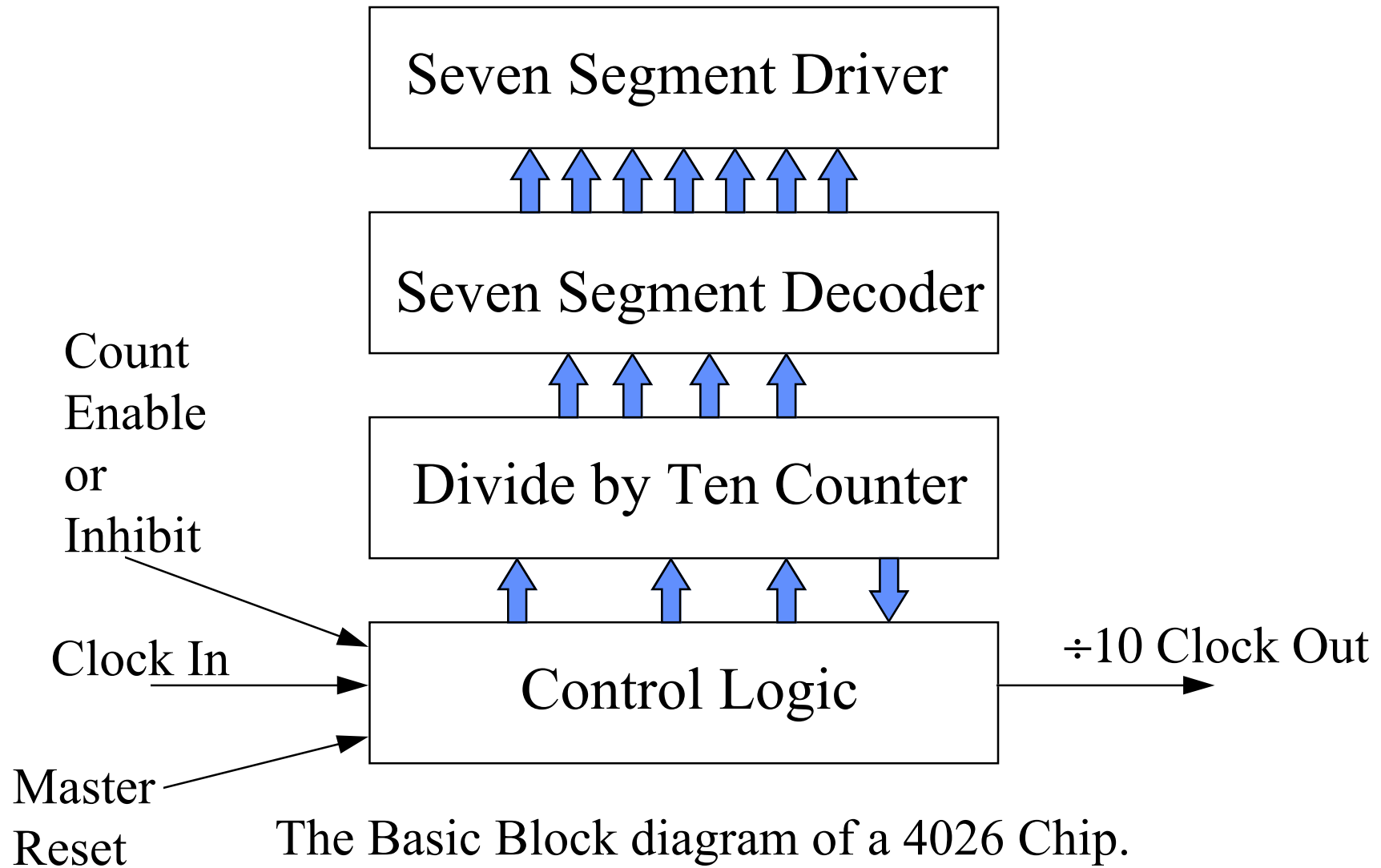


The Basic Block diagram of a 4026 Chip.




# Experiment 11.

# Magnetic Flux Experiments.

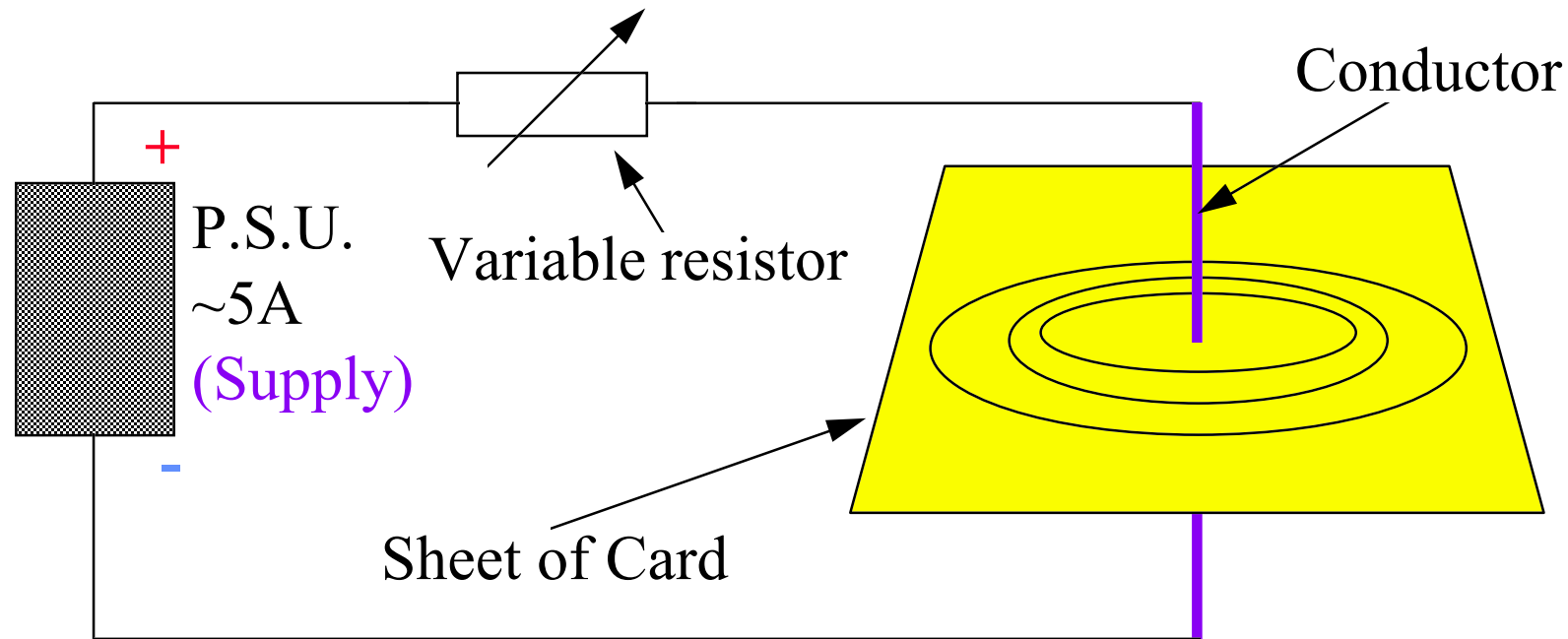


1. Apply/dust Iron filings on the card.
2. Apply current to the conductor (to set up a magnetic field)
3. Gently tap card so Iron filings mark the lines of flux
4. Sketch patterns the Iron filings make on the card.

# Magnetic Flux Experiment 1.

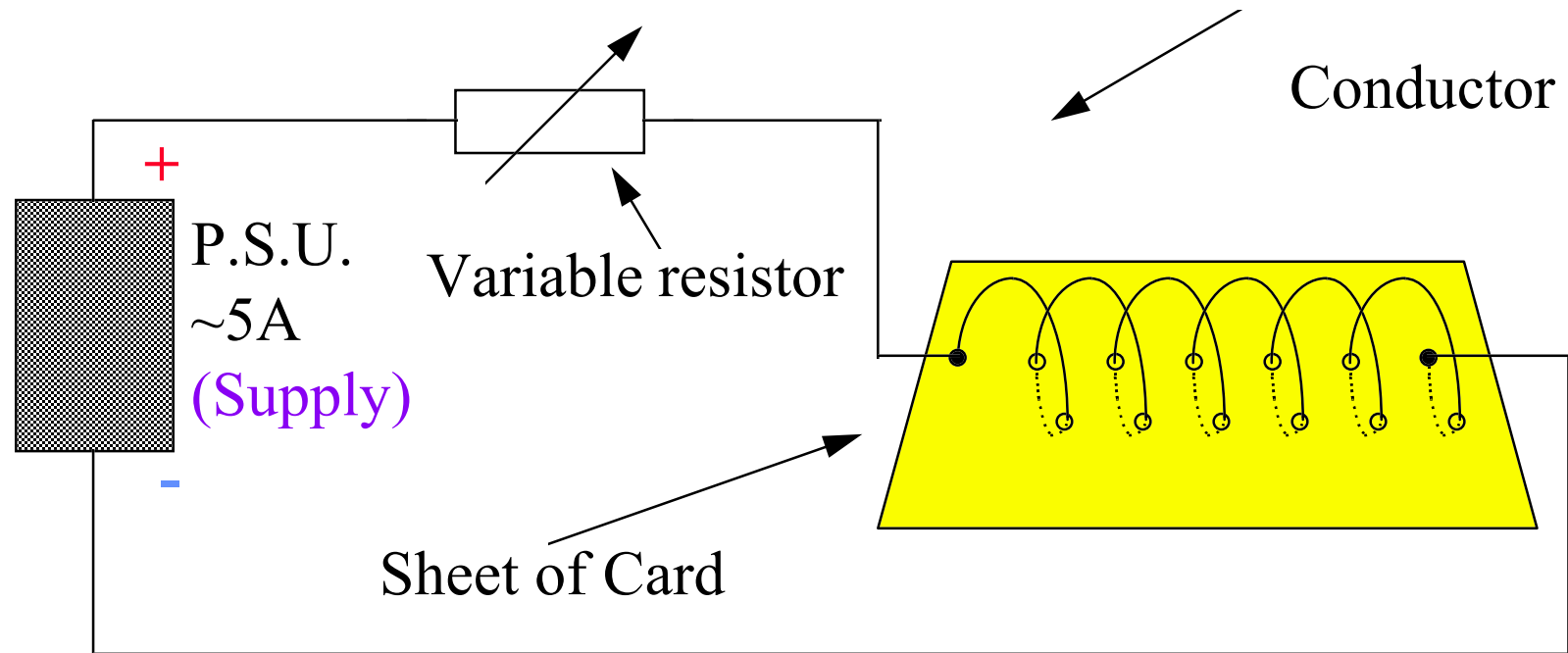


1. Apply/dust Iron filings on the card.
2. Apply current to the conductor (to set up a magnetic field)
3. Gently tap card so Iron filings mark the lines of flux
4. Sketch patterns the Iron filings make on the card.

# Magnetic Flux Experiment 2.

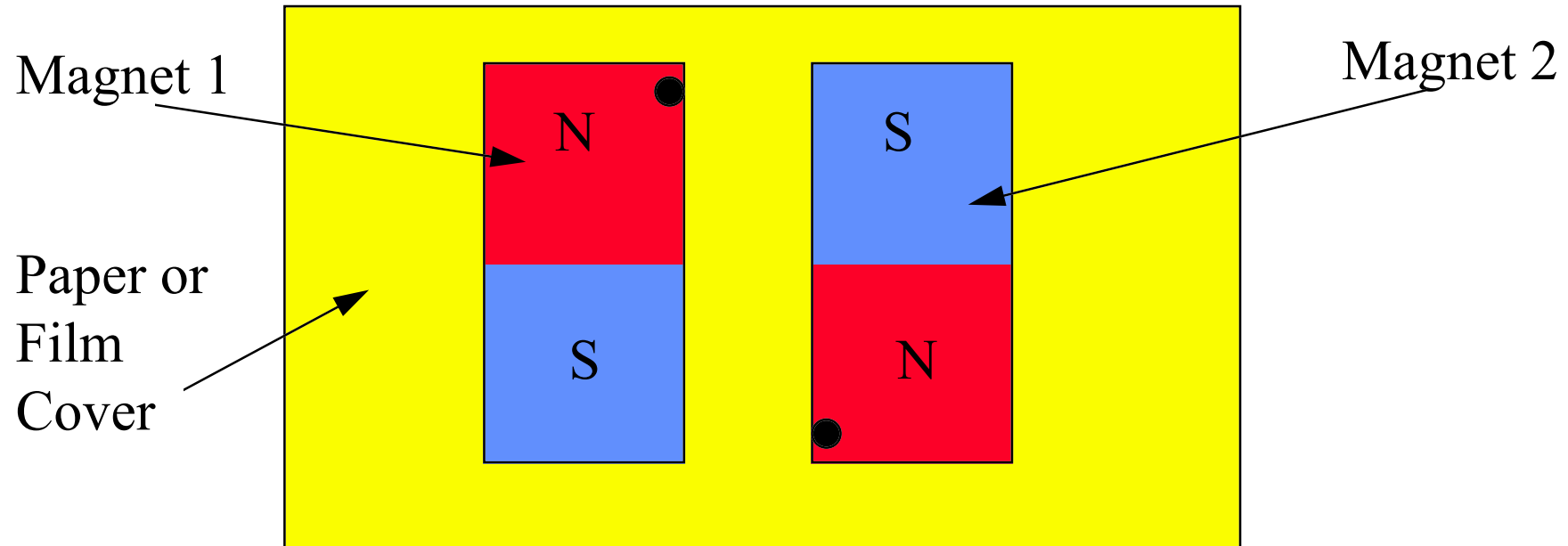

1. Position magnets in holder as shown above.
2. Protect magnets with cover.
3. Apply/dust Iron filings on the card.
4. Gently tap card so Iron filings mark the lines of flux
5. Sketch patterns the Iron filings make on the card.

# Magnetic Flux Experiment 3.

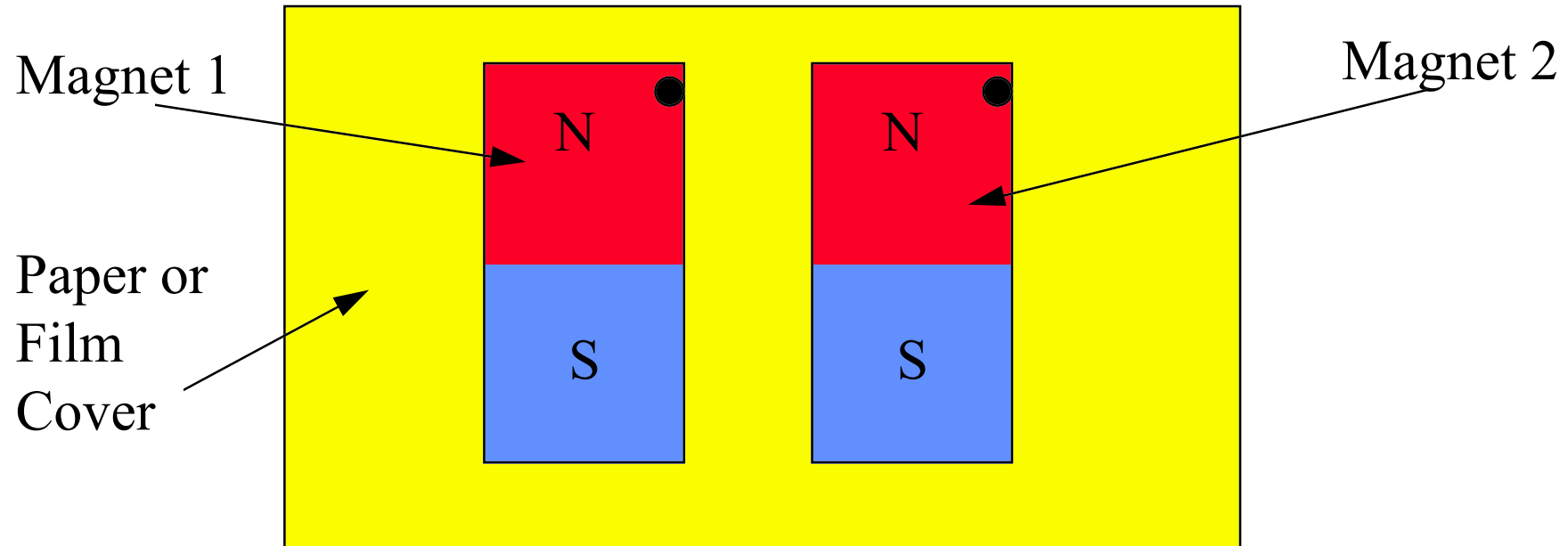

1. Position magnets in holder as shown above.
2. Protect magnets with cover.
3. Apply/dust Iron filings on the card.
4. Gently tap card so Iron filings mark the lines of flux
5. Sketch patterns the Iron filings make on the card.

# Experiment 12.

# Motors.

- Questions concerning the powering of a mechanical device using an electrical motor.
- How are we going to find how much **Power** is **used** by the electric motor that drives the mechanical device ?
- How are we going to find how much **Power** is **developed** by the electric motor that is driving the mechanical device ?

# Motors.

- Most motors are reversible that is to say:
  - (1) They can convert electrical energy into mechanical power.  
and conversely
  - (2) They can convert mechanical power into electrical energy.



# Motors.

- We can measure electrical power easily:
  - (1) Use a meter to measure Voltage in Volts.  
and
  - (2) Use a meter to measure Current in Amps.
  - (3)  $\text{Power} = \text{Volts} * \text{Current}$


# Motors.

- Purpose of the Experiment:
- To find how efficiently a motor converts electrical energy into mechanical energy.
- Assumptions:
- Any losses in the system will be equally divided between the motor and the generator.
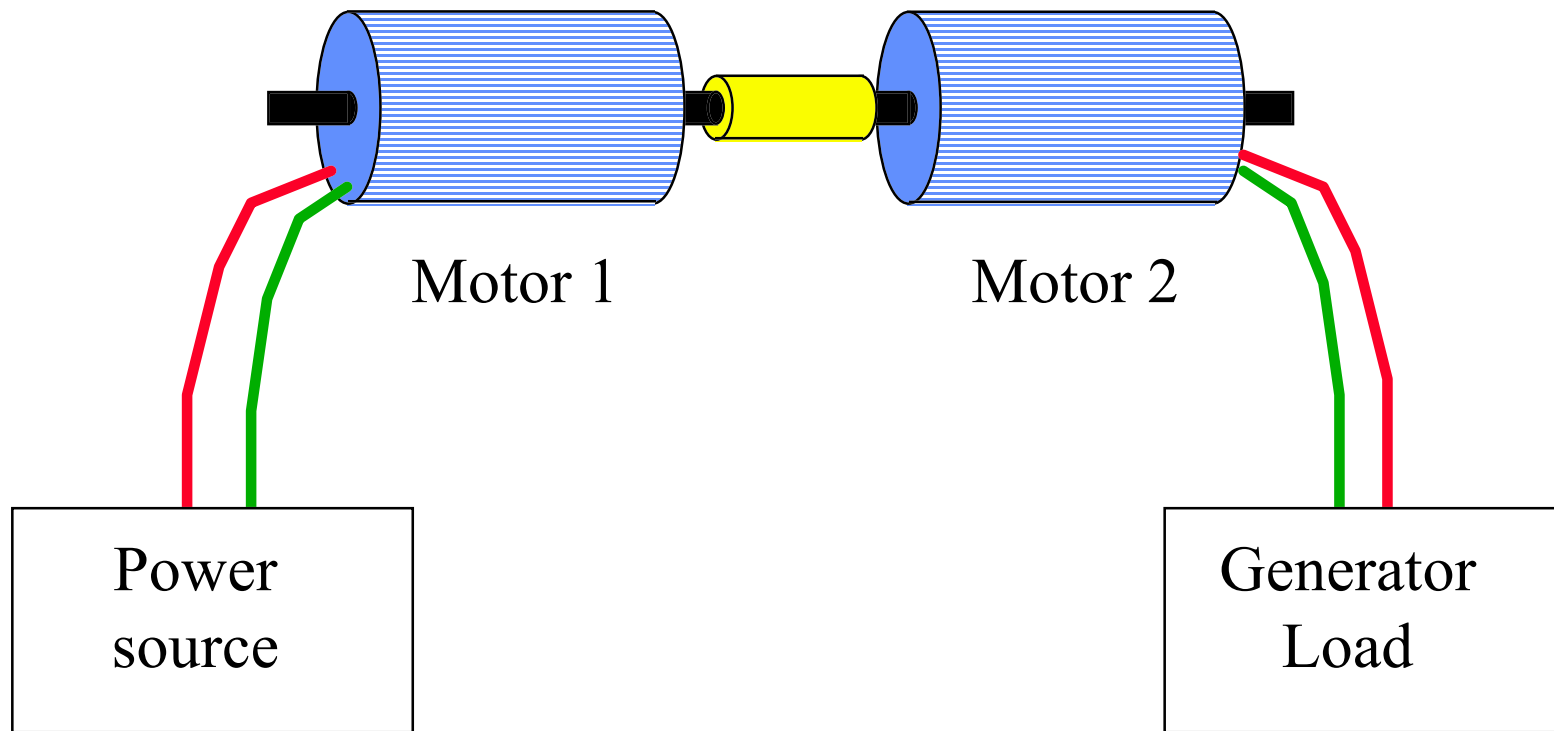
# Motors.

Connect motors as follows:

One motor will drive the shaft and the other motor will act as a power generator.



# Motors.

(1)  $\text{Power} = \text{Volts} * \text{Current}$

(2)  $\text{Current} = \text{Voltage} / \text{Resistance}$

Substitute (2) into (1)

$$\text{Power} = \text{Voltage} * \text{Voltage} / \text{Resistance}$$

or

$$\text{Power} = \text{Voltage}^2 / \text{Resistance}$$

# Motors.

Method (part 1)

1. Measure Power used by the motor.
2. Measure Power created by the generator.

Use Loads in table and then calculate efficiency  $\eta$  {Eta} as a percentage.

$$\eta = \frac{\text{Shaft Power}}{\text{Input Power}} = \frac{\text{Input Power} - \text{Losses} * 100\%}{\text{Input Power}}$$

# Motors.

Method (Part 2)

Calculate:

Power Loss = Input Power - Output Power

Power Loss per Motor = Power Loss / 2

# Motors.

I/P Voltage	I/P Current	Load Resistance	O/P Voltage
12V		50Ω	
12V		100Ω	
12V		200Ω	
12V		300Ω	
12V		400Ω	

# Motors.

Load Resistance	I/P Power	O/P Power	Losses
50Ω			
100Ω			
200Ω			
300Ω			
400Ω			



# Motors.


Load Resistance	I/P Power	Losses/2	Efficiency %
50Ω			
100Ω			
200Ω			
300Ω			
400Ω			

# Experiment 13.

# Transistors.

- Build “Circuit 1”.
- Monitor the Base Voltage.
- Adjust ( $V_{in}$ ) from 1.5V to 25V.
- On your worksheet:-
  - Record Voltage level ( $V_b$ ) when Collector Voltage ( $V_c$ ) starts to change.
  - Record Voltage level of ( $V_b$ ) when ( $V_{in}$ ) reaches 25V.
- What happened to ( $V_c$ ) as ( $V_b$ ) approached 0.5V as ( $V_{in}$ ) was adjusted from 1.5V ?

# Transistors.

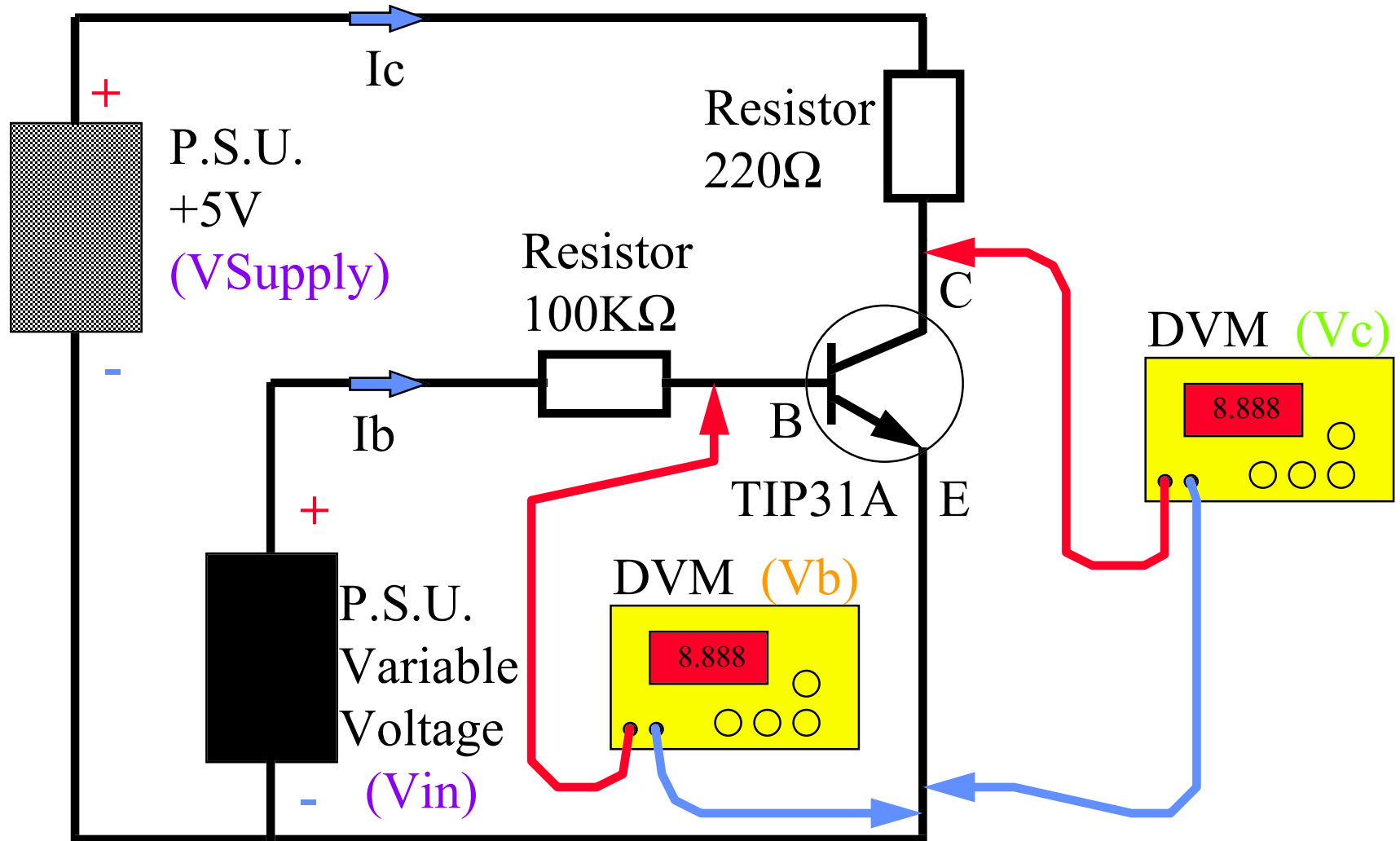


Circuit 1

# Transistors.

- Build “Circuit 2”.
- Monitor the Collector Voltage ( $V_c$ ).
- Adjust ( $V_{in}$ ) from 0V to 29V in 1V steps.
- On your worksheet:-
  - Record Voltage level at the Collector for each change of ( $V_{in}$ ). and enter them into the spreadsheet.
  - Identify on your graph where the Transistor becomes saturated.
  - Show how you may use your graph to calculate the current gain of the transistor.


# Transistors.

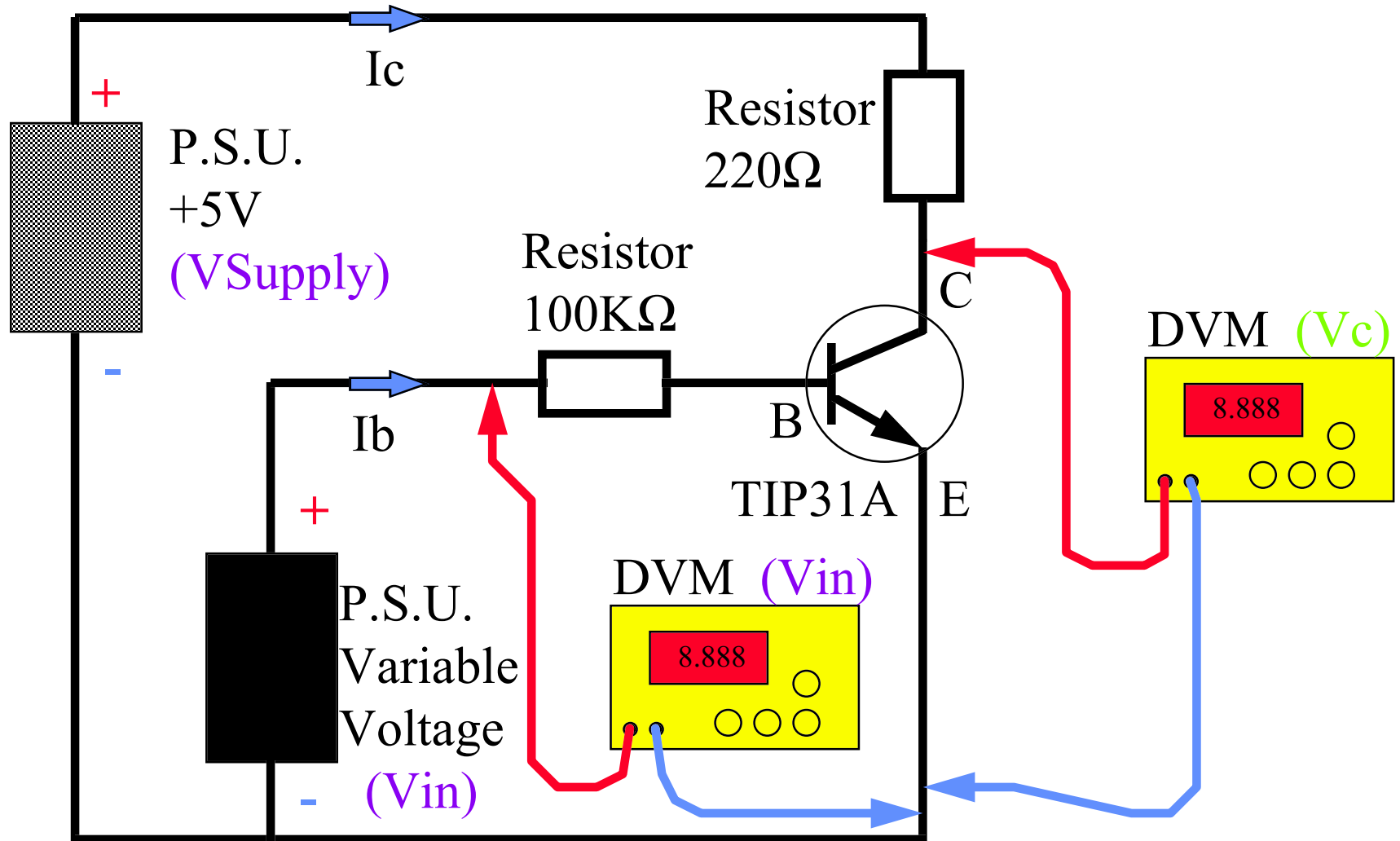


Circuit 2

# Transistors.


Face on View

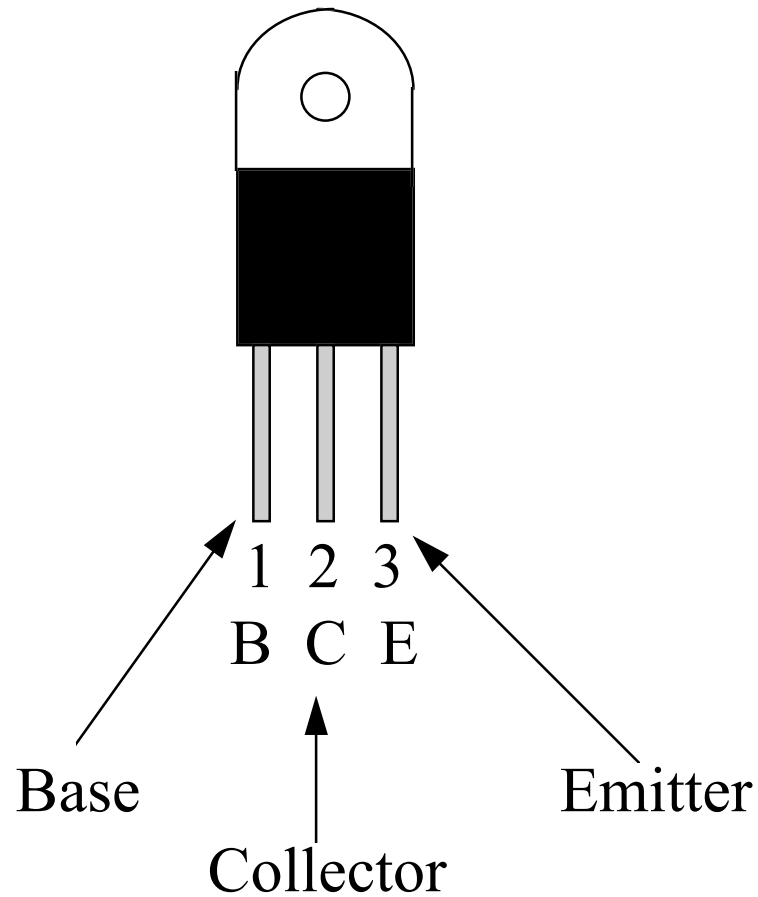

NPN  
Transistor

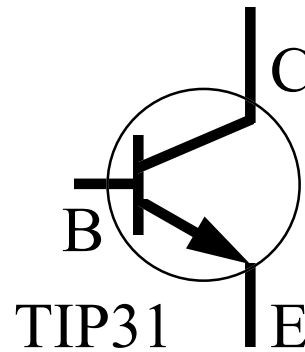

PNP  
Transistor

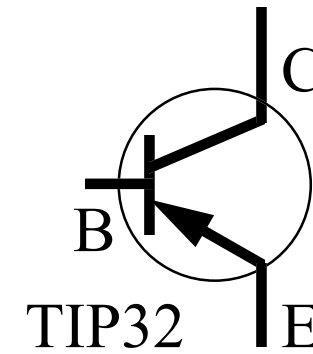


Pin Layout for these  
particular transistors.

# Experiment 14.



# Inductors and Capacitors.

Set Signal generator to a Sine wave with a frequency of 30KHz and an amplitude of 2 Volts peak to peak.

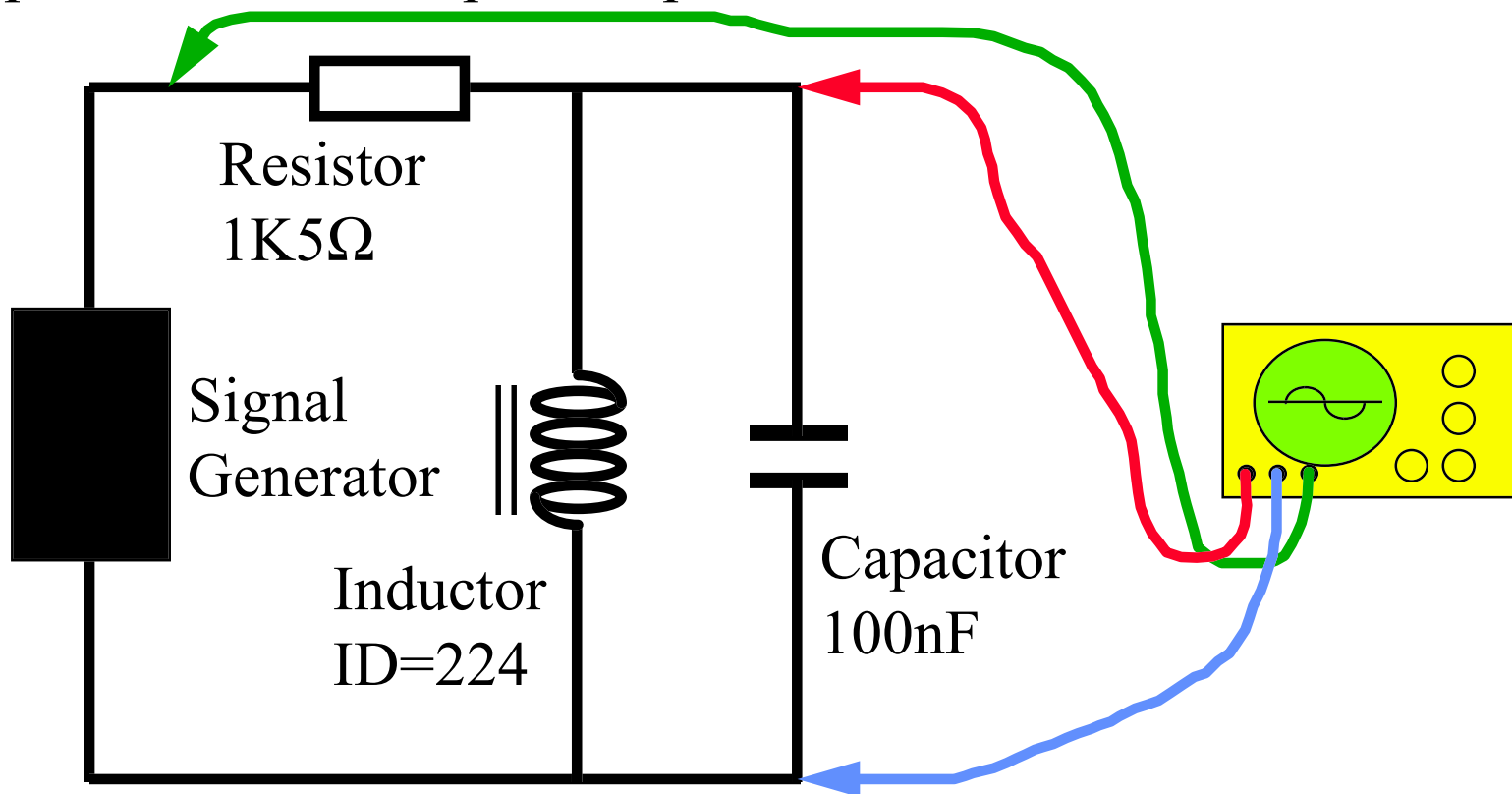

**Circuit 1**

# Inductors and Capacitors.

- Build “Circuit 1”.
- With initial settings sketch the CRO display.
- Increase frequency to 40KHz sketch the CRO display.
- Decrease frequency to 30KHz in 1KHz steps. Record the amplitude of the the voltage across the Inductor.
- Plot a graph of the amplitude recordings against frequencies .

# Inductors and Capacitors.

- If the value of Inductance was 0.22mH calculate the frequency where  $X_l = X_c$  using the formulae.

$$\text{Frequency } f = \frac{1}{2 \pi \sqrt{LC}}$$

# Inductors and Capacitors.

- Conclusion:-
- What did you notice about the position of the Source Voltage with respect to the Voltage across the Capacitor, Inductor?
  - Did frequency effect this position/phase and if so how did it effect it?
- In what way did the frequency have an effect on the reactance of the Capacitor, Inductor circuit?
- What happened at frequency where  $X_c = X_l$ ?


# Experiment 15.

# Power Units.

- Build “Circuit 1”.
- With initial setting sketch CRO display.
- Reduce the **Resistance Box** value in steps to its lowest value and produce a table of measured Output voltage against Switched Resistance value.
- Sketch the CRO display on lowest resistance setting.
- Reset **Resistance Box** value back to 470K $\Omega$ .

# Power Units.

Using a Transformer module to supply the Low Voltage AC Source build circuit shown below:-

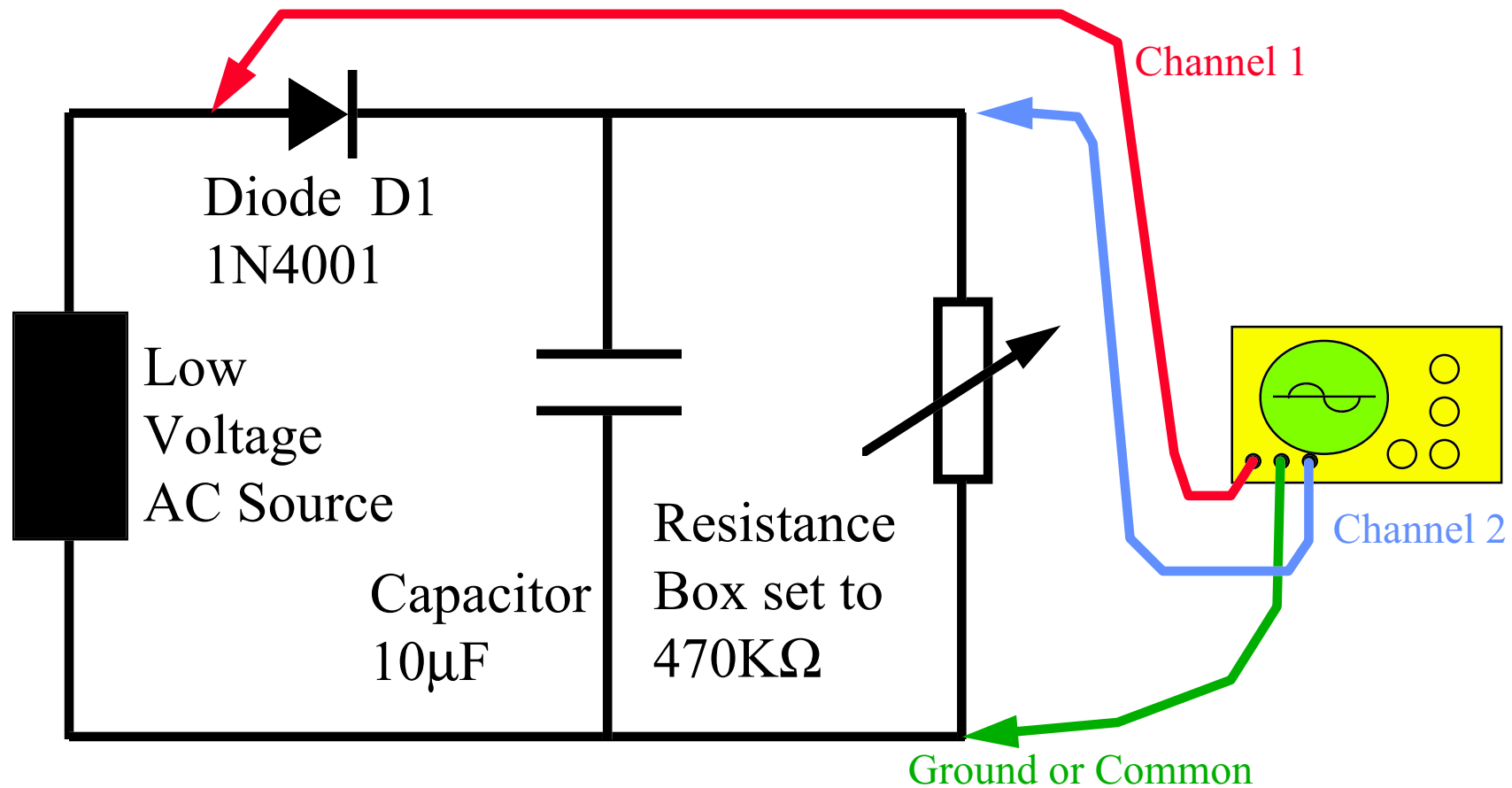

**Circuit 1**


# Power Units.

- Build “Circuit 2”.
- With initial setting sketch CRO display.
- Reduce the **Resistance box** values in steps to its lowest value and produce a table of measured Output voltage against Switched Resistance value.
- Sketch the CRO display on lowest resistance setting.



# Power Units.

Using a Transformer module to supply the Low Voltage AC Source build circuit shown below:-

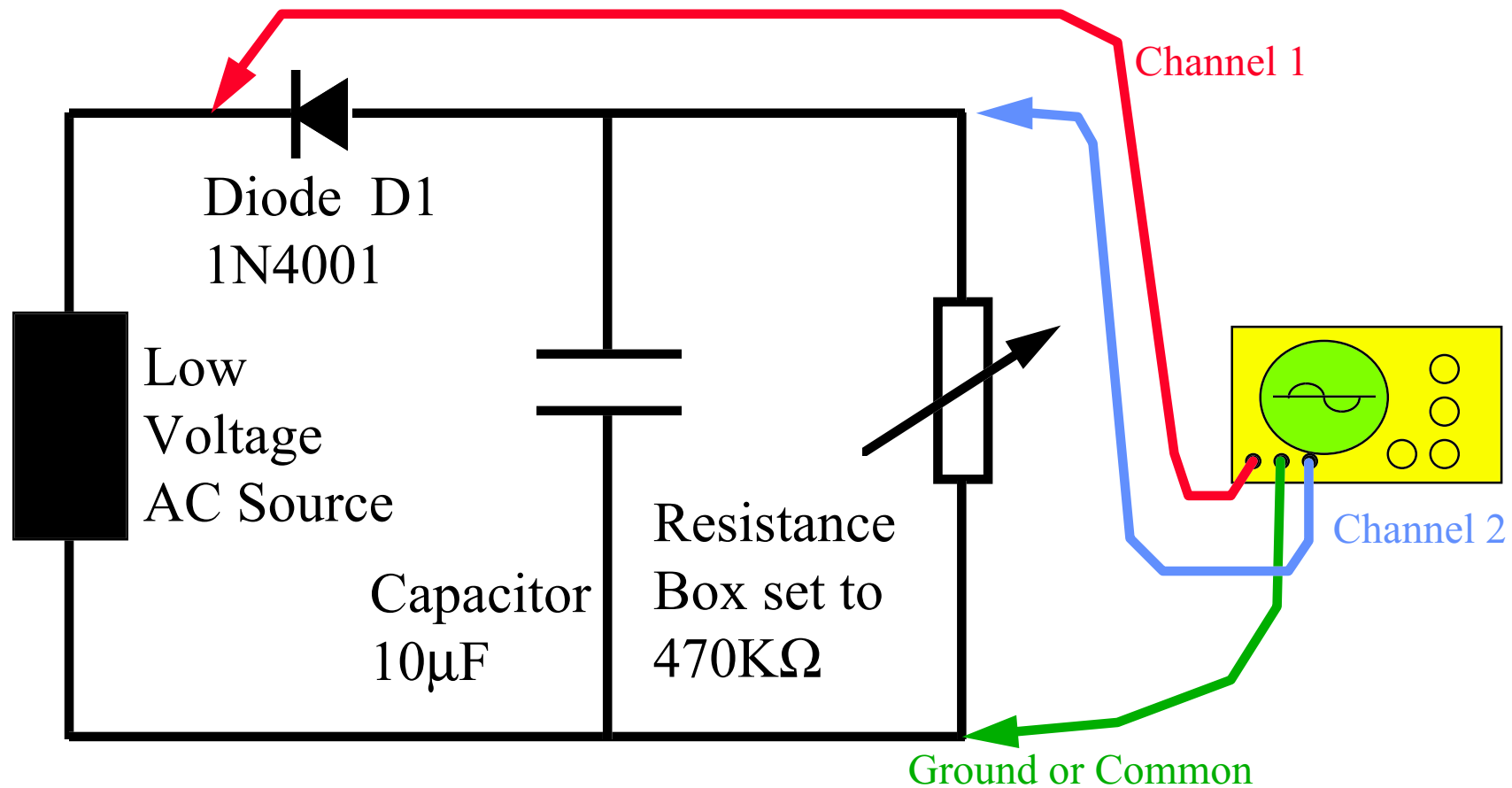

**Circuit 2**

# Power Units.

- Conclusion.
- When you reversed the Diode in Circuit 2 what happened to the output voltage ?
- What happened to the output voltage as the **Resistance box** value changed from  $470\text{K}\Omega$  down to ... $\text{K}\Omega$ ?
- What frequency was the ripple on the output voltage and what effect might this have on audio equipment ?


# Experiment 16.

# **Power Units.**

- Build “Circuit 1”.
- With initial setting sketch CRO display.
- Measure voltage across ZD1.
- Measure and calculate voltage across R1.
- Calculate current flowing through R1.

# Power Units.

Using a Transformer module to supply the Low Voltage AC Source build circuit shown below:-

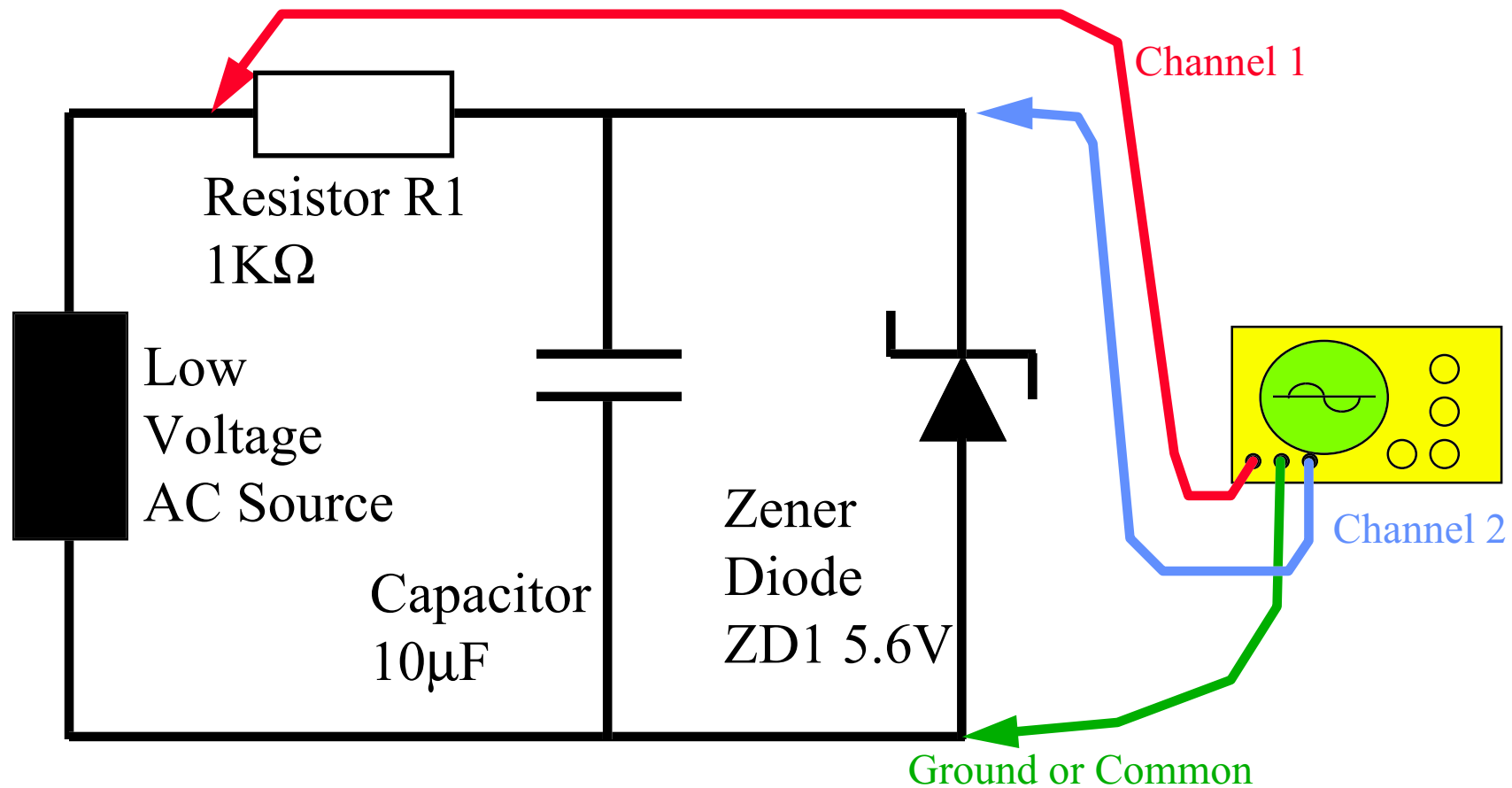


**Circuit 1**

# Power Units.

- Build “Circuit 2”.
- With initial setting sketch CRO display.
- Measure voltage across ZD1.
- Measure voltage across R1.
- Reduce value of the Resistance box to less than circa  $1000\Omega$  and record what happens to the output voltage.
- Conclusion: explain your observations.

# Power Units.

Using a Transformer module to supply the Low Voltage AC Source build circuit shown below:-

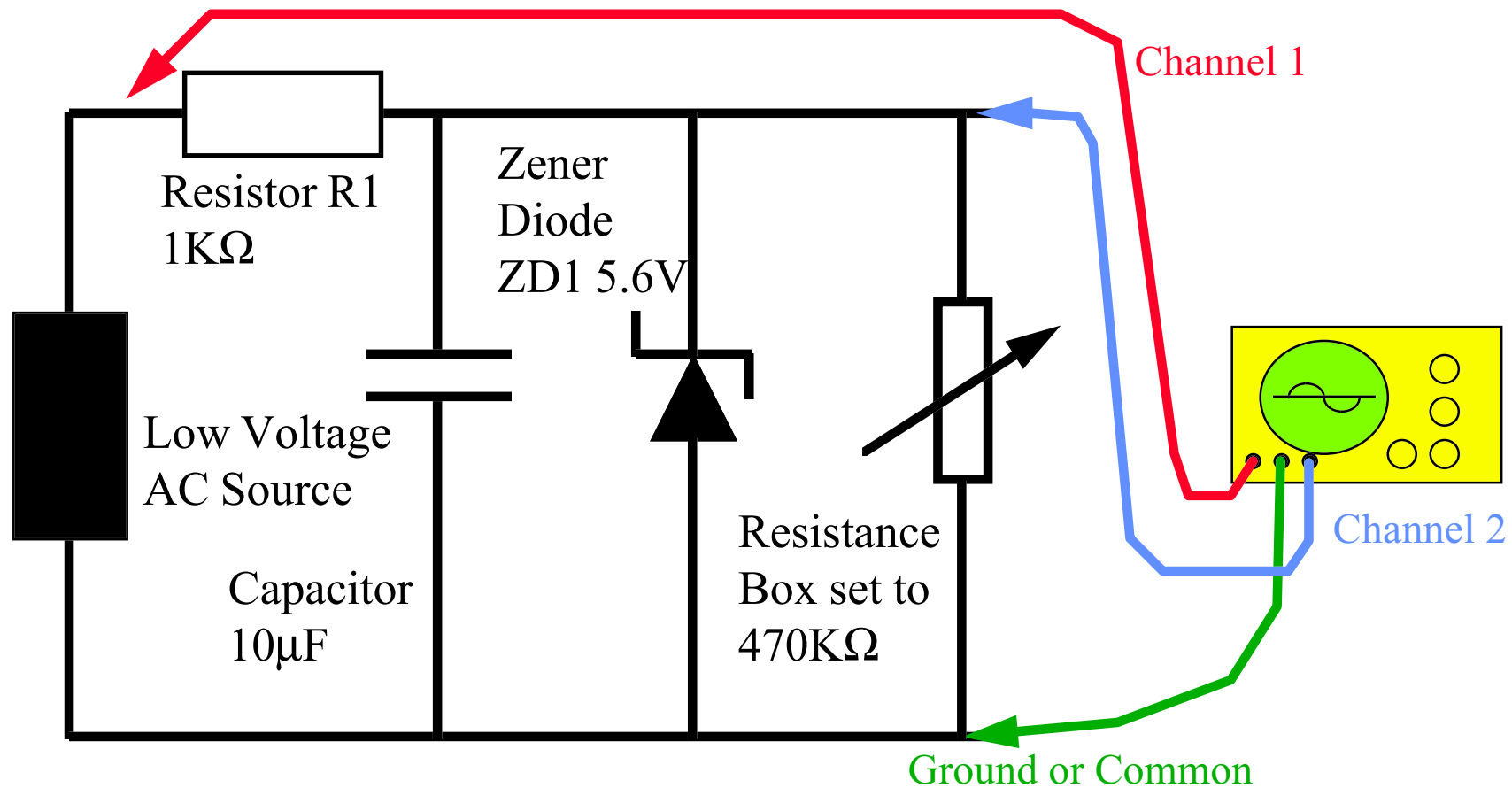

**Circuit 2**

# Experiment 17.




# Comparator.

Using the LM324

Pin 4 is +ve Supply

Pin 11 is -ve Supply

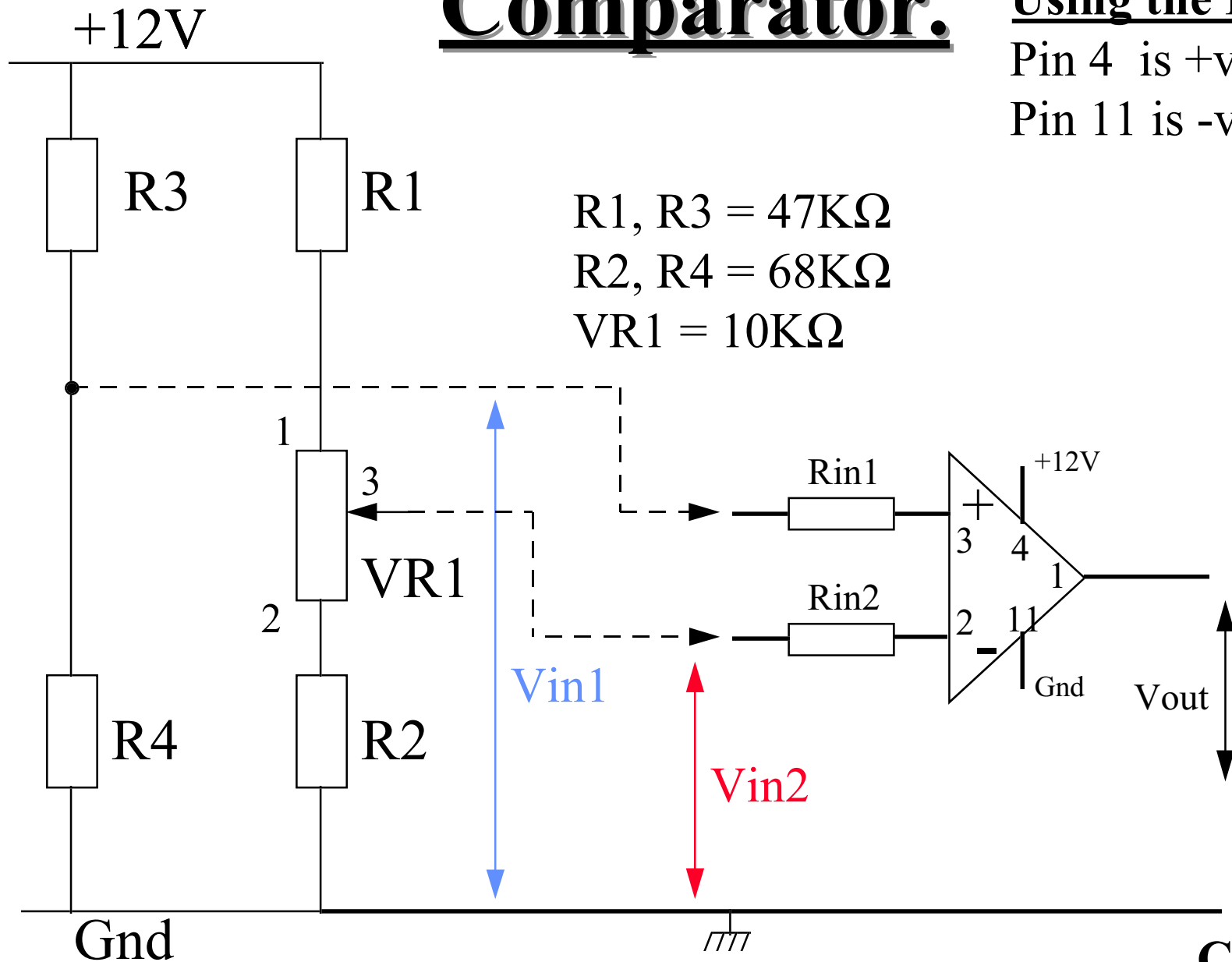


Circuit 1

# Comparator.

- DC **Test 1**      Build “Circuit 1”.
- Set  $R_{in1}$  and  $R_{in2} = 10K\Omega$
- Measure and record the voltage across R4.
- Measure and record the voltage across R3.
- Adjust VR1 in approximately  $30^\circ$  Steps covering the devices whole rotational range.
- Monitor and record voltages  $V_{in}$  and  $V_{out}$  for each adjustment of VR1.

# Comparator.

Set PSU  
voltage to 12V

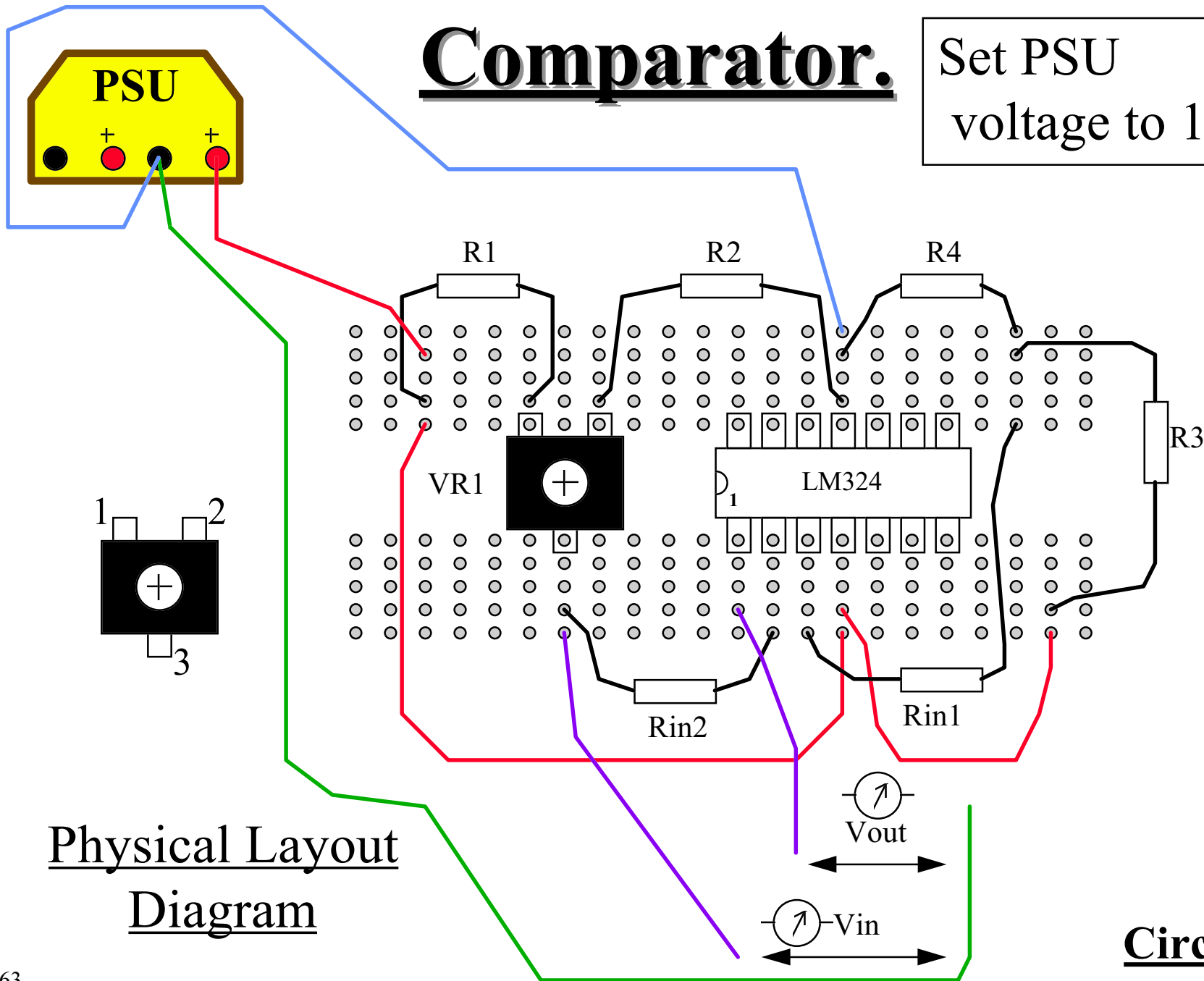

Physical Layout  
Diagram

Circuit 1

# Comparator.


- DC **Test 2**      Build “Circuit 2”.
- Set  $R_{in1}$  and  $R_{in2} = 10K\Omega$
- Measure and record the voltage across R4.
- Measure and record the voltage across R3.
- Adjust VR1 to the point where the LED changes from **OFF** to **ON** State.
- Monitor and record voltage  $V_{in}$  where the LED just switches **OFF**.
- Monitor and record voltage  $V_{in}$  where the LED just switches **ON**.

# Comparator.

Using the LM324

Pin 4 is +ve Supply

Pin 11 is -ve Supply

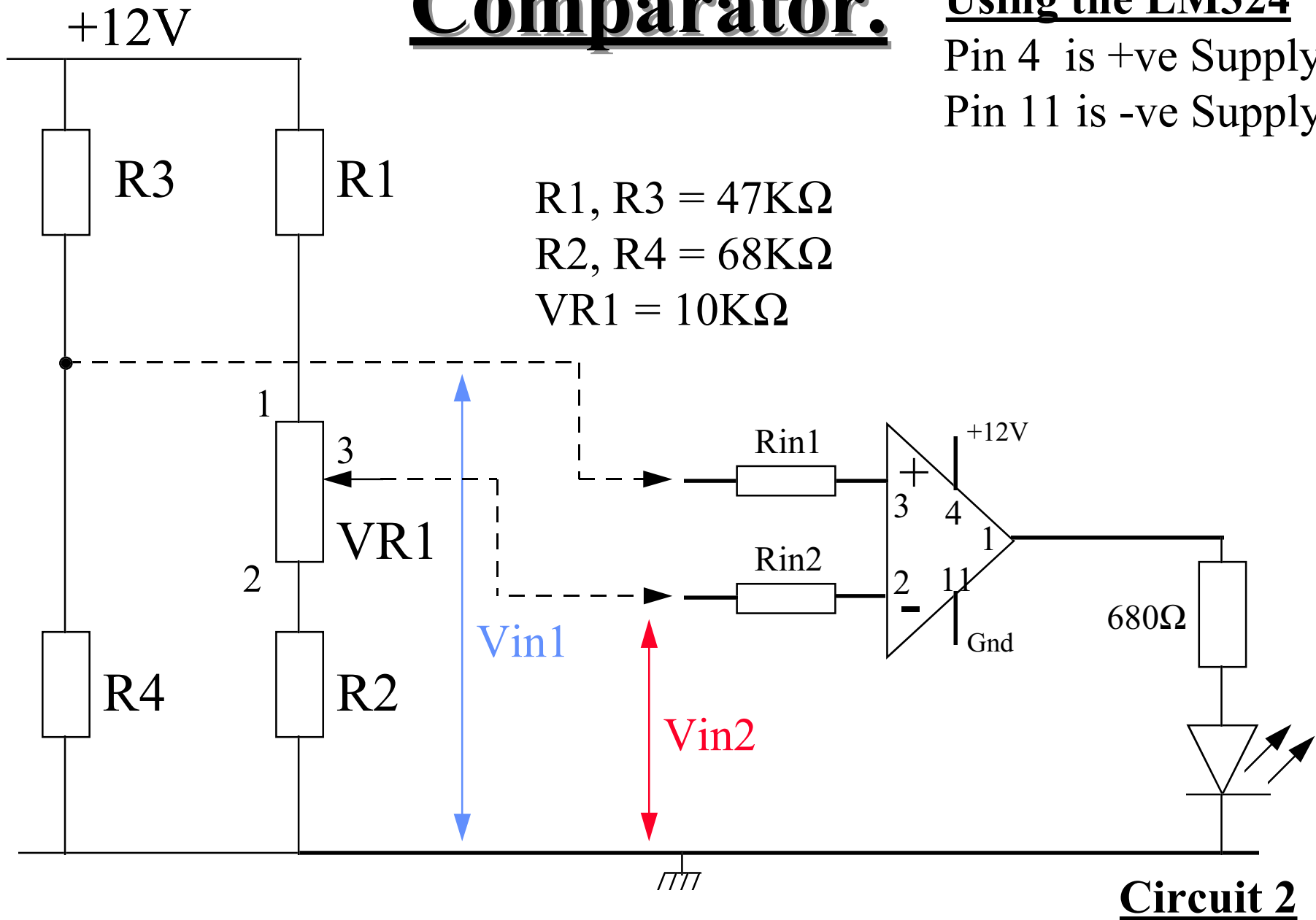

# Comparator.

- DC **Test 3** Using “Circuit 2”.
- Set R3 and R1 = 33K $\Omega$
- Measure and record the voltage across R4.
- Measure and record the voltage across R3.
- Adjust VR1 to the point where the LED changes from **OFF** to **ON** State.
- Monitor and record voltage  $V_{in}$  where the LED just switches **OFF**.
- Monitor and record voltage  $V_{in}$  where the LED just switches **ON**.


# Comparator.

- Conclusion
- Calculate the voltages across R3 and R4 when R3= 47K $\Omega$  and R4= 68K $\Omega$  .
- Calculate the voltages across R3 and R4 when R3= 33K $\Omega$  and R4= 68K $\Omega$  .
- Compare you calculated values with the measured values.

# Experiment 18.



# Voltage Dividers 2.

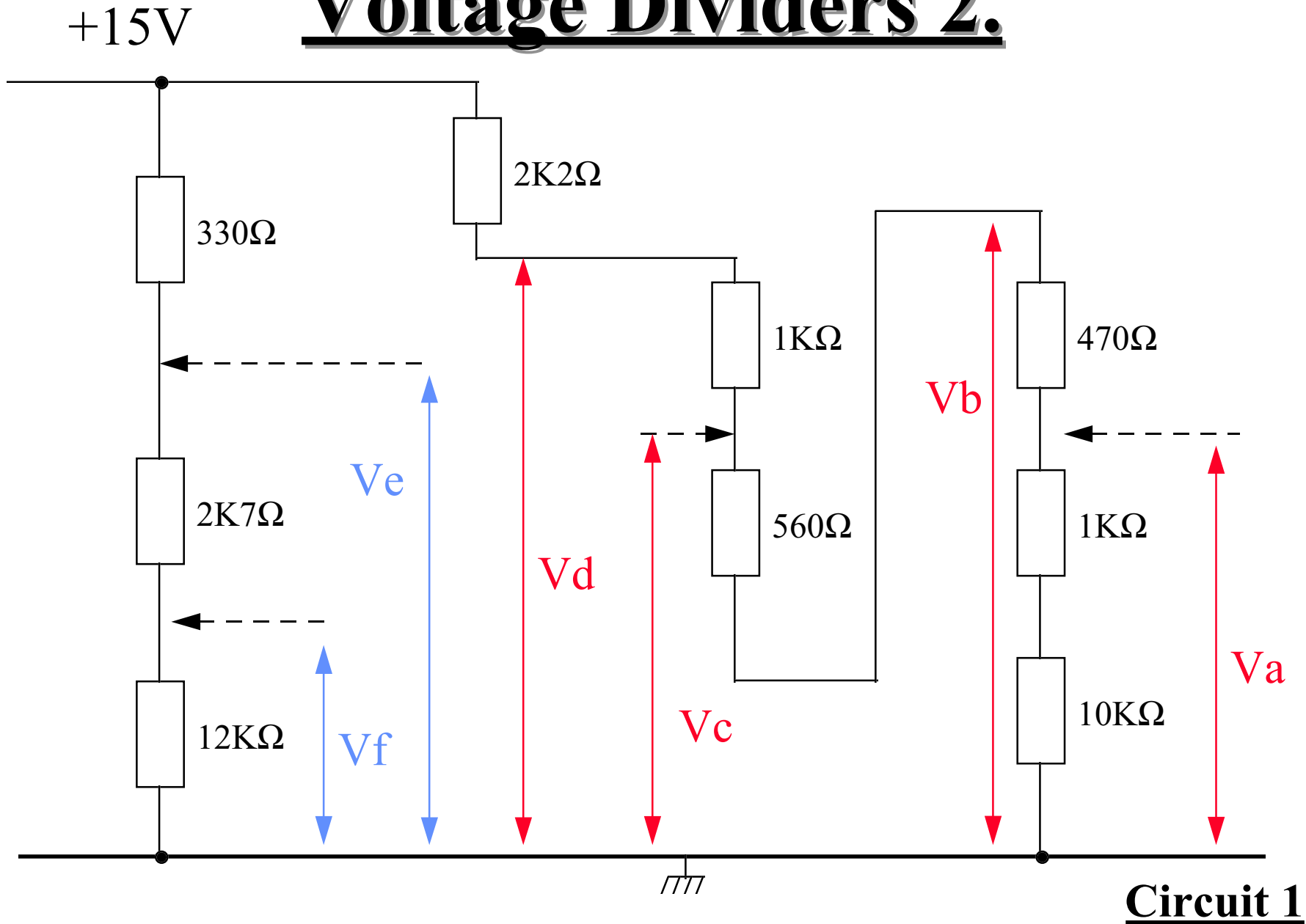

# Voltage Dividers 2.

- DC **Test 1**      Build “Circuit 1”.
- (1) Calculate expected voltages for  $V_a$  to  $V_f$ .
- (2) Measure and record all the marked voltage points  $V_a$  to  $V_f$ .
- (3) What is the voltage difference between the points  $V_f$  and  $V_c$ .
- Reduce the supply voltage to +5.6V
- Repeat activities (1),(2) and (3) above.
- Conclusion what happened to  $V_f$  and  $V_c$


# Experiment 19.

# Amplifier Gain Bandwidth Tests.

**Test Conditions** Set AC Input Signal Amplitude to 50mV P/P.

Set test frequencies at 100Hz, 1KHz, 10KHz, 30KHz and 100KHz.

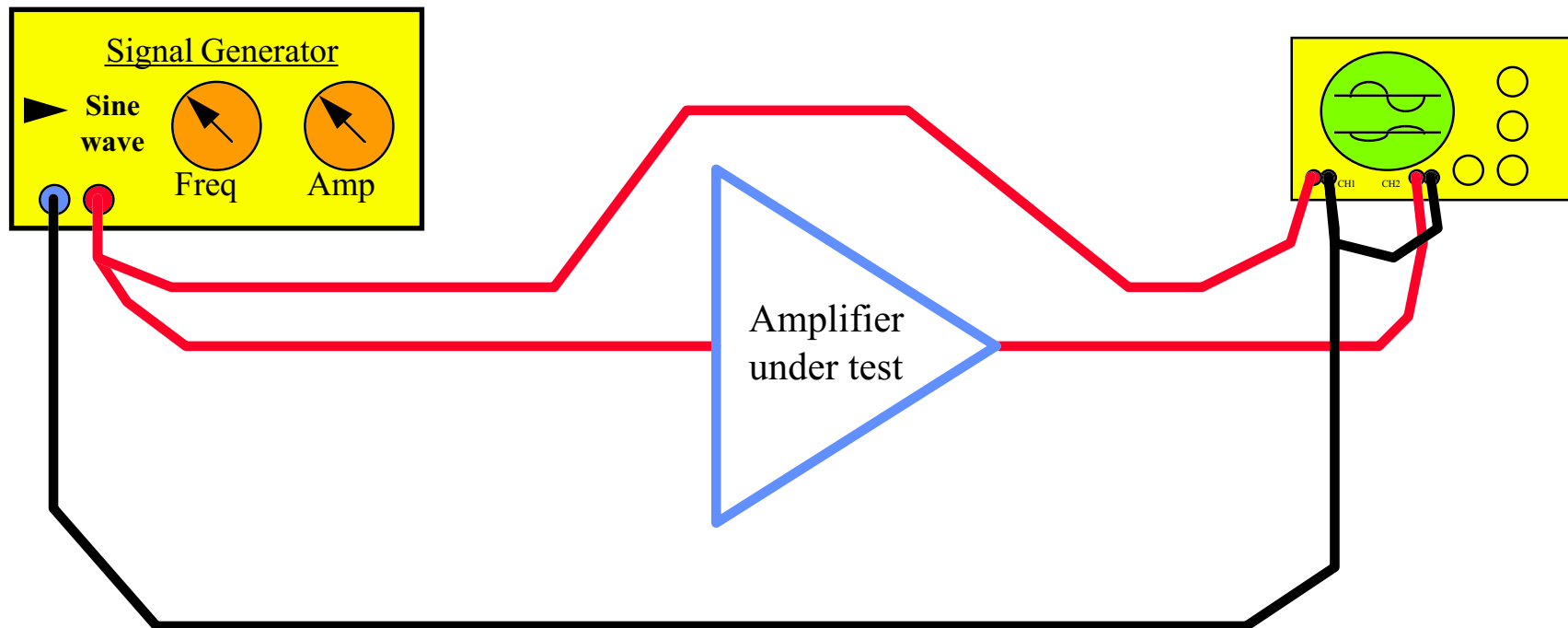Set Amplifier gain to (Times 10), (Times 100) and (Times 470).



# Amplifier Gain Bandwidth Tests.

## Control Conditions


AC Input Signal Amplitude 50mV Peak to Peak.

Set  $R_{in}$  to  $1K\Omega$  and therefore  $R_f = 10K\Omega$ ,  $100K\Omega$  and  $470K\Omega$

Input Frequency in Hz	Output Voltage Volts P/P Gain = *10	Output Voltage Volts P/P Gain = *100	Output Voltage Volts P/P Gain = *470
100 Hz	? mV P/P	? mV P/P	? V P/P
1000 Hz	? mV P/P	? mV P/P	? V P/P
10000 Hz	? mV P/P	? mV P/P	? V P/P
30000 Hz	? mV P/P	? mV P/P	? V P/P
100000 Hz	? mV P/P	? mV P/P	? mV P/P

# Amplifier Gain Bandwidth Tests.

## Typical Graph

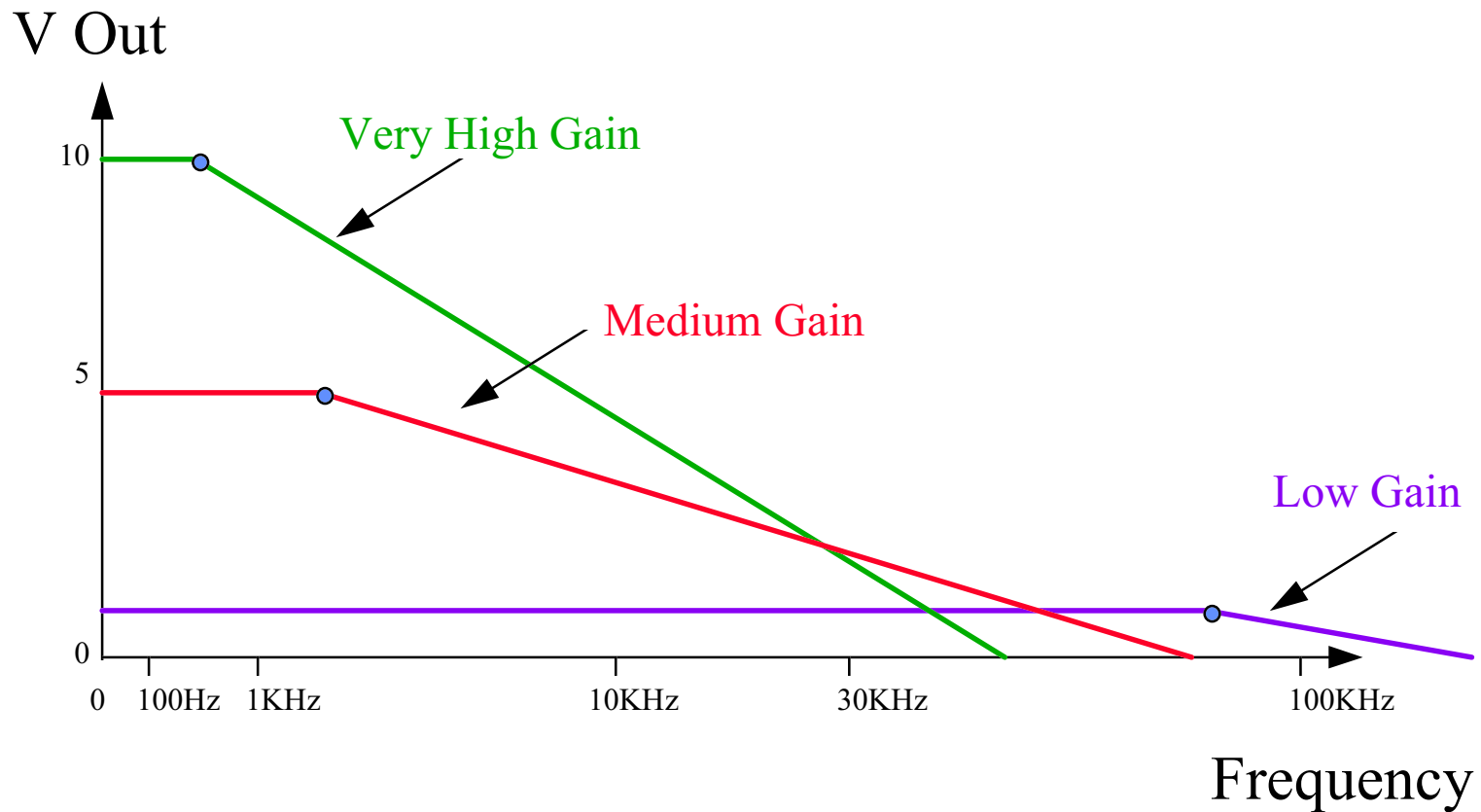


# Experiment 20.

# Using the Oscilloscope.

Using the Scope Signal Simulator connected as below:-

Use scope worksheet to record and analyse waveforms.

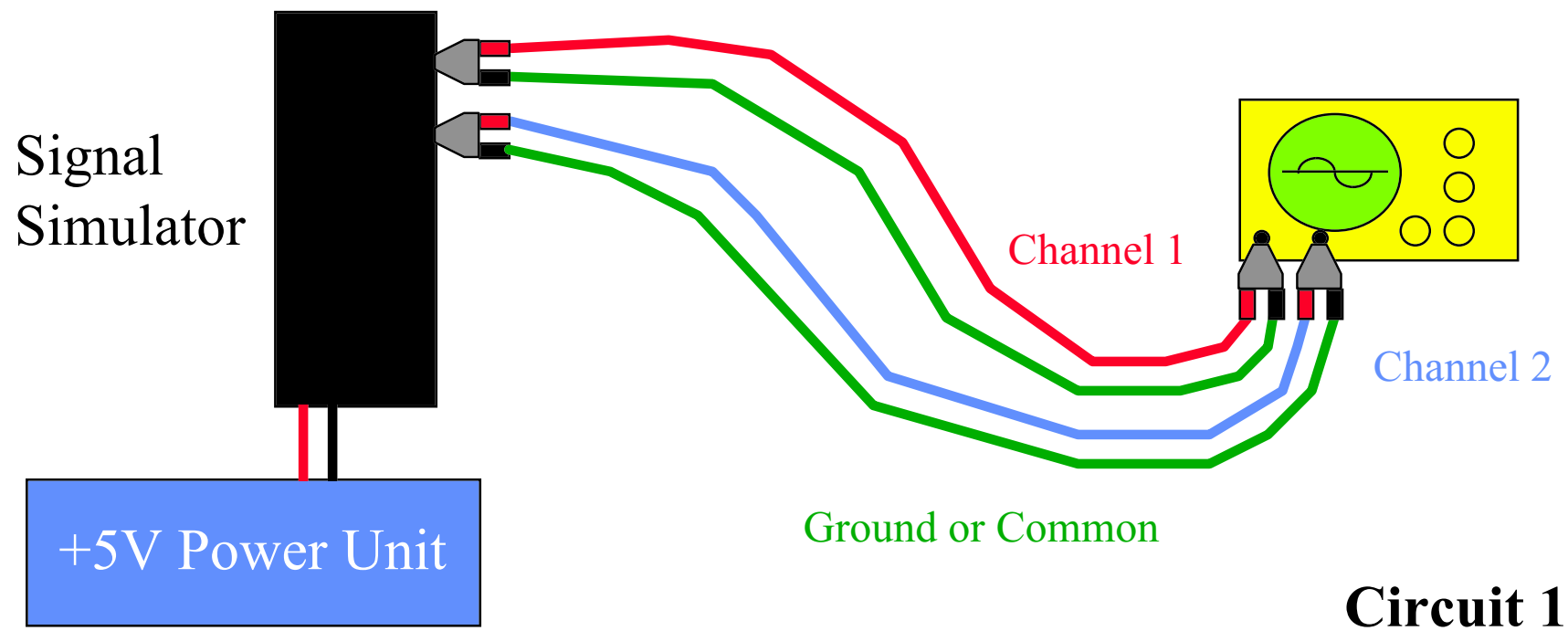**Note:** Record status of Switch settings on simulator so you can repeat experiment if required






# Experiment 21.


# Transformers.

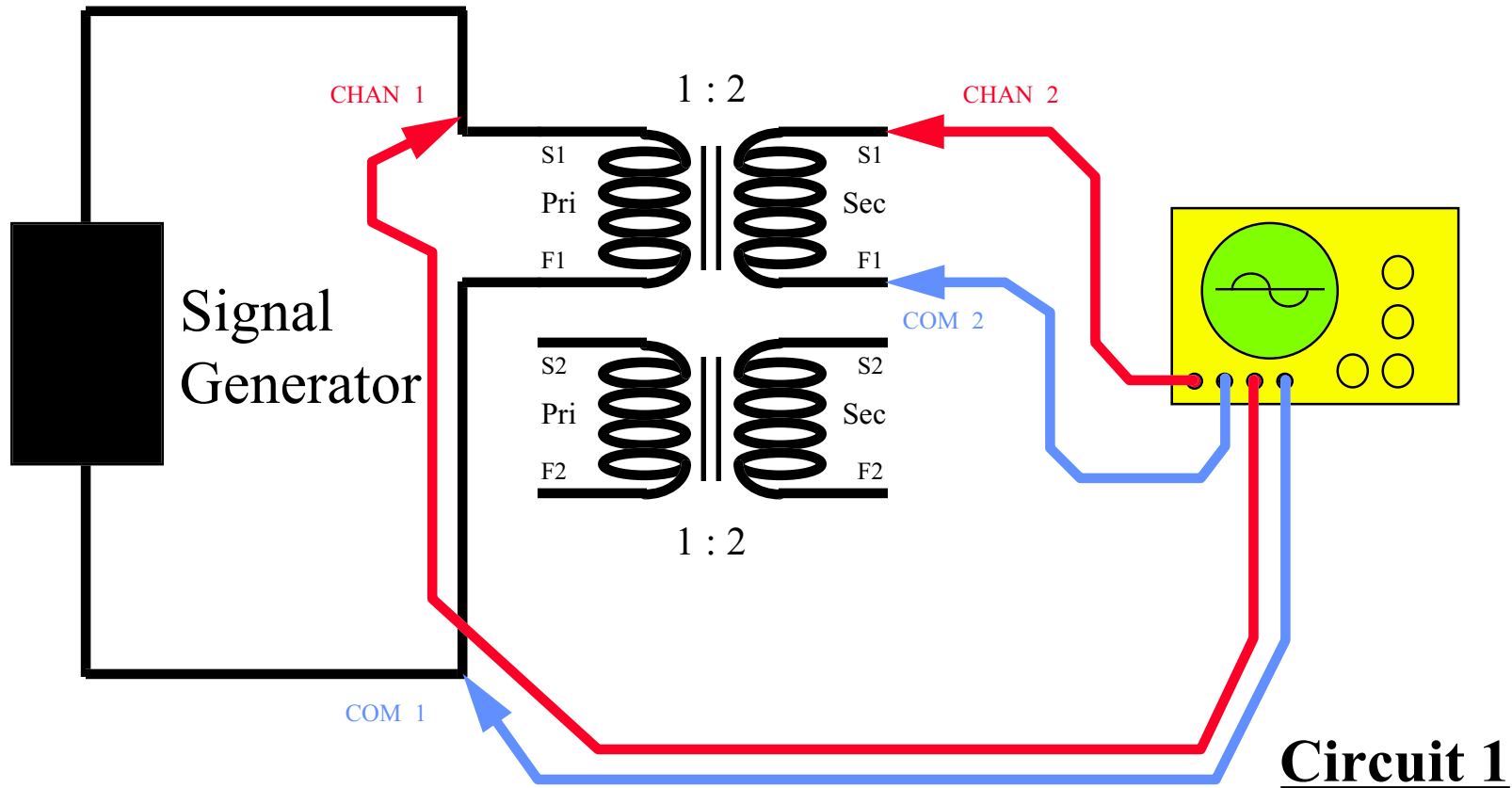1. Set Signal generator to a Sine wave at a frequency of 1KHz and an amplitude of 2 Volts peak to peak.
2. Calculate and Measure and sketch Secondary Voltage.




# Transformers.

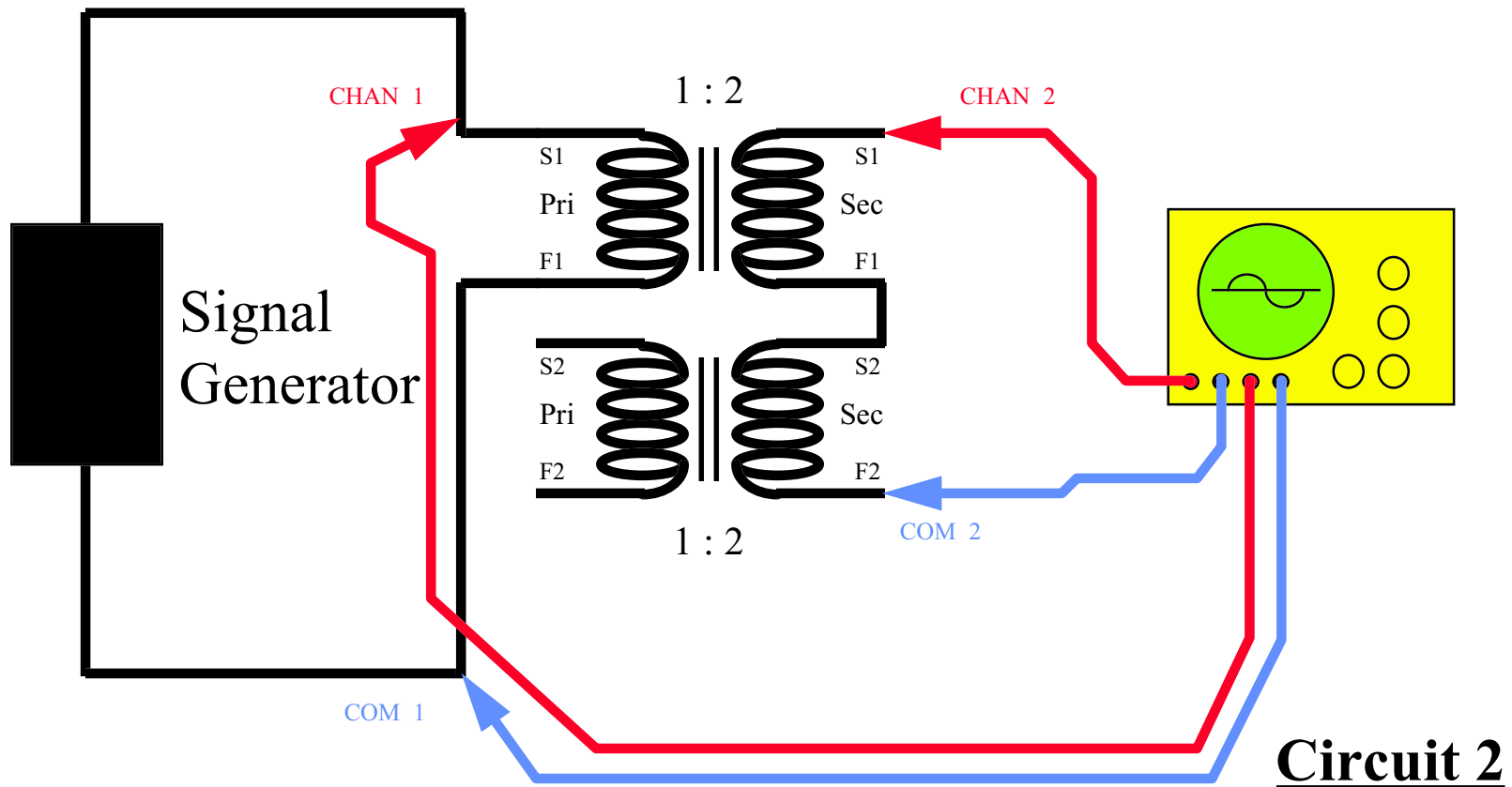1. Set Signal generator to a Sine wave at a frequency of 1KHz and an amplitude of 2 Volts peak to peak.
2. Calculate and Measure and sketch Secondary Voltage.




# Transformers.

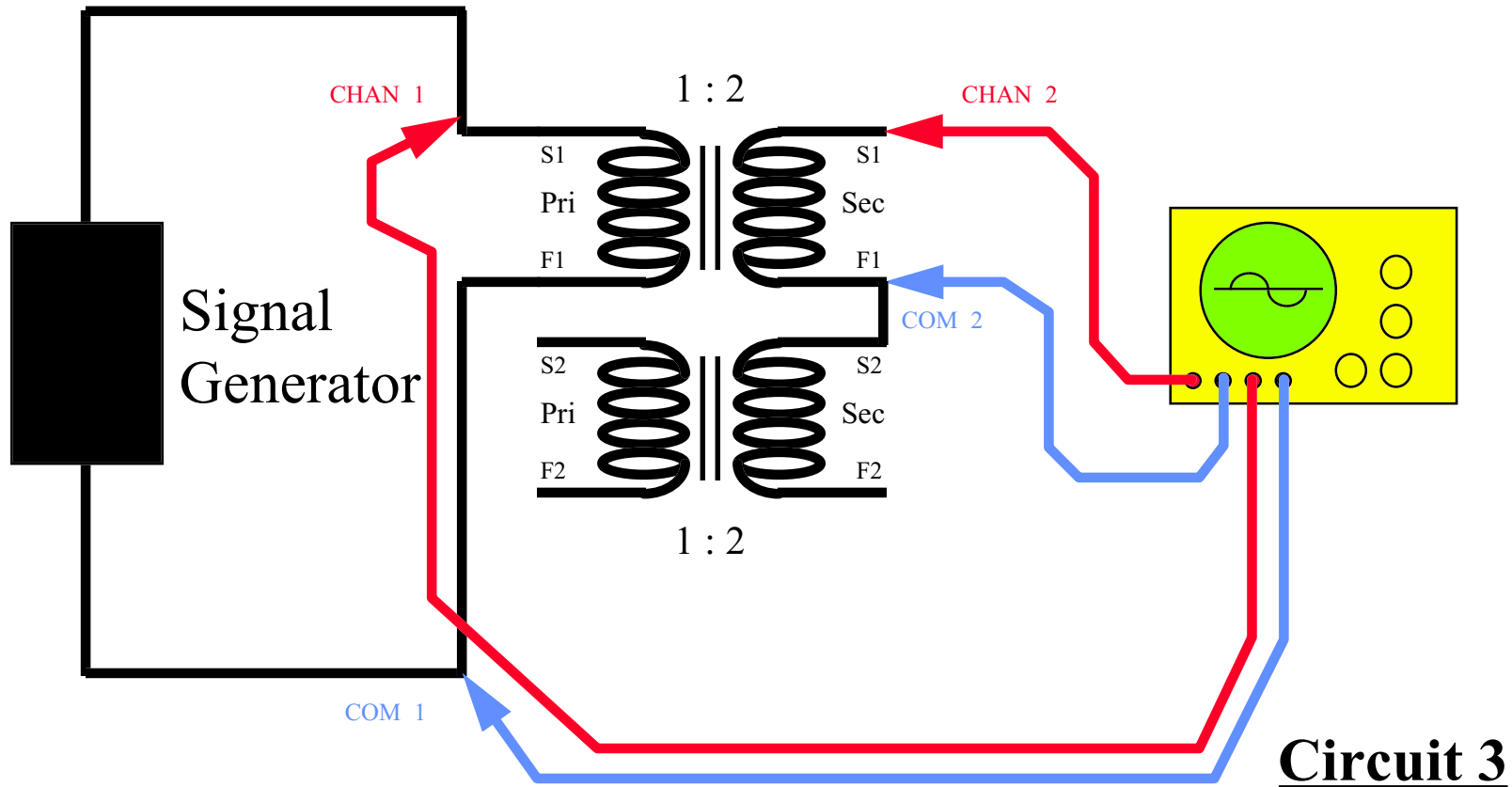1. Set Signal generator to a Sine wave at a frequency of 1KHz and an amplitude of 2 Volts peak to peak.
2. Calculate and Measure and sketch Secondary Voltage.




# Transformers.

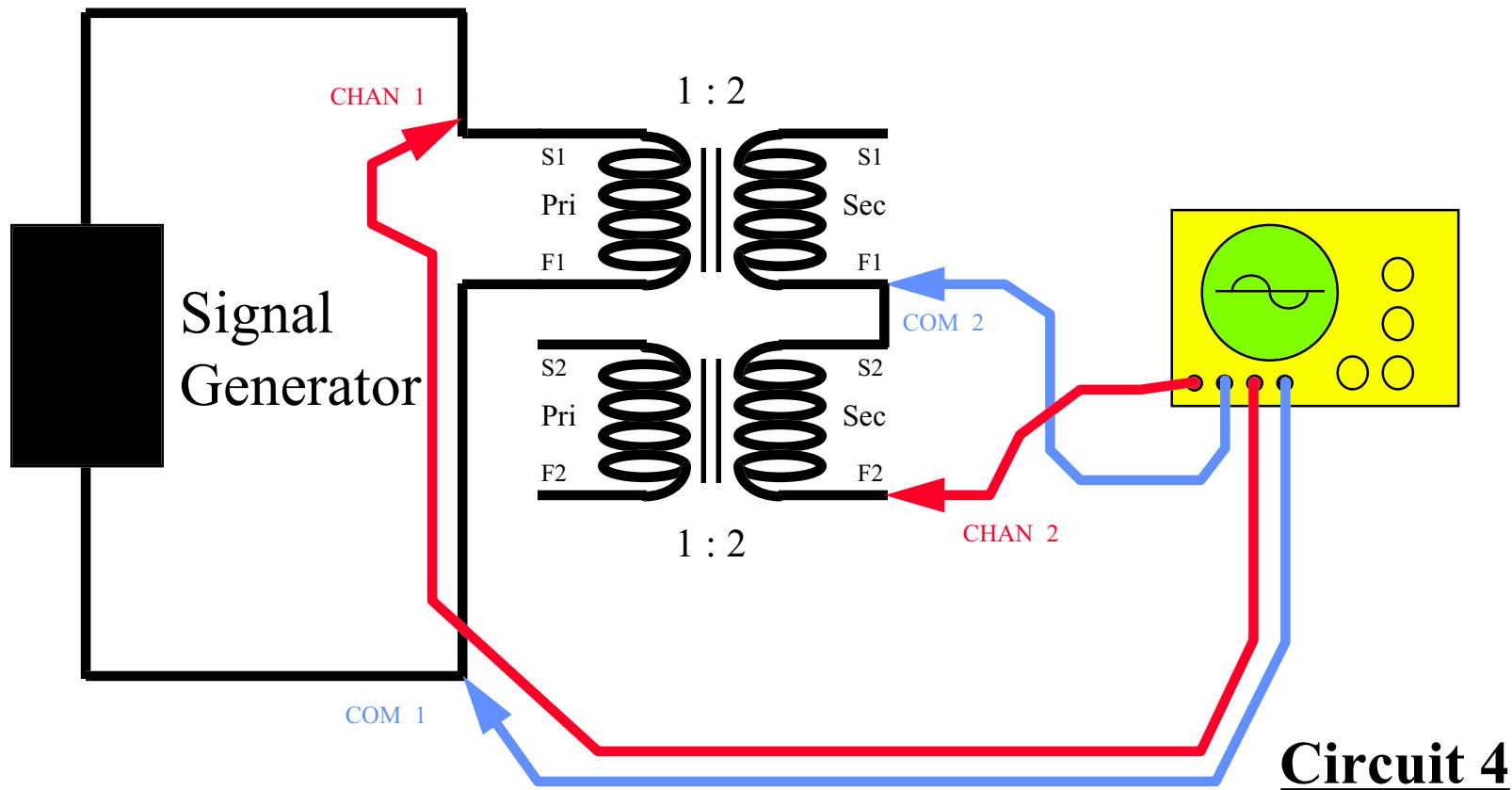1. Set Signal generator to a Sine wave at a frequency of 1KHz and an amplitude of 2 Volts peak to peak.
2. Calculate and Measure and sketch Secondary Voltage.




# Transformers.

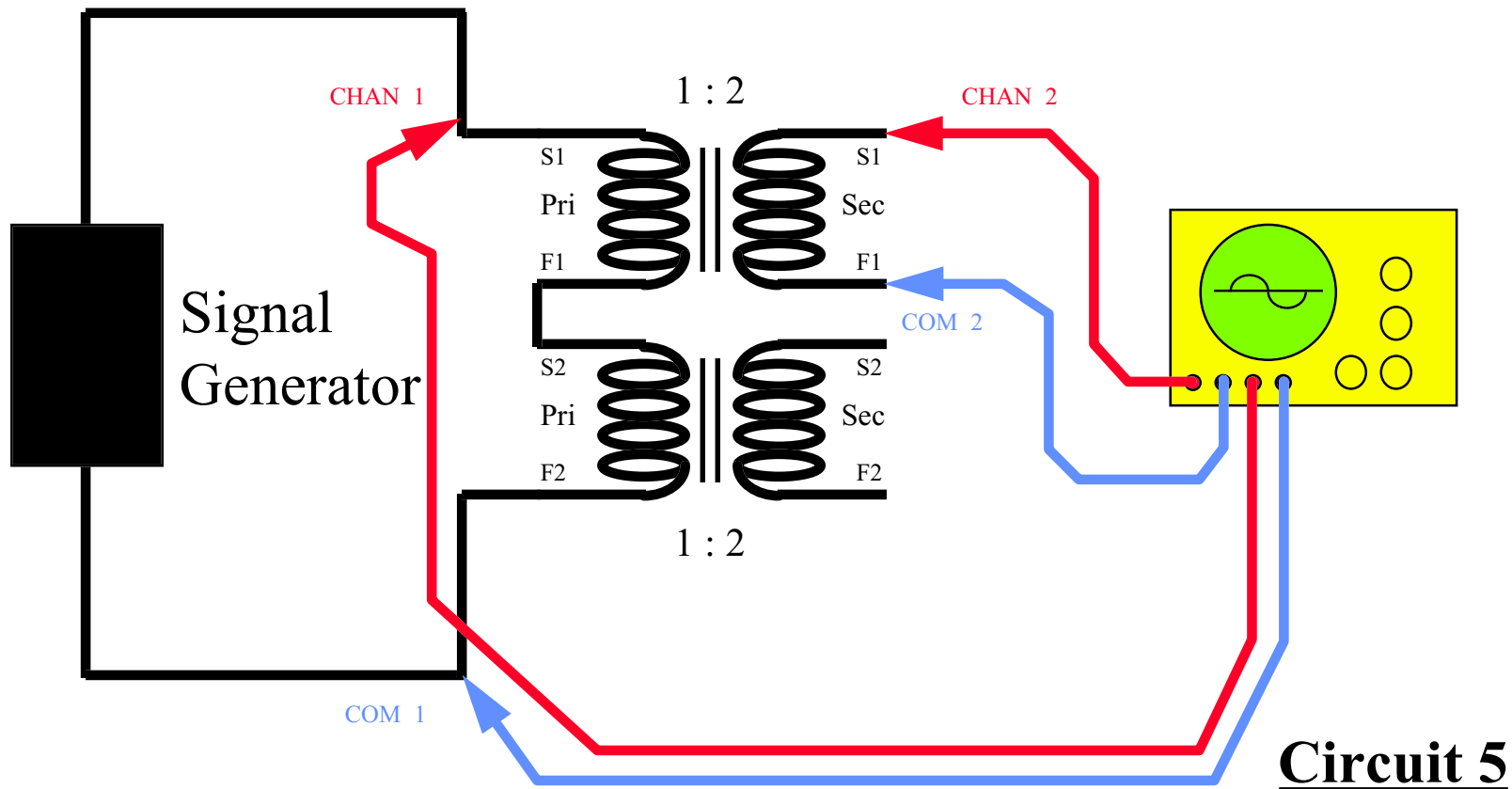1. Set Signal generator to a Sine wave at a frequency of 1KHz and an amplitude of 2 Volts peak to peak.
2. Calculate and Measure and sketch Secondary Voltage.



# Transformers.

1. Set Signal generator to a Sine wave at a frequency of 1KHz and an amplitude of 2 Volts peak to peak.
2. Calculate and Measure and sketch Secondary Voltage.

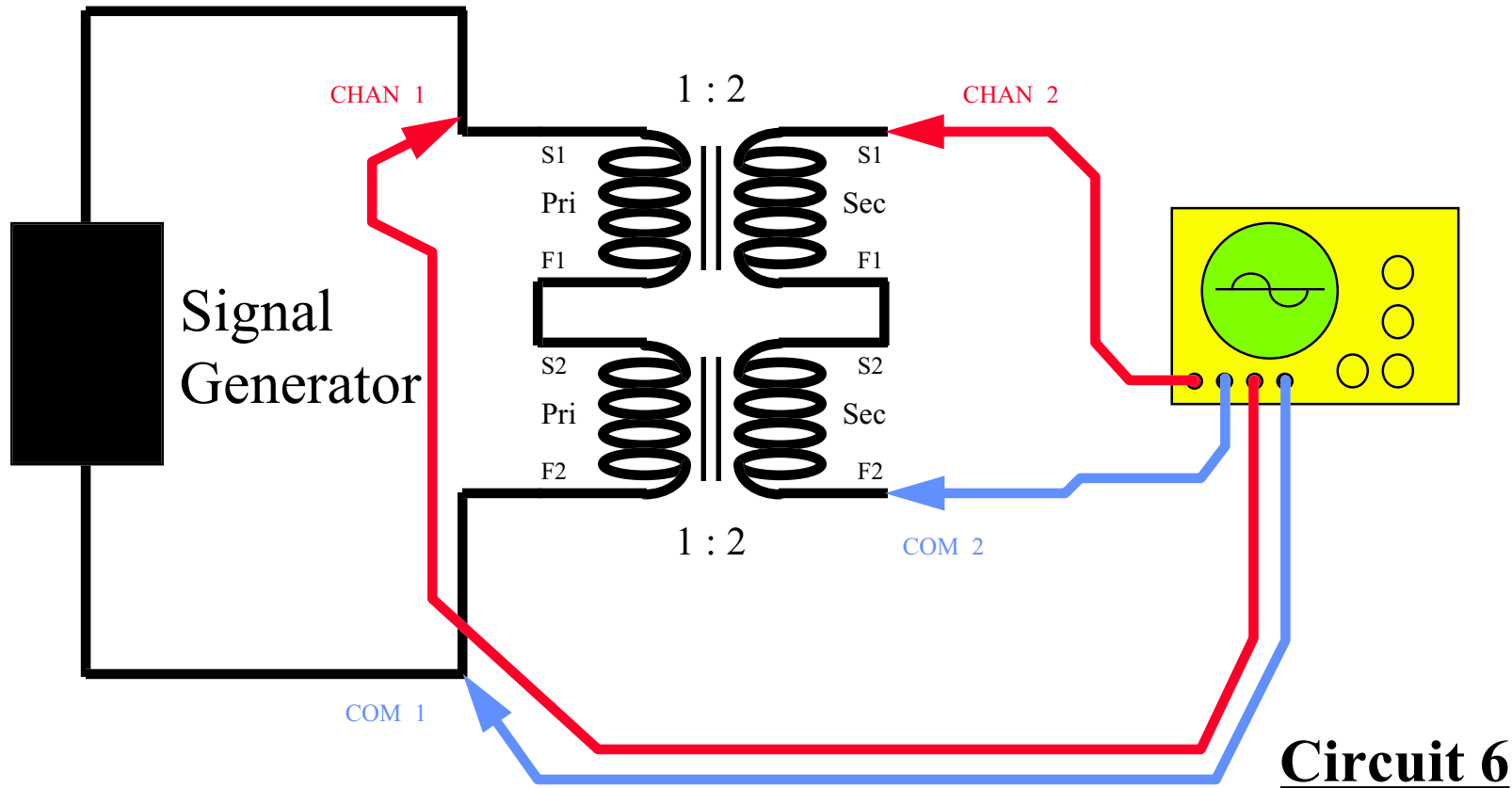

**Circuit 6**

# Experiment 22.




# Plot Diode Characteristics.

- Use the process described in the following slides to plot the characteristics of the diodes identified below :-
  - a Germanium Diode.
  - a Silicon Diode.
  - a Zener Diode.
  - a Red Light Emitting Diode (LED).
  - a Yellow Light Emitting Diode (LED).
  - a Green Light Emitting Diode (LED).

# Plot Diode Characteristics.

Prepare your graph paper as shown :-

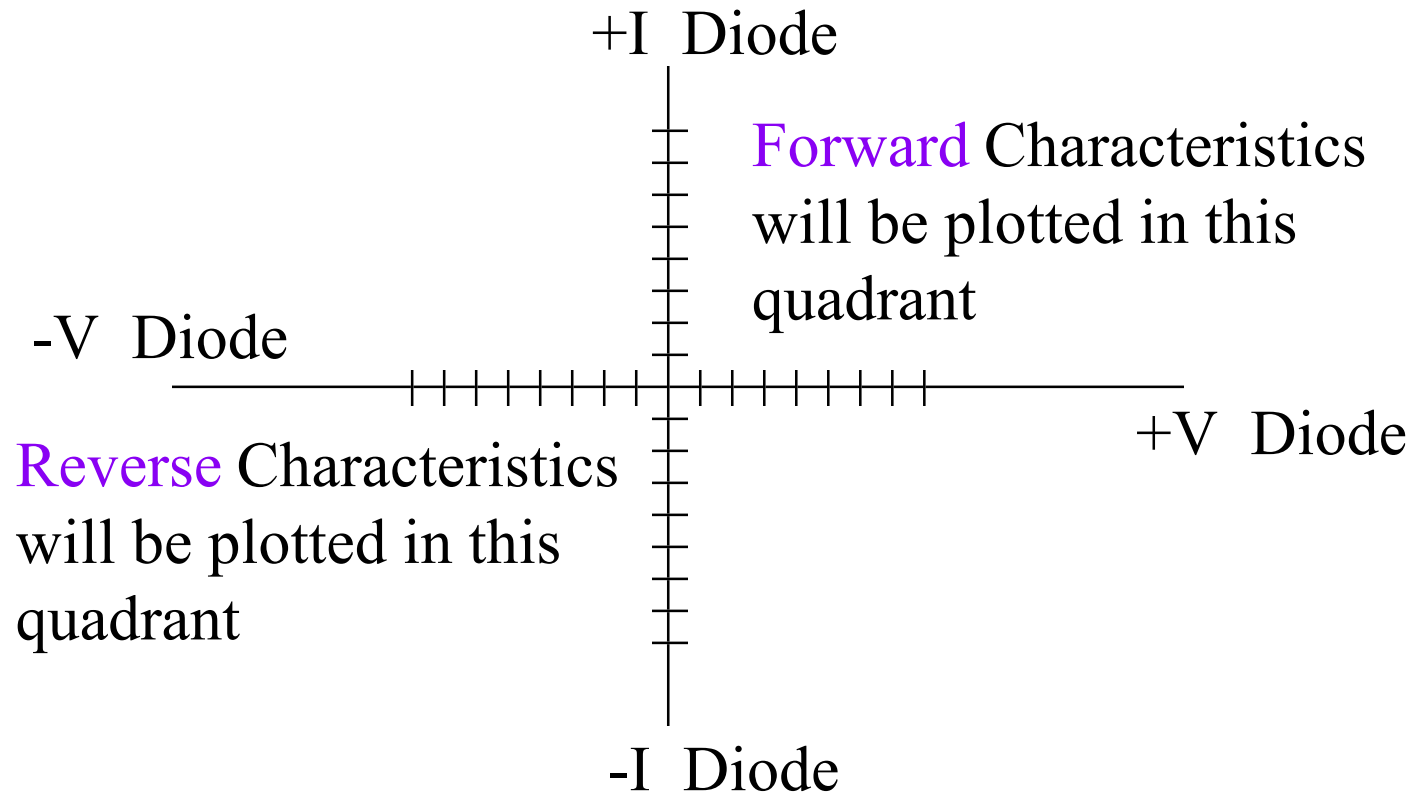


**Remember** to mark all scales and units on your graph.

# Plot Diode Characteristics.

- To calculate Diode Current :-
- Calculate voltage across RLoad
- $V_{RLoad} = V_{Supply} \text{ DVM,S} - V_{Diode} \text{ DVM,D.}$
- Calculate current flowing through RLoad which is also the current flowing through the Diode.
- $I_{RLoad} = V_{RLoad} / 10K\Omega$
- Diode Current =  $I_{RLoad}$

# Plot Diode Characteristics.

Using a Variable Voltage DC Source build circuit shown below:-

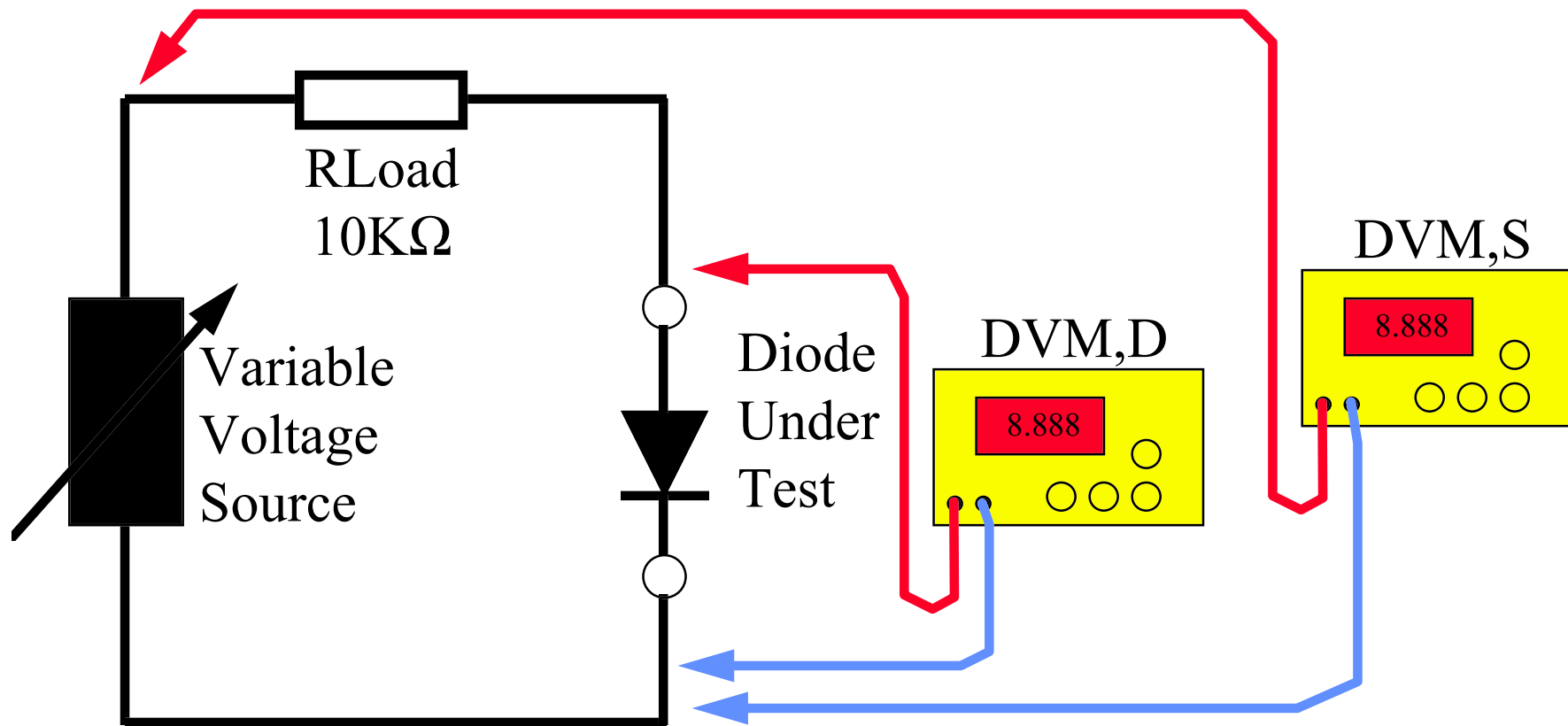


**Circuit 1**

# Plot Diode Characteristics.

- Forward Characteristics Build “Circuit 1”.
- Adjust the variable voltage supply in small increments as indicated of record sheet.
- Measure and record the **+Diode** voltage **DVM,D** and its associated **+Supply** voltage **DVM,S** after each adjustment .
- Using the above results calculate the **+Diode current** that flows in the circuit.
- Plot **+Diode current** (Y Axis) against **+Diode** voltage (X axis) on Circuit 1 graph.

# Plot Diode Characteristics.

Using a Variable Voltage DC Source build circuit shown below:-

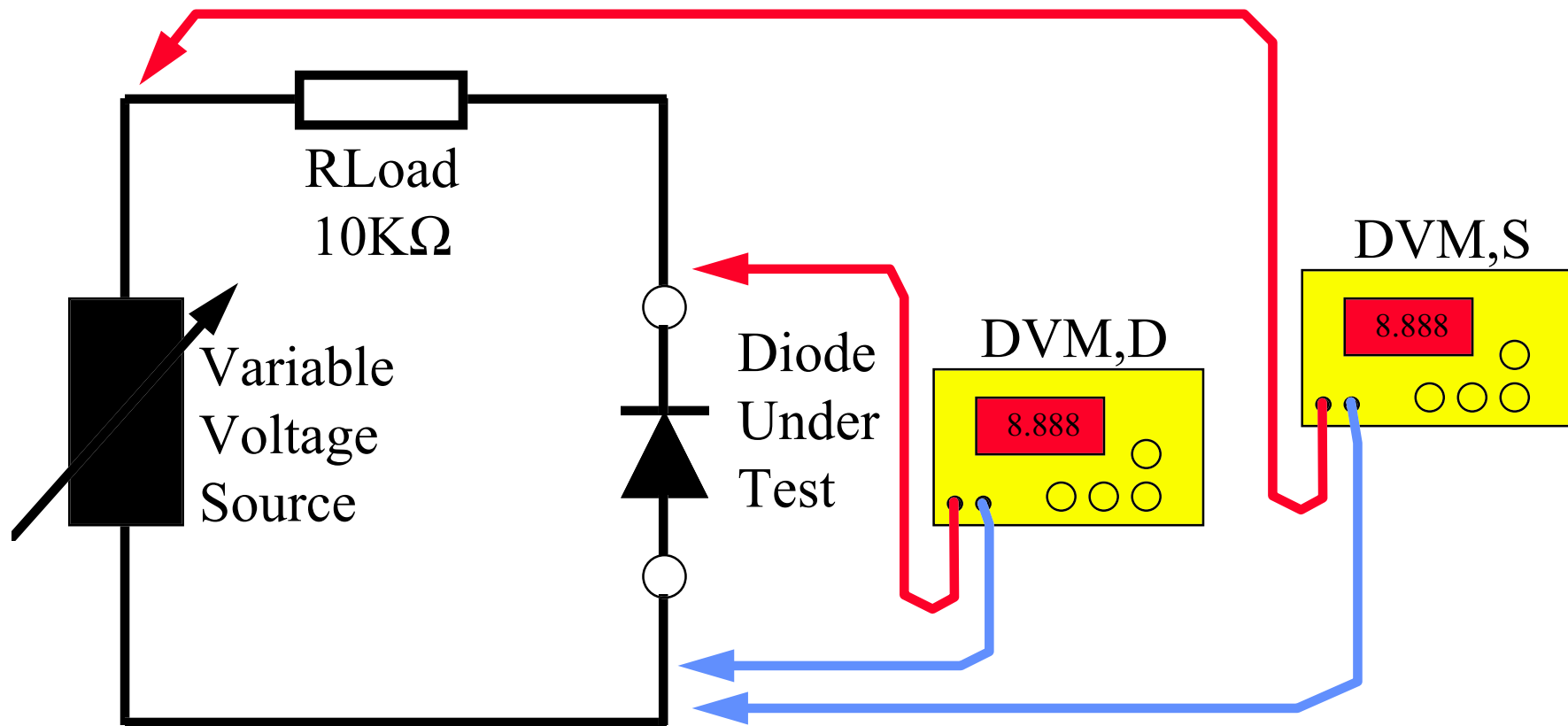

**Circuit 1**

# Plot Diode Characteristics.


- Reverse Characteristics Build “Circuit 2”.
- Adjust the variable voltage supply in small increments as indicated of record sheet.
- Measure and record the -Diode voltage  $V_{M,D}$  and its associated -Supply voltage  $V_{M,S}$  after each adjustment .
- Using the above results calculate the -Diode current that flows in the circuit.
- Plot -Diode current (Y Axis) against -Diode voltage (X axis) on Circuit 1 graph.

# Experiment 23.



# Thyristors - SCRs.

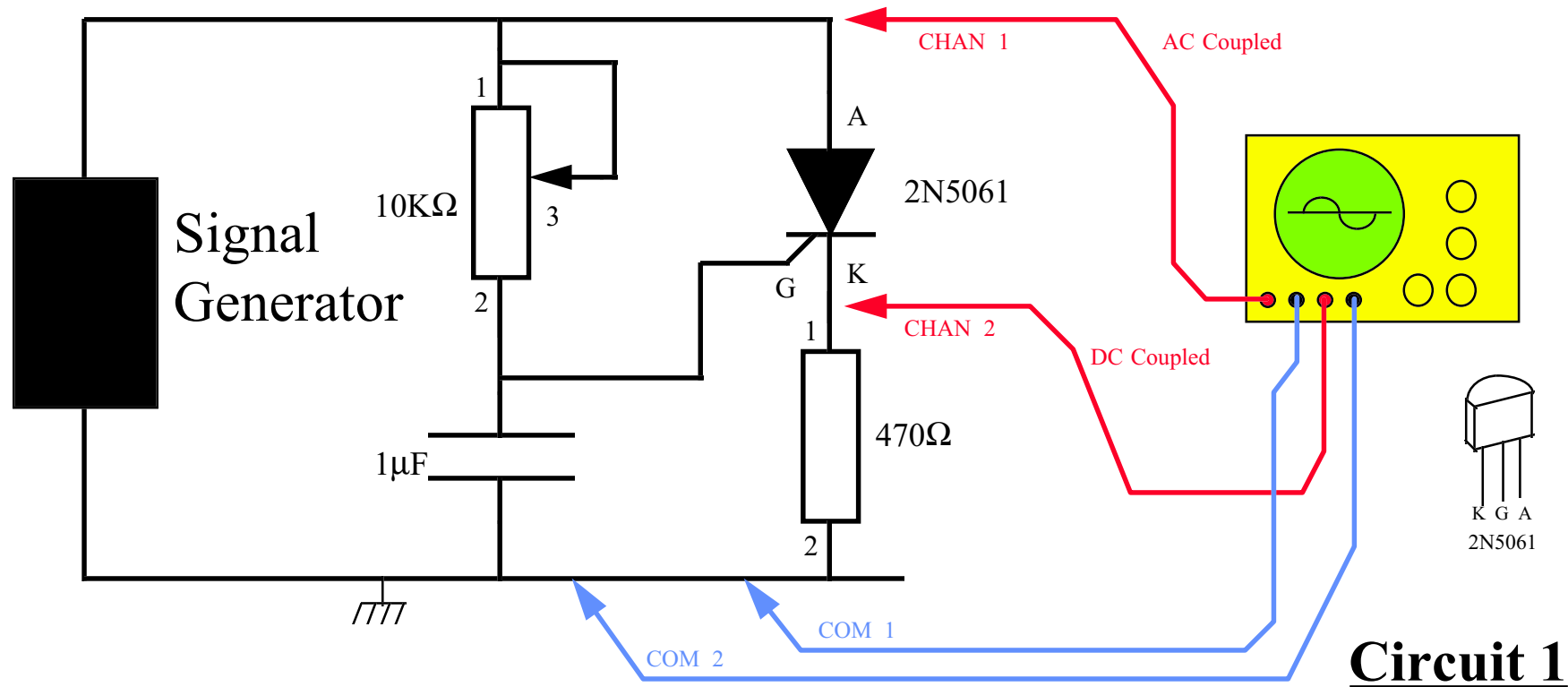1. Build Circuit 1 shown below.
2. Set Signal generator to a Sine wave at a frequency of 200Hz and an amplitude of 10 Volts peak to peak.
3. Adjust VR1 to give firing angles  $0^\circ$ ,  $90^\circ$  and  $180^\circ$  sketching Input and Output Waveforms and Annotate points of interest .



**End Slide**

# Revision Page

**Title**

Laboratory Experiments

**Author**

R. J. Spriggs

**Last Update**

11/March/2007

**Version**

2.30

**Edit**

0209

