

ELECTRONICS

Amplifiers


Amplifiers.

- What is covered ?
 - Some basic concepts.
- What is an Amplifier ?
- What do we mean by Gain ?
 - A , AOL and ACL.
- Effects of Input and Output Impedance.
- Gain/Bandwidth product.

Amplifiers.

Let us consider a Plant System

We start with the Seed

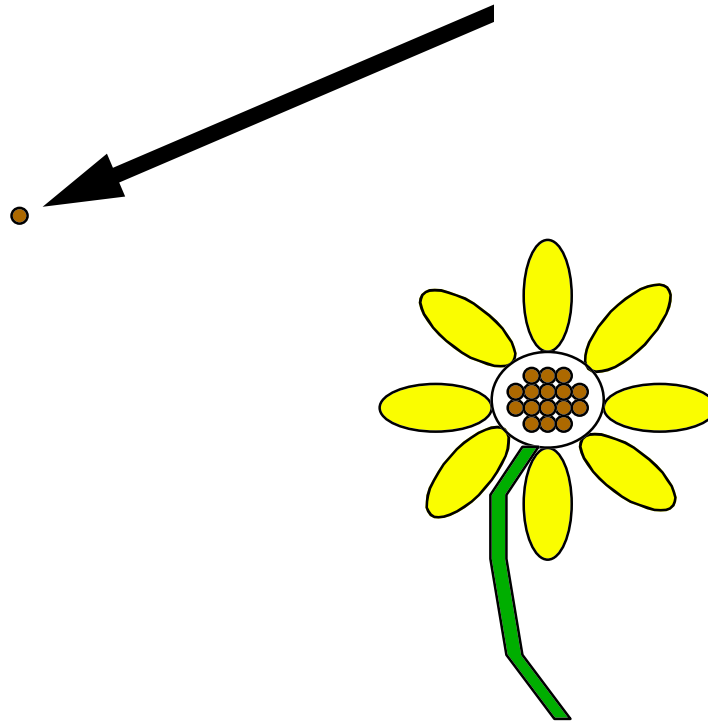


Amplifiers.

Let us consider a Plant System

We start with the Seed

Add Soil, Sunlight and
Water.

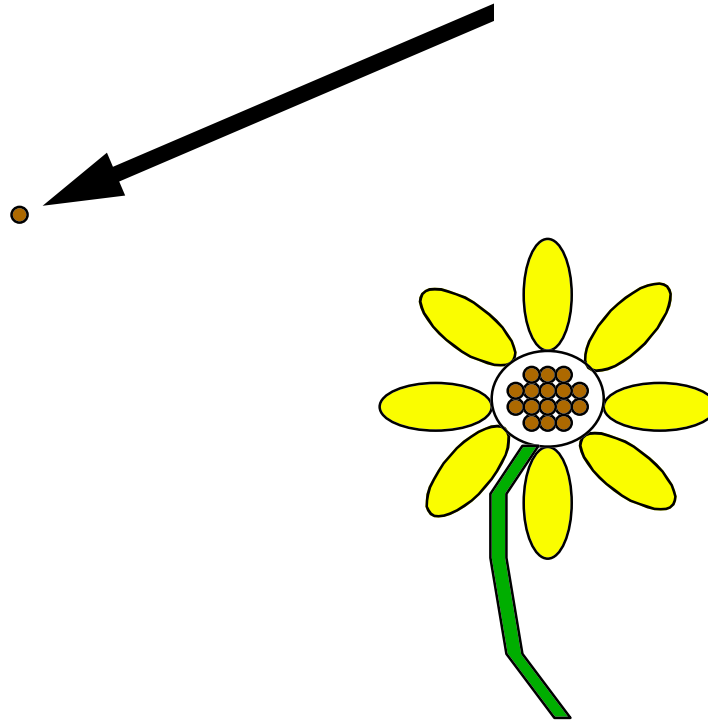


Amplifiers.

Let us consider a Plant System

We start with the Seed

Add Soil, Sunlight and
Water.


The Plant Grows.

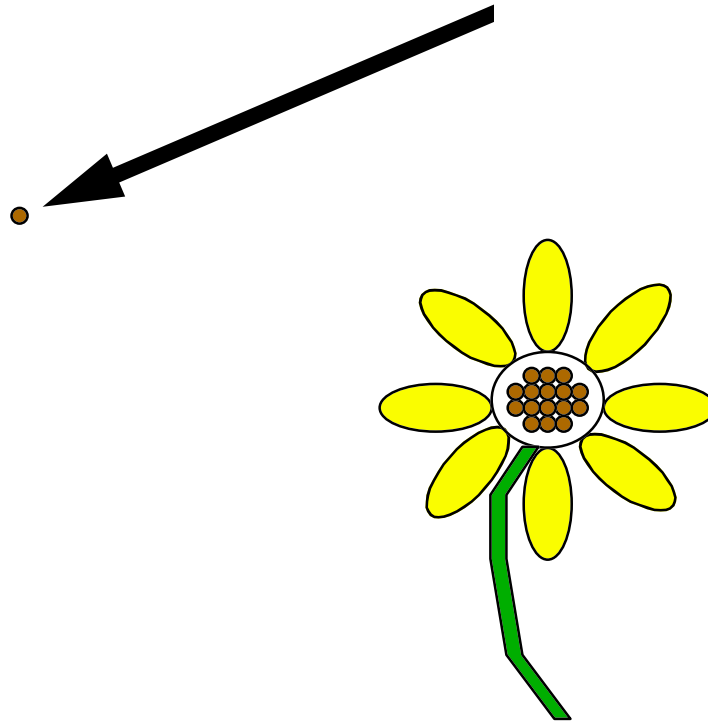

Amplifiers.


Let us consider a Plant System

We start with the Seed

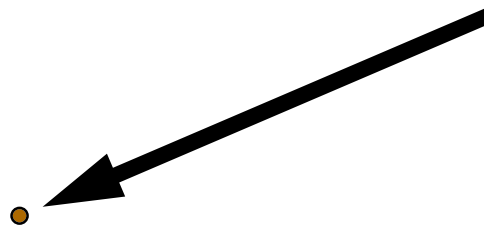

Add Soil, Sunlight and Water.

The Plant Grows.

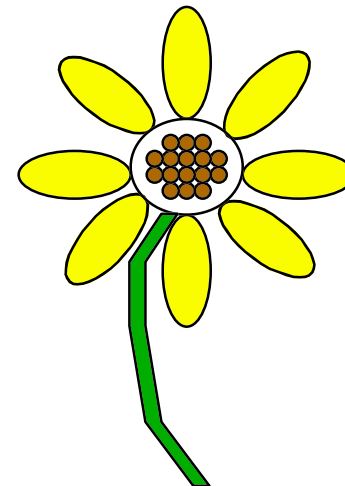

We end up with more Seeds.



Amplifiers.

- What have we seen ?
- Overall we have increased the number of seeds (**GAIN**). { $A = \text{Output} / \text{Input}$ }
- The plant needs **power**. (Sunlight, Water etc.)
- A time delay occurs from (seeds in) to (seeds out). (**Propagation delay**)
- We usually tend to ignore any side effects, waste products etc.

Amplifiers.

- How can we control the **GAIN** of our plant system ?
- Rather than plant all the seeds we just plant one or just some of them.
- This control when implemented in electronics is referred to as **FEEDBACK** because we feed back some of the output to the input of the system.

Amplifiers.


- With no control applied to the amplifier, then its natural **GAIN** is known as **(AOL)** the **OPEN LOOP GAIN** of the amplifier.
- With a controlled system where we ensure that the system has a specific gain less than the **(AOL)** then we say we have introduced **NEGATIVE FEEDBACK**.
- The letter “**A**” is used to define the gain of an amplifier. **(ACL)** closed loop gain i.e. gain with feedback.

Amplifiers.

Amplifier Configuration.

Single Ended

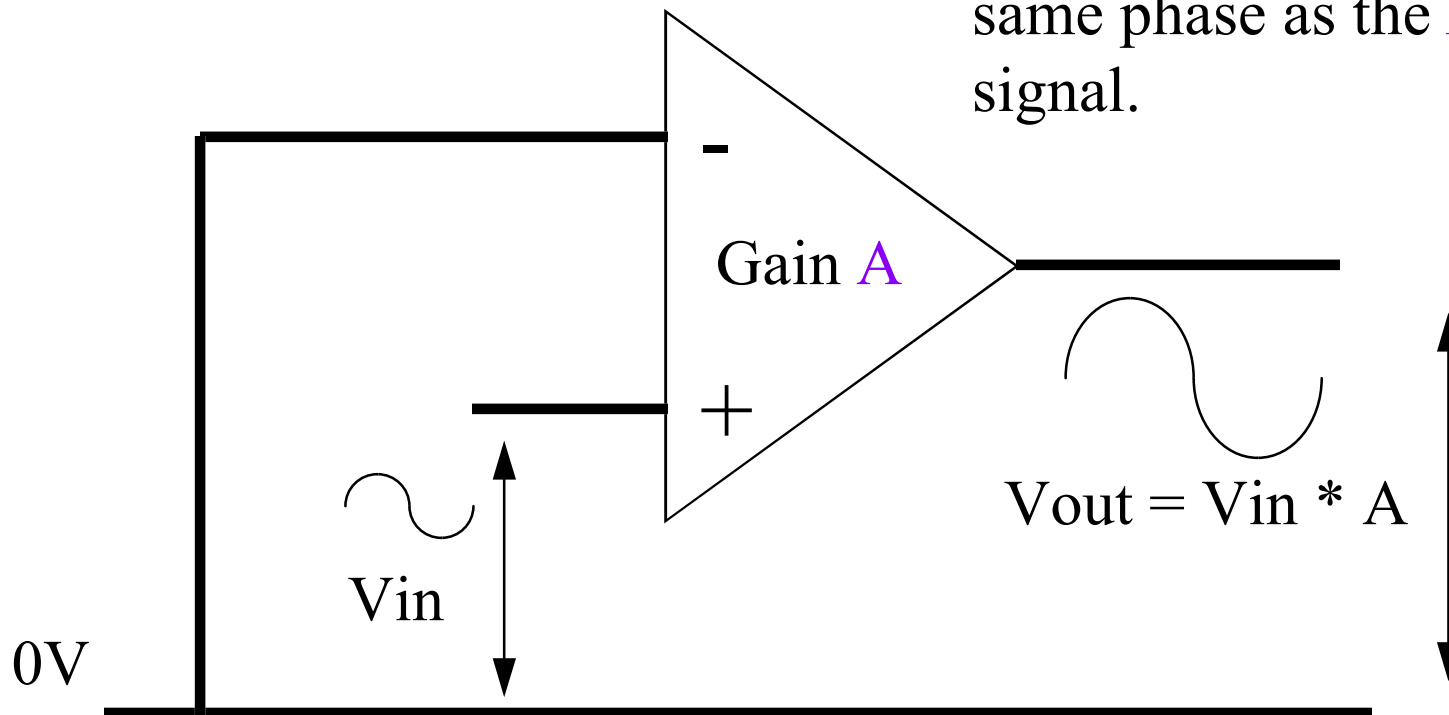When a signal is applied to the Non Inverting input then the **Output** is the same phase as the **Input** signal.




Amplifiers.

Amplifier Configuration.

Single Ended

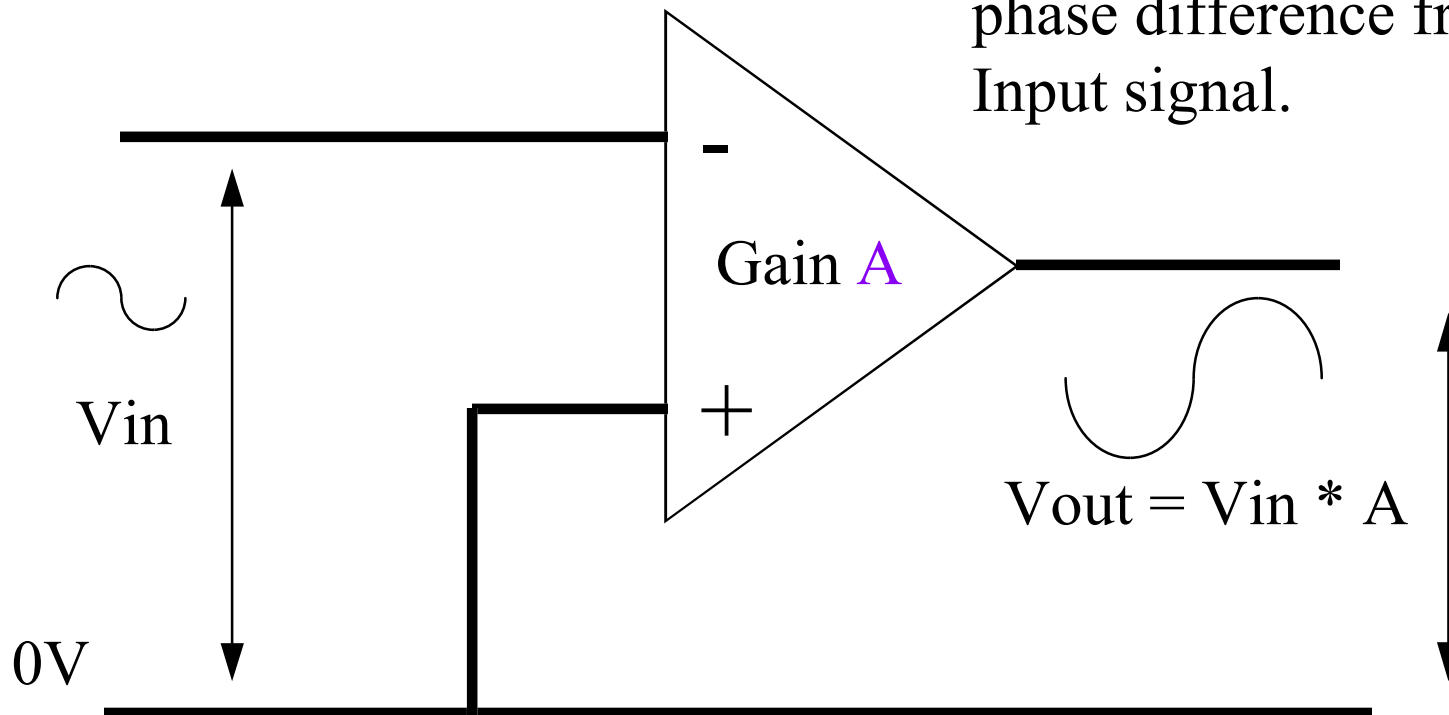When a signal is applied to the Inverting **Input** then the **Output** has a 180° phase difference from the Input signal.




Amplifiers.

Amplifier Configuration.

Differential

The Amplifier in
Differential mode.

Note the polarity of the
input signal

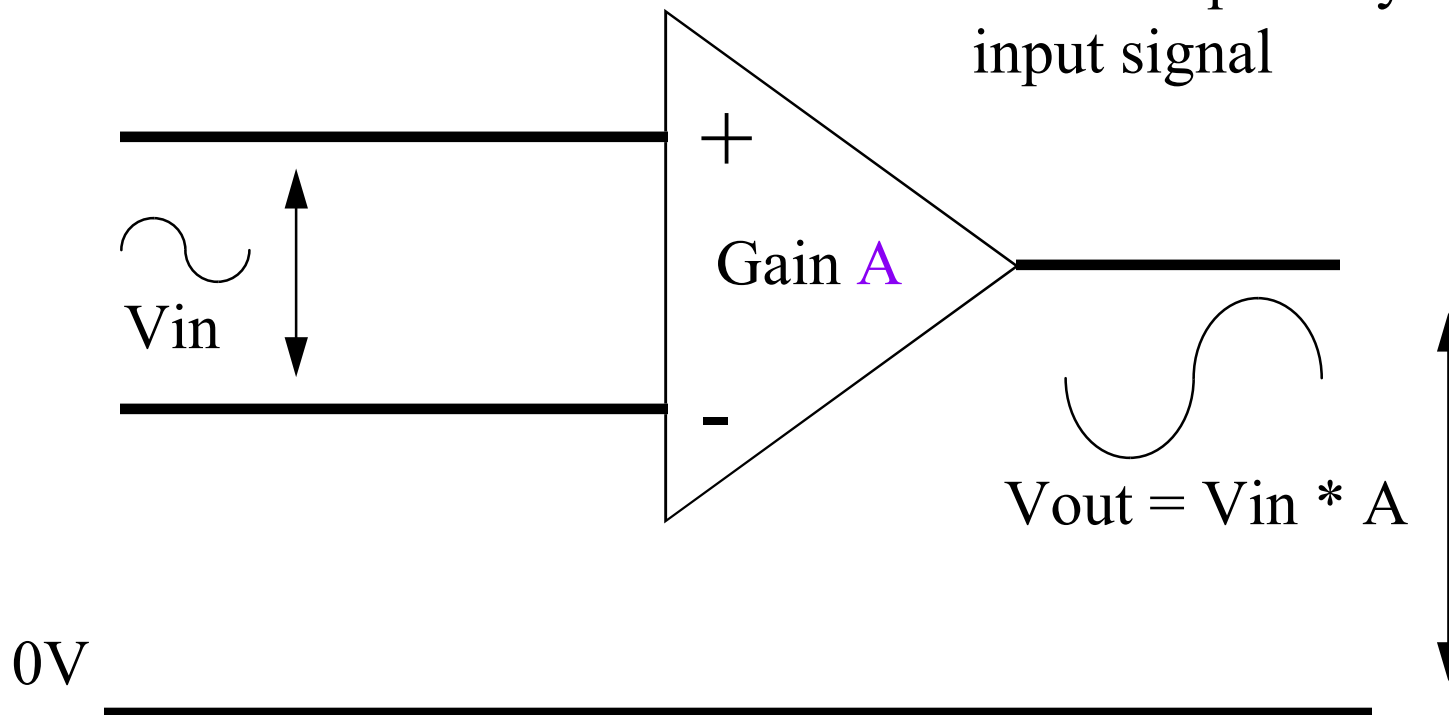


Amplifiers.

Amplifier Configuration.

Differential

The Amplifier in Inverter Differential mode.

Note the polarity of the input signal

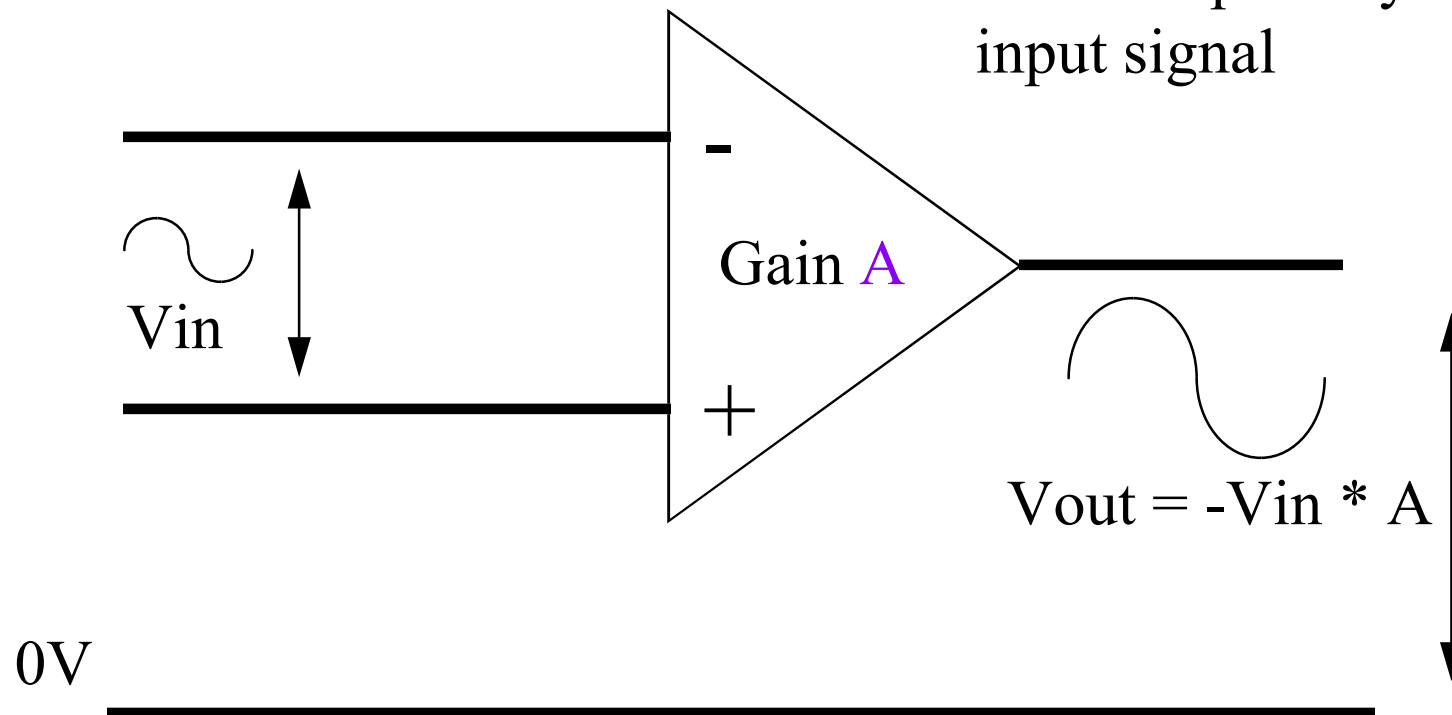


Amplifiers.

The Proof

The Ideal Amplifier Model.


Z is used to define the resistance when both AC and also DC components may be present.

Measured in Ohms

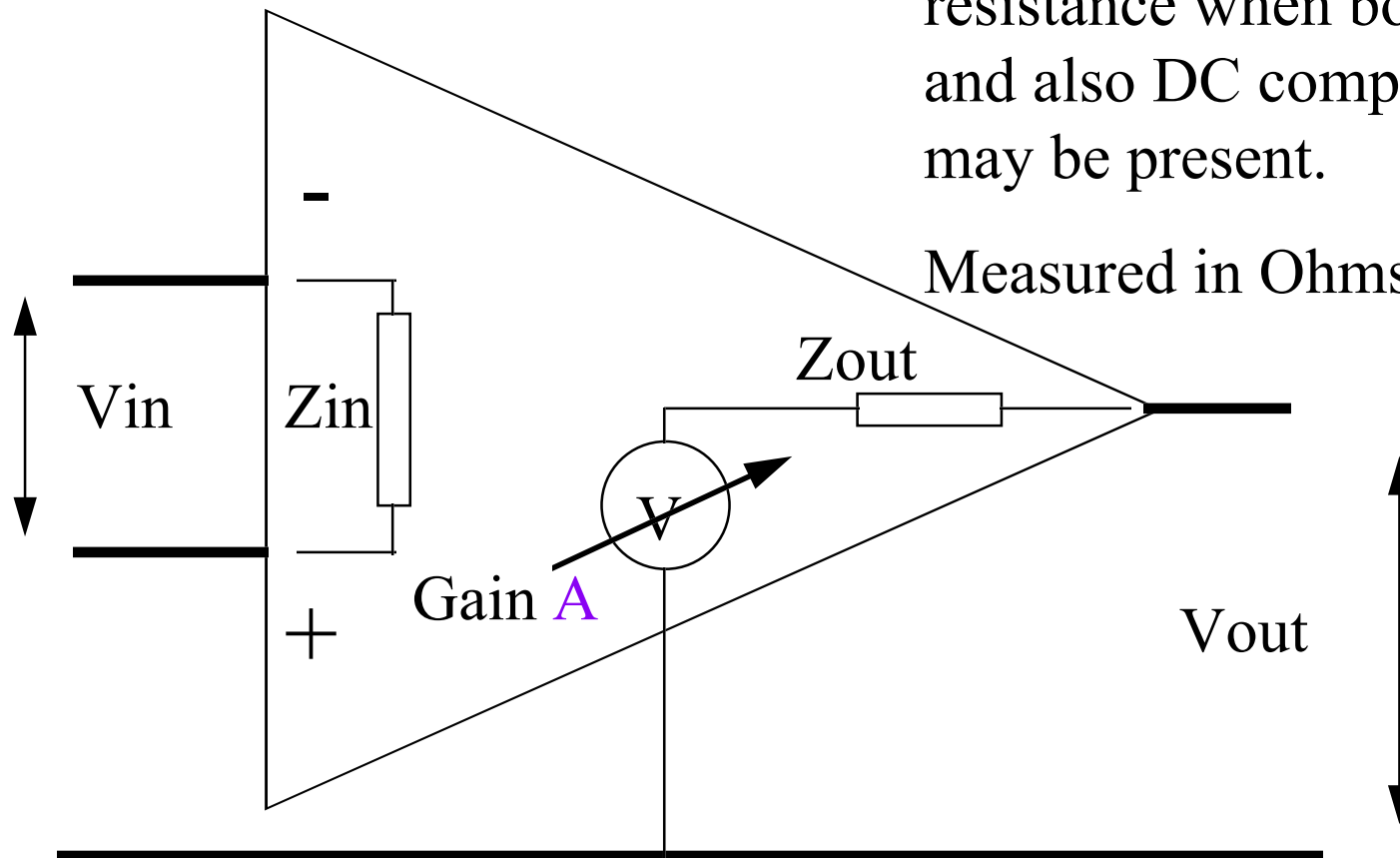


Amplifiers.

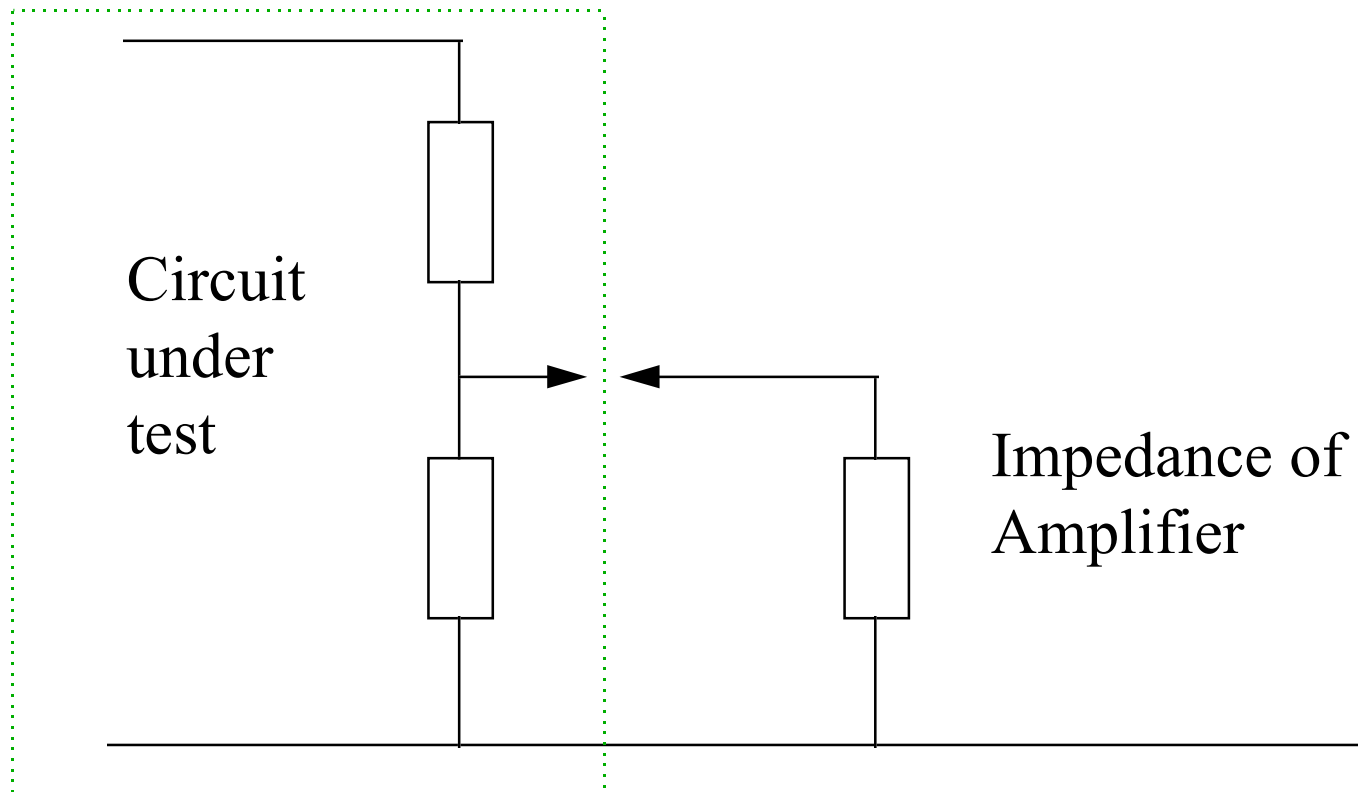- If the input of the Amplifier is to be connected to some other circuit then what should its Input Resistance/Impedance be ?




Amplifiers.

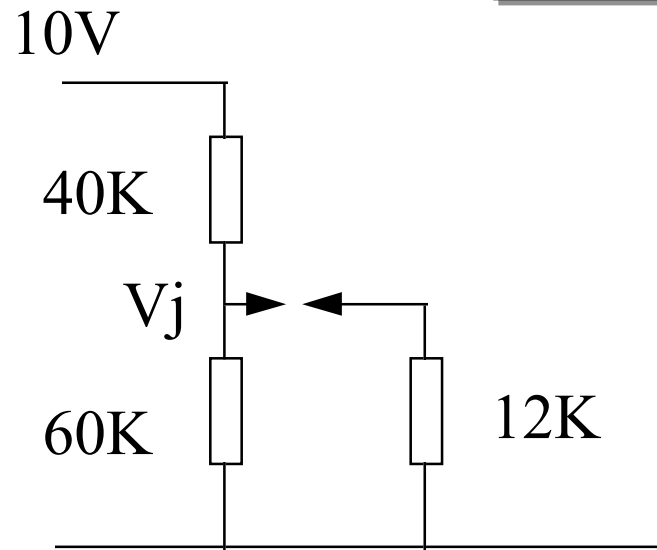

V_j before connection is ?V


V_j after connection is ?V

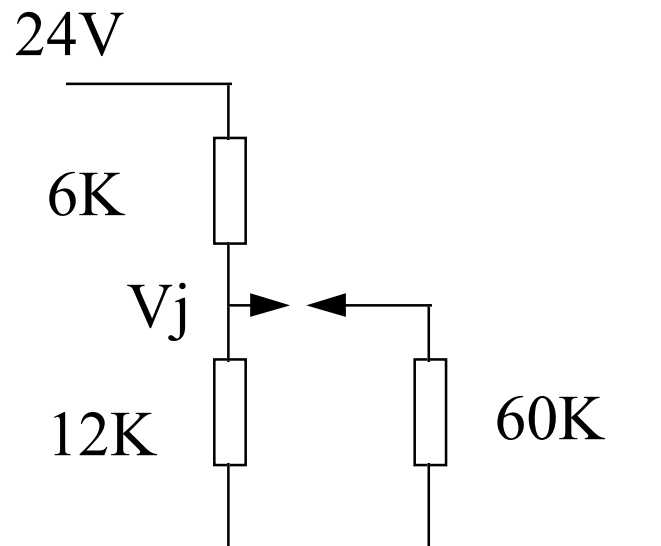

V_j before connection is ?V


V_j after connection is ?V

Amplifiers.

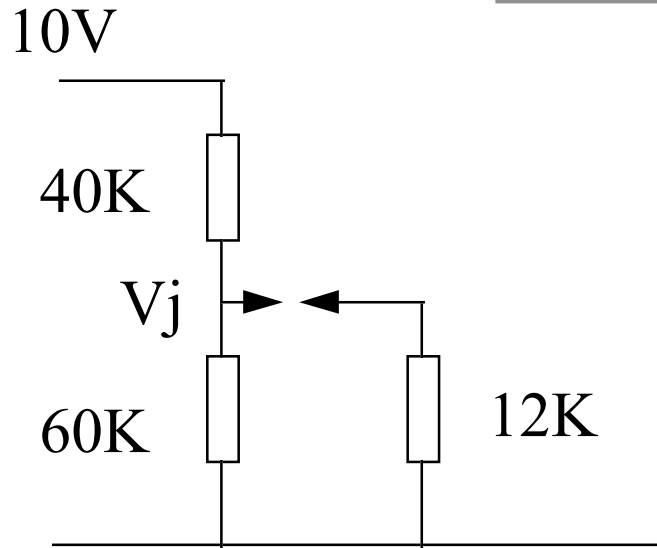

Vj before connection is 6V

Vj after connection is 2V

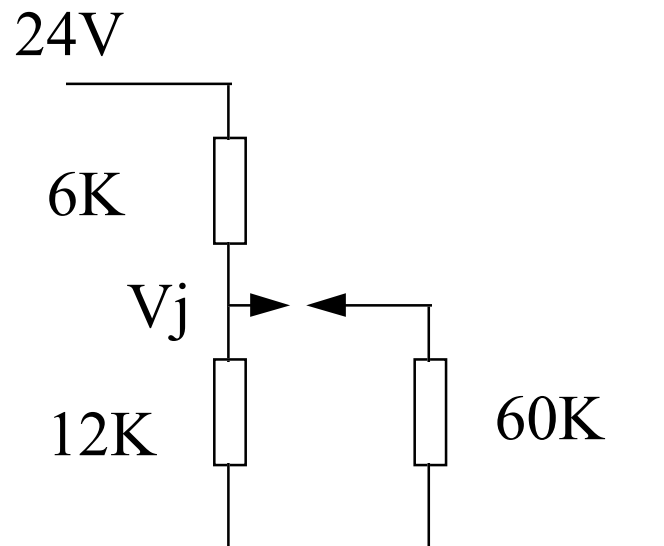


Vj before connection is 16V

Vj after connection is 15V


Amplifiers.

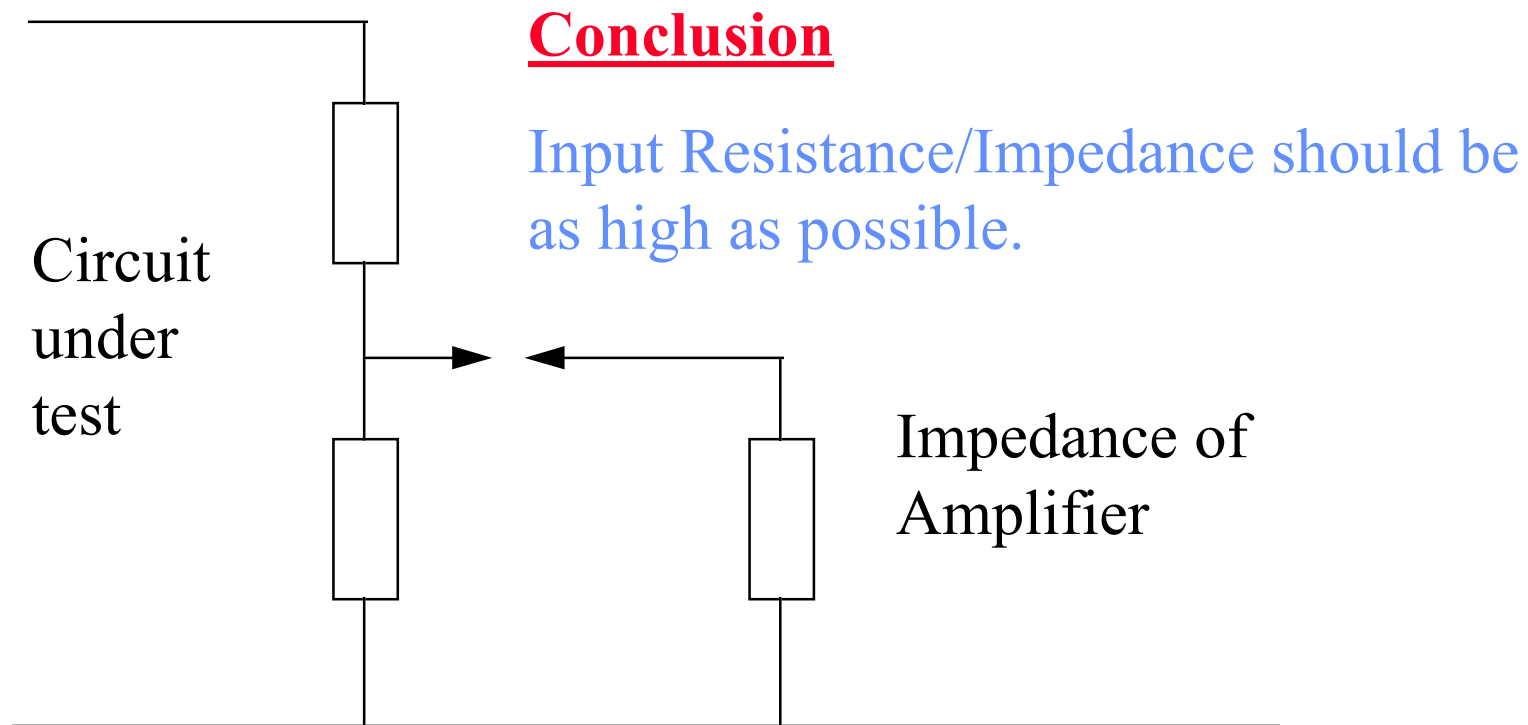- If the input of the Amplifier is to be connected to some other circuit then what should its input resistance/impedance be ?





Amplifiers.


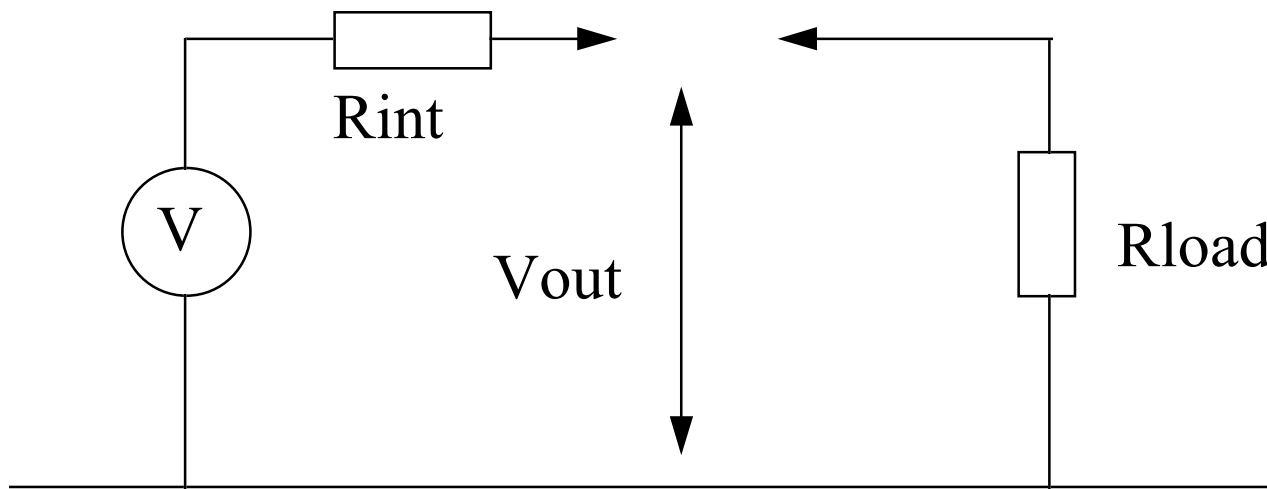
- If the Output of the Amplifier is to be connected to some other circuit then what should its Output Resistance/Impedance “ R_{int} ” be?



Amplifiers.

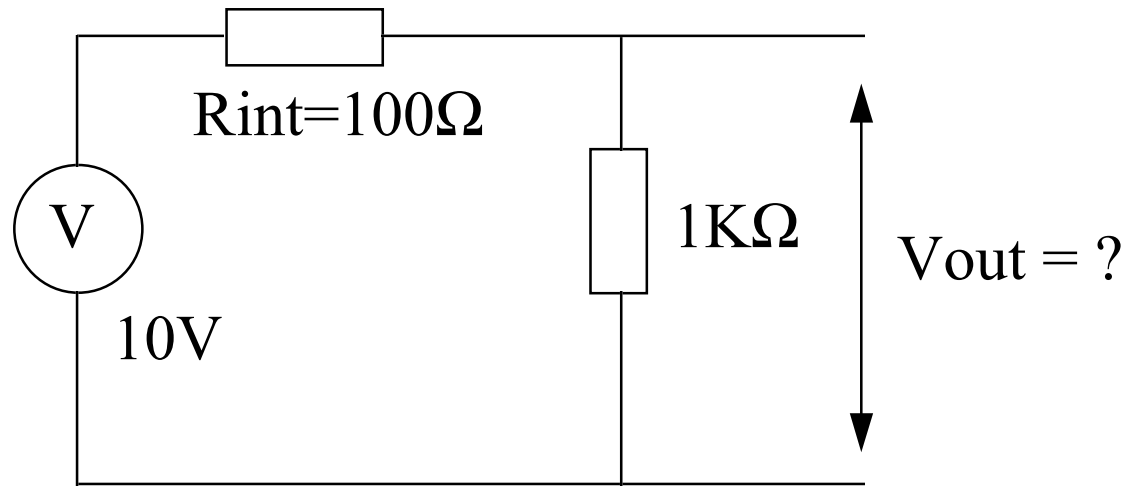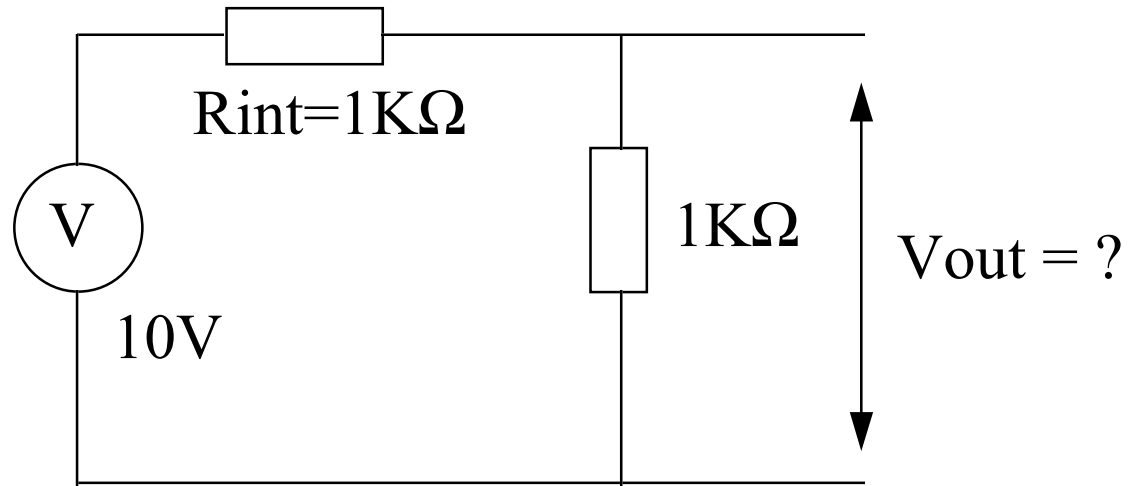

Amplifiers.

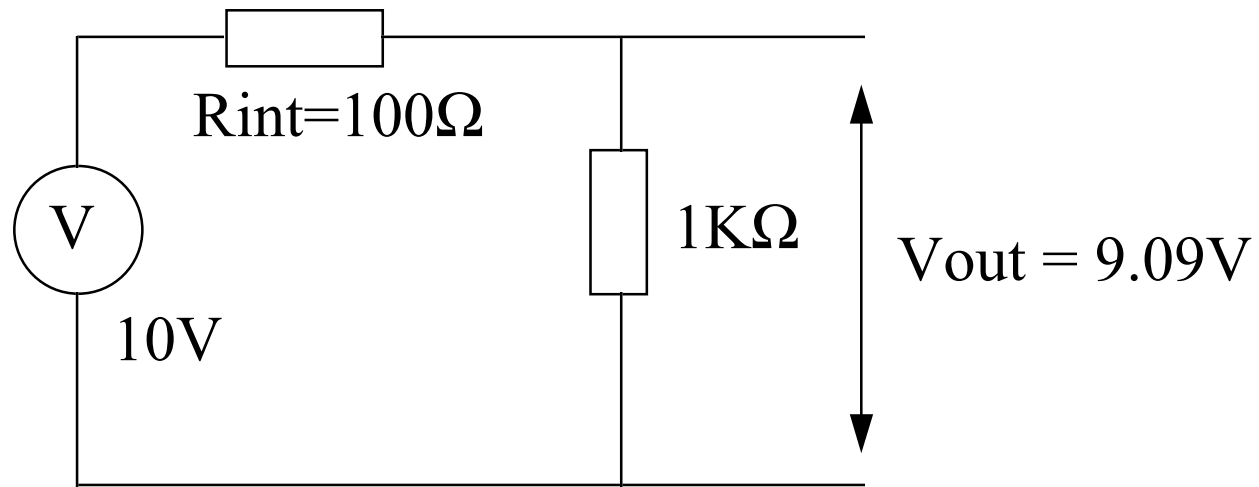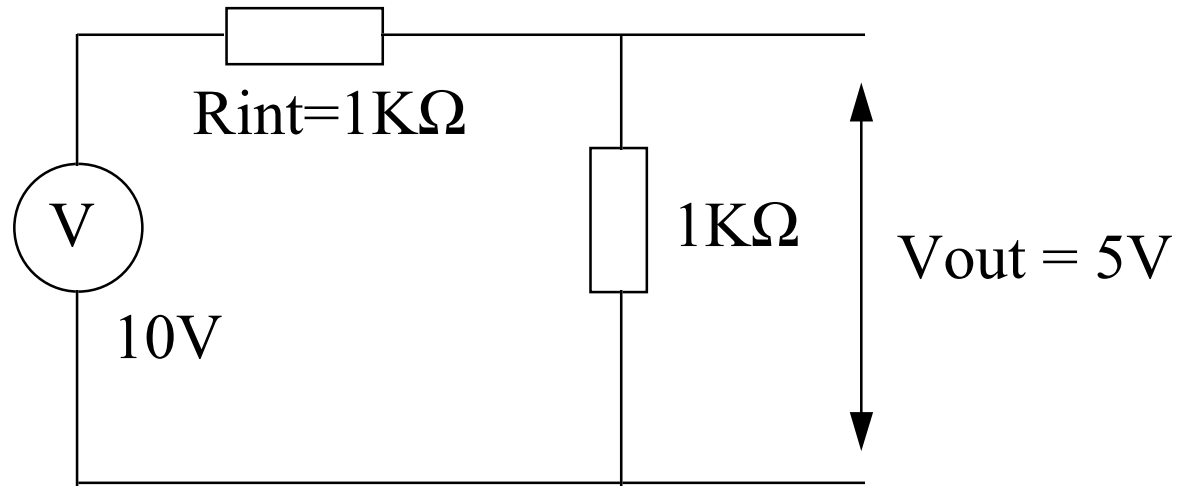


Amplifiers.

- If the Output of the Amplifier is to be connected to some other circuit then what should its Output Resistance/Impedance “ R_{int} ” be?

Conclusion

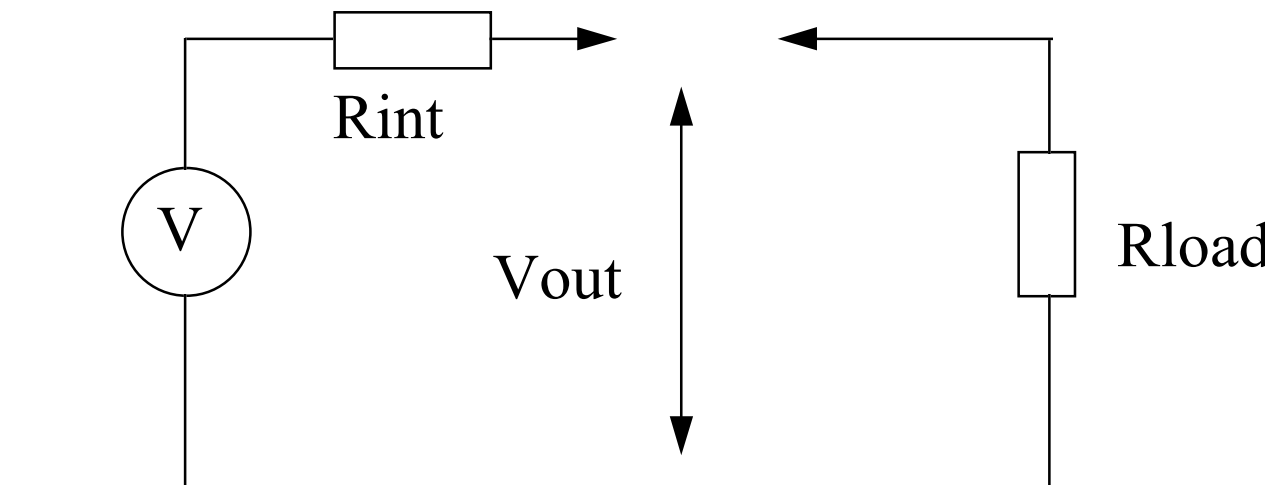Output Resistance/Impedance should be as low as possible.



Amplifiers.


- Summary :-
- The Ideal Amplifier should have **Infinite** Input Impedance.
- The Ideal Amplifier should have **Zero** Output Impedance.
- The Ideal Amplifier should have an **Infinite** Gain.

Amplifiers


Feedback.

Amplifiers.

Feedback How do we recognize it ?

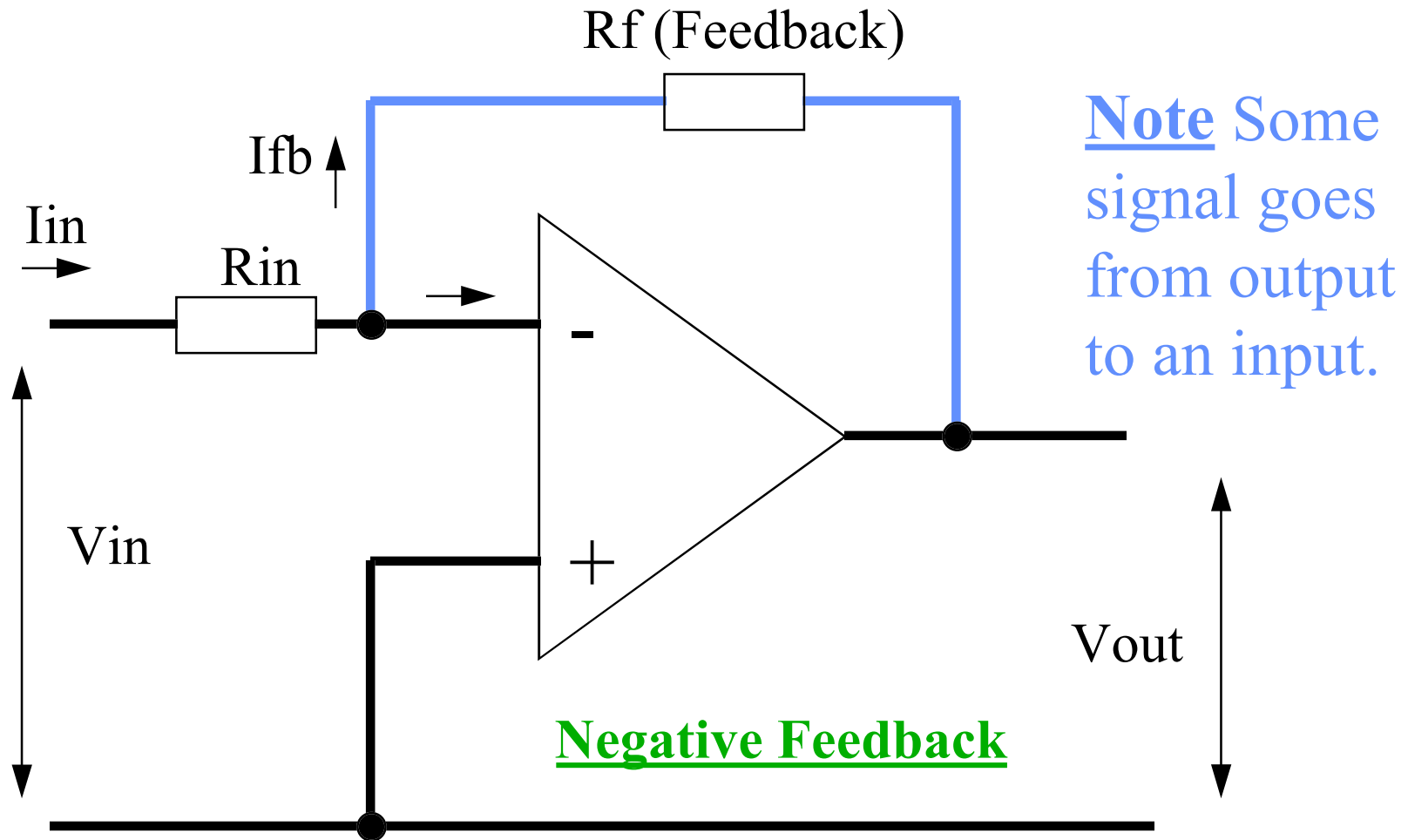


Amplifiers.

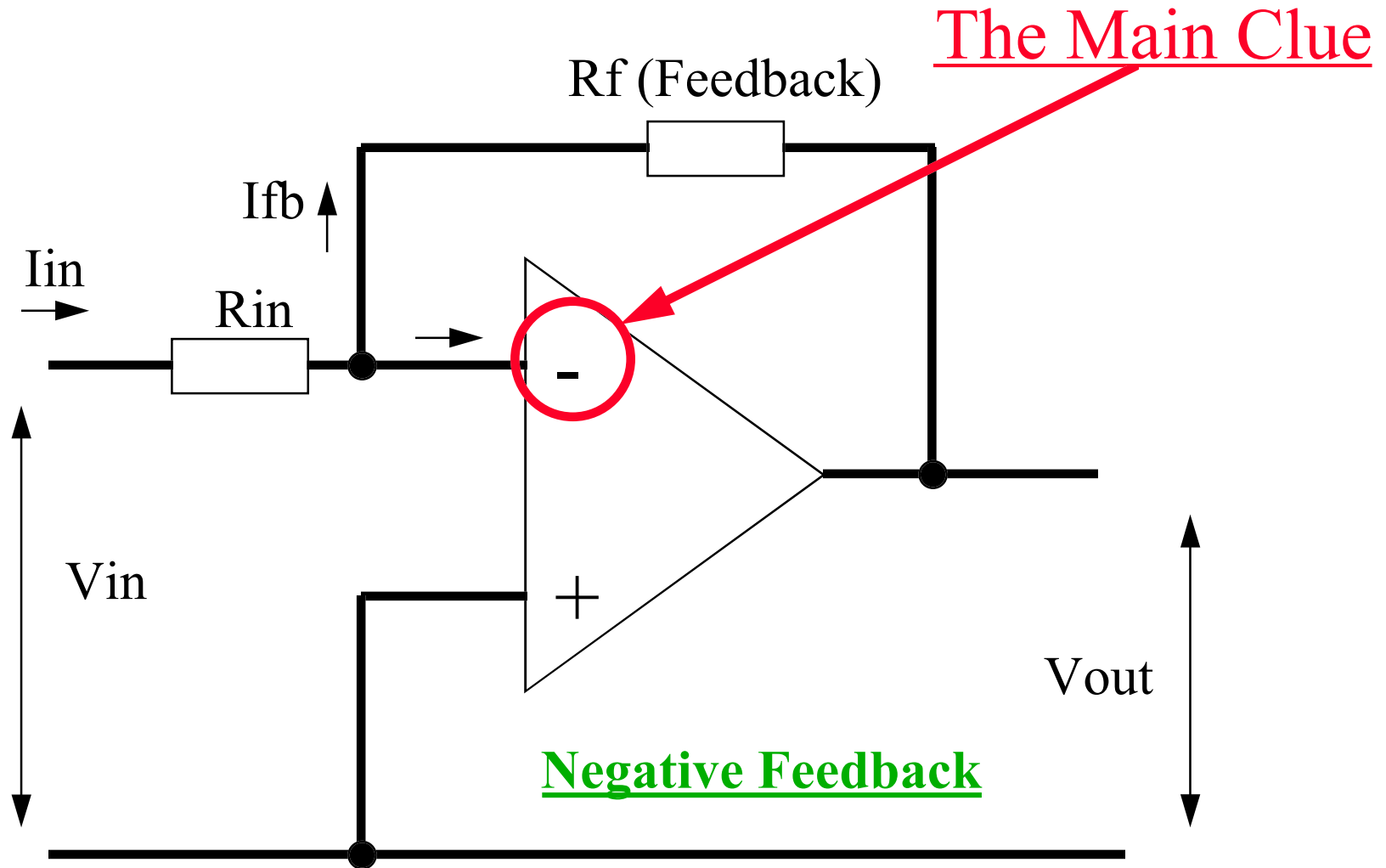


Amplifiers.

Feedback How do we recognize it ?

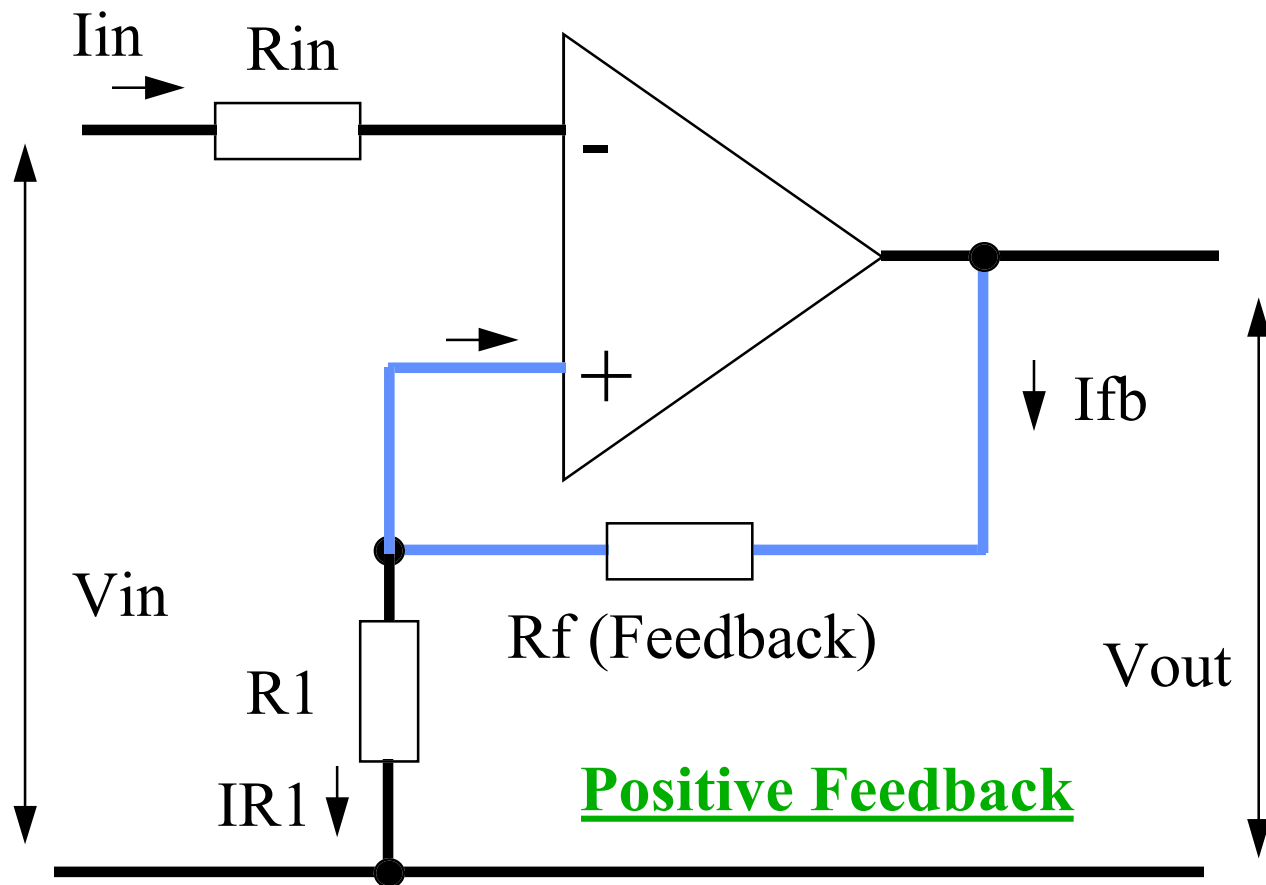

Note Some signal goes from output to an input.

Amplifiers.

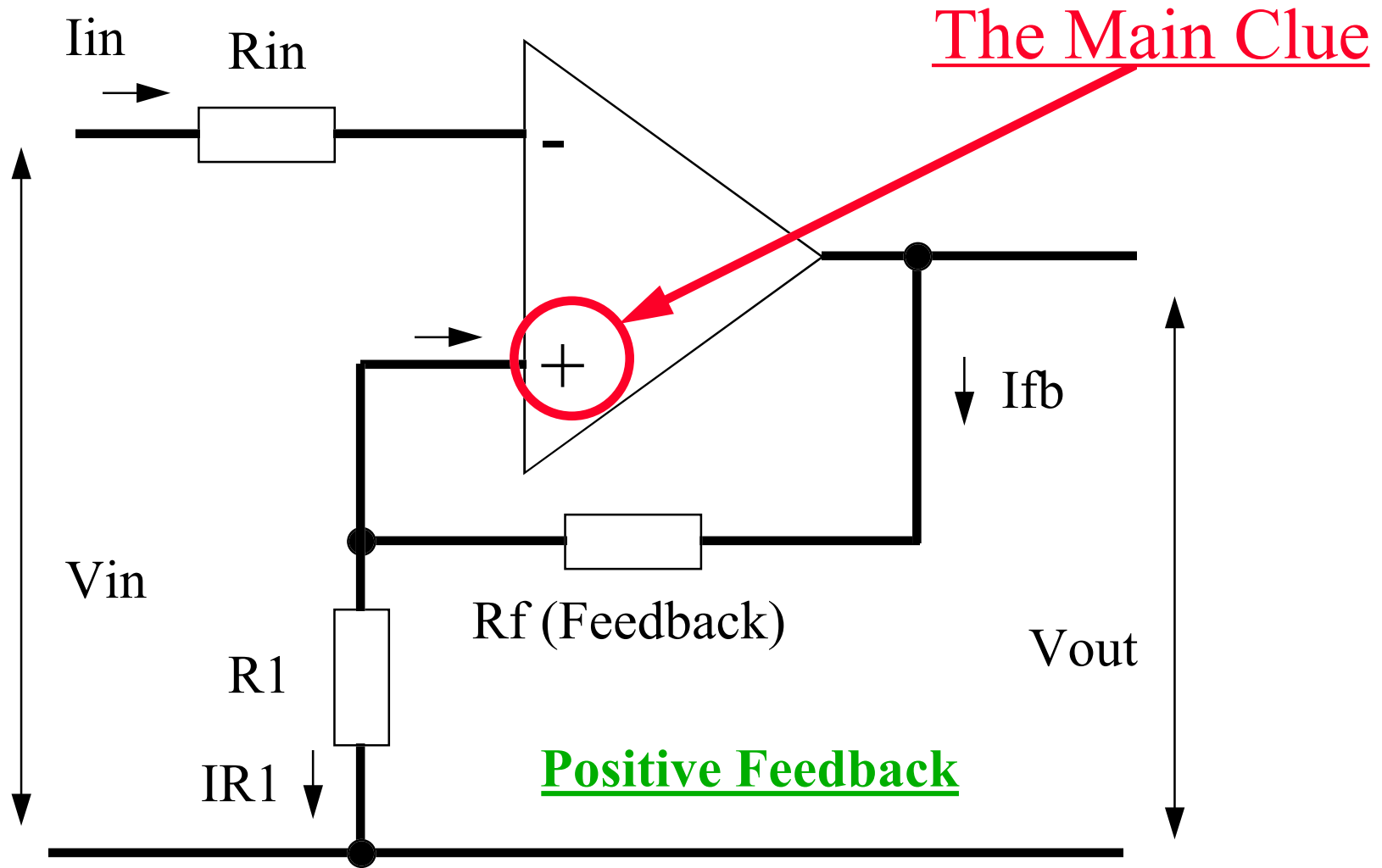

Amplifiers.


Effect of Gain

- Assume Gain of amplifier G is 10^7 and power rails of Amplifier are ± 12 Volts.
- If an Input voltage of One Volt is applied.
 - The amplifier would try to give an Output of 10^7 Volts. (Input voltage * Gain)
 - However it is the power rails that would limit the Output to 12Volts.
- Therefore once the Input voltage exceeds the (power rails voltage) divided by the Gain no further effect will be noticed.

Amplifiers.

The Proof

The effects of Feedback on an Amplifier.

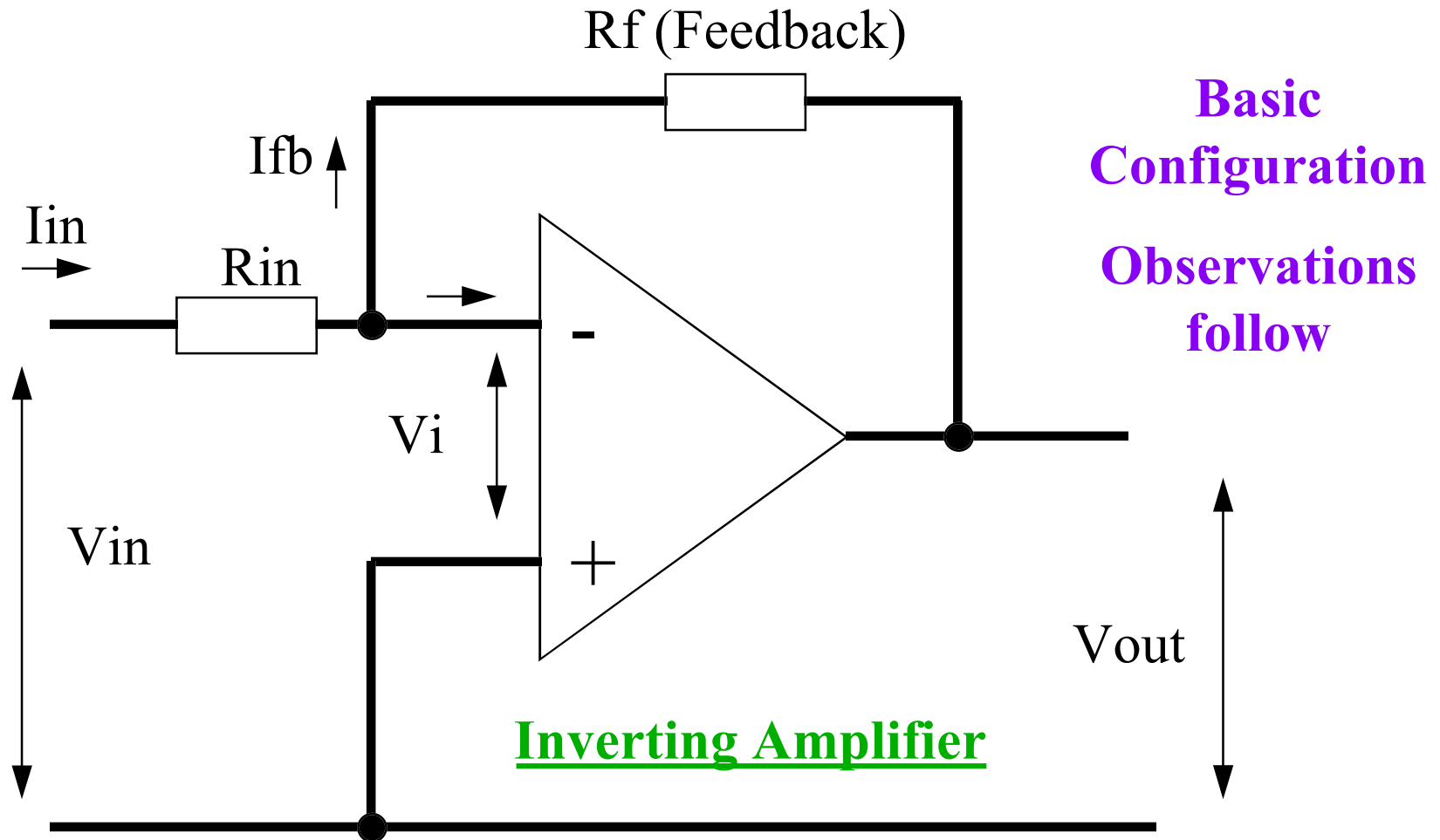


Amplifiers.

The Proof

Observation 1. $V_{out} = V_i * \text{Gain}$. As Gain is very large then even when V_{out} reaches Power rail voltage then V_i will still be insignificant. Therefore when the +ve input is tied to ground then the -ve input will be virtually at the same potential. In this configuration the -ve input is said to be a Virtual Earth.

Observation 2. As the input impedance of the amplifier is very high it can be assumed by default that $I_{in} = I_{fb}$.

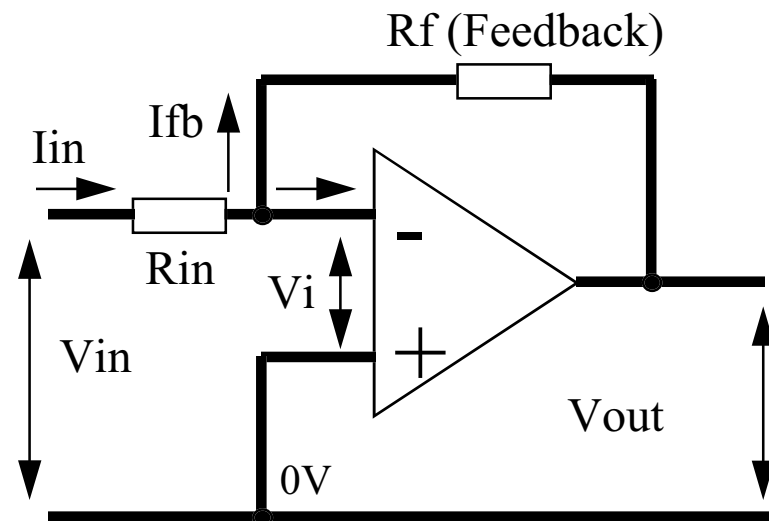Observation 3. If V_{in} goes Positive then V_{out} will go negative. It is an Inverting Amplifier.



Amplifiers.

The Proof

Using Ohms law $I_{in} = \frac{(V_{in} - 0V)}{R_{in}} = \frac{V_{in}}{R_{in}}$

Voltage across R_{in}

and $I_{fb} = \frac{(0V - V_{out})}{R_f} = \frac{-V_{out}}{R_f}$

Voltage across R_f


However as $I_{in} = I_{fb}$

Therefore $\frac{V_{in}}{R_{in}} = \frac{-V_{out}}{R_f}$

By default this point is also $0V$ because it is a virtual earth point

and we Remember that
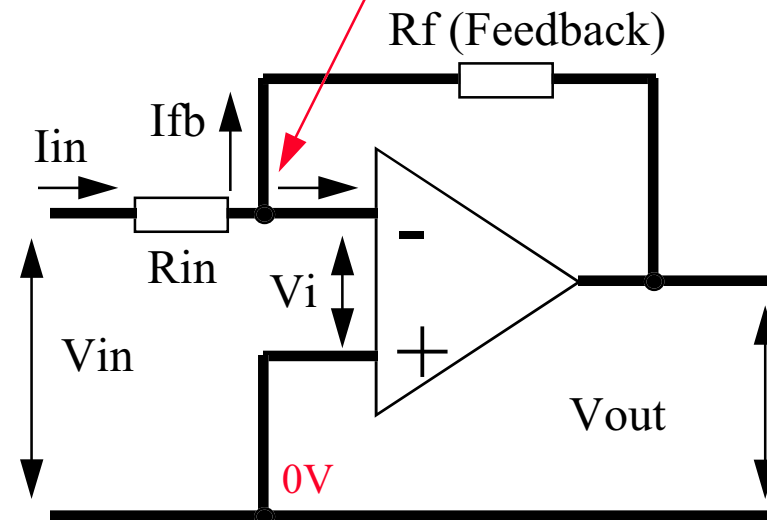
$$\text{Gain } A = \frac{V_{out}}{V_{in}}$$



Amplifiers.

The Proof

$$\frac{V_{in}}{R_{in}} = \frac{-V_{out}}{R_f}$$


$$\frac{(-1) * R_f * V_{in}}{V_{in} * R_{in}} = \frac{-V_{out} * R_f * (-1)}{R_f * V_{in}}$$

$$\frac{(-1) * R_f * \cancel{V_{in}}}{\cancel{V_{in}} * R_{in}} = \frac{\cancel{-V_{out}} * R_f * (-1)}{\cancel{R_f} * V_{in}}$$


This gives us :-

$$\text{Gain } A = \frac{V_{out}}{V_{in}} = \frac{-R_f}{R_{in}}$$

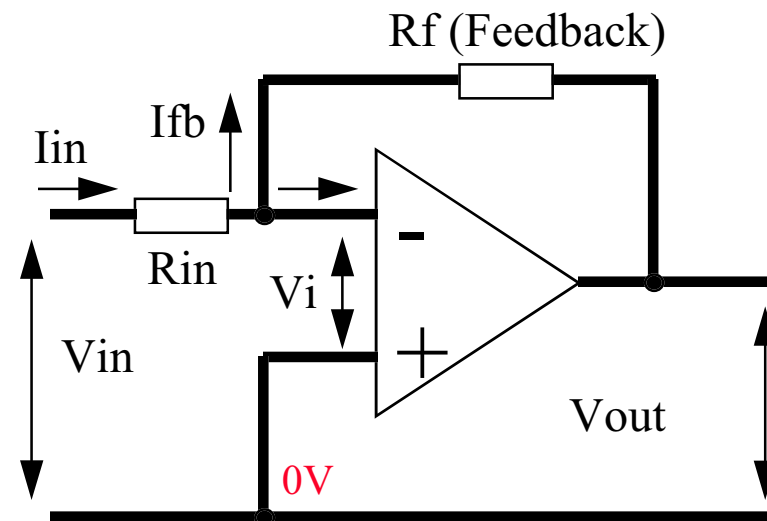Note The **minus** only indicates an Inverting Amplifier.



Amplifiers.

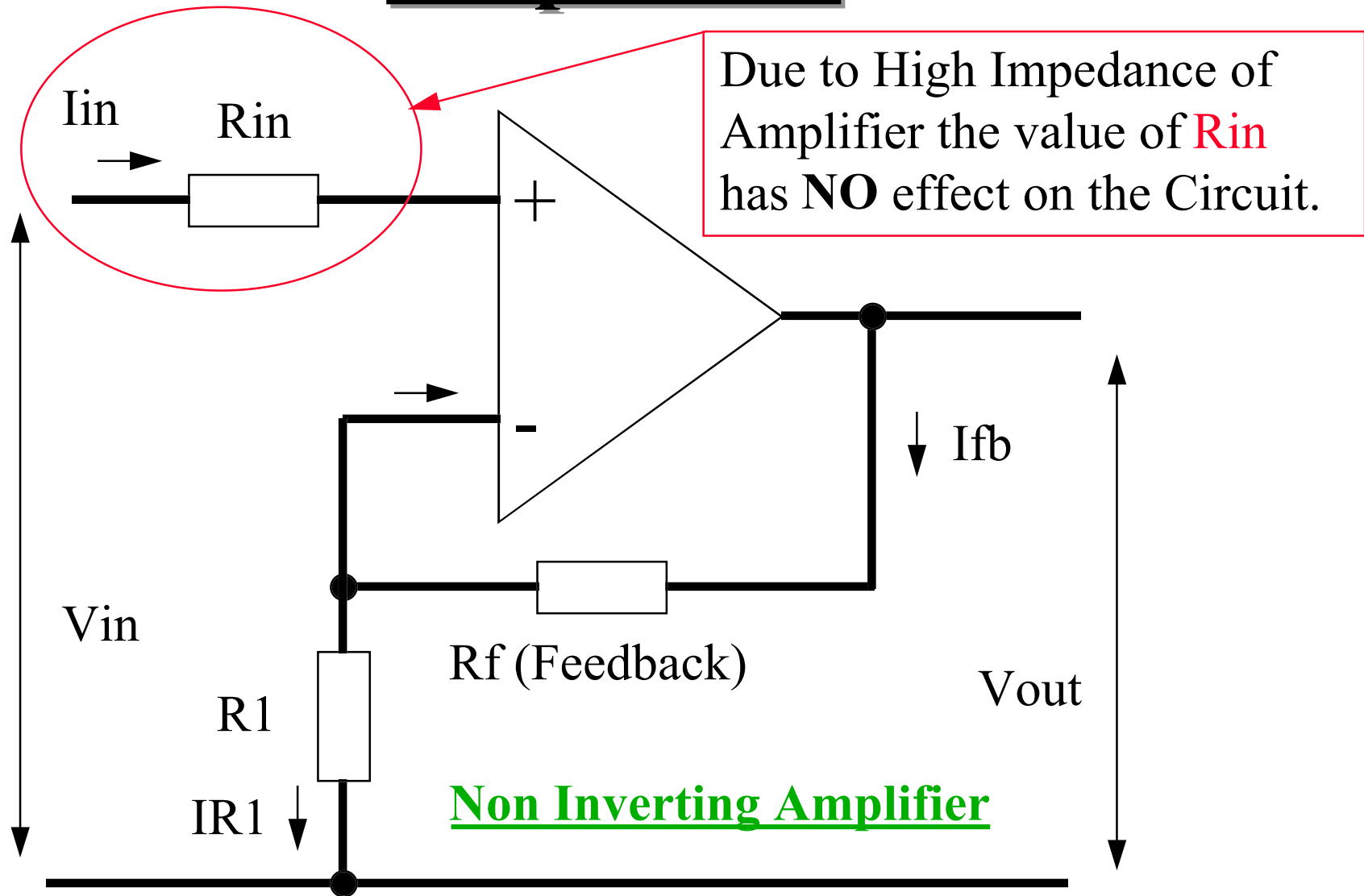


Amplifiers.

The Proof

Observation 1. $V_{out} = V_i * \text{Gain}$. As Gain is very large then even when V_{out} reaches Power rail voltage then V_i will still be insignificant. Therefore V_{in} effectively appears across $R1$ or $V_{in} = V_{R1}$.

Observation 2. As the input impedance of the amplifier is very high it can be assumed by default that No current will flow into either the Positive (+) or Negative (-) inputs .

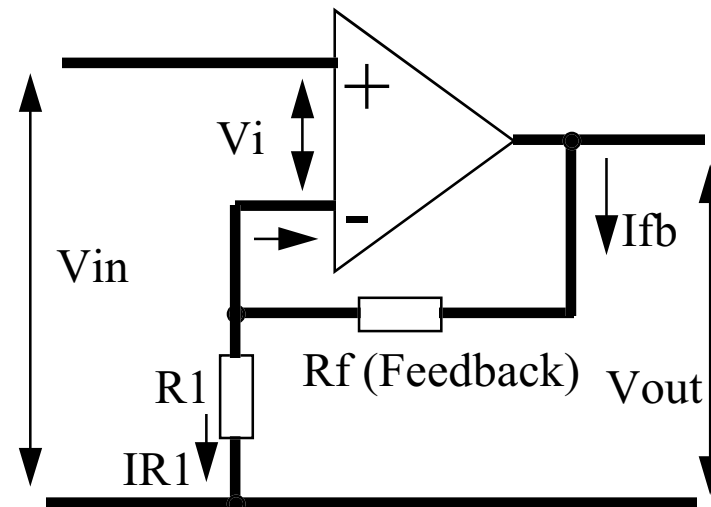Observation 3. If V_{in} goes Positive then V_{out} will also go positive. It this is an Non-Inverting Amplifier.



Amplifiers.

The Proof

Using Ohms law $IR1 = \frac{V_{in}}{R1}$


and $I_{fb} = \frac{(V_{out} - V_{in})}{R_f}$

However as $IR1 = I_{fb}$

Therefore $\frac{V_{in}}{R1} = \frac{V_{out} - V_{in}}{R_f}$

and we Remember that
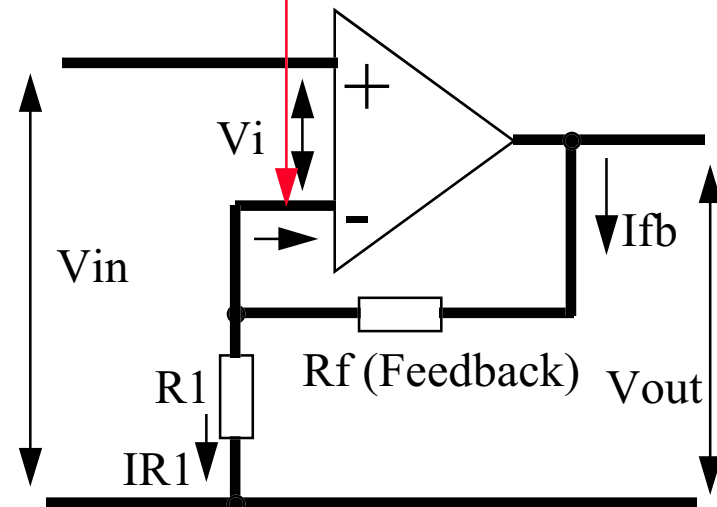
$$\text{Gain } A = \frac{V_{out}}{V_{in}}$$



Amplifiers.

The Proof


$$\frac{V_{in}}{R1} = \frac{(V_{out} - V_{in})}{Rf}$$

$$\frac{Rf * V_{in}}{V_{in} * R1} = \frac{(V_{out} - V_{in}) * Rf}{Rf * V_{in}}$$

$$\frac{\cancel{Rf} * \cancel{V_{in}}}{\cancel{V_{in}} * R1} = \frac{(V_{out} - V_{in}) * \cancel{Rf}}{\cancel{Rf} * V_{in}}$$

This gives us :-
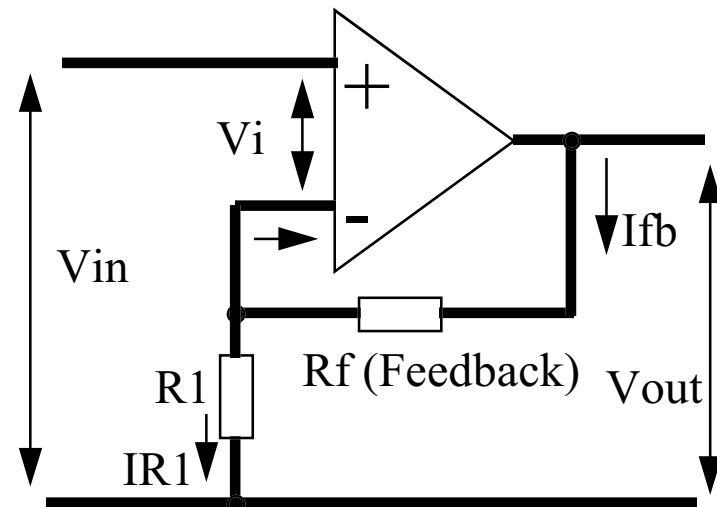
$$\frac{V_{out} - V_{in}}{V_{in}} = \frac{Rf}{R1}$$



Amplifiers.

The Proof

$$\frac{V_{out} - V_{in}}{V_{in}} = \frac{R_f}{R_1}$$

$$\frac{V_{out}}{V_{in}} - \frac{V_{in}}{V_{in}} = \frac{R_f}{R_1}$$


$$\frac{V_{out}}{V_{in}} - \frac{1}{1} = \frac{R_f}{R_1}$$

This gives us :-

Adding one to both sides


$$\left(\frac{V_{out}}{V_{in}}\right) - 1 + 1 = \frac{R_f}{R_1} + 1$$
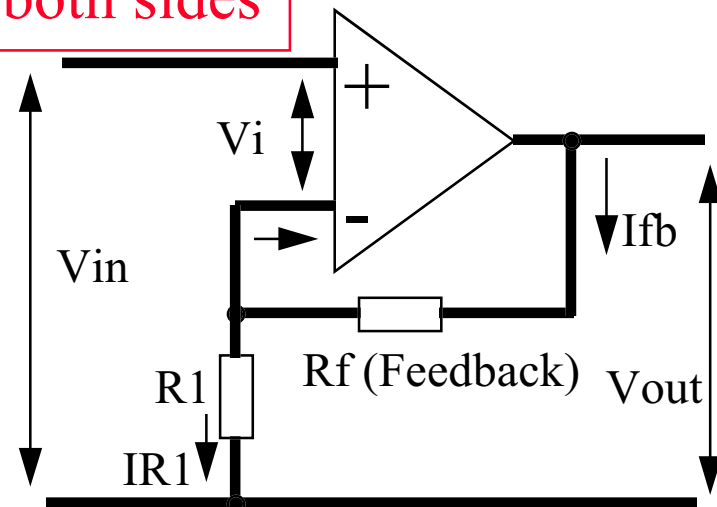
$$\text{Gain } A = \frac{V_{out}}{V_{in}} = \frac{R_f}{R_1} + 1$$




Amplifiers.

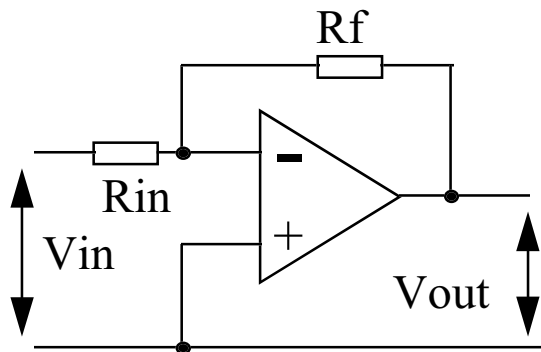- Summary
- Gain for Inverting amplifier is :-



$$\text{Gain } A = \frac{V_{out}}{V_{in}} = \frac{-R_f}{R_{in}}$$

- Gain for Non-Inverting amplifier is :-

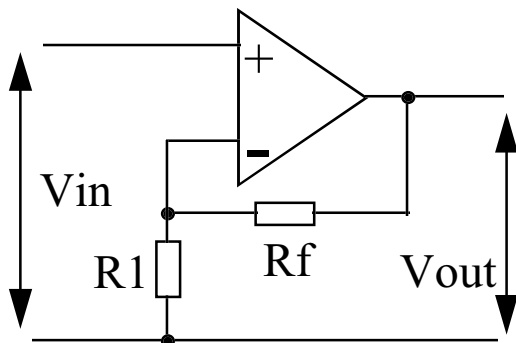


$$\text{Gain } A = \frac{V_{out}}{V_{in}} = \frac{R_f}{R_1} + 1$$

Amplifiers

Configurations.


Amplifiers.

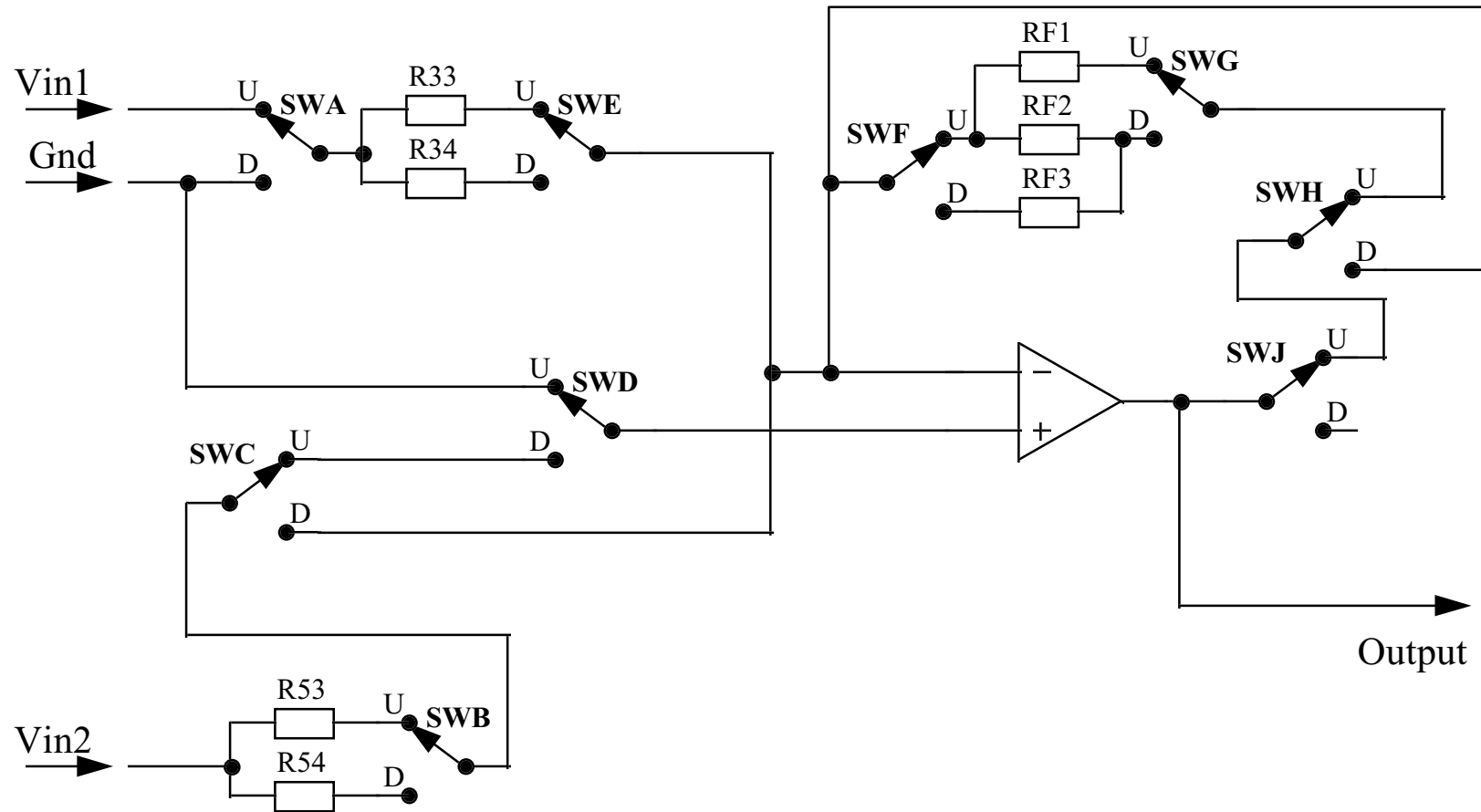

Generic Circuit Diagram.

- ✗ Remove
- ✓ Choice
- Link


Amplifiers.

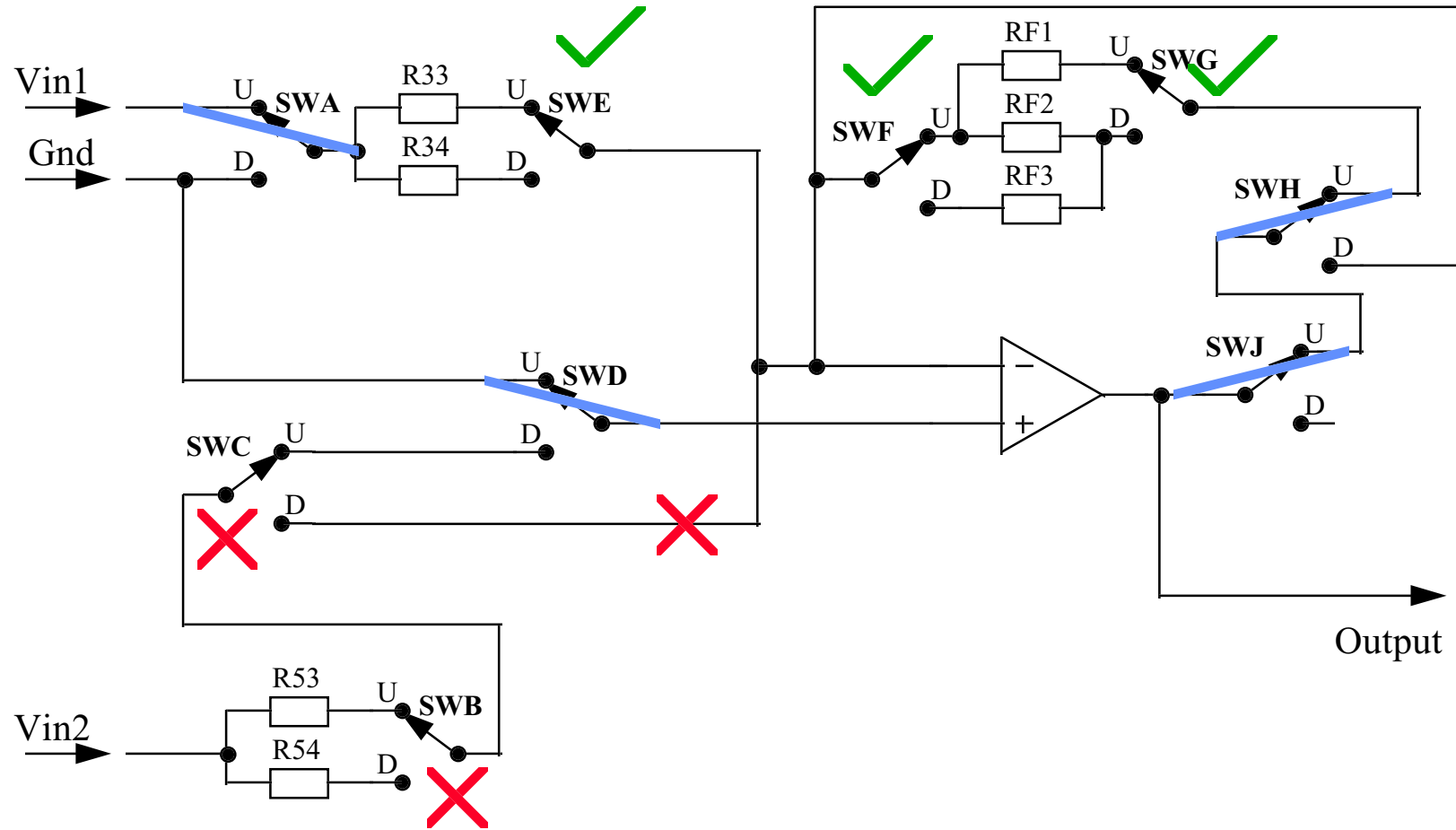

Inverting Amplifier Circuit Diagram.

- ✗ Remove
- ✓ Choice
- Link


Amplifiers.

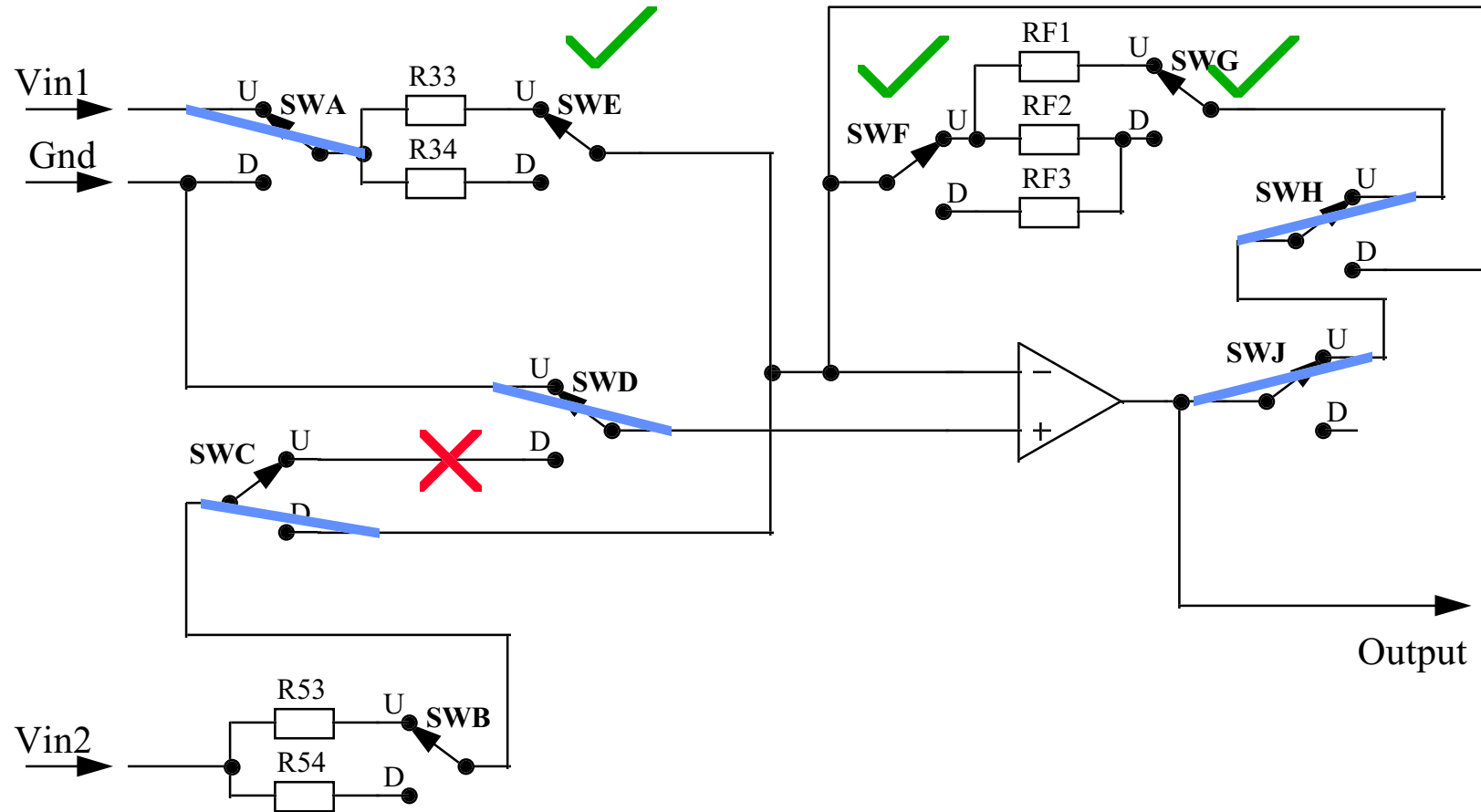

Inverting Summing Amplifier Circuit Diagram.

- ✗ Remove
- ✓ Choice
- Link

Amplifiers.

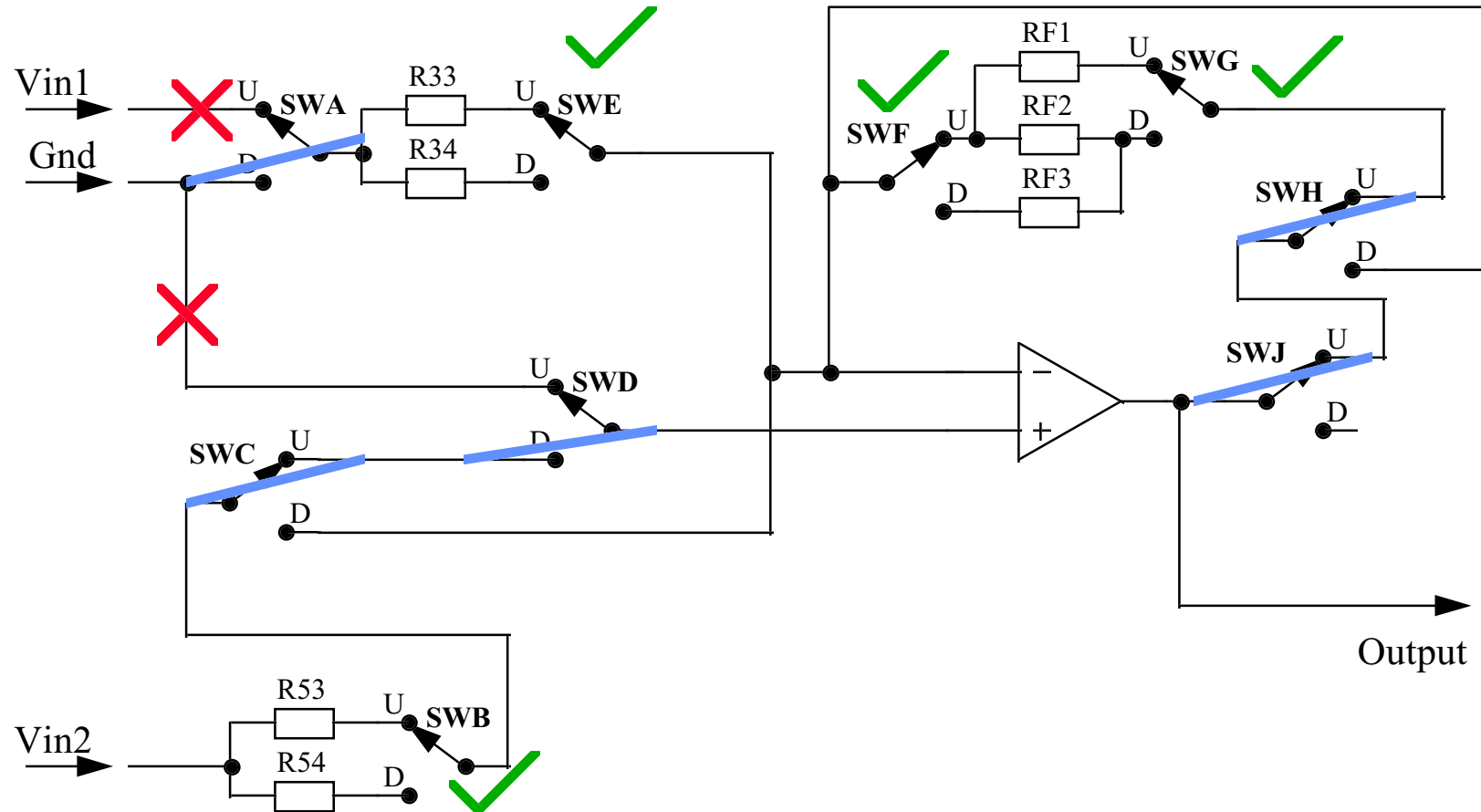

Non-Inverting Amplifier Circuit Diagram.



Transistor.

Amplifiers

Used as a Switch.

Amplifiers.

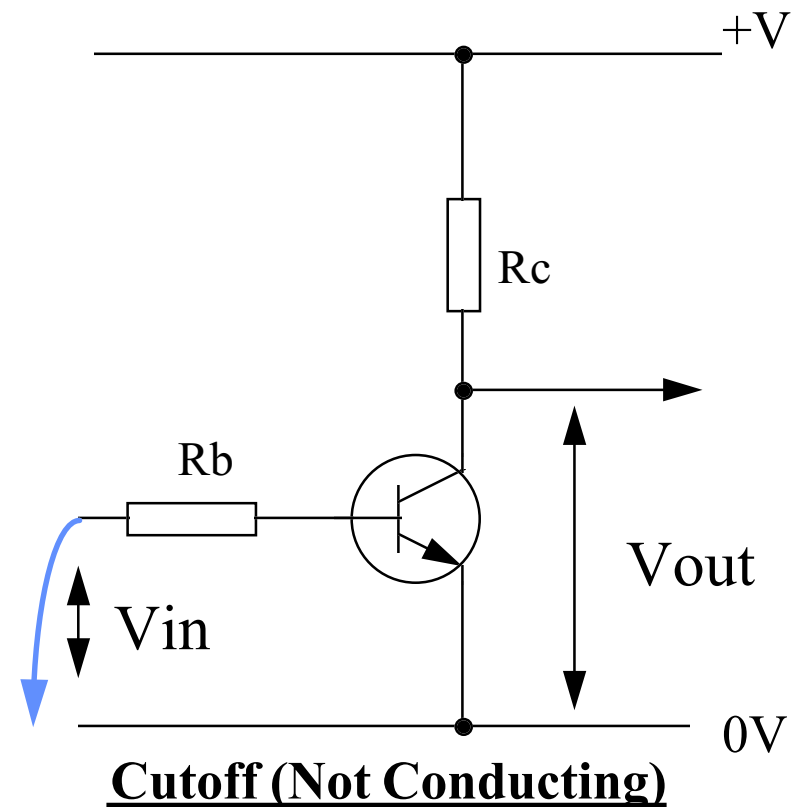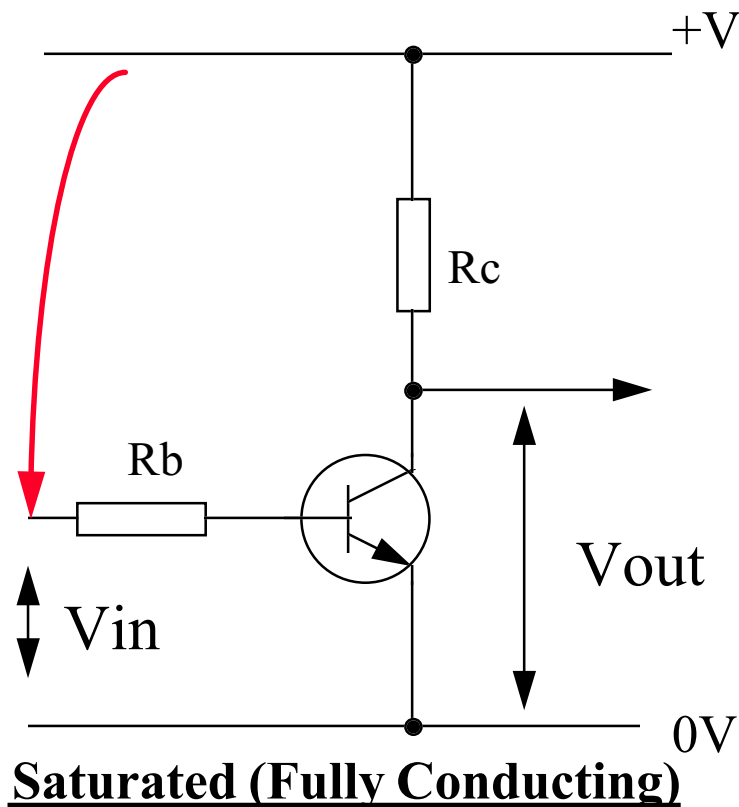- Using a Transistor as a Switch.
- V_{CE} virtually 0Volts



Amplifiers.

- Information to collect from the data sheets.
- Using Transistor type locate :-
 - Transistor Gain (H_{fe})
 - Maximum I_c (Collector Current)
 - Maximum Voltage Collector/Emitter
 - Maximum Voltage Base/Emitter
- Circuit specification Information :-
 - Supply voltage
 - Input and Output Voltages and Current.

Amplifiers.

- Assume Gain of Transistor $H_{fe} = 150$ and $+V = 9V$, $R_c = 1K\Omega$: Calculate minimum value of R_b to saturate the transistor.
- Voltage across $R_c = 9V - V_{sat} \cong 9V$
- Current through $R_c = I_C = V/R$
 $= 9/1000 = 9mA$
- Gain = $I_C/I_B = 150 \therefore I_B = I_C/150 = 60\mu A$
- Voltage across $R_b = 9V - 0.7V = 8.3V$
- $R_b = V/I = 8.3/60\mu = 138K\Omega \cong 120K\Omega$


Transistor.

Amplifiers

Characteristics.

Amplifiers.

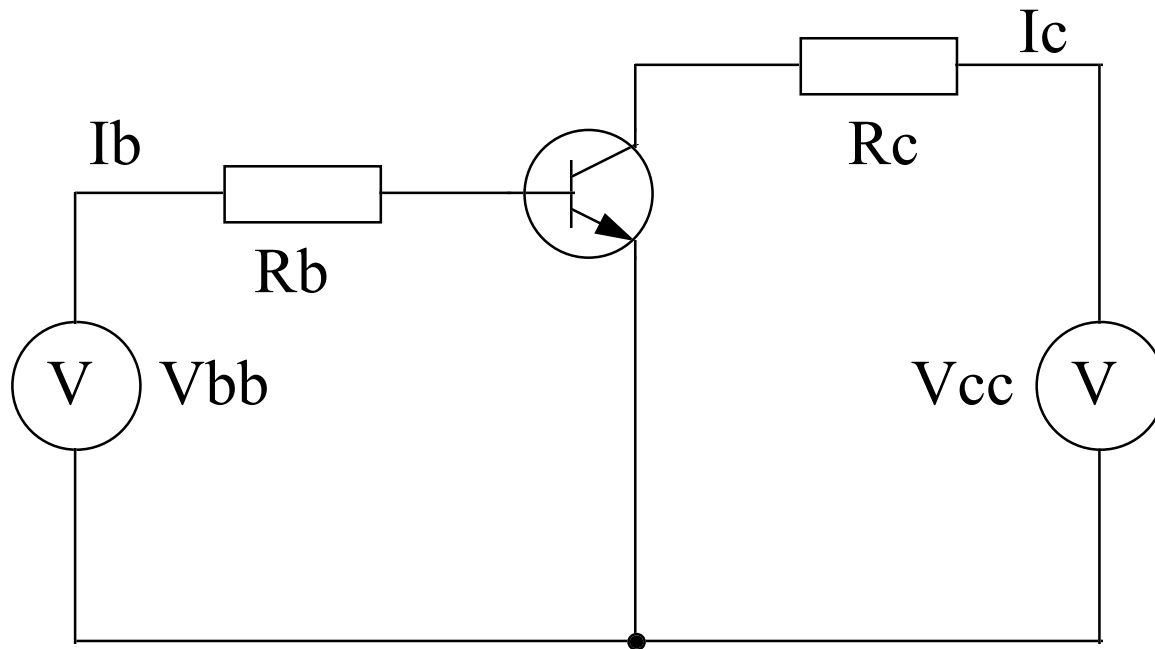- Circuit to identify the characteristics of a transistor.
- Set V_{bb} and adjust V_{cc} (Record I_b , I_c , V_{ce}).




Amplifiers.

Transistors


Common Emitter Characteristics

Saturation
Region

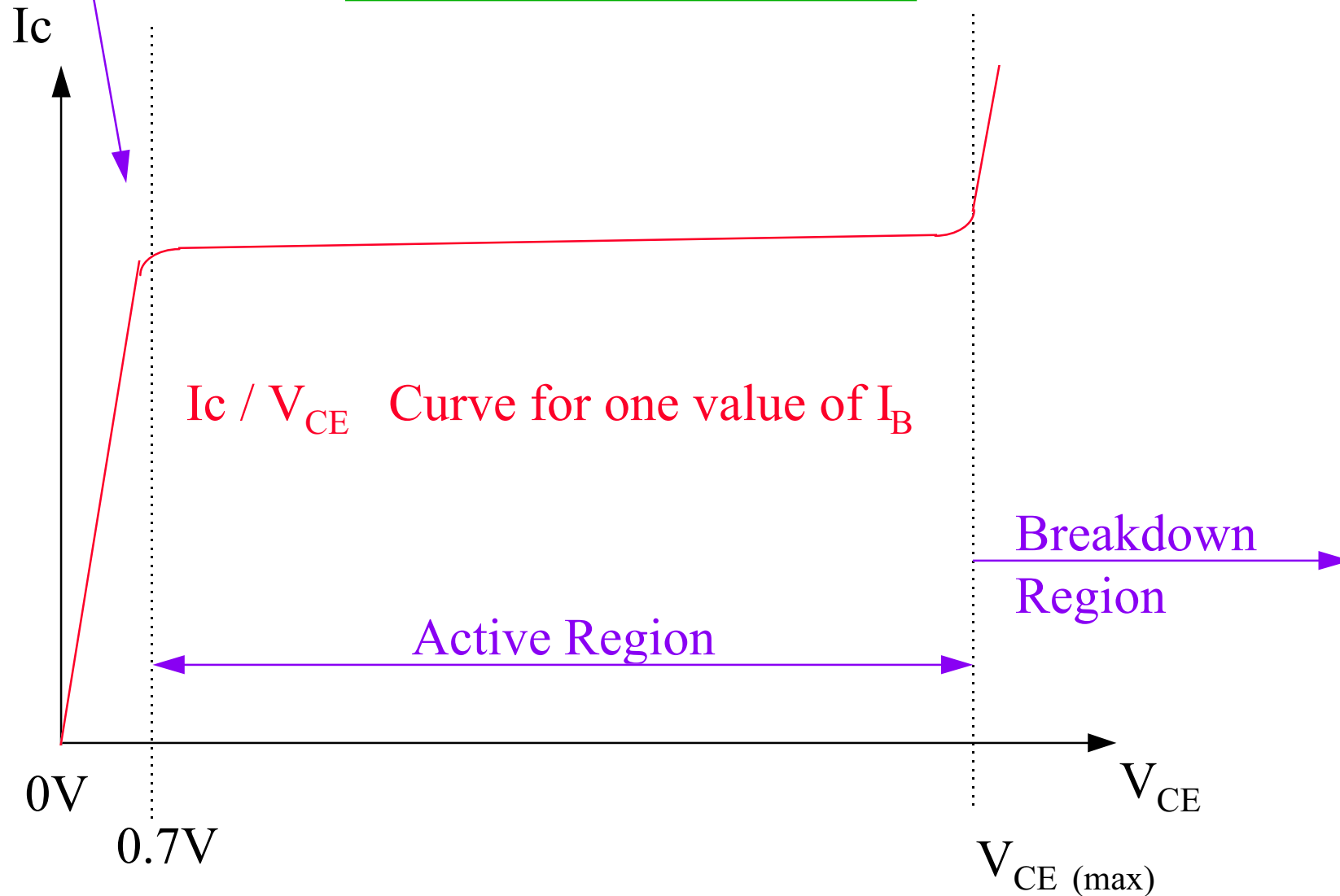


Amplifiers.

Transistors

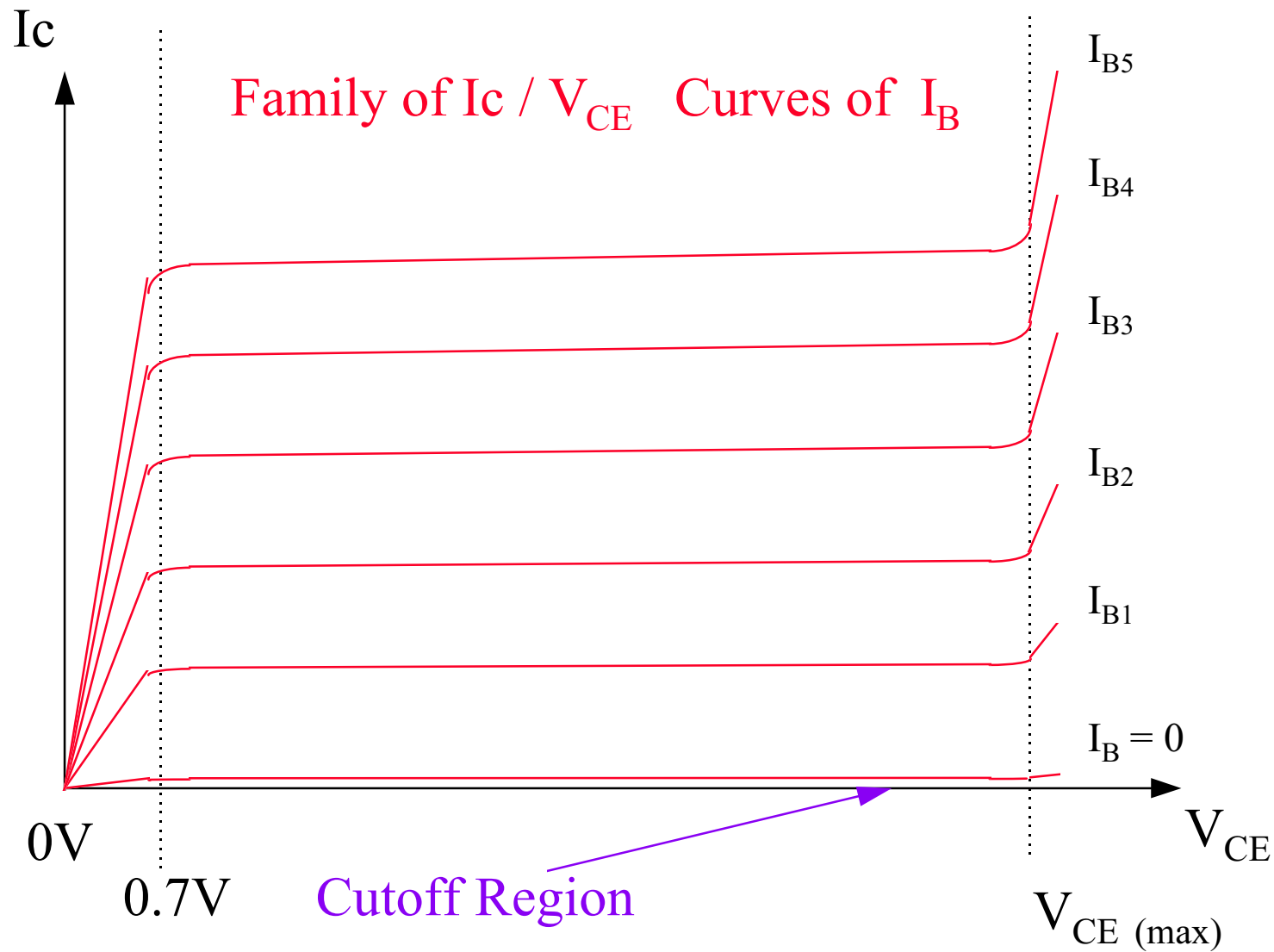

Amplifiers.

Transistors

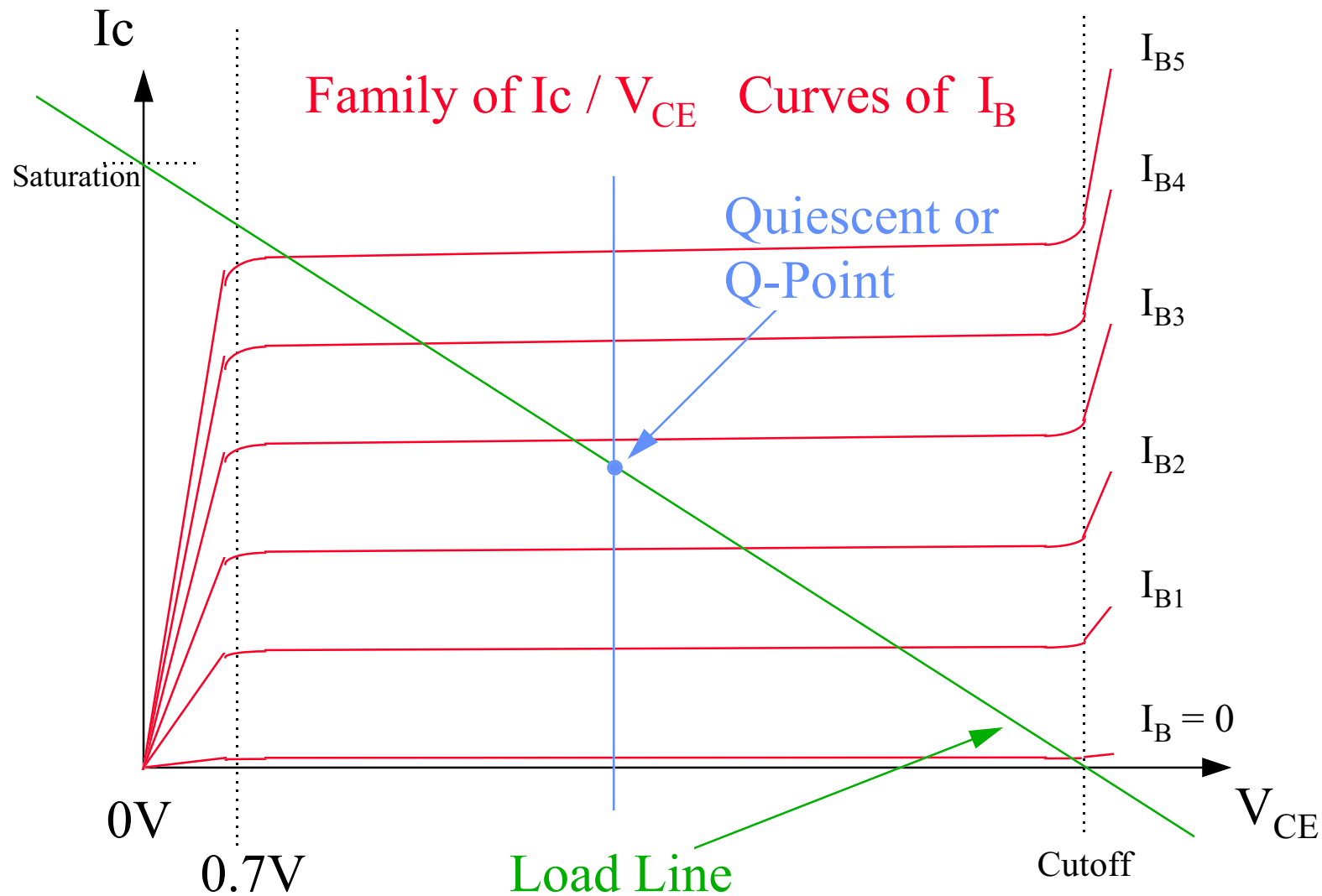



Transistor.

Amplifiers

Unregulated.

Amplifiers.

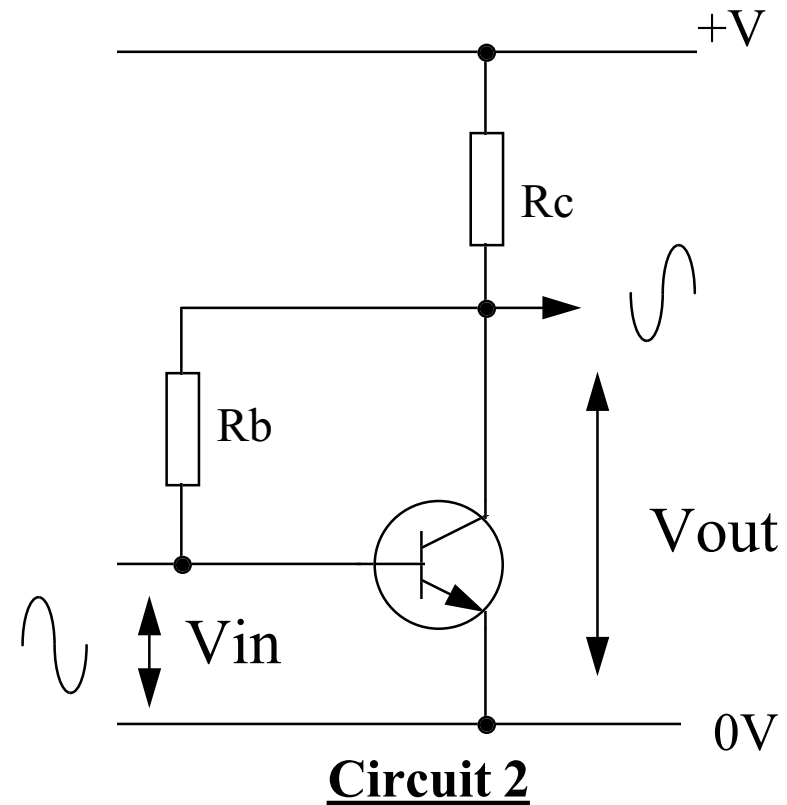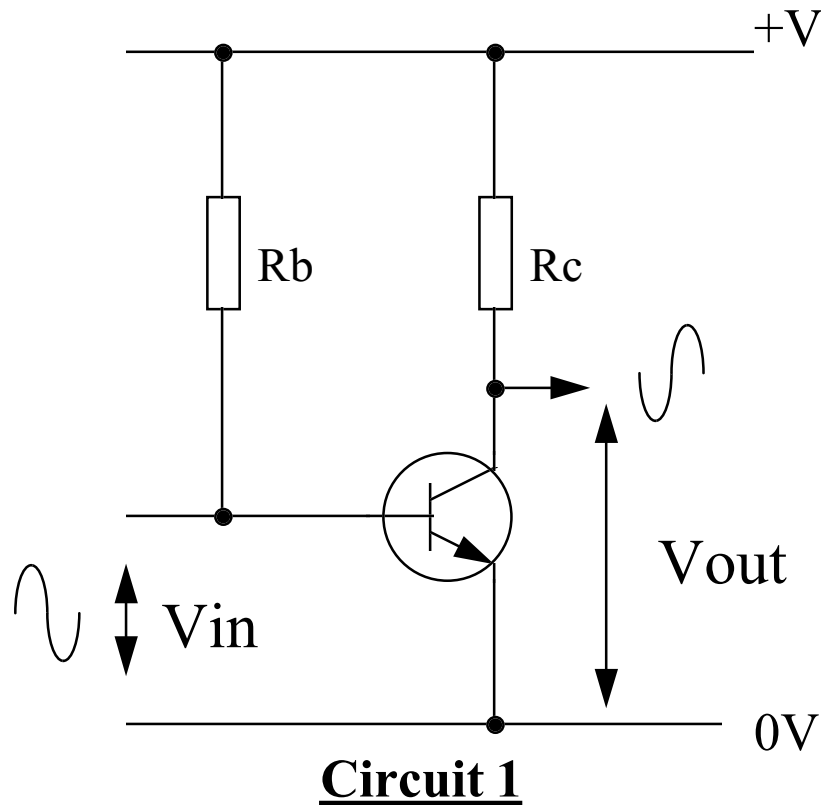- Transistor Unregulated Bias methods
- Disadvantage R_b dependent on H_{fe}



Using Worksheet
& Circuit 1

Amplifiers.

- Transistor $H_{fe} = 100$: $+V = 12V$: $I_c = 10mA$
- Calculate values of R_b and R_c .
- If $I_c = 10mA$ then V_{out} biased @ 8.5 Volts.
- Voltage across $R_c = 12V - 8.5V = 3.5V$
- Current through $R_c = I_C = 10mA$
- then $R_c = 3.5/10mA = 350\Omega$
- Gain = $I_C/I_B = 100 \therefore I_B = I_C/100 = 100\mu A$
- Voltage across $R_b = 12V - 0.7V = 11.3V$
- $R_b = V/I = 11.3/100\mu A = 113K\Omega$

Using Circuit 1
Example 2

Amplifiers.

- Assume $H_{fe} = 200$ and $+V = 15V$, $R_c = 560\Omega$ and V_{out} biased @ 8.5 Volts
- Calculate value of R_b and I_c .
- Voltage across $R_c = 15V - 8.5V = 6.5V$
- Current through $R_c = V/R = 6.5/560 = 11.6mA = I_C$
- Gain = $I_C/I_B = 200 \therefore I_B = I_C/200 = 58\mu A$
- Voltage across $R_b = 15V - 0.7V = 14.3V$
- $R_b = V/I = 14.3V / 58\mu A = 246.55K\Omega$

Transistor.

Amplifiers

Regulated.

Amplifiers.

- Transistor Regulated Bias method

Guidelines:-

Get I_c from Characteristics

Design to required Gain

$$V_{R_E} = V_{\text{supply}} / \text{Gain}$$

$$V_{BE} = 0.7V$$

$$I_b = I_c / H_{fe}$$


$$I_{\text{Bias}} = I_b * 10$$

$$V_{\text{Sat}} = 0 \text{ to } 0.2V$$

$$I_e = I_c + I_b$$

Check that the

$$\text{Gain} = R_C / R_E$$

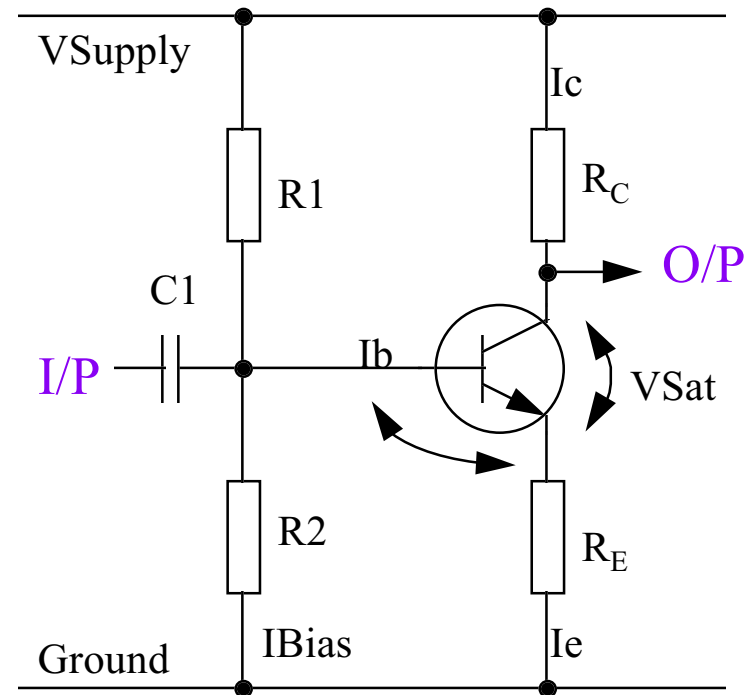

Regulated Using Worksheet Amplifiers.

- Transistor $H_{fe} = 100$: $+V = 12V$:
Target Gain = 18 : V_{out} Bias = 6 Volts
- If Bias = 6 Volts then $I_C = 17.5mA$
- Calculate Emitter Resistance Voltage
- $V_{R_E} = V_{supply} / \text{Gain} = 12/18 = 0.66 V$
- Calculate Collector Resistance
- Voltage across $R_C = 12V - (V_{Sat} + V_{R_E})$
 $= 12 - (0 + 0.66) = 11.34V$
- $R_C = V/I = 11.34/17.5*10^{-3} = 648\Omega \cong 680\Omega$
- Gain $\cong R_C/R_E = 18 \therefore R_E = 648/18 = 36\Omega$
- Preferred values $R_E = 33\Omega$ and $R_C = 680\Omega$

Regulated Using Worksheet Amplifiers.


- Calculate base **Current** and **Voltage**
- $I_b = I_c / H_{fe} = 17.5 * 10^{-3} / 100 = 175 \mu A$
- $V_b = V_e + 0.7V = 0.66 + 0.7 = 1.36V$
- Use times ten rule for bias chain **Current**.
- $I_{Bias} = I_b * 10 = 1.75mA$
- Calculate Resistance of Bias **Resistors**
- $R_2 = V_b / I_{Bias} = 1.36 / 1.75 * 10^{-3} = 777 \Omega$
- $R_1 = (V_{supply} - V_b) / I_{Bias}$
 $(12 - 1.36) / (1.75 * 10^{-3}) =$
 $10.64 / (1.75 * 10^{-3}) = 6080 \Omega$
- Preferred values $R_1 = 5K6 \Omega$ and $R_2 = 680 \Omega$

Transistor.


Amplifiers

Configurations.


Amplifiers.

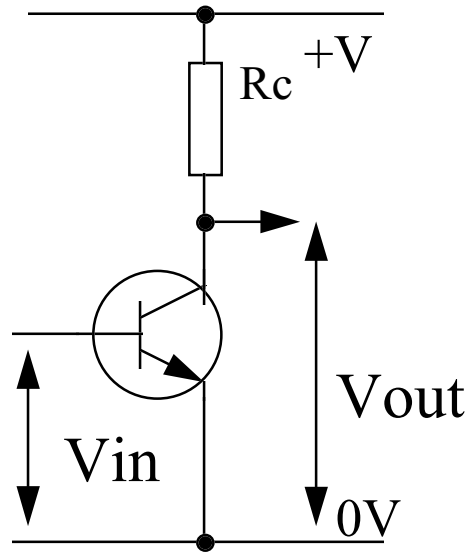

Common Emitter

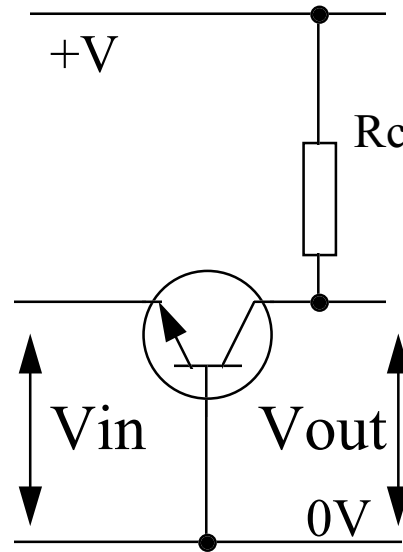

Common Base

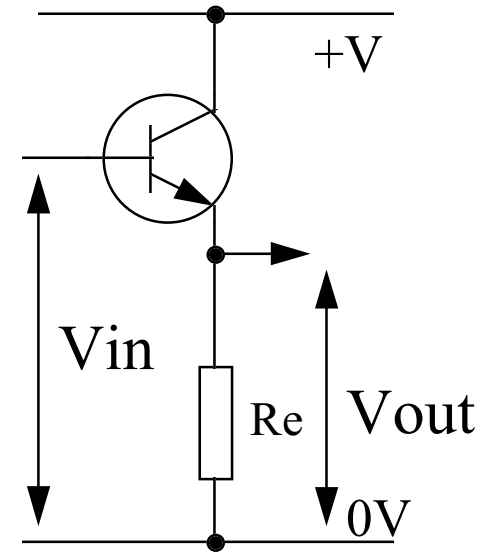

Common Collector

Mode	Gain		Impedance	
	Voltage	Current	Input	Output
Common Emitter	High	High	Medium	Medium
Common Base	High	Less than 1	Low	High
Common Collector	Less than 1	High	High	Low

Transistor.

Amplifiers

Operation Classes.


Classes

Amplifiers.


- Class “A”
- Main Characteristics.
- The amplifier biased so that all 360° of input signal is amplified.
- Advantages.
- Little or low distortion in output signal.
- Linear output.
- Disadvantages.
- Efficiency max 25%.

Amplifiers.

- Class “A” Amplifiers.

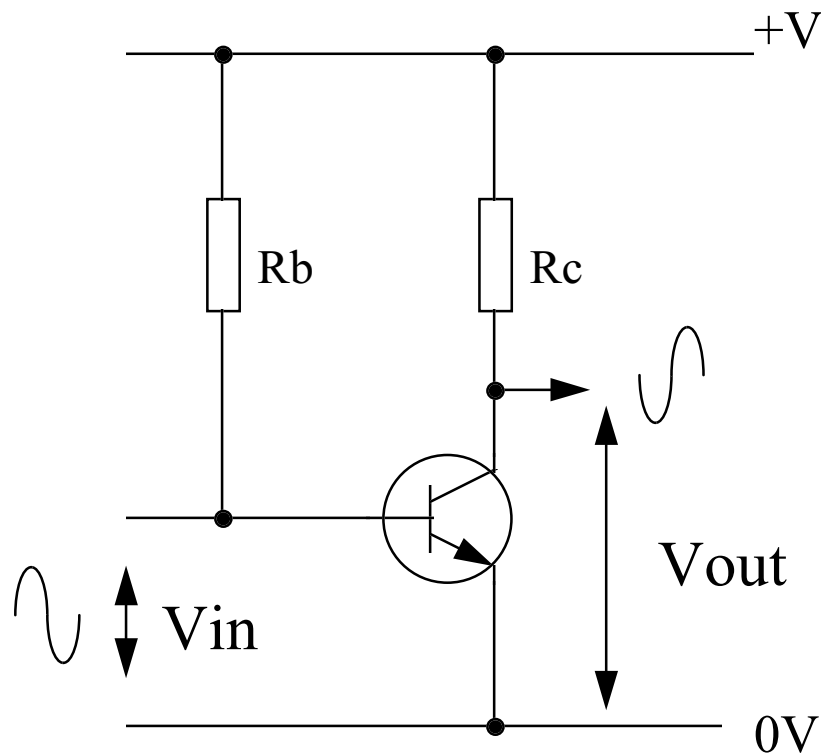

Class “A” Amplifier
Un-Regulated

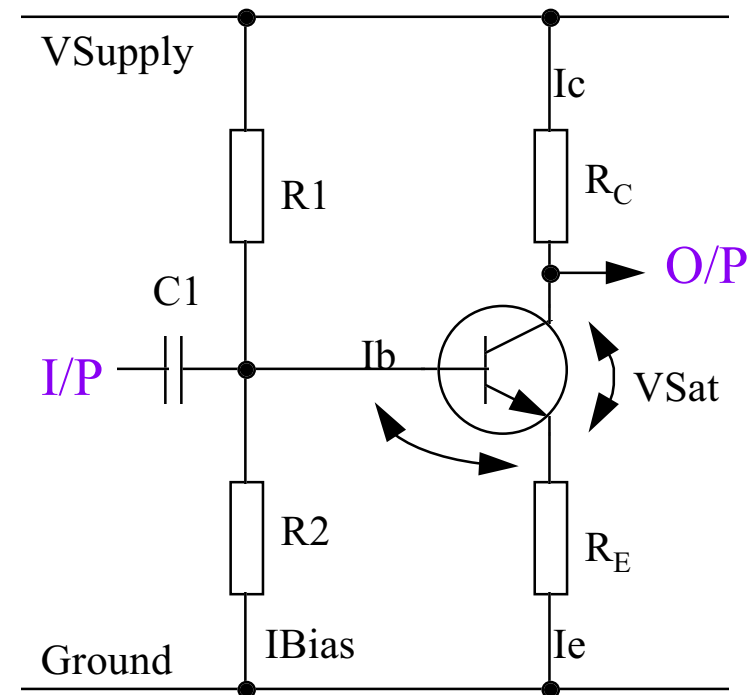

Class “A” Amplifier
Regulated

Classes

Amplifiers.

- Class “B”
- Main Characteristics.
- The amplifier biased so that only 180° of input signal is amplified.
- Advantages.
- Efficiency max 78.5%
- Disadvantages.
- Subject to Cross over distortion in output signal.


Classes

Amplifiers.


- Class “AB”
- Main Characteristics.
- The amplifier biased so that over 180° of input signal is amplified.
- Advantages.
- Efficiency much better than Class “A”
- Subject to less Cross over distortion in output signal than Class “B”.
- Disadvantages.
- Less efficient than Class “B”

Amplifiers.

- Push Pull Amplifiers (Class B or AB).

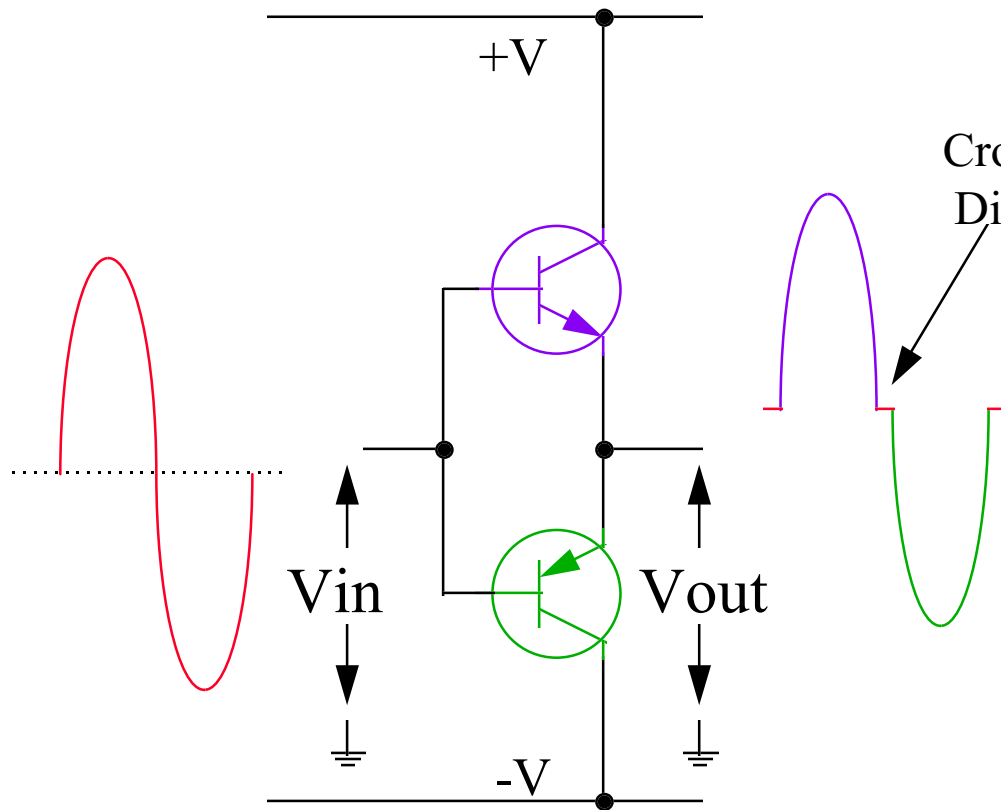

Class "B" Amplifier

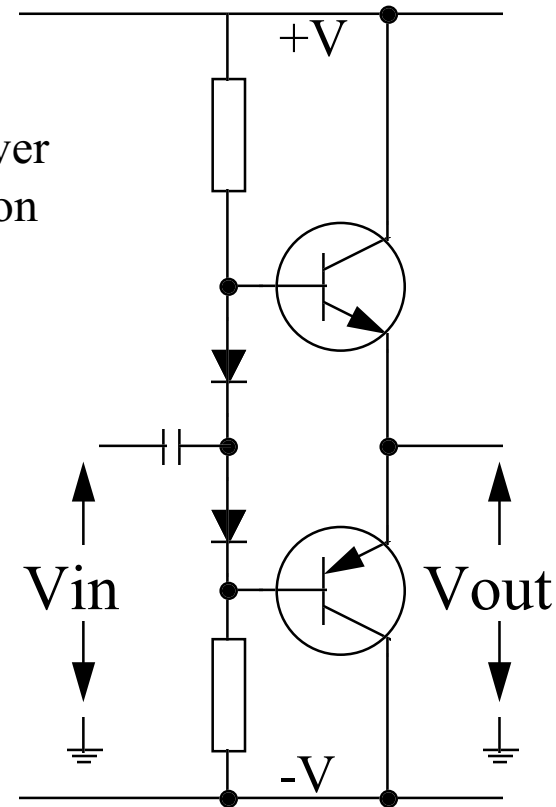

Class "AB" Amplifier
Not Thermally Stable


Classes

Amplifiers.

- Class “C”
- Main Characteristics.
- The amplifier biased so that only part of input signal is amplified. Restoration of signal by Tuned Circuits
- Advantages.
- Up to 100% efficient.
- Disadvantages.
- Subject to significant distortion in output signal if input signal not symmetrical.

Amplifiers.


- Class “C” Amplifiers.

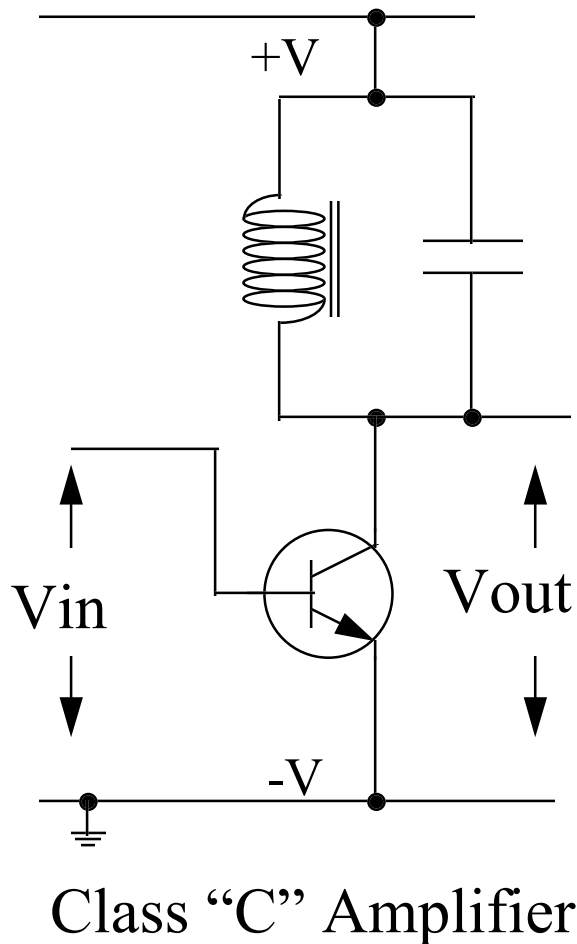

This Part of the signal
is restored by the tuned
circuit



Input
Signal

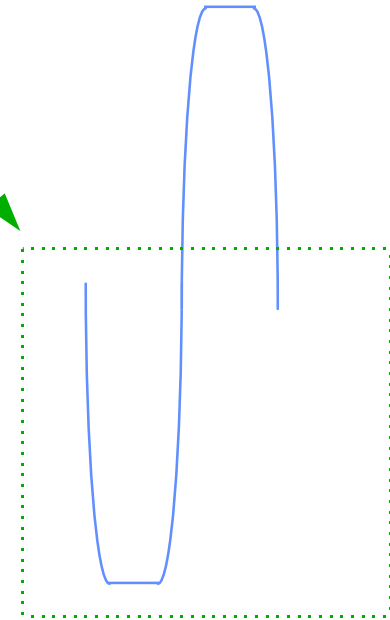

Output
Signal

End Slide

Revision Page

Title Operational Amplifiers.

Author R. J. Spriggs

Last Update 14/May/2007

Version 1.03

Edit 0011

